

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



A 20 to 25 Watt, Low Cost, Off-line Power Supply

ON Semiconductor

Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
NCP1251B NCP431 NDD04N60	White Goods, Small Instruments, E-Meters, Industrial Equipment	90 – 267 Vac	20 to 25 Watts	DCM Flyback	3 kV

Other Specification

	Output 1	Output 2	Output 3	Output 4
Output Voltage	5Vdc or 12 Vdc	N/A	N/A	N/A
Ripple	< 2%	N/A	N/A	N/A
Nominal Current	1.8 or 4 Amps	N/A	N/A	N/A
Max Current	1.8 or 4 Amps	N/A	N/A	N/A
Min Current	zero	N/A	N/A	N/A

PFC (Yes/No)	No
Minimum Efficiency	78% for 5Vout; 81% for 12Vout
Inrush Limiting / Fuse	Yes
Operating Temp. Range	0 to 50C
Cooling Method / Supply Orientation	Convection NA
Signal Level Control	No

Others	Input EMI filter
---------------	------------------

Circuit Description

This Design Note describes a very simple, low cost, yet high performance off-line flyback power supply using ON Semiconductor's NCP1251B controller (TSOP6 package), NDD04N60 D-Pak Mosfet, and the NCP431 programmable zener (SOT23 package).

The flyback design operates in discontinuous conduction mode and uses the conventional optocoupler (U2) feedback scheme for the voltage loop and an auxiliary Vcc winding on the flyback transformer to power the NCP1251. The Design Note provides the complete circuit and transformer design details for 5 volt, 4 amp, and 12 volt, 1.8 amp output models. Other output voltages from 3.3 up to 28 Vdc are easy to implement by modifying the values (or ratings) of R11, R12, D9, C9 and T1's secondary turns.

Over-current limiting is provided by sensing the peak current in the MOSFET Q1 via R8. Once the 800 mV threshold level on U1's pin 4 is exceeded the circuit will go a "hiccup" mode until the over-current condition is removed. An optional OVP circuit is implemented via Z1.


Depending on the application, it may be necessary to add a small pi-network ripple filter to the output as shown in the lower section of the schematic below.

Key Features

- Input EMI filter for conducted EMI compliance
- Schottky output rectifier for high efficiency
- Very low standby (no load) power
- Current mode control with adjustable output current
- Small pc board footprint
- Low cost components

DN05012/D

Schematic

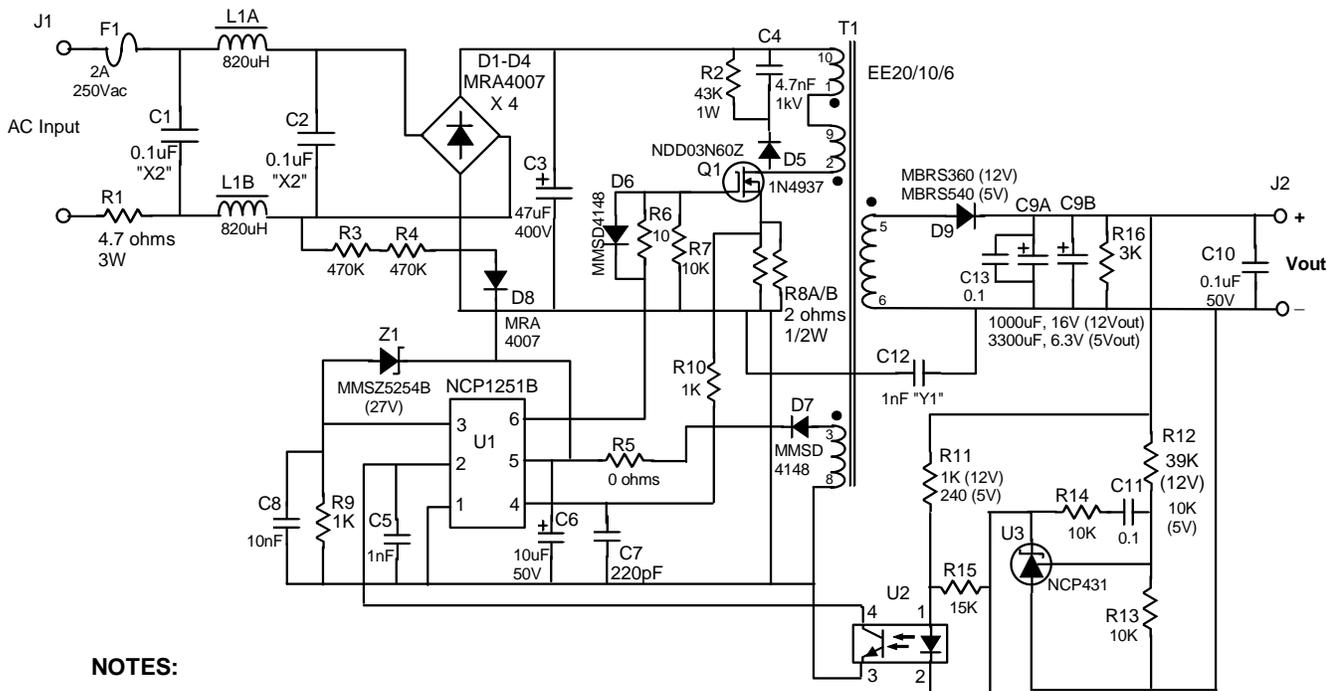


NOTES:

1. Crossed lines on schematic are NOT connected.
2. U2 is NEC PS2561L-1 or equivalent optocoupler (CTR > 50%).
3. R1 is for inrush limiting - use carbon comp or wire wound.
4. L1A/L1B are Wurth 7447728215 components (820 uH, 500mA).
5. Output caps (C9A/B) are radial lead, low impedance types (UCC LXV series or similar).
6. Z1 sets OVP trip level.
7. R5 is for Vcc trimming (< 28Vmax), typically zero ohms.
8. R8A/B sets max output current.
9. U1 is 100 kHz version
10. See drawing for T1 details.

20 Watt NCP1251 Power Supply with Universal AC Input (Rev 5A)

Optional Ripple Filter

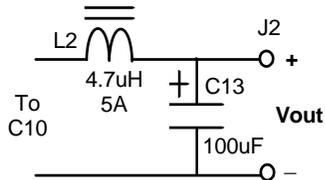

© 2011 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Frank Cathell, e-mail: f.cathell@onsemi.com

DN05012/D
MAGNETICS DESIGN DATA SHEET

Project / Customer: ON Semiconductor - 20 watt, 5 Vout NCP1251 Flyback

Part Description: 20 watt, 100 kHz flyback transformer, 5Vout (Wurth # 750312279)

Schematic ID: T1

Core Type: EE20/10/6 ferrite core; 3C90 material or similar

Core Gap: Gap for 190 +/- 200uH across Primary A (pins 1 - 10)


Inductance: 750 uH total (+/- 5%) measured from pin 1 to pin 9 with pins 2 and 10 connected

Bobbin Type: 10 pin horizontal mount for EE20/10/6

Windings (in order):

Winding # / type	Turns / Material / Gauge / Insulation Data
Primary A (1 - 10)	30T of #28HN over 1 layer (30 TPL). Insulate for 1 kV to next winding. Self leads to pins.
Vcc (3 - 8)	8 turns of #28 HN over 1 layer, spiral wound over primary A. Self leads to pins. Insulate to 1 kV to next winding with tape.
5V Secondary (5 - 6)	3 turns trifilar of #24 triple insulated wire over one. layer (three strands). Self leads to single pins as shown in drawing below.
Primary B (2 - 9)	Same as Primary A. Insulate with tape and self-leads to pins.

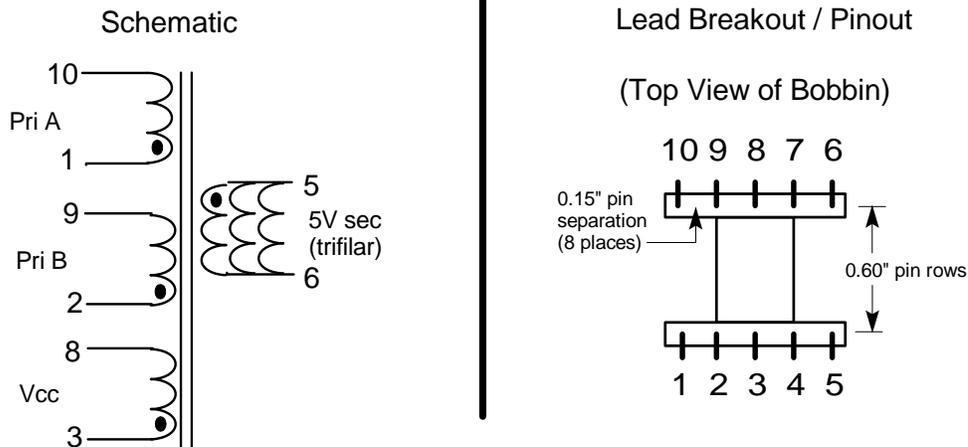Hipot: 3 kV from primaries & Vcc to secondary for 1 minute.



DN05012/D
MAGNETICS DESIGN DATA SHEET

Project / Customer: ON Semiconductor - 24 watt, 12 vout NCP1251 Flyback

Part Description: 24 watt flyback transformer, 12vout, 100 kHz (Wurth part # 750312495)

Schematic ID: T1

Core Type: EE20/10/6 ferrite core; 3C90 material or similar

Core Gap: Gap for 190 +/- 200uH across Primary A (pins 1 - 10)



Inductance: 750 uH total (+/- 5%) measured from pin 1 to pin 9 with pins 2 and 10 connected

Bobbin Type: 10 pin horizontal mount for EE20/10/6

Windings (in order):


Winding # / type	Turns / Material / Gauge / Insulation Data
Primary A (1 - 10)	30T of #28HN over 1 layer (25 TPL). Insulate for 1 kV to next winding. Self leads to pins.
Vcc (3 - 8)	7 turns of #28 HN over 1 layer, spiral wound over primary A. Self leads to pins. Insulate to 1 kV to next winding with tape.
12V Secondary (5 - 6)	6 turns bifilar of #24 triple insulated wire over one layer (two strands). Self leads to pins. (Note: #26 is also acceptable here if the fit is too tight for one layer)
Primary B (2 - 9)	Same as Primary A. Insulate with tape and self-leads to pins.

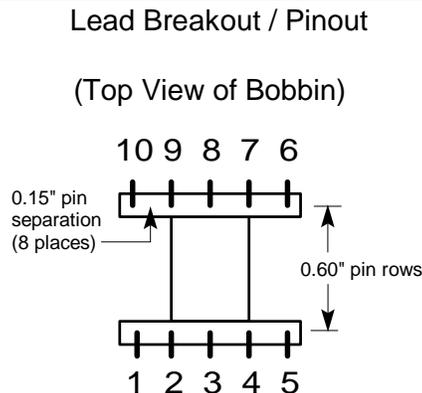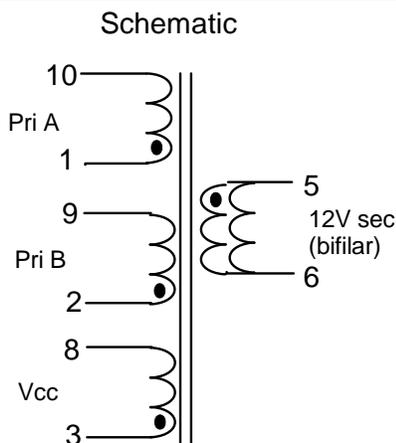Hipot: 3 kV from primaries & Vcc to secondary for 1 minute.




Efficiency Plots

12 Volt Output

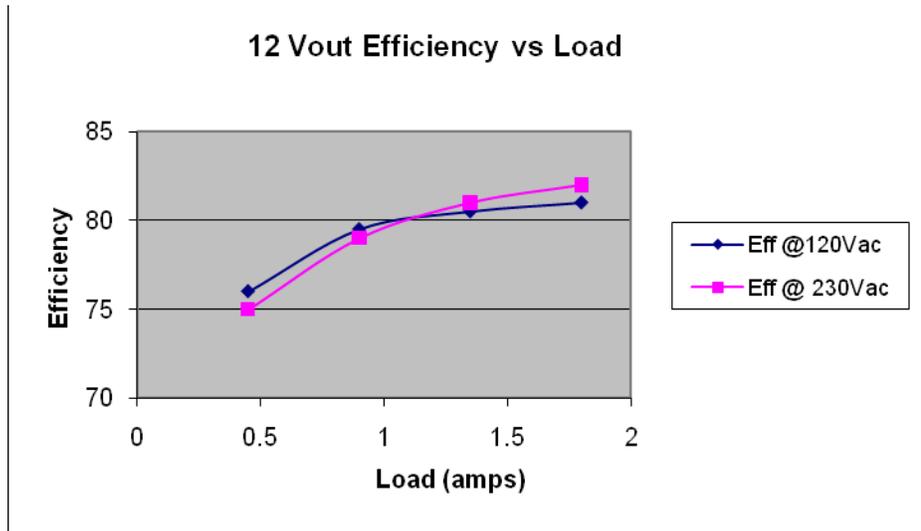


5 Volt Output

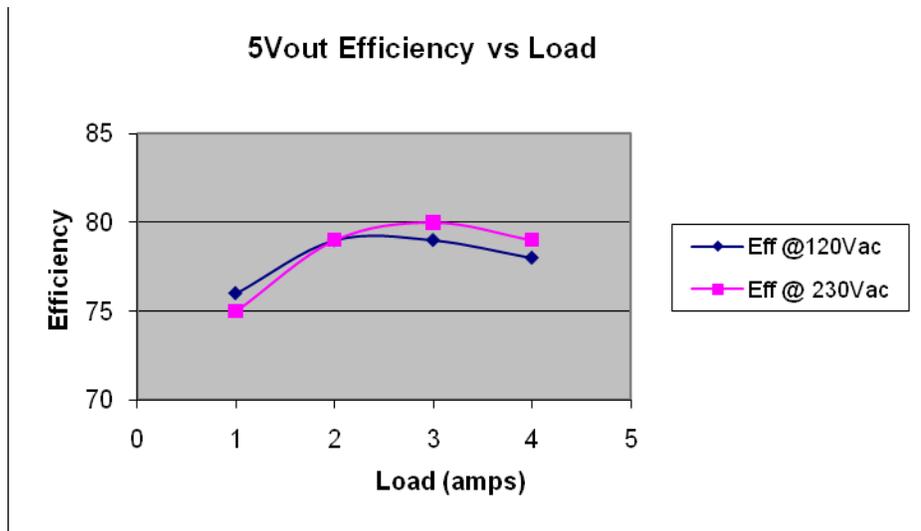

DN05012/D

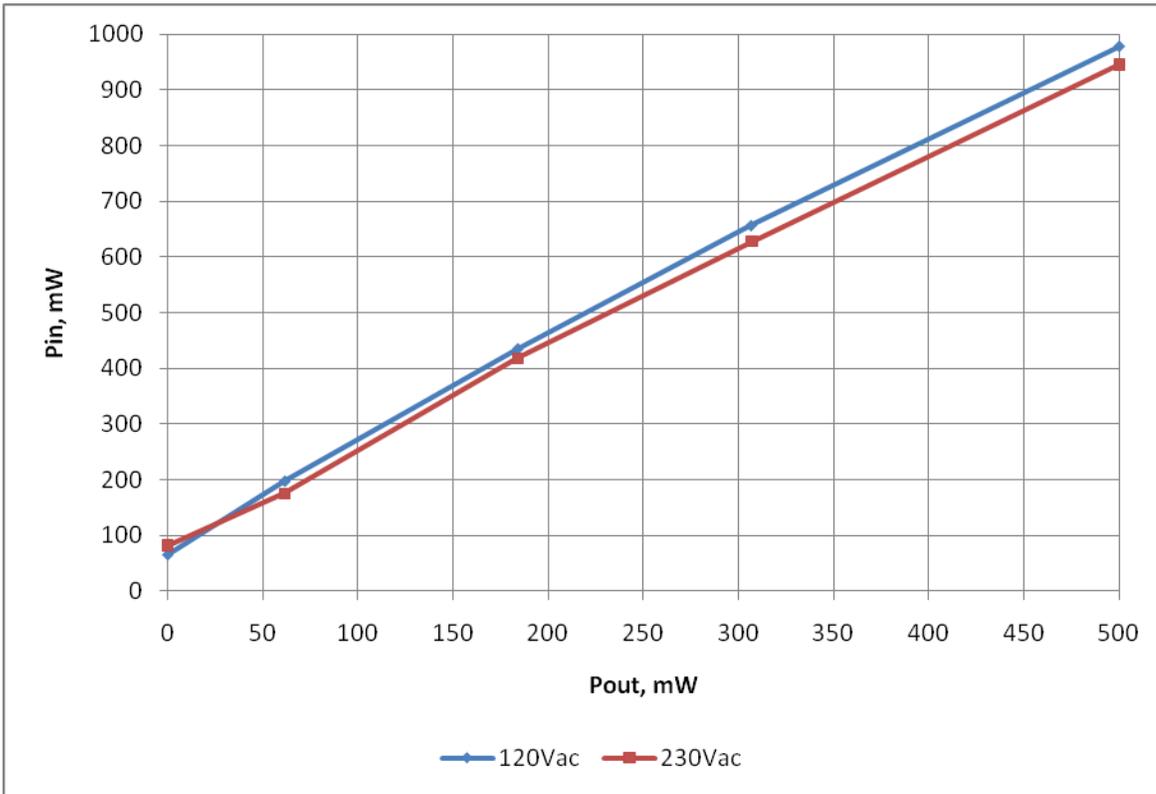Light Load (< 500mW out) and Standby (no load) Power Plots



DN05012/D

Bill of Materials for 12Vout, 20W NCP1251 Flyback (Rev5)

ON Semiconductor



6/2/2011

Designator	Qty	Description	Value	Tolerance	Footprint	Manufacturer	Manufacturer Part Number	Substitution Allowed	Lead Free	Comments
D9 (12Vout)	1	Schottky diode	3A, 60V		SMC	ON Semi	MBRS360T3G	No	Y	12V version
D9 (5Vout)	1	Schottky diode	5A, 40V		SMC	ON Semi	MBRS540T3	No	Y	5V version
Q1	1	Mosfet - NDD04N60Z	4A, 600V		DPak	ON Semi	NDD04N60Z	No	Y	
D1, 2, 3, 4, 8	5	Diode - 60 Hz,	1A, 800V		SMA	ON Semi	MRA4007	No	Y	
D5	1	Diode - fast recov	1A, 600V		axial lead	ON Semi	1N4937	No	Y	
D6, D7	2	Signal diode	100mA, 100V		SOD-123	ON Semi	MMSD4148A	No	Y	
Z1	1	Zener diode	27V (OVP)		SOD-123	ON Semi	MMSZ5254B	No	Y	
U3	1	Programmable zener	2.5V		SOIC8 / SOT23	ON Semi	NCP431A	No	Y	
U2	1	Optocoupler	CTR >= 0.5		4-pin	Vishay or NEC	SFH6156A-4 or PS2561L-1	Yes	Y	
U1	1	Controller - NCP1251B	100 kHz		TSOP6	ON Semi	NCP1251BSN100	No	Y	
C1, C2	2	"X" cap, box type	100nF, X2	20%	LS = 15 mm	Rifa, Wima	Digi-Key P/N = 399-5426-ND	Yes	Y	
C12	1	"Y1" cap, disc type	1nF, Y1	20%	LS = 7.5 mm	Rifa, Wima	Mouser P/N = 75-WKP102MCPEJ0KR	Yes	Y	
C4	1	Ceramic cap, disc	4.7nF, 1kV	5%	LS = 7.5 mm	Rifa, Wima	Digi-Key P/N = 490-4266-ND	Yes	Y	
C5	1	Ceramic cap, monolythic	1 nF, 50V	10%	1206	AVX, Murata	Digi-Key P/N = 311-1170-1-ND	Yes	Y	
C10, 11, 13	3	Ceramic cap, monolythic	100nF, 50V	10%	1206	AVX, Murata	Digi-Key P/N = 311-1179-1-ND	Yes	Y	
C7	1	Ceramic cap, monolythic	220pF, 50V	5%	1206	AVX, Murata	Digi-Key P/N = 478-1484-1-ND	Yes	Y	
C8	1	Ceramic cap, monolythic	10nF, 50V	5%	1206	AVX, Murata	Digi-Key P/N = 445-7688-1-ND	Yes	Y	
C3	1	Electrolytic cap	47uF, 400V	10%	LS=7.5mm, D=16mm	UCC, Panasonic	Mouser P/N = 647-UCY2G470MHD	Yes	Y	
C6	1	Electrolytic cap	10uF, 25Vdc	10%	LS=2.5mm, D=6.3mm	UCC, Panasonic	Digi-Key P/N = 565-1055-ND	Yes	Y	
C9A, C9B	2	Electrolytic cap	1000uF, 16V	10%	LS=5mm, D=12.5mm	UCC, Panasonic	Mouser P/N = 661-EKY160ELL102MK1	Yes	Y	12V version
(5Vout)	2	Electrolytic cap	3300uF, 6.3V	10%	LS=5mm, D=12.5mm	UCC, Panasonic	Newark P/N = 23K4009	Yes	Y	5V version
R1	1	Resistor, 3W, Wire wound	4.7 ohm, 3W	5%	LS=7.5mm, D=7mm	Ohmite, Dale	Digi-Key P/N = 4.7AECT-ND	Yes	Y	
R2	1	Resistor, 1W, metal film	43K, 1W	5%	Axial lead; LS=25mm	Ohmite, Dale	Digi-Key P/N = PPC43KW-1CT-ND	Yes	Y	
R8A/B	2	Resistor, 1/2W metal film	2 ohms, 1/2W	1%	Axial lead; LS=12.5mm	Ohmite, Dale	Mouser P/N = 660-MF1/2DCT52R2R00F	Yes	Y	
R6	1	Resistor, 1/4W SMD	10 ohms	1%	SMD 1206	AVX, Vishay, Dale	Digi-Key P/N = 541-10.0FCT-ND	Yes	Y	
R3, R4	2	Resistor, 1/4W SMD	470K	1%	SMD 1206	AVX, Vishay, Dale	Digi-Key P/N = 541-470KFCT-ND	Yes	Y	
R7, 13, 14	3	Resistor, 1/4W SMD	10K	1%	SMD 1206	AVX, Vishay, Dale	Digi-Key P/N = 541-10.0KFCT-ND	Yes	Y	
R11 (12Vout)	1	Resistor, 1/4W SMD	1K	1%	SMD 1206	AVX, Vishay, Dale	Digi-Key P/N = 541-1.00KFCT-ND	Yes	Y	12V version
R11 (5Vout)	1	Resistor, 1/4W SMD	240 ohms	1%	SMD 1206	AVX, Vishay, Dale	Digi-Key P/N = 541-240FCT-ND	Yes	Y	5V version
R5	1	Resistor, 1/4W SMD	Zero ohm	1%	SMD 1206	AVX, Vishay, Dale	Digi-Key P/N = 541-0.0ECT-ND	Yes	Y	
R9, 10, 15	3	Resistor, 1/4W SMD	1K	1%	SMD 1206	AVX, Vishay, Dale	Digi-Key P/N = 541-1.00KFCT-ND	Yes	Y	
R16	1	Resistor, 1/4W SMD	3K	1%	SMD 1206	AVX, Vishay, Dale	Digi-Key P/N = 541-3.00KFCT-ND	Yes	Y	
R12 (12Vout)	1	Resistor, 1/4W SMD	39K	1%	SMD 1206	AVX, Vishay, Dale	Digi-Key P/N = 541-39.0KFCT-ND	Yes	Y	12V version
R12 (5Vout)	1	Resistor, 1/4W SMD	10K	1%	SMD 1206	AVX, Vishay, Dale	Digi-Key P/N = 541-10.0KFCT-ND	Yes	Y	5V version
F1	1	Fuse, TR-5 style	2A		TR-5, LS=5mm	Minifuse	Newark P/N = 67K2094	Yes	Y	
L1A/B	1	Inductor (EMI choke)	820 uH, 500 mA		See Wurth Drawing	Wurth Magnetics	7447728215	Yes	Y	
T1 (12Vout)	1	Transformer	E20/10/6 core		See Mag Drawing	Wurth Magnetics	750312495	Yes	Y	12V version
T1 (5Vout)	1	Transformer	E20/10/6 core		See Mag Drawing	Wurth Magnetics	750312279	Yes	Y	5V version
J1, J2	2	Screw Terminal			LS = 0.2"	DigiKey	# 281-1435-ND	Yes	Y	
J1, J2	2	Screw Terminal			LS = 0.2"	DigiKey	# 281-1435-ND	Yes	Y	

Blue indicates part change with Vout change

© 2012 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Frank Cathell, e-mail: Frank.Cathell@onsemi.com