DN05016/D



# Design Note – DN05016/D

# 100V, 450mA Off-Line LED Driver with High PF

**ON Semiconductor** 

Device	Application	Input Voltage	e Output Power	Topology	I/O Isolation
NCL30001 NCS1002	High PF CVCC LED Driver with Dimming	85 – 266 Vac	35 to 60 Watts	Single Stage PFC/Flyback	Yes – 3 kV
			Output	1	
	Output	Output Voltage		100 Vdc max	
	Rip	Ripple		100 mA max	
	Nominal	Nominal Current		450 mA (adjustable)	
	Max C	Max Current		600 mA	
	Min Cu	Min Current		350 mA	
					7
	PFC (Yes/	PFC (Yes/No)		Yes	
	Typical Effic	Typical Efficiency		86%	
	Inrush Limitin	Inrush Limiting / Fuse		Yes	
	Operating Tem	Operating Temp. Range		0 to +40 °C	
	Cooling Me	Cooling Method /		Convection	
	Supply Orier	Supply Orientation		NA	
	Signal Level	Signal Level Control		Yes – Dimming functions	
Others PWM dimming to 3% with external digital input signal					

# **Circuit Description**

This Design Note (DN) is an extension to ON Semiconductor's Application Note AND8470/D and features a 100 volt max, 0.45 amp version of the off-line, NCL30001 based constant voltage, constant current (CVCC) LED driver with inherent PFC described in that app note. The original app note features a 50 volt max, constant current, 1 to 2 amp (current settable) LED driver with multiple dimming capabilities and active power factor correction in a single continuous conduction mode (CCM) flyback converter stage. This DN presents a similar version that is suitable for driving series LED strings up to 100 volts at a max current of up to about 600 millamps. This design is suitable for LED strip lighting and fluorescent lamp replacements. The maximum voltage and output current can be adjusted via resistors R34 and R32 respectively. The detailed circuit operational description can be found in the original mentioned app note (AND8470/D) and is essentially identical circuit-wise with the exception of the component changes that are indicated in the BOM. The flyback transformer design for this DN was merely ratioed from the secondary winding on the original design to meet the new maximum voltage and current requirements. The primary winding, required inductance, and overall construction are essentially the same.

# Key Features

- Single stage, isolated PFC converter for strip lighting and fluorescent tube replacements.
- Constant voltage, constant current output characteristic for LED drive
- Dimming features including pulse width dimming to 3%
- Over current, over voltage and over temperature capabilities
- Typical efficiencies above 86%

### DN05016/D Primary Side Schematic



#### © 2011 ON Semiconductor.

**Disclaimer**: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Frank Cathell, e-mail: f.cathell@onsemi.com

www.onsemi.com

#### DN05016/D





#### DN05016/D

### **MAGNETICS DESIGN DATA SHEET**

Project: NCL30001, 40 W, 100 Vout, isolated, single stage CVCC PFC LED driver
Part Description: CCM Flyback transformer, 50-70 kHz, 100 Vout, 450 mA
Schematic ID: T1
Core Type: PQ3230, 3C94 (Ferroxcube) or P material (Mag Inc.)
Core Gap: Gap core for 900 to 1,100 uH across pins 1 to 2.
Inductance: 1000 uH nominal measured across primary (pins 1 to 2)
Bobbin Type: 12 pin pc mount (Mag Inc PC-B3230-12 or equivalent)

Windings (in order): Winding # / type	Turns / Material / Gauge / Insulation Data
Primary A: (1 - 3)	28 turns of #24HN over one layer (no margins). Self-leads to pins. Insulate for 3 kV to next winding.
100V Secondary (8 - 11)	50 turns of #30HN close wound over one layer and centered with 1.5 mm end margins. Insulate with tape for 3 kV to next winding.
Primary B: (3 - 2)	Same as primary A. Insulate for 1.5 kV to Vcc/Aux.
Vcc/Aux (5 - 6)	13 turns of #24HN spiral wound and centered with 8 mm end margins. Insulate with tape and terminate self-leads to pins.

Safety margins not necessary as long as specified Hipot below can be met.

Hipot: 3 kV from primary/Vcc to 100V secondary winding.

