



ON Semiconductor®

Simulating Power Supplies with SPICE

Agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion

Agenda

- Why simulating power supplies?
 - Average modeling techniques
 - The PWM switch concept, CCM
 - The PWM switch concept, DCM
 - The voltage-mode model at work
 - Current-mode modeling
 - The current-mode model at work
 - Power factor correction
 - Switching models
 - EMI filtering
 - Conclusion

Why Simulate Switch Mode Power Supplies?


- Simulation helps feeling how the product behaves before breadboard
- Experiment What If? at any level. Power libraries do not blow!
- Easily shows impact of parameter variations: ESR, Load etc.
- Draw Bode plots without using costly equipments
- Avoid trials and errors: compensate the loop on the PC first!
- Use SPICE to assess current amplitudes, voltage stresses etc.
- Go to the lab. and check if the assumptions were valid.

SPICE does **NOT** replace the breadboard!




Why Average Simulations?

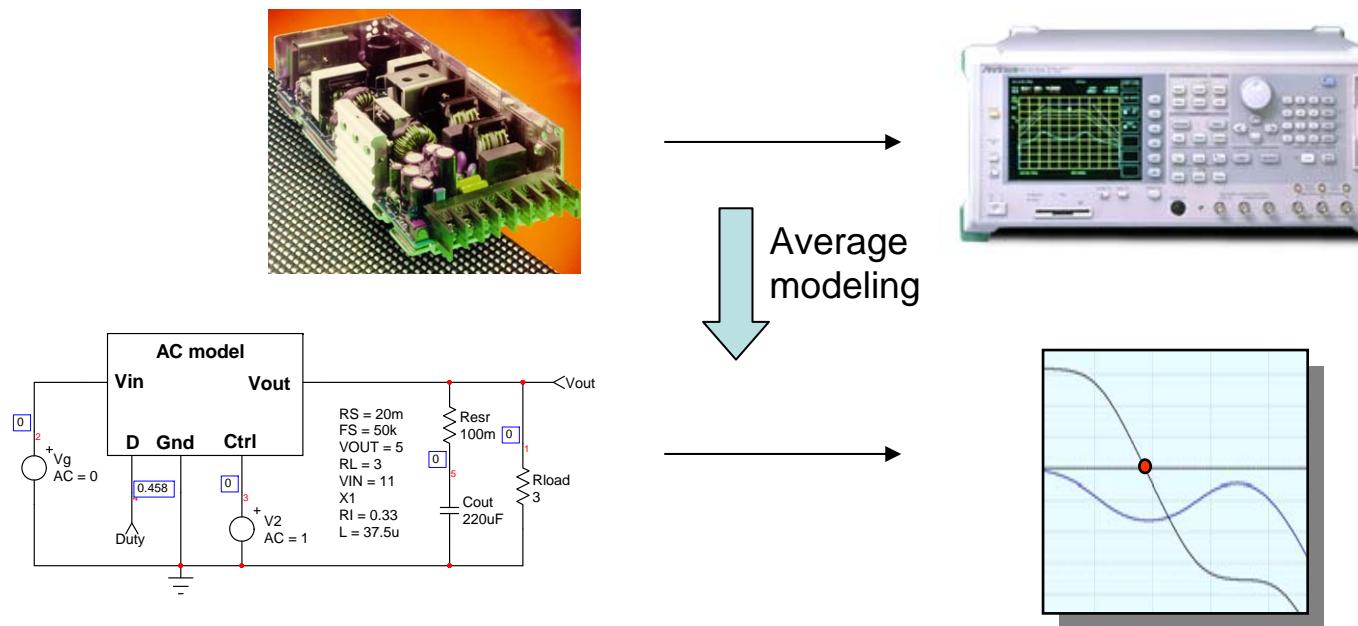- An average model is made of equations that are continuous in time
- The switching component has disappeared, leading to:
 - ❖ a simpler ac analysis of the power supply
 - ❖ the study of the stability margins in various conditions
 - ❖ the assessment of the ESRs contributions in the loop stability
 - ❖ a flashing simulation time!



Why **Switching** Simulations?

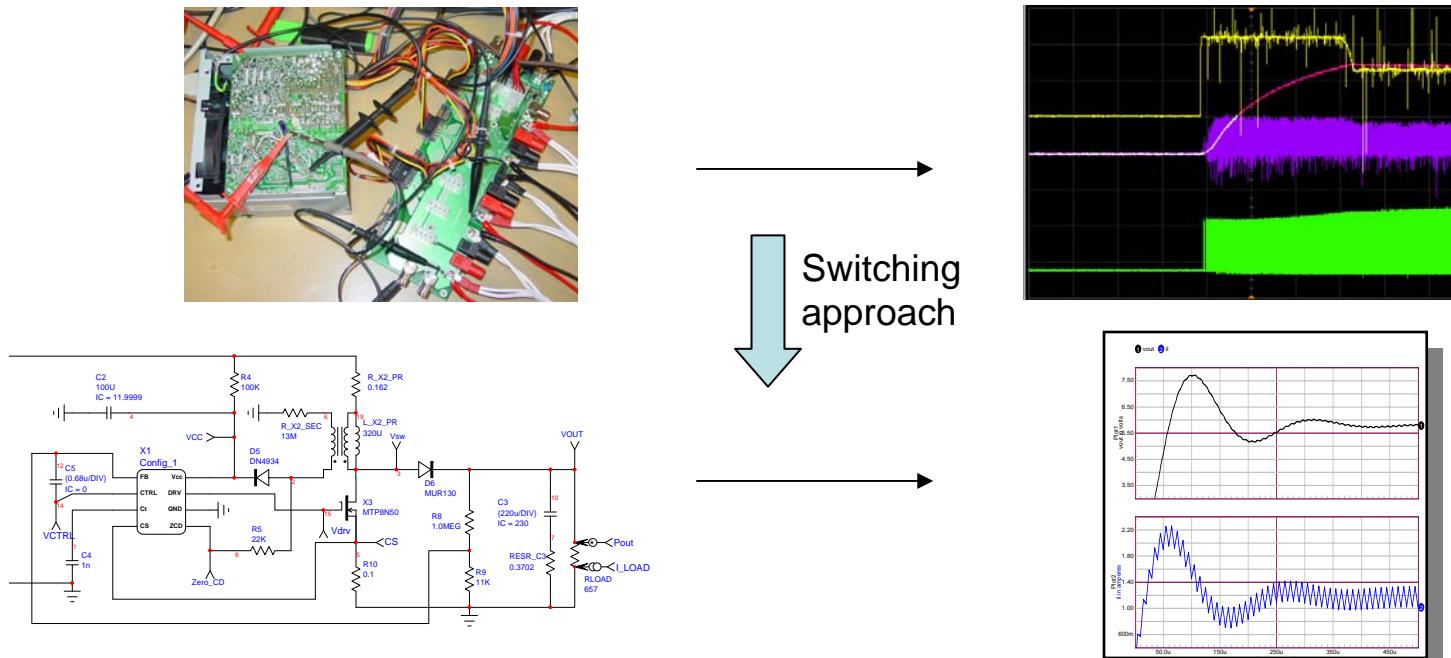- An switching model is like breadboarding on the PC
- The switching component is back in place, leading to:
 - ❖ the analysis of current and voltage stresses
 - ❖ the study of leakage and stray elements impacts
 - ❖ the analysis of the input current signature – EMI
 - ❖ a longer simulation time...




Agenda

- ❑ Why simulating power supplies?
- ❑ **Average modeling techniques**
 - ❑ The PWM switch concept, CCM
 - ❑ The PWM switch concept, DCM
 - ❑ The voltage-mode model at work
 - ❑ Current-mode modeling
 - ❑ The current-mode model at work
 - ❑ Power factor correction
 - ❑ Switching models
 - ❑ EMI filtering
 - ❑ Conclusion




Average Modeling, the SSA

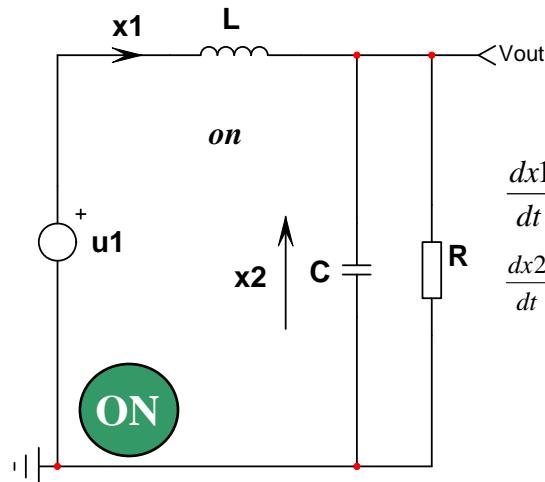- State-Space Averaging (SSA)
- Introduced by Slobodan Ćuk in the 80'
- Long and painful process
- **Fails** to predict sub-harmonic oscillations


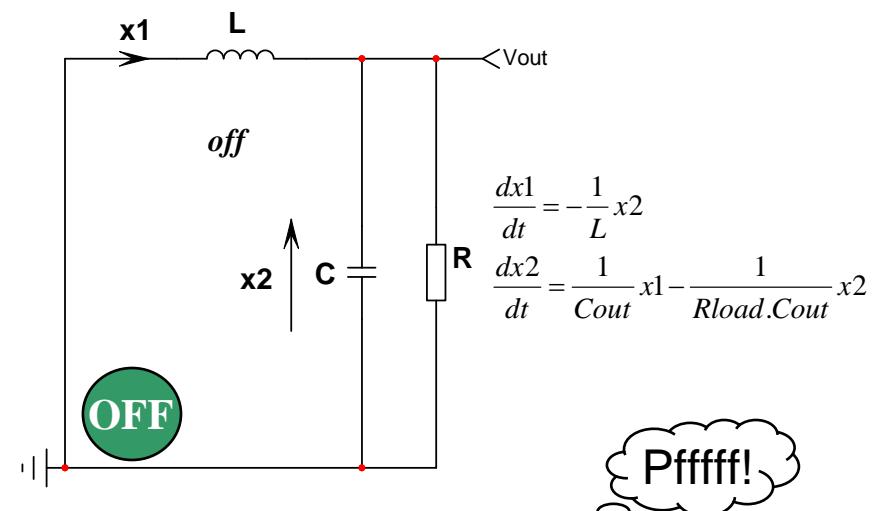
$$\begin{aligned}\frac{dx_1}{dt} &= -\frac{1}{L}x_2 + \frac{1}{L}u \\ \frac{dx_2}{dt} &= \frac{1}{C_{out}}x_1 - \frac{1}{R_{load}.C_{out}}x_2\end{aligned}$$





Pfffff!

→ Apply smoothing process → Linearize 😞


Average Modeling, the PWM Switch

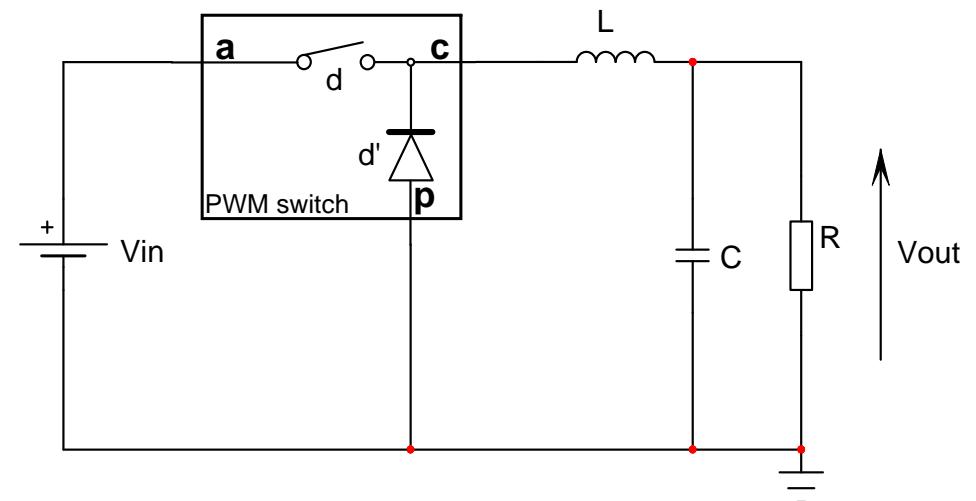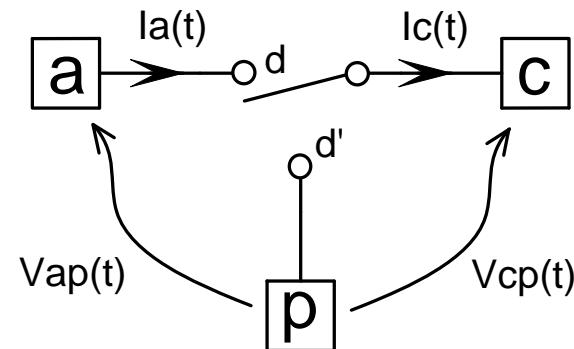- The PWM Switch
- Introduced by Vatché Vorperian in the mid-80'
- Easy to derive and fully invariant
- **No** auto-toggling mode models
- **Can** predict sub-harmonic oscillations in CCM
- DCM model in current-mode was never published!



The PWM Switch Concept

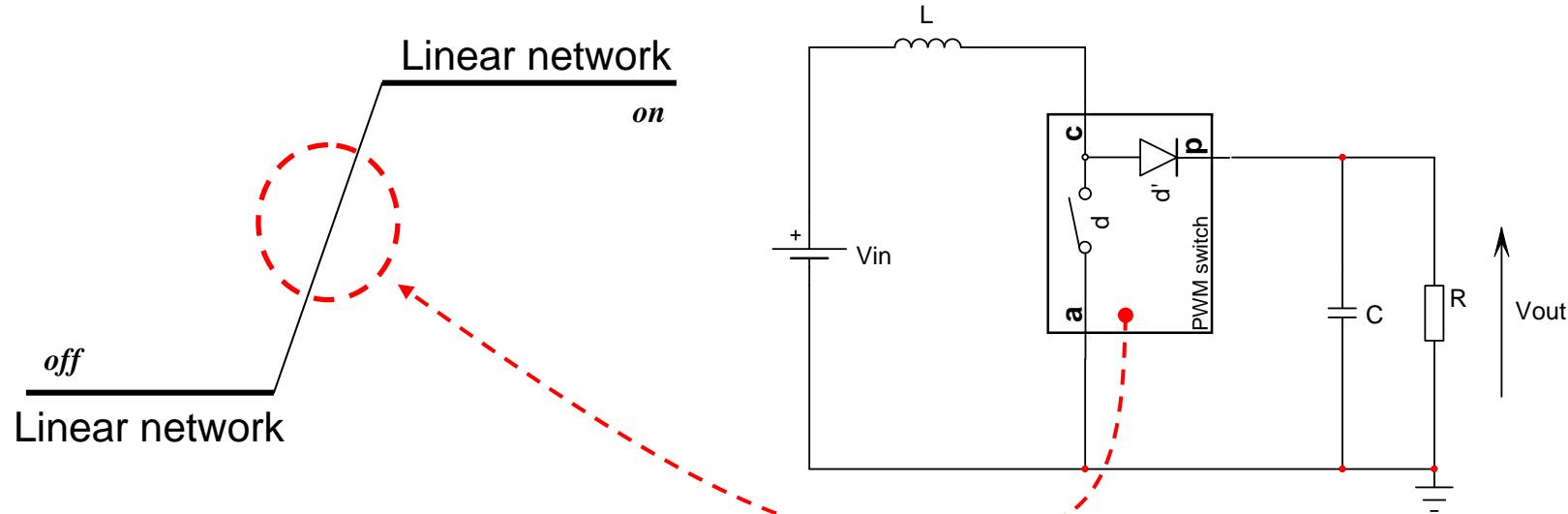- Identify the guilty network: the transistor and the diode
 - ❖ Average their voltage and current waveforms: large-signal model
 - ❖ Linearize the equations around a dc point: small-signal model




diode + transistor = guilty for non-linearity!

Agenda

- Why simulating power supplies?
- Average modeling techniques
- **The PWM switch concept, CCM**
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion

The PWM Switch Concept

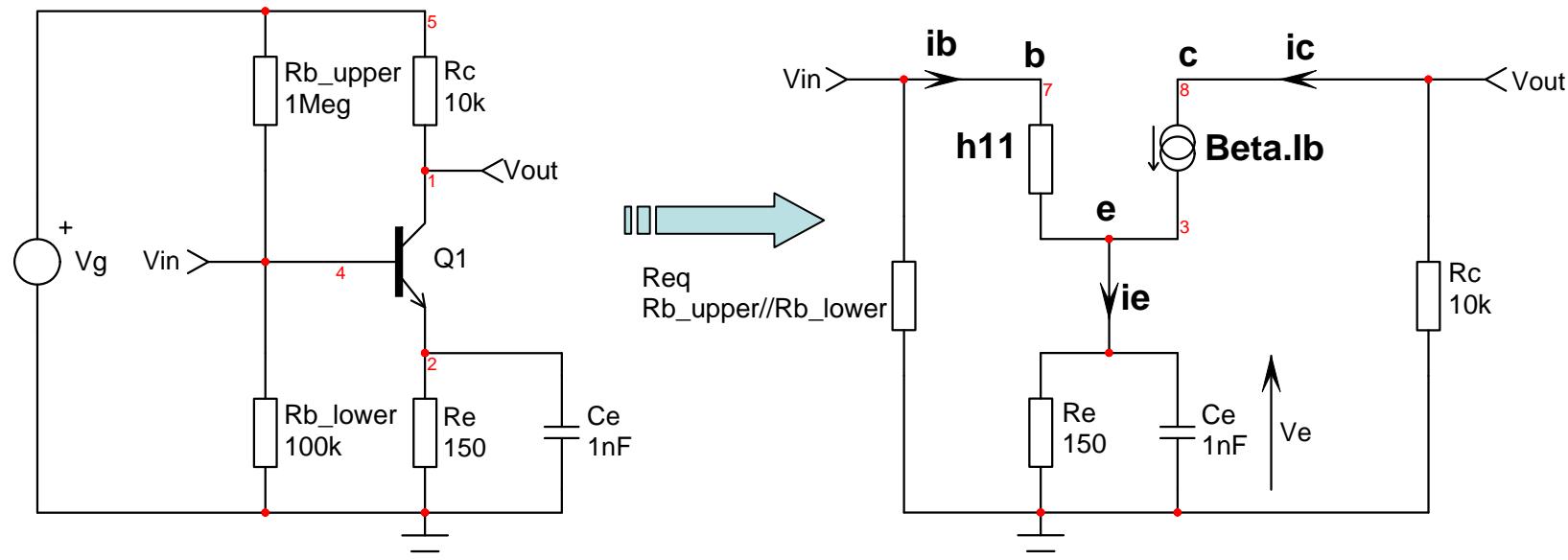- The transistor is a highly non-linear device:
 - ❖ Replace the transistor with its small-signal model
 - ❖ Solve a system of linear equations




Remember the **bipolars**
Ebers-Moll model...



Replace Q_1 by its small-signal model

The PWM Switch Concept

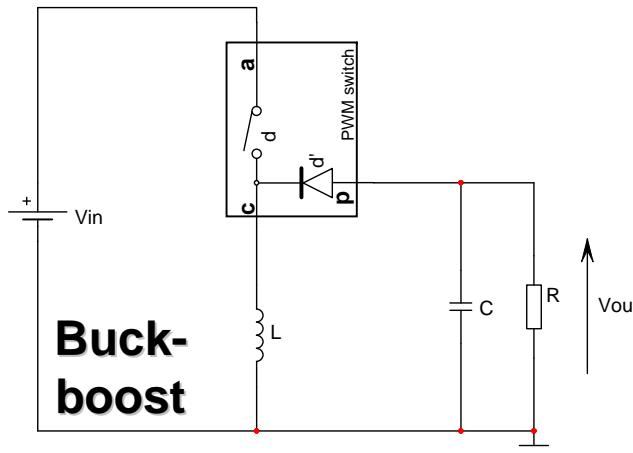
- The PWM switch model works in all two switch converters:
 - ❖ Rotate the model to match the switch and diode connections
 - ❖ Solve a system of linear equations



Buck-boost

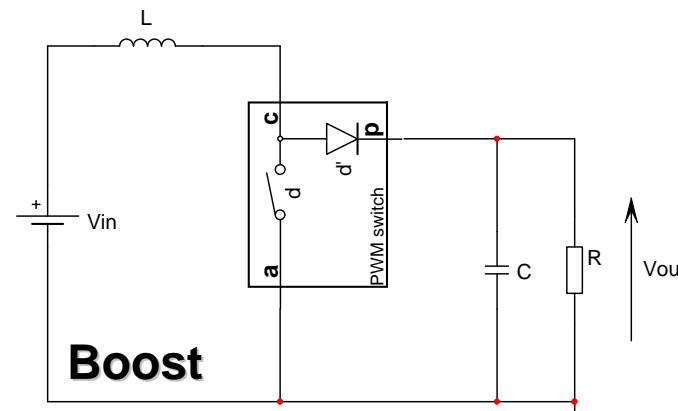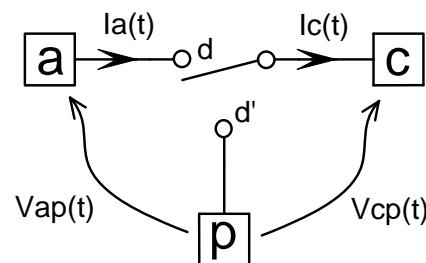



Boost

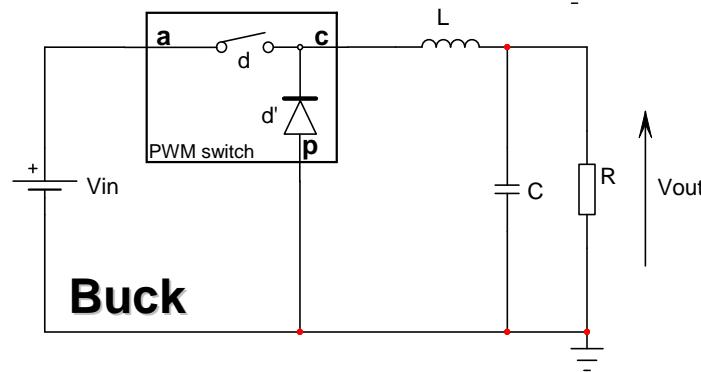


Buck

The PWM Switch Concept

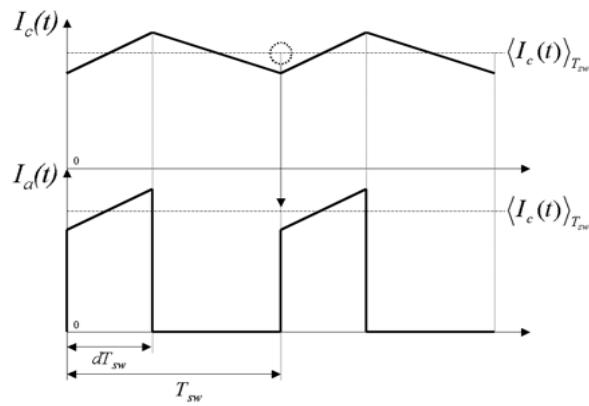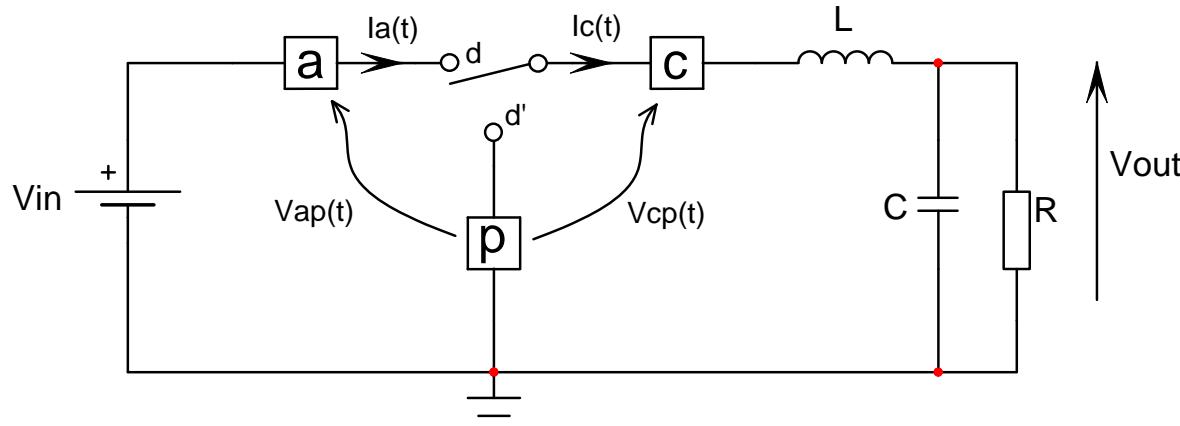- The keyword with average modeling: waveforms averaging



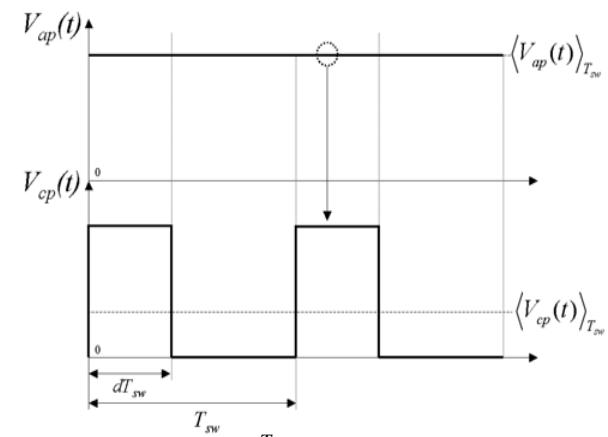
$$\langle I_a(t) \rangle_{T_{sw}} = I_a = \frac{1}{T_{sw}} \int_0^{T_{sw}} I_a(t) dt = d \langle I_c(t) \rangle_{T_{sw}} = \boxed{dI_c}$$



$$\langle V_{cp}(t) \rangle_{T_{sw}} = V_{cp} = \frac{1}{T_{sw}} \int_0^{T_{sw}} V_{cp}(t) dt = d \langle V_{ap}(t) \rangle_{T_{sw}} = \boxed{dV_{ap}}$$



The PWM Switch Concept

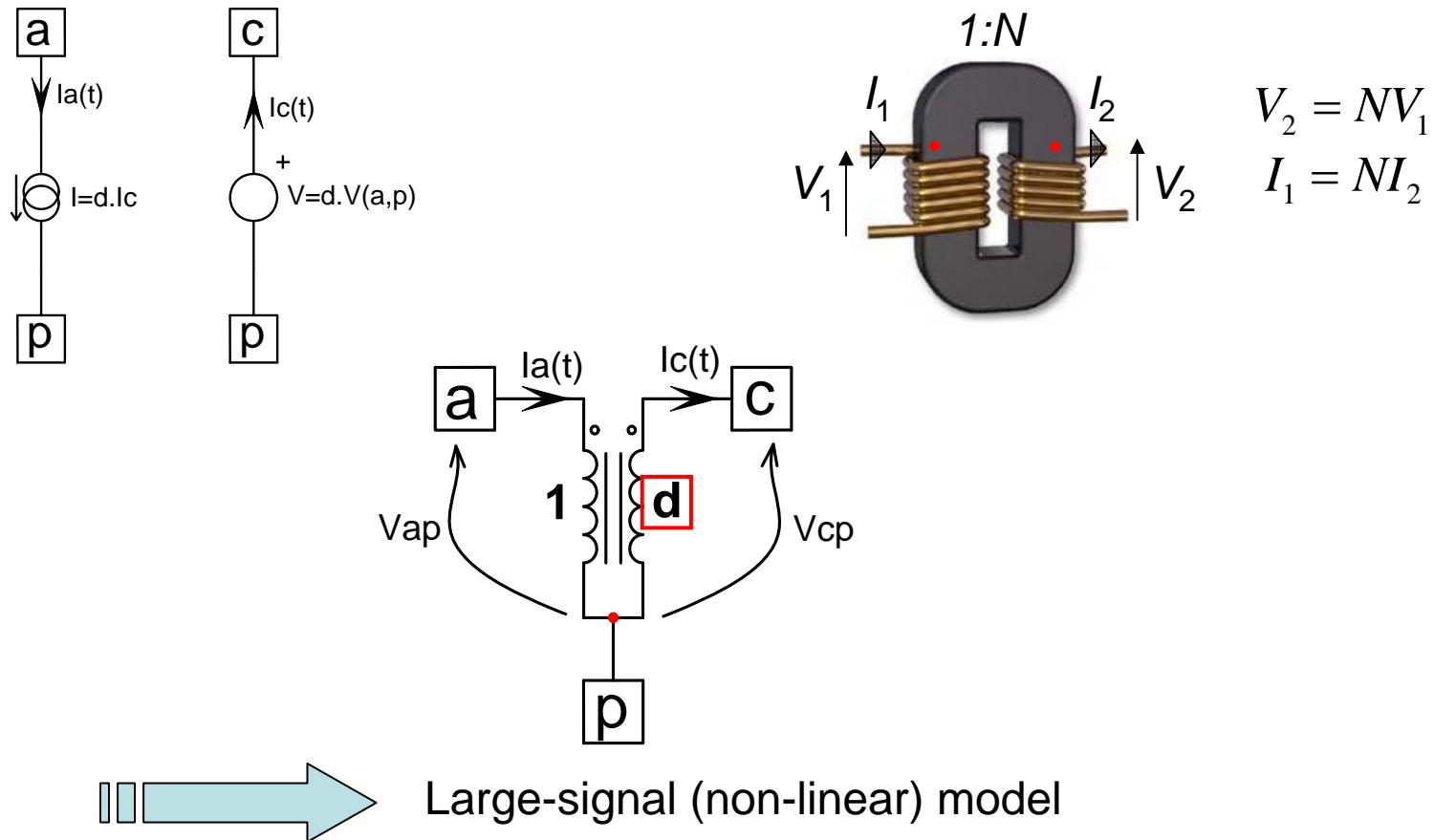- The obtained set of equations is that of a transformer
 - A CCM two-switch DC-DC can be modeled like a $1:D$ transformer!



The PWM Switch Concept

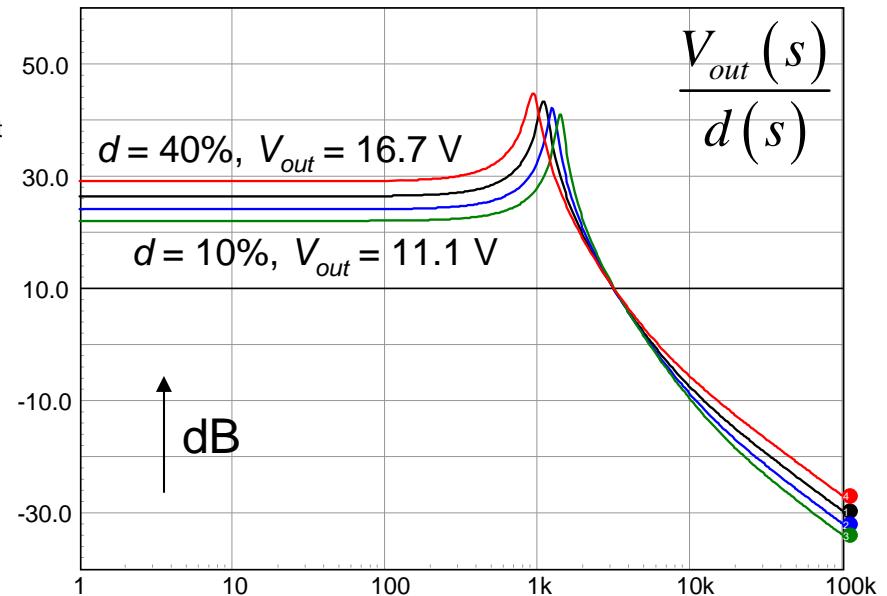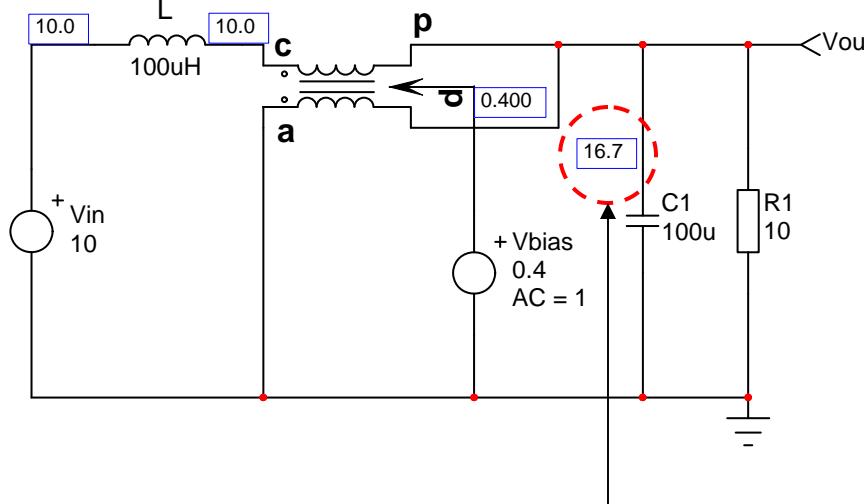- SPICE only deals with linear equations
- It first computes a bias point then it linearizes the network



Always verify the dc operating point!

- No equations, result appears in a second!
- Make sure the bias point is correct...

The PWM Switch Concept

- We have a set of non-linear equations: can't derive transfer functions!
- We need a small-signal model: linearize the equations by hand
- ❖ two options: perturbation or partial derivatives...

Perturbation

$$I_a = dI_c \quad V_{cp} = dV_{ap}$$

$$I_a = I_{a0} + \hat{i}_a \quad V_{cp} = V_{cp0} + \hat{v}_{cp}$$

$$I_c = I_{c0} + \hat{i}_c \quad d = d_0 + \hat{d}$$

$$d = d_0 + \hat{d}$$

same

$$I_{a0} + \hat{i}_a = (d_0 + \hat{d})(I_{c0} + \hat{i}_c)$$

$$I_{a0} = d_0 I_{c0} \quad V_{cp0} = d_0 V_{ap0}$$

$$\hat{i}_a = d_0 \hat{i}_c + \hat{d} I_{c0} \quad \hat{v}_{cp} = d_0 \hat{v}_{ap} + \hat{d} V_{ap0}$$

Partial derivatives

$$I_a = dI_c \quad V_{cp} = dV_{ap}$$


$$\hat{i}_a = \frac{\partial I_a}{\partial I_c} \hat{i}_c + \frac{\partial I_a}{\partial d} \hat{d} \quad \hat{v}_{cp} = \frac{\partial V_{cp}}{\partial V_{ap}} \hat{v}_{ap} + \frac{\partial V_{cp}}{\partial d} \hat{d}$$

$$\hat{i}_a = d_0 \hat{i}_c + \hat{d} I_{c0} \quad \hat{v}_{cp} = d_0 \hat{v}_{ap} + \hat{d} V_{ap0}$$

ac and dc equations ac equations
No dc point

The PWM Switch Concept

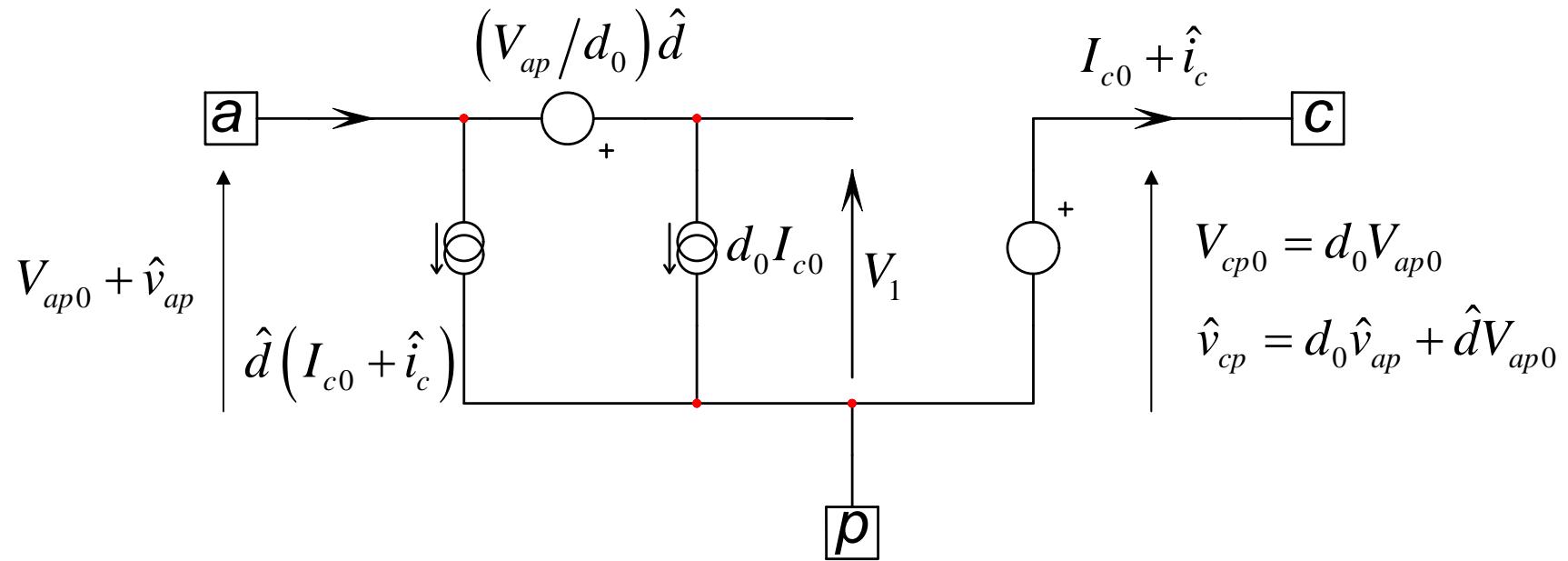- Put the small-signal sources in the large-signal model
 - ❖ You obtain the small-signal model of the CCM PWM switch





- You can now analytically find the dc bias and the ac response!

Agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- **The PWM switch concept, DCM**
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion

The PWM Switch in DCM

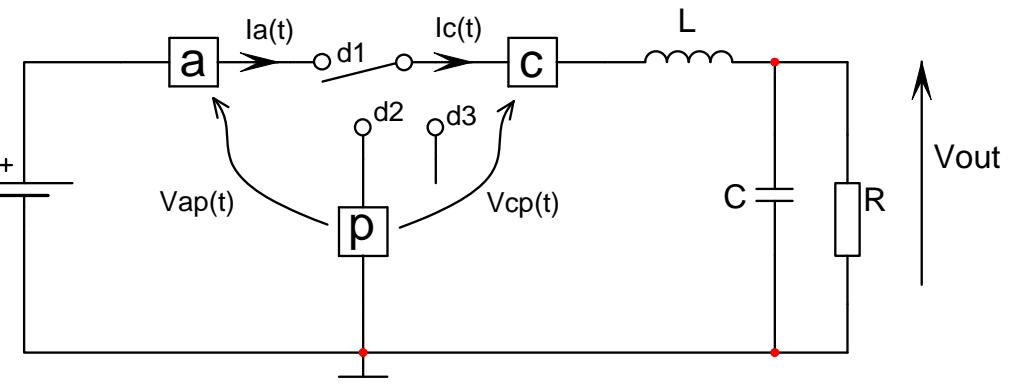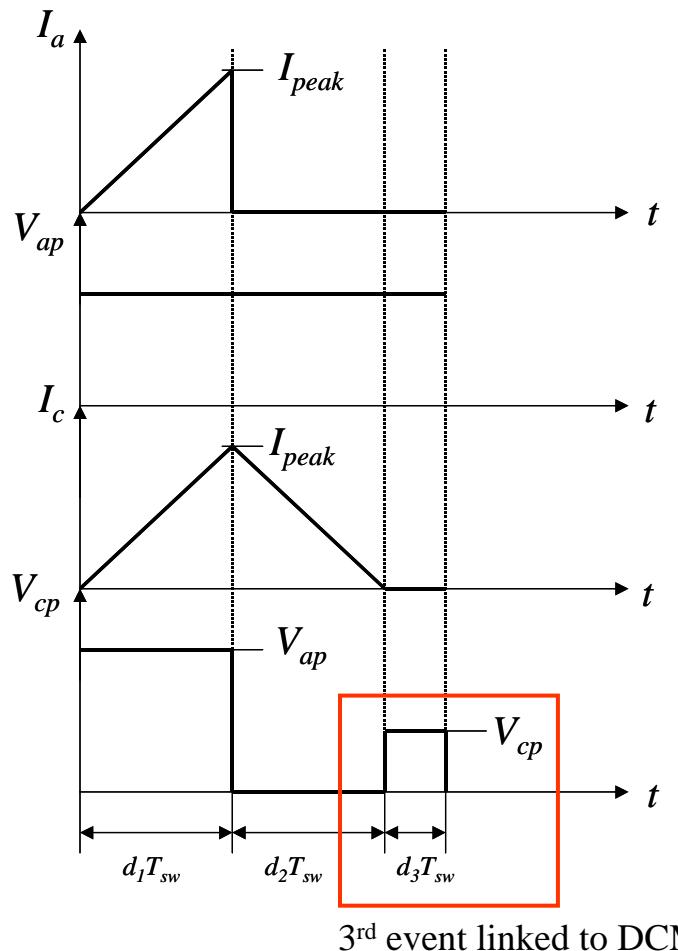- The original model could not be auto-toggling
- A new DCM-CCM model has been derived



Extract and replace


$$I_a = \frac{I_{peak} d_1}{2}$$

$$I_c = \frac{I_{peak} (d_1 + d_2)}{2}$$

$$I_c = I_a \frac{(d_1 + d_2)}{d_1}$$

The PWM Switch in DCM

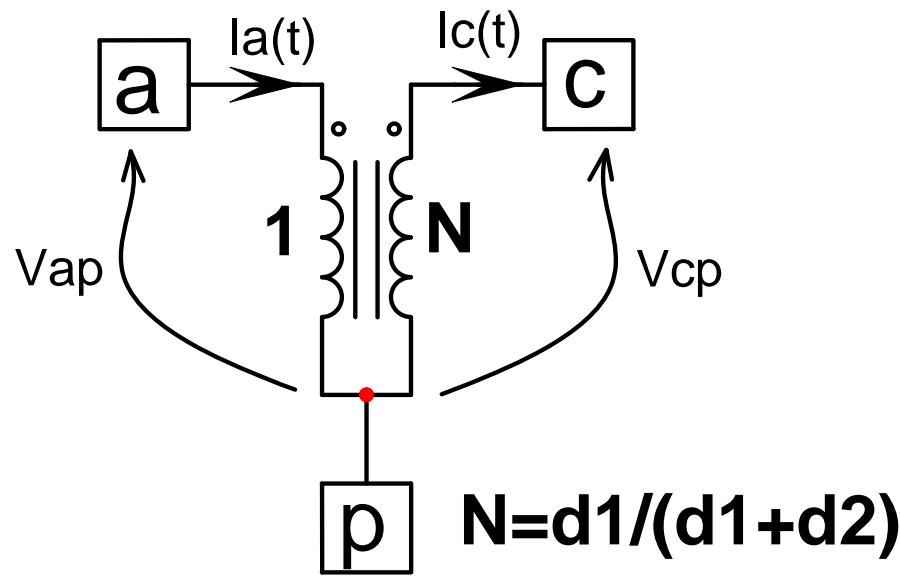- By clamping the d_2 equation, the circuit toggles between the modes



Clamp d_2 :

$$d_2 \text{ CCM} = 1 - d_1$$

$$d_2 \text{ DCM} = 1 - d_1 - d_3$$



$$d_2 < 1 - d_1$$

model is in DCM!

$$d_2 = \frac{2I_c L - V_{ac} d_1^2 T_{sw}}{V_{ac} d_1 T_{sw}} = \frac{2LF_{sw}}{d_1} \frac{I_c}{V_{ac}} - [d_1]$$


Model input

Agenda


- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- **The voltage-mode model at work**
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion

The PWM Switch in DCM

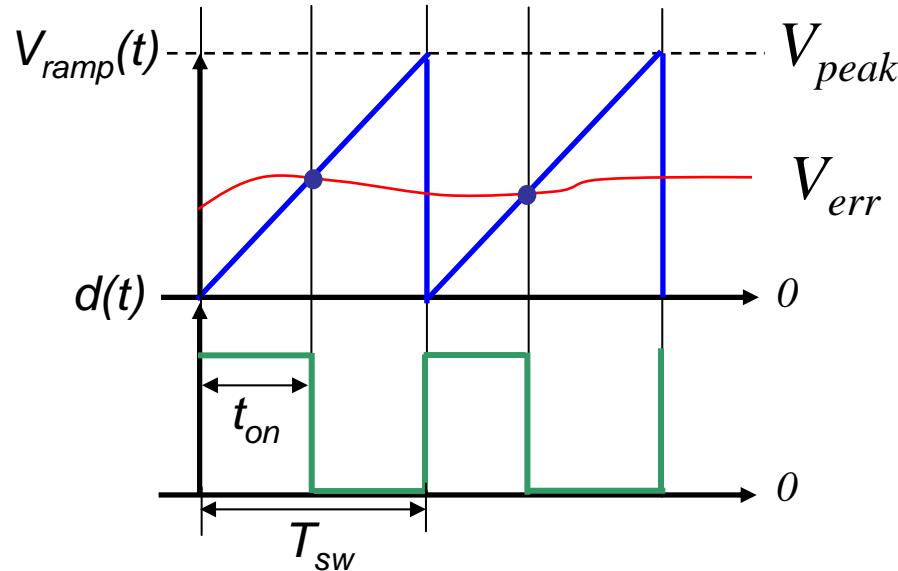- In voltage-mode, the duty-cycle is built with a ramp generator
- The transition occurs when the error voltage crosses the ramp



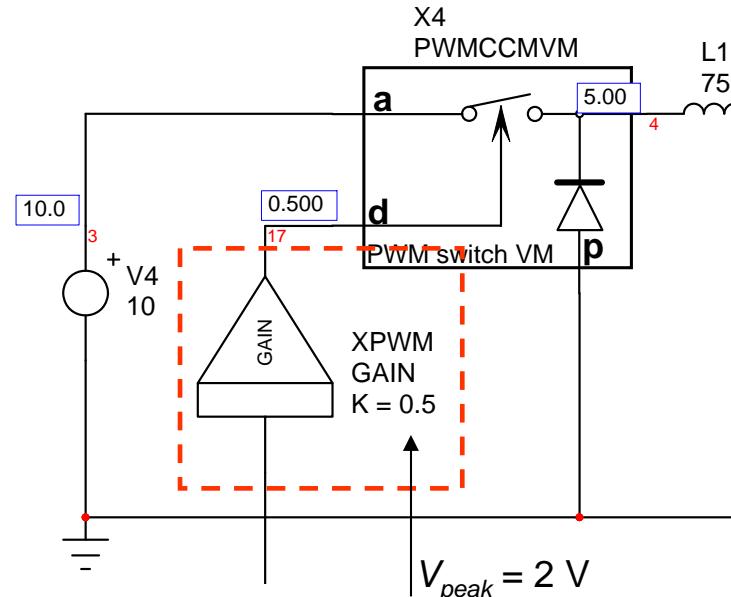
$$\left. \begin{aligned} V_{err}(t) &= V_{peak} \frac{t_{on}(t)}{T_{sw}} = V_{peak} d(t) \\ d(t) &= \frac{V_{err}(t)}{V_{peak}} \end{aligned} \right\} \frac{d}{d} \left(\frac{d(t)}{V_{err}(t)} \right) = \frac{1}{V_{peak}} = K_{PWM}$$





The Voltage-Mode Model at Work

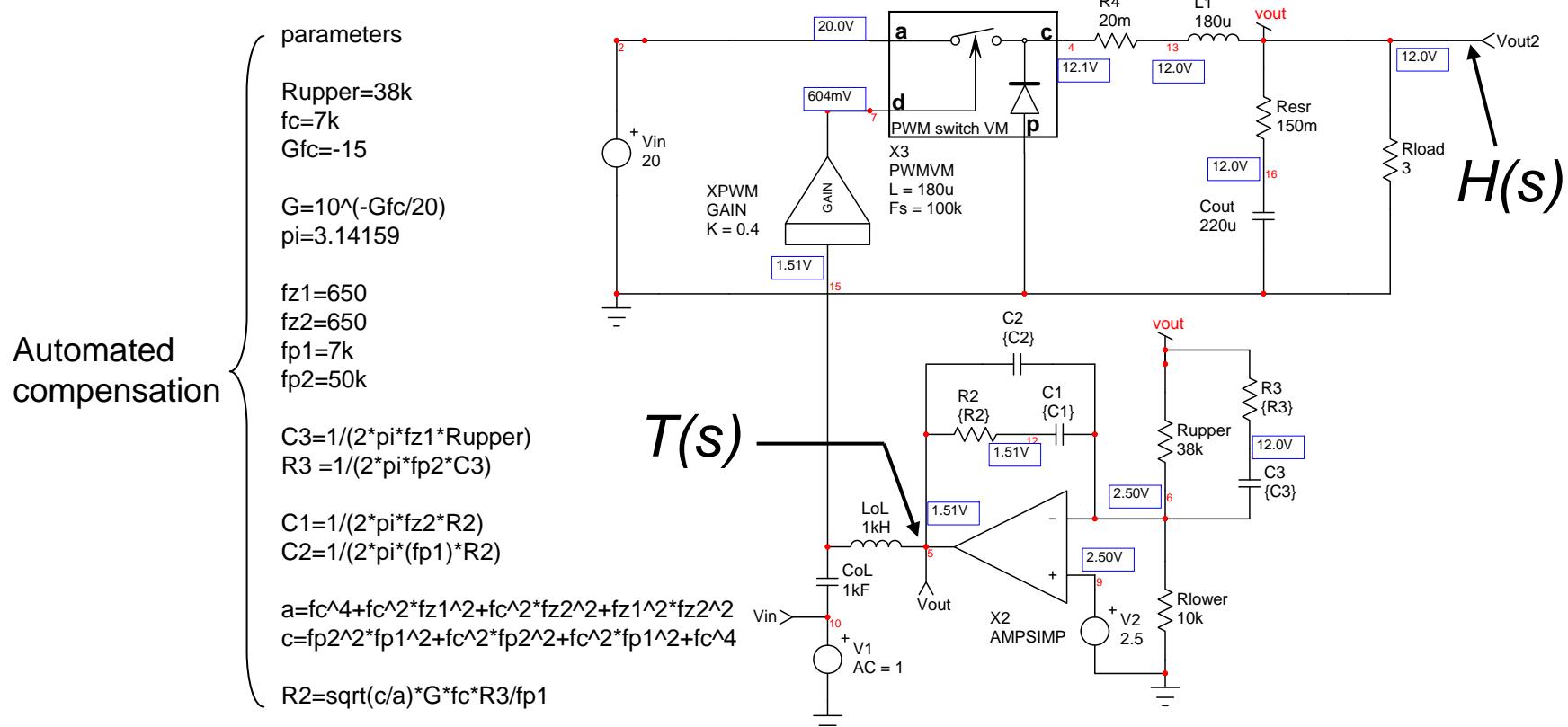- Let us compensate a buck converter operated in CCM and DCM
1. Run an open-loop Bode plot at full load, lowest input
 2. Identify the excess/deficiency of gain at the selected cross over
 3. Place a double zero at f_0 , a pole at the ESR zero and a pole at $F_{sw}/2$
 4. Check final loop gain and run a transient load test



The Voltage-Mode Model at Work

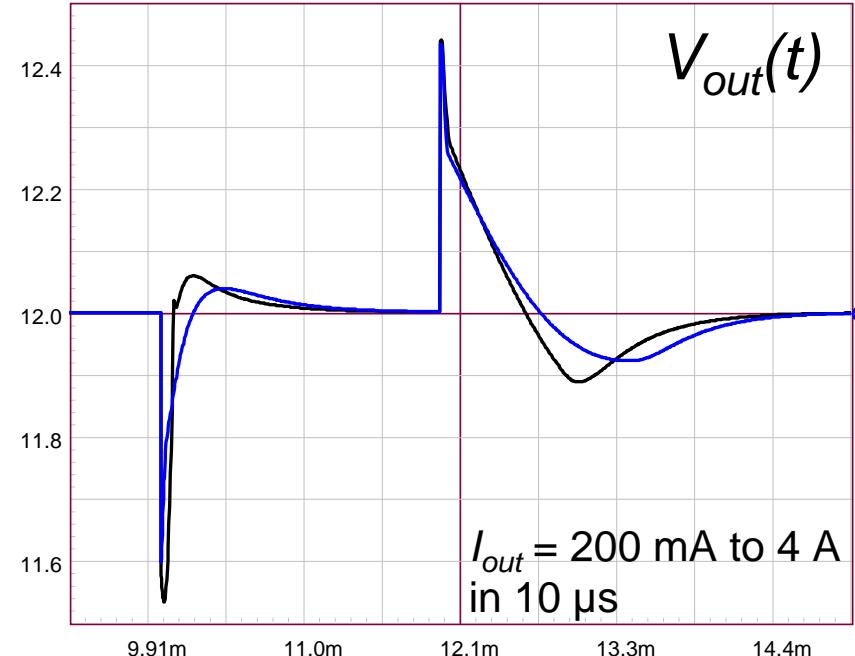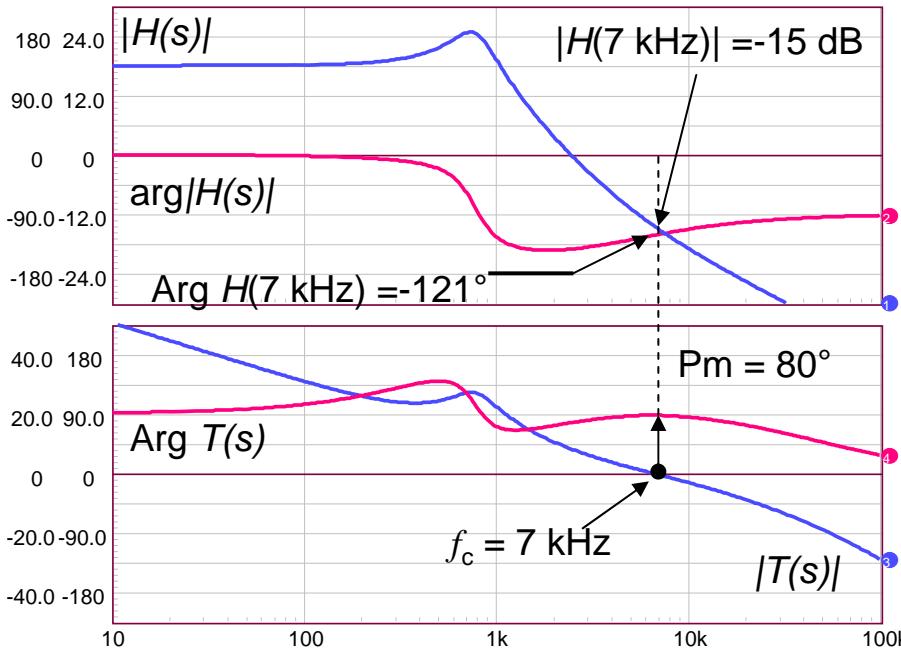- The Bode plot reveals a gain loss of -15 dB at 7 kHz
- The compensator provides a +15 dB gain increase plus phase boost




- The final loop gain shows a comfortable phase margin
- The transient response at both input levels shows a stable signal

Agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- **Current-mode modeling**
- The current-mode model at work
- Power factor correction
- Switching models
- EMI filtering
- Conclusion

Current-Mode Operation

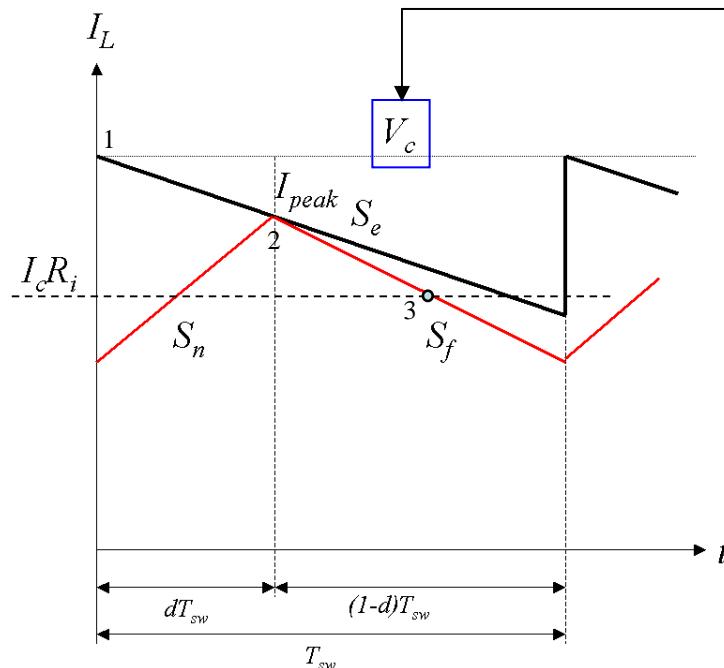- In voltage-mode, the error signal directly controls the duty cycle
- In current mode, the error voltage sets the inductor peak current
- To derive a model, observe the current signals and average them!



CCM

$$I_c(t)R_i = V_c(t) - d(t)T_{sw}S_e - \frac{S_f d'(t)T_{sw}}{2}$$

$$I_c = \frac{V_c}{R_i} + \boxed{d \frac{T_{sw}S_e}{R_i} - V_{cp}(1-d)\frac{T_{sw}}{2L}}$$


Diagram illustrating the derivation of the current expression:

Point **a**: $I_a(t) = I_c(t)$
p: $I = d \cdot I_c$

Point **c**: $I_c(t) = I_c(t)$
p: $I = V_c / R_i$
 $I = I_u$
 C_s

Current-Mode Operation

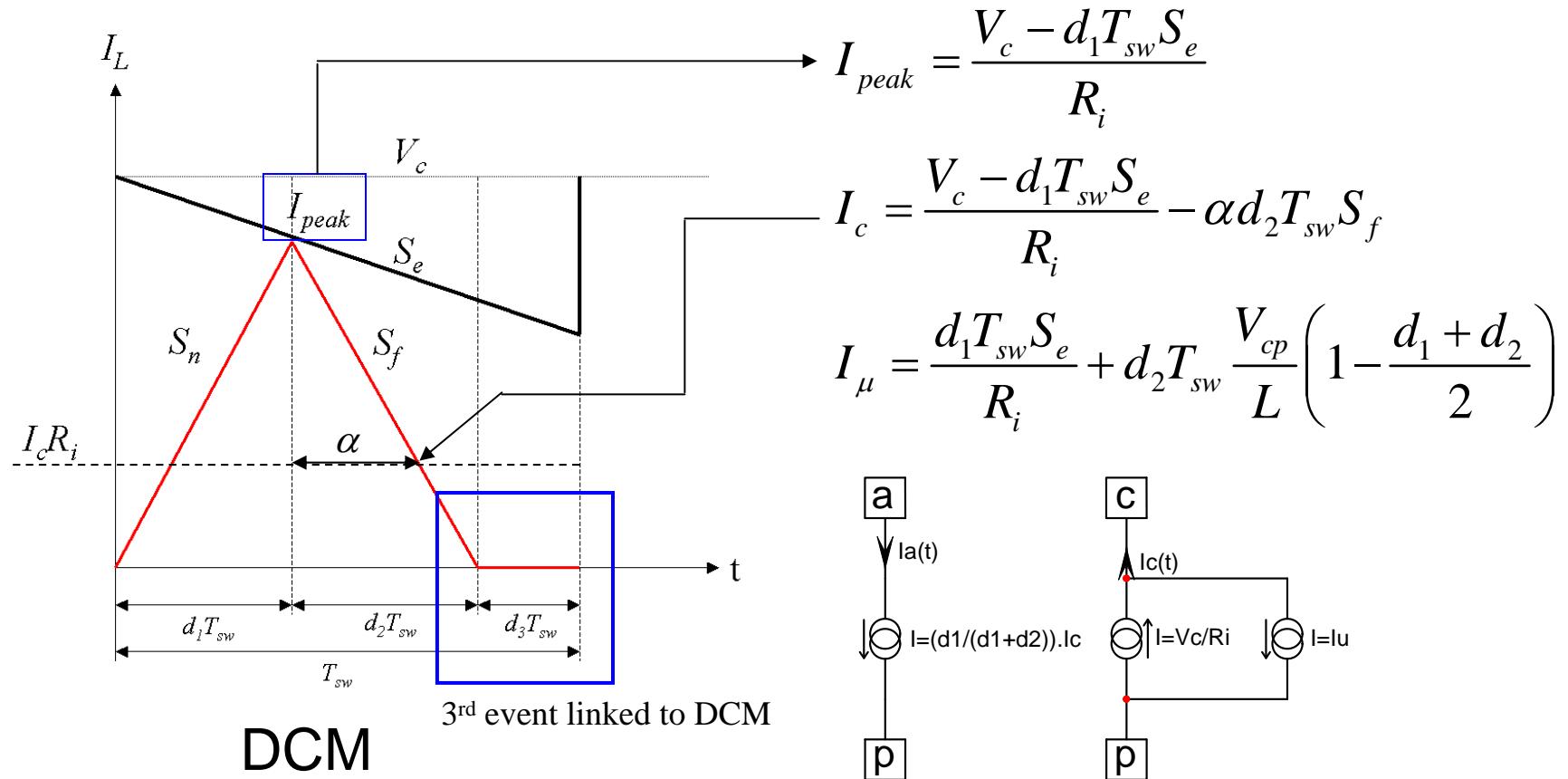- Do the same for DCM signals
- Match the previous structure to build a CCM/DCM model



Agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work**
 - Power factor correction
 - Switching models
 - EMI filtering
 - Conclusion

The Current-Mode Model at Work


- To study a converter, we can write down the equations
- Or use a SPICE simulation to get the Bode plot in a second
- Take the example of a current-mode flyback converter

$$|H(f)| = 20 \log_{10} \left[G_0 \frac{\sqrt{1 + \left(\frac{f}{f_{z1}}\right)^2} \sqrt{1 + \left(\frac{f}{f_{z2}}\right)^2} \sqrt{1 + \left(\frac{f}{f_{z3}}\right)^2}}{\sqrt{1 + \left(\frac{f}{f_{p1}}\right)^2}} \frac{1}{\sqrt{\left(1 - \left(\frac{f}{f_n}\right)^2\right)^2 + \left(\frac{f}{f_n Q_p}\right)^2}} \right]$$

$$\arg H(f) = \tan^{-1} \left(\frac{f}{f_{z1}} \right) - \tan^{-1} \left(\frac{f}{f_{z2}} \right) + \tan^{-1} \left(\frac{f}{f_{z3}} \right) - \tan^{-1} \left(\frac{f}{f_{p1}} \right) - \tan^{-1} \left(\frac{f}{f_n Q_p} \frac{1}{1 - \left(\frac{f}{f_n}\right)^2} \right)$$

Stabilizing a CCM Flyback Converter

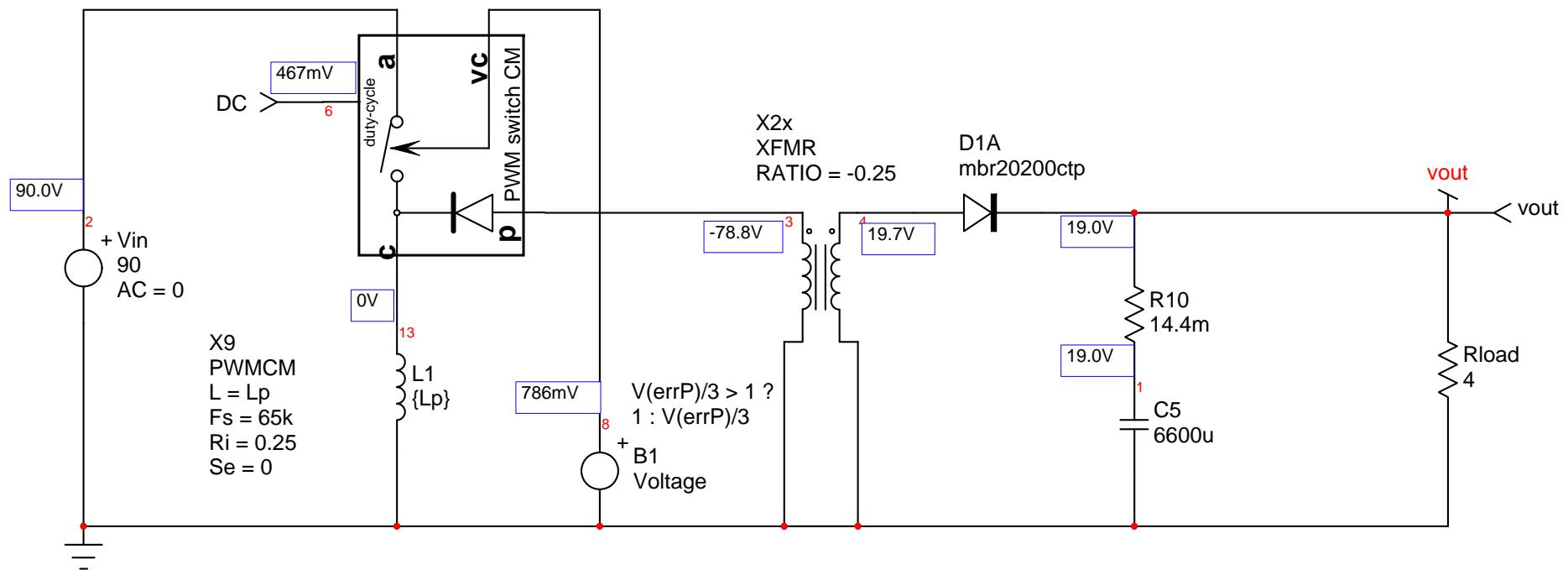
- Capture a SPICE schematic with an averaged model



- Look for the bias points values: $V_{out} = 19 \text{ V}$, ok
- $V_{setpoint} < 1 \text{ V}$, enough margin on current sense


Stabilizing a CCM Flyback Converter

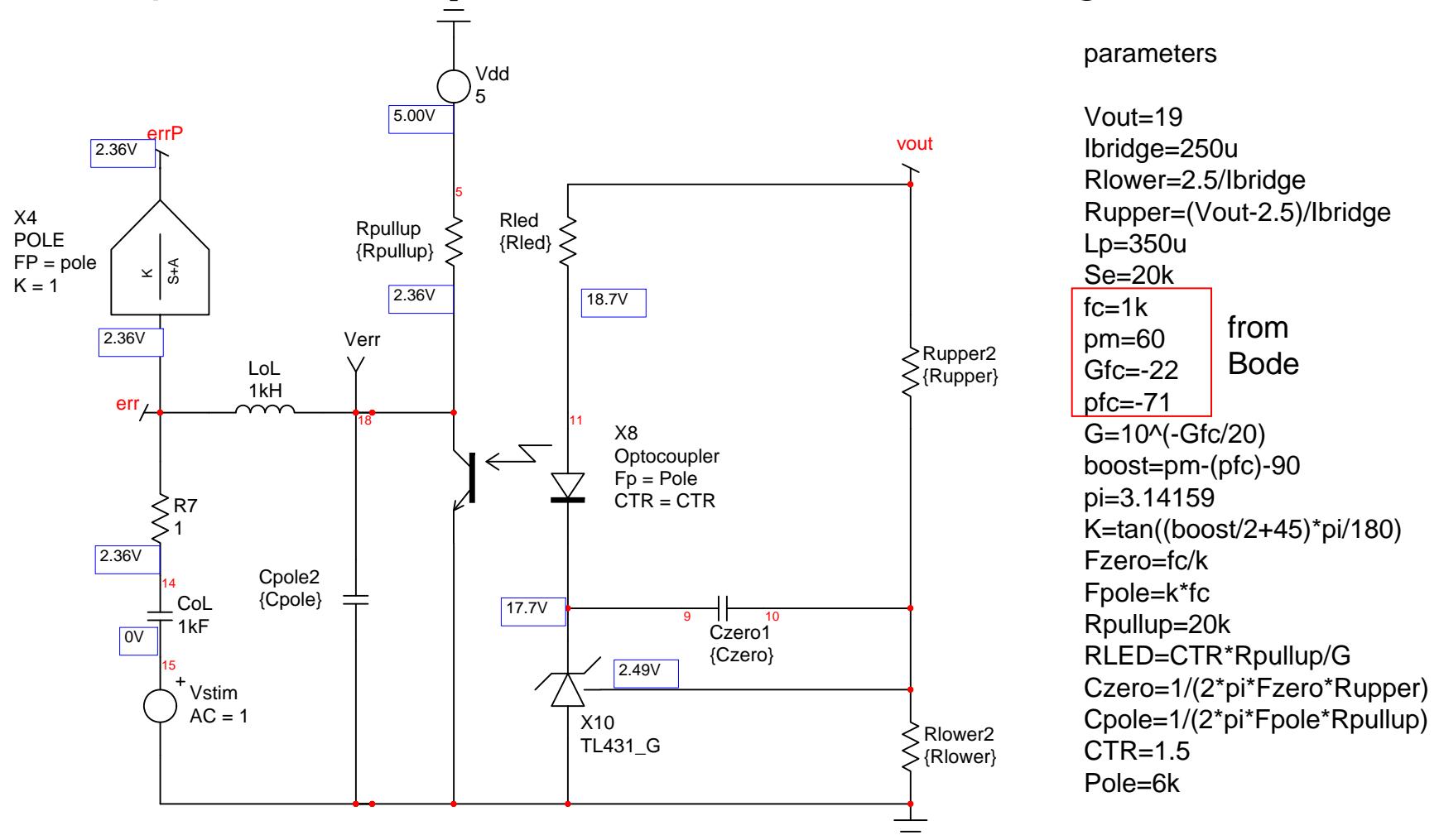- Capture a SPICE schematic with an averaged model



Stabilizing a CCM Flyback Converter

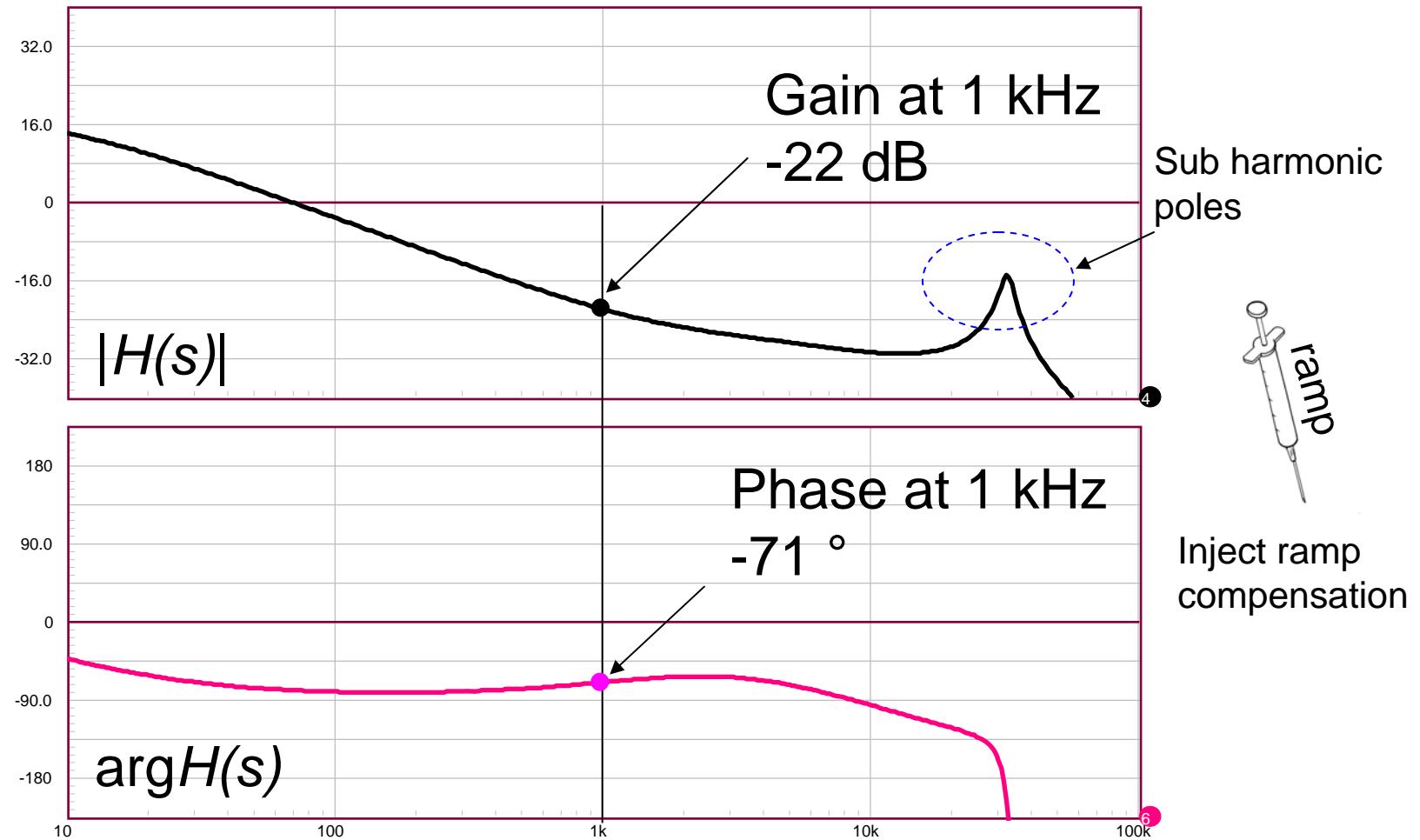- Capture a SPICE schematic with an averaged model




Stabilizing a CCM Flyback Converter

- The easiest way to damp the poles:
- Calculate the equivalent quality coefficient at $F_{sw}/2$
- Calculate the external ramp to make Q less than 1

$$Q = \frac{1}{\pi \left(D \cdot \frac{S_e}{S_n} + \frac{1}{2} - D \right)} = \frac{1}{3.14 \times (0.5 - 0.46)} = 8$$
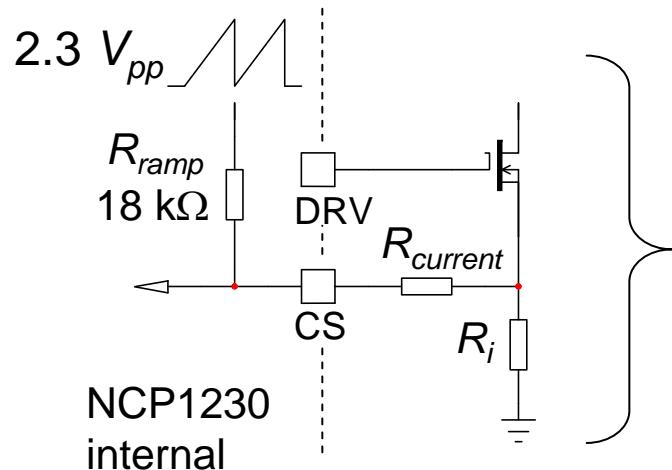
$$S_e = \frac{S_n}{D} \left(\frac{1}{\pi} - 0.5 + D \right) = \frac{V_{in} R_i}{L_p D} \left(\frac{1}{\pi} - 0.5 + D \right) = \frac{90 \times 0.25}{320 \mu \times (1 - 0.46)} \left(\frac{1}{3.14} - 0.5 + 0.46 \right) = 36 \text{ kV/s}$$




$$M_r = \frac{S_e}{S_n} = \frac{36k}{70k} = 51\% \quad \text{On-time slope } \frac{V_{in} R_i}{L_p}$$

$$S_{ramp} = \frac{2.3}{15\mu} = 153 \text{ kV/s}$$

$$R_{current} = \frac{M_r S_n R_{ramp}}{S_{ramp}} = \frac{0.51 \times 70k \times 18k}{153k} = 4.1 k\Omega$$


Stabilizing a CCM Flyback Converter

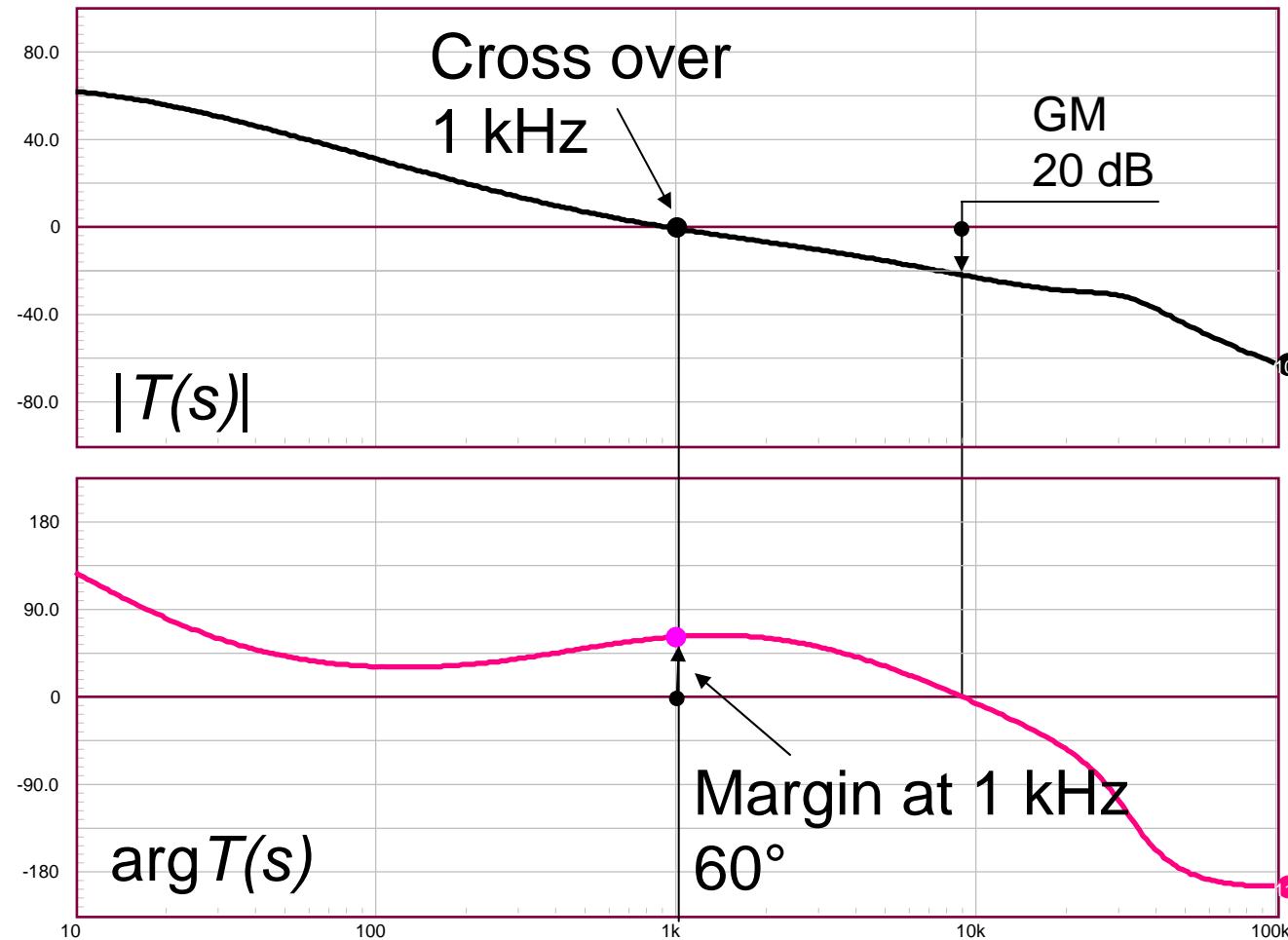- Boost the gain by +22 dB, boost the phase at f_c



Stabilizing a CCM Flyback Converter

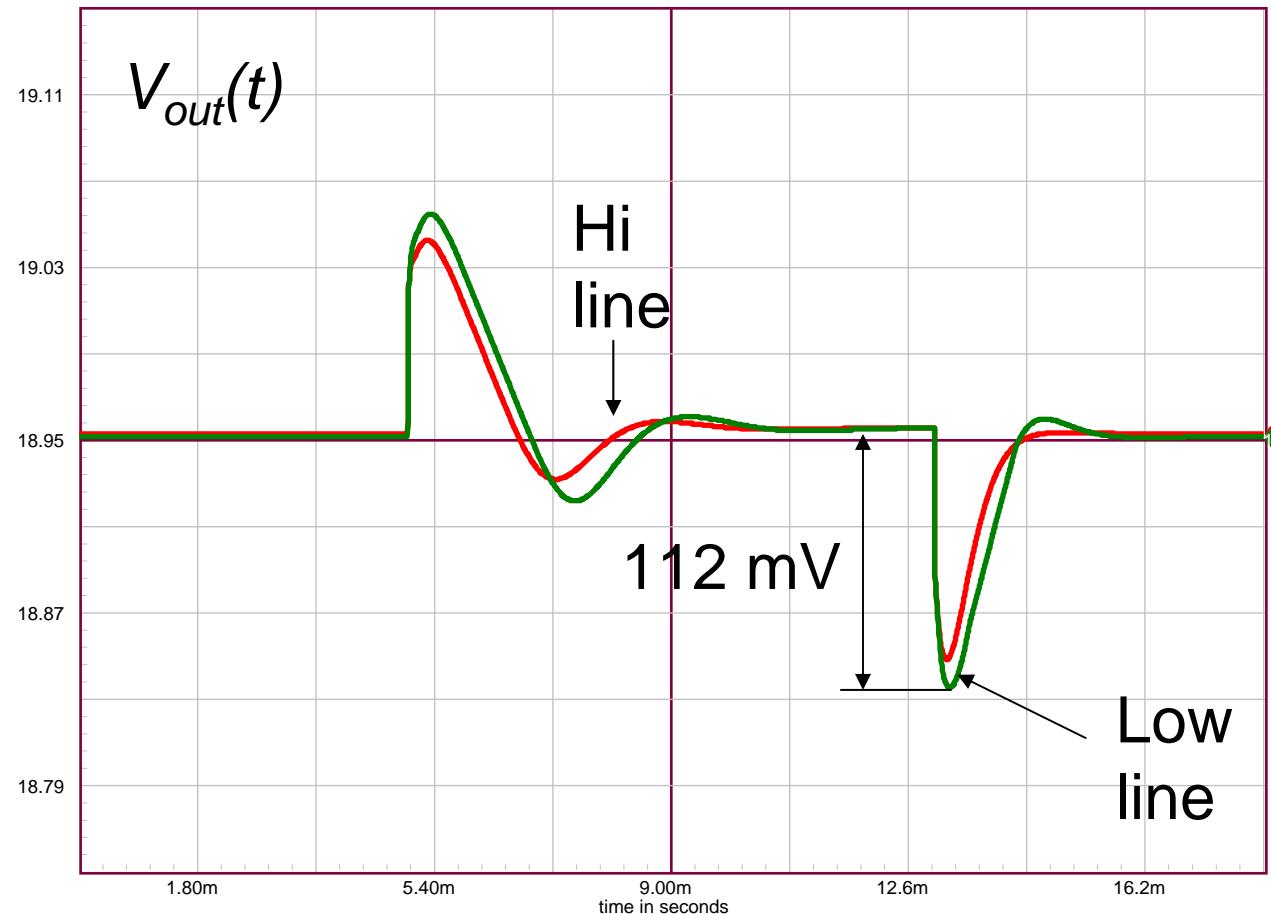- Test the response at both input levels, 90 and 265 Vrms
- Sweep ESR values and check margins again





Agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- **Power factor correction**
 - Switching models
 - EMI filtering
 - Conclusion


Power Factor Correction

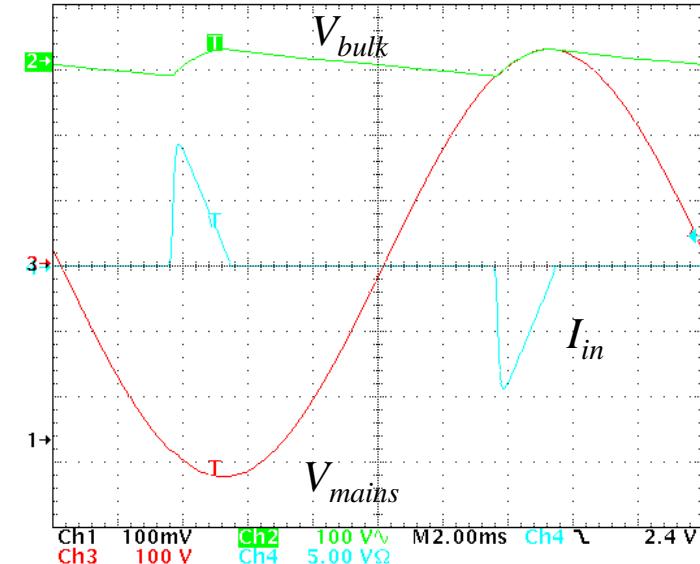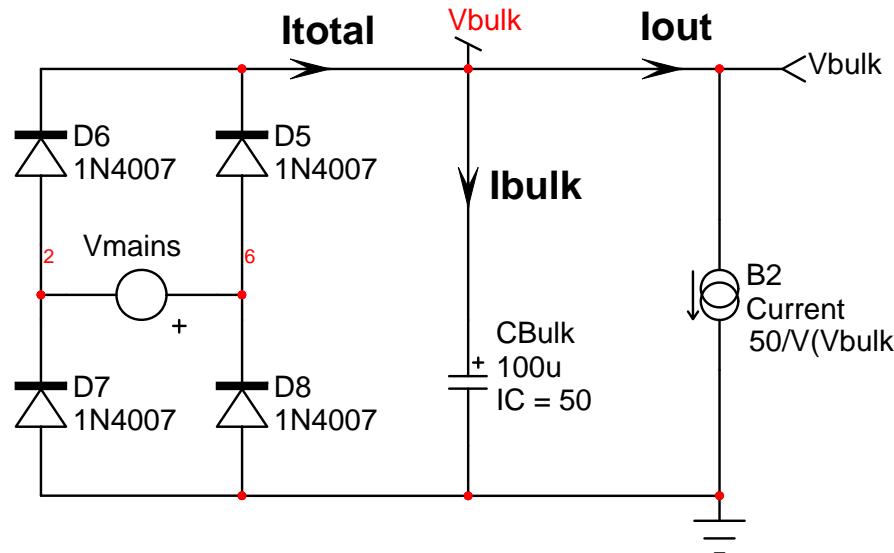- The bulk capacitor connects to a low-impedance source
- At the bulk capacitor refueling, a narrow peak current flows
- This peak conveys a large harmonic content




Power Factor Correction

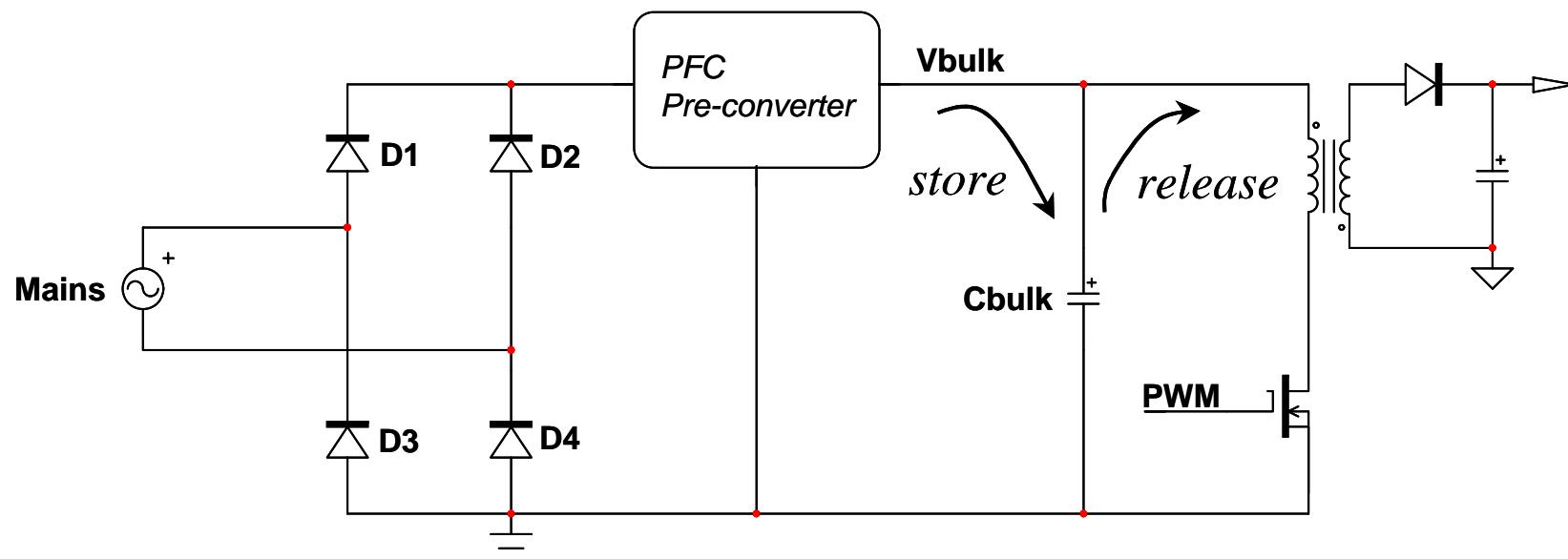- A pre-converter is installed as a front-end section
- The pre-converter draws a sinusoidal current
- The energy is stored and released in/by the bulk capacitor



Power Factor Correction

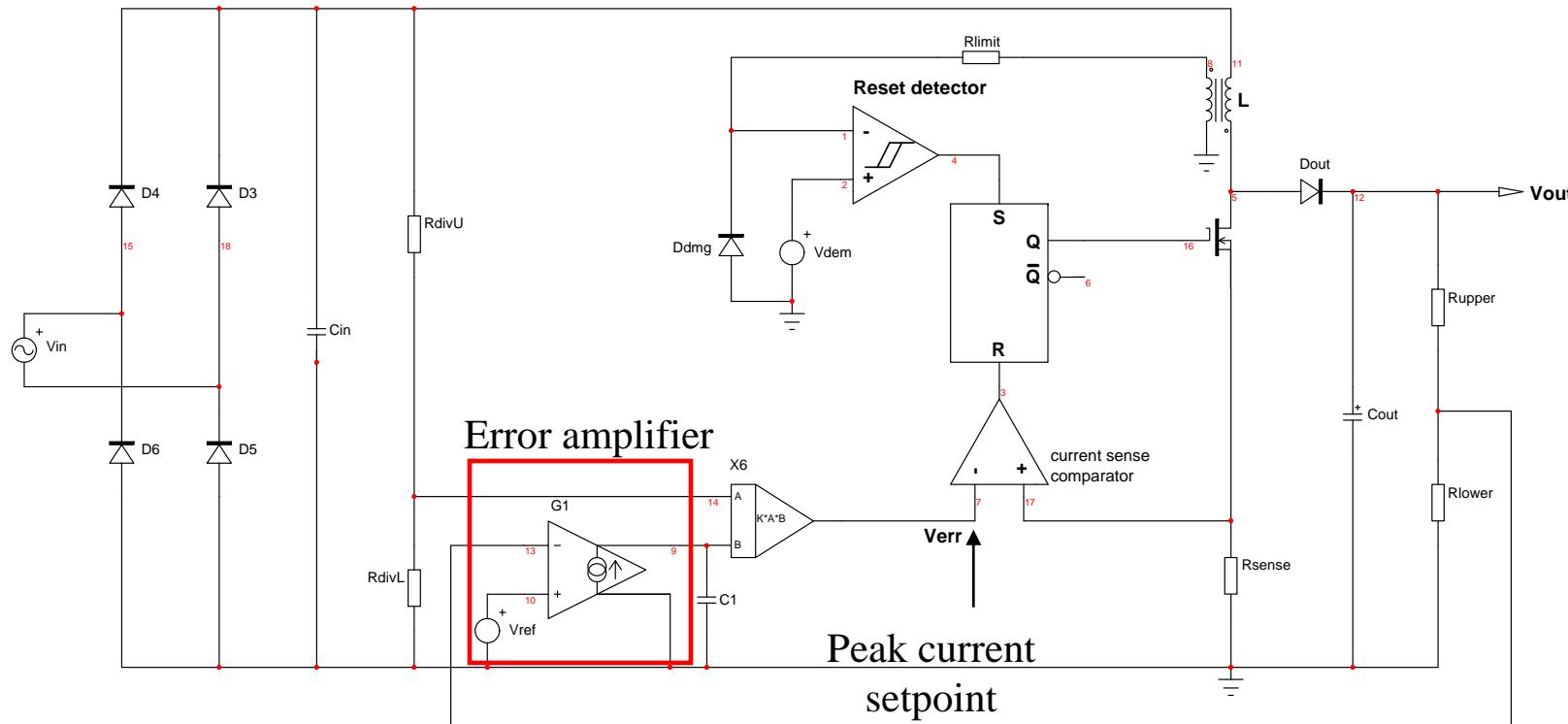
- One of the most popular technique uses Borderline mode
- The MC33262 operates in peak current mode control



- The NCP1606 also operates in constant-on time

Power Factor Correction

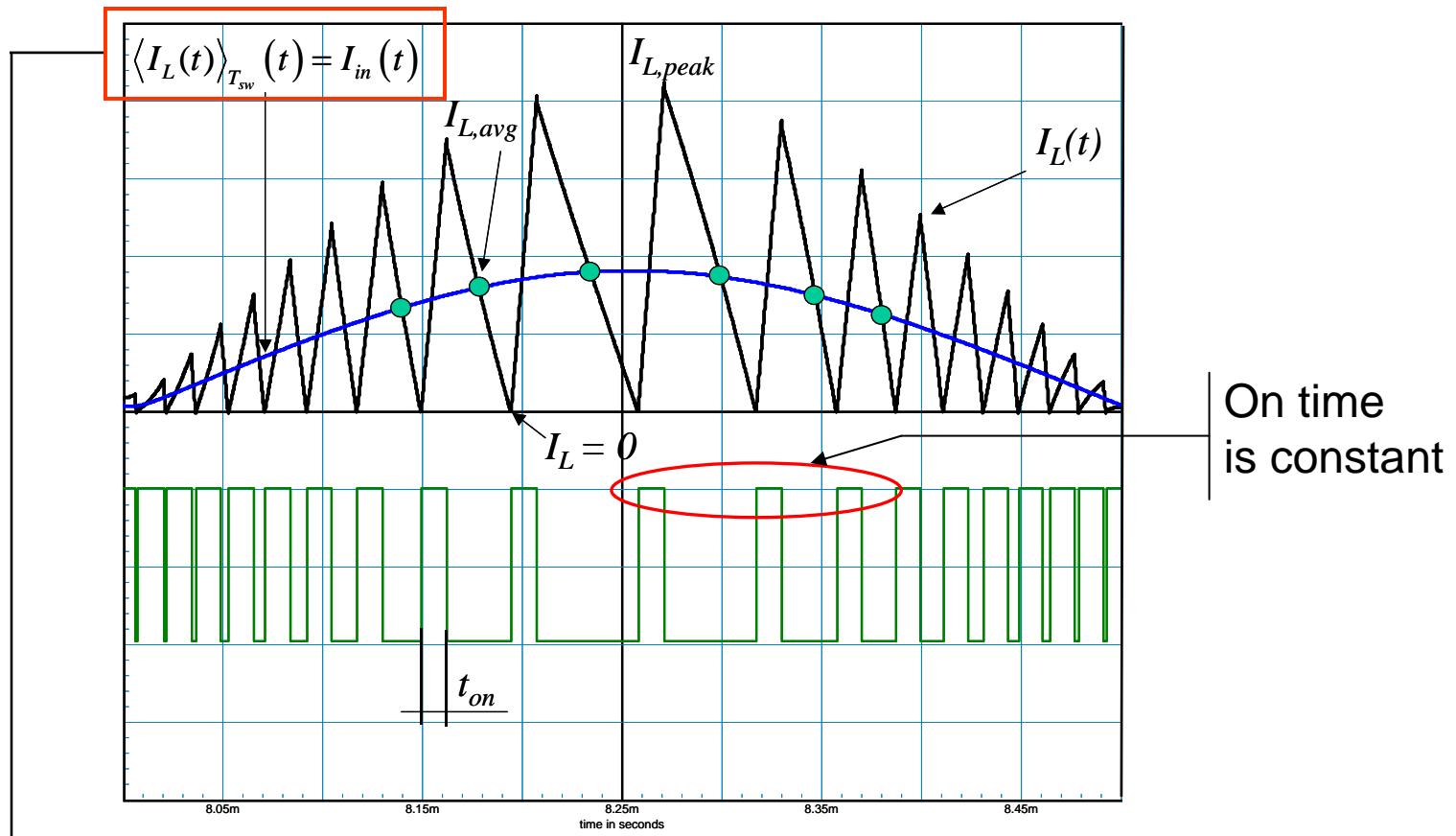
- The core is always reset from cycle to the other



- the average inductor current is half the inductor peak current value


Power Factor Correction

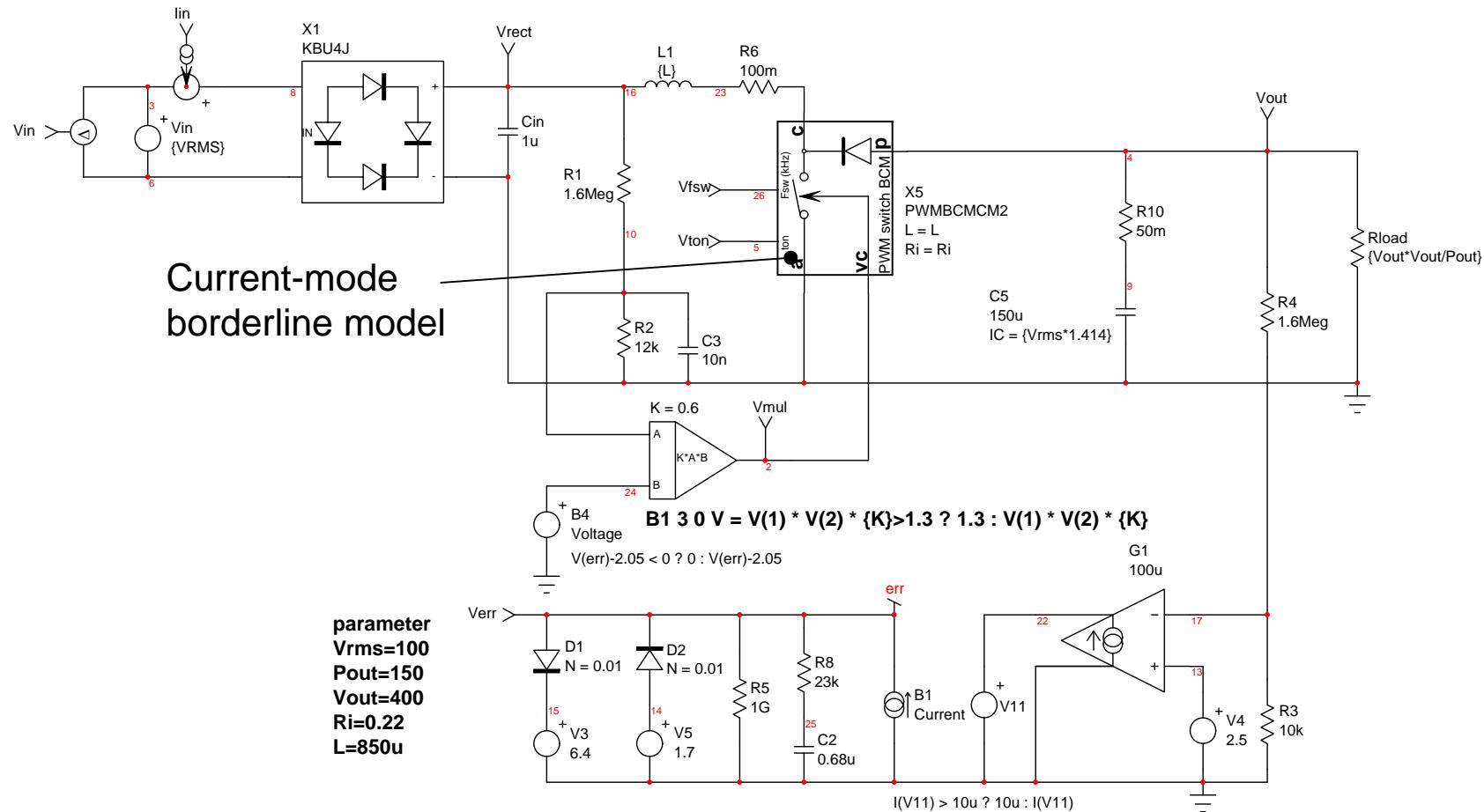- A 150 W BCM PFC average example with the MC33262





Power Factor Correction

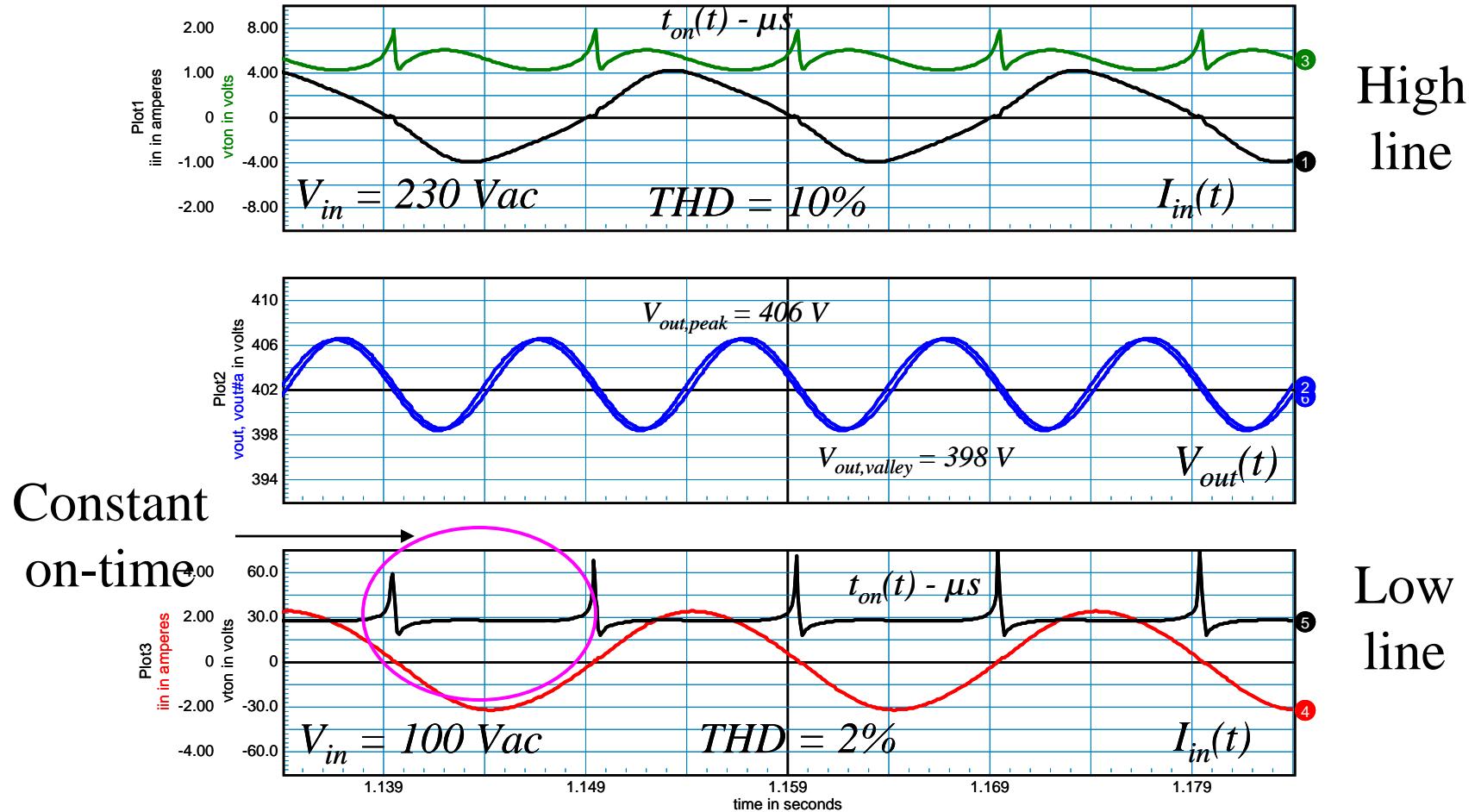- Average models can also work in transient conditions





Power Factor Correction

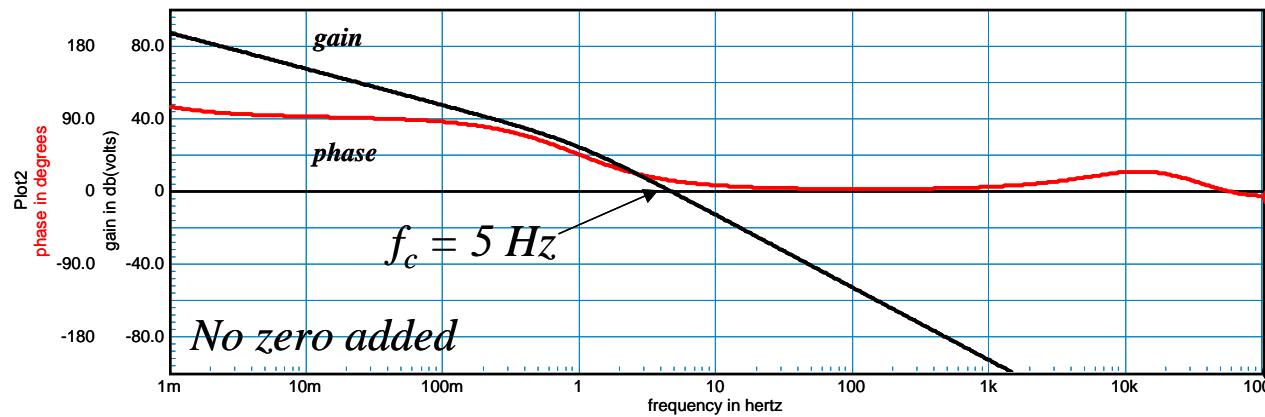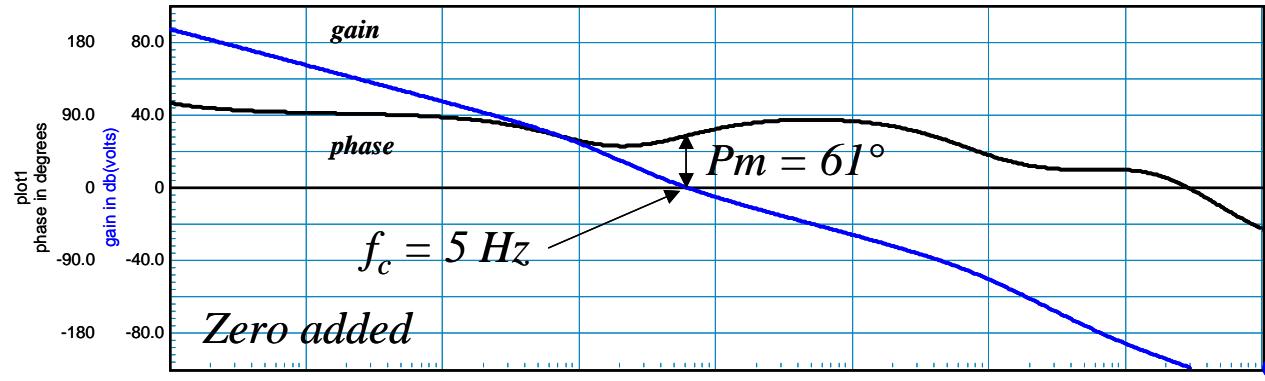- Use the model to boost the phase at the cross over point



Power Factor Correction

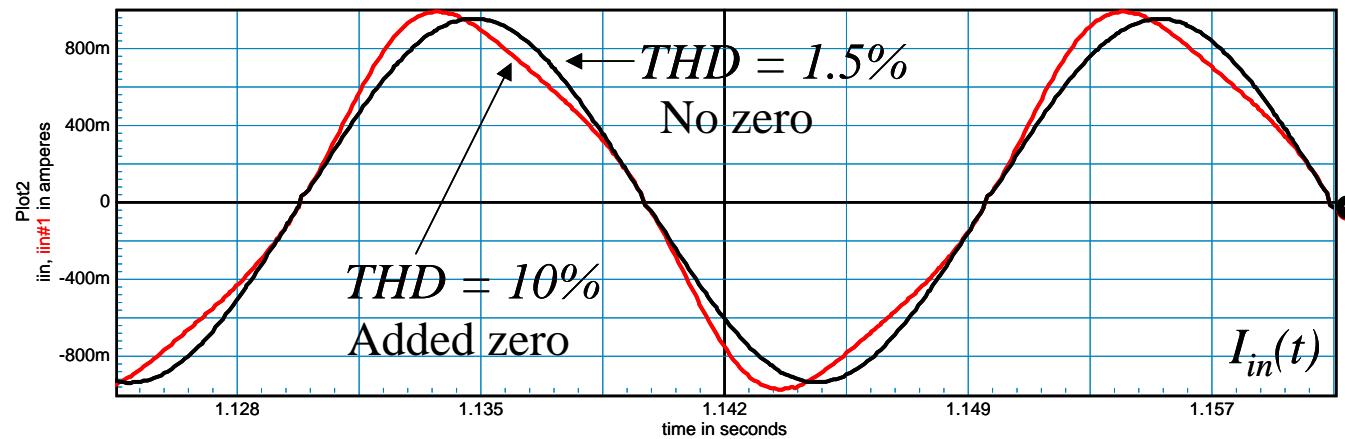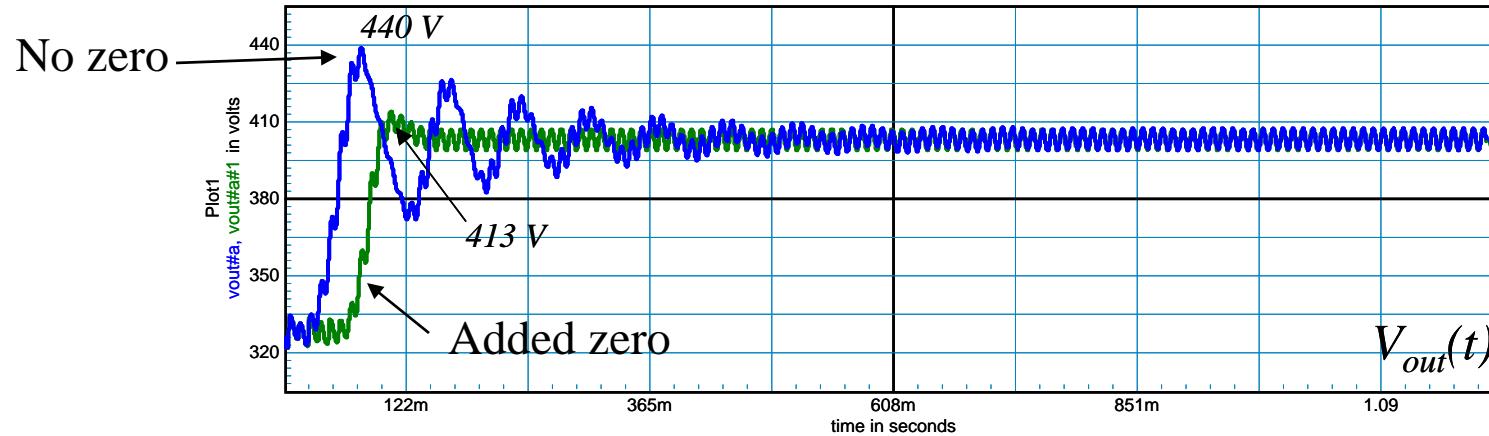- The zero improves the overshoot but degrades the THD...




Agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- **Switching models**
- EMI filtering
- Conclusion


Switching Models, the Breadboard on PC

- Turn your PC into a virtual breadboard

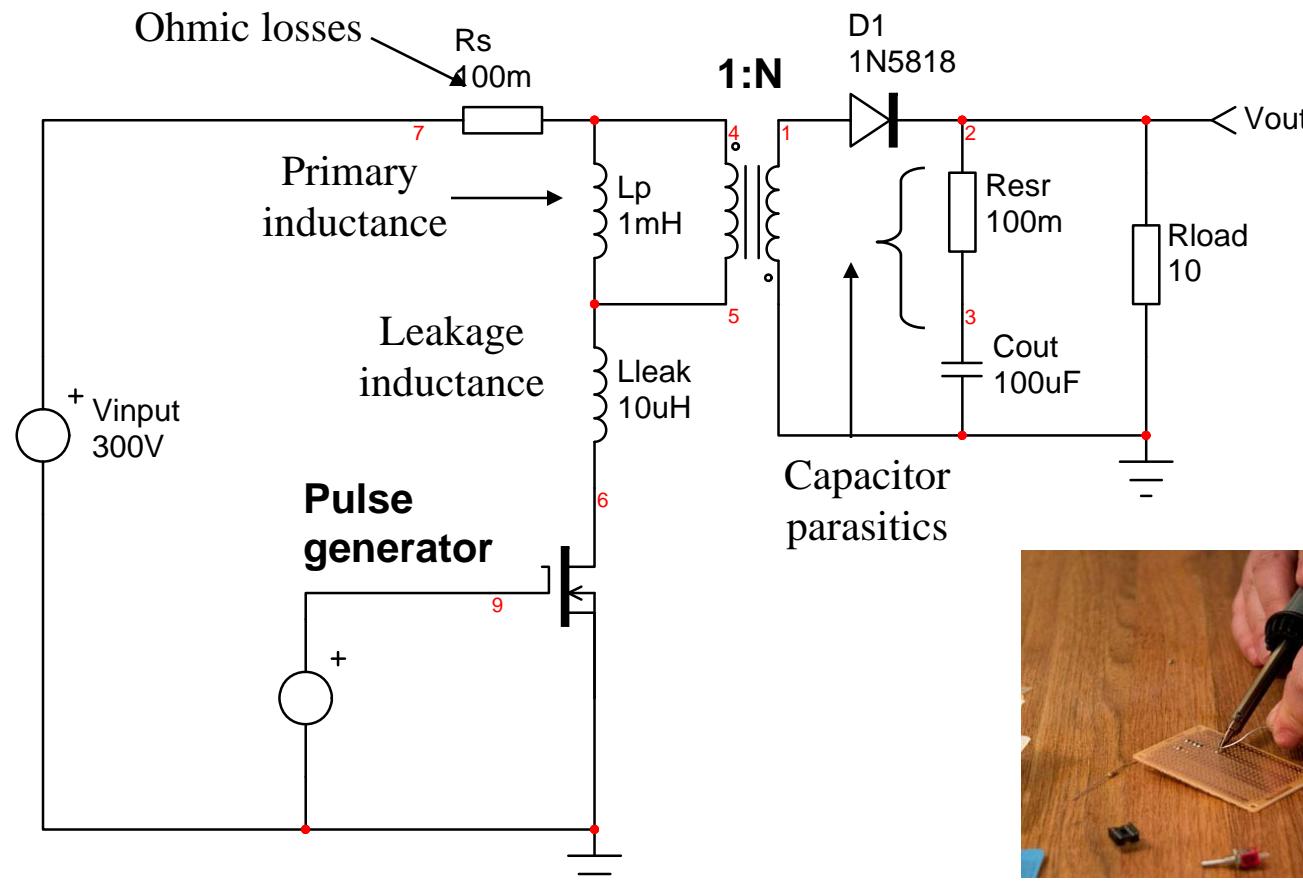


Switching Models, the Breadboard on PC

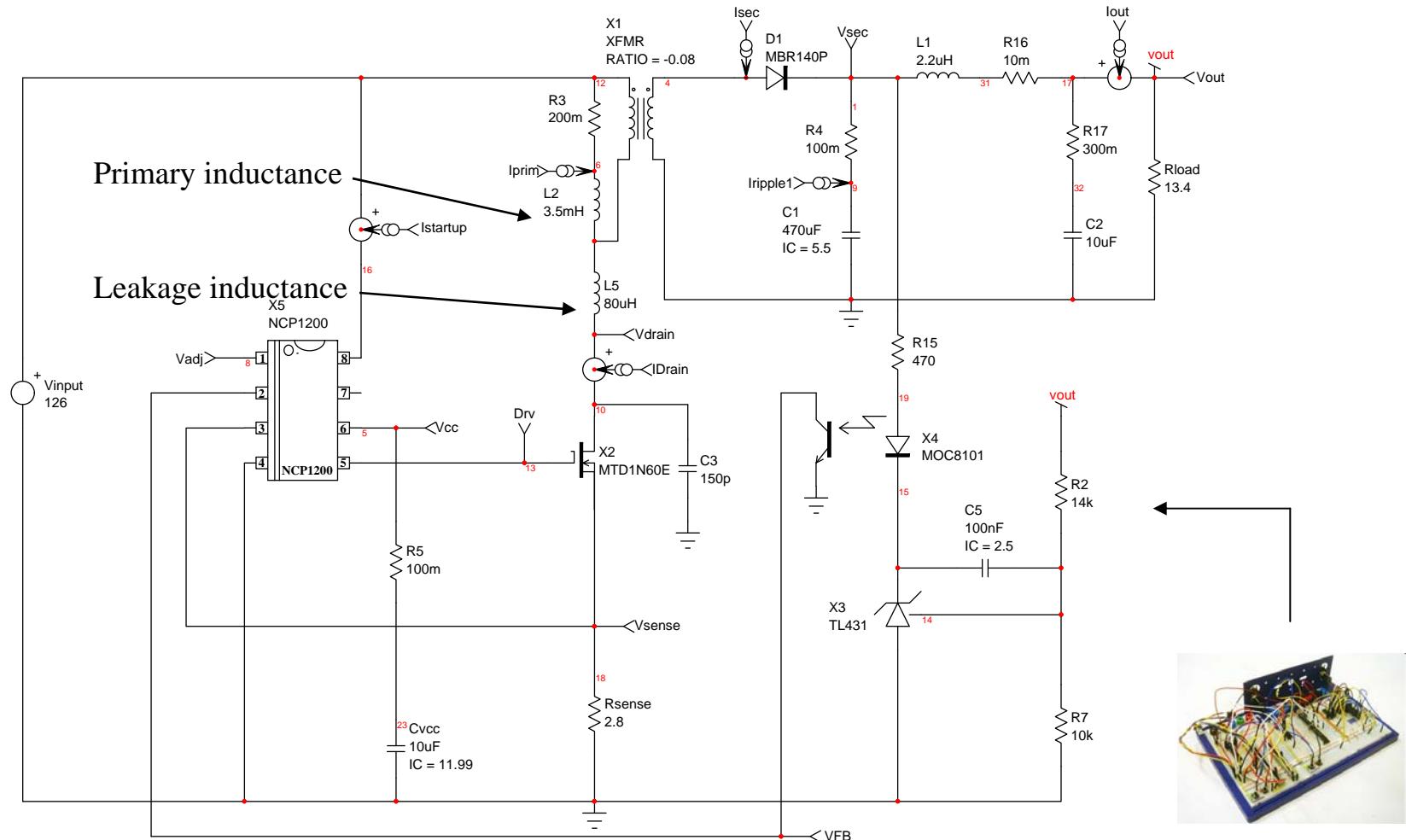- Wire your device as you would do in the lab.




Simulations (Really) Work!

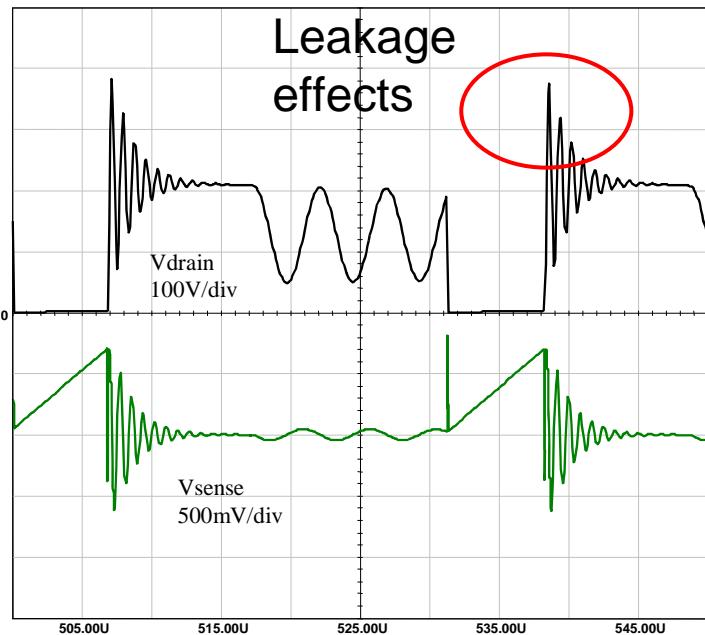- ❑ Assess the average, rms currents in your circuit
- ❑ Check if enough margins exist on your semiconductors



simulated


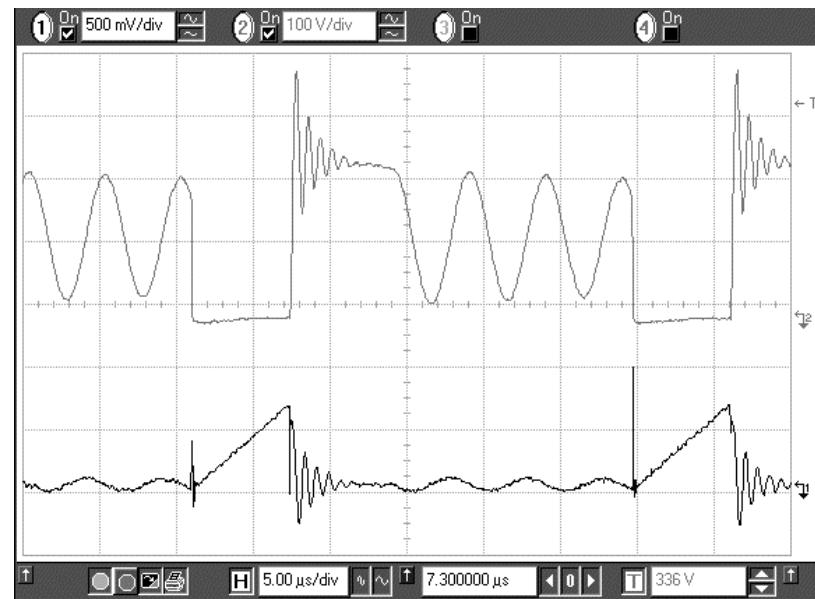


measured



Simulations (Really) Work!!

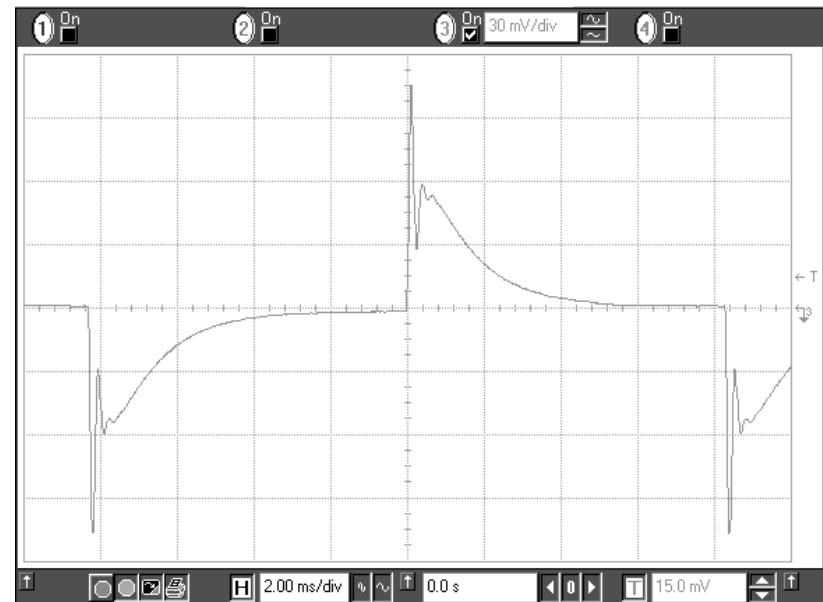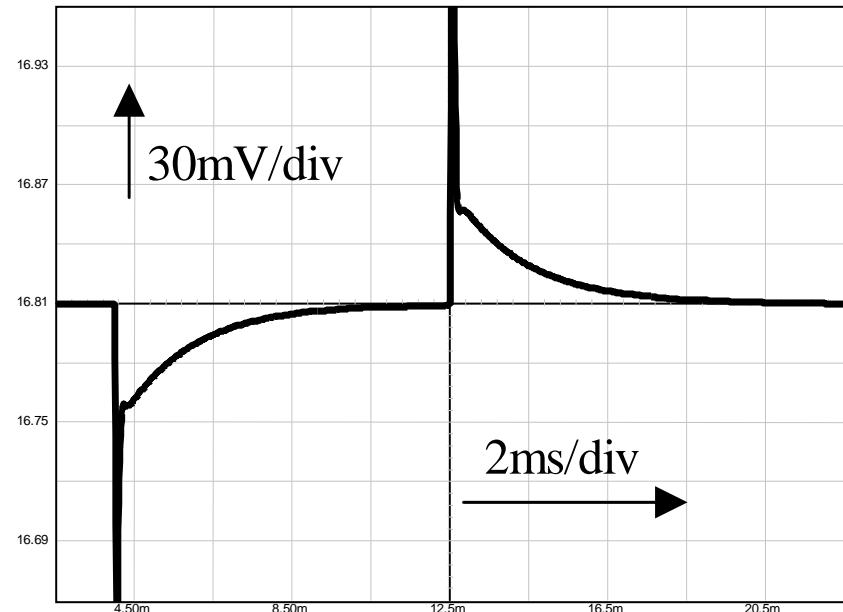- With accurate models, the simulation results are excellent
- You can then vary the parasitic terms and see their impact



simulated




measured

Agenda

- Why simulating power supplies?
- Average modeling techniques
- The PWM switch concept, CCM
- The PWM switch concept, DCM
- The voltage-mode model at work
- Current-mode modeling
- The current-mode model at work
- Power factor correction
- Switching models
- **EMI filtering**
- Conclusion


EMI Filtering on a DC-DC

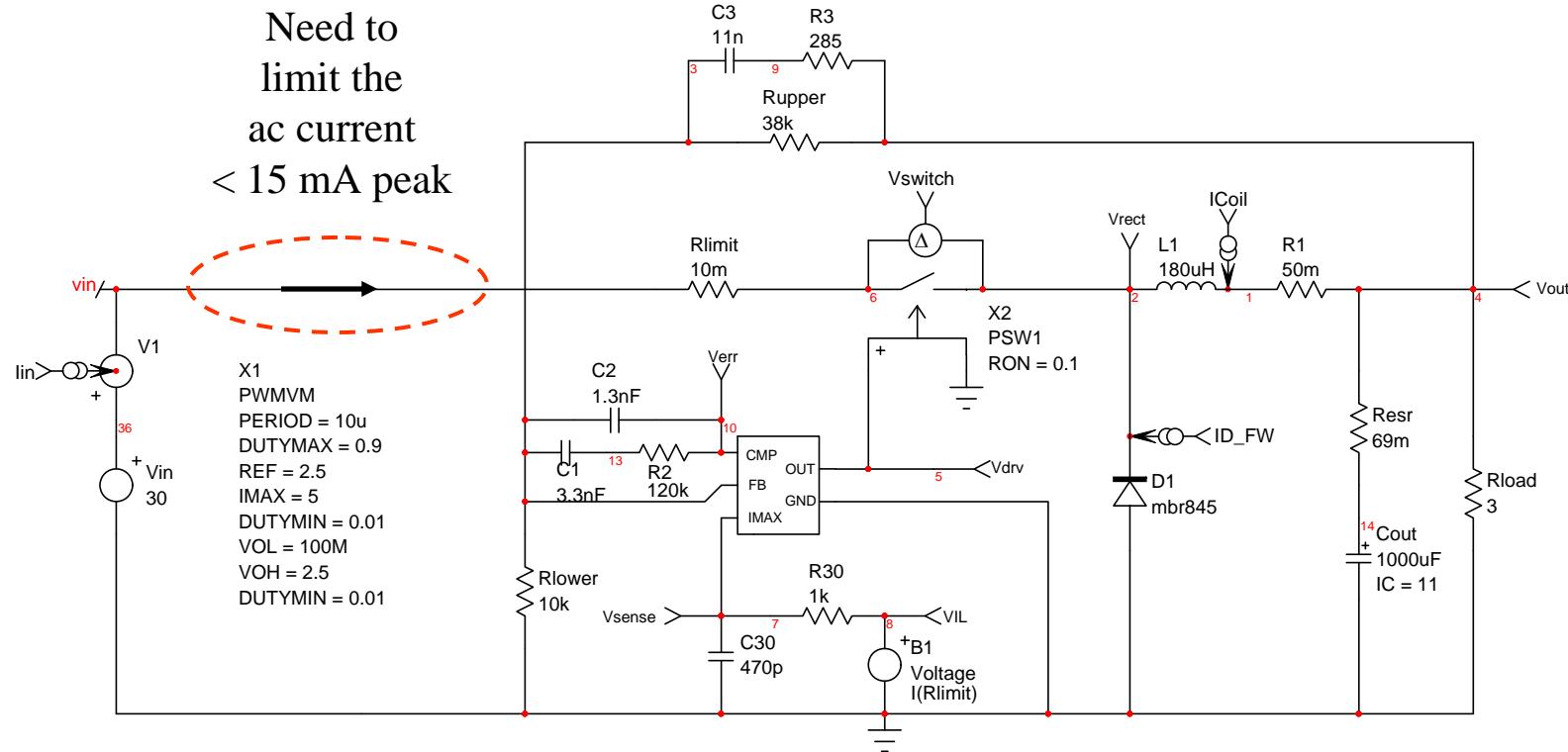- DC-DC are highly EMI polluting systems
- A filter has to be installed to avoid noise in the source



EMI Filtering on a DC-DC

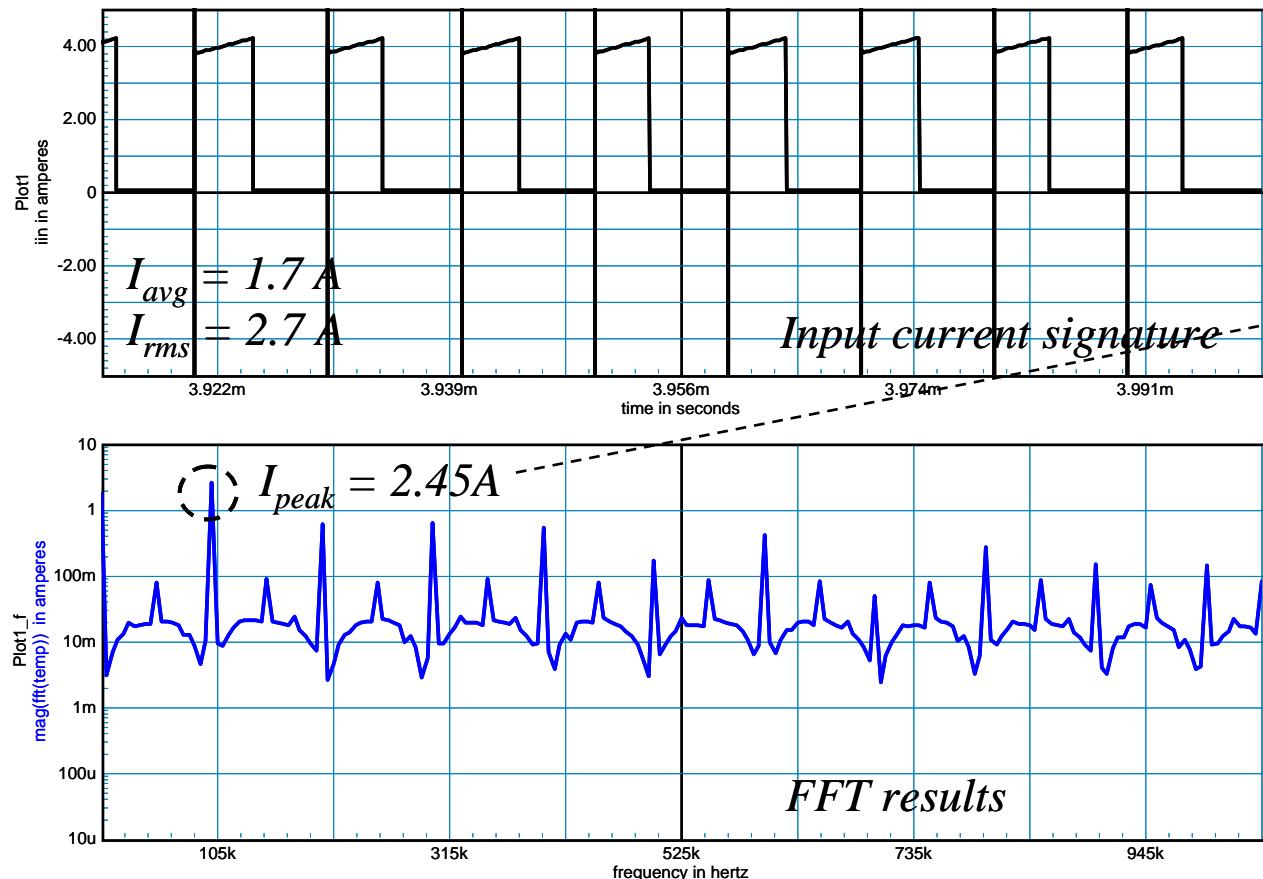- Use SPICE to extract the current signature
- Run Fourier analysis to look at the spectrum




$$\begin{aligned}
 I_{ripple} &< 15 \text{ mA} \\
 \downarrow \text{attenuation} \\
 A_{filter} &< \frac{15}{2.45} < 6 \text{ m} \\
 \downarrow \\
 f_0 &< \sqrt{0.006 \times F_{sw}} < 7.7 \text{ kHz}
 \end{aligned}$$

Position the cutoff frequency of the *LC* filter

EMI Filtering on a DC-DC

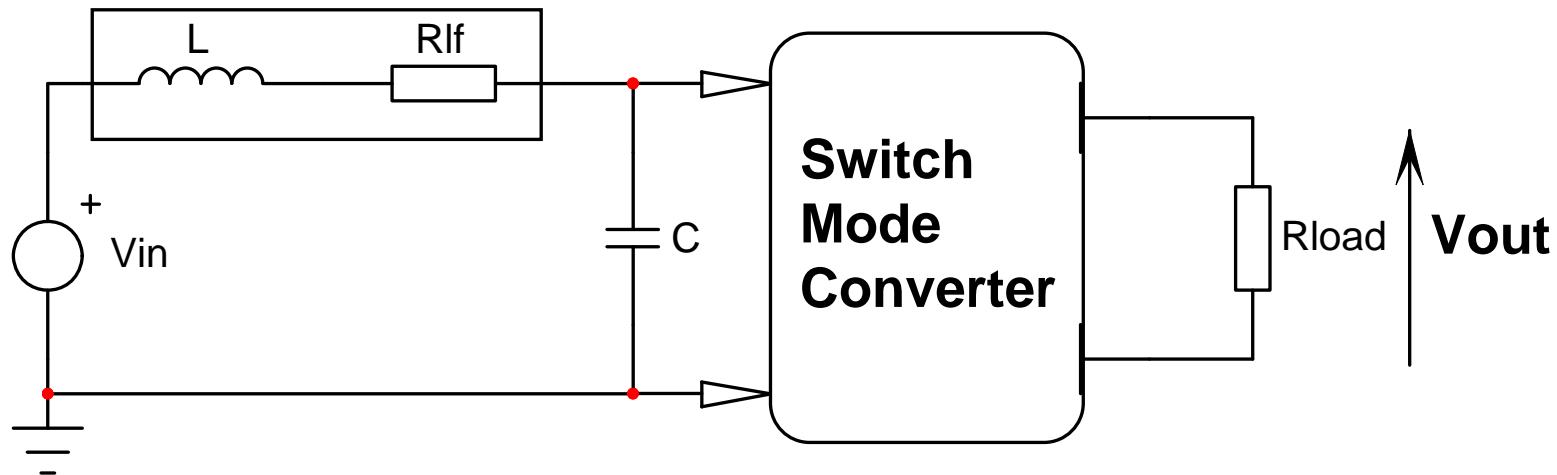- A *LC* configuration offers the best efficiency
- As any *LC* network, it is subject to resonances



$$L = 100 \mu H$$

$$C = \frac{1}{4\pi^2 f_0^2 L} = 5.2 \mu F$$


↑
7.7 kHz

Check
impedance
peaking

$$\|Z_{outFILTER}\|_{max} = \frac{Z_0^2}{R_1} \sqrt{1 + \left(\frac{R_1}{Z_0}\right)^2}$$


EMI Filtering on a DC-DC

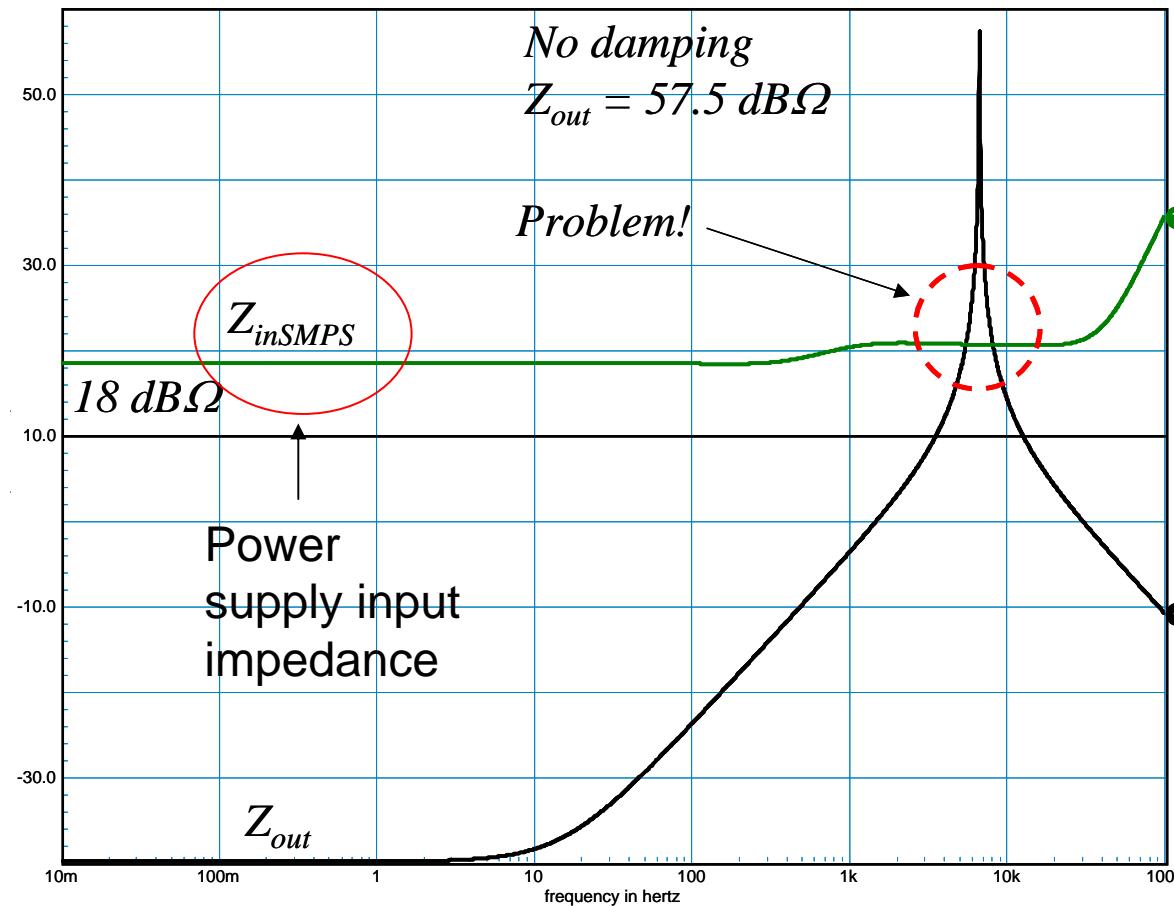- The incremental input resistance of a DC-DC in negative
- A LC filter loaded by a negative resistance can oscillate!




EMI Filtering on a DC-DC

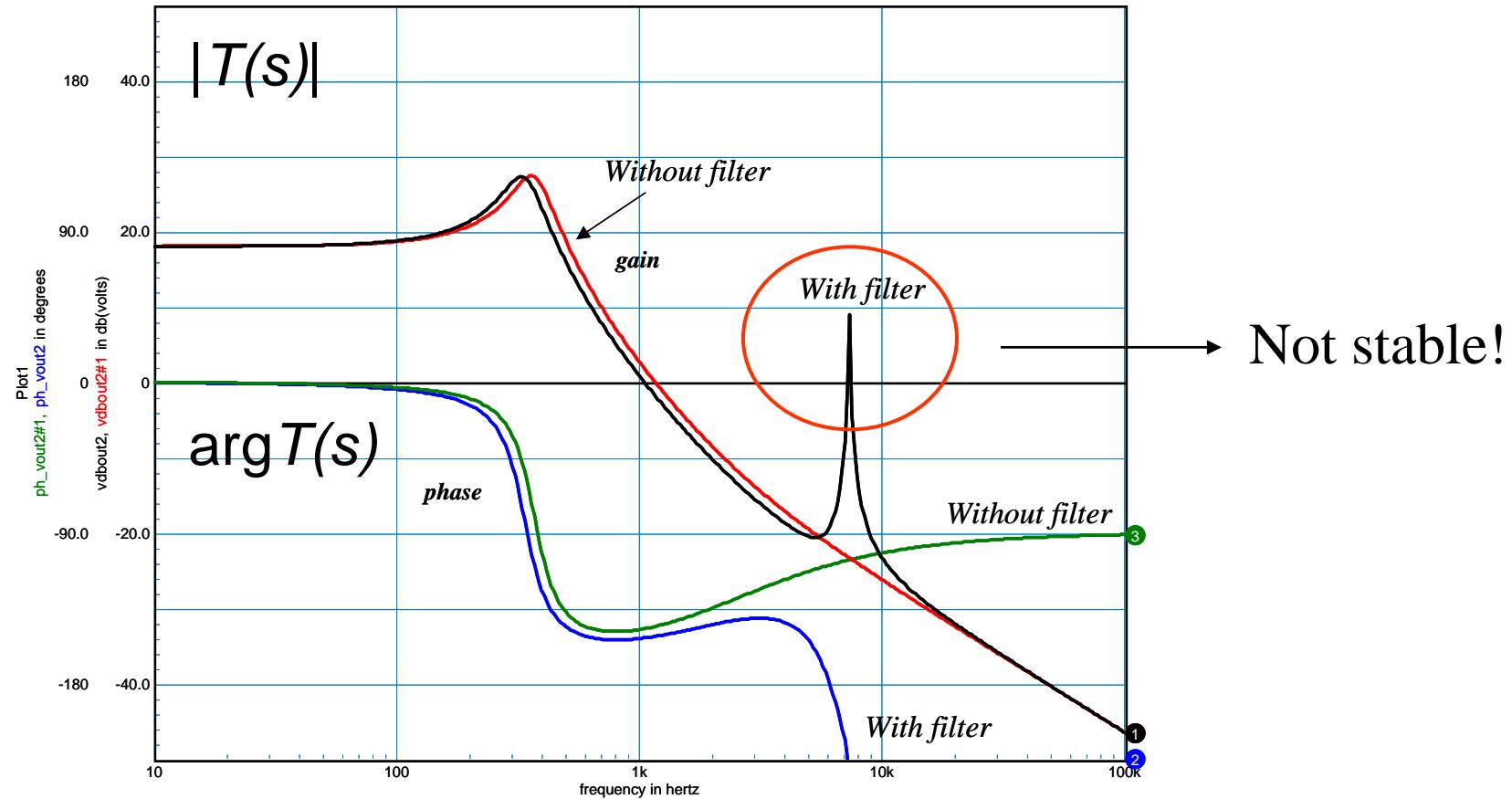- If the resonance is too peaky, problems can arise



EMI Filtering on a DC-DC

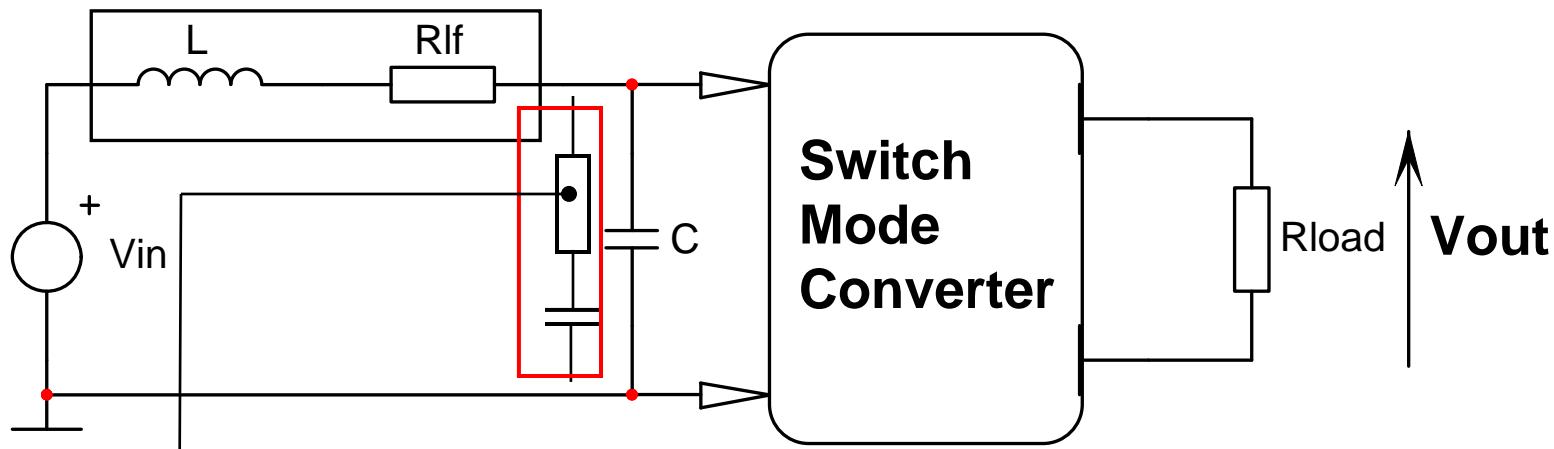
- A resistor is damping the LC filter by creating losses
- A dc-block capacitor is installed to limit dissipation



$$R_{damp} = -Z_{inSMPS} \frac{L + CR_1 R_2 - \frac{R_1}{\omega_0}}{2Z_{inSMPS} CR_1 - \frac{Z_{inSMPS}}{\omega_0} + L + CR_2 R_1 - \frac{R_1}{\omega_0}}$$


EMI Filtering on a DC-DC

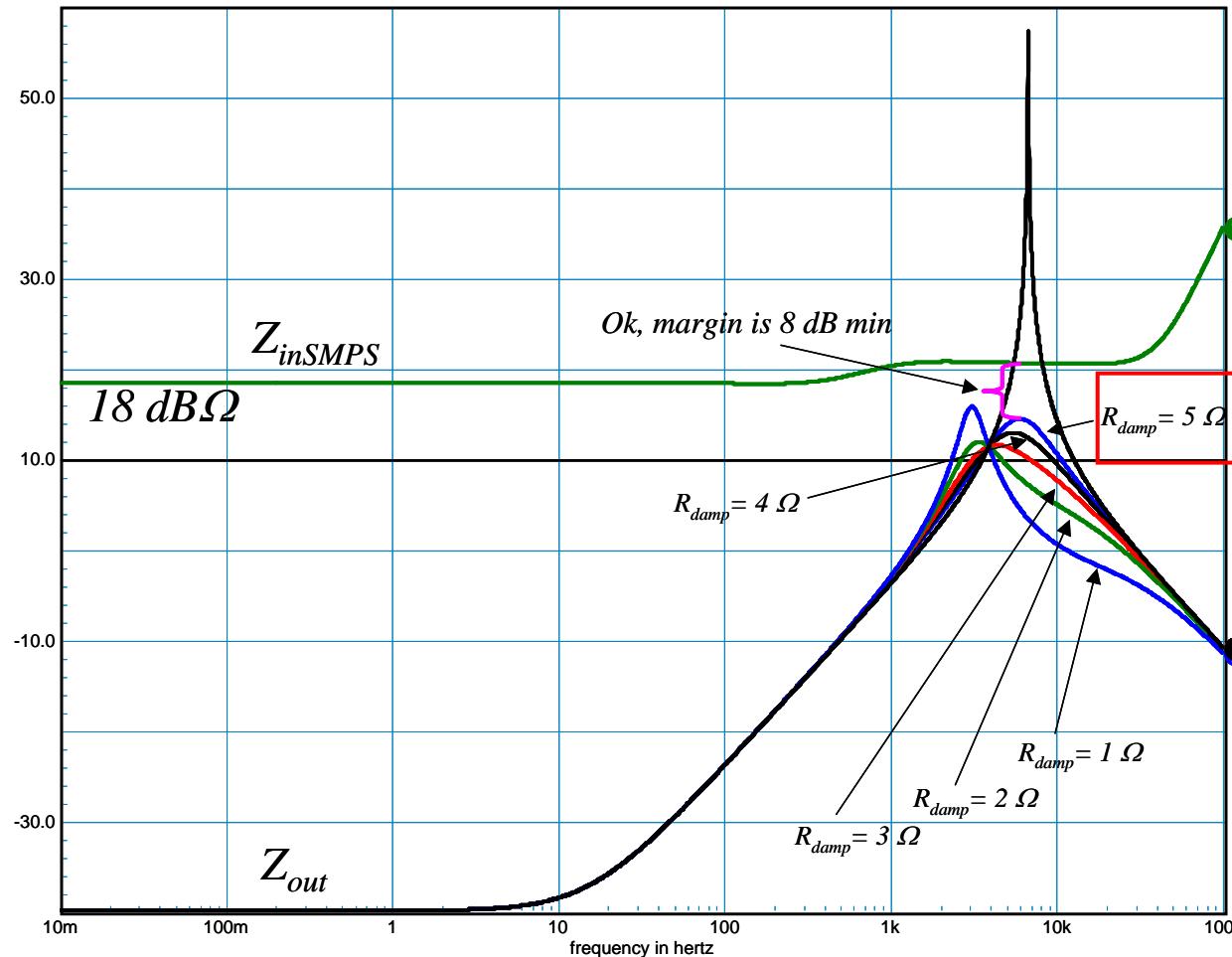- The right resistor prevents the overlaps between curves



EMI Filtering on a DC-DC

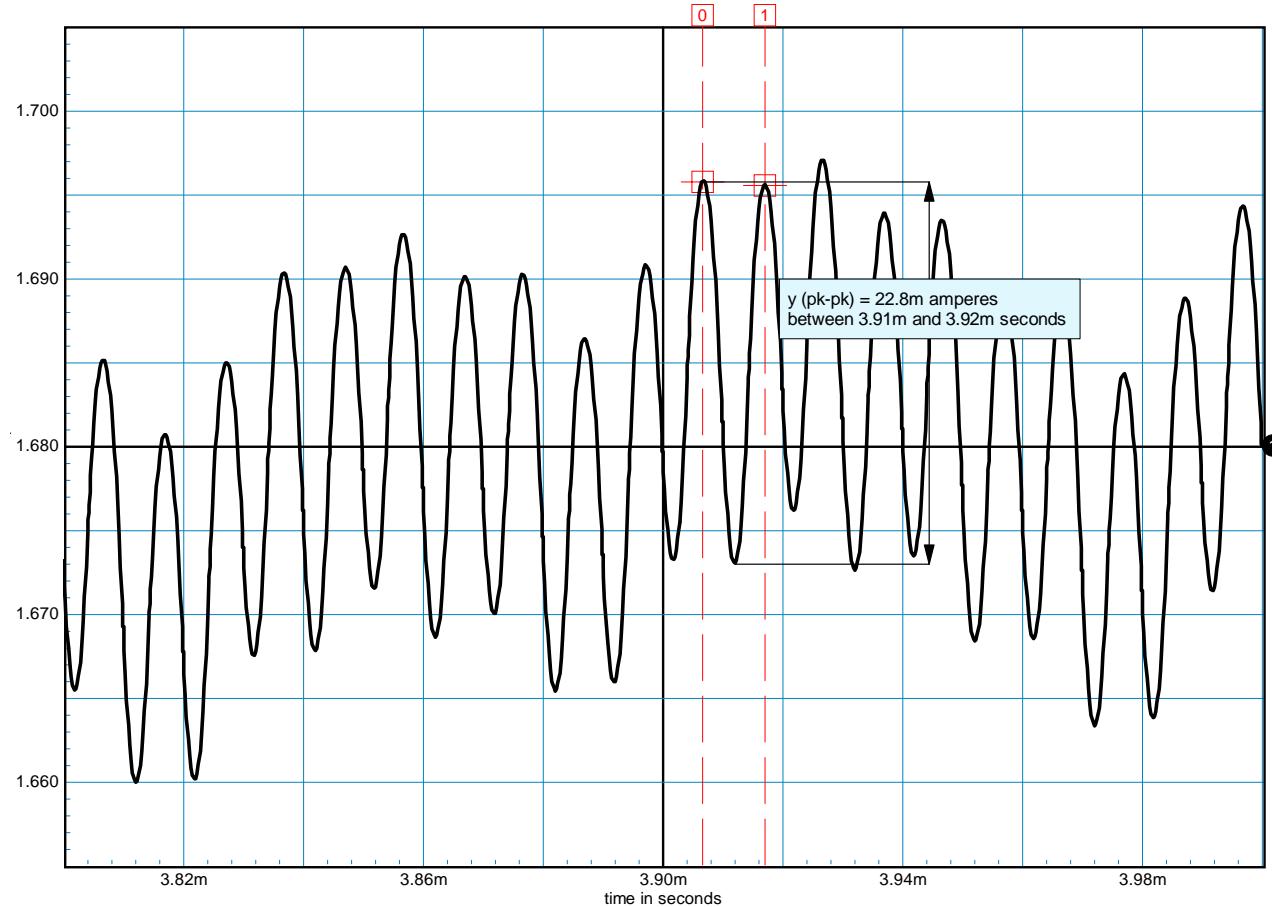
- A final check shows a noise amplitude under control



A Book on Power Supply Design

- To learn more about power supplies and simulations...

886 pages, 8 chapters

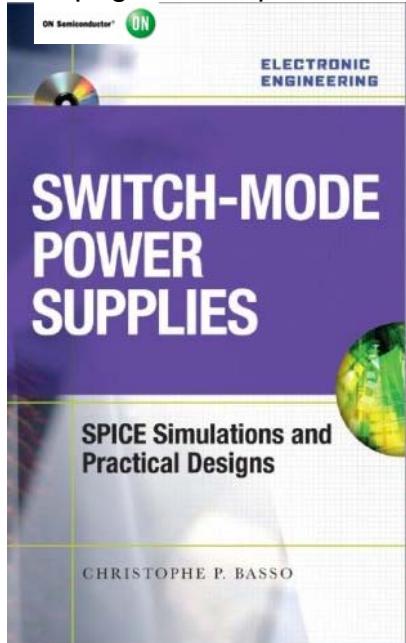

- Learn DC-DC converters theory
- Understand average modeling
- Feedback and loop control
- Design examples of DC-DC and AC-DC
- Power Factor Correction
- Chapters on flyback and forward converters
- Supplied CDROM with working examples

I already
have ideas
for the next
edition!!



Conclusion

- SPICE can be seen as a design companion
- It shields us from going through complex equations
- Simulation time is short and PC helps to run tests
- Use SPICE before going to the bench: NO trial and error!
- Once the simulation is stable, build the prototype
- Simulations and laboratory debug: the success recipe!

For More Information

- View the extensive portfolio of power management products from ON Semiconductor at www.onsemi.com
- View reference designs, design notes, and other material supporting the design of highly efficient power supplies at www.onsemi.com/powersupplies

