

# Enabling Zero Volt Drive Capability for EliteSiC

## AND90255/D

### Abstract

Silicon carbide (SiC) devices have become popular for power electronics world applications due to the increasing demand for efficiency driven by mobility electrification and renewable energy. These applications require power semiconductors capable of operating at higher frequencies with minimized losses. Compared to Silicon-based technologies such as IGBT or Super-Junction, SiC MOSFET offers remarkable advantages such as lower specific drain-source on resistance ( $R_{DS(on)}$ ) per area, higher breakdown voltages, reduced switching losses, optimized reverse recovery body diodes, and lower gate charges. The relationship between the threshold voltage ( $V_{th}$ ) and specific  $R_{DS(on)}$  per area ( $R_{sp}$ ) is particularly significant for planar MOSFET structures: this relationship imposes practical limitations on achieving the desired high value of  $V_{th}$  to ensure competitive  $R_{DS(on)}$ . The relatively low  $V_{th}$  is often seen as a potential risk for parasitic gate turn-on and subsequent punch-through damage, especially considering the extremely low capacitances achieved through the latest SiC MOSFET planar technology. To address this risk, SiC planar manufacturers often recommend utilizing negative turn off driving techniques. This application note examines the implications of driving onsemi SiC MOSFETs with a unipolar gate voltage (0 V/+18 V). The study investigates the relationship between device parameters such as capacitances and threshold voltage and the occurrence of parasitic turn on through simulations and experimental test setups. The objective is to address system concerns and establish safe operating conditions for this type of operation.

### Introduction

SiC devices have many benefits over their silicon counterparts, namely lower  $R_{DS(on)}$ , device capacitances, and reverse recovery charge. Lower device capacitances give rise to higher  $dV/dt$  values. However, high  $dV/dt$  can cause unwanted turn on of SiC MOSFET devices within bridge topologies [1]–[6], such as the half bridge leg shown in Figure 1. When one device turns on, the  $dV/dt$  imposed on the complimentary device causes the Miller capacitance to discharge into the gate which may cause a false turn on if the induced voltage on the gate is higher than the threshold voltage of the MOSFET. The severity of the parasitic turn on depends mainly on Miller capacitance  $C_{gd}$ ,  $C_{gs}/C_{gd}$  ratio, drain voltage slew rate  $dV_{ds}/dt$  and total gate resistance as shown in equation 1.

$$V_{gs} = R_g C_{gd} \frac{dV_{ds}}{dt} \left( 1 - e^{-\frac{t}{R_g(C_{gd} + C_{gs})}} \right) \quad (\text{eq. 1})$$

Where  $R_g$  is the total gate loop resistance, capacitance  $C_{gd}$  and  $C_{gs}$  are the device internal capacitances, and  $dV_{ds}/dt$  is the slew rate of the drain-to-source voltage.

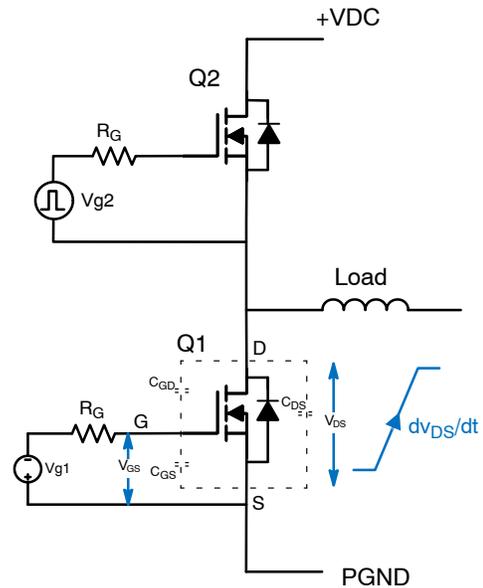


Figure 1. Half-Bridge Configuration

Basically, the high transition rate ( $dV_{ds}/dt$ ) of drain to source voltage induces a current in the device capacitance  $C_{gd}$  which elevates the gate to source voltage ( $V_{gs}$ ) of the device. As can be seen from equation 2,  $i_{C_{gd}}$  current depends on  $C_{gd}$  value and  $dV/dt$  value. Since  $C_{gd}$  is a device parameter (which cannot be reduced externally),  $dV/dt$  is the only variable in this equation can be controlled.

$$i_{C_{gd}} = C_{gd} \frac{dV_{C_{gd}}}{dt} \quad (\text{eq. 2})$$

Parasitic turn on can be also caused by large parasitic printed circuit board (PCB) inductances of the gate loop and the main power loop which may cause significant oscillation in the device's gate to source voltage and drain-to source voltage ( $V_{ds}$ ). Figure 2 shows the equivalent circuit of the MOSFET for switching behavior analysis.  $V_{driver}$  represents the gate driver,  $R_{g\_ext}$  is the external gate resistor,  $R_{g\_int}$  is the internal gate resistor of the device,  $C_{gd}$ ,  $C_{gs}$  and  $C_{ds}$  are the device parasitic capacitances and  $L_S$  is the total

source parasitic inductance of the device and the PCB. Supply voltage of the gate driver and  $R_{g\_ext}$  are the main parameters that can be tuned to overcome parasitic turn on issues.

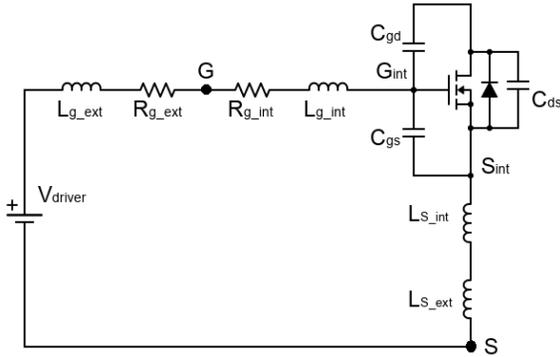


Figure 2. MOSFET Switching Equivalent Circuit

On the other hand, internal source inductance ( $L_{S\_int}$ ) and external source inductance ( $L_{S\_ext}$ ) can also affect the gate source voltage behavior, especially in 3-pin devices. 3-pin devices share the source pin for the main drain current and the gate driver current [3], [4]. Since the source pin of the device might be exposed to high di/dt values, an induced voltage can be observed on the source pin and gate-source voltage. Equation 3 gives the formula for the induced voltage caused by di/dt.

$$V_{L_S} = L_S \times \frac{di_{L_S}}{dt} \quad (\text{eq. 3})$$

As can be seen from equation 3, di/dt and source inductance affect the induced voltage. Thus, the lower  $L_S$  ( $L_{S\_int} + L_{S\_ext}$ ), the lower  $V_{L_S}$ . Note that when drain current is decreasing (as during turn off),  $V_{L_S}$  has a negative polarity which increases the net gate-source voltage applied by  $V_{driver}$ , tending to keep the device on.  $L_S$  consists of two stray inductances:  $L_{S\_int}$  and  $L_{S\_ext}$ . The use of a device package with a Kelvin source connection helps to deliver a more stable source signal of the device (Kelvin source) to the gate of the SiC MOSFET since it provides separated path for gate current and there is no voltage drop caused by rapid changes in drain current [5].

### Application (The Half Bridge Topology Simulation)

In this section simulation results produced using Simetrix [6], are given for the half bridge circuit with constant duty cycle around 50%. The  $V_{gs}$ ,  $V_{ds}$ ,  $V_{gs\_int}$ , channel current, and body diode current of both the high side and the low side MOSFETs are measured. Where,

- $V_{gs}$  is gate to source voltage of MOSFET measured from the pins of the device
- $V_{ds}$  is drain to source voltage of MOSFET measured from the pins of the device
- $V_{gs\_int}$  is internal gate to source voltage of MOSFET measured from the dies of the device
- *Channel current* is the current of the device that flows through device's channel, and it is measured from the die of the device
- *Body diode current* is the die current that flows through body diode of the device
- *High Side MOSFET* is the MOSFET that its source pin is connected to drain of other MOSFET
- *Low Side MOSFET* is the MOSFET that its source pin is connected to ground.

Simulated waveforms are taken from Simetrix for various gate resistor values. The test conditions for the half bridge topology are set as follows:

- $V_{in} = 800 \text{ V}$
- $R_g = 4.7 \Omega - 25 \Omega$
- $V_{gs\_on} = +18 \text{ V}$
- $V_{gs\_off} = 0 \text{ V}, -3 \text{ V}$
- Load current = 20 A – 40 A
- Duty Cycle = 48.7%
- Frequency = 100 kHz

Figure 3 shows the Simetrix schematic representation of circuit with  $4.7 \Omega$  on and off gate resistors. The NVBG040N120M3S from **onsemi's** EliteSiC M3S portfolio is used as switching device for simulations. NVBG040N120M3S is 1200 V device with  $40 \text{ m}\Omega$   $R_{DS(on)}$  value [7].

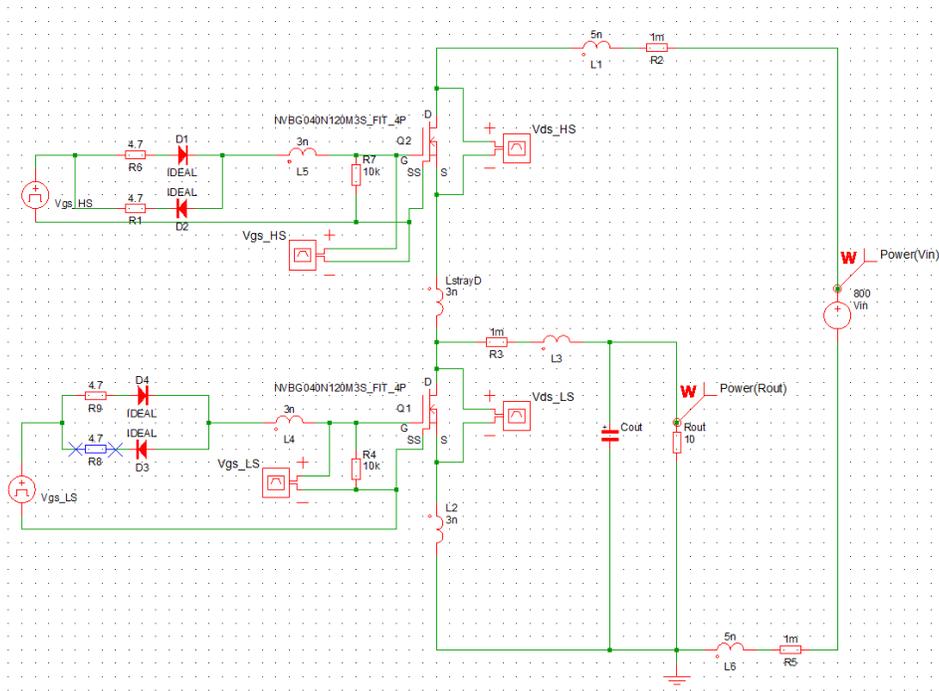


Figure 3. Simetrix Schematic of the Half Bridge Converter

During drain to source voltage  $V_{ds}$  transitions, there is a possibility of parasitic turn on of the switching device due to high  $dV_{ds}/dt$ . Figure 4 illustrates the impact of parasitic

turn on of the low side MOSFET when it should remain off. This simulation result was obtained using 4.7  $\Omega$  on and off gate resistors as in the schematic shown in Figure 3.

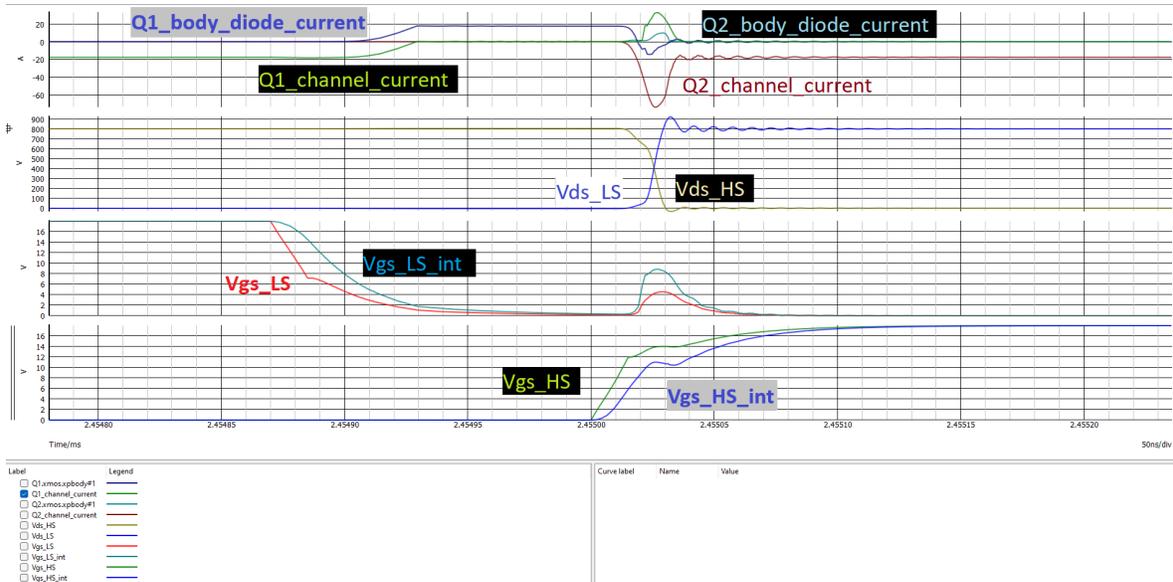


Figure 4. Parasitic Turn-On Issue of Low Side MOSFET on the Half-Bridge Converter

It can be seen from Figure 4 that  $V_{gs}$  of the low side MOSFET increases when  $V_{ds}$  of low side switching device starts ramping up. This is because the fast rate  $dV_{ds}/dt$  induces a current through  $C_{gd}$  according to equation 2. The flowing current passes through both  $C_{gd}$  and  $C_{gs}$ , creating a voltage divider effect between  $C_{gd}$  and  $C_{gs}$ , and causes gate voltage rise. Therefore, it's essential to take into account the


$C_{gs}/C_{gd}$  ratio for parasitic turn on (PTO) considerations in addition to  $dV_{ds}/dt$ ,  $R_{g\_int}$  and  $R_{g\_ext}$ . This unwanted increase of  $V_{gs\_LS}$  due to  $i_{Cgd}$  current opens the channel of low side MOSFET to conduct current as seen from Figure 4. It needs to be pointed out that the  $V_{gs\_int}$  value of the low side MOSFET is higher than  $V_{gs}$  during the time  $V_{ds}$  is changing. This phenomenon can be explained as follows: The current

# AND90255/D

$i_{Cgd}$  leads to  $V_{gs}$  voltage increase and this increased  $V_{gs}$  discharges through internal and external gate resistors so that the external  $V_{gs}$  is lower than  $V_{gs\_int}$  during PTO.

On the other hand, when low side MOSFET is turning on and high side MOSFET is turning off, there is no such parasitic turn on issue because the gate will be pulled down to negative value due to negative  $dV_{ds}/dt$  (Figure 5). It is


important to ensure that this negative voltage does not exceed the recommended maximum voltage rating provided by the manufacturer, which is  $-8$  V for the present example. Exceeding this limit can result in increased stress on the oxide electric field, ultimately leading to a shortened lifespan of the device [8], [9].

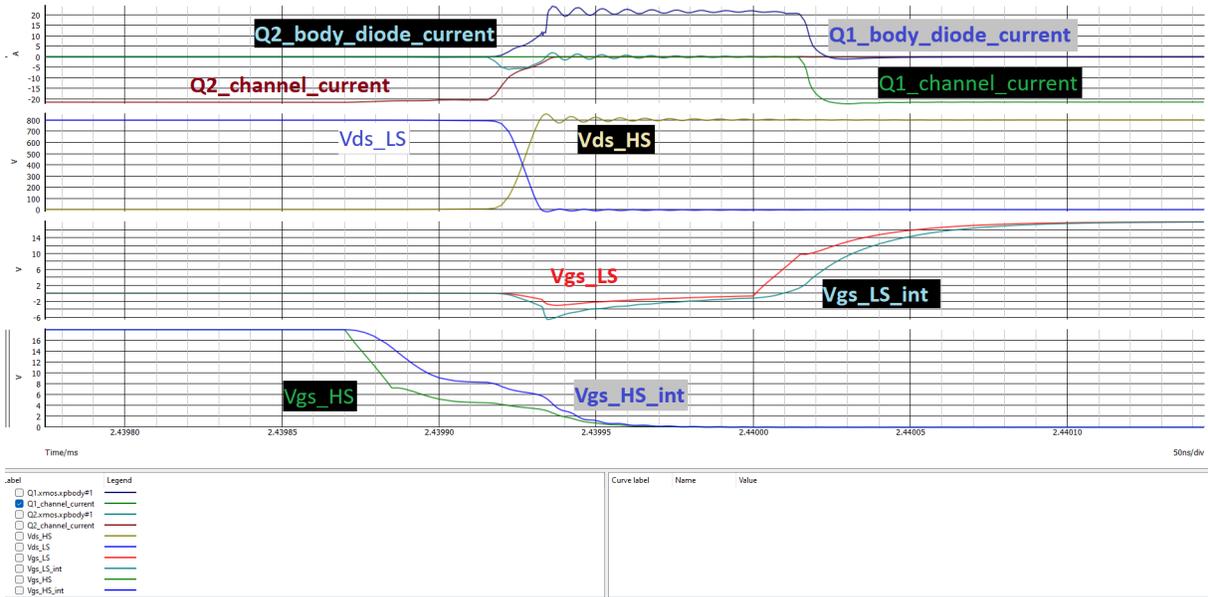

**Figure 5. High Side MOSFET Turning Off Transition of the Half-Bridge Converter**


Additionally, second illustration is also provided with  $25 \Omega$  gate resistor. The purpose of the larger  $R_{g\_ext}$  is to achieve a lower  $dV_{ds}/dt$  which, according to equation 1, results in lower  $i_{Cgd}$ . It is expected that the difference

between  $V_{gs\_int}$  and  $V_{gs}$  with  $25 \Omega$  gate resistor compared to  $4.7 \Omega$  gate resistor will be lower due to lower  $i_{Cgd}$ . Figure 6 and Figure 7 show the results for this condition for both switch transitions.

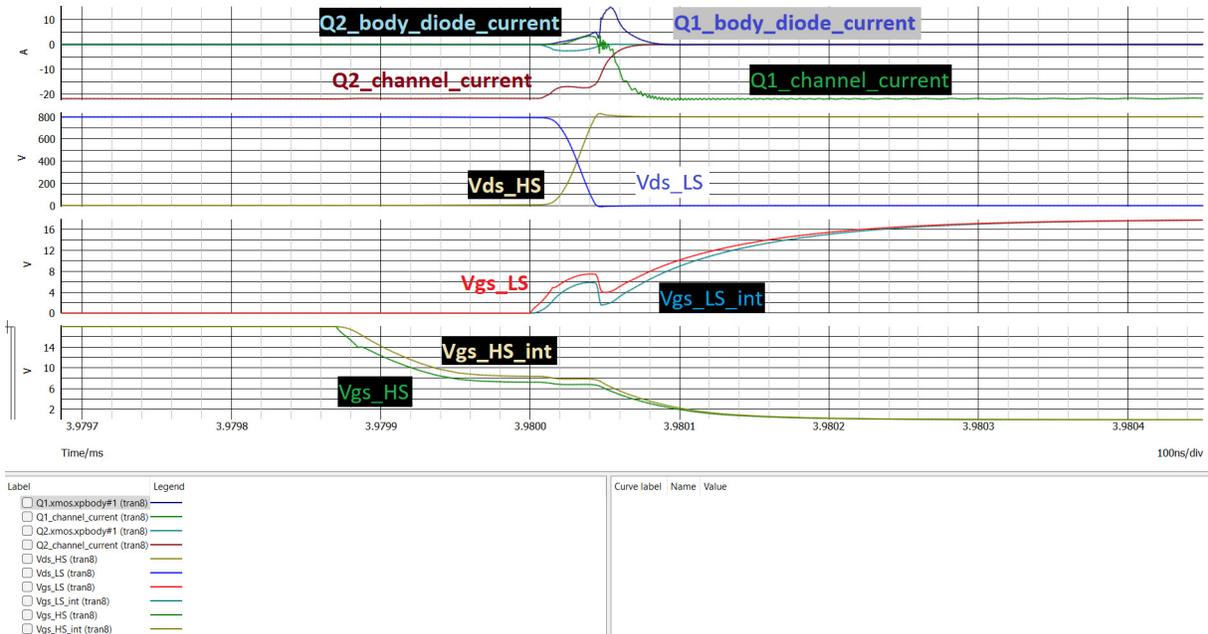

**Figure 6. Turning On of Low Side with  $25 \Omega$  Gate Resistor for the Half-Bridge Converter**

## AND90255/D

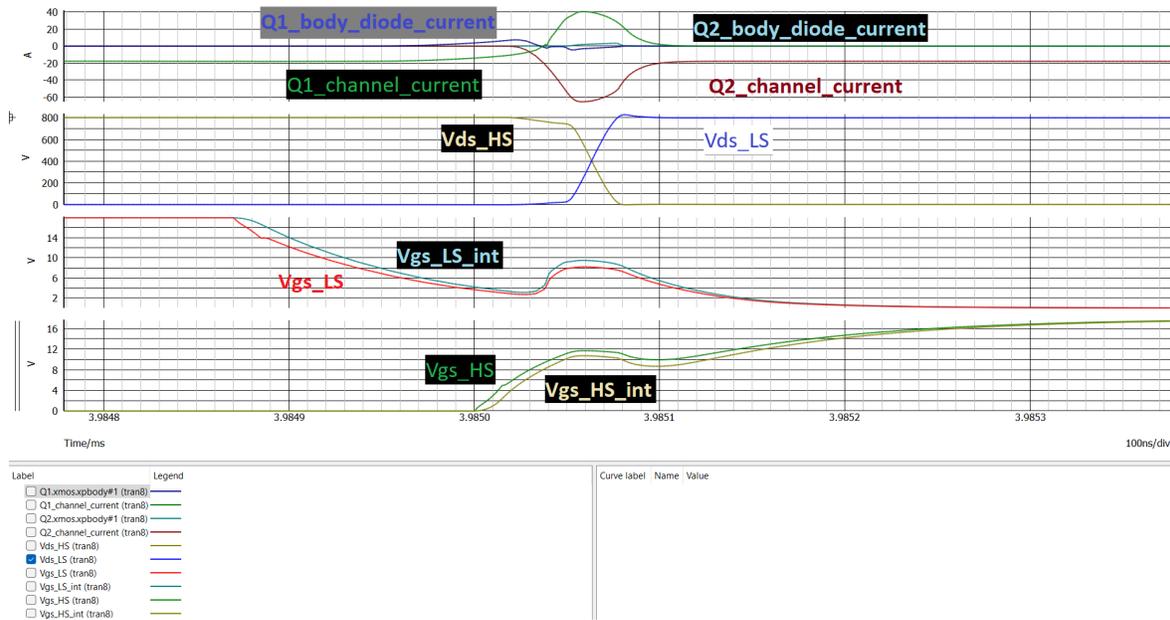

**Figure 7. Turning On of High Side with 25  $\Omega$  Gate Resistor for the Half-Bridge Converter**

According to the simulation results presented in Figure 4 and Figure 7, parasitic turn on happens with the 4.7  $\Omega$  and 25  $\Omega$  gate resistors cases but 25  $\Omega$  gate circuit has less channel current and less  $V_{gs\_int}$  of LS device peak voltage due to lower  $dV_{ds}/dt$ . It can be concluded that by choosing a suitably high gate resistor value parasitic turn on can be eliminated. However, since  $dV_{ds}/dt$  will be lower with higher gate resistor value, switching losses will be higher as a penalty. Reverse recovery current of the body diode of a related MOSFET leads to higher  $dV_{ds}/dt$  so reverse recovery current is another parameter that affects  $dV_{ds}/dt$  value of the switching device in addition to gate resistor value [10]. Thus, it needs to be pointed out that reverse recovery charge of body diode plays a crucial role on parasitic turn on phenomenon in addition to its importance for switching loss.

Table 1 is prepared by using two different gate resistors (4.7  $\Omega$  and 10  $\Omega$ ) and two different turn off driving voltage (0 V and -3 V) with different arrangements to show the effect of gate resistor and turn off driving voltage on efficiency of the system,  $dV_{ds}/dt$  and presence of parasitic turn on for the half bridge converter.

Based on the results shown in Figure 5, it is observed that in the case of soft switching, specifically zero voltage switching, there is an absence of parasitic turn on phenomenon. Soft switching occurs when the high side MOSFET turns off and the low side one turns on in the case of a half bridge converter that is shown in Figure 3. In this transition period, there is a flow of current through the body diode during the dead time and related SiC MOSFET turns on with body diode voltage drop, that is almost zero, on it.

**Table 1. EFFECT OF GATE RESISTOR VALUE ON EFFICIENCY, DVDS/DT AND PARASITIC TURN ON OF THE HALF BRIDGE CONVERTER**

Parameters					
Rg_off ( $\Omega$ )	Rg_on ( $\Omega$ )	Efficiency (%)	$dV_{ds}/dt$ of Low Side MOSFET's $V_{ds}$ Rising Edge (V/ns)	Parasitic Turn On	Turn Off Driving Voltage ( $V_{gs\_off}$ )
4.7	4.7	98.11	74.78	Present	0 V
4.7	4.7	98.3	77.24	Present	-3 V
4.7	10	98.03	60.52	Present	0 V
4.7	10	98.10	60.42	Present*	-3 V

\*Peak current value of PTO is smaller compared to 0 V turn off driving case with same Rg values.

### Experimental Verification

A simple experiment using double pulse circuit, Figure 8 is used to analyze the crosstalk phenomenon. In the experiment, it is assumed that one device is switching while the other device is held in the off state using  $V_{gs\_off}$  0 V or -3 V. For simplicity, to measure the switch current a 50 m $\Omega$

current shunt is used in series with the lower device. Therefore, to study the crosstalk effect on the upper device, we considered the lower device is switching on/off and the upper device (DUT) is held off. Since we do not have access to measure the internal channel current of the MOSFET to confirm the event of parasitic turn on, we can observe the



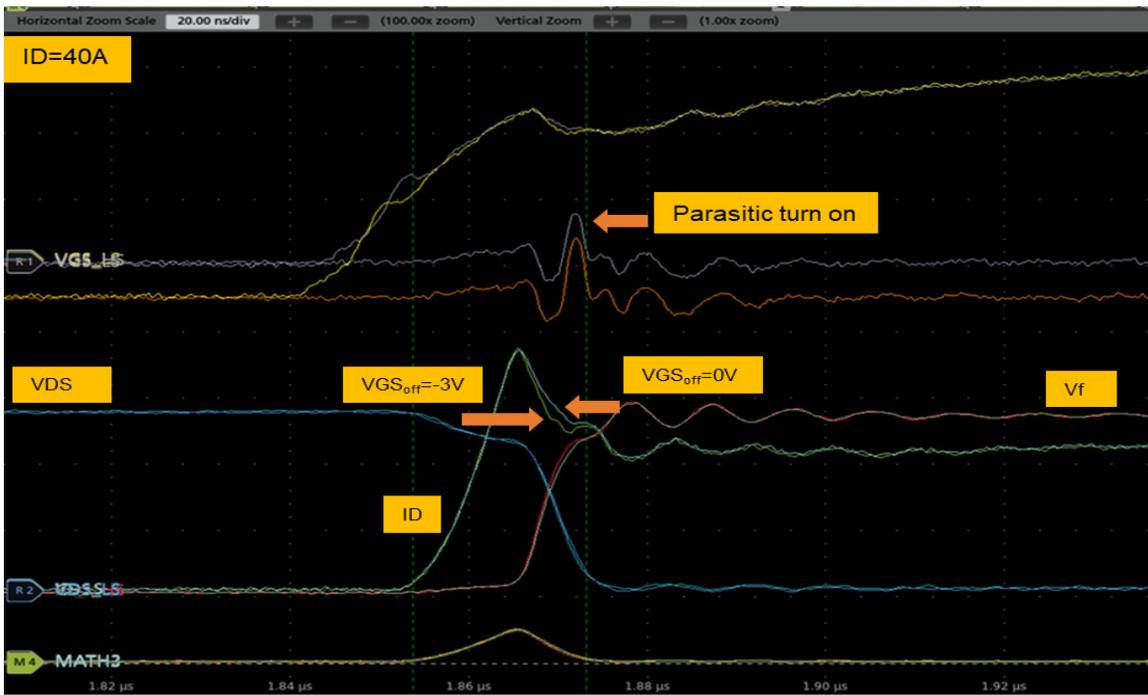


Figure 9. Switching Waveforms  $V_{gs\_off} = 0\text{ V}$  vs.  $-3\text{ V}$ ,  $I_D = 40\text{ A}$  (20 A/div),  $R_{g\_on/off} = 4.7/4.7\ \Omega$  (Both Devices). Active Clamp Function Enabled

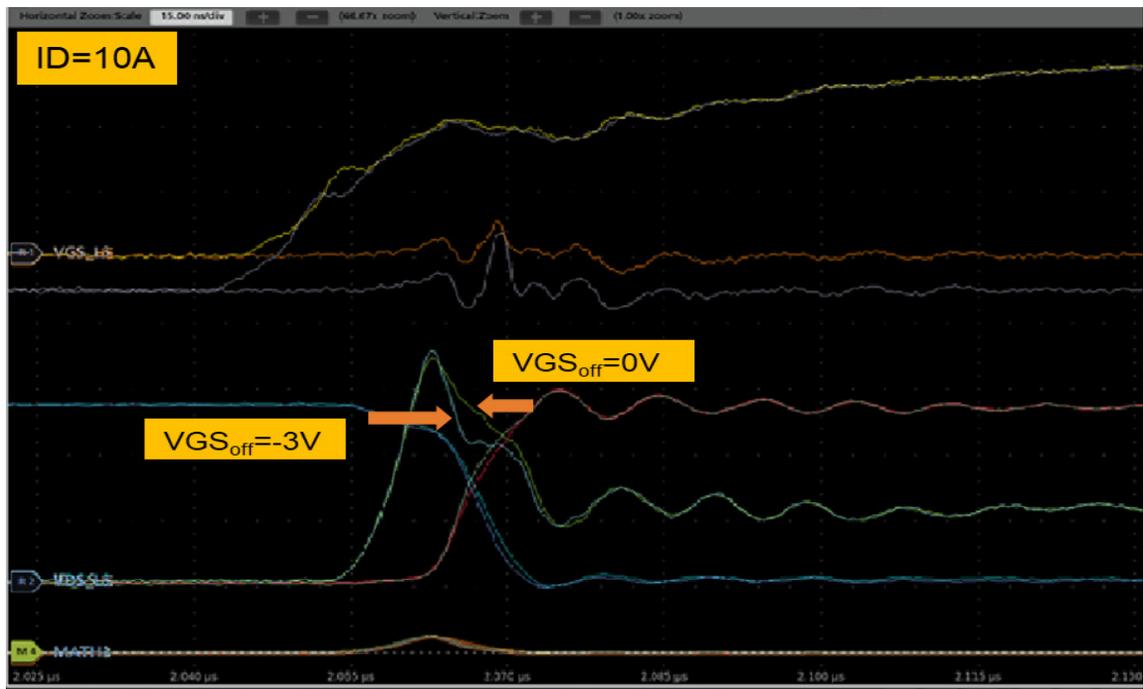


Figure 10. Switching Waveforms  $V_{gs\_off} = 0\text{ V}$  vs.  $-3\text{ V}$ ,  $I_D = 10\text{ A}$  (10 A/div),  $R_{g\_on/off} = 4.7/4.7\ \Omega$  (Both Devices). Active Clamp Function Enabled

# AND90255/D

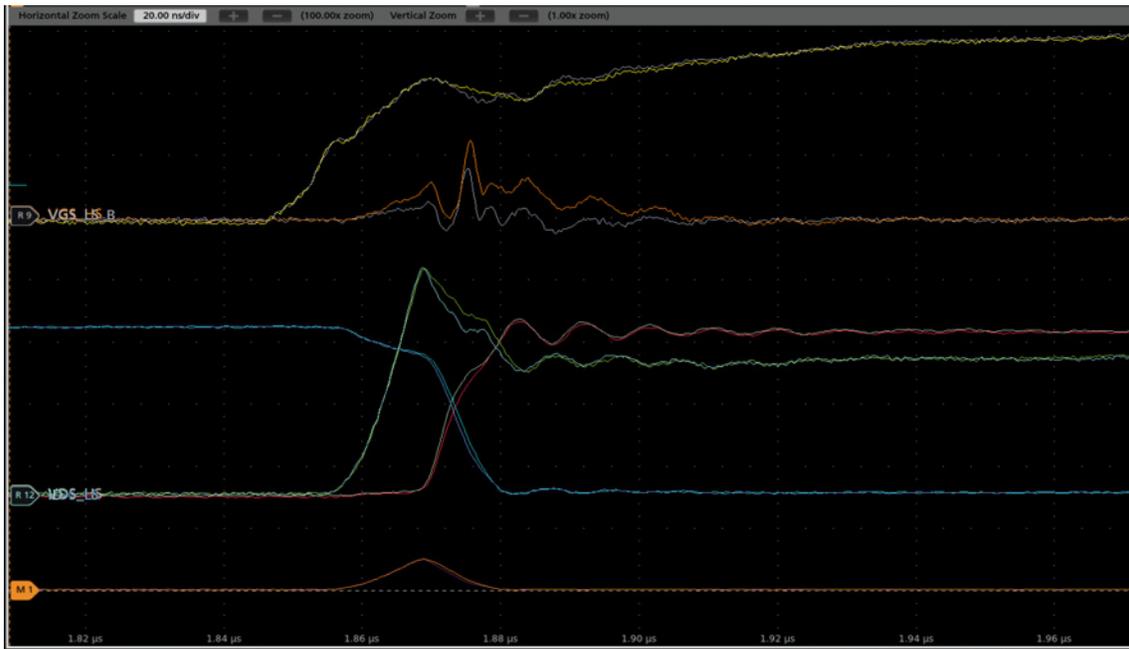


Figure 11. Switching Waveforms  $V_{gs\_off} = 0\text{ V}$ ,  $I_D = 40\text{ A}$ ,  $R_{g\_on/off} = 4.7/4.7\ \Omega$  (Both Devices), with and without Active Clamp


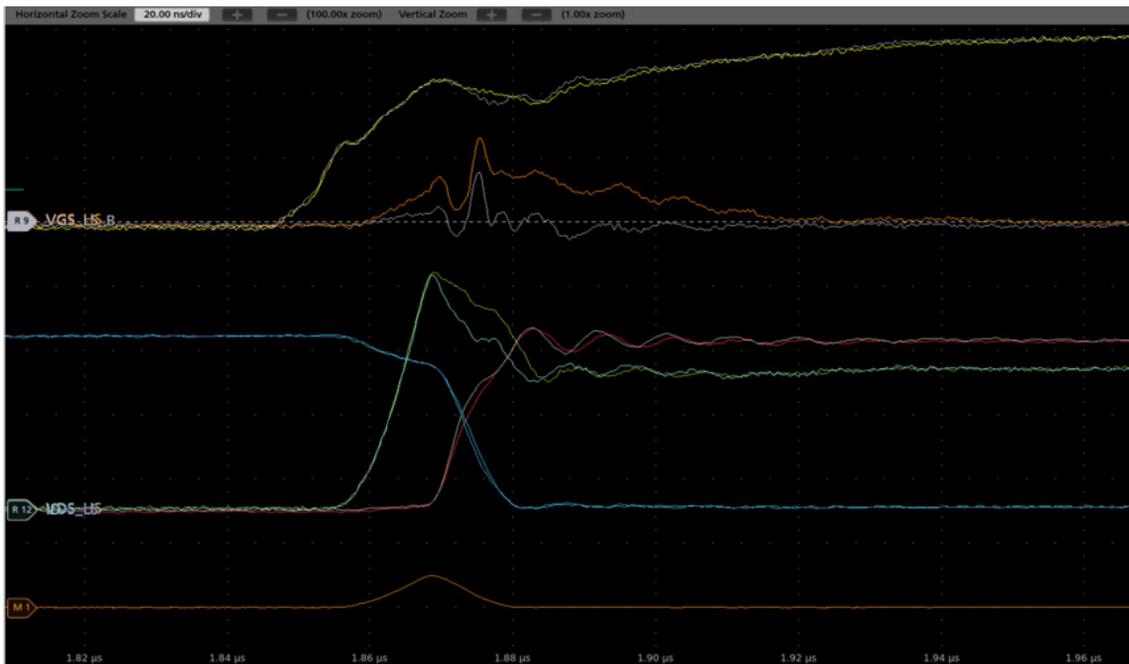


Figure 12. Switching Waveforms  $V_{gs\_off} = 0\text{ V}$ ,  $I_D = 40\text{ A}$ ,  $R_{g\_on/off} = 4.7/4.7\ \Omega$  (LS) and  $10\ \Omega$  (HS), with and without Active Clamp

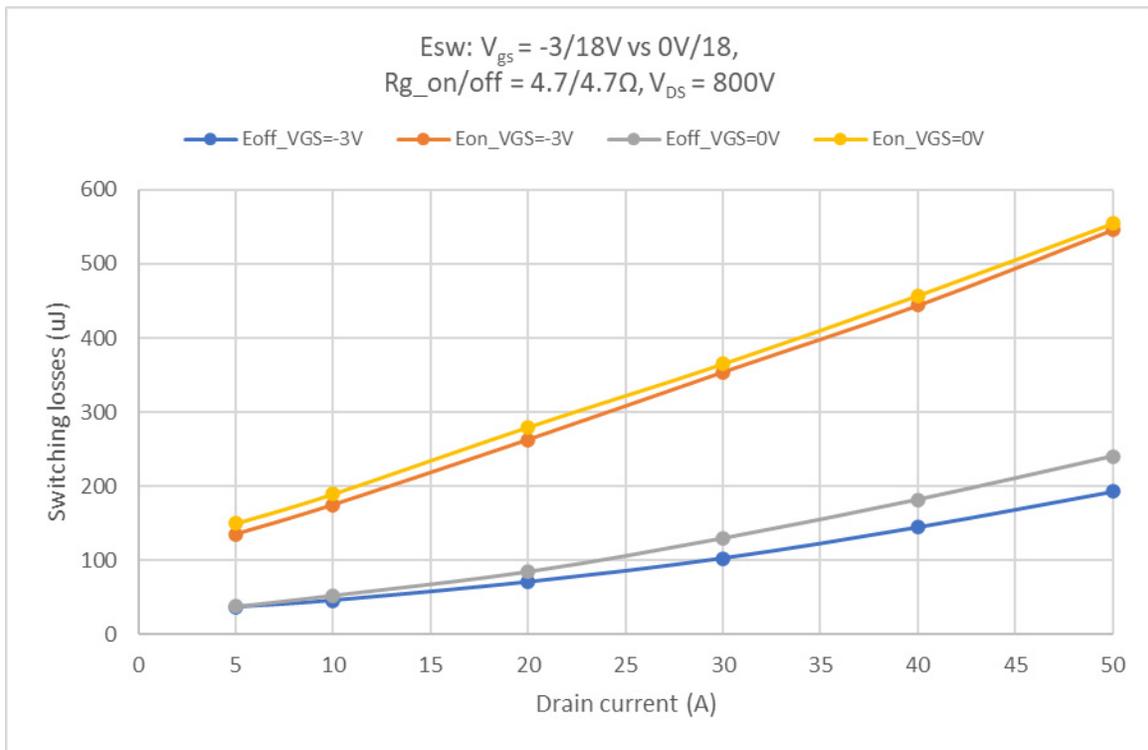

**Figure 13. Switching Losses Comparison  $V_{gs\_off} = 0$  V vs.  $-3$  V, with  $R_{g\_on/off} = 4.7/4.7 \Omega$ . With and without Active Clamp**

To mitigate the parasitic turn on, along with active clamp function, the turn on gate resistor can be tuned to reduce the  $dV_{ds}/dt$ . This concept is demonstrated in Figure 14–17 which is performed with active clamp enabled. With active clamp function enabled the turn off gate resistor can be reduced just enough to avoid larger negative stress on the gate voltage which might affects the gate reliability and Electromagnetic Interference (EMI) compliance. As it can be seen for  $R_{g\_on/off} = 10/4.7$  or  $R_{g\_on/off} = 10/2.35$  all

switching waveforms almost aligned even for low current and there is minimum loss increment when  $V_{gs} = 0/18$  V is used compared to  $-3/18$  V. Table 2 compares the switching speed of the device with  $V_{gs\_off} 0$  V versus  $-3$  V. It can be noted that for  $R_g = 4.7 \Omega$ , there is  $10 \mu J$  increase in Eon while Eoff increased by  $37 \mu J$ . The  $dV_{ds}/dt$  is slightly lower when  $V_{gs\_off} = 0$  V. When  $R_{g\_on}$  increases to  $10 \Omega$ , Eon increased by  $166 \mu J$  and  $dV_{ds}/dt$  drops to approximately  $85$  V/ns and no severe parasitic turn on is observed.

**Table 2. SWITCHING PARAMETERS FOR  $I_D = 40$  A**

$I_D$ (A)	$R_{g\_on}$ ( $\Omega$ )	$R_{g\_off}$ ( $\Omega$ )	$V_{gs\_off}$ (V)	$dv/dt$ Rising (V/ns)	$dv/dt$ Falling (V/ns)	$di/dt$ (A/ns)	Eon ( $\mu J$ )	Eoff ( $\mu J$ )
40	4.7	4.7	-3	129	103	7.137	444	146
40	4.7	4.7	0	120	95.74	7.133	456	182
40	10	4.7	-3	89.29	45.82	4.745	611	146
40	10	4.7	0	50	46	4.6	622	182

Without active clamp the turn on resistor must be larger than that with active clamp and vice versa for the turn off resistor which can be set to zero to avoid the PTO, but this will generate larger negative spike. Figure 17 show the result without active clamp. As it can be seen in Figure 17, if turn off gate resistor  $R_{g\_off} = 4.7 \Omega$ , the turn on resistor has to increase  $R_{g\_on} = 20 \Omega$  to avoid the PTO. However, with higher  $R_{g\_on}$  the switching losses will increase. Lower  $R_{g\_on}$

value can be selected if we reduce  $R_{g\_off}$  just enough to avoid PTO and reduce switching losses.

Finally, Figure 18 shows the switching losses with  $V_{gs} = 0/18$  V,  $R_{g\_off} = 2.35 \Omega$  and  $R_{g\_on} = 4.7 \Omega$  versus  $10 \Omega$ . In the range of 5–40 A, there is 10% average increase in Eon (Eon is 10% higher with  $10 \Omega$  compared to  $R_{g\_on} = 4.7 \Omega$  case). In typical OBC application ( $7.2$  kW –  $22$  kW), the current range is typically between

## AND90255/D

10–30 A. So, a 10% increase in Eon loss can be considered acceptable.  $R_{g\_off}$  can be reduced when  $V_{gs\_off} = 0\text{ V}$  in order to boost the efficiency of the converter but this may

cause higher common mode noise and as result failing to comply with EMI standard. Therefore, a tradeoff has to be made between efficiency and EMI.

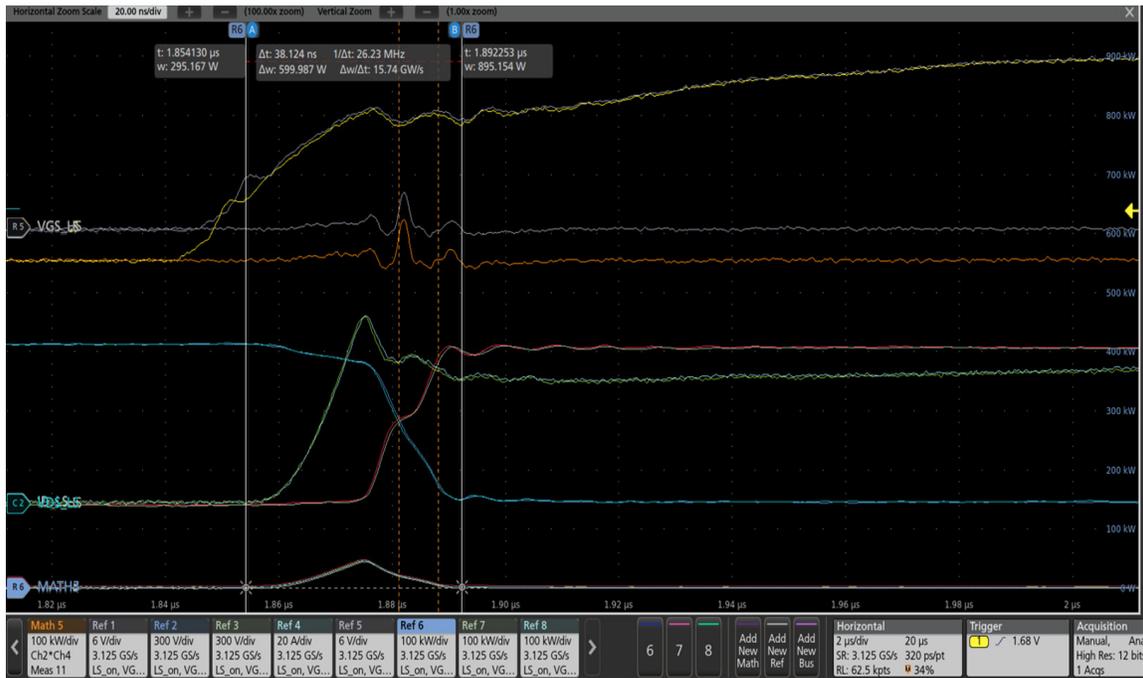


Figure 14. Switching Waveforms Comparison  $V_{gs\_off} = 0\text{ V}$  vs.  $-3\text{ V}$ ,  $I_D = 40\text{ A}$ ,  $R_{g\_on/off} = 4.7/4.7\ \Omega$ ,  $V_{ds} = 800\text{ V}$

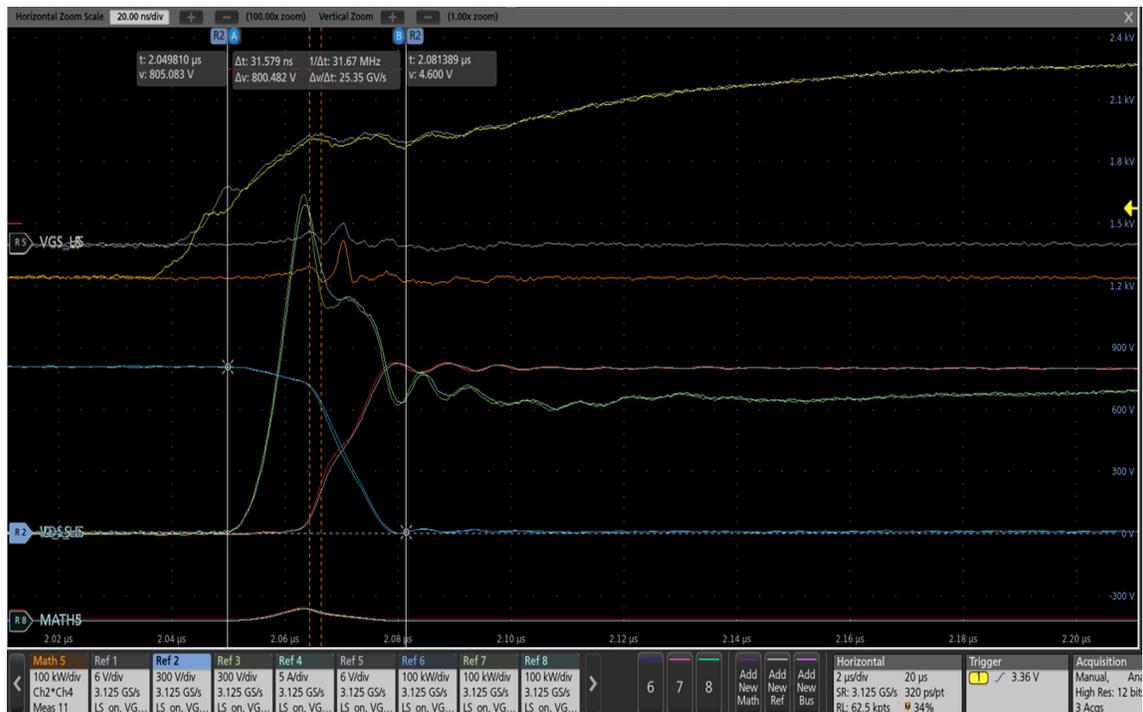


Figure 15. Switching Waveforms Comparison  $V_{gs\_off} = 0\text{ V}$  vs.  $-3\text{ V}$ ,  $I_D = 10\text{ A}$ ,  $R_{g\_on/off} = 4.7/4.7\ \Omega$ ,  $V_{ds} = 800\text{ V}$

# AND90255/D

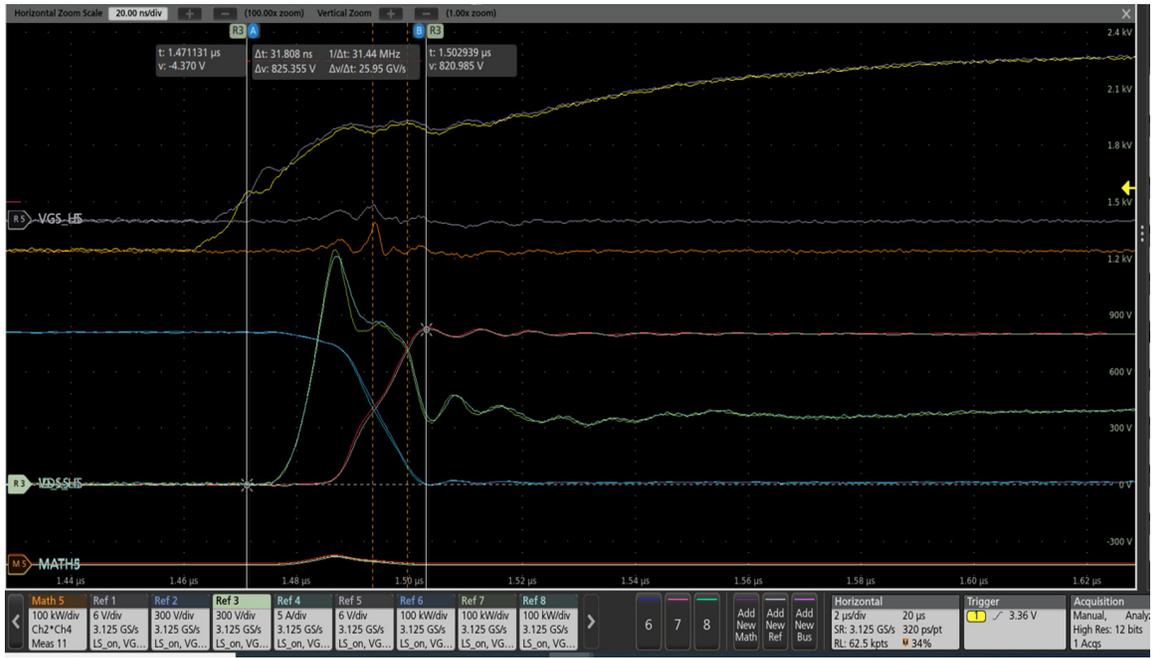


Figure 16. Switching Waveforms Comparison  $V_{gs\_off} = 0\text{ V}$  vs.  $-3\text{ V}$ ,  $I_D = 40\text{ A}$ ,  $R_{g\_on/off} = 10/4.7\ \Omega$ ,  $V_{ds} = 800\text{ V}$


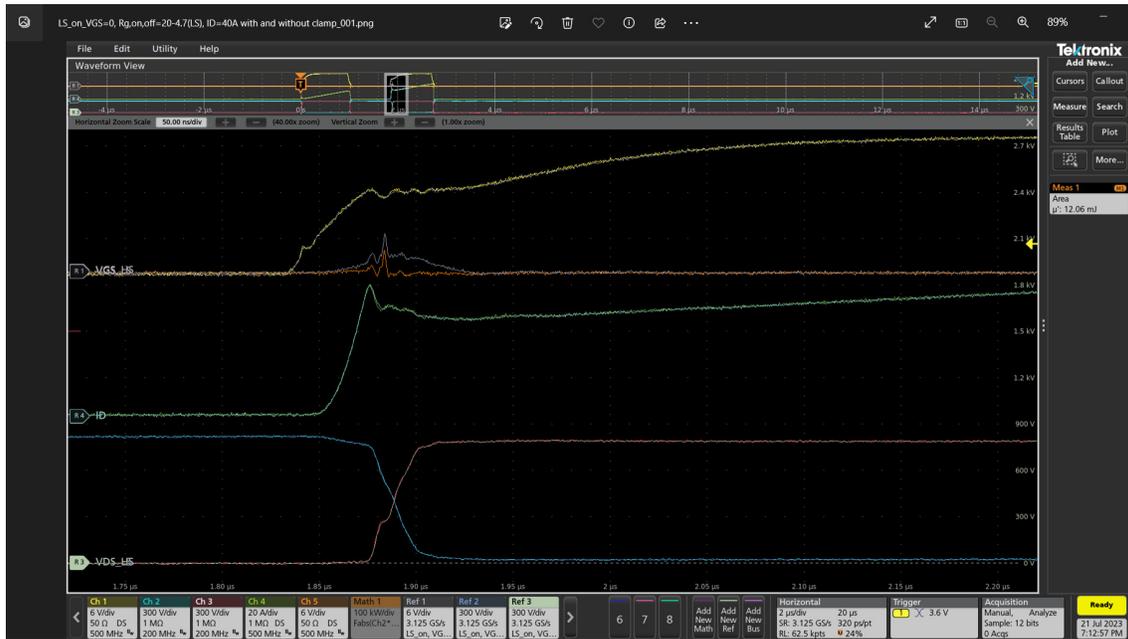


Figure 17. Without Active Clamp,  $V_{gs\_off} = 0\text{ V}$ ,  $R_{g\_on}$  of Low Side Increased to 20 and  $R_{g\_off} = 4.7/4.7\ \Omega$  to Reduce  $dv/dt$  and Prevent PTO

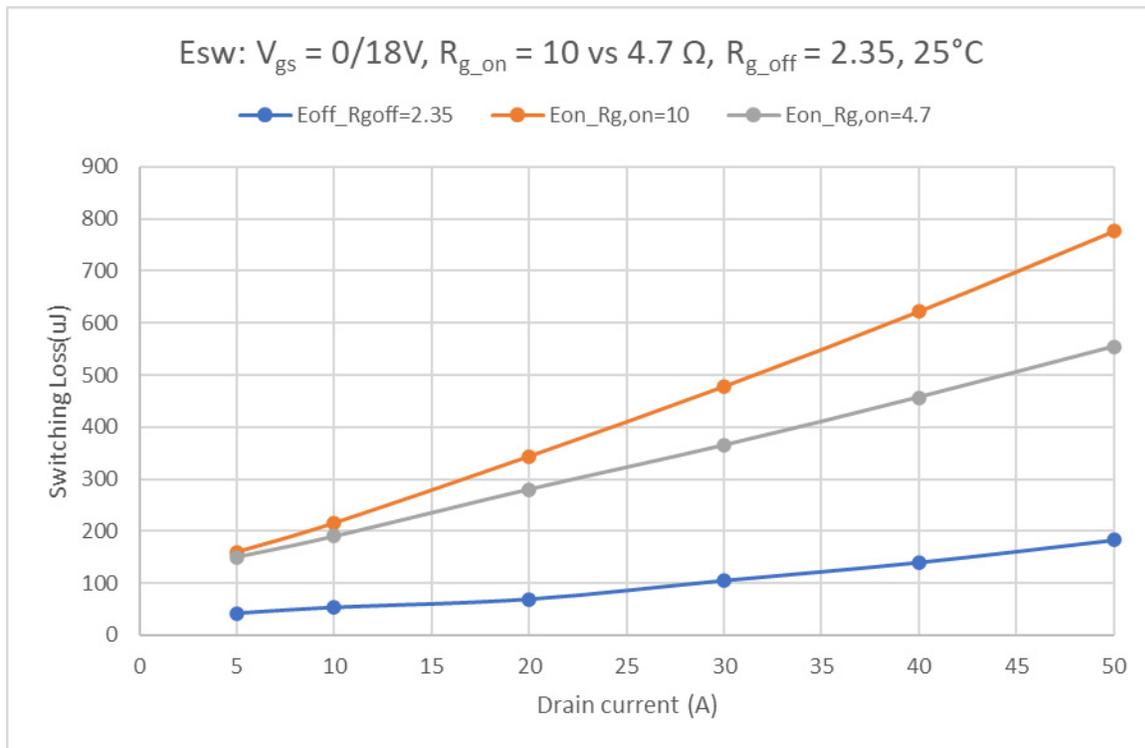

**Figure 18. Switching Losses Comparison  $V_{gs} = 0 V/18 V$ , with  $R_{g\_on} = 4.7 \Omega$  vs.  $10 \Omega$ . With Active Clamp Enabled**

### Conclusion

This paper discusses mainly the ability to drive **onsemi**'s SiC MOSFETs with unipolar gate to source voltage (0 V/+18 V) and its impact on system efficiency. Due to the fast switching speed and low threshold voltage of SiC MOSFET a crosstalk between power devices in a half bridge configuration becomes a concern especially when it turns off with  $V_{gs\_off} = 0 V$ . When one device turns on, the  $dV_{ds}/dt$  imposed on the complimentary device causes Miller capacitance to discharge into the gate which may cause a parasitic turn on if the induced voltage on the gate is high enough. The severity of the crosstalk depends mainly on Miller capacitance  $C_{gd}$ , switching rate  $dV_{ds}/dt$ ,  $C_{gs}/C_{gd}$  ratio and total gate resistance ( $R_{g\_ext} + R_{g\_int}$ ). In this paper the issue of parasitic turn on and its impact on switching losses are studied using simulation and hardware test setups. To prevent the parasitic turn on, the turn on gate resistor must be increased to reduce the  $dV_{ds}/dt$  and Miller capacitance effect or  $V_{gs\_off}$  must have a sufficiently high value. For example, based on the test results,  $R_{g\_on} = 10 \Omega$  is good compromise between switching losses and potential for

PTO. When  $V_{gs\_off} = 0 V$  is used, it is also recommended to reduce  $R_{g\_off}$  to enable discharge of  $V_{gs}$  during times when PTO may occur.

Active Miller clamp helps to mitigate the PTO effect on switching losses, but tuning the  $R_{g\_on/off}$  to control the  $dV_{ds}/dt$  is also necessary to prevent the PTO completely for the case of  $V_{gs\_off} = 0 V$ . If no active clamp is used,  $R_{g\_off}$  must be minimum to reduce the need to increase  $R_{g\_on}$  to mitigate PTO while keeping low switching losses.  $R_{g\_off} = 0 \Omega$  is equivalent to an active clamp function.

Ultimately, from practical perspective, it is feasible to drive **onsemi**'s SiC MOSFETs with  $V_{gs\_off} = 0 V$  even when experiencing  $dV_{ds}/dt = 50 V/ns$ . However, assuming proper PCB design, the designer must consider the tradeoffs between the target efficiency, reliability and EMI compliance. A gate driver with active clamp is highly recommended when unipolar gate voltage is used. Finally, driving the SiC MOSFET with sufficient negative turn off voltage is recommended to eliminate PTO and reach higher system efficiency.

## References

- [1] Rabkowski, J., Pefitsis, D., & Nee, H. (2012). Silicon Carbide Power Transistors: A New Era in Power Electronics Is Initiated. *IEEE Industrial Electronics Magazine*, 6(2), 17–26.  
<https://doi.org/10.1109/mie.2012.2193291>
- [2] Wang, F., & Zhang, Z. (2016). Overview of Silicon Carbide Technology: Device, Converter, System, and Application. *CPSS Transactions on Power Electronics and Applications*, 1(1), 13–32.  
<https://doi.org/10.24295/cpsstpea.2016.00003>
- [3] Zhao, S. G., Zhao, X., Wei, Y., Zhao, Y., & Mantooth, H. A. (2021). A Review of Switching Slew Rate Control for Silicon Carbide Devices Using Active Gate Drivers. *IEEE Journal of Emerging and Selected Topics in Power Electronics*, 9(4), 4096–4114.  
<https://doi.org/10.1109/jestpe.2020.3008344>
- [4] Shao, T., Li, Z., Zheng, T. Q., Li, H., Huang, B., Wang, Z., & Zhang, Z. (2020). Impact of Common Source Inductance on the Gate–Source Voltage Negative Spike of SiC MOSFET in Phase–Leg Configuration.  
<https://doi.org/10.1109/ipemc-ecceasia48364.2020.9368245>
- [5] Li, Z., Wang, Z., Zheng, T., Li, H., Huang, B., & Shao, T. (2020). Efficiency Optimization for All–Silicon Carbide (SiC) PWM Rectifier Considering the Impact of Gate–Source Voltage Interference. In *Energies* (Vol. 13, Issue 6, p. 1421). MDPI AG.  
<https://doi.org/10.3390/en13061421>
- [6] (2018). *Simetrix/Simplis User’s Manual*. Simetrix Technologies Ltd. & Simplis Technologies Inc. Retrieved from:  
<http://www.simetrix.co.uk/Files/manuals/8.2/UsersManual.pdf> (accessed May 27, 2023).
- [7] **onsemi**, “Silicon Carbide (SiC) MOSFET – EliteSiC, 40mΩ, 1200 V, M3S, D2PAK–7L” NVBG040N120M3S–D datasheet, May, 2023. Retrieved from:  
<https://www.onsemi.com/download/data-sheet/pdf/nvbg040n120m3s-d.pdf> (accessed June 6, 2023).
- [8] Shi L., Tianshi L., Zhu S., Qian J., Jin M., Maddi H. L. R., White M. H., and Agarwal A. K. ”Effects of Oxide Electric Field Stress on the Gate Oxide Reliability of Commercial SiC Power MOSFETs,” 2022 IEEE 9th Workshop on Wide Bandgap Power Devices & Applications (WiPDA), Redondo Beach, CA, USA, 2022, pp. 45–48, [doi: 10.1109/WiPDA56483.2022.9955295](https://doi.org/10.1109/WiPDA56483.2022.9955295)
- [9] Saha, A. (2023). *AC gate bias stress of 4H–SiC MOSFETs, an investigation into threshold voltage instability of SiC Power MOSFETs under the influence of bipolar gate stress* (Unpublished master thesis). KTH Royal Institute of Technology, Stockholm, Sweden.
- [10] Hefner, A. R., Singh, R. P., Lai, J., Berning, D. W., Bouche, S., & Chapuy, C. (2001). SiC power diodes provide breakthrough performance for a wide range of applications. *IEEE Transactions on Power Electronics*, 16(2), 273–280.  
[doi: 10.1109/63.911152](https://doi.org/10.1109/63.911152)
- [11] Pham T., Frachi J., Lee K., and Domeij M. “1.2 kV SiC MOSFET Body Diode Turn–Off in Fast Switching Channel Conduction, Carrier Plasma and Parasitic Turn–On” in 35th Int. Symposium on Power Semiconductor Devices & ICs, May 28, 2023.

**onsemi**, **ONSEMI**, and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba “**onsemi**” or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi**’s product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided “as-is” and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. “Typical” parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including “Typicals” must be validated for each customer application by customer’s technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## ADDITIONAL INFORMATION

## TECHNICAL PUBLICATIONS:

Technical Library: [www.onsemi.com/design/resources/technical-documentation](http://www.onsemi.com/design/resources/technical-documentation)  
onsemi Website: [www.onsemi.com](http://www.onsemi.com)

ONLINE SUPPORT: [www.onsemi.com/support](http://www.onsemi.com/support)

For additional information, please contact your local Sales Representative at [www.onsemi.com/support/sales](http://www.onsemi.com/support/sales)