

Test Procedure for the NCV8163MXTBGEVB Evaluation Board

There is a collection test procedures for NCP163 demoboards. This paper offers some helpful test configuration for first contact with ON SEMICONDUCTOR NCP163 LDO. Same procedure is also valid for automotive NCV8163 demoboards

1. QUIESCENT CURRENT

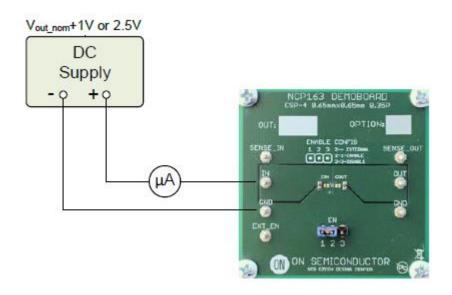


Figure 1: Test configuration for measurement Iq, Quiescent Current

- 1. Connect circuit as shown figure on 1
- 2. Apply voltage at V_{Input}. Default test V_{input} is V_{out_nom}+1 V or 2.5 V whichever is greater
- 3. Value shown µA meter is measured quiescent current.
- 4. Measurement is finished. Disconnect supply voltage.

^{*}Note – Be carefully if any device is connected on output, because leakage current can affect measurement accuracy.



2. LOAD REGULATION

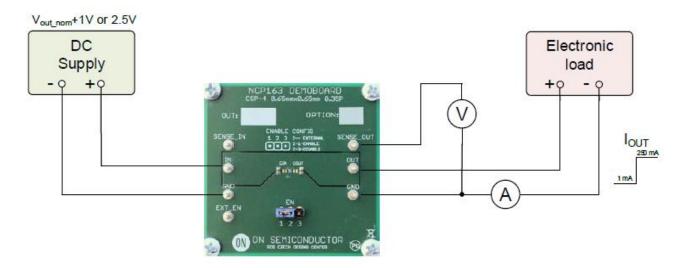


Figure 2: Test configuration for measurement REGLOAD, Load Regulation

- 1. Connect circuit as shown figure on 2
- 2. Apply voltage at V_{Input}. Default test V_{input} is V_{out_nom}+1 V or 2.5 V whichever is greater



- 3. Set minimal required current I₁, e.g. 1 mA, and switch load ON.
- 4. Note the value V1 from voltmeter Vo.
- 5. Switch load OFF and set maximal required current I2, e.g. 250 mA and switch load ON.
- 6. Note the value V2 from voltmeter Vo.
- 7. Load regulation is obtained via following formula: REGLOAD=(V1-V2), [V]
- 8. Measurement is finished. Disconnect supply voltage.

3. LINE REGULATION

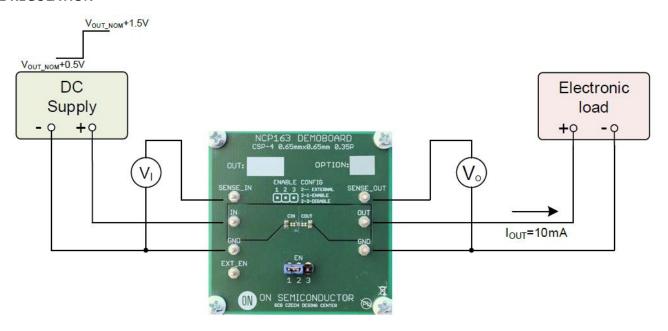


Figure 3: Test configuration for measurement REGLINE, Line Regulation

- 1. Connect circuit as shown on figure 3
- 2. Set load to the required current e.g. 10 mA
- 3. Set minimal input voltage V_{I1}, V_{OUT_NOM}+1V or 2.5V whichever is greater
- 4. Note the value V₁₁ and V₀₁.
- 5. Set maximal input voltage V₁₂ = 5.5 V
- 6. Note the value V₁₂ and V₀₂.
- 7. Load regulation is obtained via following formula: REGLINE=(Vo1-Vo2)/(VI1-VI2), [V/V]
- 8. Measurement is finished. Disconnect supply voltage.



4. ENABLE START-UP

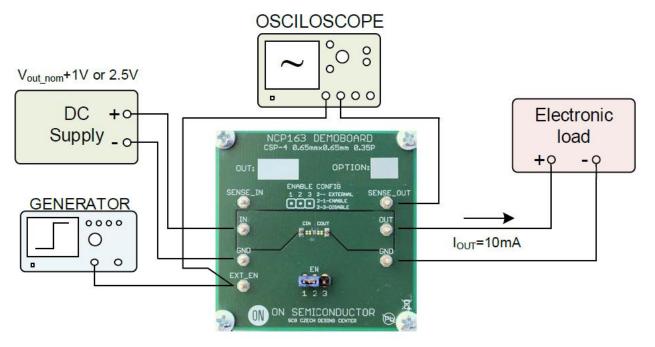


Figure 4: Test configuration for measurement enables response

- 1. Connect circuit as shown on figure 4
- 2. Set generator to SQUARE PULSE, 0.9 ≤ AMPLITUDE ≤ VIN, FREQUENCY=10Hz, DUTY=10%
- 3. Apply voltage at V_{Input}. Default test V_{input} is V_{out_nom}+1 V or 2.5 V whichever is greater
- 4. Set required lout, e.g. 10 mA
- 5. Connect oscilloscope to EN signal and Voutput.
- 6. Watch enable response of the regulator after asserting EN pin.
- 7. Measurement is finished. Disconnect supply voltage.