



Is Now Part of



ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at

www.onsemi.com

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

Application Guide for FSHDMI08

FSHDMI08 Target Applications and Switch Overview

Summary

The FSHDMI08 is designed for single-link digital video formats, including both DVI and HDMI. The FSHDMI08 utilizes a passive design architecture capable of handling data rates up to and including 1.65Gbps. It is fully compatible with HDMI version 1.2a and can be used in HDMI version 1.3a applications in which total data rates do not exceed 1.65Gbps. One such example might be an application that requires 720p resolution, but utilizes the higher color depths (e.g. 16-bit) available in the 1.3a specification. The FSHDMI08 offers several enhancements over its predecessor, the FSHDMI04; one of which is the incorporation of four additional signal switches designed to handle the specific needs of the Display Data Channel (DDC) signal routing. These additional paths eliminate the need for a second switch. Additionally, the FSHDMI08 also allows direct flow-through signal routing and offers built-in voltage translation of the SDA and SCL data lines.

Key Switch Parameters

HDMI and DVI data rates are extremely high for transmission of uncompressed digital video. In a single-link HDMI connection, each TMDS¹ pair transmits data at rates up to 1.65Gbps. Designing with high-speed data transfer protocols brings new application challenges. In such environments, previously insignificant amounts of stray capacitance, line loading, and signal mismatch can result in increased bit error rates and failure to successfully transmit or receive data. Both the HDMI and DVI specifications allow very little tolerance in the electrical specifications to accommodate the addition of a non-ideal switch. As a result, board layout, ESD suppression, and switch selection all must be taken in to account. Following are some key performance characteristics in selecting an HDMI switch.

On Capacitance vs. On Resistance

On capacitance most significantly determines the impact of the switch on the TMDS data stream. Excess switch capacitance results in attenuation of the signals' harmonic content. This is observed as rounded off edges and slower rise and fall times. Mismatches in channel on capacitance are of great importance relative to the HDMI and DVI specifications, making it increasingly difficult to meet the very tight skew specification. For example, when transmitting at the highest data rate, intra-pair skew cannot exceed $0.15T_{bit}$, which is equivalent to no more than 90ps at 1.65Gbps. One of the design tradeoffs that HDMI/DVI switch designers confront is between on capacitance and on resistance. Low on capacitance and high-bandwidth performance come at the expense of increased on resistance. Because this is unavoidable, it is a fundamental reason HDMI/DVI switches must be designed for the application.

Bandwidth

A second crucial switch characteristic is bandwidth. To transmit data at the highest data rates, an HDMI/DVI switch must have at least 825MHz bandwidth. This number is derived by knowing that data can be transmitted at speeds as great as 1.65Gbps. Considering that pixel data is triggered on both the rising and falling edges, the switch must have no more than 3dB of signal loss over the frequency range 0 to 825MHz. A switch without such performance severely attenuates the data stream when transmitting the highest video resolutions. This can result in failure to recover data by an HDMI or DVI receiver.

¹ For more background on HDMI signaling, consult the following application note for the FSHDMI04, <http://www.fairchildsemi.com/an/AN/AN-6015.pdf>.

Applications Guidance

The following sections provide guidance on several topics of PCB design. For more information, please contact your Fairchild Semiconductor representative.

Using the FSHDMI08 to Isolate Voltages on the SDA, SCL, and CEC Data Lines

HDMI uses the DDC signal lines, SDA and SCL based, on the I²C specification. These signals lines and the HPD (Hot Plug Detect) signal are used to communicate between sink and source during the initial connection, allowing the system to properly configure. The FSHDMI08 is designed to route these three signals along with the CEC control line in addition to the TMDS signals. The SDA and SCL signal lines use a pull-up referenced, open-drain signaling scheme which, per the I²C-bus™ specification, can be referenced to voltages as high as 5V. Many HDMI receiver chips are limited to a maximum input signal of 3.3V, setting the stage for a potential problem. Some designers have resorted to adding voltage translators on the SDA and SCL lines to prevent damage to sensitive HDMI receivers. The FSHDMI08 SDA, SCL, HPD, and CEC inputs are inherently over-voltage tolerant, which allows them to be used to isolate the different voltages on either side of the switch, eliminating the need for additional components. To use this feature, the V_{DDC} supply pin should be set to no more than the maximum input voltage acceptable to the most sensitive device. For a typical case, the V_{DDC} pin voltage is 3.3V, which results in the FSHDMI08 automatically isolating the 5V source-side I²C pull-ups from the sink-side, 3.3V I²C pull-ups (illustrated in Figure 1).

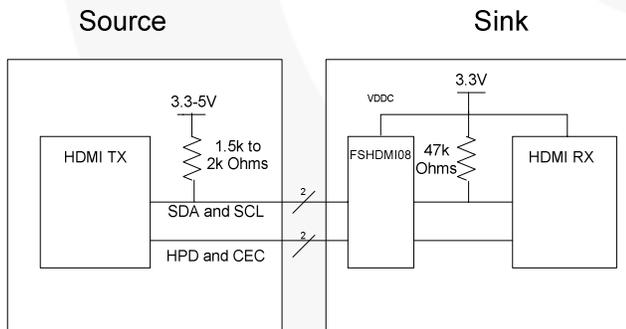


Figure 1. Configure FSHDMI08 to Isolate Voltages on SDA and SCL

If this feature is implemented, it should also be noted that, when using such a configuration, not only do the SDA and SCL lines have their outputs clamped by the V_{DDC} supply voltage, but the HPD and CEC lines are limited. During initial HDMI cable plug-in, the HPD signal is asserted by the receiver when it detects the 5V supply from the source supplied through the HDMI cable. According to the HDMI specification version 1.3a, the HPD output signal must be

asserted to a high value (in the range 2.3V-5.5V). The output of a voltage-driven signal being passed through the FSHDMI08 on HPD and CEC paths is limited to the chosen V_{DDC} supply, less 0.7V. For the above example (V_{DDC} = 3.3V), the resultant output is 2.6V for any input voltage in the range 2.6V to 5.5V. Inputs less than 2.6V pass through the FSHDMI08 without any attenuation. The CEC output minimum level is specified to be 2.5V. For this reason, it is recommended that the minimum V_{DDC} supply be 3.3V for such an application. For greater margin, increase the V_{DDC} supply voltage to a value slightly above 3.3V, such that V_{DDC}-0.7V remains less than or equal to the maximum allowable input voltage on the SDA and SCL lines. In the example above, the acceptable V_{DDC} supply range would be 3.3 to 4.0V. By following this guidance, the FSHDMI08 can be used to route and isolate voltage levels on the SDA and SCL lines and simultaneously route the HPD and CEC lines.

Applications with Powered-off Cases When Active Input Could be Present

The FSHDMI08 TMDS signal lines do not have over-voltage protection to prevent device damage when signals are applied to the inputs with no V_{CC} present. In applications where signals could be applied to the FSHDMI08 when the voltage supply is not on, precautions should be taken to ensure the FSHDMI08 is not damaged and that no TMDS signals are transmitted through the FSHDMI08 to other downstream devices.

One method to avoid having active HDMI signals present with no V_{CC3} applied to the FSHDMI08 is to power the FSHDMI08 V_{CC3} off the HDMI cable. The FSHDMI08's low-power operation allows the device to be powered from the cable. An example circuit is shown in Figure 2.

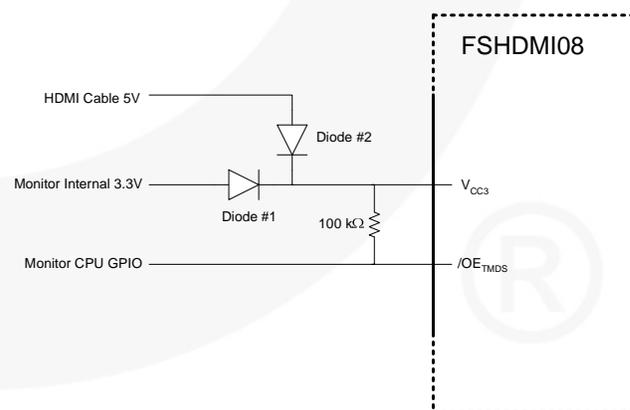


Figure 2. Recommended Applications with Powered-Off Cases When Active Input Could be Present

In Figure 2, the voltage from the HDMI cable power is 5V. The 5V supply from the cable cannot be directly applied to the V_{CC3} of the FSHDMI08 because the FSHDMI08's maximum recommended operating supply voltage for V_{CC3} is 4.3V. To prevent exceeding the maximum recommended supply, one or more diodes can be placed between the cables 5V supply and the supply pins of the FSHDMI08 (diode #2 in Figure 2). The voltage drop of the diode must total a minimum of 1.0V to keep the supply of the FSHDMI08 below 4.3V. A diode is also placed on the system's 3.3V supply (diode #1 in Figure 2), to prevent the 5V from the cable trying to drive the whole system's supply. For Diode #1, a Schottky diode with a forward voltage of no more than 0.2V is recommended. This ensures that voltage supplying the VCC3 pin is adequate for device operation. Diode #2 can be two diodes in series. A possible solution is two Fairchild 1N4148 diodes in series (0.6V drop each, 1.2V total) for diode #2 and a Fairchild MBR0530 diode (0.2V drop) for diode #1. Note that the FSHDMI08 quiescent current consumption is very low ($<1\mu\text{A}$), so the voltage drop through the diodes may be lower than expected.

Once the device is powered from the cable, the voltage from the cable can also be used to pull the FSHDMI08's output enable pins HIGH, which disables the outputs. Signals are not transmitted to parts of the system that are powered down. This can be accomplished by placing a 100-k Ω resistor between the device's power pins and the TMDS output enable pin, as shown in Figure 2. When the system is powered up, the TMDS output enable pin must be pulled LOW. This can be accomplished by using the system processor GPIO pins. When the system is powered and enabled, the GPIO pin pulls the TMDS output enable LOW. When the system is not powered, the TMDS output enable is pulled HIGH through the 100-k Ω resistors.

ESD Protection and the FSHDMI08

The FSHDMI08 is often the first IC on the signal line next to the HDMI connector and, generally, must provide the first line of defense against an ESD event. The FSHDMI08 has very robust ESD performance and is designed to protect against human body model ESD events per JEDEC JESD22-A114, up to and including 8kV. This is generally more than adequate to protect systems from ESD events. For designers who require higher ESD protection, use only ultra-low capacitive, ESD-suppression devices designed for high-speed signaling. As a point of reference, these devices should contribute no more than 0.8pF of capacitive loading to the TMDS signal lines to avoid causing signal integrity issues. There are several different suppliers with such devices available.

For more information on Fairchild's ESD test methodology, please refer to the following application note:

<http://www.fairchildsemi.com/an/AN/AN-6019.pdf>

FSHDMI08 Layout Guidelines

HDMI applications use high-frequency, digital-data transfer on each line; making board layout an important factor in determining successful system implementation. The following board layout guidelines are provided as a point of reference to aid in high-speed board design. There is no a perfect board design in a real-world application, so these bulleted suggestions act guidelines that should be followed as closely as possible:

- Minimize trace lengths by placing the FSHDMI08 as close to the HDMI receiver as possible. Place both parts as close to the HDMI connectors as possible.
- Use closely coupled 100-Ohm differential controlled impedance traces for each TMDS pair (TMDS0, TMDS1, TMDS2) or loosely coupled 50-Ohm, controlled-impedance, single-ended traces.
- Minimize via usage on the FSHDMI08 TMDS signal lines. Only use vias where necessary to connect with the HDMI connector or HDMI receiver chip.
- Verify that all TMDS pair trace lengths are matched (less than 250mil difference between TMDS+, TMDS-) to minimize intra-pair skew.
- Match all TMDS sets; TMDS0, TMDS1, TMDS2 traces, to within 30mils to minimize inter-pair skew.
- Maintain individual spacing of at least three times the dielectric height between adjacent, closely coupled differential pairs or loosely coupled 50-Ohm traces. If possible, place a GND strip between parallel differential pairs on the same layer.
- Use a single, shared, uniform GND plane for all TMDS signaling lines.
- Isolate any other high-frequency data lines from the TMDS signal lines to avoid cross coupling (minimum 3X dielectric height spacing).
- Place a 0.1 μF bypass capacitor as close as possible to the VCC pin of the FSHDMI08. Because the FSHDMI08 is a passive device and uses less than 1 μA of current during steady-state operation, a single bypass capacitor is sufficient.
- **Optional:** There is debate among high-speed board layout experts regarding whether 90-degree corners should be avoided to reduce signal reflections and skew. Some published papers propose this is not critical to maintaining signal integrity. If you have room to round signal corners, it is a suggested precaution.

Fairchild has FSHDMI08 example layouts prepared for all three packages and Gerber files are provided upon request to aid board design and layout. Contact your Fairchild representative to request copies of these files or demonstration boards. An example of a schematic and Gerber file for FSHDMI08 applications board follow.

Example Layout

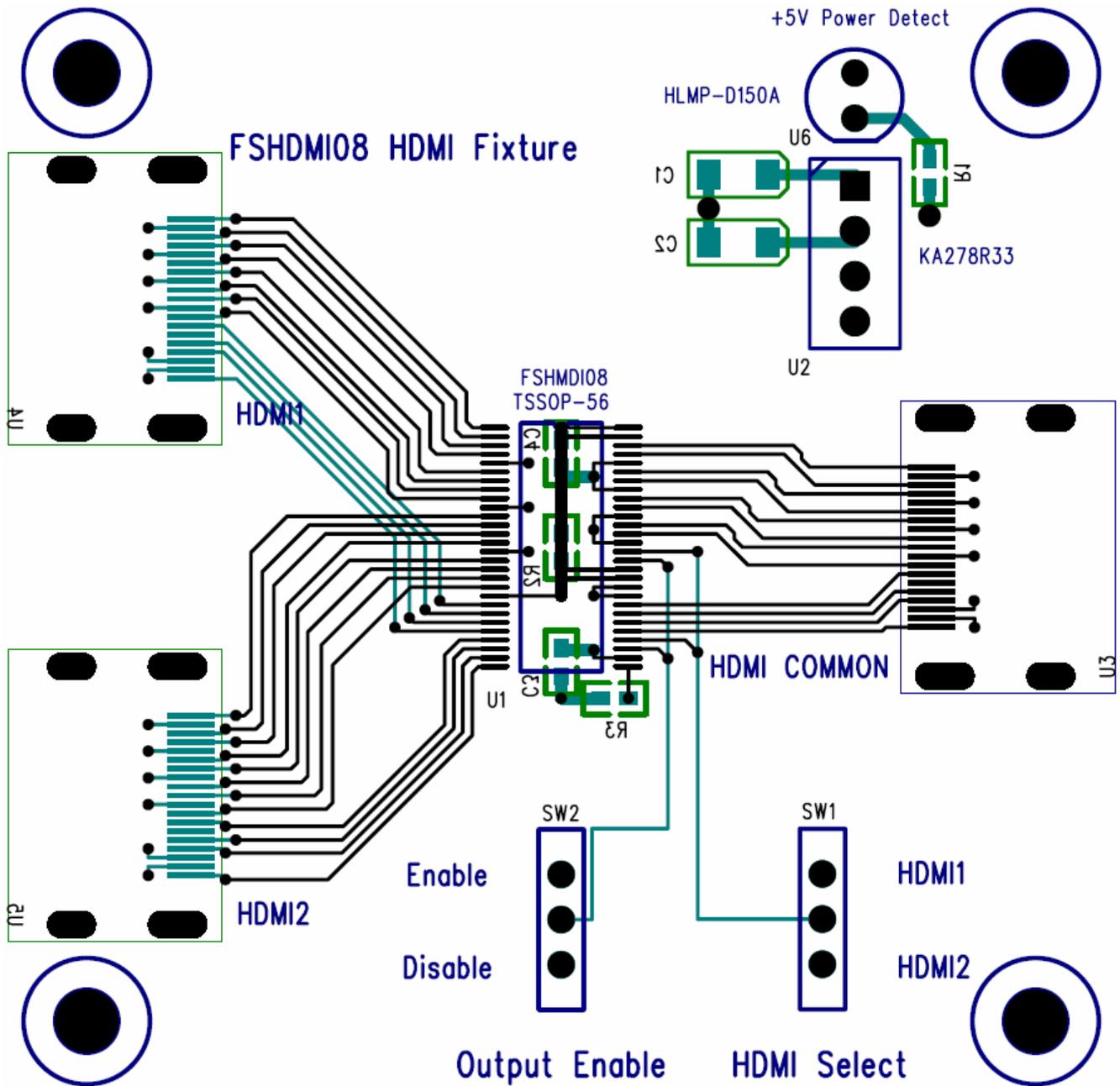


Figure 3. FSHDMI08 Example Layout – Evaluation Board

Example Schematic

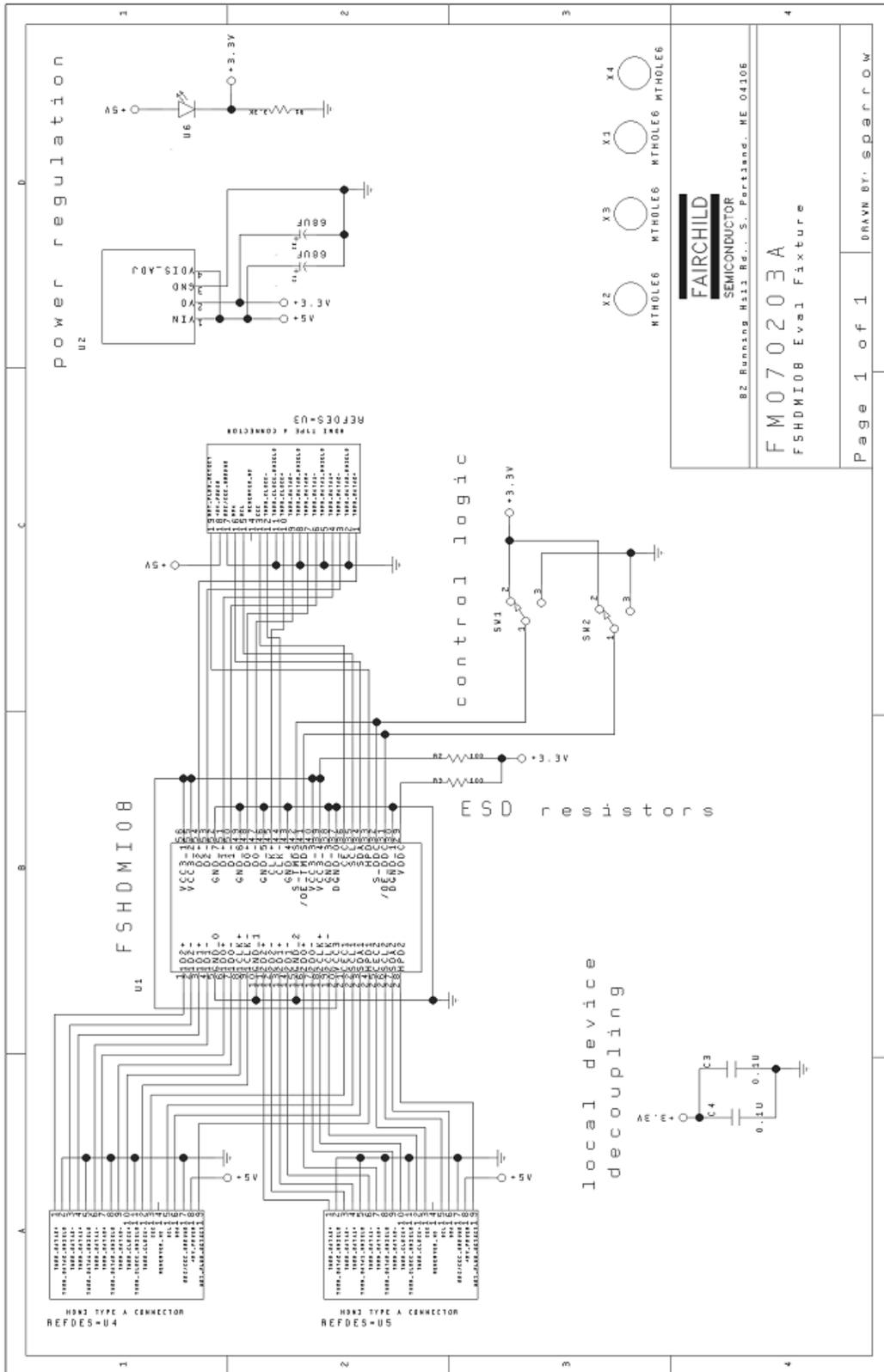


Figure 4. FSHDMI08 Example Schematic – Evaluation Board

Related Resources

AN-6015 — FSHDMI04 Applications Guide

<http://www.fairchildsemi.com/an/AN/AN-6015.pdf>

AN-6019 — Fairchild Analog Switch Products ESD Test Methodology Overview

<http://www.fairchildsemi.com/an/AN/AN-6019.pdf>

The I²C-BUS Specification, Version 2.1, January 2000

http://www.nxp.com/acrobat_download/literature/9398/39340011.pdf

THE “I²C Specification” and Information Page

http://www.nxp.com/news/backgrounders/bg_esc9727/index.html

I²C-bus™ is a trademark of Philips Electronics, NV / NXP Semiconductors.

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative