

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



Is Now Part of



ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at

www.onsemi.com

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

AN-7730 FL7730 Design Tool Flow

Overview

This document is intended to provide in-depth guidance to using the Fairchild Design Tool for FL7730. Use the Design Tool with the product datasheet.


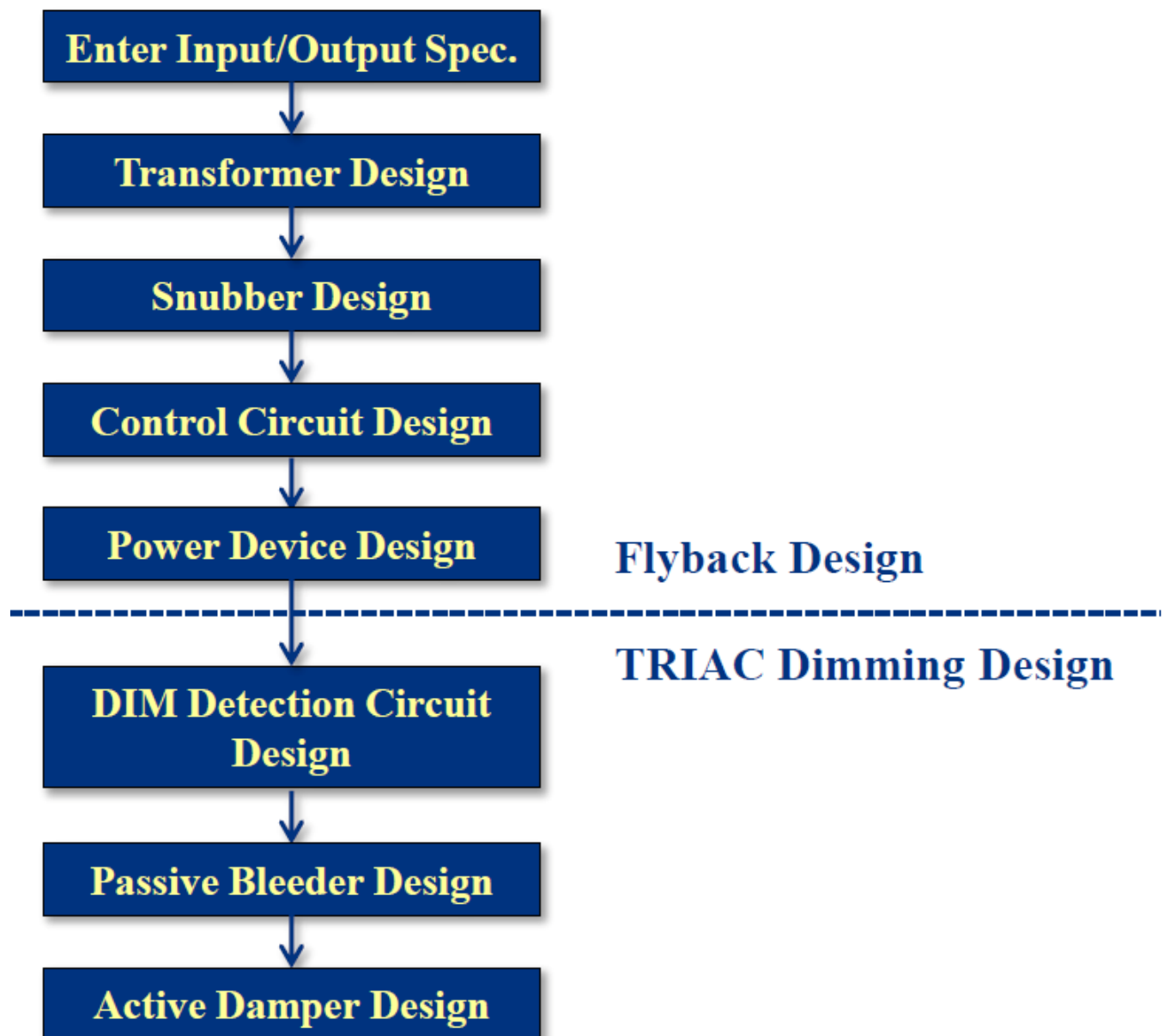


Figure 1. Design Flow

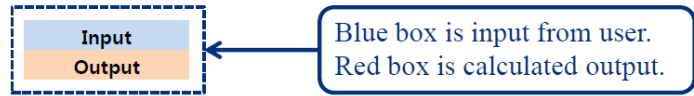Step 1 — Enter Input Output Specification



Input Spec		
Min. Vin	90	Vac
Max. Vin	140	Vac
Output Spec		
Vout	22	V
Max. Vout	28	V
Iout	380	mA
Pout	8.36	W

Max. Vout is OVP level.

Step 2 — Transformer Design

Transformer Design		
Max. Duty	39	%
Max. Ton	6.500	us
Switching freq.	60	kHz
Max. Vcs	0.5	V
Efficiency	80	%
Ae	36.6	mm ²
Bmax	0.3	
Lm	0.982	mH
Nps	3.223	
Nas	0.821	
Nap	0.255	
Np.min	75.347	T
Np	76	T
Ns	23.578	T
Na	19.368	T
Llk	10	uH

- Max. duty is generally between 20 ~ 50%.
High max. duty = · Low conduction loss. Suitable for low-line
Low max. duty = · More Bmax margin. Suitable for high-line
- Max. Ton should be less than 10us.
- This switching frequency is the operating frequency at the rated Vout condition.
The switching frequency should be less than 65kHz.
- Max. Vcs is max. peak CS voltage.
Enter Max. Vcs less than 0.67V because pulse by pulse CS voltage limit is 0.67V.
Higher Nps makes higher max. Vcs in the primary side CC regulation.
So, when max. Vcs is highly set, Nps becomes higher.
- Enter Np over Np.min.
If Np is too big to fit in transformer window, reduce Max. Duty.
- Make transformer according to the above spec.
Then, enter Llk (Leakage inductance) after measuring.

Step 3 — Snubber Design


Snubber Design		
Vsn	200	V
ΔVsn	5	V
Rsn	242.7247	kohm
Csn	2.746596	nF

- Vsn is snubber voltage.
Vsn is generally set as 2~2.5 times Nps · Vo.
- ΔVsn is generally set as 5% ripple of Vsn.

Step 4 — Control Circuit Design

Control Circuit Design		
Rsense	0.593767	ohm
Rcc	100	ohm
Vin.bnk	50	V
Vf	0.5	V
Rvs1	165.2367	kohm
Rvs2	19.75502	kohm
Cvs	10	pF
Ccomi	1	uF
Cvdd	33	uF
Dvdd Vmax	73.95584	V
Rstr	155.8442	kohm

- Rcc is line CC compensation resistor. When Iout becomes higher at higher input voltage, increase Rcc. Rcc should be limited less than 500ohm. Large Rcc can make CS noise, inducing Vcs peak detection error.
- Vin.bnk is COMI/VS blanking level. COMI blanking : Error amp. input is fixed, working as open loop. VS blanking : VS voltage detection is disabled. Vin.bnk is generally set as 30~70V.
- Vf is secondary diode forward voltage.
- Cvs is VS filter capacitor, generally set as 10~30pF.
- COMI capacitor is generally 0.68~3.3uF. Check output voltage overshoot at startup in max. Vin condition. If output voltage overshoot is too big, increase Ccomi.
- Vdd capacitor is generally in 10~47uF. If Vdd drops too close to Vdd-off at startup, increase Cvdd.

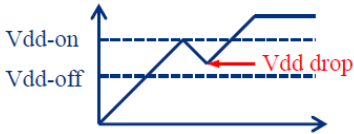

Step 5 — Power Device Design

Power Device Design		
MOSFET Vmax	397.9899	V
MOSFET Ipk	0.842082	A
Diode Vmax	89.4245	V
Diode Ipk	2.714286	A

- Vmax is MOSFET drain-source maximum voltage. Ipk is MOSFET peak current.
- Vmax is maximum reverse voltage of secondary diode. Ipk is peak current of secondary diode.

Step 6 — DIM Detection Circuit Design

DIM Detection Circuit Design		
ZDdim	11	V
Rdim1	1	Mohm
Rdim2	75	kohm
Rdim3	62	kohm
Cdim	3.3	uF

Zener voltage of ZDdim is generally in 10~40V.

Rdim1 is generally around 1Mohm.

If Rdim1 is too small,

- effieincy is reduced.

- Dim pin voltage is changed a lot when line voltage changes.

If Rdim1 is too big,

- ZDdim biasing current becomes too small, inducing error in dimming angle detection.

TRIAC dimmers have different max. dimming angle.

So, Rdim2/3 can not be calculated and found by testing with dimmers.

Rdim2/3 are tens to hundreds kohm.

Rdim2/3 determine dimming control range.

For wider dimming control range, reduce Rdim2 and Rdim3.

(But, wider dimming control makes higher flicker possibility specially in high-line and low output power condition.)

Cdim is 0.1~5uF as a filter to supply DC voltage to Dim pin.

If Cdim is too big, Dim pin voltage rises slowly at startup and it can affect powering speed.

Step 7 — Passive Bleeder Design

Passive Bleeder Design		
Cbleeder	330	nF
Rbleeder	0.5	kohm

Cbleeder is generally 47~470nF.

If Cbleeder is increased,

- Flicker is relieved.

- Efficiency and PF become worse.

Rbleeder is determined after selecting Cbleeder.

Rbleeder is generally 0.1~10kohm.

Too big Rbleeder limits bleeder current, which makes flicker.

Too small Rbleeder induces input current ringing at dimmer firing, which also can make flicker.

So, change Rbleeder by checking input current at firing.

Find the min. Rbleeder to satisfy below.

- input current at firing is higher enough than dimmer holding current.

- there is no mis-fire right after firing.

The min. Rbleeder is proper value for no flicker and high efficiency.

Step 8 — Active Damper Design

Active Damper Design		
Rdamp	100	ohm
SWdamp Vmax	300	V
Ddelay Vmax	300	V
Cdelay	100	nF
Rdelay	20	kohm

Rdamp is generally 10~1kohm.
 Rdamp is to limit input spike current at fire and remove flicker.
 Large Rdamp can considerably reduce spike current and remove flicker, but it will reduce efficiency.

So, find min. Rdamp to satisfy below without active damping circuit.
 - Input spike current at 90° dimming angle is less than customer spec.
 - There is no flicker caused by Rdamp current ringing.
 (Check input current and Rdamp current at the same time. Then, you can find if input current ringing is affected by Rdamp current.)

Check the Rdamp temperature after finding the min. Rdamp.
 If the temperature is too high and efficiency is too low, active damper is necessary and go to **active damper design**.

Active Damper Design		
Rdamp	100	ohm
SWdamp Vmax	300	V
Ddelay Vmax	300	V
Cdelay	100	nF
Rdelay	20	kohm

Check Rdamp voltage at 90° dimming angle firing.
 That is SWdamp max voltage .

Tip! SWdamp with low threshold voltage can reduce power loss.
 (Because Rdamp voltage is regulated as threshold voltage.)

Ddelay max. voltage is same as SWdamp max. voltage.

Cdelay is generally around 100nF.

Rdelay is tens to hundreds kohm.
 Large Rdelay lengthens delay time between dimmer fire and SWdamp turn-on.

Find the min. Rdelay to satisfy below.
 - At 90° dimming angle, SWdamp should be turned on after input current is dampened by Rdamp.
 (Check if input current ringing is finished before SWdamp turns on.)
 The min. Rdelay is proper value for high efficiency.

Related Resources

Locate the Design Tool at:

http://www.fairchildsemi.com/design_tools/led-driver-design-tool/

Consult the product datasheet at:

[*FL7730 — Dimmable Single-Stage PFC PSR Offline LED Driver*](#)

Follow us on Twitter at:

twitter.com/fairchildSemi

View product and company videos, listen to podcasts, and comment on our blog at:

www.fairchildsemi.com/engineeringconnections

Visit us on Facebook at:

www.facebook.com/FairchildSemiconductor

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative