## **ON Semiconductor**

### Is Now



To learn more about onsemi™, please visit our website at www.onsemi.com

onsemi and ONSEMI. and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "onsemi" or its affiliates and/or subsidiaries in the United States and/or other countries. onsemi owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of onsemi product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. onsemi reserves the right to make changes at any time to any products or information herein is provided "as-is" and onsemi makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does onsemi assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using onsemi products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by onsemi. "Typical" parameters which may be provided in onsemi data sheets and/ or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. onsemi does not convey any license under any of its intellectual property rights nor the rights of others. onsemi products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use onsemi products for any such unintended or unauthorized application,



#### Is Now Part of



## ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at <a href="https://www.onsemi.com">www.onsemi.com</a>

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any EDA Class 3 medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, emplo



# AN-7732 FL7732 Design Tool Flow (Flyback)

#### **Overview**

This document is intended to provide in-depth guidance to using the Fairchild Design Tool for FL7732. Use the Design Tool with the product datasheet.

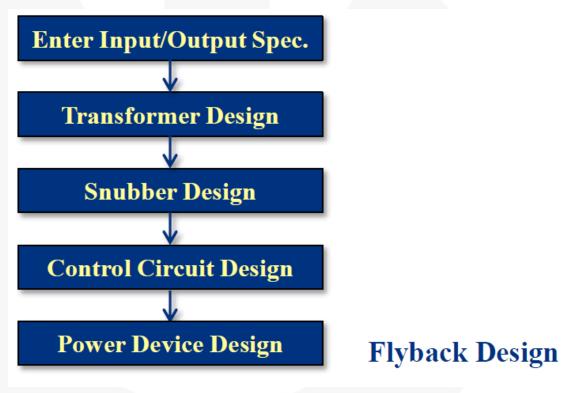


Figure 1. Design Flow

AN-7732 APPLICATION NOTE

## Step 1 — Enter Input Output Specification



Inj	out Spec		
Min. Vin	90	Vac	
Max. Vin	140	Vac	
Out	tput Spec		
Vout	22	V	
Max. Vout	28	V	$\leftarrow$
Iout	380	mA	
Pout	8.36	W	

## Step 2 — Transformer Design

Max. duty is generally between  $20 \sim 50\%$ .

High max. duty = · Low conduction loss, Suitable for low-line Low max. duty = · More Bmax margin, Suitable for high-line

Max. Duty Max. Ton Switching freq kHz 60 Max. Vcs 0.5 ٧ **Efficiency** 80 % 36.6  $mm^2$ Ae **Bmax** 0.3 Lm 0.982 mΗ 3.223 Nps 0.821 Nas 0.255 Nap 75.347 Np.min Т Nρ 76 Т 23.578 Ns Na 19.368 Llk 10 uΗ

Max. Ton should be less than 10us.

This switching frequency is the operating frequency at the rated Vout condition.

The switching frequency should be less than 65kHz.

Max. Vcs is max. peak CS voltage.

Enter Max. Vcs less than 0.67V because pulse by pulse CS voltage limit is 0.67V.

Higher Nps makes higher max. Vcs in the primary side CC regulation.

So, when max. Vcs is highly set, Nps becomes higher.

Enter Np over Np.min.

If Np is too big to fit in transformer window, reduce Max. Duty.

Make transformer according to the above spec.

Then, enter Llk (Leakage inductance) after measuring.

## Step 3 — Snubber Design

Snubber Design							
Vsn	200	V	4				
∆Vsn	5	V	*				
Rsn	242.7247	kohm					
Csn	2.746596	nF					

Vsn is snubber voltage.

Vsn is generally set as 2~2.5 times Nps·Vo.

 $\Delta V$ sn is generally set as 5% ripple of Vsn.

## Step 4 — Control Circuit Design

Rcc is line CC compensation resistor.

When Iout becomes higher at higher input voltage, increase Rcc.

Rcc should be limited les than 500ohm.

Large Rcc can make CS noise, inducing Vcs peak detection error.

Control Circuit Design 0.593767 Rsense ohm 100 ohm Rcc Vin.bnk 50 ٧ 0.5 ۷f Rvs1 165.2367 kohm Rvs2 19.75502 kohm 10 Cvs рF uЕ Ccomi Cvdd 33 uF V **Dvdd Vmax** 73.95584

155.8442

kohm

Rstr

Vin.bnk is VS blanking level.

VS blanking: VS voltage detection is disabled.

Vin.bnk is generally set as 30~70V.

Vf is secondary diode forward voltage.

Cvs is VS filter capacitor, generally set as 10~30pF.

COMI capacitor is generally 0.68~3.3uF.

Check output voltage overshoot at startup in max. Vin condition.

If output voltage overshoot is too big, increase Ccomi.

Vdd capacitor is generally in 10~47uF.

If Vdd drops too close to Vdd-off at startup, increase Cvdd.



## Step 5 — Power Device Design

Power Device Design							
397.9899	V	2					
0.842082	Α						
89.4245	V						
2.714286	Α	1					
	397.9899 0.842082 89.4245	397.9899 V 0.842082 A 89.4245 V					

Vmax is MOSFET drain-source maximum voltage. Ipk is MOSFET peak current.

Vmax is maximum reverse voltage of secondary diode. Ipk is peak current of secondary diode.

AN-7732 APPLICATION NOTE

#### **Related Resources**

Locate the Design Tool at:

http://www.fairchildsemi.com/design\_tools/led-driver-design-tool/

Consult the product datasheet at:

FL7732 —Single-Stage PFC Primary-Side-Regulation Offline LED Driver

Follow us on Twitter at:

twitter.com/fairchildSemi

View product and company videos, listen to podcasts, and comment on our blog at:

www.fairchildsemi.com/engineeringconnections

Visit us on Facebook at:

www.facebook.com/FairchildSemiconductor

#### DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

#### LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
- A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and in are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at <a href="www.onsemi.com/site/pdt/Patent-Marking.pdf">www.onsemi.com/site/pdt/Patent-Marking.pdf</a>. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and exp

#### **PUBLICATION ORDERING INFORMATION**

#### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor 19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada Email: orderlit@onsemi.com N. American Technical Support: 800–282–9855 Toll Free USA/Canada
Europe, Middle East and Africa Technical Support: Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81–3–5817–1050

ON Semiconductor Website: www.onsemi.com

Order Literature: http://www.onsemi.com/orderlit

For additional information, please contact your local Sales Representative