

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.

ON Semiconductor's D2 Series Transistors for Fluorescent Converters

Prepared by: Pascal M. Otero
 ON Semiconductor
 Applications Engineer



ON Semiconductor®

<http://onsemi.com>

APPLICATION NOTE

INTRODUCTION

Switching bipolar transistors are very popular in the fluorescent ballast field where they provide cheap designs. Nevertheless, the use of bipolar transistors is not straightforward; they are based on minority carrier operation, making switching simulation difficult and inaccurate. Designing fluorescent converters with standard bipolar transistors requires a certain amount of skill.

Due to the inductive storage time (t_{si}) variations and the optimization of fall time, the switching losses and the case

temperature are probably the most critical issues the designer has to deal with.

The aim of the D2 series is to drastically simplify the design of electronic ballasts for fluorescent tubes. This is possible due to the integration of two extra devices (D2): a freewheeling diode; and an anti-saturation network.

This application note presents the interest of the D2 structure and how to utilize this new series to solve the critical issues that the designer must deal with.

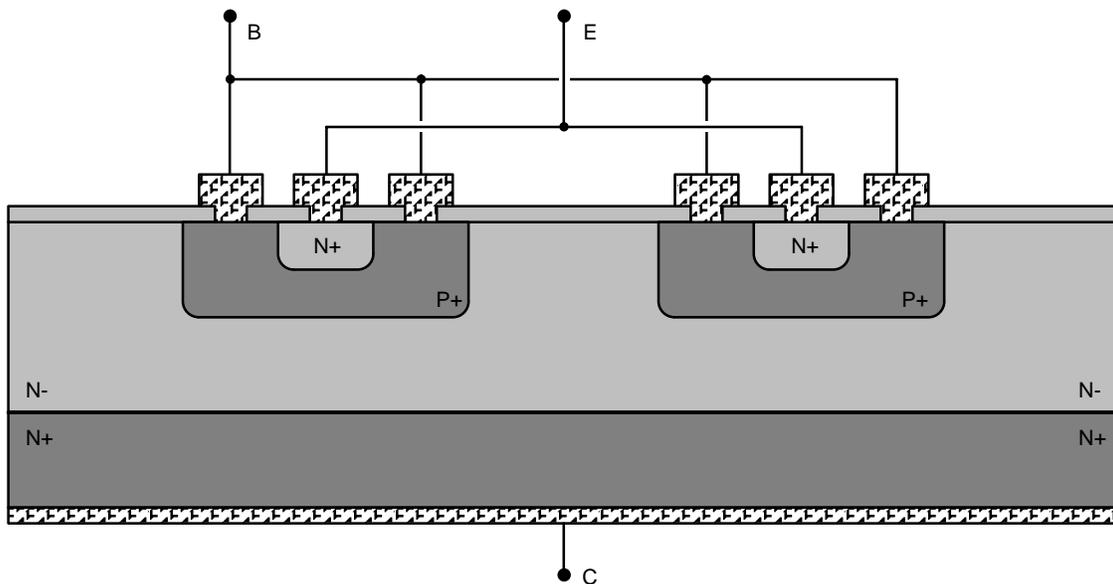


Figure 1. Standard Bipolar Transistor, Two Emitter Fingers Cross Section

Standard Bipolar Transistors Structure

During the saturation phase, the base and collector regions are filled with carriers that significantly reduce the resistivity of these areas.

This phenomenon has two consequences:

1. During turn off, the base resistance is either shorted to the emitter or connected to a negative voltage, so as the internal base voltage is still positive, the minority carriers are extracted from the base area (see Figures 21 and 22).

This phase takes time because the base resistivity depends on the carrier density of each part of the base area. The faster the carriers located near the base contact are extracted, the faster the resistivity increases near the base contact and the slower the carriers located under the emitter fingers will be extracted (Figure 2).

During this phase, the base current (named I_{B2}) is negative, but V_{CE} is still V_{CEsat} and I_C is still flowing. This phase corresponds to the storage time (t_{si}).

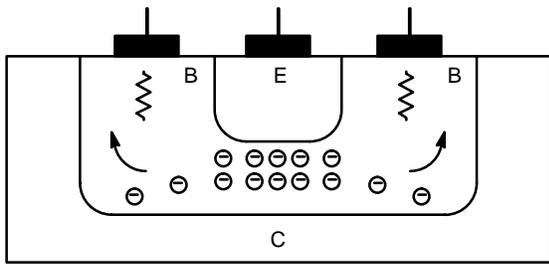


Figure 2. Poor Minority Carriers Extraction

When no charge remains trapped within the base, I_{B2} decreases to zero and I_C goes to zero as well. This is the fall-time phase (see Figure 3 and Reference 3).

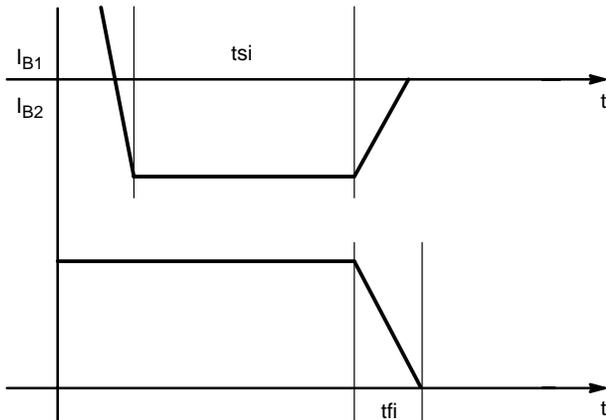


Figure 3. tsi and tfi Definition

- The drop of resistivity of the base and collector areas allows very low collector to emitter voltage, even if the current density is high (V_{CEsat}) (see Figure 4).

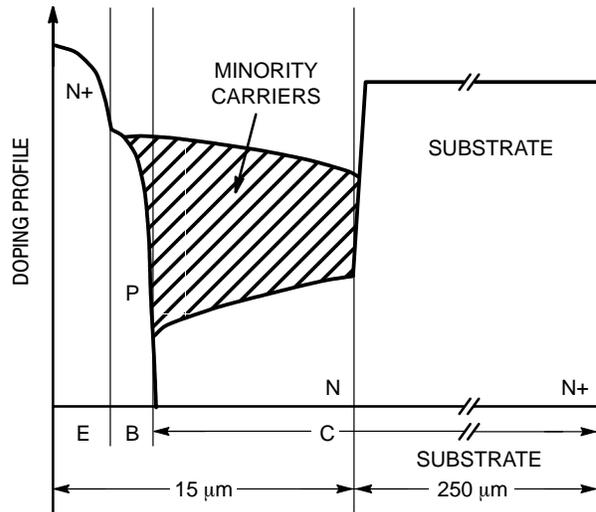


Figure 4. Minority Carriers Distribution During Saturation Condition

The low resistivity of the emitter, base, and active collector areas, combined with their small depth, make the resistance of these areas very low compared to the substrate.

This modulation mechanism of the resistivity explains why bipolar on losses are smaller than those of MOSFET for a given die size.

D2 Series Structure

Figure 5 shows the cross section of a D2 device. The main difference between D2 series and other transistors having built-in freewheeling diodes is the way the freewheeling diode is designed.

Instead of adding the diode in a corner of the die, the D2 devices have the diode distributed across the active area of the transistor. This protected geometry gives an extra lateral PNP and unique advantages.

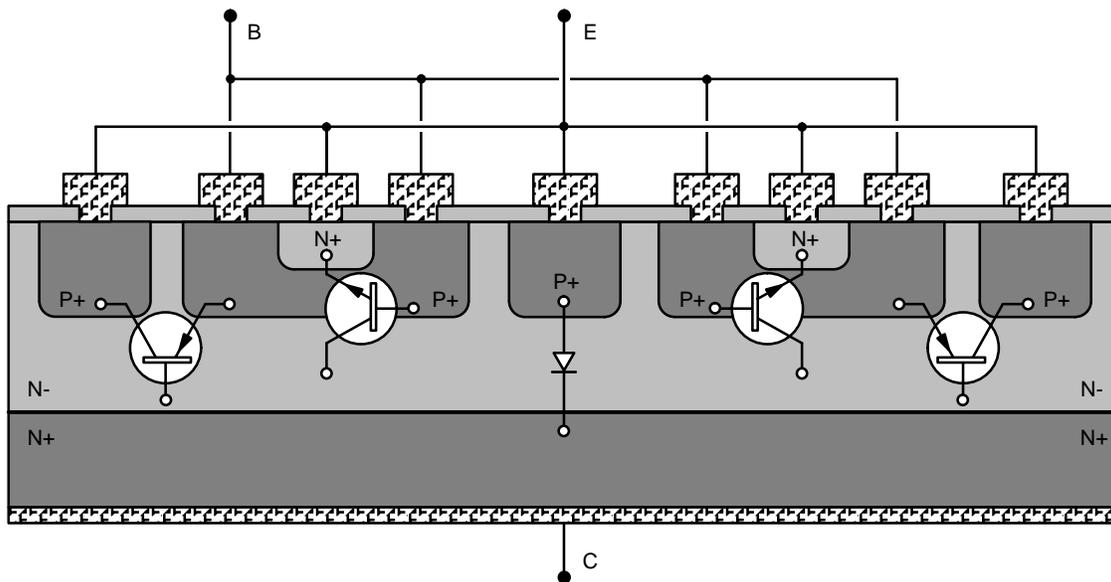


Figure 5. D2 Transistor Simplified Cross Section

Freewheeling Diode

An important point would be to measure the dynamic parameters of this diode. Unfortunately, the measurement of the t_{TR} and Q_{TR} is impossible because it is not possible to isolate the distributed diode from the transistor structure.

However, we can compare I_C waveforms coming from the application between BUL44 (standard switching transistor using external freewheeling diode), against BUL44D2.

Figure 6 shows the typical waveform of the BUL44 collector current associated with 1N4937, Figure 7 with

MUR160, and Figure 8 depicts BUL44D2 I_C curves. As we can see, the distributed diode behavior is close by the MUR160 one from a t_{TR} point of view.

One must point out that there is no advantage to connect an extra freewheeling diode across a D2 device. This external diode sets a different Q_{TR} than that of the internal one, and the PNP behavior is highly modified, implying an increase of power losses and heat dissipation within the switch.

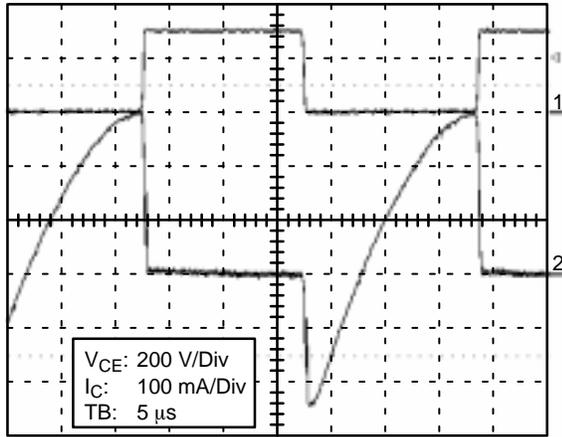


Figure 6. BUL44 and 1N4937

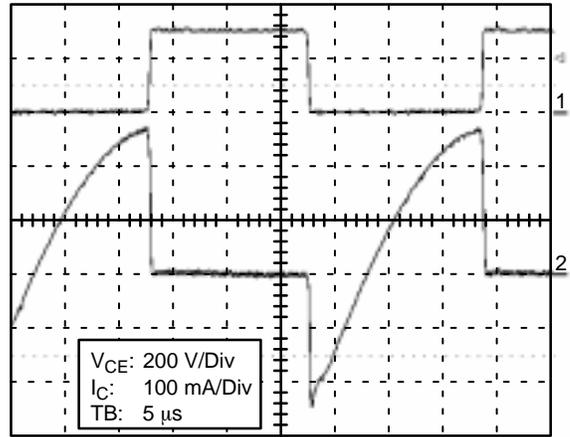


Figure 7. BUL44 and MUR160

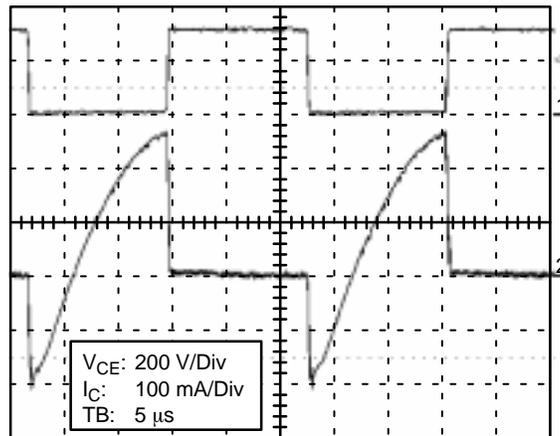


Figure 8. BUL44D2

Anti-Saturation Network

The anti-saturation network is built around the extra PNP connected, as shown in Figure 9. The effective I_B current of the main transistor is controlled by the feedback provided through the PNP and the V_{CEsat} sense of the NPN structure.


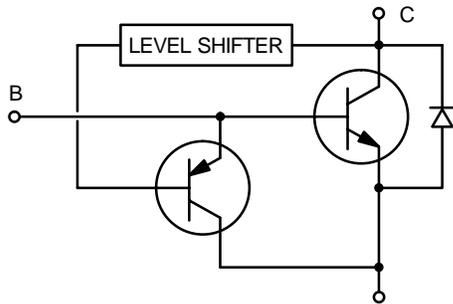


Figure 9. D2 Equivalent Schematic

Like the Baker clamp (Figure 10), this network either allows proportional drive or avoids hard saturation. The base current of the power transistor is limited when its V_{CE} voltage becomes too low. In case of a Baker clamp, the minimum V_{CE} is about two diode drops, as given by equation [1].
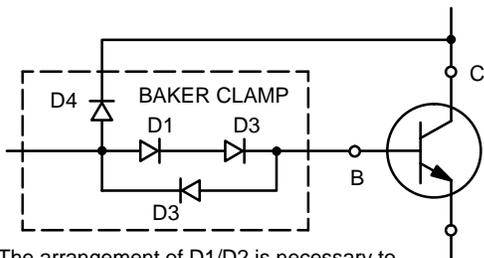
$$V_{CEsat} = V_{BE} + V_{D1} + V_{D2} - V_{D4} \quad (\text{eq. 1})$$



The arrangement of D1/D2 is necessary to compensate for the drop coming from D4.

Figure 10. Baker Clamp Schematic

The anti-saturation network built in the D2 devices gives the same advantages as the Baker clamp, but without the drawback of a high V_{CEsat} . Figures 11 and 12 show two curves comparing dynamic V_{CEsat} observed in case of a BUL44D2, and the Baker clamp topology built around a BUL44 and 1N4937.

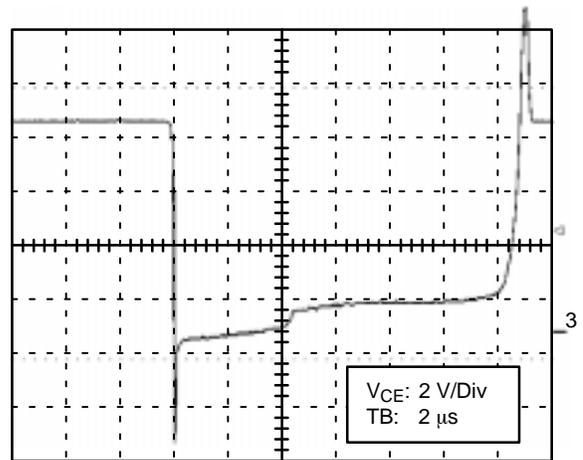


Figure 11. BUL44D2 Dynamic V_{CEdyn}


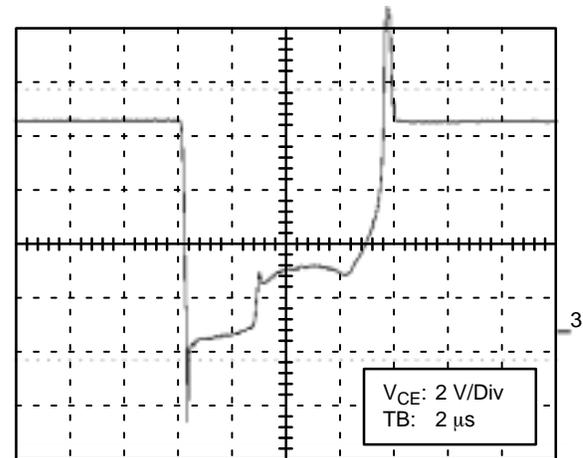


Figure 12. BUL44/Baker Clamp V_{CEdyn}

Note: Due to the test jig depicted in Figure 13, we must subtract 600 mV (calibrated) from the values observed coming from the diode drop.

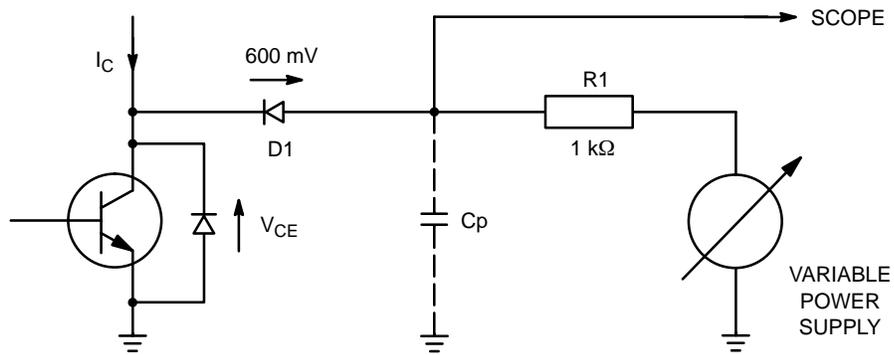This gives a net V_{CEsat} of 507 mV for BUL44D2, compared to 1.92 V for the Baker clamp topology. Since R1 is small, this circuit has a small parasitic time constant $R1Cp$.



Since R1 is Small, this Schematic Allows a Small Parasitic Time Constant $R1Cp$.

Figure 13. Dynamic V_{CEsat} Test Jig

Critical Application Requirements

The purpose of this paragraph is not to establish an exhaustive list of the switches technical requirements, but to point out the most critical ones (refer to AN1543/D “Electronic Lamp Ballast,” where switch selection is described).

Inductive Storage Time (tsi) Dispersion

The inductive storage time corresponds to the time required to extract the charges stored within the base, the collector load being inductive.

Since the tsi is a part of the converter half period, tsi variations can be pernicious to the lifetime of the tube. Due to the inductive load, frequency variations mean power dissipation variations within the tube. Figure 14 shows the consequences of tsi variations on the power dissipated.

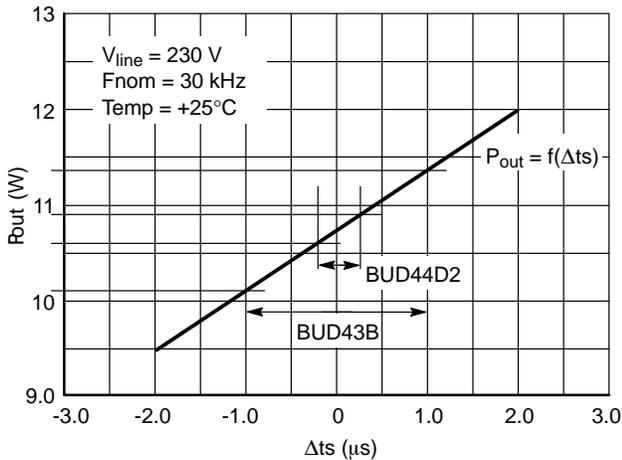


Figure 14. Ptube versus Δ (tsi)

We can observe the extremely tight tsi dispersion of D2 devices compared to standard ones. The specification

guarantees the tsi dispersion at ± 150 ns (whatever be the temperature within the specified range), and the output power follows the same dispersion.

Figure 15 shows the t_{off} variation of the BUL45D2 versus the temperature between -40°C and $+125^{\circ}\text{C}$. Leaving aside the tolerances coming from the measurements, the t_{off} variation follows a straight line and, due to the tight dispersion of this parameter, is absolutely predictable.

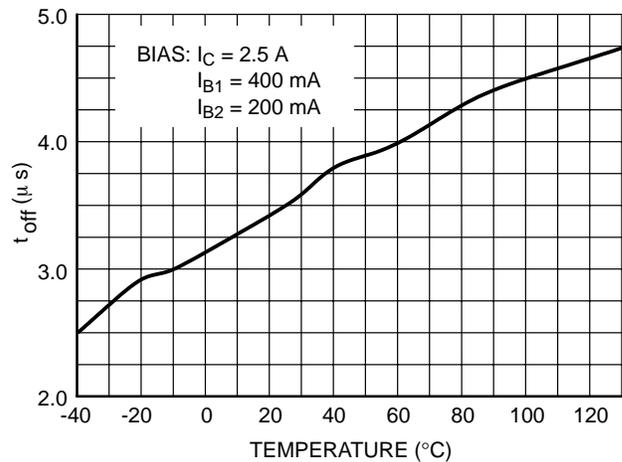


Figure 15. BUL45D2 t_{off} Variation versus Temperature

Manufacturing standard fluorescent converters using bipolar transistors requires to guaranty an h_{FE} window to correlate a tsi window.

In the case of D2 devices, h_{FE} windows no longer make sense. Since the power transistor and the PNP are diffused on the same die, h_{FE} variations are equivalent for both transistors. PNP h_{FE} variation tends to compensate the NPN, making tsi nearly constant when h_{FE} varies.

Fall Time and Power Losses

Power losses are an important criterion since they are responsible for the operating case temperature which can be approximated using equation [2]:

$$T_c - T_a = P_1 \times R_{thJA} \quad (\text{eq. 2})$$

- where T_c = Case temperature
- T_a = Ambient temperature
- P_1 = Power losses within the switch
- R_{thJA} = Thermal resistance between Junction to Ambient

(Assuming $R_{thJA} \gg R_{thJC}$).

Since for reliability reasons the junction temperature is limited at 150°C max, the lower the losses, the higher the ambient temperature can be. Following the usual analysis, power losses can be split in four different parts corresponding to the four phases of a switching sequence (Figure 16).

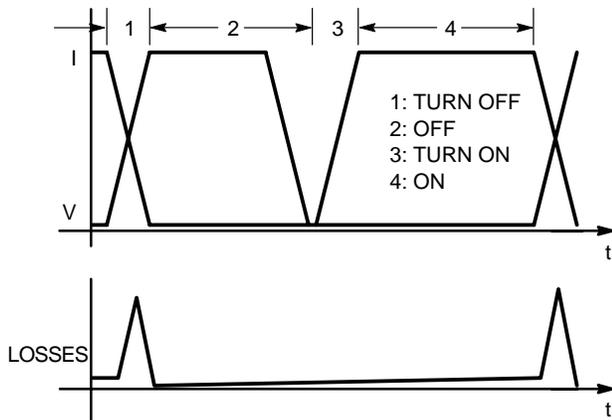


Figure 16. Switching Sequence

1. Turn off losses: The minority carriers trapped into the base and the collector areas, during the on phase, are responsible of fall time. This produces losses only during switch off as the dV_{CE}/dt is high due to inductive switching. Figure 17 shows BUL45D2 and BUL45 tfi under the same bias condition.
2. Off losses are negligible due to the low value of the leakage current.
3. Turn on losses are negligible as well because V_{CE} drops to V_{CEsat} before I_C increases.
4. On losses: They are characterized by the product $V_{CEsat} \times I_C$.

During the saturation phase, the base and the collector areas are filled with minority carriers. This reduces the resistivity of the silicon and provides low losses (Figure 4).

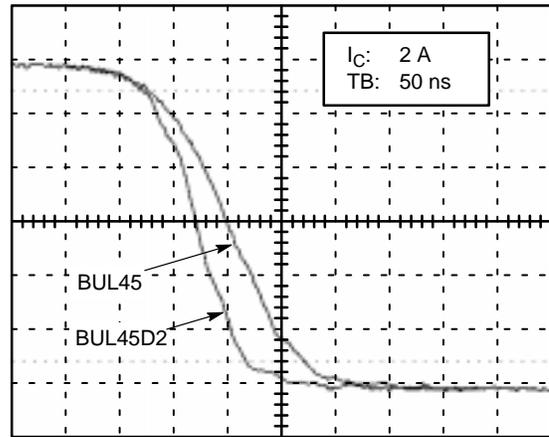


Figure 17. BUL45D2 tfi: 95 ns, BUL45 tfi: 150 ns

Due to the D2 design, the power dissipated within the switch is no longer related to the switching phase, but comes from the on phase⁽¹⁾. This is extremely important from a design safety point of view.

During the turn off phase, the transistor is reverse biased (I_B is negative, V_{CE} and I_C positive) and has to sustain a moving I_C/V_{CE} operating point. The switch can be destroyed in few microseconds if this point goes out of the Reverse Bias Safe Operating Area as shown in Figure 18 (see AN873/D and AN875/D). Power losses produced during the on phase are safer because they follow thermal laws.

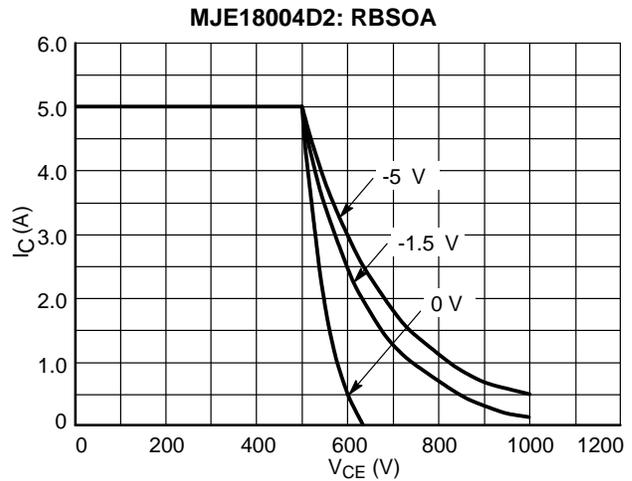


Figure 18. Typical RBSOA Curve versus Different Reverse Bias Voltages Applied on the Base

⁽¹⁾It is important to notice this new way to manage the power dissipated within the bipolar transistor allows operating frequencies up to 100 kHz.

D2 in Fluorescent Application

Another important advantage of this network consists in the drastic simplification of the calculation of the drive and so the development time of the designer. Usually designers have to adapt the oscillation transformer output to the transistor.

The base drive conditions set up the behavior of the transistor as follows:

I_{B1} peak must be high enough to guaranty low V_{CEsat}

I_{B1} negative going slope must be optimized to adjust the t_{si} and the frequency

I_{B2} shall be adjusted to minimize turn off losses.

We must point out that it is difficult to achieve the accurate control of the negative-going slope of the base current in a cheap way. The use of the D2 device is simpler as it is less sensible to the I_{B1} to I_{B2} transition, and it accommodates sharp edges and high I_{B2} level. The same principle allows proportional drive.

One of the interests of the Baker clamp is the proportional drive that consists in the possibility to drive either one or two tubes or more, keeping the bias network of the transistor constant.

By connecting several tubes to a single converter, the I_C current varies proportionally to the number of tubes. This means I_B current must be able to follow this variation according to the transistor transfer curve.

This is not possible due to the nonlinear response of the saturable core of the oscillation transformer.

The use of D2 devices is a way to overcome this nonlinearity.

How to Get the Best Benefits Out of the D2 Series

We demonstrated that the D2 series works fine within a wide range of biases. Most of the time designers need transistors operating at a high ambient temperature. (Due to the housing, compact fluorescent ambient temperature can reach 125°C, the transistors must operate safely. The thermal constraint is more sensitive for DPAK packaged devices.) Generally speaking, the problem consists in pushing further the thermal runaway occurrence.

A possible cause of a thermal runaway is a preswitching off desaturation (V_{CE} begins to increase at the end of the t_{si} phase, as I_C is maximum, before switch off). This phenomenon can occur, mainly with the D2 series, because of

its specific structure. The operating principle of these devices is to never run in hard saturation (Figure 9); this means the amount of charges trapped within the base is small. As soon as I_{B2} extracts a certain amount of charge, V_{CE} tends to increase and the device is desaturated.

Based on the cheapest and the most common drive circuits shown in Figures 19 and 20, the analysis of this specific bipolar transistor operation gives two ways to stabilize the device at high operating temperature, when the I_C current tends to runaway:

1. Increase the emitter resistance value (R_E).

As the collector current is high, the drop voltage across the emitter resistance provides a negative feedback to the base of the D2 device. During I_{B1} phases, the net voltage available across the base circuit (out of the secondary of the toroid) is reduced by the feedback voltage.

During I_{B2} phases, the oscillator transformer does not provide any driving voltage and the secondary winding shorts the base resistance to the ground. As the I_C value is still high, the emitter voltage is positive (Figure 22). This increases I_{B2} (as if a negative voltage were applied across the base), limits any preswitching off desaturation, and significantly improves the thermal behavior of the device.

2. Increase I_{B1} value.

The value of I_{B1} current can be very different without having significant impact on switching parameters, due to the anti-saturation network.

The h_{FE} of the built in PNP, like other bipolar transistors, is limited by the level of I_C current (see typical h_{FE} versus I_C curves) so the extra base current derived via the PNP is limited as well. When I_{B1} is higher than the PNP can handle, its h_{FE} drops and the anti-saturation network no longer works. The amount of charges trapped within the power NPN transistor base can be larger and the preswitching desaturation phenomenon disappears.

Both solutions generally imply an adjustment of the toroid turns ratio to adjust the operating frequency.

Designers used to driving standard bipolar transistors know that the negative slope of I_{B1} and the value of I_{B2} are critical to optimize t_s , t_f , and the switching losses.

Using a D2 device is simple; t_s , t_f , and switching losses will be optimized as soon as the I_{B2} value is high (this value can be higher than that of I_{B1}), and the I_{B2} waveform is as square as possible (fast falling edge).

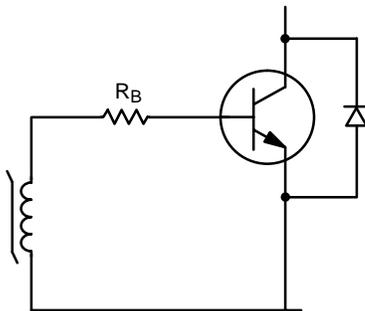


Figure 19.

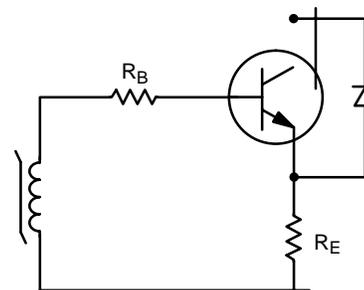


Figure 20.

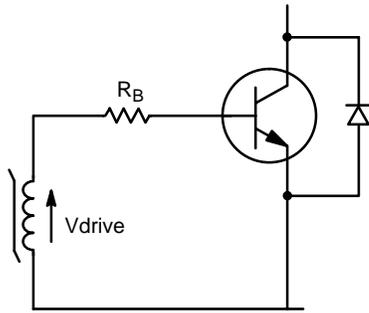


Figure 21.

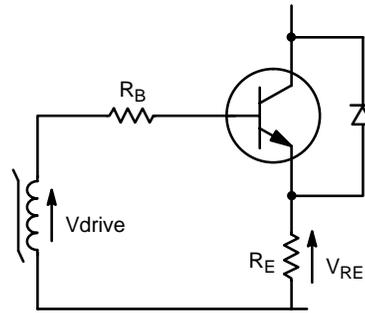


Figure 22.

CONCLUSION

Standard bipolar transistors are attractive in the lamp ballast field because of their price and performances; nevertheless, designing bipolar transistors requires a certain skill, mainly due to t_{si} variation from lot to lot.

The new D2 family combines cost advantage and simplifies the design.

The coming of the D2 series allows the saving of PCB space because the freewheeling diode is built in and some drive components can be removed. Due to the specific way the diode is laid out, an anti-saturation network is integrated, providing significant advantages such as extremely tight t_{si} distribution (typically: ± 80 ns), inexpensive designs, high operating speed (up to 100 kHz, under accurate biases conditions), lower power dissipation, and proportional drive-enabling variable load.

The D2 family of application specific transistors enables the design of bipolar-based fluorescent converters. They are not only cost effective, but simple and straightforward as well.

SELECTOR GUIDE

DEVICE TYPE	V_{CEO}	V_{CES}	I_{Cmax}	PACKAGE
BUD44D2	400 V	700 V	2 A	DPAK
MJD18002D2	450 V	1000 V	2 A	DPAK
BUL44D2	400 V	700 V	2 A	TO220
BUL45D2	400 V	700 V	5 A	TO220
MJE18002D2	450 V	1000 V	2 A	TO220
MJE18004D2	450 V	1000 V	5 A	TO220
MJE18604D2	800 V	1600 V	2 A	TO220

References

1. ON Semiconductor, AN873/D: Understanding Power Transistor Dynamic Behavior.
2. ON Semiconductor, AN875/D: Power Transistor Safe Operating Area.
3. ON Semiconductor, AN1543/D: Electronic Lamp Ballast Design.

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer.

PUBLICATION ORDERING INFORMATION

Literature Fulfillment:

Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: ONlit@hibbertco.com

N. American Technical Support: 800-282-9855 Toll Free USA/Canada

JAPAN: ON Semiconductor, Japan Customer Focus Center
2-9-1 Kamimeguro, Meguro-ku, Tokyo, Japan 153-0051
Phone: 81-3-5773-3850

ON Semiconductor Website: <http://onsemi.com>

For additional information, please contact your local Sales Representative.