

# ON Semiconductor

## Is Now

# onsemi™

To learn more about onsemi™, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

---

**onsemi** and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.

## Offline LED Driver



ON Semiconductor®

<http://onsemi.com>

### APPLICATION NOTE

This application note provides a simple approach to designing an LED driver utilizing the ON Semiconductor NCP1014 self-supplied monolithic switcher. The easy-to-follow, step-by-step procedure guides the user into designing the different blocks that constitute the power supply, mainly the input block, the power stage, the magnetics, the snubber, the output block, and the feedback loop. The circuit diagram, bill of material, and PCB layout are also included at the end of the application note. This power supply is specifically designed to drive three LED's. It meets IEC and UL requirements. EMI is minimal and a 70% achievable efficiency or greater is possible.

The NCP1014 integrates a fixed-frequency current mode controller and a 700 V MOSFET. This device is housed in a PDIP-7 package and features soft-start, frequency jittering, short-circuit protection, skip-cycle, and a dynamic self-supply (no need for an auxiliary winding).

#### Design Parameters

The first step in designing a power supply is to define and predetermine the input and output parameters.

Universal Input Voltage Range:

$$V_{ac(min)} = 85 \text{ Vac}, V_{ac(max)} = 265 \text{ Vac}$$

Output Specifications:

$$V_{out} \approx 11.75 \text{ V} \pm 2\%, I_{out} = 350 \text{ mA}$$

Input Power:

$$P_{in} = \frac{P_{out}}{\eta}, \text{ where } \eta = 78\% \text{ estimated efficiency}$$

$$P_{out} = V_{out} \cdot I_{out} = 11.75 \cdot 0.350 \approx 4.1 \text{ W}$$

$$\therefore P_{in} = \frac{4.1}{0.78} = 5.25 \text{ W}$$

DC Rail Voltages at Low Line and High Line:

$$V_{dc(min)} = V_{ac(min)} \cdot \sqrt{2} = 85 \cdot \sqrt{2} = 120 \text{ Vdc}$$

$$V_{dc(max)} = V_{ac(max)} \cdot \sqrt{2} = 265 \cdot \sqrt{2} = 375 \text{ Vdc}$$

Average Input Current:

$$I_{in(avg)} = \frac{P_{in}}{V_{dc(min)}} \approx \frac{5.25}{120} \approx 44 \text{ mA}$$

Input Peak Current:

$$I_{peak} = 5 \cdot I_{in(avg)} = 220 \text{ mA}$$

#### Circuit Description

##### Input Block

The input block of the power supply consists of a fuse, an EMI filter, a diode bridge rectifier, and an input bulk capacitor.

##### Fuse

The fuse F1 is protecting the circuit from current surges occurring at turn on. In this application, F1 is rated for 2.0 A, 125 Vac.

##### EMI Filter

The EMI filter suppresses common mode and differential mode noise and is very dependent upon board layout, component selection, etc. An X capacitor C1 and a common mode choke L1 are placed across the AC lines to attenuate differential mode noise, see Figure 1. The EMI inductor is slowing down any transient voltage surge to reduce high frequency noise. Both the capacitor and choke should be placed before the diode bridge and as close to the ac line input as possible to minimize RFI.

##### Diode Bridge Rectifier

In order to choose the right diode bridge rectifier, the values of the forward and surge currents and DC blocking voltage must be considered. The surge current can reach values up to five times that of the average input rms current. It is therefore necessary to select a rectifier capable of handling such large currents.

DC Blocking Voltage is calculated at high line:

$$V_R \geq V_{dc(max)} = 375 \text{ Vdc}$$

Forward Current:

$$I_F \geq 1.5 \cdot I_{in(avg)} = 1.5 \cdot 0.044 = 66 \text{ mA}$$

Surge Current:

$$I_{FSM} \geq 5 \cdot I_F = 5 \cdot 0.066 = 330 \text{ mA}$$

**Input Bulk Capacitor**

The purpose of the input bulk capacitor C2 is to hold up the rectified line voltage and also to filter out common mode noise. It is placed between the bridge rectifier output and ground. The size of the bulk capacitor depends on peak rectified input voltage and the ripple voltage magnitude. A larger capacitor will lower the ripple voltage on the dc input line, but will induce a larger surge current when the supply is powered up. Assuming a ripple magnitude of about 20% of the peak rectified voltage at low line, C<sub>bulk</sub> can then be calculated using:

$$C_{bulk} = \frac{P_{in}}{f_{ac} \cdot (V_{peak(min)}^2 - V_{in(min)}^2)}$$

$$= \frac{4.1}{60 \cdot (120^2 - 96^2)} = 13 \mu F$$

In this case, we chose a 33 μF aluminum electrolytic due to availability.

**Power Stage**

At the heart of the power stage is the ON Semiconductor NCP1014. The NCP1014 is a current-mode controller with a high voltage power MOSFET in a monolithic structure. The NCP1014 features soft-start, frequency jittering, short circuit protection, a maximum peak current set point, and a dynamic self-supply. It operates in skip-cycle mode below ¼ of the maximum peak current limit, thus no acoustic noise is present. For more information on this device, please go to [www.onsemi.com](http://www.onsemi.com).

**Magnetics Calculations**

The next step is the design of the flyback transformer. The design of the magnetics block is the most important and delicate part of the whole design process because it will determine how well the power supply will perform. The flyback-mode transformer functions by first conducting current in the primary winding, thus storing energy in the core of the transformer. The core energy is then transferred to the secondary winding when the primary side is turned off. The core and bobbin are standard EFD20 sizes.

In order for the regulator to operate in discontinuous mode under worse case conditions and to maximize power, the maximum on time is 48% of the full period, therefore the maximum primary inductance is calculated based on a maximum duty cycle of 48%. Using a larger inductance than

calculated will cause the power supply output to fall out of regulation.

- Let  $f_{op} = 100 \text{ kHz}$  (operating frequency)
- $\delta_{max} = 48\%$  (maximum duty cycle)
- $V_{in(min)} = V_{dc(min)} - 20\% \approx 96 \text{ V}$   
(minimum input voltage)
- $P_{out} = 4.1 \text{ W}$  (output power)
- $\eta = 78\%$  (estimated efficiency)
- $I_{peak} = 220 \text{ mA}$  (input peak current)

$$L_{pri} = \frac{V_{in(min)} \cdot \delta_{max}}{I_{peak} \cdot f_{op}} = \frac{96 \cdot 0.48}{0.220 \cdot 100 \text{ kHz}} = 2.09 \text{ mH}$$

Primary to secondary turns ratio:

$$\frac{N_{pri}}{N_{sec}} = \frac{V_{in(min)} \cdot \delta_{max}}{V_{out} + V_F \cdot (1 - \delta_{max})}$$

$$= \frac{120 \cdot 0.48}{11.75 + 0.875 \cdot (1 - 0.48)} \approx 7 \text{ turns}$$

An easy way to check if the power capability of the transformer is large enough to supply the output is with the following equation:

$$P_{in(core)} = \frac{L_{pri} \cdot I_{peak}^2}{2} \cdot f_{op} > P_{out}$$

$$P_{in(core)} = \frac{2.09 \text{ mH} \cdot 0.220^2}{2} \cdot 100 \text{ kHz} = 5.05 > 4.1 \text{ W}$$

**Input Snubber**

Because of the high dv/dt characteristic of the power transistor drain voltage and of the transformer leakage inductance, voltage spikes and ringing occur at the drain when the power switch is turned off. Resistor R1, C3, D5 compromise an RCD snubber. In parallel to the primary winding are R2 and C4 which compromise an RC ringing damper which slows down the dv/dt and reduces the peak voltage therefore decreasing the ringing due to high frequency noise. Since  $i = C \cdot \frac{dv}{dt}$ , increasing the capacitance will also reduce the magnitude of the voltage ripple. The snubber and ringing damper act together to protect the IC from voltage transients greater than 700 V and reduce radiated noise.



## AND8136/D

**Table 1. Bill of Materials**

Ref.	Component Value	Qty	Part Number	Manufacturer
IC1	450 mA, 100 kHz, PDIP-7	1	NCP1014AP100	ON Semiconductor
IC2	Opto Coupler, Dip	1	SFH615A-4	Isocom
IC3	1.25 V Shunt Reg., TO-92	1	TLV431ALP	ON Semiconductor
D1-4	1.0 A, 800 V, Gen Purp	4	1N4006	ON Semiconductor
D5	1.0 A, 600 V, Ultrafast	1	MUR160	ON Semiconductor
D6,D10	1.0 A, 200 V, Ultrafast	1	MUR120	ON Semiconductor
D7	5.1 V, 5.0 W, Zener	1	1N5338B	ON Semiconductor
D8	1.0 V, Switching diode	1	MMSD914	ON Semiconductor
D9	47 V, 3.0 W, Zener	1	1N5941B	ON Semiconductor
D11,12,13	4.7 V, 3.0 W, Zener	3	1N5917	ON Semiconductor
T1	Flyback Transformer	1	31842	Midcom
L1	Choke, Common Mode, 10 mH	1	40479	Midcom
C1	0.1 mF, film, radial	1	R46104M275BIS	Nissei
C2	33 mF, 400 V, radial	1	KME400VB33RM16X31LL	United Chem-Con
C3	220 pF, 1 kV, 10%, disc	1	NCD221K1KVY5F	NIC Components
C4	47 pF, 1 kV, 10%, disc	1	NCD470K1KVSL	NIC Components
C5	22 uF,radial	1	ECA-1HHG220	Panasonic
C6	100 uF,radial	1	ECA-1HHG101	Panasonic
C7	0.001mF, ceramic	1	SR155C102KAA	AVX
C8	10 mF, 16 V, 20%, radial	1	SME16VB10RM5X11LL	United Chem-Con
C13*	1 mF, 16 V, radial	1	SR215E105MAA	AVX
C9	100 pF, 1 kV, 10%, disc	1	NCD101K1KVY5F	NIC Components
R1	91 kW, 1 W	1	RS-1W-91K-5	SEI
R2	2.2 kW, 1/2 W, 5%	1	CF-1/2W-2.2K-5	SEI
R3	1 kW, 1/4 W, 5%	1	CF-1/4W-1k-5	SEI
R4	2.2 kW, 1/4 W, 5%	1	CF-1/4W-2.2K-5	SEI
R4*	2 kW, 1/4 W, 5%	1	CF-1/4W-2K-5	SEI
R5	100,1/4,5%	1	RN-1/4W-T1-100-5	SEI
R7*	0.5 W, 1 W	1	RS-1-R5-5TR	SEI
R8*	1.2 W, 1 W	1	RS-1-1R2-5TR	SEI
R9*	22 W, 1/4 W, 5%	1	CF-1/4W-22R-5	SEI
R10*	220 W 1/4W, 5%	1	CF-1/4W-221-5	SEI
R6	3.6,1W,5%	1	CF-1W-3.6-5	SEI
LED1-3	Luxeon Star	3	LXHL-MW1C	Luxeon
F1	2A, axial	1	251002TR1	LittleFuse
Connector 1		1	1715035	Phoenix Contact

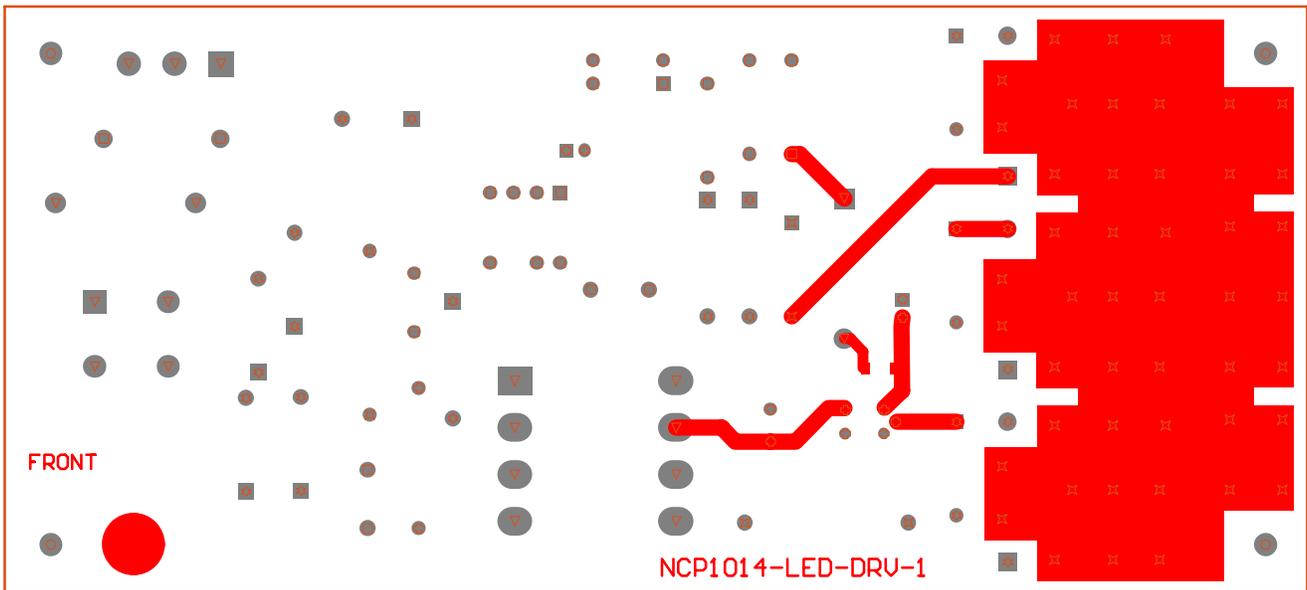


Figure 2. PCB Metal Layer (front)

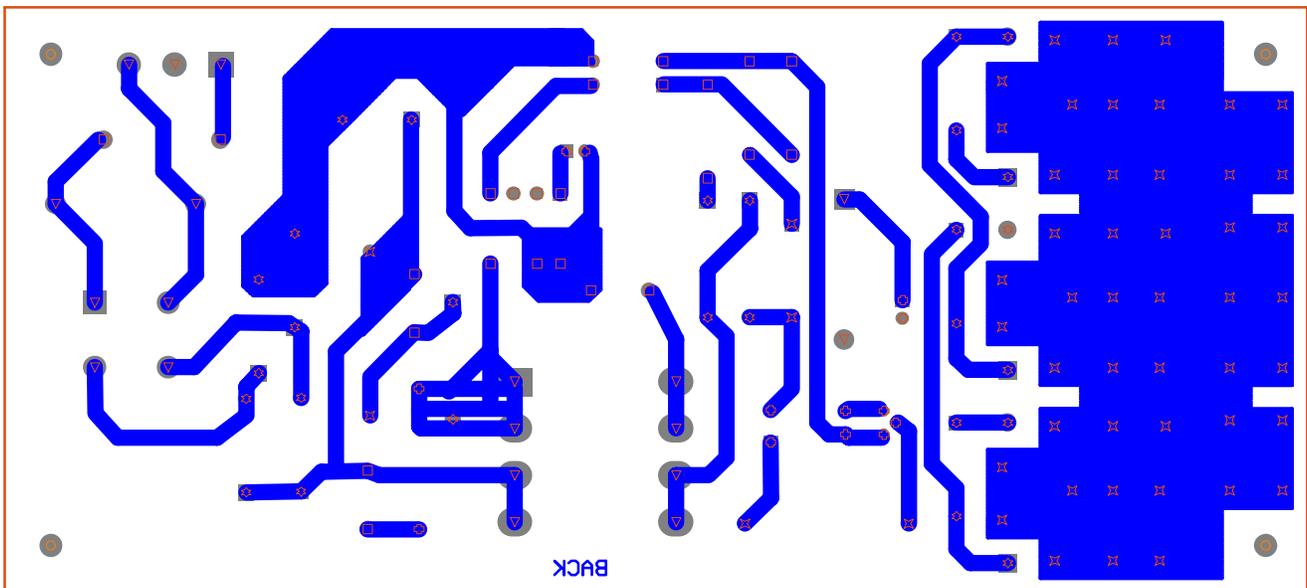


Figure 3. PCB Metal Layer (back)

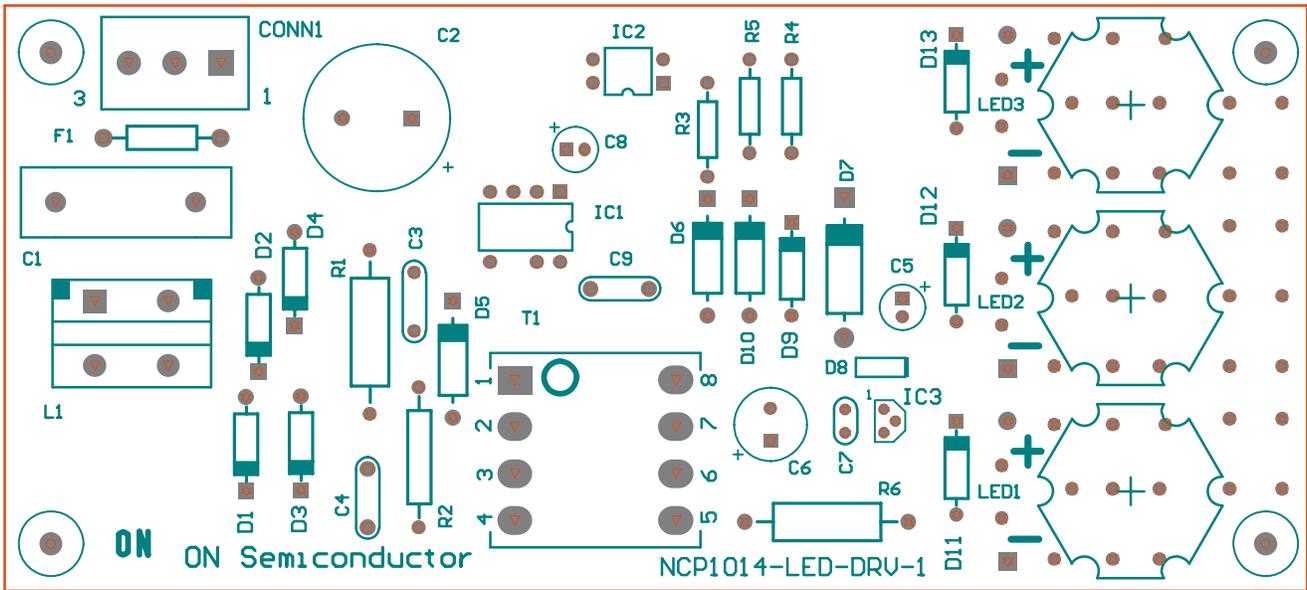


Figure 4. PCB Silk Screen

References

1. Brown, Marty, *Power Supply Cookbook*, Butterworth-Heinemann, 1994.
2. Pressman, Abraham I., *Switching Power Supply Design, Second Edition*, McGraw-Hill, 1998.
3. Motorola, Inc., *Handling EMI in Switch Mode Power Supply Design*, AN-SMPS-EMI, Motorola, Inc., 1998.
4. NCP1014 Datasheet, ON Semiconductor, [www.onsemi.com](http://www.onsemi.com)
5. Spangler, J., Hayes, L., AND8024 Application Note, ON Semiconductor, [www.onsemi.com](http://www.onsemi.com)

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

**LITERATURE FULFILLMENT:**  
 Literature Distribution Center for ON Semiconductor  
 P.O. Box 61312, Phoenix, Arizona 85082-1312 USA  
**Phone:** 480-829-7710 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 480-829-7709 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free USA/Canada

**Japan:** ON Semiconductor, Japan Customer Focus Center  
 2-9-1 Kamimeguro, Meguro-ku, Tokyo, Japan 153-0051  
**Phone:** 81-3-5773-3850

**ON Semiconductor Website:** <http://onsemi.com>

**Order Literature:** <http://www.onsemi.com/litorder>

For additional information, please contact your local Sales Representative.