



Programming the Hysteresis Voltage Of Universal Voltage Monitors MC34161, MC33161 and NCV33161

Prepared by: Cimiy Chan
ON Semiconductor

APPLICATION NOTE

Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
MC34161 MC33161 NCV33161	Universal Voltage Monitor	N/A	N/A	N/A	N/A

Circuit Description

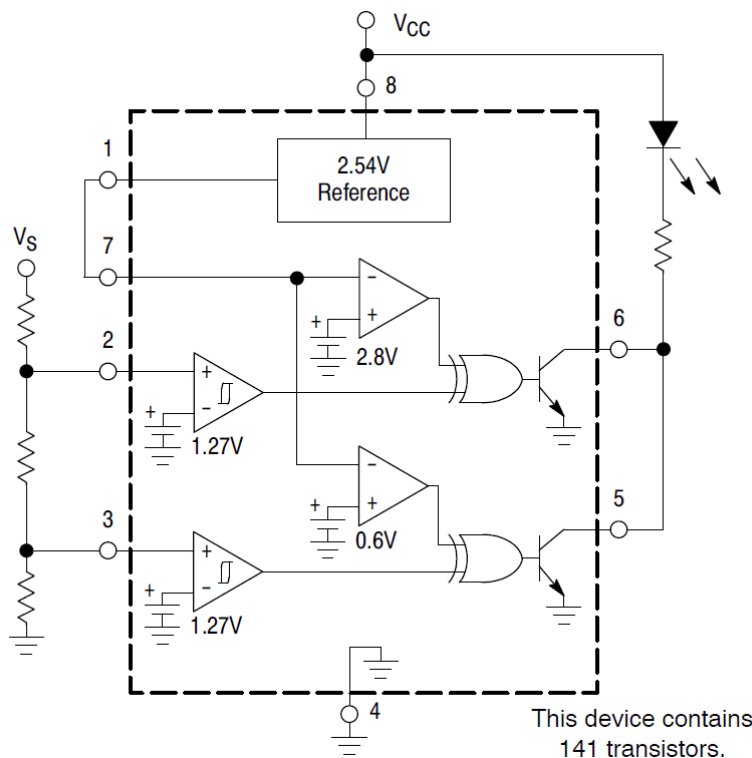


Figure 1. General Block Diagram of MC34161/MC33161

The Figure 1 shows the basic block diagram of MC34161/MC33161. It can be used for wide variety of voltage sensing application. They offer the circuit designer an economical solution for positive and negative voltage detection. The circuit consists of two comparators with hysteresis, a unique mode select input for channel programming, a output of 2.54 V reference, and two open collector outputs capable of sinking in excess of 10 mA.

Most of the comparators for the voltage monitoring provide hysteresis which is used for reducing the sensitivity to noise or a slowly moving input (low slew rate) signal. From the information of MC34161/MC33161 datasheet, the hysteresis is fixed to around 25 mV typically. However, this hysteresis value may not be enough for some applications for reducing the sensitivity

AND8426/D

to noise or comparator input voltage fluctuation. For example, at the automotive application, the noise level or voltage fluctuation (divided down to comparator input) may be as high as 300 mV – 400 mV during system operating. Therefore, a comprehensive and easy way to increase the hysteresis is definitely a need for the MC34161/MC33161 application under high noise level.

This document demonstrates the steps to show how to program the hysteresis voltage. And also, simulation results together with laboratory bench test verification will be shown.

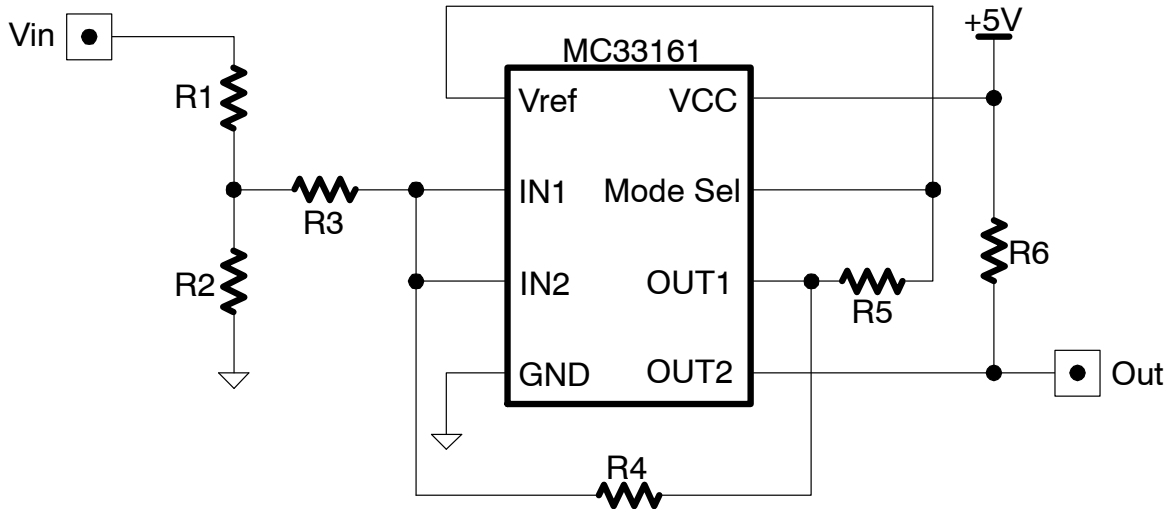


Figure 2. Schematic for Programming the Hysteresis Voltage

The configuration in the Figure 2 shows the circuit schematic for programming the hysteresis voltage. Basically, the hysteresis can be adjusted by varying R2, R3 and R4. Moreover, R1 and R2 are also used for the purpose of dividing down the external V_{IN} voltage. As mentioned before, R2, R3 and R4 can affect the amount of hysteresis voltage, it is necessary to find the easy way for the user to set the hysteresis voltage to fit for his own application. For R5 and R6, for typical application it sets as $R5 = 200k$ and $R6 = 10k$.

From the circuit simulation result, it is found that R3 variation (fix R1, R2 and R4) can provide very good linear relationship with hysteresis voltage and Figure 3 depicts it:

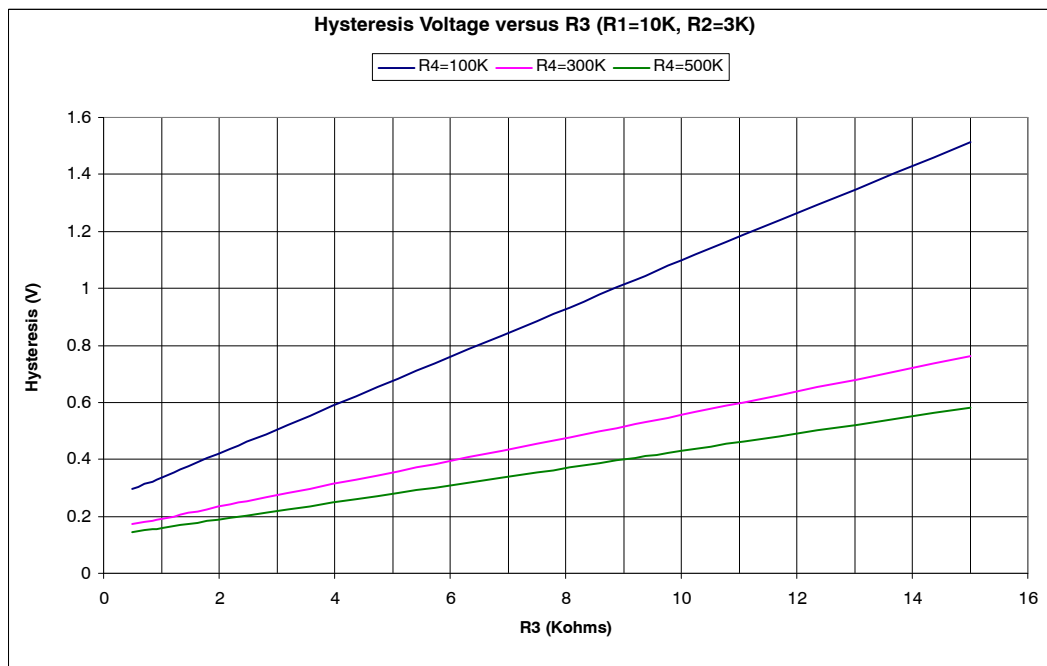


Figure 3. Chart to Show the Linear Relationship Between R3 and Hysteresis Voltage

AND8426/D

For given V_{IN+} and ΔV_{IN} (i.e. Hysteresis Voltage) with fixed R_2 and R_4 , we are required to evaluate R_1 and R_3 to complete the system configuration. The charts shown at next page will help us how to evaluate R_1 and R_3 . All the equations attached at charts are formed by the method of linear regression using known values which are acquired from simulation results.

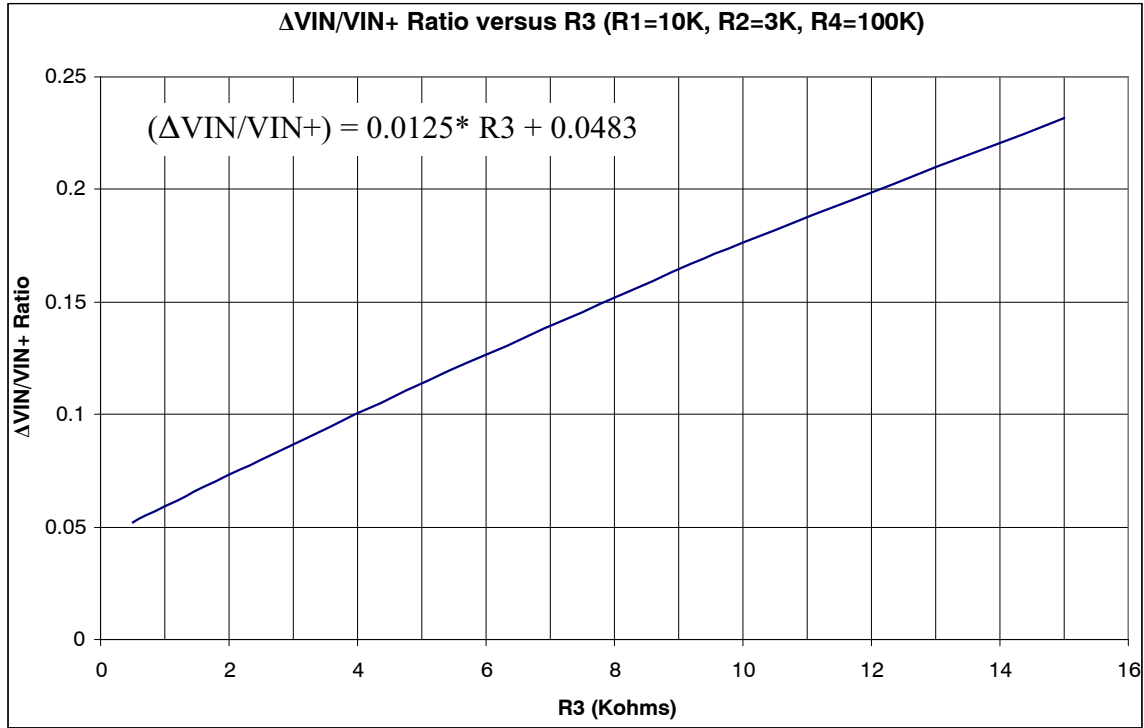


Figure 4. Chart for $\Delta V_{IN}/V_{IN+}$ Ratio versus R3

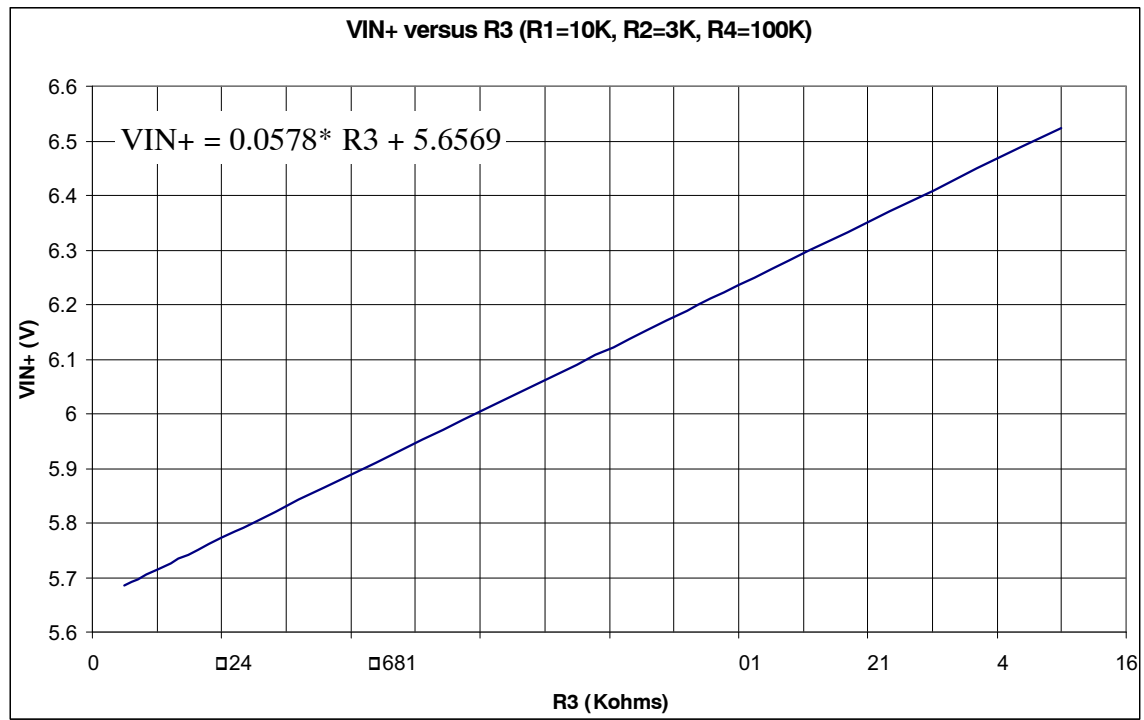


Figure 5. Chart for V_{IN+} versus R3

AND8426/D

Steps to Evaluate R1 and R3 for Given V_{IN+} and ΔV_{IN}

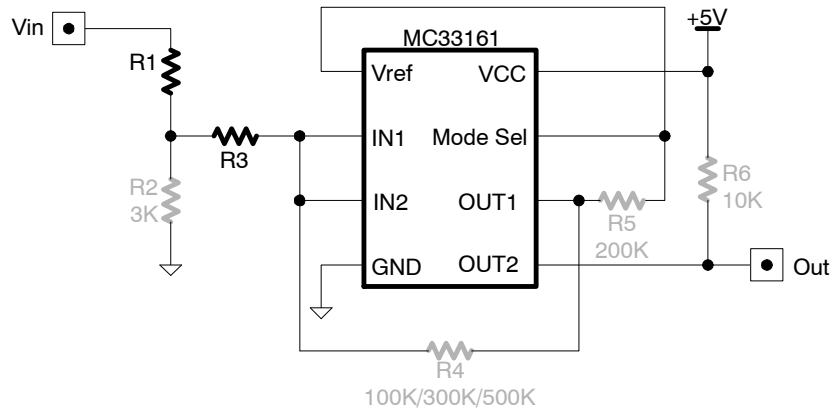


Figure 6. Circuit for Evaluation of R1 and R3

1. Fix $R_2 = 3k$, $R_4 = 100k/300k/500k$ (see step 3 for detail)
2. For given V_{IN+} and ΔV_{IN} , calculate the ratio of $\Delta V_{IN}/V_{IN+}$.
3. From Figure 4 chart with make use of the equation provided, evaluate R_3 based on the calculated $\Delta V_{IN}/V_{IN+}$. If R_3 is found to be negative, try to use $R_4 = 300k$ (use Figure 10) or $R_4 = 500k$ (use Figure 12) and repeat R_3 evaluation.
4. From Figure 5 (if $R_4 = 300k$, use Figure 11. If $R_4 = 500k$ use Figure 13) chart with make use of the equation provided, evaluate $V_{IN+'}$ based on the R_3 which is defined at step 3, say $V_{IN+'}$. It should be noted that the $V_{IN+'}$ value here is NOT the one that will be used, it is just for intermediate value to proceed the calculation.
5. Evaluate R_1' based on the formula: $(V_{IN+'}) * (R_1' + R_2) = (V_{IN+}) * (R_1 + R_2)$ where $R_1 = 10k$, $R_2 = 3k$.
6. So, R_1 (notate as R_1' at step 5), R_2 , R_3 and R_4 are evaluated.

Example

The customer wants to have the application of which Output is low when $V_{IN} = 3V$ and output is high when $V_{IN} = 2.75V$.

Step 1: Fix $R_2 = 3K$, $R_4 = 100k$

Step 2: $V_{IN+} = 3V$ and required hysteresis ΔV_{IN}
 $= 3 - 2.75$
 $= 0.25V$
 So the $(\Delta V_{IN}/V_{IN+})$ ratio $= 0.25 / 3$
 $= 0.0833$

Step 3: From the Figure 4 chart with make use of equation, we have
 $0.08333 = 0.0125 * R_3 + 0.0483$
 Therefore, $R_3 = (0.08333 - 0.0483)/0.0125$
 $R_3 = 2.803k$

Step 4: From the Figure 5 chart with make use of equation, we have
 $V_{IN+'} = 0.0578 * 2.803 + 5.6569$
 $V_{IN+'} = 5.819V$

Step 5: Evaluate R_1 by the formula mentioned at step 5,
 $5.819 * (R_1 + 3) = 3 * (10 + 3)$
 $R_1 = 3.702k$

So, the system will give $V_{IN+} = 3V$ with $\Delta V_{IN} = 0.25V$ for $R_1 = 3.702k$, $R_2 = 3k$, $R_3 = 2.803k$, $R_4 = 100k$.

AND8426/D

Validation by PSPICE Simulation

Now, we put those resistor values into PSPICE for functional validation.

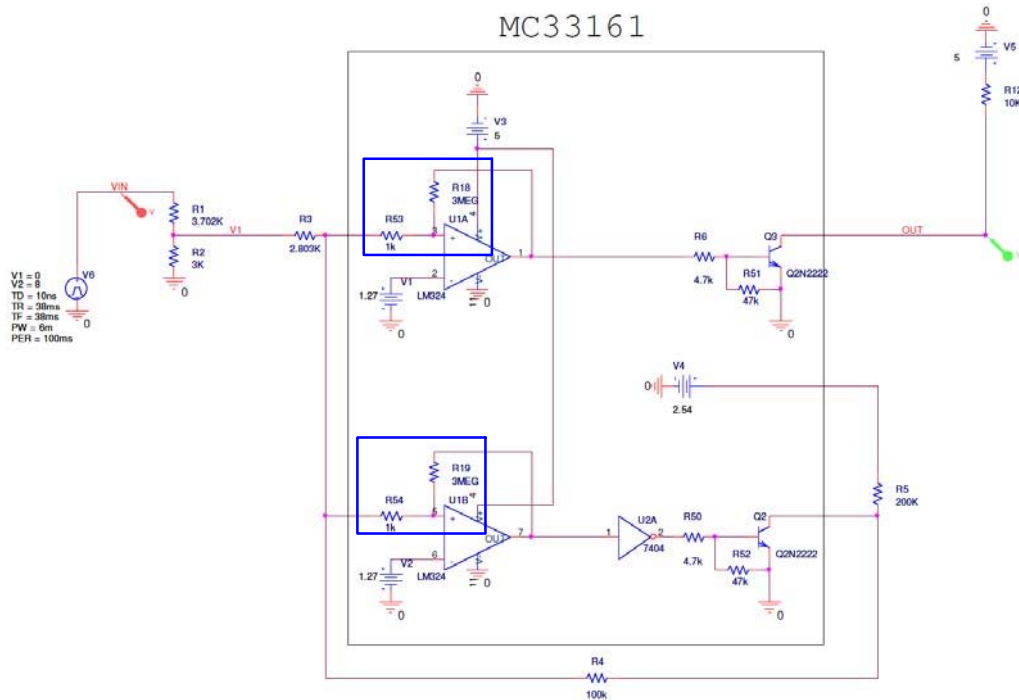


Figure 7. MC33161 PSPICE Schematic Model

Note: For the comparators portion, LM324 (U1A/U1B), R18(R19) and R53(R54) are used to provide 25 mV hysteresis which is the “intrinsic” amount per datasheet quoted. And input characteristics of LM324 is quite similar to those of real MC33161.

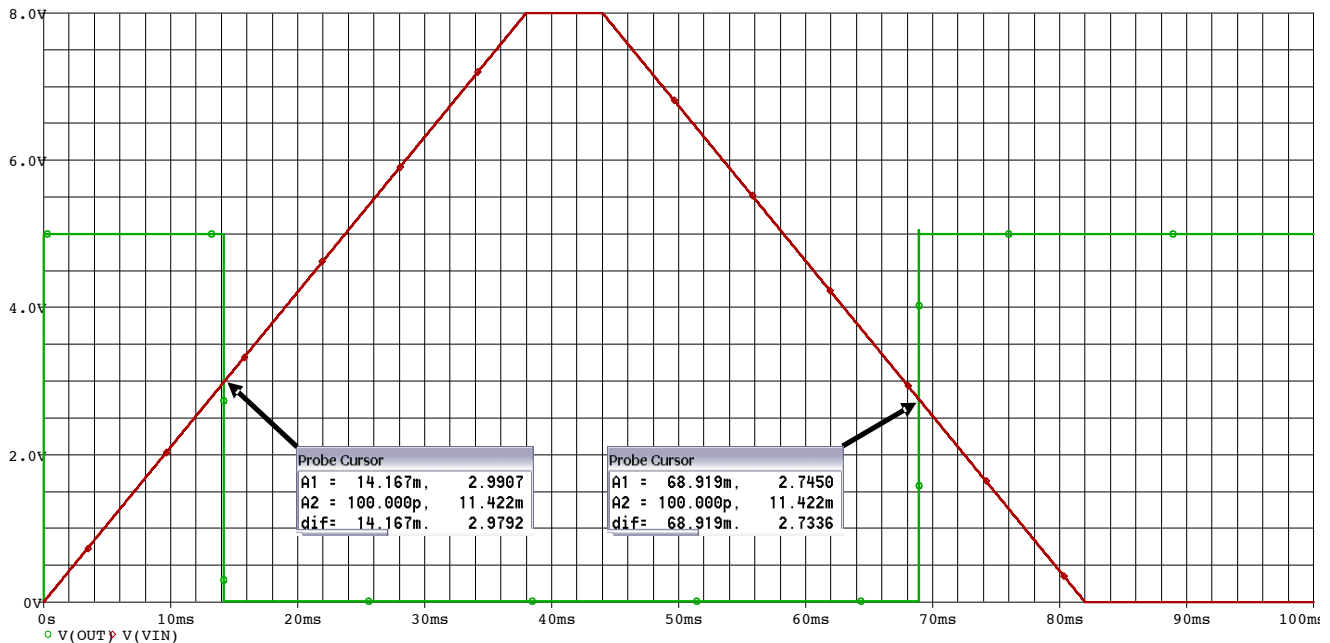


Figure 8. Simulation Result ($V_{IN+} = 2.9907\text{ V}$, $V_{IN-} = 2.7450\text{ V}$, $\Delta V_{IN} = 2.9907 - 2.7450 = 0.2457\text{ V}$)

So, the simulation result is consistent with theoretical calculation.

Validation by Laboratory Evaluation

Recall the resistor sets R1 to R4

R1 = 3.702k

R2 = 3k

R3 = 2.803k

R4 = 100k

At laboratory, the following resistor values are used:

R1 = 3.6k + 100 Ω = 3.70k

R2 = 3k

R3 = 2.7k + 100 Ω = 2.80k

R4 = 100k

All resistors are tolerance 1%

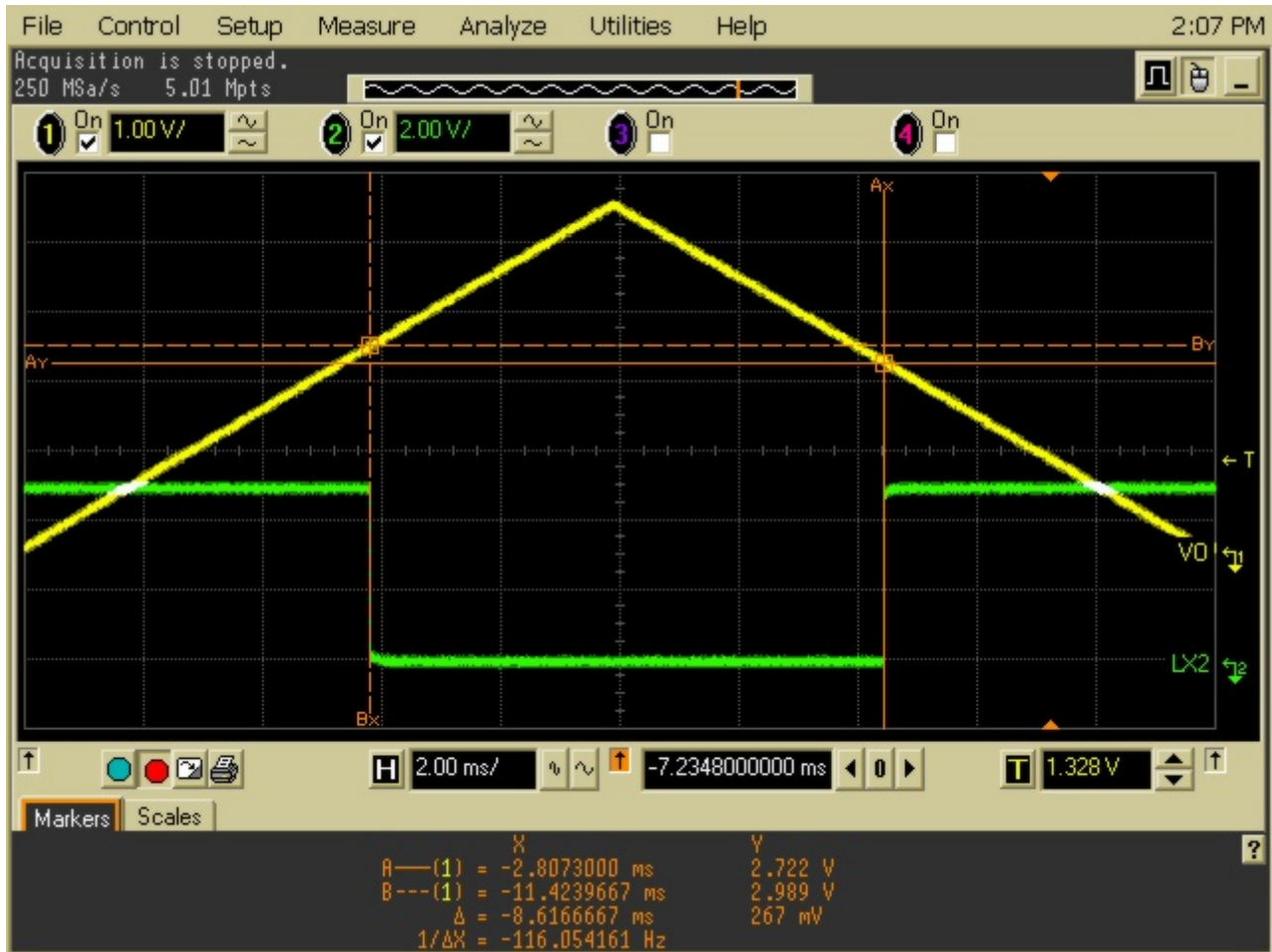


Figure 9. Scope Capture ($V_{IN+} = 2.989$ V, $V_{IN-} = 2.722$ V, $\Delta V_{IN} = 2.989 - 2.722 = 0.267$ V)

So the evaluation result in laboratory bench is also consistent with theoretical calculation.

Cautions For Selection of Resistor R3 to R4

1. R3 should be used lower than 15k, otherwise there will have some non linear behavior with either V_{IN+} or $\Delta V_{IN}/V_{IN+}$
2. R4 should be used higher than 100k.

The following charts provide V_{IN+} and $\Delta V_{IN}/V_{IN+}$ versus R3 for R4 = 300k and R4 = 500k. Those may be used if $\Delta V_{IN}/V_{IN+}$ are too small for R4 = 100k configuration.

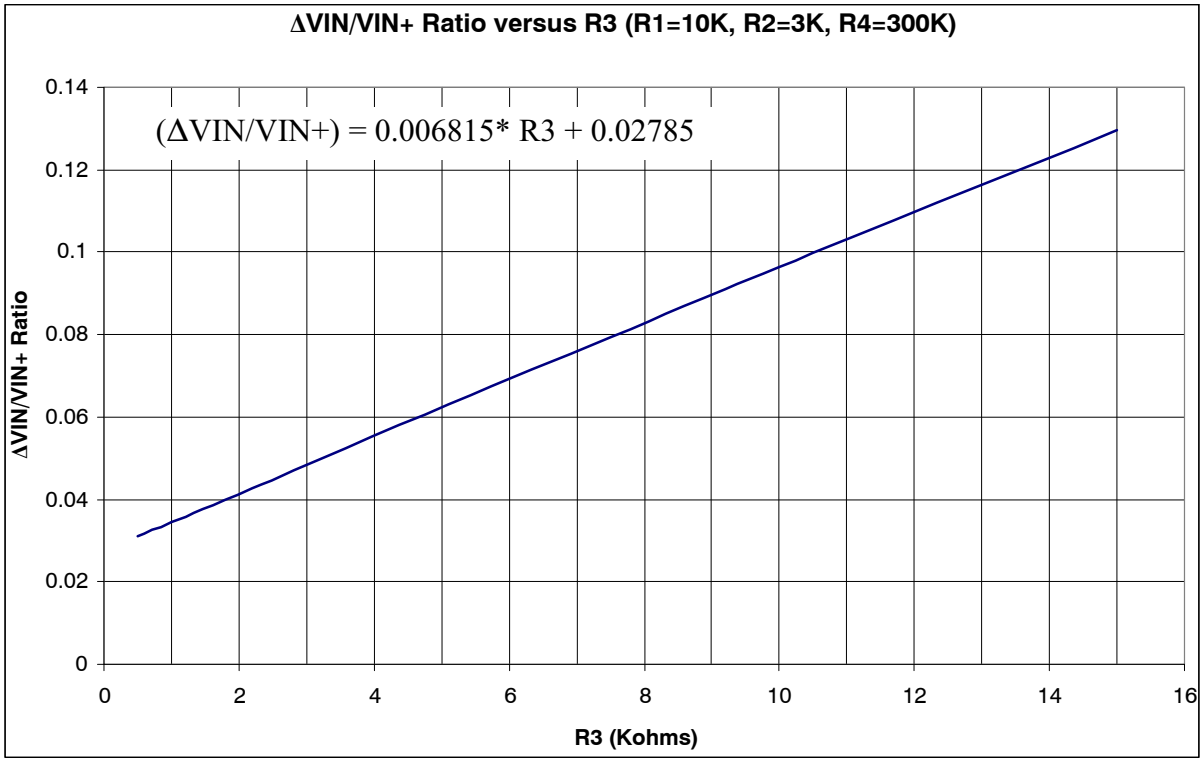


Figure 10. Chart for $\Delta V_{IN}/V_{IN+}$ Ratio versus R3 (R4 = 300k)

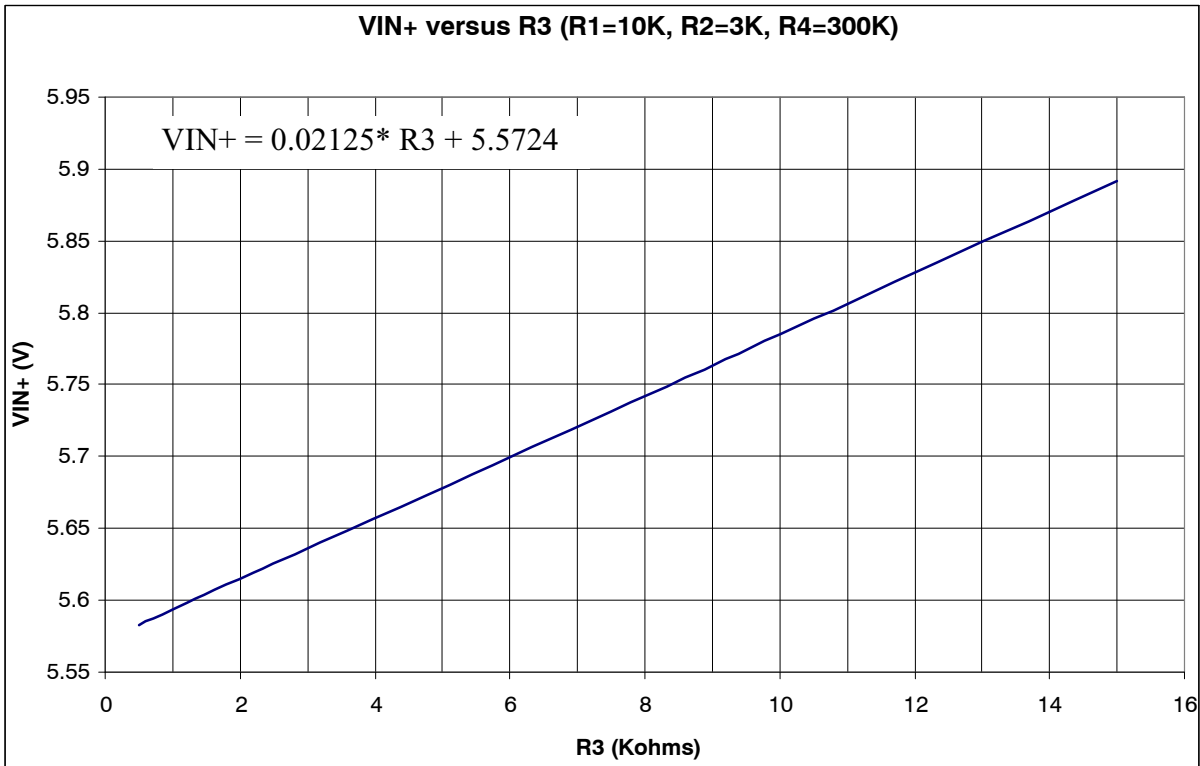


Figure 11. Chart for V_{IN+} versus R3 (R4 = 300k)

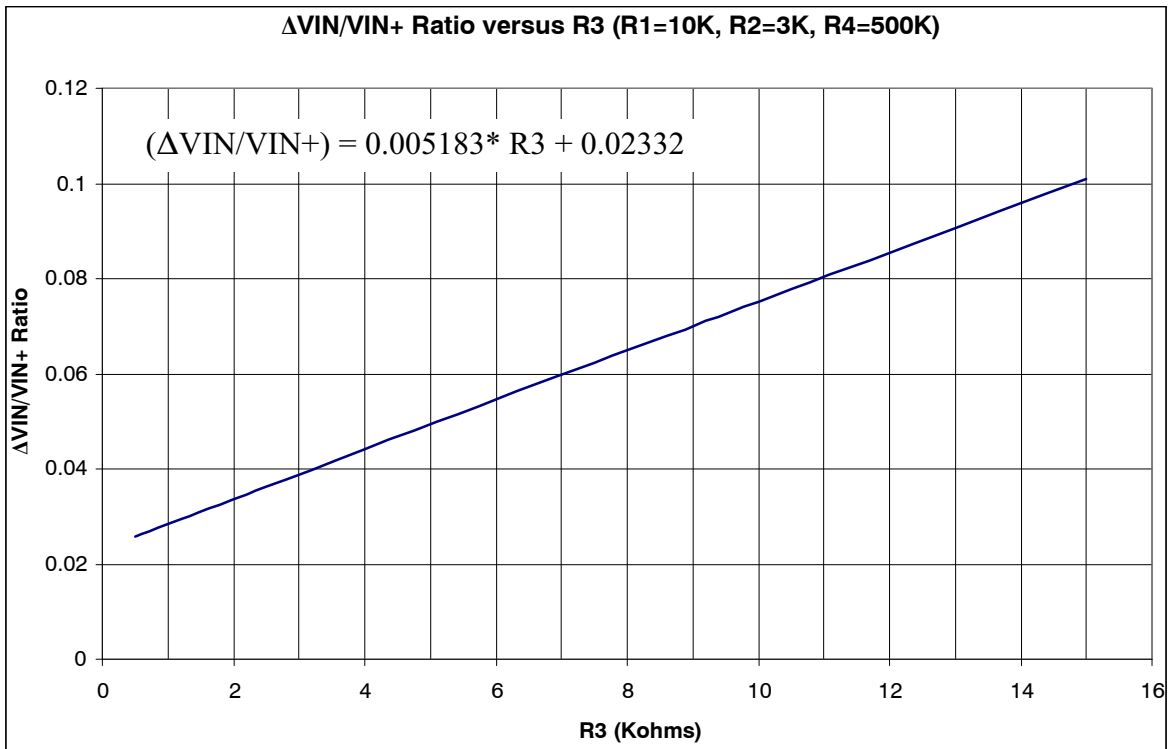


Figure 12. Chart for $\Delta V_{IN}/V_{IN+}$ Ratio versus R3 (R4 = 500k)

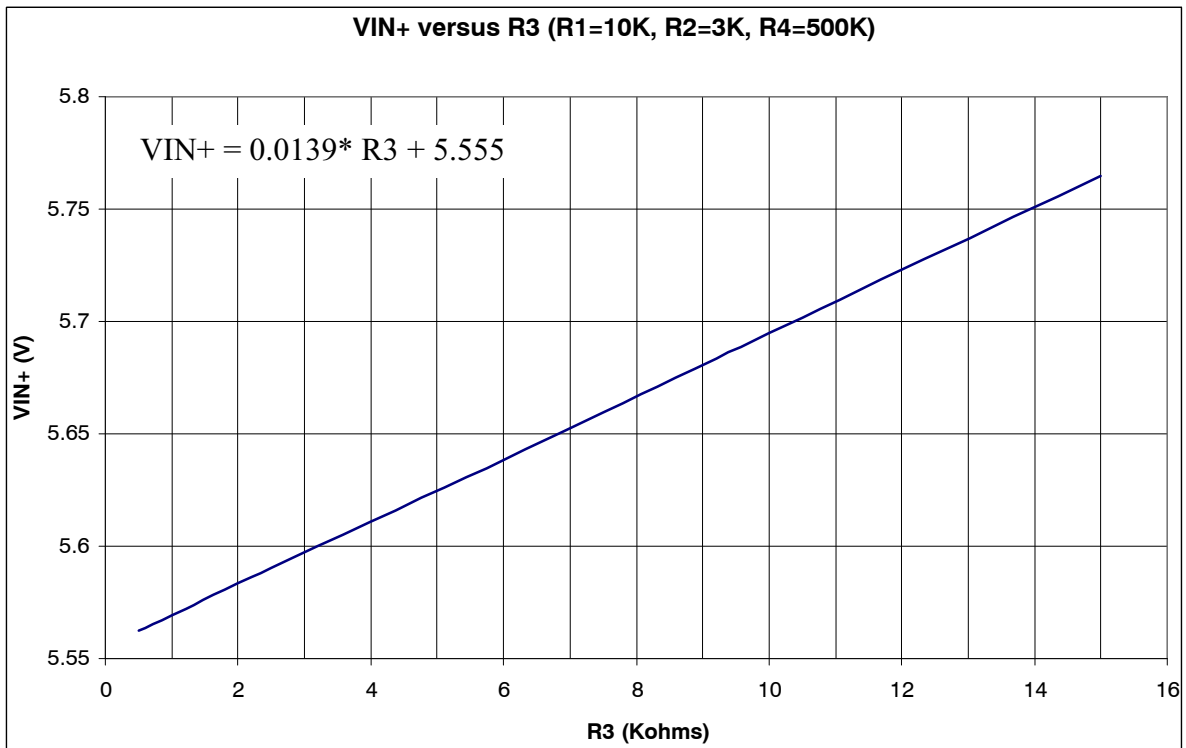


Figure 13. Chart for V_{IN+} versus R3 (R4 = 500k)

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5773-3850

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative