

# ON Semiconductor

## Is Now

# onsemi™

To learn more about onsemi™, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

---

**onsemi** and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.

# Performance Comparison of 1200 V SiC MOSFET and Si IGBT Used in Power Integrated Module for 1100 V Solar Boost Stage



ON Semiconductor®

[www.onsemi.com](http://www.onsemi.com)

## AND90082/D

### APPLICATION NOTE

#### Introduction

This application note compares the performance of two power integrated modules (PIMs) in the boost stage of an 1100 V solar inverter. One PIM used state-of-the-art silicon 1200 V IGBT (part number NXH100B120H3Q0 [1]) defined as PIM-IGBT and the other PIM used a new 1200 V SiC MOSFET (part number NXH40B120MNQ0 [2]) defined as PIM-SiC. These two PIMs utilized the same Q0 package technology and SiC Schottky boost diode. They are pin-to-pin compatible allowing customers to upgrade from Si IGBT to the SiC MOSFET version. Due to faster switching characteristics of the SiC device, this paper explains gate driver and PCB layout topics which must be considered when using fast switching devices like SiC MOSFETs.

#### Performance Comparison

For the design of a solar inverter, the critical operating conditions include:

- maximum solar panel input current
- inverter dc bus voltage
- dc inductor ripple
- budget of cooling system (forced air or convection cooling)

It is important to evaluate the highest junction temperature ( $T_j$ ) of the semiconductor device under all conditions, and guarantee they do not exceed the rated value in the datasheet. Users also prefer to operate as close as possible to the  $T_j$  limit (after allowing for a safety margin) to lower the overall cost/Watt. Loss and  $T_j$  simulation is a useful method to answer above questions. High temperature (for example 125°C) characteristic is more important than room temperature because designers must consider worst conditions while solar inverters work at full load and high environment temperature. In this paper, only high temperature data is considered.

Key performance comparison of Si IGBT and SiC MOSFET is shown in Table 1.

Until 2019, a common output current of a solar string was around 12 A. These two PIMs were designed for connecting two strings in parallel for a MPPT (maximum power point tracking) of 26 A. Table 1 shows current of 30 A which is a typical operating point. SiC has faster switching speed because of unipolar device nature (no turn off tail current) and smaller  $Q_g$ . Due to lower switching losses ( $E_{on}$  and  $E_{off}$ ), PIM-SiC has a significantly lower total loss compared with PIM-IGBT under the same operating conditions. Figure 1 shows a comparison of conduction loss and switching loss for the switches used in the two PIMs.

**Table 1. KEY PERFORMANCE COMPARISON OF SI IGBT AND SiC MOSFET**

Parameter	PIM-IGBT	PIM-SiC
Rated Current	50 A	38 A
Voltage Drop (30 A)	1.55 V	1.85 V
$E_{on}$ (30 A)	400 ( $\mu$ J)	240 ( $\mu$ J)
$E_{off}$ (30 A)	1730 ( $\mu$ J)	140 ( $\mu$ J)
$Q_g$ (0 to 15 V)	410 (nC)	80 (nC)
Gate Voltage	+15 V/-9 V	+20 V/-4 V
$R_{thjc}$ ( $^{\circ}$ C/W)	0.51	0.81
Cost	100%	180%

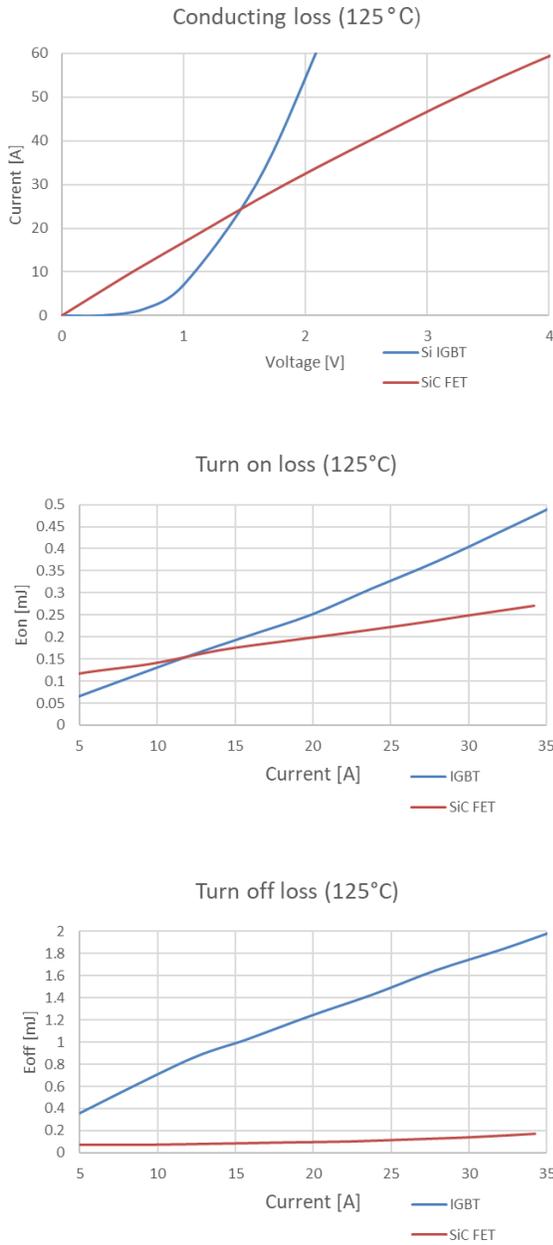


Figure 1. Comparison of Conduction Loss and Switching Loss

Table 2. SYSTEM PARAMETERS OF A TYPICAL SOLAR BOOST CONVERTER

Parameter	Value
PV Input Voltage/Current	500 V/25 A
Output DC Bus Voltage	800 V
Switching Frequency	16 kHz
Inductor	600 $\mu$ H
Module Case Temperature	95°C

System parameters of a typical solar boost converter using an IGBT solution are shown in Table 2. SiC MOSFETs are

more expensive than IGBTs due to a more complex manufacturing process. It is reasonable to design SiC MOSFET with a smaller die size. This smaller die area results in higher thermal resistance, which is not favorable for reducing  $T_j$ . Table 3 shows the power loss and  $T_j$  simulation results for a circuit using PIM-IGBT and PIM-SiC operating under the same conditions. The Si IGBT has significantly higher  $E_{off}$  due to slower  $dv/dt$   $di/dt$  and tail current. For conduction loss, the SiC MOSFET has lower  $V_{ds}$  when current is below cross point of 25 A due to unipolar nature.

Assumed the dc inductor has fix inductance value (no saturation), the switch current waveform is shown as the red line in Figure 2. PIM-IGBT and PIM-SiC have similar conducting loss and turn on loss in conditions given in Table 3. PIM-IGBT has much higher turn off losses than PIM-SiC. Gate driver parameters, such as gate resistance ( $R_g$ ), also have strong impact on  $E_{on}$  and  $E_{off}$ . Only  $R_g = 5 \Omega$  is discussed in this paper for simplifying the comparison.

Table 3. COMPARISON OF LOSS SIMULATION

Parameter	PIM-IGBT	PIM-SiC
Conducting Loss	13.33 W	12.17 W
Switching Frequency	16 kHz	16 kHz
Turn On Loss $E_{on}$	3.8 W	3.17 W
Turn Off Loss $E_{off}$	34.66 W	3.06 W
Total Loss	51.79 W	18.39 W
$T_j$ ( $T_c = 95^\circ\text{C}$ )	137.9°C	109.9°C

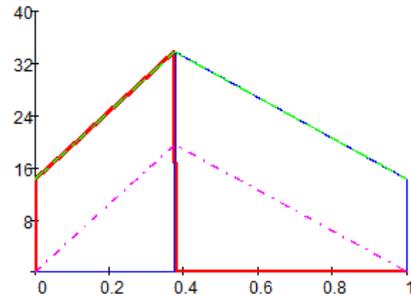


Figure 2. IGBT Current Waveform

System cost is one of the most critical considerations for a solar application. If a SiC solution is used, the PIM is more expensive. This is justified only if using a SiC solution reduces the cost of other parts of the inverter such as a lower cost inductor and a cheaper and lighter cooling system.

An optimal design of PIM-SiC increases switching frequency ( $f_{sw}$ ) to 40 kHz, so the inductor size is reduced to 1/3 as 200  $\mu$ H. Heatsink size is also reduced. Alternatively the heatsink size can be kept the same and the cooling is changed from forced air cooling to natural cooling. As a result of the reduction of heatsink size, the PIM case temperature is assumed to rise to 110°C whereas it was 95°C in the previous configuration.

Loss simulation results under these new conditions are shown in Table 4 and compared with the PIM-IGBT losses from the previous table. Even when operating at a higher frequency, the PIM-SiC solution has lower losses than the PIM-IGBT solution, indicating a higher system efficiency of SiC solution.

**Table 4. COMPARISON OF LOSS SIMULATION**

Parameter	Si IGBT	SiC MOSFET
Conduction Loss	13.33 W	13.6 W
Switching Frequency	16 kHz	40 kHz
Turn On Loss $E_{on}$	3.8 W	7.22 W
Turn Off Loss $E_{off}$	34.66 W	8.34 W
Total Loss	51.79 W	29.16 W
$T_j$	137.9°C ( $T_c = 95^\circ\text{C}$ )	133.6°C ( $T_c = 110^\circ\text{C}$ )

**Design Consideration**

Users have to pay attention at circuit design and layout while adopting SiC PIMs, because of their faster switching characteristics. A comparison of the switching speed of PIM-IGBT and PIM-SiC at maximum dv/dt and maximum di/dt is shown in Figure 3.


Place a low parasitic inductance film capacitor as close as possible to the module to make the following commuting loop as small as possible:

- film capacitor – SiC MOSFET – SiC diode

This reduces the inductance of that loop, and reduces the radiated EMI generated from that loop.

Figure 4 gave an example of the film capacitors (Wurth part# 890493427007CS) that were placed closely to pins of DC+ and DC-.

The gate driver positive bias voltage of SiC MOSFET is selected as +20 V. Higher voltage reduces conducting loss. This gives a 5 V margin to the maximum positive  $V_{gs}$  value is +25 V. Negative bias voltage of -4 V is selected which provides sufficient margin to maximum negative  $V_{gs}$  value of -15 V. The negative bias increases the cost of the gate driver but gave smaller  $E_{off}$  and less  $V_{gs}$  ringing during turn off. 2 W isolated dc-dc power supplies from Mornsun (QA01C +20 V/-4 V and QA151 +15 V/-8 V) were used here. Optocoupler FOD3120 [3] from ON Semiconductor provides galvanic isolation between control signal and power circuit. It has maximum 2.5 A peak output current. Because gate current goes as high as 5 A, BJT pairs of 2SA2016 and 2SC5569 [4] were used to buffer gate current up to 7 A.

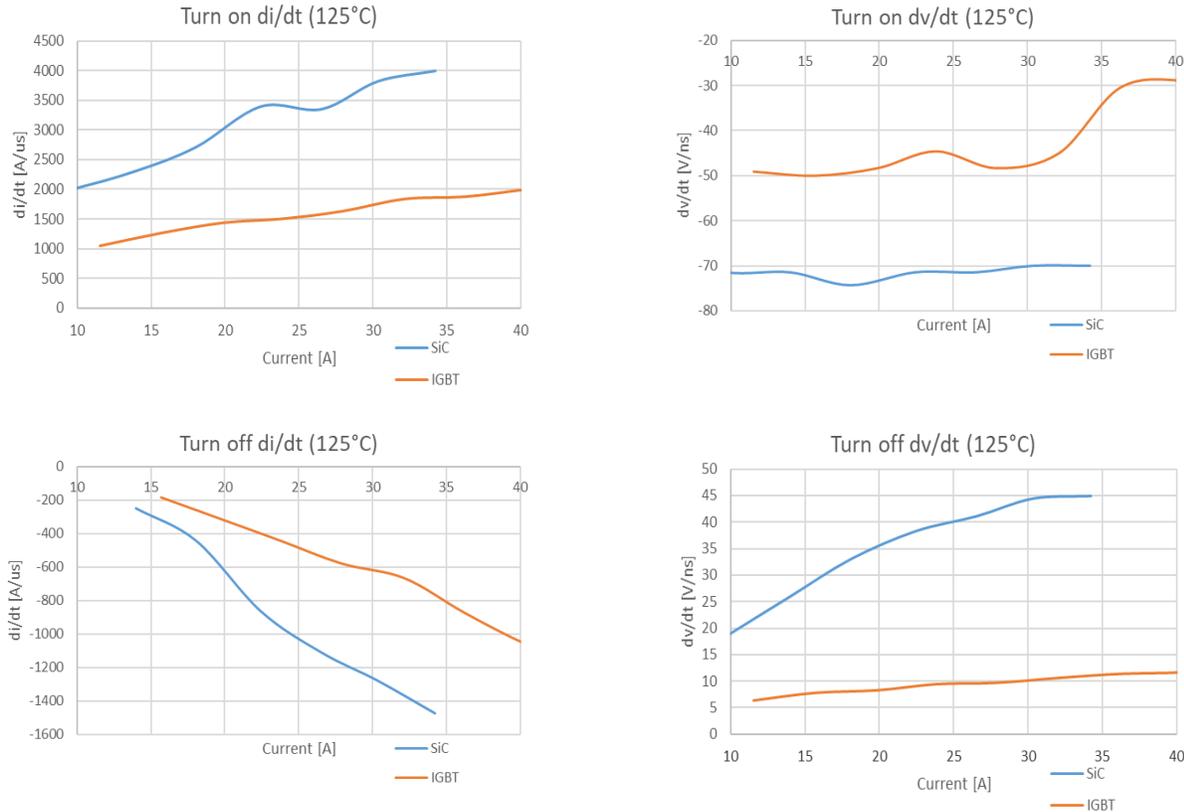

**Figure 3. Comparison of Switching Speed**

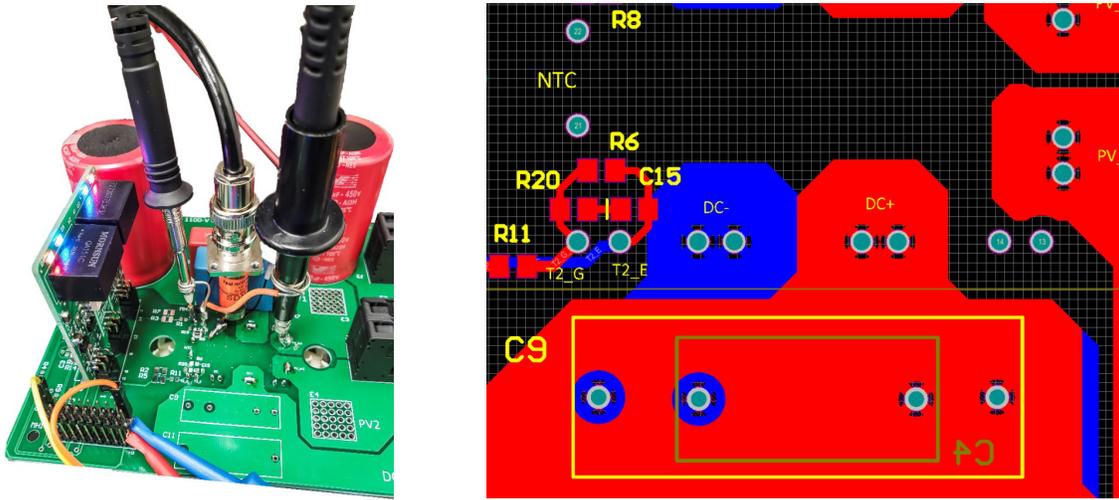


Figure 4. PCB Layout Example

Measuring voltage and current of SiC application becomes more challenging due to faster rising and falling time [5]. High bandwidth equipment and probing techniques are necessary as shown in Figure 4. The equipment used is shown in Table 5.

As shown in Figure 5, the rise time of SiC MOSFET is in range of ns. Based on  $T_r = 0.35/BW$  [6], bandwidth of all equipment must be over 300 MHz.

Long grounding loop of voltage probe should be avoided, otherwise unwanted loop inductance brings overshoot and ringing noise to scope waveform. Short ground leads were soldered here as an example. Differential voltage probe is not recommended here due to limited bandwidth (usually up to 200 MHz) and long grounding loop.

Rogowski coil (part# Iwatsu SS-665, 30 MHz bandwidth) is a preferred tool of measuring IGBT switching current, because it is very easy to assemble and disassemble into a target circuit. However, the fast speed of SiC device goes beyond bandwidth of normal Rogowski coil. For

comparison purpose, the same SiC MOSFET switching current was measured by both Rogowski coil and co-axial current shunt as shown in Figure 4. A comparison waveform is shown in Figure 5, the Rogowski coil filtered out some fast portion and induced a certain offset. Shunt resistor is able to precisely capture turn on current overshoot due to high  $dv/dt$  capacitance charge current of the commuting pair SiC schottky diode. When comparing IGBT current waveforms, there is no significant difference between shunt resistor and Rogowski coil due to IGBT's lower  $di/dt$  and  $dv/dt$ .

Table 5.

V <sub>gs</sub> Gate Voltage	Tek TPP1000 (1 GHz Bandwidth)
V <sub>ds</sub> Voltage	Tek P5100A (500 MHz Bandwidth)
I <sub>d</sub> Switching Current	T&M Research SDN-414-10 (0.1 Ω, 2 GHz Bandwidth)

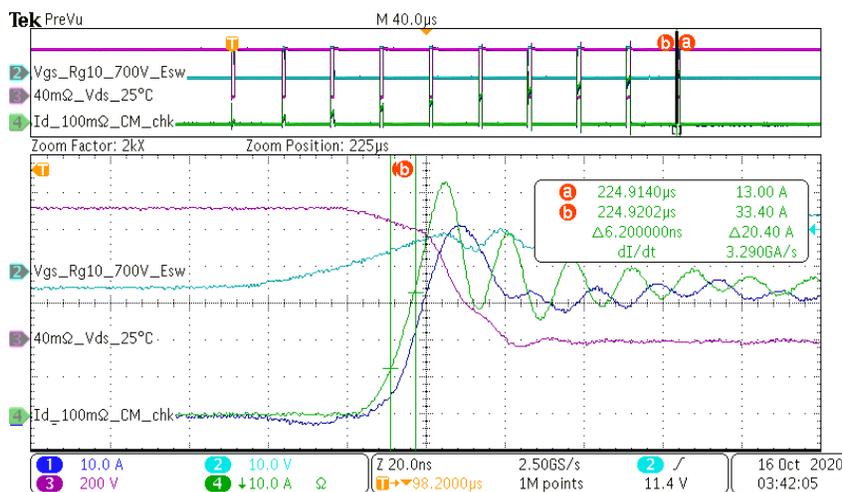


Figure 5. CH1: Current Measured by Rogowski Coil; CH2: V<sub>gs</sub> by Passive Probe TPP1000; CH3: V<sub>ds</sub> by Passive Probe P5100A; CH4: Current Measured by Co-axial Shunt

In order to reduce ringing of gate voltage  $V_{gs}$  during switching, it is recommend to keep the gate driver loop parasitic inductance  $L_g$  as small as possible. Actions shown in Figure 4 include: place gate driver IC closer to PIM, use

wider copper trace on PCB, place return trace close to active trace so magnetic cancelation reduces common inductance. A comparison of  $V_{gs}$  turn off waveform with optimized  $L_g$  is shown in Figure 6.

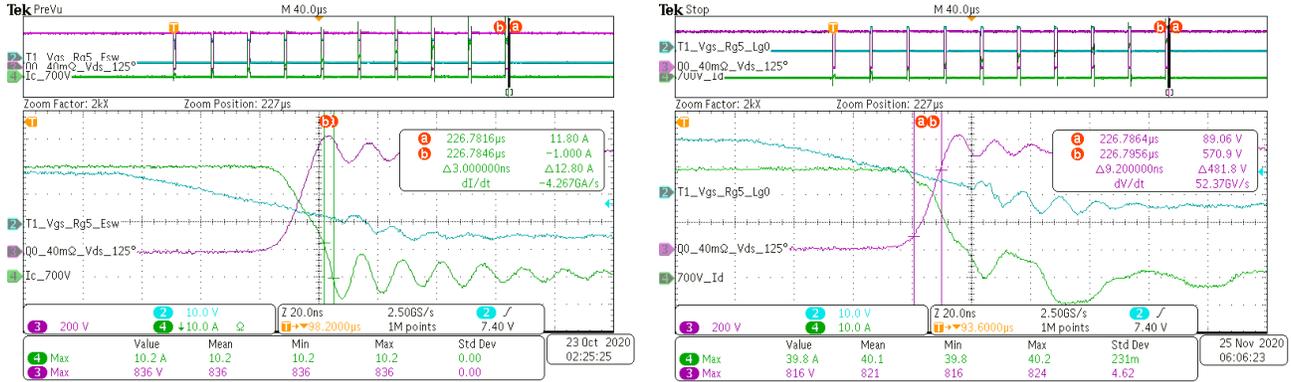


Figure 6. Optimized  $L_g$  at Left Figure (CH2:  $V_{gs}$ ) which has less Ringing, Compared with Right Figure

**Summary**

After comparing the performance of a boost module using IGBTs and a boost module using SiC MOSFETs, this application note showed the efficiency benefits of using a SiC MOSFET module even at a much higher switching frequency than with an IGBT module. Careful attention must be made to the circuit layout and measurement methods because of the fast switching speeds of the SiC component.

**References**

- [1] ON Semiconductor datasheet NXH100B120H3Q0SG. <https://www.onsemi.com/pub/Collateral/NXH100B120H3Q0-D.PDF>
- [2] ON Semiconductor datasheet NXH40B120MNQ0SNG. <https://www.onsemi.com/pub/Collateral/NXH40B120MNQ0-D.PDF>

- [3] ON Semiconductor datasheet FOD3120 <https://www.onsemi.com/pub/Collateral/FOD3120-D.pdf>
- [4] ON Semiconductor datasheet 2SA2016/2SC5569 <https://www.onsemi.com/pub/Collateral/EN6309-D.PDF>
- [5] Z. Zhang, B. Guo, F. F. Wang, E. A. Jones, L. M. Tolbert and B. J. Blalock, "Methodology for Wide Band-Gap Device Dynamic Characterization," in IEEE Transactions on Power Electronics, vol. 32, no. 12, pp. 9307-9318, Dec. 2017, doi: 10.1109/TPEL.2017.2655491.
- [6] Application Note (No. EA 60W-6053-14), Tektronix, January, 2016

ON Semiconductor and are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

**PUBLICATION ORDERING INFORMATION**

**LITERATURE FULFILLMENT:**  
 Email Requests to: [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**TECHNICAL SUPPORT**  
 North American Technical Support:  
 Voice Mail: 1 800-282-9855 Toll Free USA/Canada  
 Phone: 011 421 33 790 2910

**Europe, Middle East and Africa Technical Support:**  
 Phone: 00421 33 790 2910  
 For additional information, please contact your local Sales Representative

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)