

## A5191HRT Design for Low-power Environments

Prepared by: Koenraad Van den Eeckhout  
ON Semiconductor



ON Semiconductor®

<http://onsemi.com>

### APPLICATION NOTE

#### Introduction

The typical HART application can draw power from the current loop. However, for some applications, this power budget can be extremely restrictive.

For other applications, particularly handheld and/or movable HART devices, it may be undesirable to rely on the current loop for power, and the design could be powered by batteries. If this is the case, the design specifications often put a restriction on the minimum battery life and even the size – and thus capacity – of the batteries.

In both these cases, it is desirable to limit the power consumption of each section of the device to the bare minimum. In this design note, we will cover some actions that can be undertaken to reduce power consumption of the A5191HRT.

#### Master Power Control During Dead Times

For a master device, the modem should only be turned on when a frame needs to be transmitted, or when listening for a reply from a slave device. Since slave devices cannot send data without being asked for it, the master interface should be turned off when this is not the case. However, this entails that when the modem is activated again, it must again become synchronized with data flow from a possible secondary master. This may cause a delay in the data flow.

#### Clock Generation

The best way to reduce current consumption during the operation of the device, is to disable the internal oscillator circuit and provide an external clock signal, generated for example by a microcontroller. This will reduce current consumption of the A5191HRT by approximately 100 µA. The easiest way to do this is by generating this signal in a microcontroller operating at a clock frequency that is a multiple of 460.8 kHz, and setting a timer to toggle the XOUT pin of the A5191HRT. Table 1 lists possible frequencies that are multiples of 460.8 kHz. If this approach is chosen, care must be taken that the accuracy of the generated clock signal is less than 1%.

A slave device must always listen to the data transmitted over the network, as the minimal start of new frames is reference to the end of the previous frame. Care should be taken to release nRTS as soon as transmission is finished, as the transmitter consumes around 20 µA more than the receiver.

#### Supply Voltage

When designing for low power restrictions, it is advised to set the supply voltage as low as possible. The A5191HRT can operate down to 2.5 V. However it is advised to use a minimum of 2.7 V to prevent voltage dips from resetting the device. This may provide a current use reduction of up to 300 µA opposed to 5 V operation.

#### Reference Voltages

To achieve the lowest possible power consumption, care must be taken in the generation of reference voltages. As the required accuracy of the references is low, a low quiescent current series regulator will be a better choice than a shunt reference. The reference voltage should be able to provide at least 20 µA.

#### Conclusion

When designing with these guidelines in mind, the power consumption of the A5191HRT and the external components required for its operation can be reduced to a maximum of around 250 µA, with a typical consumption of 220 µA.

Table 1.

Operating Condition	Operating Voltage	Current Consumption
Idle, External oscillator	2.8 V	220 µA (Typ)
Idle, External oscillator	3 V	240 µA (Typ)
Normal Operation	3 V	350 µA (Typ)
Absolute maximum current consumption	3 V	450 µA (Max)

**ON Semiconductor** and **ON** are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
P.O. Box 5163, Denver, Colorado 80217 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

### N. American Technical Support: 800-282-9855 Toll Free

USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910  
**Japan Customer Focus Center**  
Phone: 81-3-5773-3850

### ON Semiconductor Website: [www.onsemi.com](http://www.onsemi.com)

**Order Literature:** <http://www.onsemi.com/orderlit>

For additional information, please contact your local  
Sales Representative