

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.

Integrated Load Detection for Video Drivers



ON Semiconductor®

<http://onsemi.com>

APPLICATION NOTE

Introduction

In this two parts application note illustrating the power saving features on the new generation of video drivers, we will continue with the output load detection explanation.

The idea of the first feature was to detect any incoming analog video signals into the driver (application note AND8473/D). The second step is now to check the status of the load to save even more power to the application.

It's costly and difficult for the chipset to detect the presence of a TV on the RCA connectors dedicated to the analog video channels, especially when the output of the video drivers need to be AC coupled. This load detection feature presented, answers the need by integrating the load detection into the video driver. Therefore the chipset does not need to manage the presence of the TV connection, resulting in simplified chipset code and lower power dissipation.

As a quick reminder, the video driver is build of a clamp or bias circuitry. The second stage is generally a 6th order Butterworth low pass filter (LPF) and last stage will be the 6 dB amplifier (see figure below).

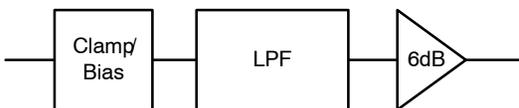


Figure 1. Typical Video Driver Architecture

One may think the load detection is a trivial function but it's only true with an amplifier driving a DC coupled line. In general, a discrete current sense technique is used to fulfill this requirement. Meanwhile video drivers are also required to drive AC coupled output lines through a large capacitor, generally more the 220 μ F. In order to answer the widest range of applications, the newest video drivers like the NCS2584 are also able to detect the load when the outputs are AC coupled. The main idea is put the driver in a very low power consumption mode when the television is unplugged.

To have a good sense of the function, the focus needs to be brought on the amplifier stage. Two cases need to be demonstrated when the driver is OFF:

- ♦ AC coupled output
- ♦ DC coupled output

AC Coupled Output

When the output of the driver is OFF and AC coupled, two phases occur.

Phase 1:

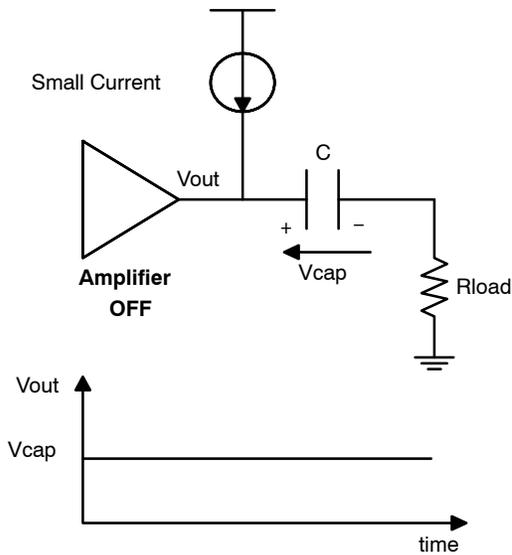


Figure 2. Phase 1, AC Coupled and Loaded Output

Phase 2:

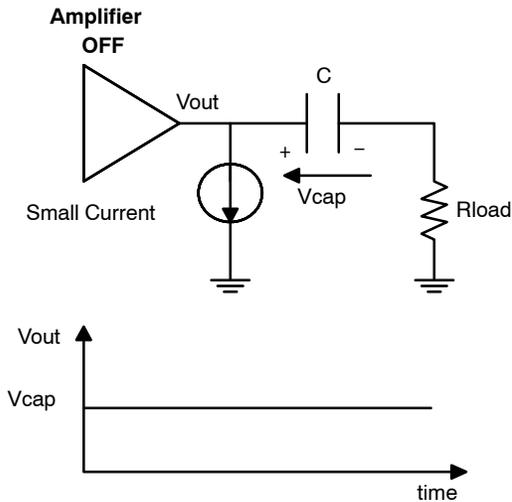


Figure 3. Phase 2, AC Coupled and Loaded Output

In the phase 1, a small current is pushed in the node of the output buffer stage. The output voltage V_{out} becomes equal to the voltage across the capacitor V_{cap} . V_{cap} is equal to the initial capacitor voltage and we assume the drop across the load due to the small current is negligible. The value of C (the output capacitor) is important (220 μ F). Consequently, its charging time by the the small current can be considered as negligible. During the second phase the current on the output node is sunk and V_{out} is still equal to V_{cap} which remains unchanged.

Now, when the load is removed, the output voltage is going to vary from 0 to the device supply voltage level V_{CC} .

Phase 1:

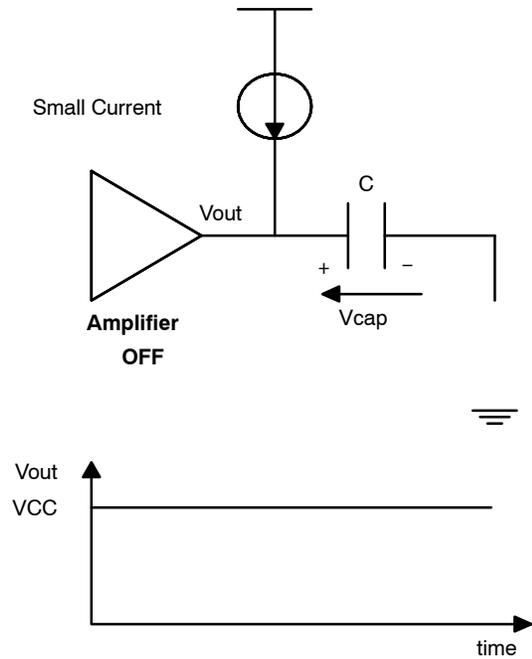


Figure 4. Phase 1, AC Coupled and Unloaded Output

Phase 2 :

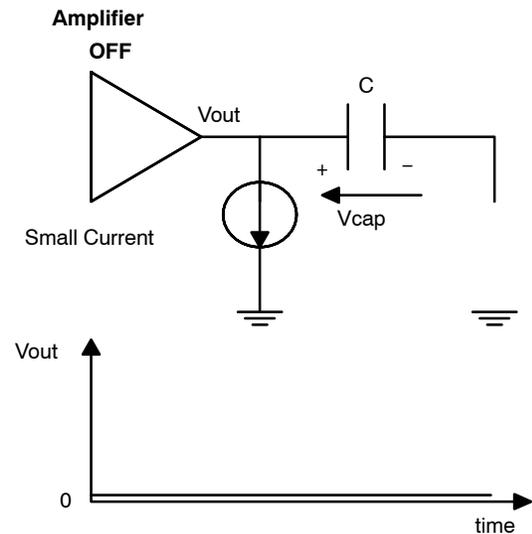


Figure 5. Phase 2, AC Coupled and Unloaded Output

In the phase 1, there is no more load to absorb the current fed into the output node. That's why the voltage at this point goes to V_{CC} . For the same reason, in phase 2, the output voltage is brought to the ground.

In AC coupling configuration without load, the output voltage before the capacitor varies from 0 to V_{CC} periodically.

DC Coupled Output

Now, when the output of the driver is OFF and DC coupled, two phases also occur.

Phase 1:

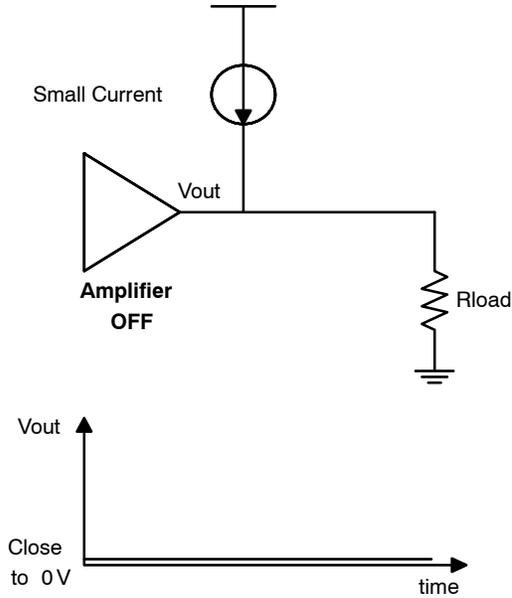


Figure 6. Phase 1, DC Coupled and Loaded Output

Phase 2 :

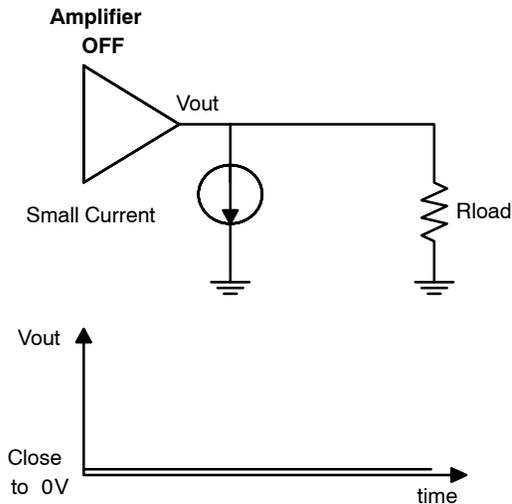


Figure 7. Phase 2, DC coupled and loaded output

During phase 1 and phase 2, the output capacitor is not present anymore to hold a voltage when the load is

connected. The output voltage is consequently pulled close to 0 V.

When the load is disconnected and the output is DC coupled, the output voltage will swing between the rails. The same two phases occur as described when the output is AC coupled.

Phase 1:

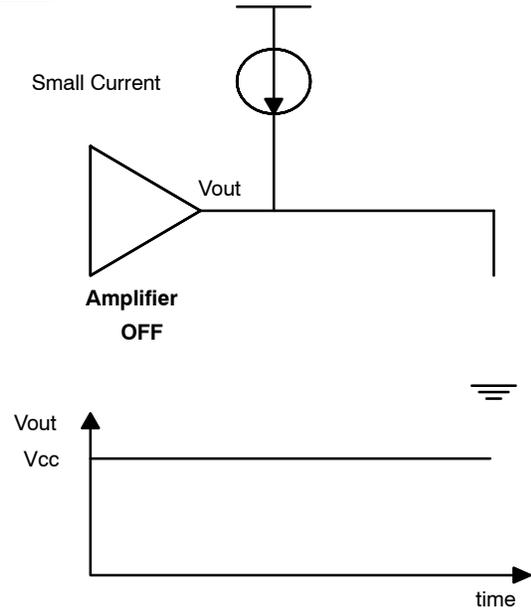


Figure 8. Phase 1, DC Coupled and Unloaded Output

Phase 2 :

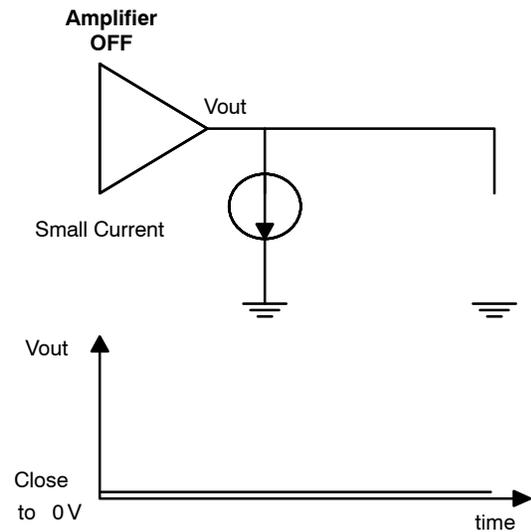


Figure 9. Phase 2, DC Coupled and Unloaded Output

Now understanding those phenomenons, a simple voltage comparator is needed to operate the detection of the load.

Conclusion

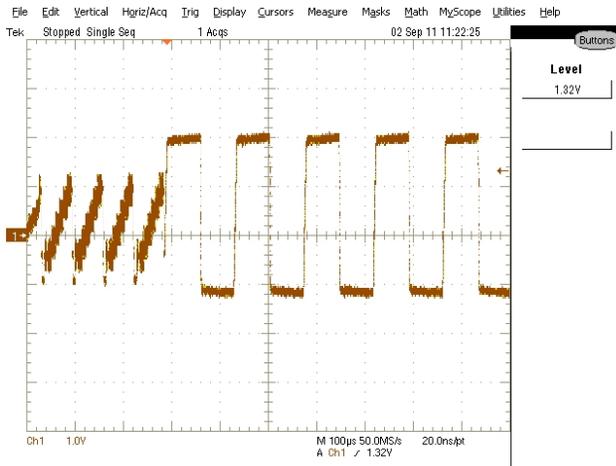


Figure 10. Transition from Loaded to Unloaded AC Coupled Output

The figure above illustrates a Cvbs type signal sent through the driver until the TV is unplugged. At this point of time, the output swings between the rails. The square signal is centered on 0 because it is measured after the capacitor.

The Figure 11 illustrates what is happening on the driver output when the user plugs the TV RCA cable back in the player. The device leaves its switching mode and directly drives the video signal.

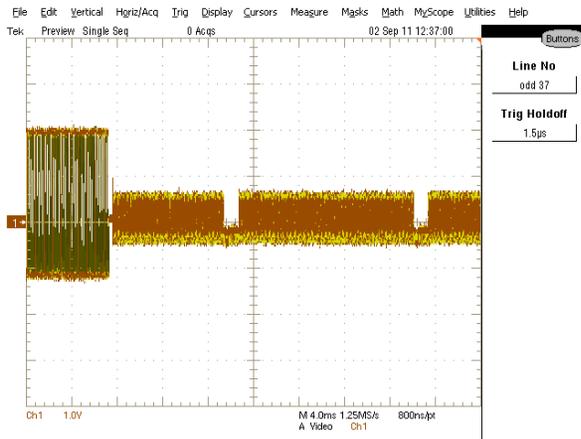


Figure 11. Transition from Unloaded to Loaded AC Coupled Output

It’s best to understand the general behavior of those two types of detection through a state machine. The input video signal detection being treated in the application note AND8473/D “Integrated Input Auto-Detection Mode for Video Drivers”.

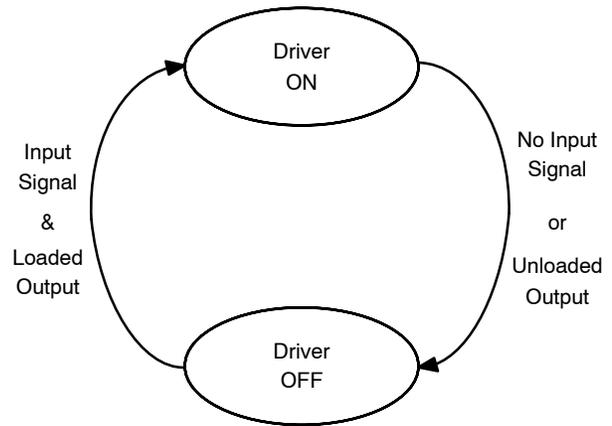


Figure 12. State Machine

The driver is only turned ON when both conditions are met: receiving the proper video signal from the micro controller and having the TV plugged into the player to create a load for the driver. In any other case, the driver will be turned OFF.

This latest generation of analog video drivers has been designed to support the power saving challenges of the consumer industry. Due to this embedded detection feature, system designers will not have to worry about how to improve their design for the analog video outputs. The NCS2584 will help to simplify the control of the video driver and will also be the best fit in an Energy Star® design compliance environment.

ENERGY STAR and the ENERGY STAR mark are registered U.S. marks.

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative