

Adjusting the Over Temperature Protection Trip Point in NCP1250-Based Adapters



ON Semiconductor®

<http://onsemi.com>

APPLICATION NOTE

The NCP1250 features a multi-function pin in which the user can implement Over Power Protection (OPP) and Over Voltage Protection (OVP). If you add a Negative Temperature Coefficient (NTC) resistor in parallel with the OVP Zener diode, you have a means to protect the adapter against thermal runaway. The operating principle is simple: the latch detection is made by observing the OPP pin level via a comparator featuring a 3 V reference voltage. When the NTC resistance decreases as the temperature increases, the off-time voltage on the OPP pin goes up. When it touches the 3 V reference four consecutive times, the controller permanently latches off.

Customers often re-use an NTC they have already implemented in previous projects and define the pull-down

resistor on the OPP pin in relationship with this NTC value. This technique can lead to rather high pull-down resistors on the OPP pin to ground. If this resistance is too high and the converter noisy, the converter immunity can be reduced with possible erratic operations. The solution to fix this kind of problem is to reduce the pull-down resistance. Values below 3 kΩ give good operating results. There are cases where the noise in the adapter will require low values such as 1 kΩ. To still meet the OTP trip point, you will need to install a resistor in parallel with the existing NTC device. The solution appears in Figure 1.

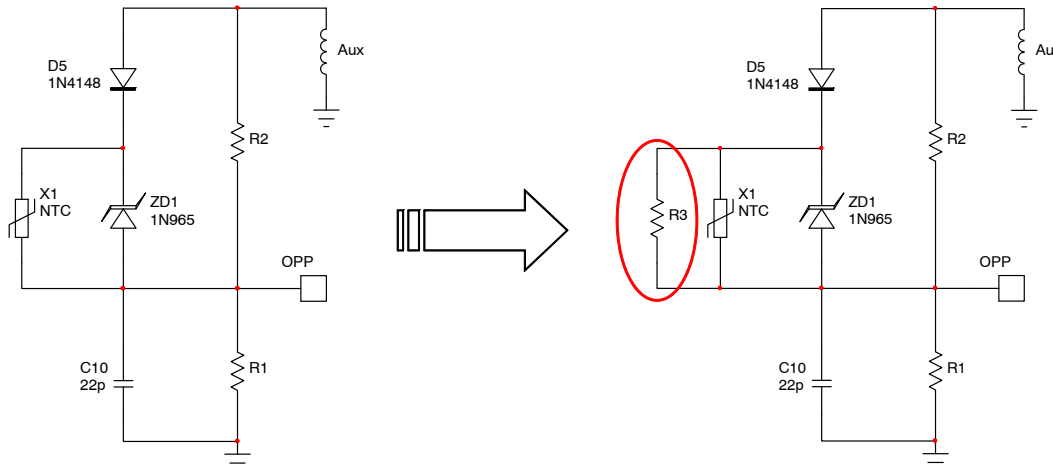


Figure 1. This Picture Shows How to Adapt an Existing NTC Value to Adjust the OTP Trip Point

As a design example, let us assume that we have the following component values around the NCP1250:

- $R_1 = 1 \text{ k}\Omega$; the NCP1250 pull-down resistor on the OPP pin.
- $R_{NTC} = 15 \text{ k}\Omega$; the NTC value at the select OTP trip point.
- $N_{pa} = 0.2$; the turns ratio between the primary and auxiliary windings.
- $N_{ps} = 0.09$; the turns ratio between the primary and secondary windings.
- $V_{out} = 5 \text{ V}$; the converter output voltage.
- $V_f = 0.6 \text{ V}$; the diodes forward drops in the auxiliary and secondary windings.

At first, we need to know the voltage across the NTC in fault mode, e.g. when the OPP pin level reaches 3 V. This voltage is defined by the plateau voltage on the auxiliary

winding during the off time. It also depends on the 0.6 V forward drop of diode D₁ and the 3 V OVP level:

$$V_{NTC} = (V_{out} + V_f) \times \frac{N_{pa}}{N_{ps}} - V_{OVP} - V_f \quad (\text{eq. 1})$$

$$= (5 + 0.6) \times \frac{0.2}{0.09} - 3 - 0.6 = 8.8 \text{ V}$$

Based on 1 kΩ pull-down OPP resistor, the current in fault mode ($V_{OVP} = 3 \text{ V}$) is:

$$I_{R1} = \frac{V_{OVP}}{R_1} = \frac{3}{1000} = 3 \text{ mA} \quad (\text{eq. 2})$$

From Equations 1 and 2, we can derive the equivalent resistance made of the NTC in parallel with the resistor we are looking for (R_3):

$$R_{eq} = \frac{V_{NTC}}{I_{R1}} = \frac{8.8}{3\text{m}} = 2.9 \text{ k}\Omega \quad (\text{eq. 3})$$

Knowing that the equivalent resistor is the NTC paralleled with the added resistance (R_3), we have:

$$R_{eq} = \frac{R_3 R_{NTC}}{R_{NTC} + R_3} \quad (\text{eq. 4})$$

Solving for R_3 leads to:

$$R_3 = \frac{R_{eq} R_{NTC}}{R_{NTC} - R_{eq}} = \frac{2.9\text{k} \times 15\text{k}}{15\text{k} - 2.9\text{k}} = 3.7 \text{ k}\Omega \quad (\text{eq. 5})$$

The next step is to recalculate the OPP resistor (R_2 in Figure 1). For instance, if we need a 300 mV decrease from the 0.8 V setpoint at high line, then the auxiliary diode anode during the on-time swings to:

$$V_{ANODE} = -N_{pa} \times V_{IN} = -0.2 \times (264 \times \sqrt{2}) = -74.7 \text{ V} \quad (\text{eq. 6})$$

We can evaluate the voltage drop around R_2 as:

$$V_{R2} = 74.7 - 0.3 = 74.4 \text{ V} \quad (\text{eq. 7})$$

The current flowing in the pull-down resistor R_1 in this condition will be:


$$I_{R1} = \frac{300\text{m}}{1\text{k}} = 300 \mu\text{A} \quad (\text{eq. 8})$$

The R_2 value is therefore easily derived:

$$R_2 = \frac{74.4}{300\mu} = 248 \text{ k}\Omega \quad (\text{eq. 9})$$

Conclusion

This application note explains how we can easily adjust the Over Temperature Protection trip point by paralleling a resistor with an available NTC device. In case of noisy layouts, it helps to decrease the OPP pin pull-down resistor to a value close or below one kΩ, naturally improving the converter robustness to external perturbations.

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:
 Literature Distribution Center for ON Semiconductor
 P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
 USA/Canada
Europe, Middle East and Africa Technical Support:
 Phone: 421 33 790 2910
Japan Customer Focus Center
 Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
 For additional information, please contact your local Sales Representative