

ON Semiconductor

Is Now



To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and onsemi. and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "onsemi" or its affiliates and/or subsidiaries in the United States and/or other countries. onsemi owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of onsemi product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. onsemi reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and onsemi makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does onsemi assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using onsemi products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by onsemi. "Typical" parameters which may be provided in onsemi data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. onsemi does not convey any license under any of its intellectual property rights nor the rights of others. onsemi products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use onsemi products for any such unintended or unauthorized application, Buyer shall indemnify and hold onsemi and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that onsemi was negligent regarding the design or manufacture of the part. onsemi is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.

Operation of NCP5252 in Low Dropout Applications



ON Semiconductor®

<http://onsemi.com>

APPLICATION NOTE

Introduction

The NCP5252 is a single-phase buck regulator with integrated Power MOSFETs. The device is able to deliver up to 2 A current at an externally adjustable output voltage, which range is from 0.6 V to 5.0 V. The operation range of the input supply voltage is from 4.5 V to 13.2 V. To provide a design guide for low dropout applications, detailed operation behavior of the NCP5252 is described in this application note. Both measurement and calculation results of a 5 V-output application are provided.

Low Dropout PWM Operation

As a non-isolated buck converter, the input supply voltage V_{IN} of the NCP5252 needs to be higher than the output voltage V_{OUT} to provide a sustainable current to a load. In applications where V_{IN} is much higher than V_{OUT} , the NCP5252 operates in a selected fixed-frequency in CCM. When the input voltage V_{IN} drops to be close to the output voltage V_{OUT} , it is possible to see other two operation modes with the NCP5252. Figure 1 is a plot that illustrates key signals in these operation modes.

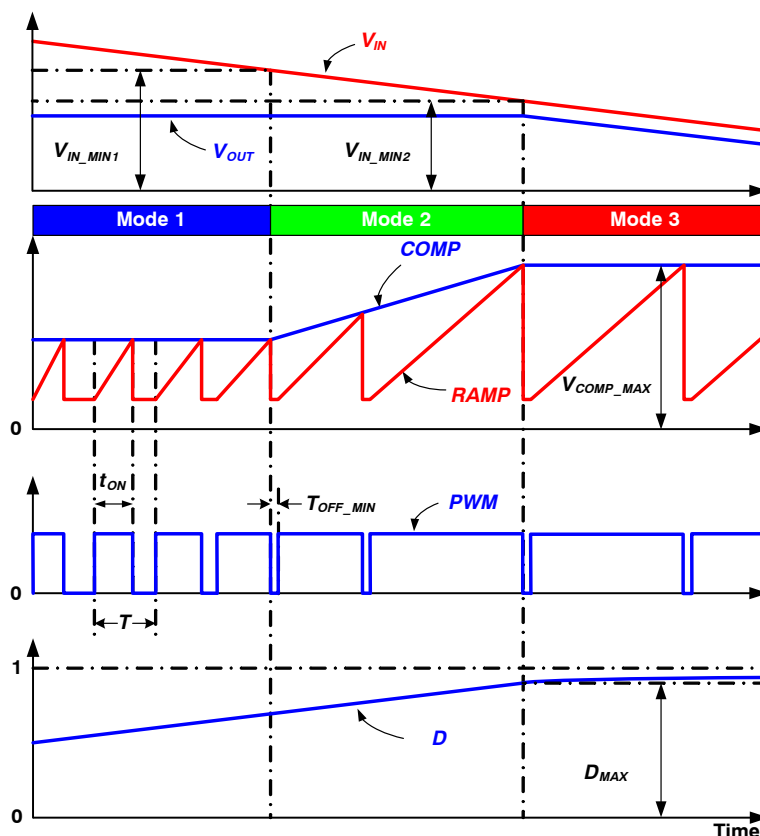


Figure 1. PWM Regulation Modes with the NCP5252

Mode 1 – Fixed-Frequency Operation

As shown in Figure 1, the NCP5252 operates in Mode 1 when the input supply voltage V_{IN} is higher than a minimum required voltage V_{IN_MIN1} . It is a fixed-frequency operation mode with an externally programmed frequency at $FREQ_SET$ pin. The duty ratio of the PWM signal can be estimated by

$$D = \frac{V_{OUT} + I_{OUT} \cdot (R_{DS_L} + DCR)}{V_{IN} - I_{OUT} \cdot (R_{DS_H} - R_{DS_L})} \quad (\text{eq. 1})$$

where I_{OUT} is the load current, DCR is the DC resistance of the output filter inductor L , R_{DS_H} is the conduction resistance of the integrated high-side MOSFET, and R_{DS_L} is the conduction resistance of the integrated low-side MOSFET. To simplify analysis, the diode voltage drops of MOSFETs during dead times have not been taken into account in this calculation.

To ensure good stability and line transient response, a V_{IN} feedforward function has been implemented in the NCP5252's ramp generator. The slew rate SR_{RAMP} of the ramp signal is proportional to both the input voltage V_{IN} and the nominal switching frequency F_{SW} .

$$SR_{RAMP} = 0.25 \cdot V_{IN} \cdot F_{SW} \quad (\text{eq. 2})$$

As a result of the input feedforward function, the voltage level V_{COMP_M1} of the error signal COMP does not change much with the input voltage V_{IN} , having a value of

$$V_{COMP_M1} = D \cdot T \cdot SR_{RAMP} + V_{RAMP_OFFSET} \quad (\text{eq. 3})$$

where V_{RAMP_OFFSET} is the offset/valley voltage (0.4 V typical) of the ramp signal.

When the input voltage V_{IN} drops, the duty ratio D increases to maintain the output regulation with the fixed

switching frequency until the off time of the PWM signal reaches its minimum limit T_{OFF_MIN} (225 ns typical in datasheet, but it would be better to use 260 ns in calculation to cover dead times of gate drivers.). The minimum required voltage V_{IN_MIN1} can be obtained by

$$V_{IN_MIN1} = \frac{V_{OUT} + I_{OUT} \cdot (R_{DS_L} + DCR)}{1 - F_{SW} \cdot T_{OFF_MIN}} + I_{OUT} \cdot (R_{DS_H} - R_{DS_L}). \quad (\text{eq. 4})$$

Mode 2 – Frequency-Deduction Operation

If the input voltage drops below V_{IN_MIN1} , the off time of the PWM signal cannot be reduced further due to T_{OFF_MIN} . This forces the NCP5252 to reduce switching frequency to maintain the output regulation. The switching frequency in Mode 2 operation is

$$F_{SW_M2} = \frac{1 - D}{T_{OFF_MIN}}. \quad (\text{eq. 5})$$

The control loop pushes the COMP voltage to a higher level V_{COMP_M2} to get a wider on time T_{ON_M2} .

$$V_{COMP_M2} = T_{ON_M2} \cdot SR_{RAMP} + V_{RAMP_OFFSET} \quad (\text{eq. 6})$$

$$T_{ON_M2} = \frac{T_{OFF_MIN}}{\frac{V_{IN} + I_{OUT} \cdot (R_{DS_L} - R_{DS_H})}{V_{OUT} + I_{OUT} \cdot (R_{DS_L} + DCR)} - 1} \quad (\text{eq. 7})$$

The maximum on time is limited by the maximum voltage level V_{COMP_MAX} of the COMP signal, which typical value is 3.5 V. A corresponding minimum input voltage V_{IN_MIN2} to maintain the target regulation voltage can be calculated by:

$$V_{IN_MIN2} = \frac{V_{OUT} + I_{OUT} \cdot (R_{DS_H} + DCR)}{1 - \frac{0.25 \cdot F_{SW} \cdot T_{OFF_MIN}}{V_{COMP_MAX} - V_{RAMP_OFFSET}}} \cdot (V_{OUT} + I_{OUT} \cdot (R_{DS_L} + DCR)) \quad (\text{eq. 8})$$

Mode 3 – Maximum-Duty Operation

If the input voltage drops below V_{IN_MIN2} , the COMP signal is clamped to V_{COMP_MAX} , and thus the NCP5252 reaches its limitation in the on time T_{ON_M3} .

$$T_{ON_M3} = \frac{V_{COMP_MAX} - V_{RAMP_OFFSET}}{SR_{RAMP}} \quad (\text{eq. 9})$$

The switching frequency F_{SW_M3} in Mode 3 does not decrease as much as that in Mode 2 when V_{IN} drops.

$$F_{SW_M3} = \frac{1}{T_{ON_M3} + T_{OFF_MIN}} \quad (\text{eq. 10})$$

The NCP5252 reaches its maximum limitation in the duty ratio, which has a value D_{MAX} when the input voltage is equal to V_{IN_MIN2} .

$$D_{MAX} = \frac{1}{1 + \frac{0.25 \cdot V_{IN_MIN2} \cdot F_{SW} \cdot T_{OFF_MIN}}{V_{COMP_MAX} - V_{RAMP_OFFSET}}} \quad (\text{eq. 11})$$

In Mode 3, the output voltage drops as input voltage drops. The output voltage can be calculated by

$$V_{OUT_M3} = \frac{V_{IN} - I_{OUT} \cdot (R_{DS_H} - R_{DS_L})}{1 + \frac{0.25 \cdot V_{IN} \cdot F_{SW} \cdot T_{OFF_MIN}}{V_{COMP_MAX} - V_{RAMP_OFFSET}} - I_{OUT} \cdot (R_{DS_L} + DCR)} \quad (\text{eq. 12})$$


The voltage drop between V_{IN} and V_{OUT} increases as I_{OUT} increases.

5 V–Output Application


To verify the operation of the NCP5252 in a low dropout application, a 5 V–output regulator has been built on a NCP5252 demo board. Three plots in Figure 2 show waveforms of three key signals (V_{OUT} , COMP, and LX) under the three operation modes when V_{IN} is close to V_{OUT} . The load current is 1 A and the selected nominal frequency is 500 kHz in this test. The switching frequency drops smoothly as V_{IN} drops. The minimum required input voltage for the 5 V/1 A output is about 5.5 V. The NCP5252 still be able to provide current to the output when V_{IN} drops further, but the output voltage starts to drop below the 5 V target.

Figure 3 shows measurement results with a 1 A load current and three nominal switching frequency options. The higher the nominal frequency is selected, the higher V_{IN_MIN2} is required to maintain the 5 V output voltage. V_{IN} Figure 4 shows measurement results of the switching frequency changing with the input voltage for three nominal frequency options. The NCP5252 is able to have about 60% off in switching frequency in this application. The 333 kHz frequency option is able to support the lowest minimum input voltage in the low dropout applications.


AND9095/D

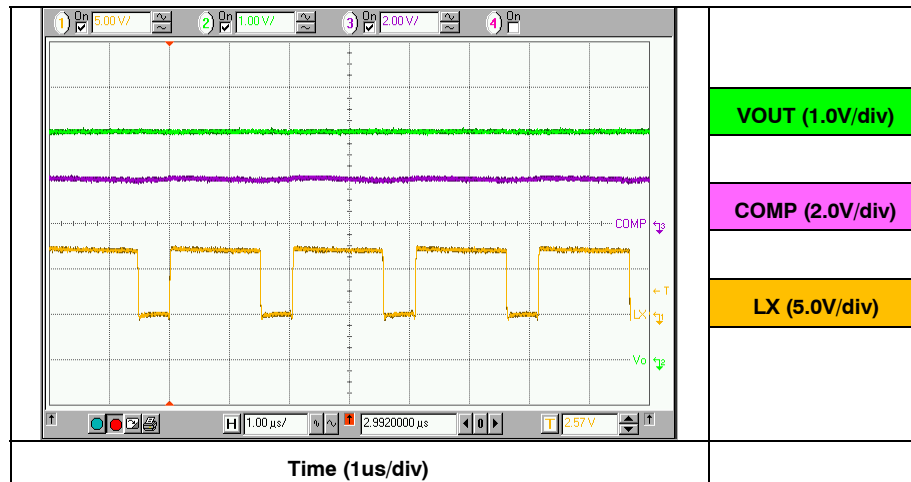

(a) $V_{IN} = 7.0 \text{ V}$ (Mode 1)

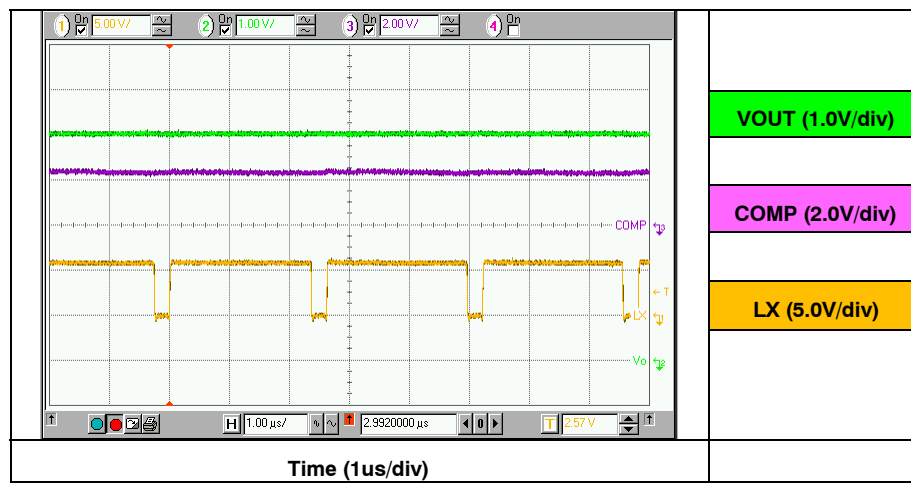

(b) $V_{IN} = 5.75 \text{ V}$ (Mode 2)

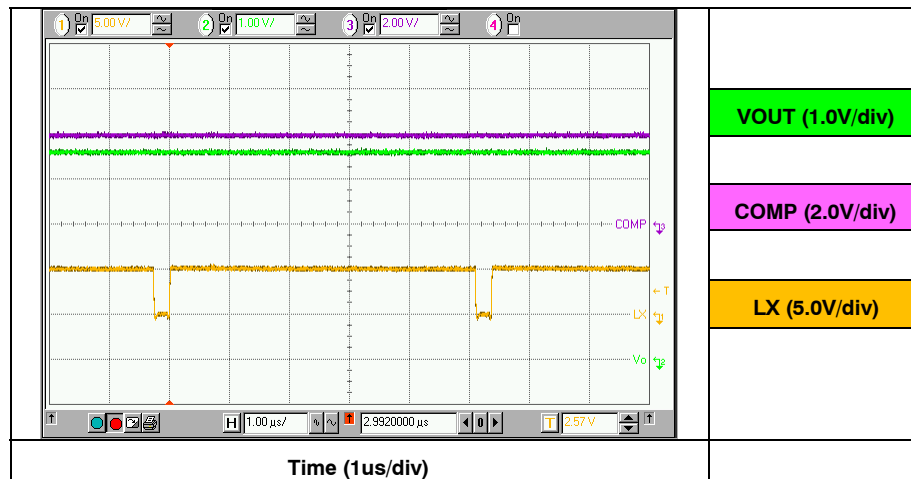

(c) $V_{IN} = 5.0 \text{ V}$ (Mode 3)

Figure 2. PWM Operation Waveforms vs. Input Voltage ($V_{OUT} = 5 \text{ V}$, $I_{OUT} = 1 \text{ A}$, 500 kHz Option)

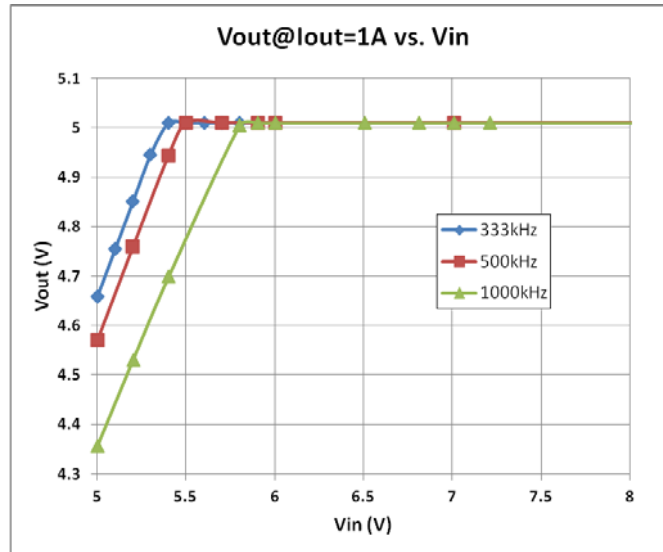


Figure 3. Output Regulation V_{OUT} vs. Input Voltage V_{IN}

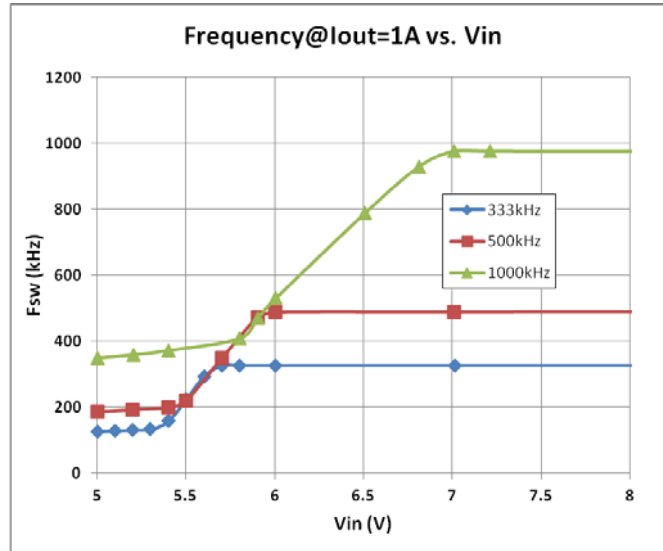


Figure 4. Switching Frequency F_{SW} vs. Input Voltage V_{IN}

As shown in Figure 5, a result comparison between measurements and calculations has been done on the minimum required input voltage V_{IN_MIN2} to maintain 5 V output voltage under different load current conditions. Both results address that higher minimum input voltage is required for higher load current. Difference between the

measurements and the calculations grows with an increasing in the load current, which may be caused by some omitted factors in the calculations such as body diode forward voltage during dead times, conduction resistance variations regarding to temperatures of inductor and MOSFETs, and other power loss factors.

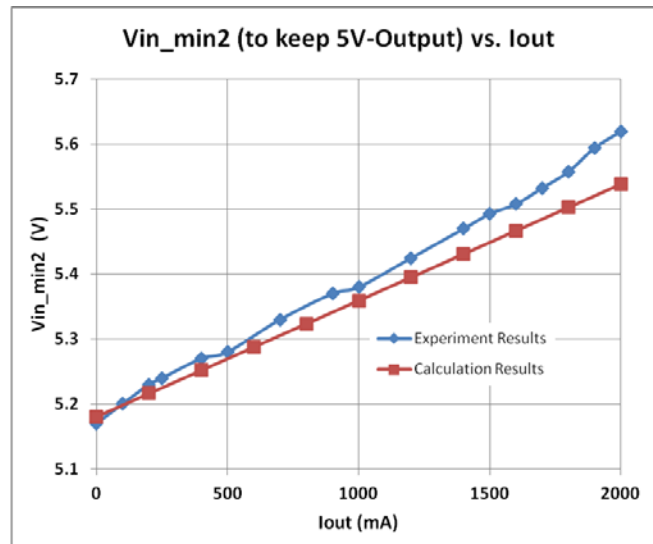


Figure 5. Minimum Input Voltage V_{IN_MIN2} vs. Load Current I_{OUT} (333 kHz Option)

ON Semiconductor and **ON** are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of SCILLC's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada

Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910

Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com

Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local
Sales Representative