

AND9535/D

434 MHz LNA for RKE using the NSVF3007SG3

Overview

This application note explains about ON Semiconductor's NSVF3007SG3 which is used as a Low Noise Amplifier (LNA) for RKE (Remote Keyless Entry).

The NSVF3007SG3 is a silicon bipolar transistor best suited for high-frequency applications which is assembled in the 3-pin surface mount package.

For information about the performance, please refer to the datasheet of this product.

Since the evaluation board is adjusted to achieve optimal performance in RKE (434 MHz), the product can provide 14 dB gain and 1.45 dB noise figure.

A standard material FR4 is used for the printed circuit board (PCB).

Please note that the losses of the PCB and the SMA connector are not excluded from the noise figure.



ON Semiconductor®

www.onsemi.com

APPLICATION NOTE


■ Summary of Data

Ta = 25°C, Input Power = -30 dBm


Parameter	Symbol	Condition	Result	Unit
DC Voltage	Vcc		3.0	V
DC Current	Icc		2.14	mA
Power Gain	Gp	f = 434 MHz	15.4	dB
Noise Figure	NF	f = 434 MHz	1.65	dB
Input Return Loss	RLin	f = 434 MHz	3.8	dB
Output Return Loss	RLout	f = 434 MHz	8.0	dB
Isolation	ISL	f = 434 MHz	21.1	dB
Gain 1 dB Compression Input Power	Pin1dB	f = 434 MHz	-22	dBm
Input 3rd Order Intercept Point	IIP3	f1 = 433 MHz f2 = 434 MHz Pin = -35 dBm	-7.1	dBm

AND9535/D

■ Circuit Design

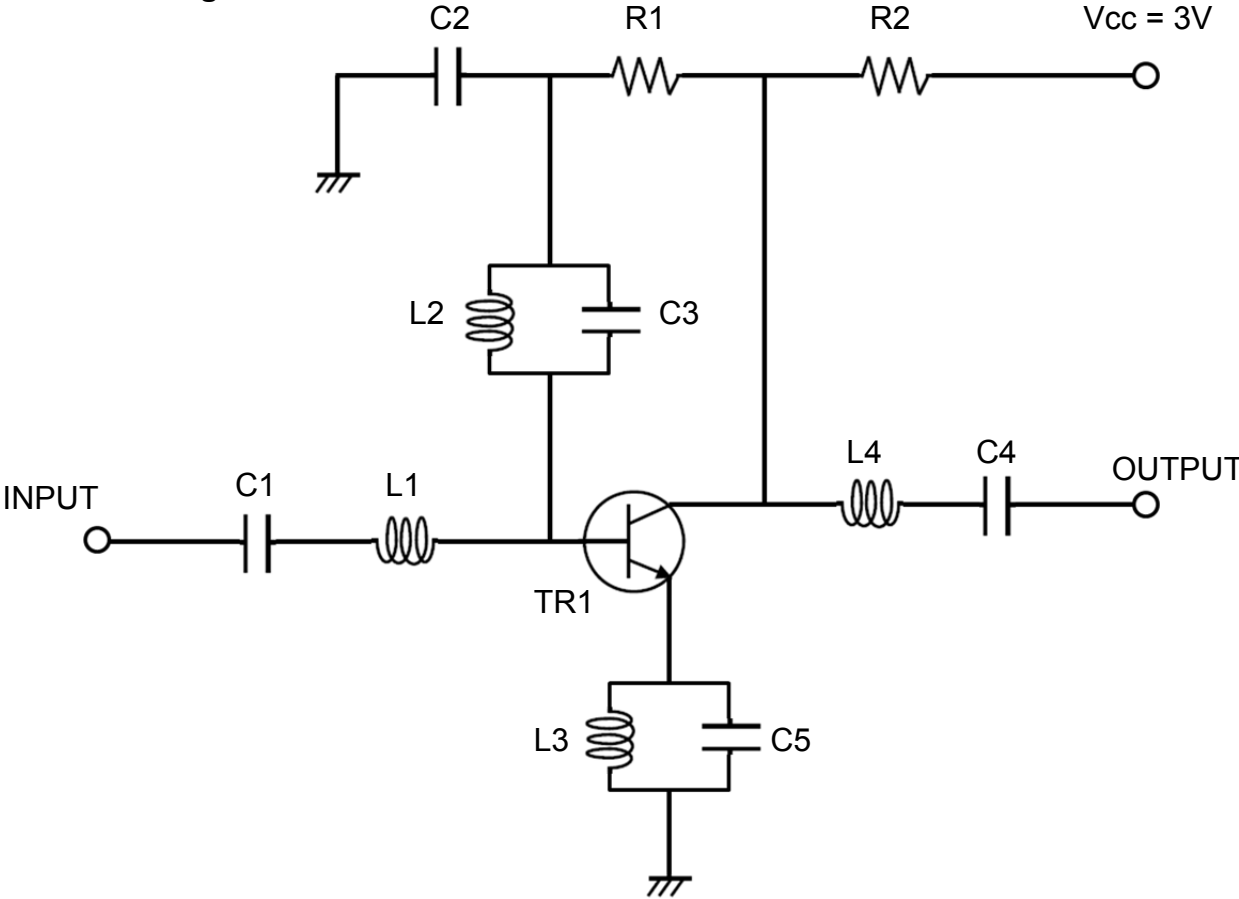

■ Evaluation Board

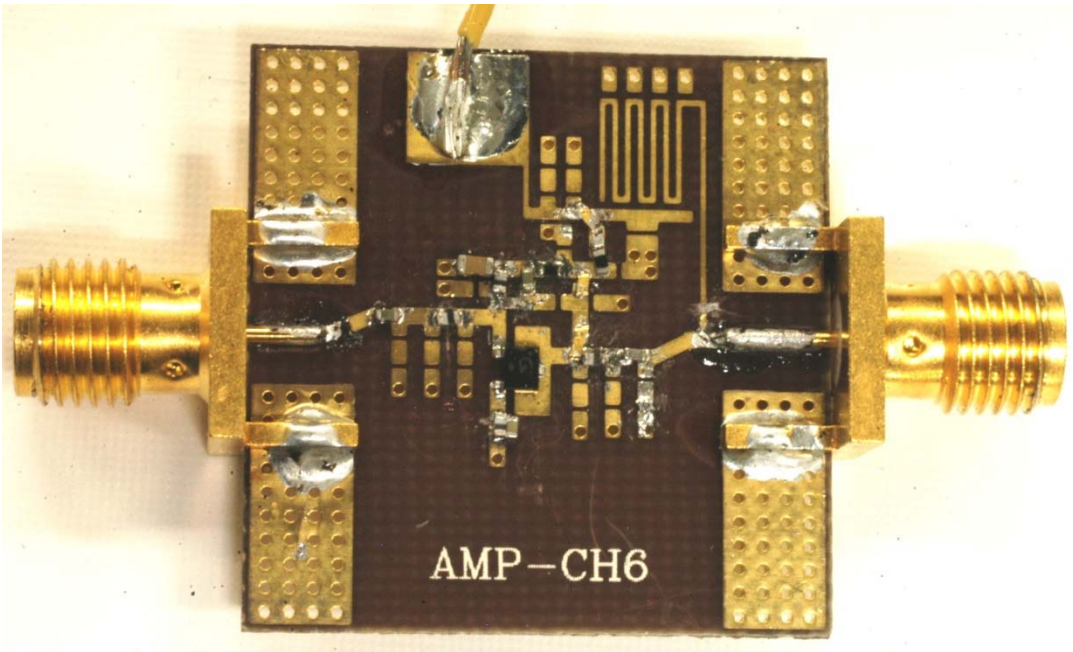


■ Bill of Materials


Item	Symbol	Value	Manufacturer	Size
Bip-Tr	TR1	NSVF3007SG3	ON Semiconductor	SC70
Capacitor	C1	100 pF	Murata GRM155	1005
	C2	47 nF	Various	1608
	C3	3 pF	Murata GRM155	1005
	C4	680 pF	Murata GRM155	1005
	C5	10 nF	Murata GRM155	1005
Resistor	R1	47 k Ω	Various	1005
	R2	470 Ω	Various	1005
Inductor	L1	12 nH	TDK MLG1005S	1005
	L2	100 nH	TDK MLG1005S	1005
	L3	3.8 nH	TDK MLG1005S	1005
	L4	18 nH	TDK MLG1005S	1005
Material	–	FR4	–	25 x 25 mm

AND9535/D

■ Power Gain

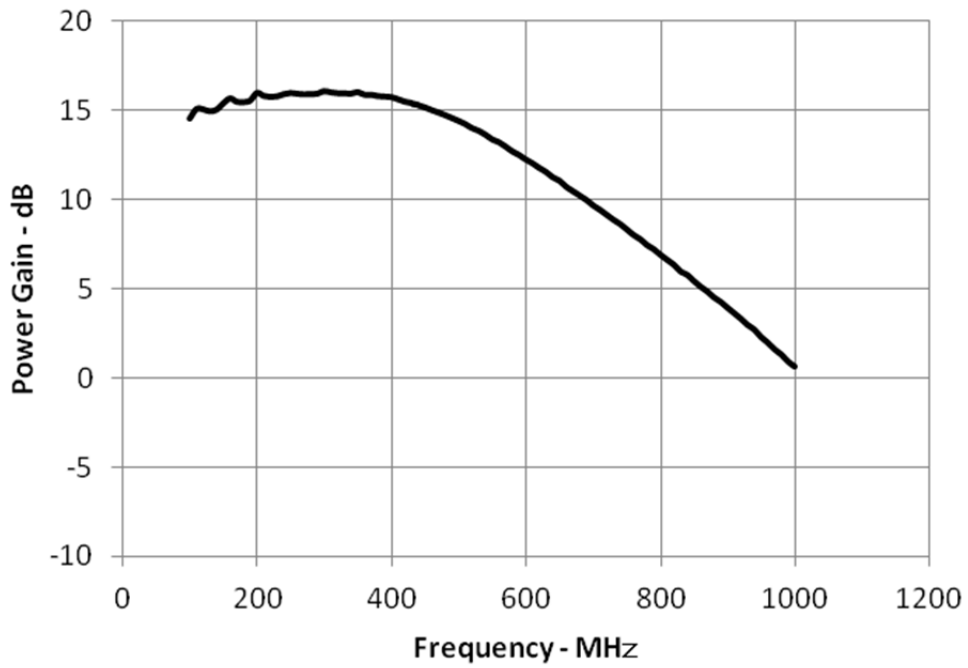


■ Isolation

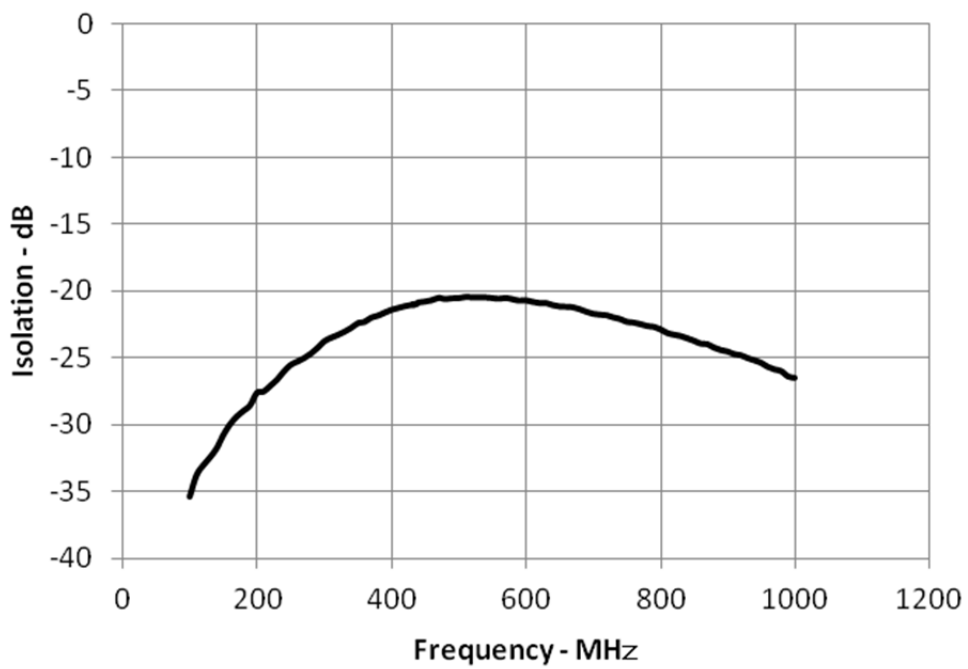


AND9535/D


■ Input Return Loss

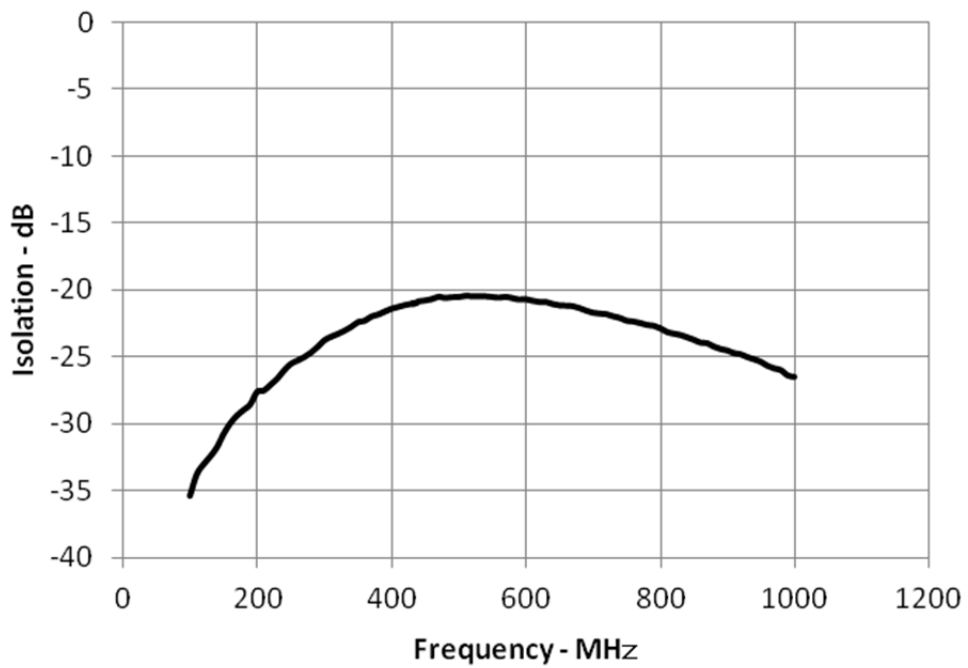


■ Output Return Loss

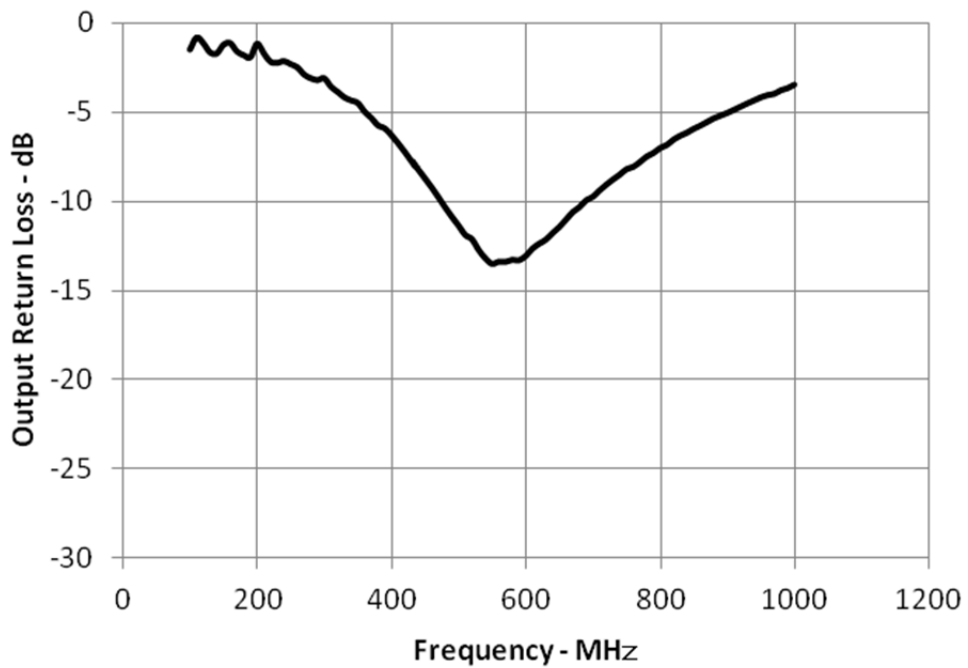

■ Noise Figure

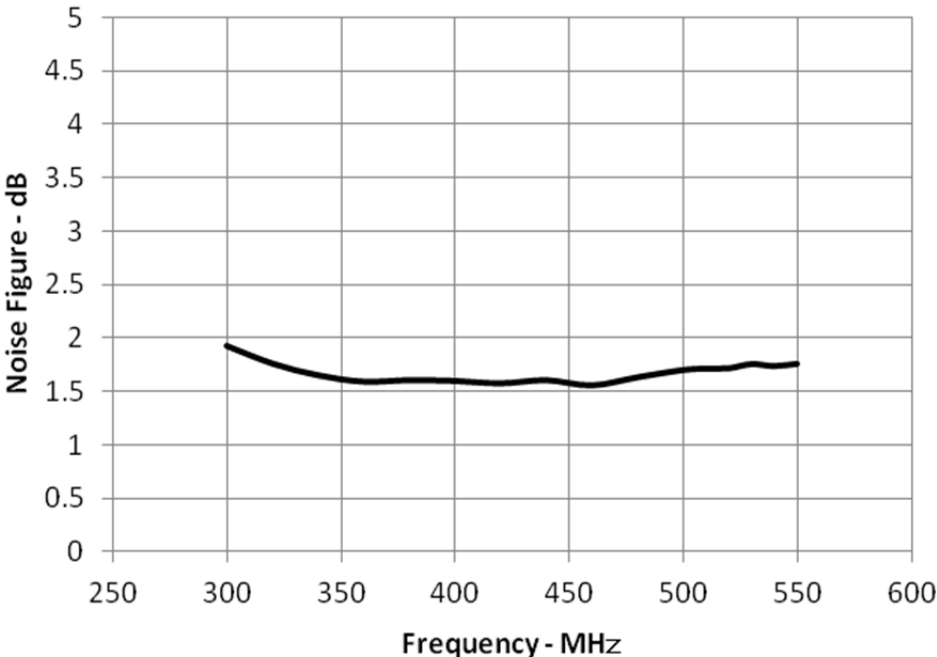


■ S11, S21, S12, S22 Wide Span

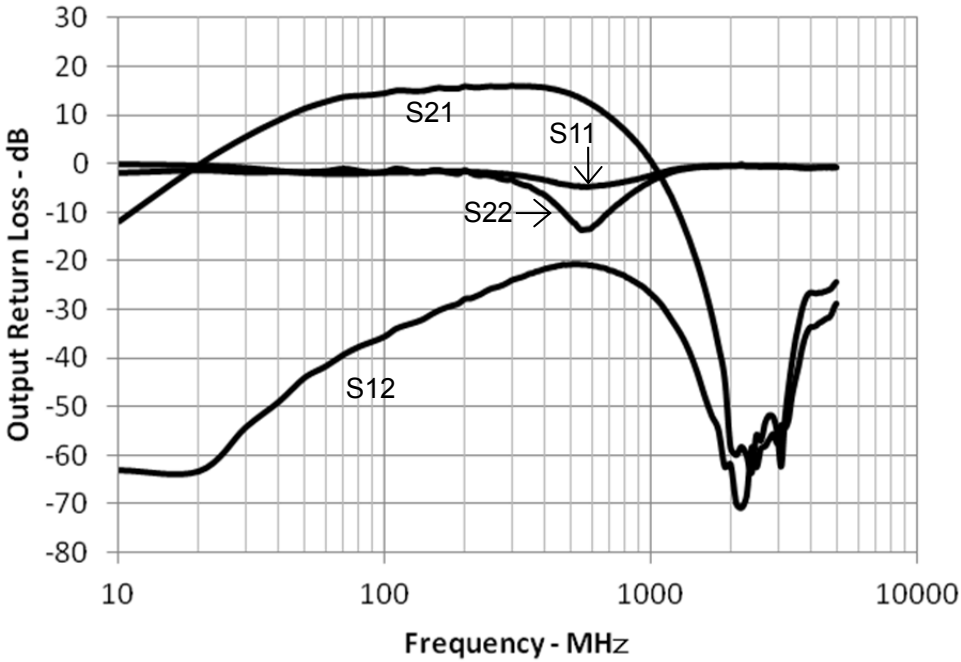


AND9535/D

■ Smith Chart
Input Return Loss

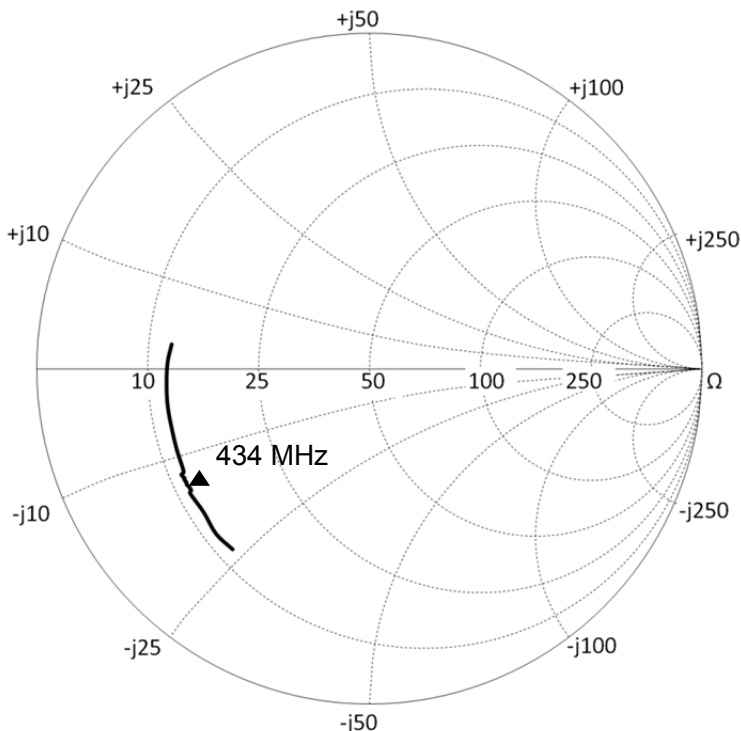


400 MHz to 500 MHz

■ Smith Chart
Output Return Loss

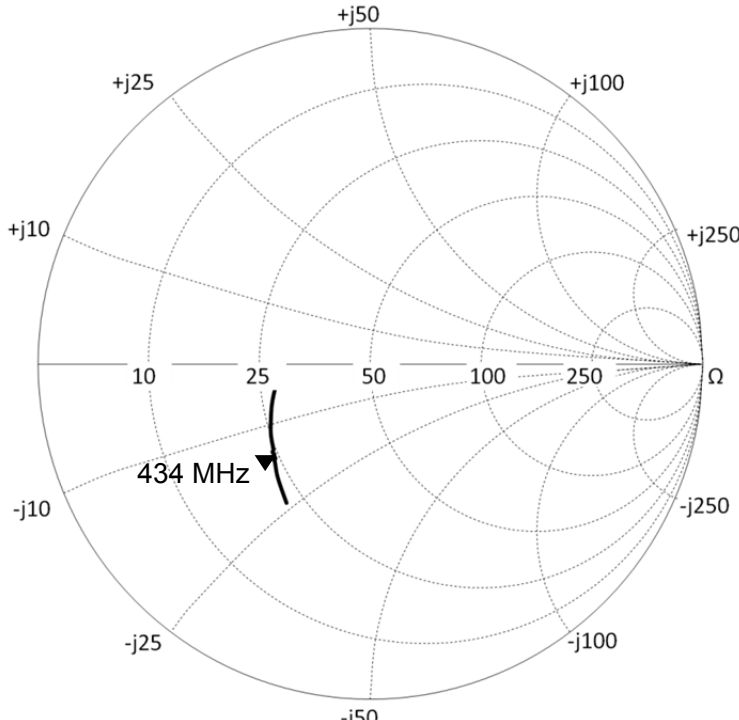


400 MHz to 500 MHz

■ Gain 1 dB Compression Point

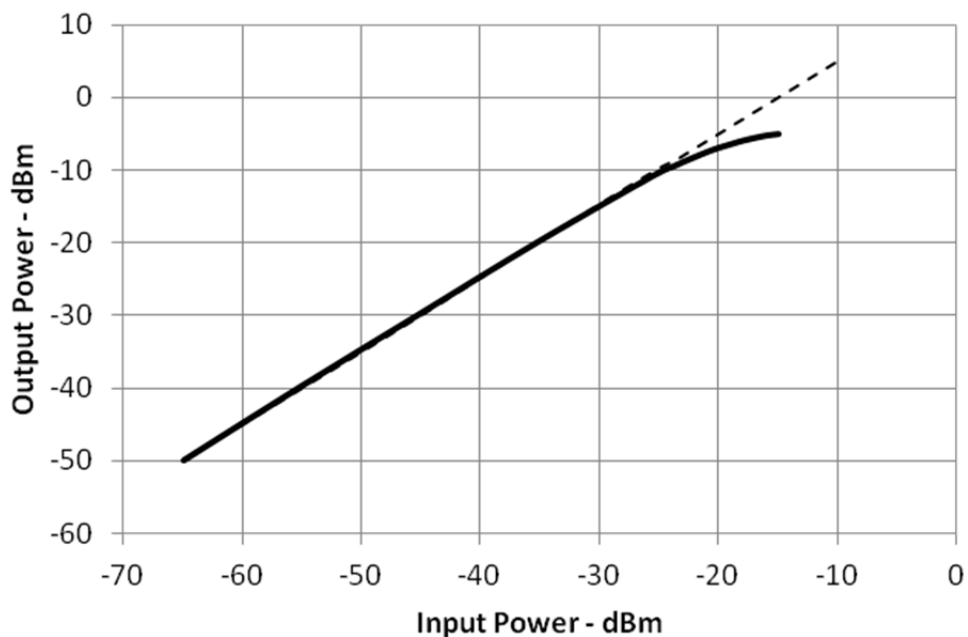

■ Input 3rd Order Intercept Point

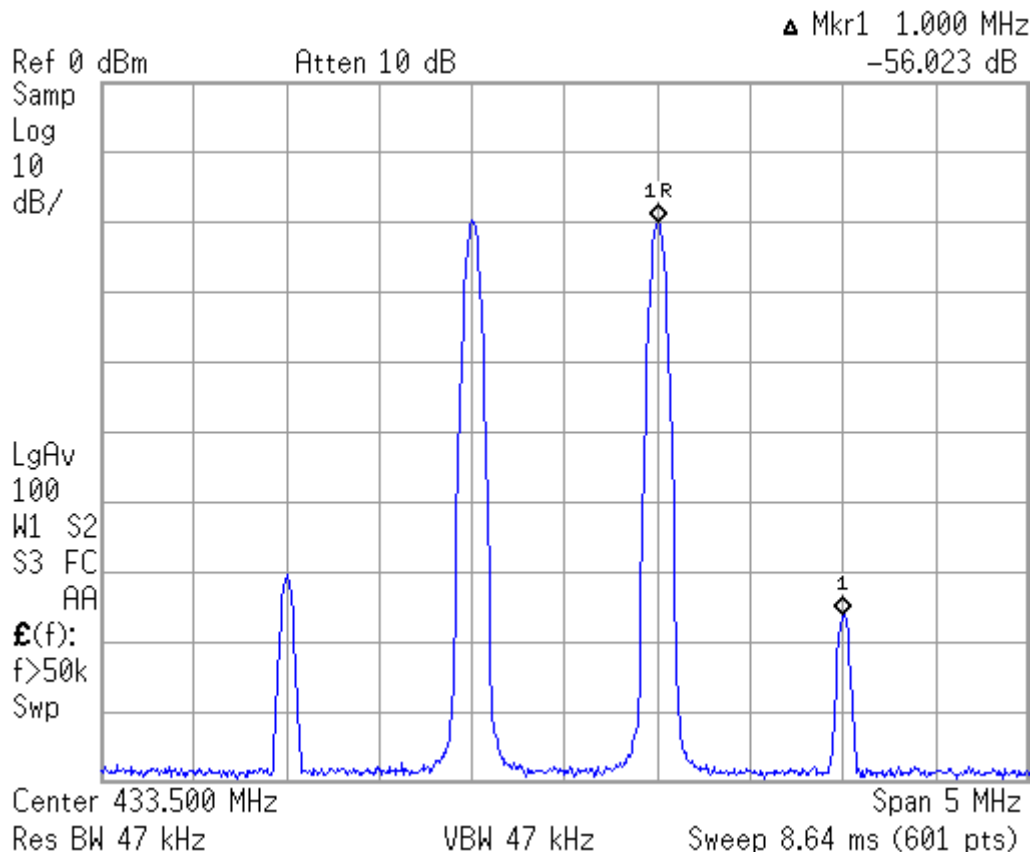$f_1 = 433 \text{ MHz}$, $f_2 = 434 \text{ MHz}$, $P_{in} = -35 \text{ dBm}$



ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.