



## Automotive Imaging Power Architecture and Design

### INTRODUCTION

Imaging system input and intermediate voltages play a critical role in total system efficiency, performance, and component selection. Proper selection of these voltages depend on multiple system variables, such as: total power consumption of the image sensor/ISP, regulator efficiency, and resistance of the coax cable and filter. This document discusses the trade-offs associated with changing module input voltages, so that informed design-decisions can be made in optimizing automotive imaging modules.

### APPLICATION NOTE

### SYSTEM POWER OVERVIEW

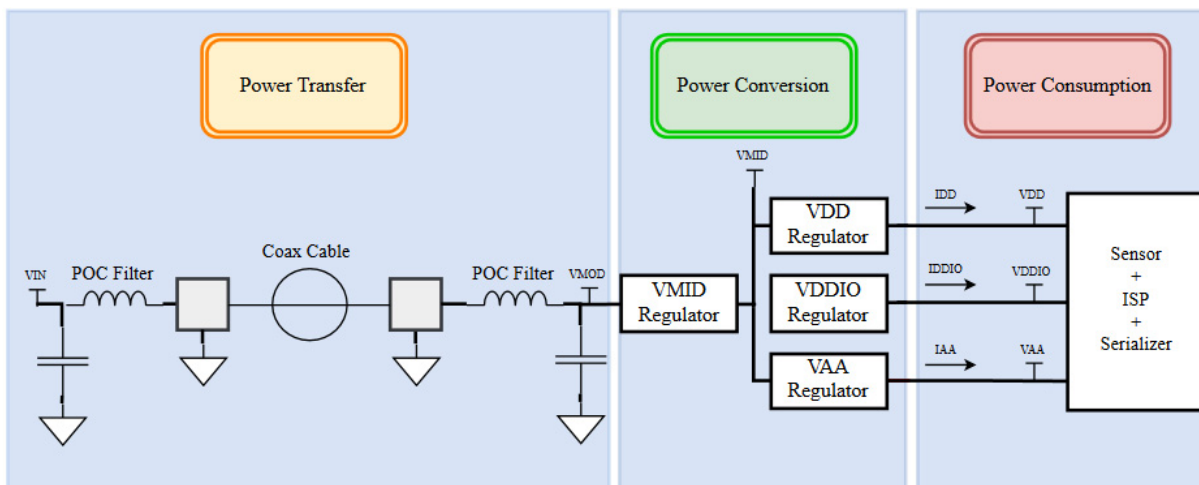


Figure 1. General Overview of an Automotive Imaging System Organized into Three Section

### POWER TRANSFER

In an automotive imaging system, power and data are combined and transferred to remote parts of the vehicle over a single coaxial cable. This implementation is known as “Power over Coax” (POC). From a power standpoint, the two main figures of merit for this stage are:

1. Conduction Losses

$$P_{\text{loss}}(I_{\text{in}}^2)(R_{\text{coax}} + 2R_{\text{DCR}}) \quad (\text{eq. 1})$$

2. DC Voltage Drop

$$V_{\text{drop}} = (I_{\text{in}})(R_{\text{coax}} + 2R_{\text{DCR}}) \quad (\text{eq. 2})$$

Both of these concerns are factors of the DC transfer current, DCR of the filter inductors at each coax connector,

and coaxial cable resistance. Higher currents contribute to higher power losses and larger DC voltage drops. Moreover, a large enough DC voltage drop could induce under voltage-lockout in downstream regulators and shut down the system.

Decreasing the transfer current ( $I_{\text{in}}$ ) will minimize both conduction losses and the DC voltage drop, however, in order to decrease the transfer current, the voltage transmitted over the coaxial cable must be increased to maintain the same amount of transferred power. This is not always ideal, as increased coaxial voltage will lead to more losses in the power conversion of the image sensor module.


**POWER CONVERSION**

Integrated circuits in automotive imaging systems (Image Sensors, Image Processors, SERDES links) normally utilize the voltages 2.8 V, 1.8 V, and 1.2 V. Because of these multiple, low-voltage rails, it is necessary to convert down from a single higher coaxial voltage. The primary power concern in this stage is voltage conversion losses. These losses can be quantified as:


$$P_{\text{loss}} = \sum_{i=1}^n P_i \left( \frac{1}{\eta_i} - 1 \right) \quad (\text{eq. 3})$$

Where  $\eta_i$  is regulator efficiency, and  $P_i$  is the regulator's output power. Given a constant output power, the loss is a factor of regulator efficiency. Furthermore, in both switching and linear regulators, efficiency is a factor of

input/output voltage ratio ( $V_{\text{in}}/V_{\text{out}}$ ). The larger the ratio, the worse the efficiency.

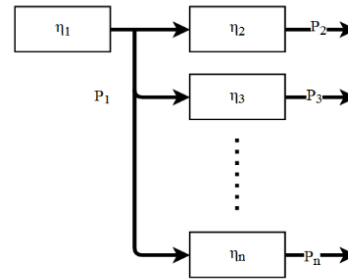

**Figure 2. Power Conversion Diagram**

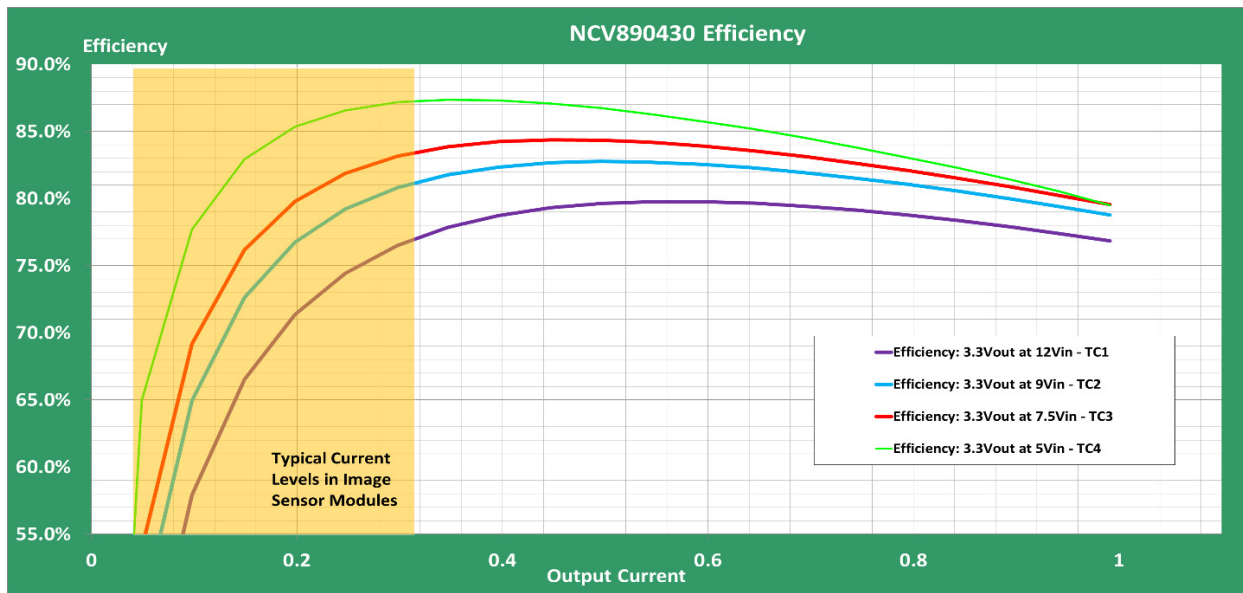

**Figure 3. Efficiency Graph of the NCV890430 5-12Vin Automotive Voltage Regulator. Note how the input-to-output voltage ratio drastically affects the efficiency.**

Lowering the  $V_{\text{IN}}/V_{\text{OUT}}$  conversion ratio of each regulator will minimize power conversion losses. Because the output voltages are defined by the image sensor, this ratio can be decreased by lowering the input voltage to the power conversion stage. Unfortunately, decreasing the input voltage will increase the transfer current, resulting in larger power transfer losses.

The trade-off between transfer and conversion losses must be considered when choosing the proper input voltage. Optimally designed power architectures select an input voltage that results in the lowest total power loss. Again, both transfer and conversion losses are factors of component parameters.

**Transfer Loss Component factors**

- Inductor DCR
- Coaxial Series Resistance
- Coaxial Connector Resistance

**Conversion Loss Component Factors**

- Regulator Efficiency at specific  $V_{\text{in}}/V_{\text{out}}$  ratio
- Voltage Conversion Topology

**SYSTEM PERFORMANCE**

Altering the system’s input voltage can pose performance risks to the system if the effects are not properly realized. A changing input voltage alters the transfer current levels which affects voltage regulator transients, filter performance, and dark current generation.

**TRANSIENT IMPACT**

Increased coaxial current consequently increases voltage transients seen at the input of the Vmid Regulator. Large enough transient events could impact the regulator’s ability to maintain regulation, or even impact the AC data traveling along the coaxial line. To mitigate the effect of these increased transients, sufficient capacitance should be placed on the input of the Vmid Regulator.

**SIGNAL INTEGRITY**

Another side-effect of larger coaxial current is the need for larger POC filter inductors. The POC filter is required to prevent the AC coaxial data from reaching the input of the Vmid regulator. If the inductors of the filter are not properly sized, the higher currents could saturate the inductors and lead to degradation of the AC signal integrity, or even lose PLL (Phase Lock Loop) locking of the serialized communication.

**DARK CURRENT TEMPERATURE VARIATION**

Dark current negatively impacts image quality by altering the black level or reference point of the image sensor. Dark current is also highly temperature dependent; larger temperatures near the sensor lead to larger levels of dark current. Minimizing the heating at or around the image sensor is essential in minimizing dark current levels, which in turn ensures proper image quality. Dark Current generation is reduced by limiting power dissipation in voltage regulators near the image sensor. Ideally, dissipated

system power should be remote to the image sensor such as the coaxial cable or filter. Within compact designs, lower conversion voltages and higher coaxial currents are preferred as because it minimizes heating around the image sensor, which reduces image sensor dark currents.

**SYSTEM INPUT VOLTAGE TRADE-OFF SUMMARY**

Table 1 organizes the discussed effects of altering system input voltage. While each design is different, these trade-offs should be balanced in a way that minimizes system power loss and ensures proper imaging performance.

**Table 1. DESIGN TRADE-OFF SUMMARY**


	Transfer Current	Transfer Losses	Conversion Losses	Dark Current
High System Input Voltage	Low	Better	Worse	Worse
Low System Input voltage	High	Worse	Better	Better

**SYSTEM RECOMMENDATIONS**

This next section will use an automotive imaging module reference design to address and quantify the aforementioned design trade-offs, and recommend a system input voltage based on the collected data.

**MODULE OVERVIEW**

The imaging module utilizes a common topology where the system input voltage (Vin) is transferred across a coax cable and converted down to an intermediate voltage (Vmid). Vmid is then converted into the voltages specified by the image sensor/processor. Figure 4 illustrates this topology, while Table 2 lists the key power components used.

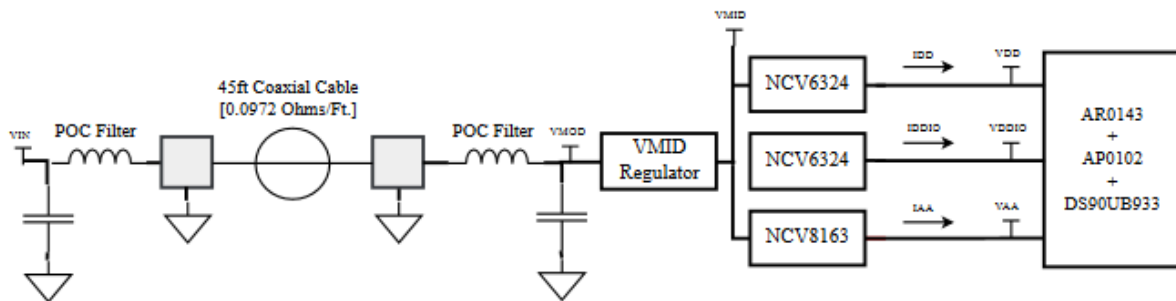

**Figure 4. Diagram of the Automotive Imaging Module used to Test Design Trade-offs**

**Table 2. COMPONENTS AFFECTING THE POWER ARCHITECTURE OF THE REFERENCE DESIGN MODULE**

Image Sensor	Image Sensor Processor	Coaxial Cable	SMPS	Linear Regulators
AR0143	AP0102	Pasternack- PE38746Z-540	NCV890430	NCV8163
			NCV6324	

## AND9708/D

Data was collected for five test cases. The input voltage and the regulators used to develop  $V_{mid}$  were altered. Table 3 lists a description of each test case. Each test was performed while the module was streaming video over

a 45 feet coaxial cable (DC resistance of  $0.972 [\Omega/\text{ft}]$ ). The image sensor and ISP were configured to consume the maximum amount of power (0.58 W),


**Table 3. DESCRIPTION OF EACH TEST CASE USED FOR DATA COLLECTION. NOTE THAT SYSTEM INPUT VOLTAGE ( $V_{in}$ ) AND THE  $V_{mid}$  REGULATOR WERE ALTERED**

Test Case	$V_{in}$	$V_{mid}$ Regulator
1	12 V	NCV890430
2	9 V	NCV890430
3	5 V	NCV890430
4	5 V	NONE
5	5 V	NCV6324

### SYSTEM EFFICIENCY

An overall system efficiency depicting the losses in the coaxial cable/filter (transfer losses) and regulator losses on

the module (conversion losses) was performed using the five test cases listed in Table 1.

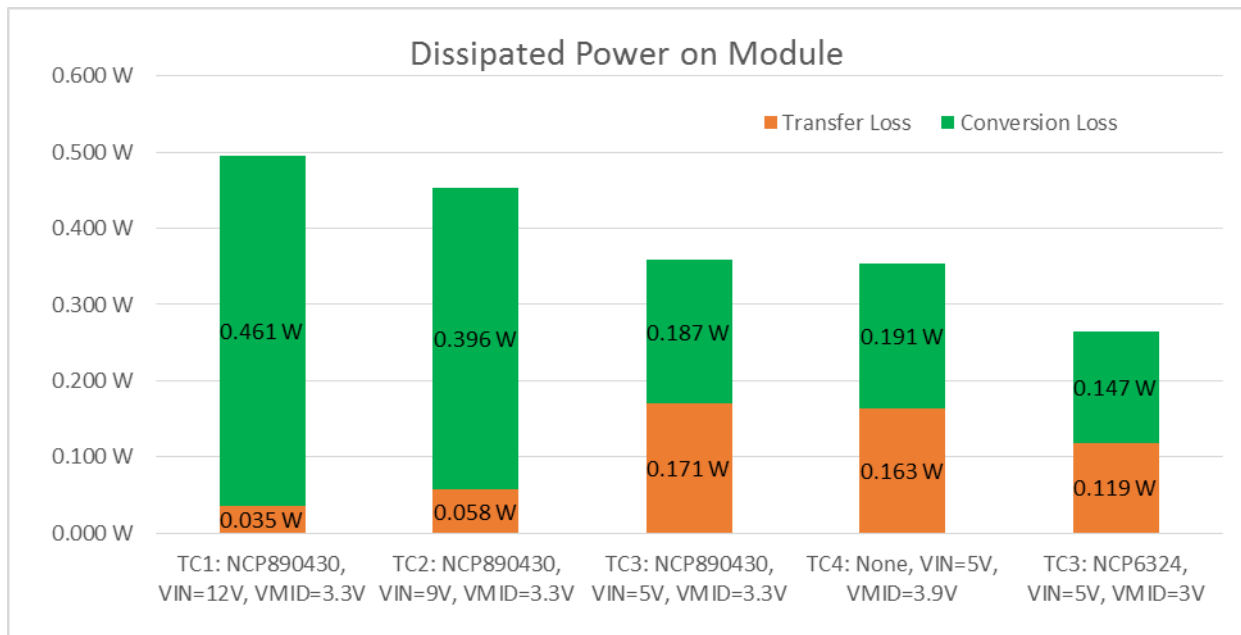

**Figure 5. Results of System Power Analysis**

Test Cases 1 & 2 show that the majority of system power loss is due to conversion losses within the regulator. The system loss is improved by decreasing the coaxial voltage ( $V_{in}$ ) to  $5V_{in}$ , where the regulator loses less power converting from 5 V to 3.3 V. There is a significant increase in transfer losses, but this increase is less than the saved conversion power, resulting in lower total system power loss. System power loss is further improved by switching to a more efficient, lower-voltage regulator— decreasing both transfer losses and conversion losses. From a system efficiency standpoint, a 5V system input voltage is preferred

as it results in the lowest amount of power dissipation on the module.

### SYSTEM HEATING

As mentioned before, higher board temperatures at or around the image sensor increases dark current generation and skews black level references. This degrades the image quality of the sensor and is a major design concern for imaging modules. System temperatures were recorded for test cases 1–4:

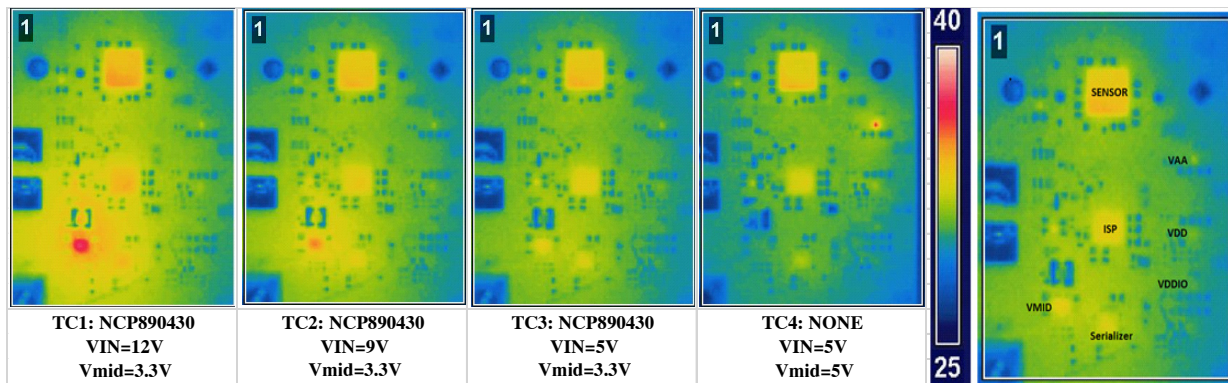


Figure 6. Thermal Images of the Reference Design Module Over Four Different Test Cases

General board heating is increased as higher Vin values are used. The reference module used provides an excessive amount of component spacing and copper surface area; despite this, the area near the image sensor sees increased temperatures with higher Vin values. In a more compact design, the heating around the sensor would be worse, emphasizing the need to dissipate unused power on the coax cable rather than the PCB. In terms of board heating, a 5 V input is preferred as it minimizes board heating, thus minimizing the potential for dark current generation.

**CONCLUSION**

There are numerous trade-offs associated with system input voltage. Higher System input voltages benefit from lower coaxial current, but suffer from increased voltage conversion losses. Lower system input voltages are the inverse. From the data collected on the automotive reference design module, a lower, 5 V system input voltage is preferred. It results in the lowest total system losses, and reduces board heating and dark current generation potential.

ON Semiconductor and are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

**PUBLICATION ORDERING INFORMATION**

**LITERATURE FULFILLMENT:**  
Literature Distribution Center for ON Semiconductor  
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free USA/Canada  
**Europe, Middle East and Africa Technical Support:** Phone: 421 33 790 2910

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)  
**Order Literature:** <http://www.onsemi.com/orderlit>

For additional information, please contact your local Sales Representative