

AND9736/D

The Best Practices for the EMC Susceptibility

NCV7693 LED Controller



ON Semiconductor®

www.onsemi.com

APPLICATION NOTE

INTRODUCTION AND DOCUMENT SCOPE

The goal of this document is to provide guidelines for the use of external components on the IOx line of the NCV7693 driver chip to achieve the best EMC performance.

The NCV7693 can be used in different applications with different possible configurations.

Based on used configuration the results and subsequently the proposed solution to increase robustness differs.

The EMC susceptibility was evaluated by use of DPI (Direct Power Injection) method according to IEC62132 part 4.

OBSERVATION

A long IOx wiring behaves like an antenna. The following guidelines describe how to limit the coupled EMC power and avoid possible system malfunction.

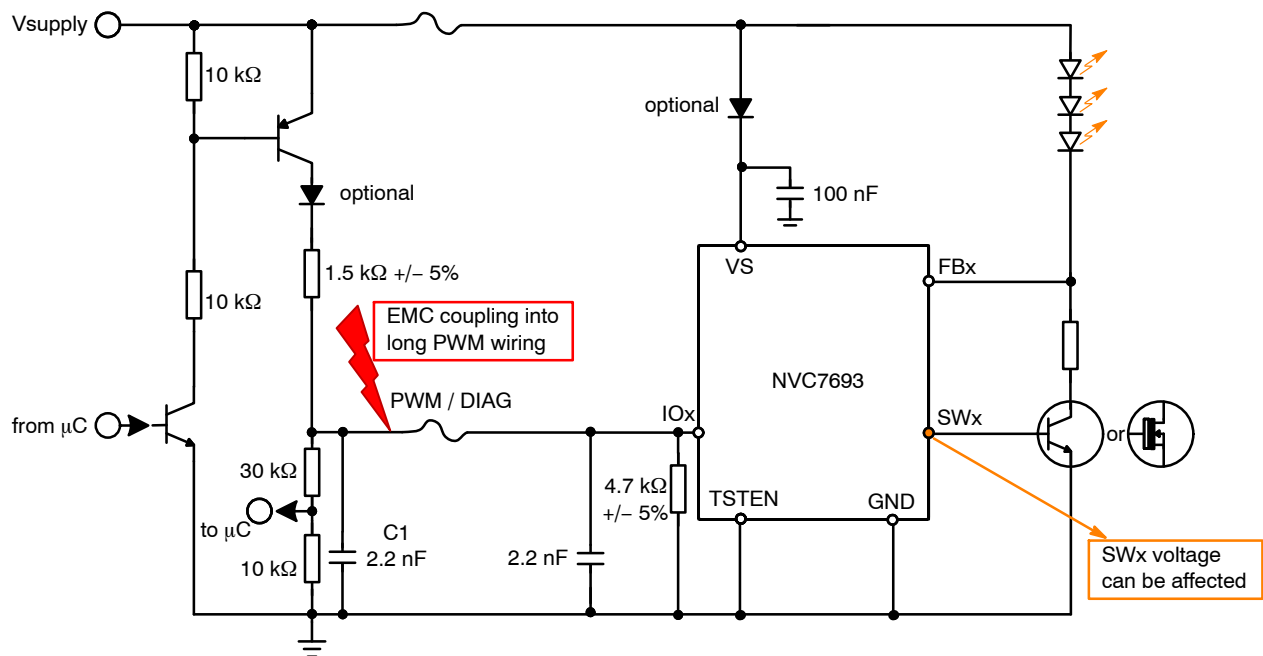


Figure 1. Application Diagram without R-C Filter

AND9736/D

The EMC sensitivity on the IOx pins can be observed. As indicated in Figure 2, the SWx voltage can be increased during EMC exposure in frequency band 400 - 1000 MHz

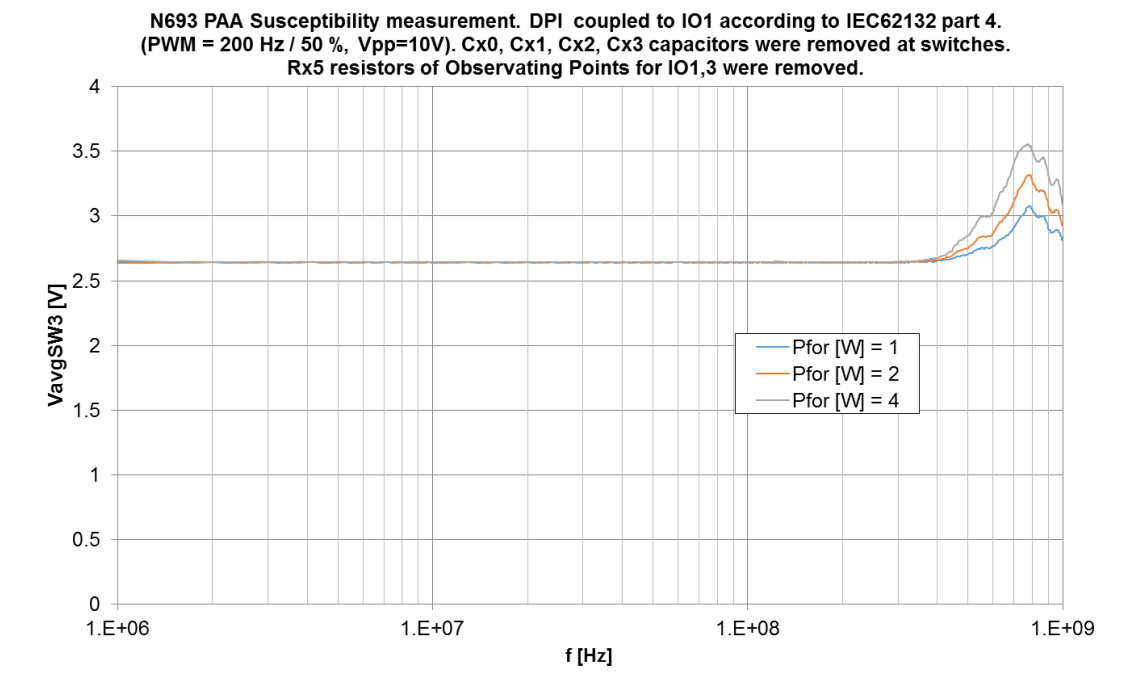


Figure 2. Increase of the SWx Signal under 1/2/4 W EMC Power [50% duty cycle; VS = 14 V]

To reduce this effect of SWx voltage increase it is highly recommended to use an external RC filter on the IOx pins as

it is described in Figure 3. With this filter the output LED current is under control.

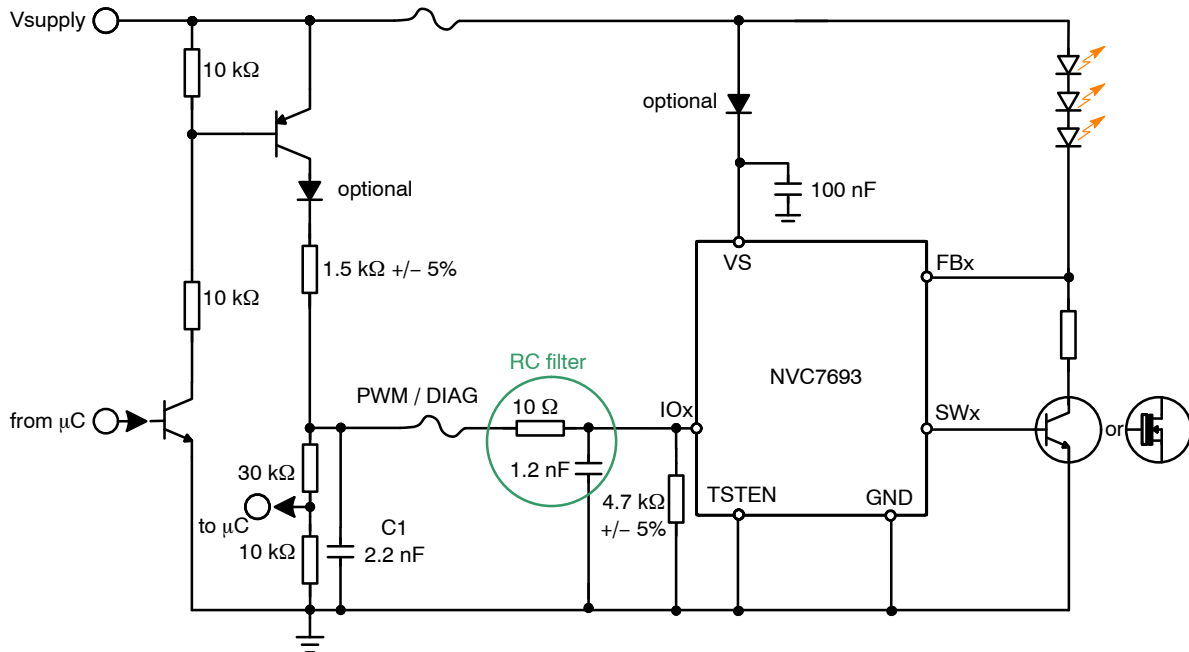


Figure 3. Application Diagram without RC Filter

TEST RESULTS

In chapters Configuration with External Bipolar Transistors and Configuration with External MOS Transistors are EMC results with proper placing of the external filters. (Should be placed as close as possible to the IOx pins, more info in chapter PCB Design Improvements) The RC filter values are 10 Ω and 1.2 nF.

Two search loops were applied to find out the maximum forward EMC power which can be applied to the IOx pins while the parameters will remain in the following tolerances:

- Pfor for Consumption Test
- Pfor for Mask test result

The maximum allowed tolerance for the consumption test is ±10% from the nominal current.

The Mask Test method observes the waveforms of the SWx signals on the oscilloscope and passes the result if the deviation from the typical waveform is less than ±10% (less than ±0.52 V and ±167 μs).

Configuration with External Bipolar Transistors

The SWx voltage and the I_{LED} current are passing EMC testing with no weakness observed (See Figure 4).

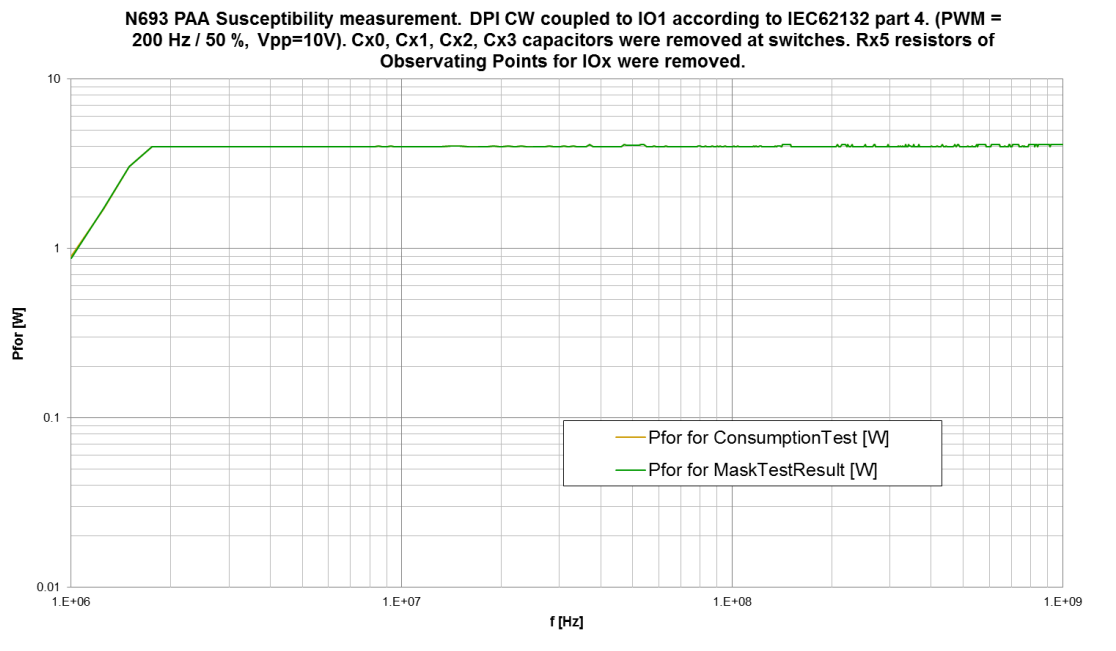


Figure 4. Bipolar Susceptibility Result Test on the IOx Pins

Configuration with External MOS Transistors

The difference between Bipolar and Mosfet drive is that the SWx outputs are not resistively loaded for the MOSFET configuration.

The results are shown in Figure 5. **The LED current is stable.** The SWx voltages are slightly increasing approx. up

to 10%. Due to the chip layout, there are differences in the EMC susceptibility between the IOx channels. The best performance in terms of the SWx voltage rise is visible for channel three.

AND9736/D

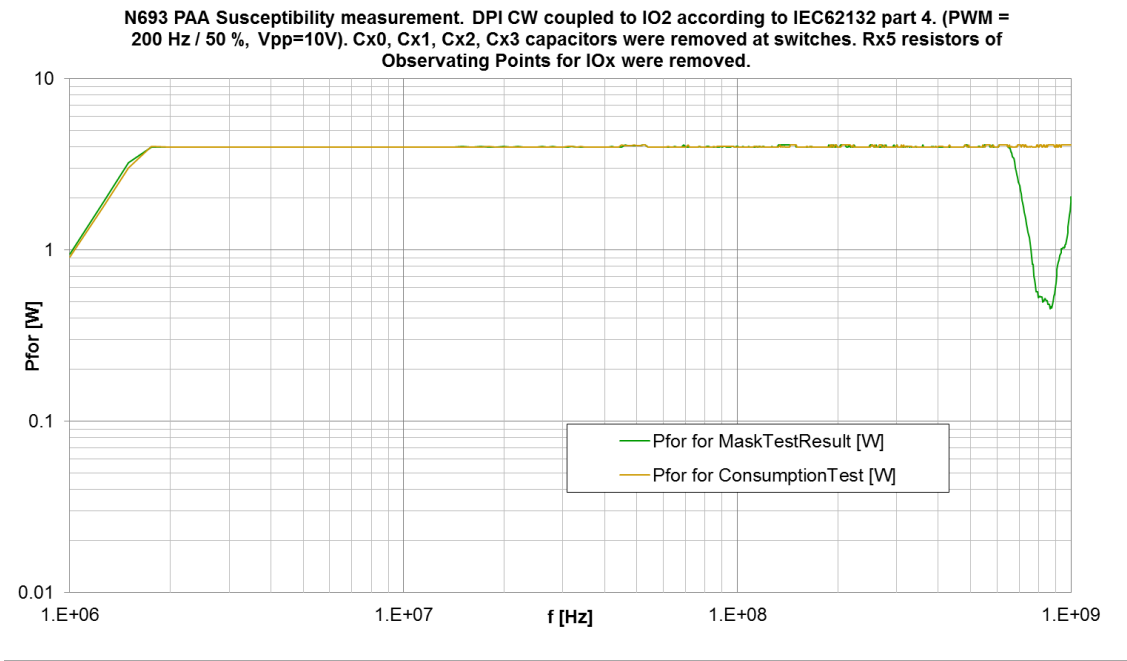


Figure 5. Mosfet Configuration for Channel 1 with the Filter

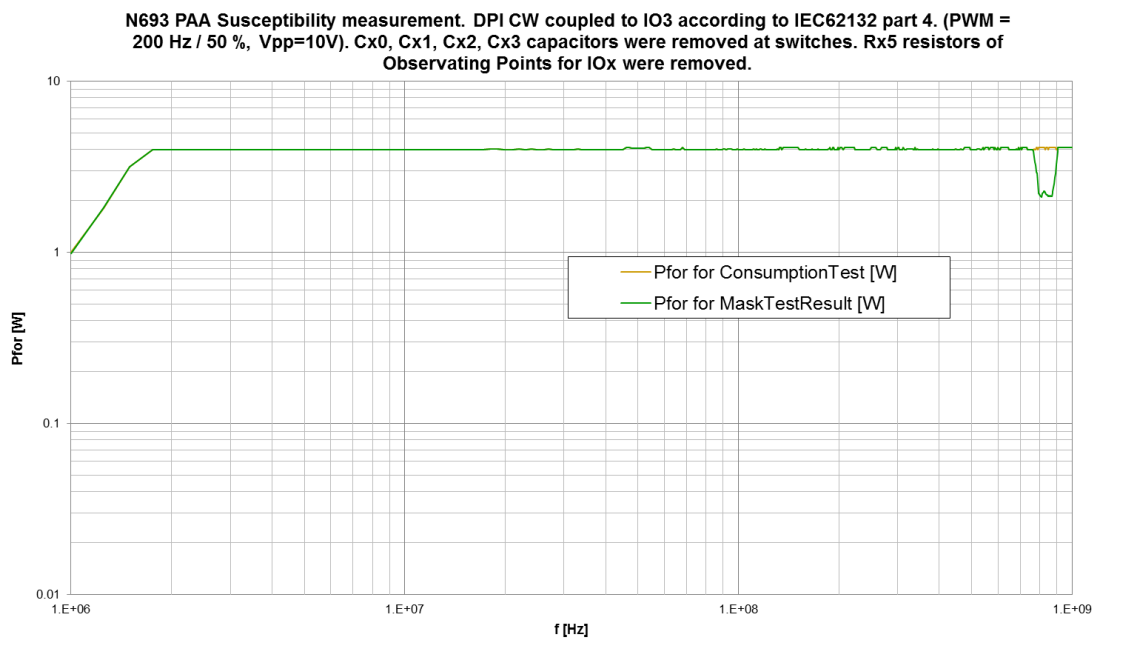


Figure 6. Mosfet Configuration for Channel 3 with the Filter

The actual value of the SWx voltage increase depends mainly on the injected power and on the supply voltage value. For the applications with DC/DC converter powered by 6.5 V supply voltage, the SWx voltage increase is practically negligible.

The applications using the Mosfet transistors having V_{GS} up to 20 V shows no deviation in I_{LED} current consumption tests.

PCB DESIGN IMPROVEMENTS

In Figure 8, there are highlighted examples of the wrong PCB design / layout which can cause higher sensitivity to the EMC noise. The Figure 9 shows better PCB design reducing the EMC sensitivity. (The notes in the figures further comment on the recommendations)

General advices:

1. The 2.2 nF capacitor on the IOx pins near the connector will absorb most of the EMC noise on the board entrance
2. The EMC power can be further reduced using R-C filter with value of 10 Ω and 1 nF
3. The 1.2 nF capacitor from R-C filter should be as close as possible to the NCV7693 IOx pins

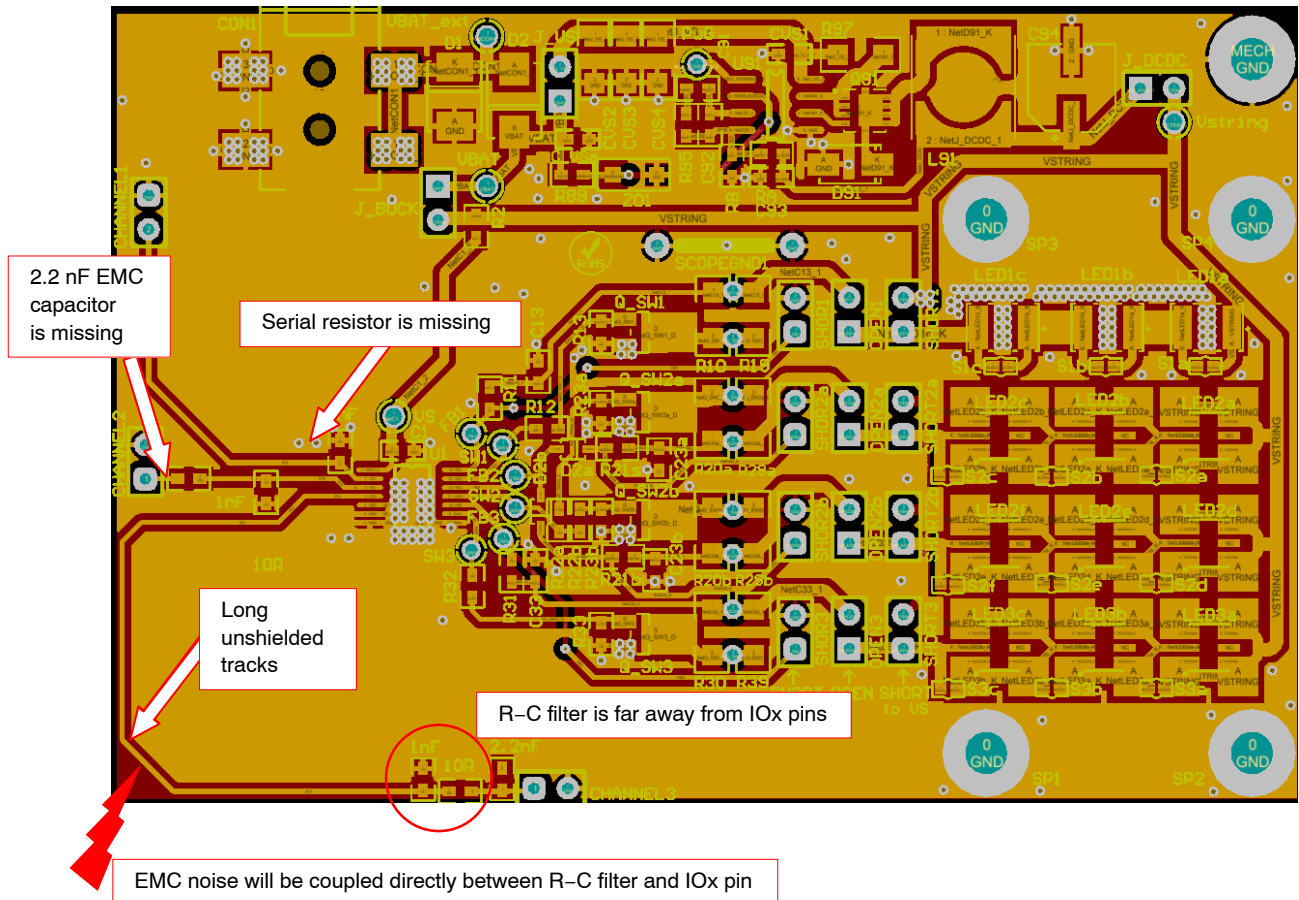


Figure 8. Example of the Wrong PCB Layout

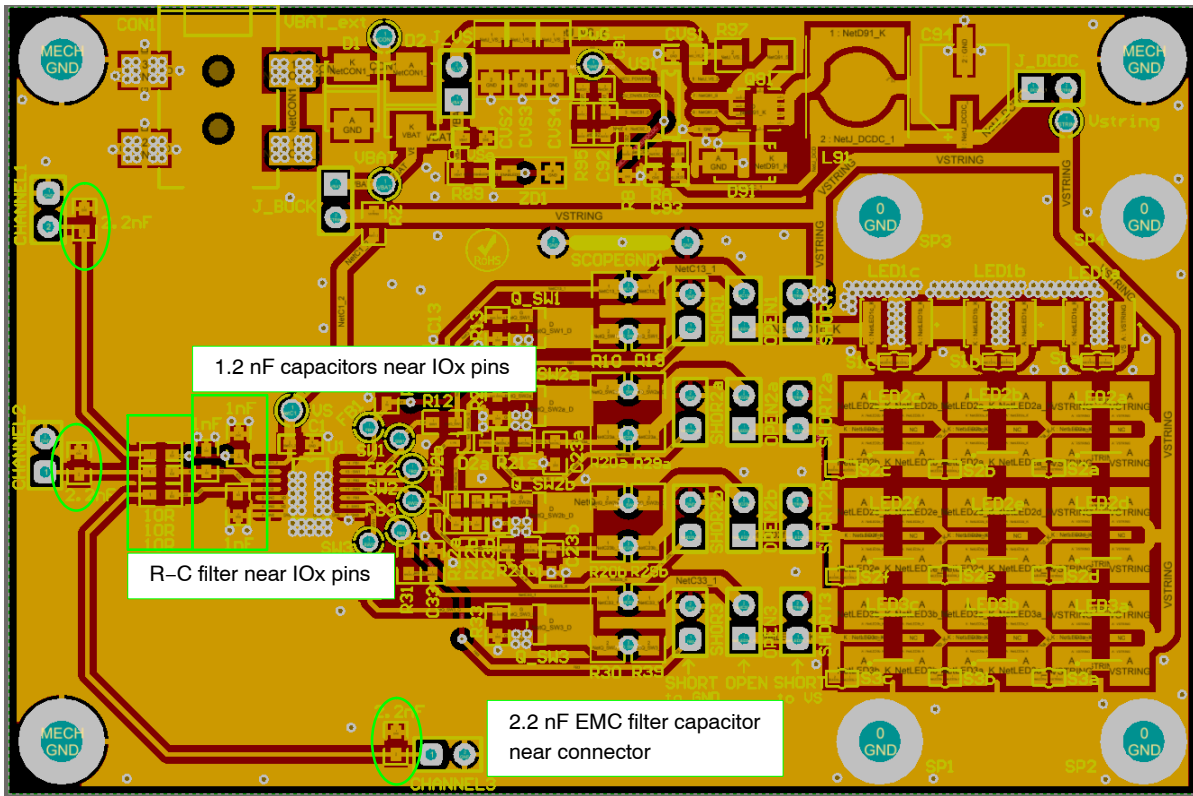


Figure 9. Example of the Correct PCB Layout

Referenced Documents

- [1] NCV7693: NCV7693 datasheet, www.onsemi.com

ON Semiconductor and are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:
 Literature Distribution Center for ON Semiconductor
 19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
 USA/Canada
Europe, Middle East and Africa Technical Support:
 Phone: 421 33 790 2910

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local Sales Representative