




The Load Switch: Application Notes on Selection and Use of ecoSWITCH™ Products

Abstract

Load switches play an important part in the management of supply domains and the protection of the loads they supply. Load switches are often used for power sequencing, standby load leakage reduction, and inrush current control. Integrated ecoSWITCH products deliver an area reducing solution, offering over current protection, load soft start, and extremely low on series resistances of sub – 20 mΩ. This article discusses the primary benefits of load switches, application considerations, and how ecoSWITCH differs from other types of integrated switch offerings. A generic cloud system application and USB power delivery example are presented to demonstrate how the addition of ecoSWITCH solves design challenges such as achieving low quiescent current, local load protection, and startup sequencing.

The Basic ecoSWITCH

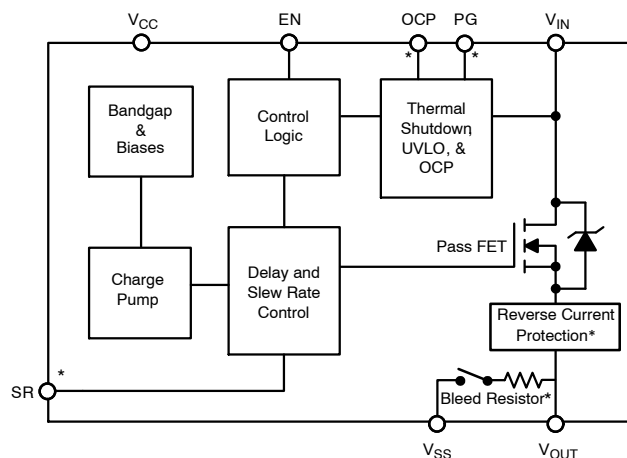Integrated load switches contain an integrated FET that allows power to be passed from VIN to VOUT when enabled. Figure 1 shows a general block diagram representing the primary functions of an ecoSWITCH.



*Not present on all ecoSWITCH products
Figure 1. Basic ecoSWITCH Diagram

The integrated pass FET is the primary component of the ecoSWITCH. All other blocks shown in Figure 1 support the pass FET in its function of passing power from Vin (source) to Vout (load).

APPLICATION NOTE

Charge Pump – The charge pump provides the voltage and current needed to charge the FET gate when turning the FET on, minimizing the on resistance of the FET.

Delay & Slew Rate Control – Turning on the FET too quickly can damage the load by allowing an in-rush current spike to pass to the load. The charging of an ecoSWITCH FET gate is controlled, thereby controlling the in-rush current and the rise time of the Vout voltage.

Control Logic – The control logic block dictates the timing and order of faults, turn on, and turn off events. The EN signal drives the control logic.

Fault Protection – Thermal protection, under-voltage lockout, and over current protection are offered on many ecoSWITCH products.

Bleed Resistor – The internal bleed resistor allows for quick dis-charge of the load and is controlled by the control logic.

Reverse Current Protection – Some ecoSWITCH products offer reverse current protection which prevents current from flowing from Vout to Vin.

All of these features play a part in the load switch trade space. Several ecoSWITCH families are offered to afford the designer with the optimal fit for their system application.

The Load Switch Trade Space

There are six key parameters that a system designer should consider when connecting and disconnecting a source from a load using an integrated FET based load switch.

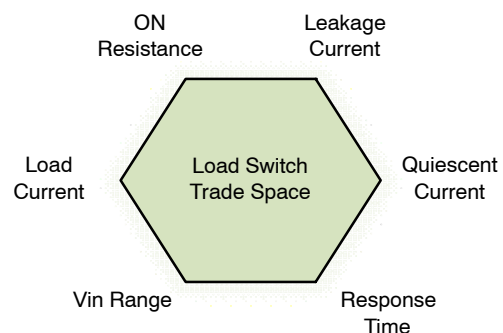


Figure 2. General Load Switch Trade Space

An ideal switch (connecting load to source) would be an open circuit when off, and a 0 Ω wire when on. Switching between an ideal open and an ideal short instantaneously can be damaging to a non-ideal source and load due to in-rush currents and transients. The load switch must intelligently deal with these transients and optimize these six parameters.

On Resistance

On resistance is directly in-line, source to load. MOSFET's have finite parasitic resistance. Electrons / holes in the inversion layer induced in a FET when its gate is charged have limited mobility. Both voltage drop from the system source to the load side of the load switch and power loss are directly proportional to the load switches ON resistance. Naturally, the lower on resistance the better. A reduction in this resistance results in direct power savings.

Max Load Current

Load switches are limited in the amount of current they can pass to a load. This is inherent due to the parasitic on resistance of the switch. Current through a resistance dissipates power through heat. Un-dissipated high levels of sustained heat damages the switch. Larger FETs are able to source more current to the load, however, a larger FET inherently has larger gate capacitance and requires more energy over time to turn on.

Response Time

Response time relates to turn ON / OFF timing, as well as fault protection timing. The size of the load switch FET is directly proportional to the energy and time it takes to turn it on. Power used to charge the gate of the FET ultimately eats into the power budget of the system. Most applications of a load switch benefit from a slower transition from OFF to ON.

Quiescent Current (Standby Current)

Quiescent current is defined by the amount of current the load switch uses when it is statically on, or off. This is in addition to any power dissipation by the load when the FET is on, and should be minimized.

Leakage Current

Current leaking from the source to the load when the load switch is OFF also eats into the system power budget. ecoSWITCH FETs are designed to maintain <1 μA leakage current.

Vin Range

The Vin Range of a load switch should exceed the application Vin supply range to provide margin. ecoSWITCH products offer minimum voltage of 1 V and lower, with maximum voltages to support 5 V, 12 V, and 24 V applications.

Benefits of ecoSWITCH

Controlled Power Up / Power Down

A load circuit is at the mercy of supply transients that can be unpredictable upon power up and power down. The diagram below shows a typical un-controlled power up / power down (in black) contrasted to the controlled current and voltage (in green) delivered to a load with an ecoSWITCH.

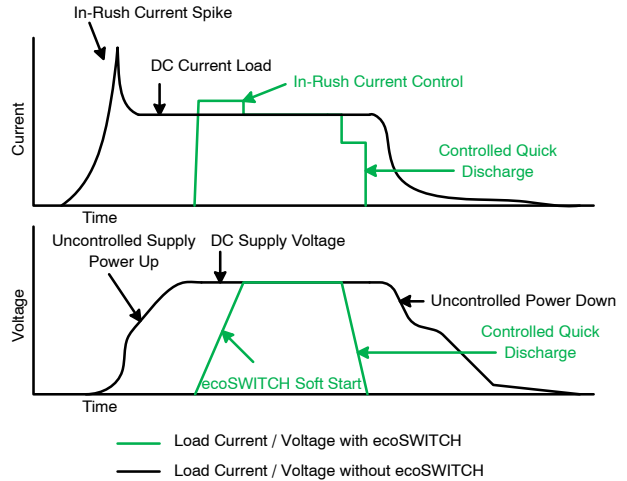


Figure 3. Load Switch Controlled Power Up / Power Down

ecoSWITCH prevents in-rush current spikes and ramps the supply voltage to the load in a controlled fashion. This is ideal for hot-swap applications where transients for power up and power down are unpredictable. On power up, ecoSWITCH provides a soft start, where the slew rate is controlled. ecoSWITCH products are available with programmable slew rate control.

Economic Cents

A discrete implementation providing base functionality uses a minimum of 9 components, adding cost to the build of materials and PCB real estate to the design. ecoSWITCH comes in package options from 2 × 2 mm to 4 × 4 mm.

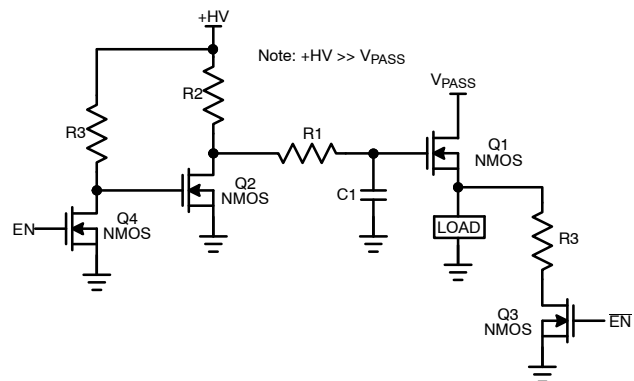


Figure 4. Typical ecoSWITCH Implementation

At a fraction of the cost an ecoSWITCH provides best in class performance with additional features not available via a 9 component discrete implementation.

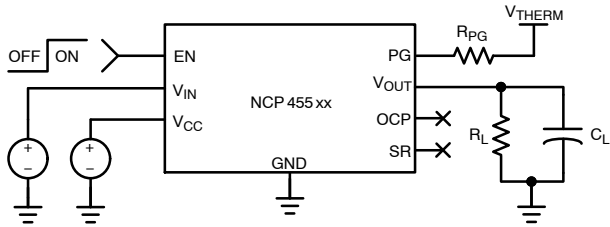


Figure 5. Typical ecoSWITCH Implementation

Reduced Leakage Current

Many designs have multiple power domains supplying sub-systems that are not needed 100% of the time. Non-critical sub-systems can be powered down using ecoSWITCH. This mitigates the leakage current from the powered down sub-systems. Load switches also allow for controlled sequencing of sub-systems.

Load Protection

Load switches can prevent damage to system loads and system supplies by disconnecting them in the event of an otherwise catastrophic failure. The ecoSWITCH offers the following load protection features:

- The over current protection (OCP) and short circuit protection features protect the part and system from sudden high-current events, such as Vout being shorted to ground or load malfunction.
- Under voltage lockout (UVLO) prevents a connection from the supply to the load when the supply voltage is too low.
- Over temperature lockout breaks the connection between the supply and the load if the temperature of the internal ecoSWITCH FET exceeds ~150°C to protect the load, switch, and supply in the event of an incorrect connection or over heating system.
- Reverse current protection is available on generation 4 ecoSWITCH products and prevents current from flowing back into the supply from the load. This is especially pertinent to USB Type C and Type C power delivery applications.

Figure 6 demonstrates OCP protection for different OCP settings on the NCP45630. By controlling the voltage on the OCP pin, the fault conditions can be catered to a specific application.

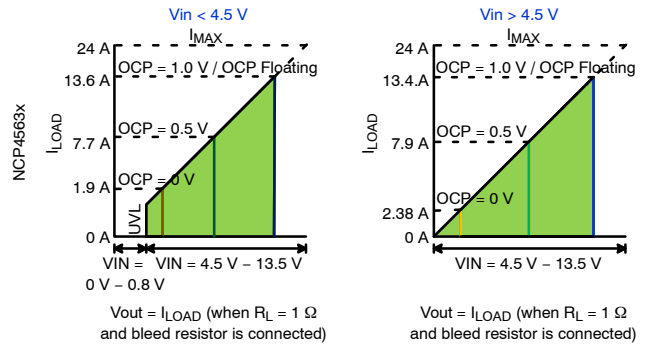


Figure 6. Safe Operating Area with Different OCP Settings

Design and Application Examples

Load switches can be used in a wide variety of applications. The feature rich ecoSWITCH family broadens the application spectrum. The following examples below show typical load switch applications. Further examples show a cloud system application, and a USB power delivery application. Load switches allow for controlled safe power supply multiplexing. Figure 7 shows one supply multiplexed to 3 loads. A controller would be used in this application to drive the EN pin to control which load gets power and when. The power for each load can be connected or disconnected to load level the system power and boost efficiency.

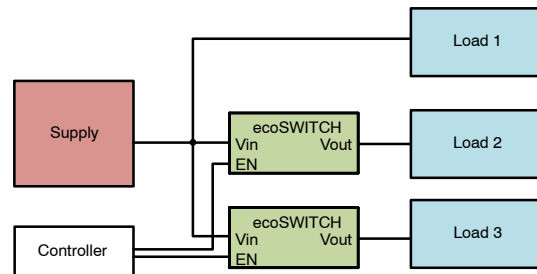


Figure 7. Basic Diagram Showing Supply Domain Management Using ecoSWITCH

Figure 8 shows a different application where one load is connected to multiple supplies through ecoSWITCH products. This application is perfect where a battery backup option exists or when the system can be powered by one of many sources.

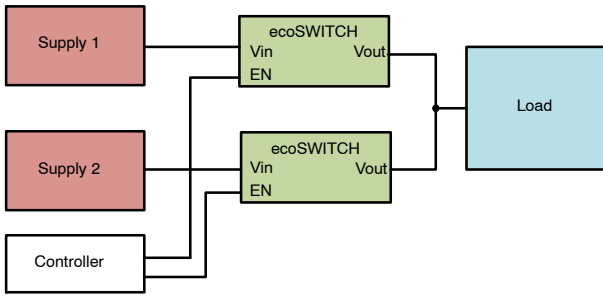


Figure 8. Power MUXing Example

Figure 9 shows yet another application where ecoSWITCH can be used to sequence the application of power to a number of loads without using a controller. Capacitance can be added to the PG outputs of each ecoSWITCH to delay the power up of the next load in the sequence.

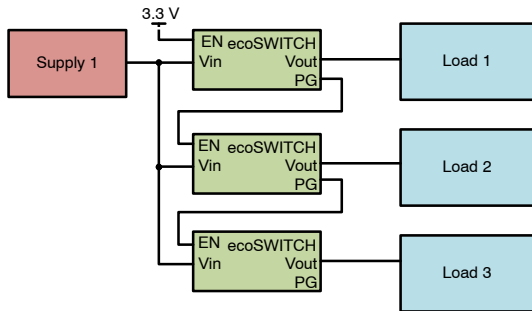


Figure 9. Power Sequencing Example without Controller

Figure 11 shows an example Cloud System application. In this application, the green boxes labeled “eS” represent ecoSWITCH products in the system. The load switches are placed after the DC/DC conversion of the primary supply, but before the internal loads, managing their connection to regulated power.

The soft start and quick power down features of ecoSWITCH products are conducive to USB applications. The diagram below shows how an ecoSWITCH with reverse current protection can be used for USB Type-C power delivery. The supply can be internal to the host, or provided from an external host, such as a device with an internal battery capable of powering other devices over USB, but can also be charged over USB.

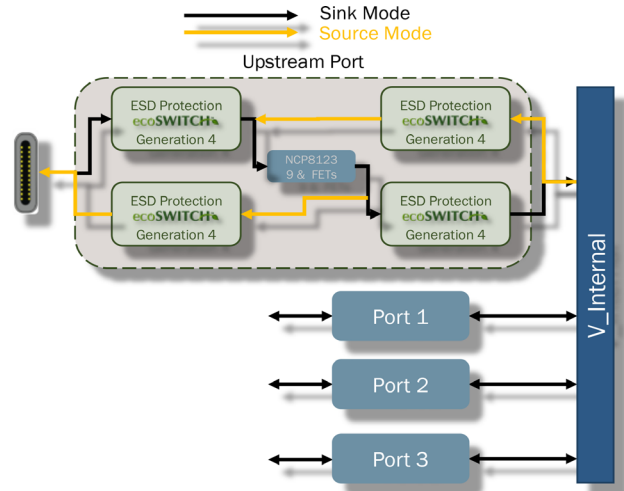


Figure 10. NCP457xx Supporting USB Type-C Power Delivery with Reverse Current Protection

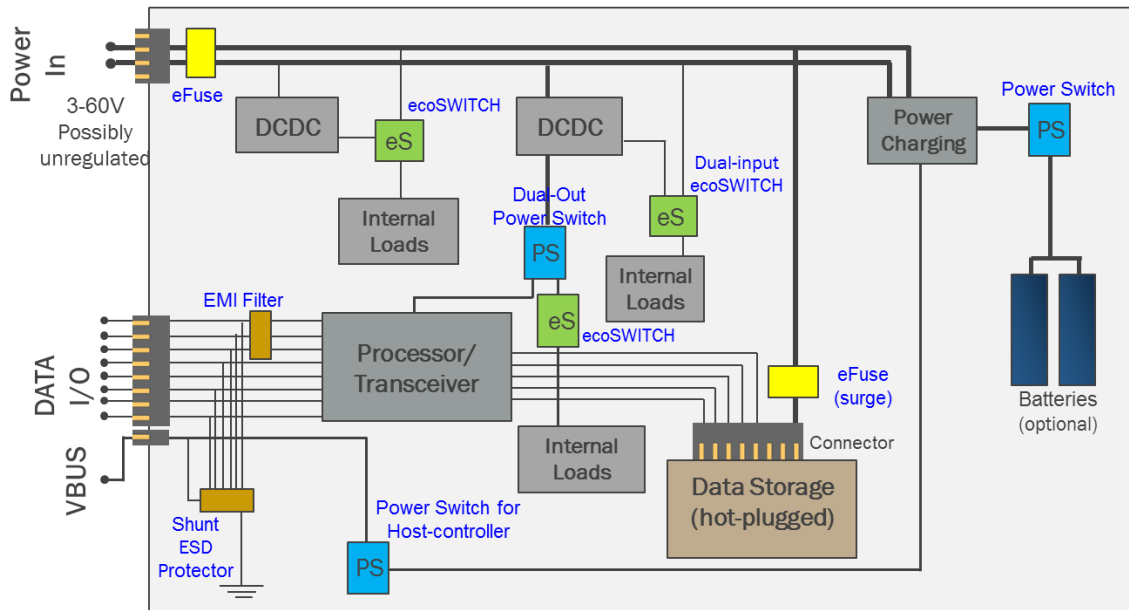


Figure 11. Generic Cloud System

AND9848/D

Basic Load Switch Calculations

The following calculations can be used when determining the specifications required the load switch.

Voltage Drop

Voltage drop requirements from the supply to the load dictate the acceptable Ron specification. Use equation 1 to determine acceptable Ron maximum.

$$R_{ON, \max} = \frac{V_{\text{Drop}}}{I_{\text{LOAD}}} \quad (\text{eq. 1})$$

In-rush Current

The total load capacitance presented to the load switch determines the in-rush current where the initial current (I_o at time 0) is very large. ecoSWITCH has slew rate control (or soft start) to limit the initial current to a known acceptable value. Equation 2 below is used to define the controlled in-rush current.

$$I_{\text{in-rush}} = \frac{dv}{dt} \cdot C_L \quad (\text{eq. 2})$$

Where:

dv/dt is the slew rate setting, programmable on most ecoSWITCH products.

C_L is the total capacitive load

Power Dissipation

Equation 3 below is used to calculate the total power dissipation of the load when powered through the load switch.

$$P_D = V_{in} \cdot I_Q + I_{\text{LOAD}}^2 \cdot R_{ON} \quad (\text{eq. 3})$$

Where:

V_{in} is the input supply voltage

I_Q is the quiescent current

I_{LOAD} is the load current

R_{ON} is the on resistance of the load switch

When the load switch is disabled, is limited to the standby current, and is limited to any leakage from V_{in} to V_{out} through the disabled load switch, which is quickly bled down as any charge held by the total load capacitance is discharged through the ecoSWITCH internal bleed resistor.

ecoSWITCH Family Pedigree

The Table 1 below shows the full ecoSWITCH product line offering. Generally, there is a trade-off between features, cost and size. Many options are available to facilitate the optimization of this trade space for any given application.

Table 1. ecoSWITCH PRODUCT OFFERING (See individual datasheets for detailed specifications)

EcoSWITCH Part Number	Operating Input Voltage	Under Voltage Lockout	Thermal Shutdown	Short Circuit	Power Good	Variable Slew Rate	Reverse Current	Load Bleed	Over Current	RoHS Compliant	Production Availability
<5 mΩ											
NCP4545	1 V – 12 V					✓				✓	Production
NCP4545-L	1 V – 12 V					✓				✓	Production
NCP45560-H	1 V – 12 V	✓	✓	✓	✓	✓		✓		✓	Production
NCP45560-L	1 V – 12 V	✓	✓	✓	✓	✓		✓		✓	Production
<10 mΩ											
NCP45650	1 V – 12 V	✓	✓	✓	✓	✓		✓	✓	✓	Q2 '19
NCP45651	1 V – 12 V	✓	✓	✓	✓	✓			✓	✓	Q2 '19
NCP45520-H	1 V – 12 V	✓	✓	✓	✓			✓		✓	Production
NCP45520-L	1 V – 12 V	✓	✓	✓	✓			✓		✓	Production
NCP45521-H	1 V – 12 V	✓	✓	✓	✓	✓		✓		✓	Production
NCP45521-L	1 V – 12 V	✓	✓	✓	✓	✓		✓		✓	Production
NCP45540-H	1 V – 12 V	✓	✓	✓	✓	✓		✓		✓	Production
NCP45540-L	1 V – 12 V	✓	✓	✓	✓	✓		✓		✓	Production
NCP45541-H	1 V – 12 V				✓	✓		✓		✓	Production
NCP45541-L	1 V – 12 V				✓	✓		✓		✓	Production
NCP45630	1 V – 12 V	✓	✓	✓	✓	✓		✓	✓	✓	Q2 '19
NCP45631	1 V – 12 V	✓	✓	✓	✓	✓			✓	✓	Q2 '19
<20 mΩ											
NCP4543	1 V – 12 V						✓	✓		✓	Production
NCP45522-H	1 V – 12 V	✓	✓	✓	✓			✓		✓	Production
NCP45522-L	1 V – 12 V	✓	✓	✓	✓			✓		✓	Production
NCP45523-H	1 V – 12 V	✓	✓	✓	✓	✓		✓		✓	Production
NCP45523-L	1 V – 12 V	✓	✓	✓	✓	✓		✓		✓	Production
NCP45524-H	1 V – 12 V				✓			✓		✓	Production
NCP45524-L	1 V – 12 V				✓			✓		✓	Production
NCP45525-H	1 V – 12 V				✓	✓		✓		✓	Production
NCP45525-L	1 V – 12 V				✓	✓		✓		✓	Production
NCP45526-H	1 V – 12 V				✓			✓		✓	Production
NCP45610	1 V – 12 V	✓	✓	✓	✓	✓		✓	✓	✓	Q2 '19

1 V – 24 V <10 mΩ

Other ON SEMICONDUCTOR Integrated Power Switch Offerings

ON Semiconductor offers other product families that further our solution diversification. ecoSWITCH products have focused on providing best in class ultra-low Ron resistance. IntellMax products focus on applications where low operational power and low cost are more important than low power dissipation in the series FET. eFuse products target high side switch applications where over-voltage protection is needed. Whatever the need, ON Semiconductor provides best in class solutions enabling customer success.

Conclusion

Integrated ecoSWITCH load switches deliver an area reducing solution, offering over current protection, load soft start, and extremely low on series resistances of sub – 20 mΩ. Load switches are a critical component to achieving efficient low cost power distribution in complex systems.

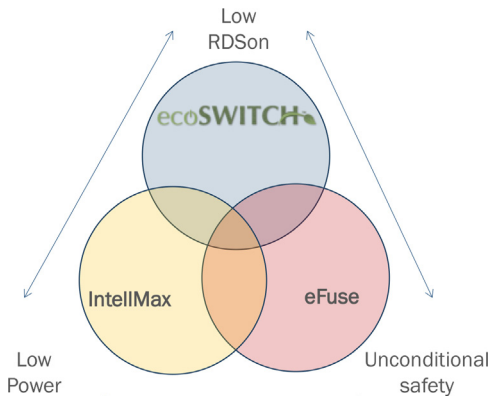



Figure 12.

ecoSWITCH is trademark of Semiconductor Components Industries, LLC (SCILLC) or its subsidiaries in the United States and/or other countries.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:
 Literature Distribution Center for ON Semiconductor
 19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
 USA/Canada
Europe, Middle East and Africa Technical Support:
 Phone: 421 33 790 2910

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local Sales Representative