

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



ON Semiconductor

Buck-Boost Converter for 3 A LEDs


Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
NCP3020A NTMFS5844	Battery-powered high current LED driver	10 to 25 Vdc	60 Watts	Buck-Boost	None

Output Voltage	15 – 22Vdc
Nominal Current	1 – 3A
Nominal Efficiency	82 - 89%

Introduction

There are situations when a converter is required to perform as a boost or a buck and to seamlessly shift from one mode to the other depending on the output to input voltage ratio. For example if 18 V / 2 A are required to drive a string of power LEDs while the input power comes from a 12 or 18V battery pack, this translates into a 10 to 25 V input range for the converter.

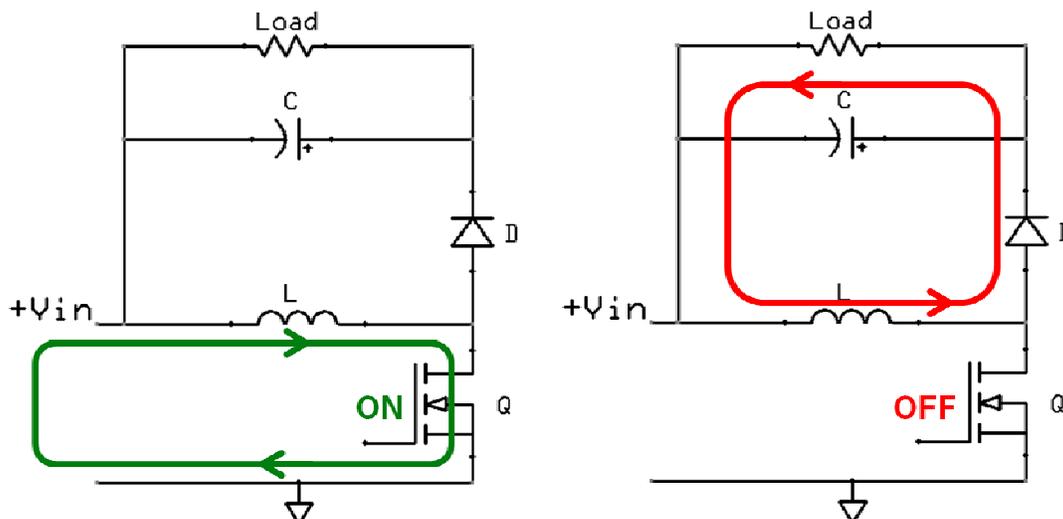Since LEDs don't necessarily need a drive voltage that's referenced to ground, a "floating" boost arrangement can be used and this pseudo buck-boost can be both simple and efficient. During the ON time, the input current flows from the input supply through the inductor and MOSFET to GND. During the OFF time, the inductor keeps flowing and its path is closed through the load.



This Design Note describes such a circuit which operates from 10 to 25 V input and produces 15 to 22 V in order to drive a string of several power LEDs at up to 3 A.

Circuit Description


Having a 5 to 28 V input range, the NCP3020A buck controller is well suited for the application. The high side driver is used to drive the boost MOSFET while the low side one is left open.

The output current is sensed by Rcs1 resistor and the current mirror circuit consisting of Q2 – Q5 makes sure a fraction of this current flows through resistor R3. The voltage across R3 is then fed to the FB pin of the controller.

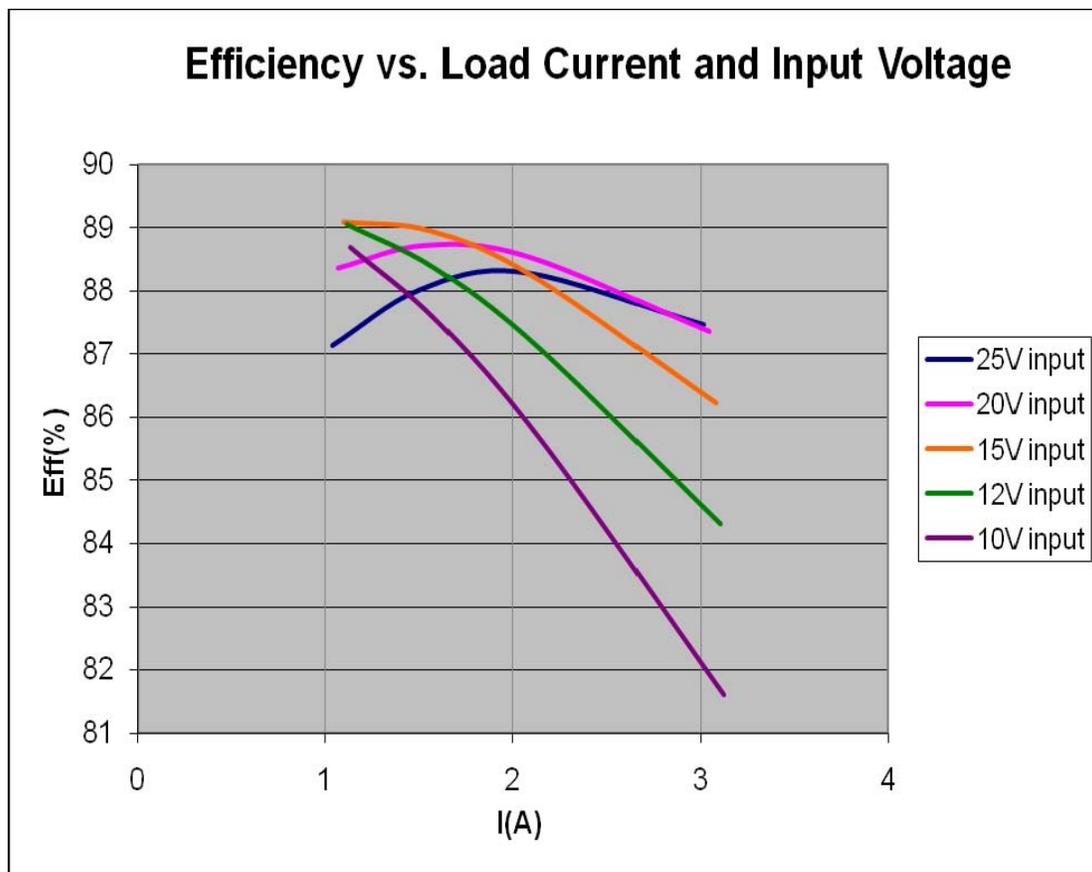
Q6 and adjacent components help implement a soft start function. At power-up, Q6 is initially off and resistor R9 appears in series with R3, ensuring a low current at start. Then the voltage across C10 slowly increases and Q6 gradually turns on and shunts R9 and from that moment on, R3 alone controls the output current.

The ON-OFF switch is placed in a low current path providing power just for the controller. This arrangement allows a low cost switch to be used, but the user must be aware that approximately 0.5 mA of leakage current exists due to the current mirror. If this situation is not acceptable, than the shown switch should be by-passed and a series power MOSFET should be used in the power path to turn on and off the converter.


MOSFET Q1 and diode D1 may seem oversized for a circuit required to provide up to 3 A, but peak currents can reach in excess of 10 A and efficiency will suffer if weaker parts are used. The efficiency was measured with an electronic load simulating a string of LED's requiring 22 V at up to 3 A.



Schematic

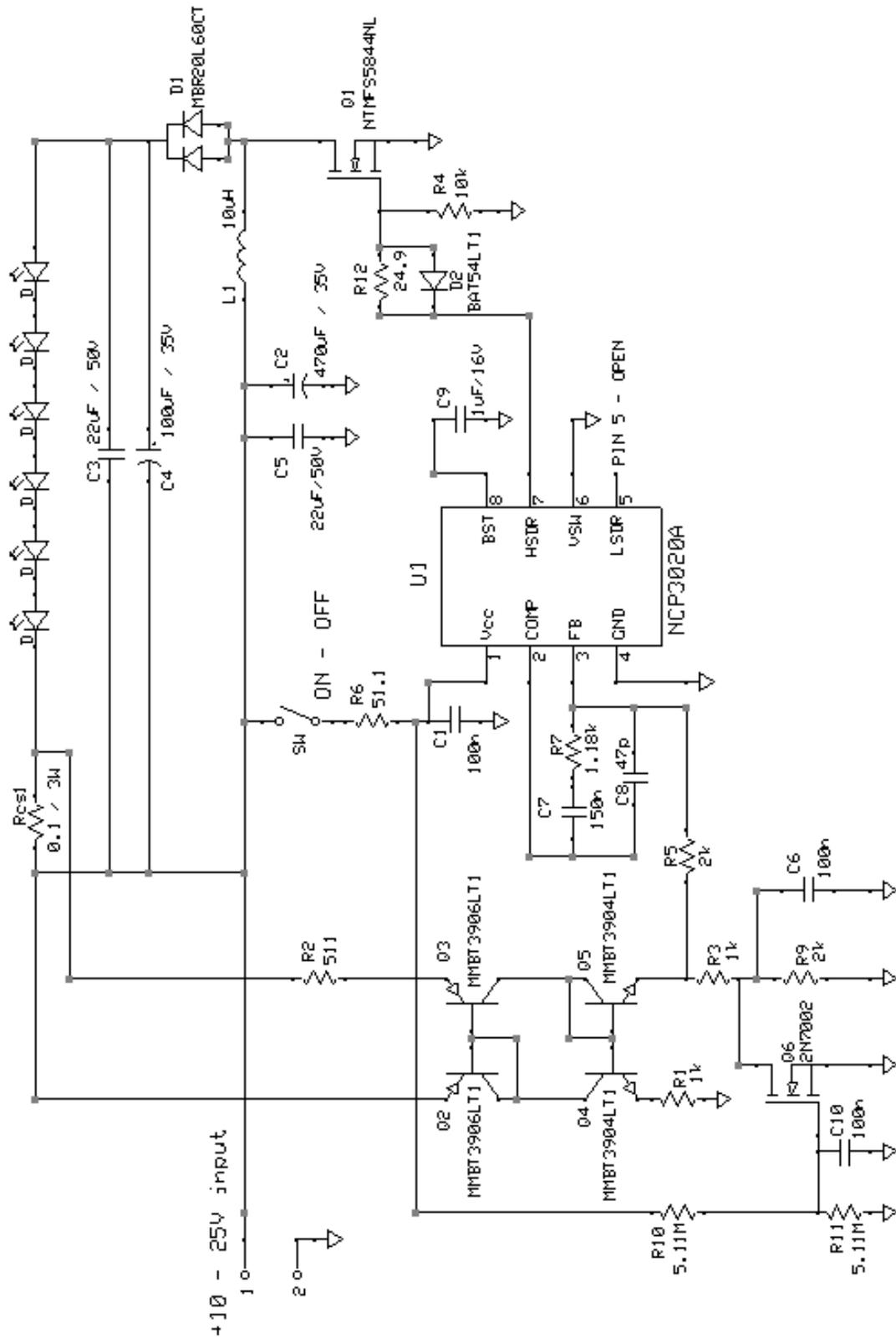


Start-up

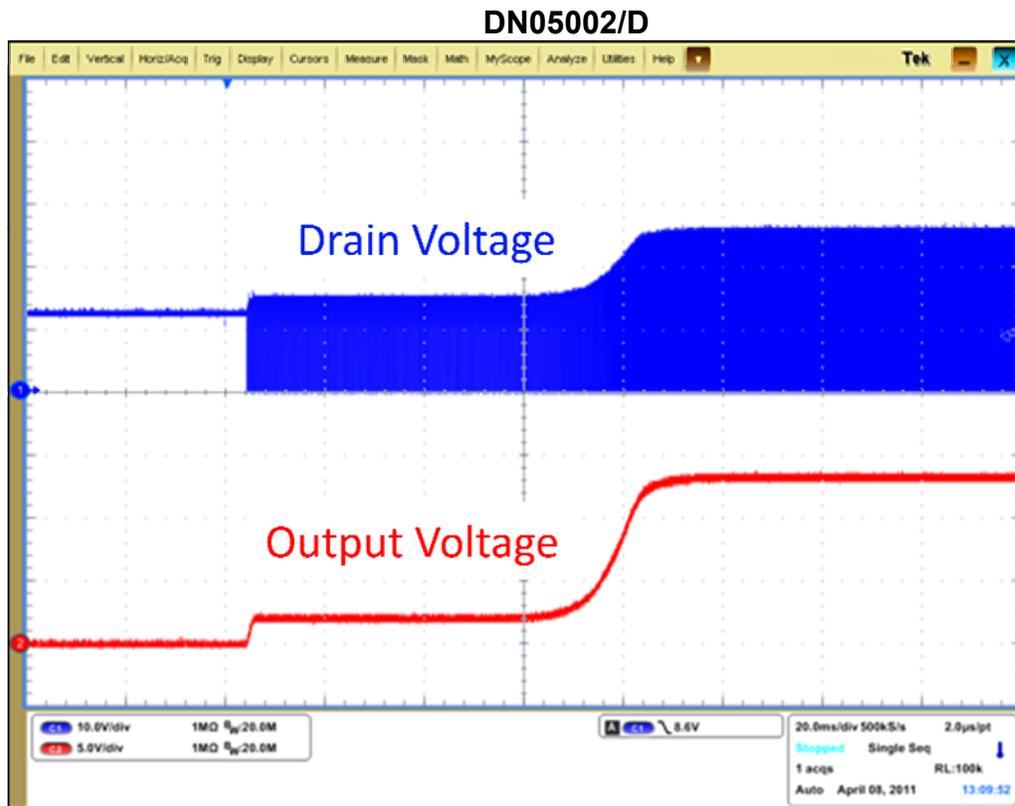

Transient Response

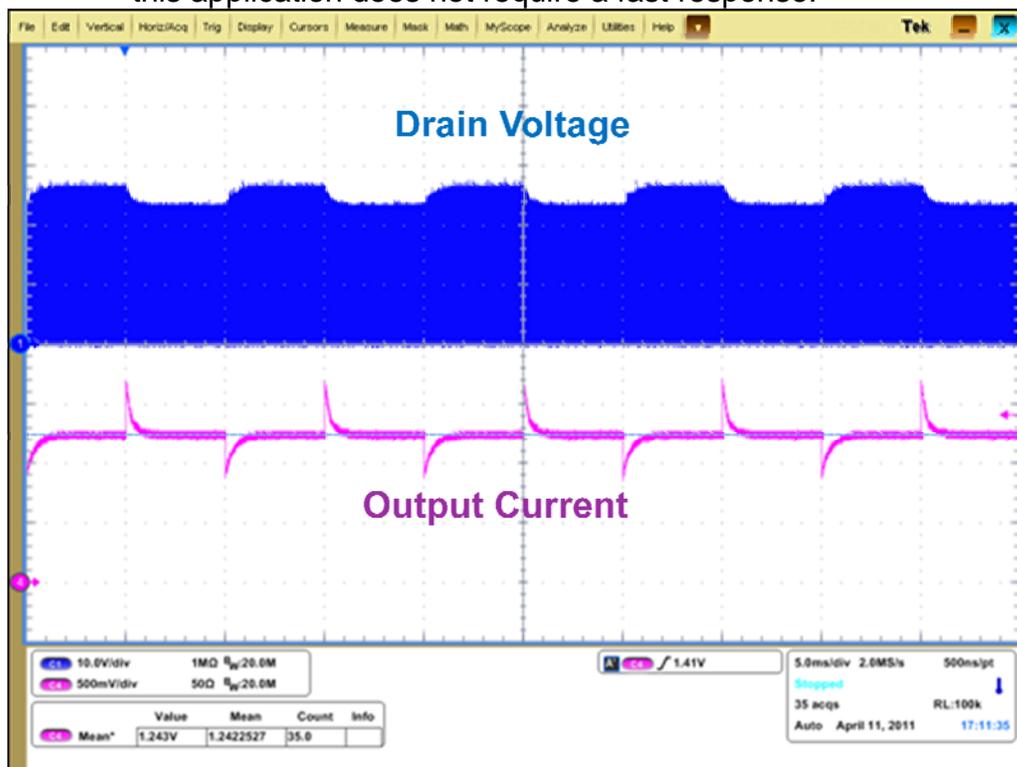For this test, a second load was switched on and off in parallel with the main load. The converter successfully maintains a constant output current. The transient spikes are totally acceptable since this application does not require a fast response.



Output Current Adjustment

DN05002/D

Output current is set by resistor R2 which can be chosen according to the table below.

I_{out} (A)	R2 (Ω)
1	187
1.5	267
2	348
3	511

Key Features

- Seamless “buck to boost” transition
- High efficiency
- Constant output current
- Simplicity

References

- Data sheet [NTMFS5844NL](#): 60 V, 60 A, 12 m Ohm Single N-Channel Power MOSFET in SO-8FL
- Data sheet [NCP3020](#): 28V Synchronous Buck Controller

© 2011 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note “AS IS” and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party’s intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Michael Borza, e-mail: mborza@onsemi.com