

# ON Semiconductor

## Is Now

# onsemi™

To learn more about onsemi™, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

---

**onsemi** and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



ON Semiconductor

## Positive Input to Negative Output Conversion using a Buck Converter

Device	Application	Input Voltage	Output Voltage	Topology	I/O Isolation
NCP3170 NCP3020	Power supplies	Positive	Negative	Buck	None

<b>Input Voltage</b>	+5, 8, 12 Vdc
<b>Output Voltage</b>	-3.3, -5 Vdc
<b>Nominal Current</b>	0.5 A or 8 A
<b>Nominal Efficiency</b>	80 - 90%

### Introduction

The buck-boost is usually the topology of choice for voltage inverting applications. There are plenty of components to choose from and most of them even come with integrated transistors or mosfets. They can work in hysteretic mode or they can switch at a fixed frequency. Very often when more power is required, an external transistor is used and while the circuit can deliver the needed power, the efficiency is very poor.

This Design Note describes an alternate solution that is very simple, but little known. It provides superior efficiency while using commonly available components.

### Circuit Description

The circuit is built around a buck converter. Depending on output power, a regulator with integrated fets or a controller with external fets can be used.

The circuit in Figure 1 uses the NCP3170A to obtain a -5 V rail from a +8 V input at up to 0.5A output current. Efficiency reaches 85%

The circuit in Figure 2 converts a +12 V input into -3.3 V or -5V at up to 8A. 90% efficiency is achievable.

There are many more options available for buck controllers and converters as well as for mosfets. The user needs to pay attention to the voltage rating of the part. In this application the controller and the mosfets will need to withstand a voltage equal to input voltage plus output voltage. For example the circuit in figure 1 needs to be able to handle  $8 + 5 = 13$  V.

Figure 1



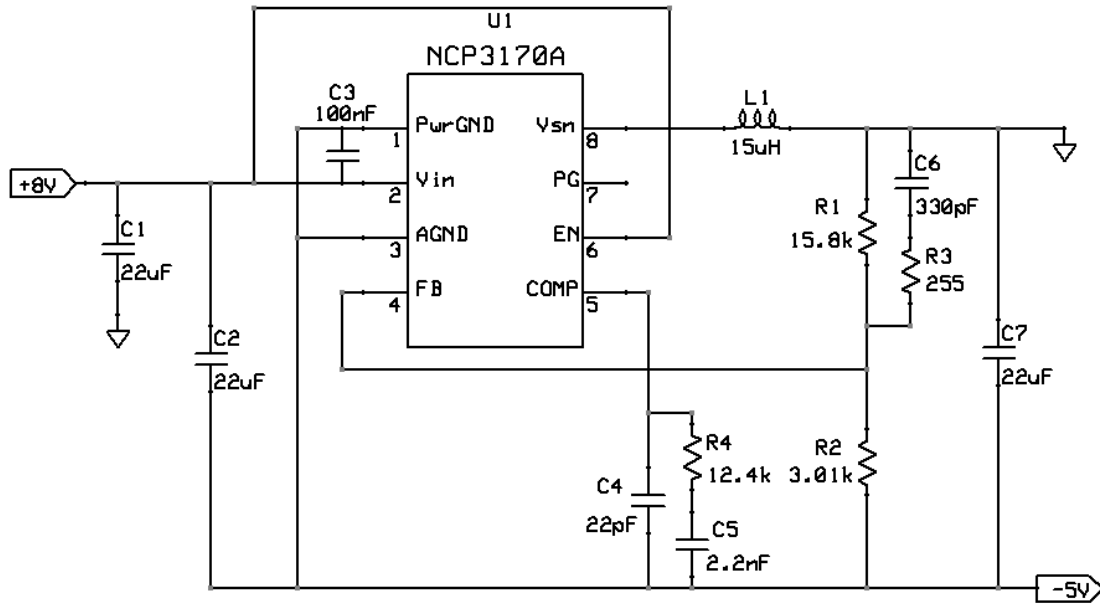
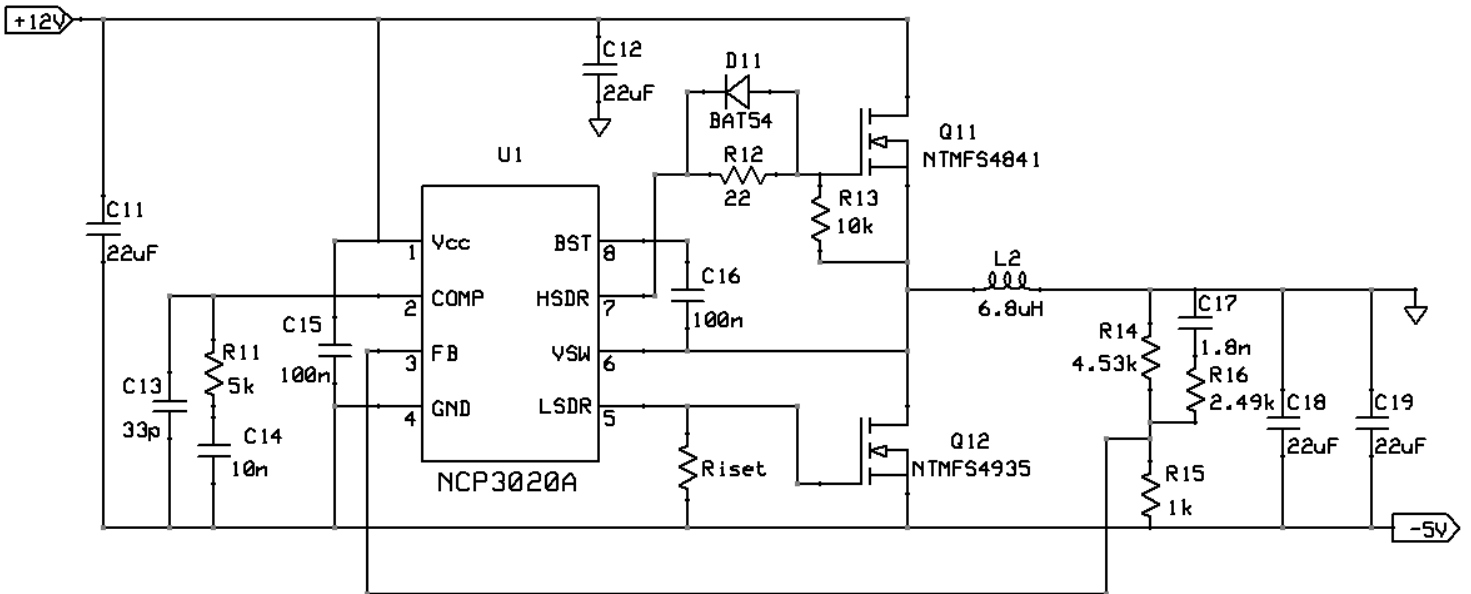


Figure 2

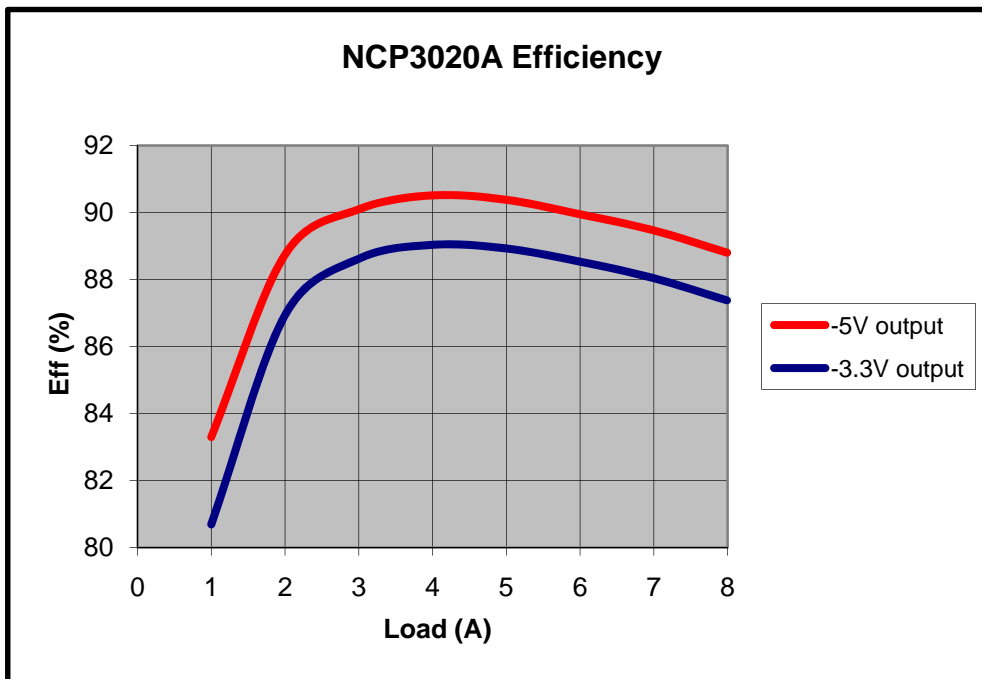

### Efficiency Curves

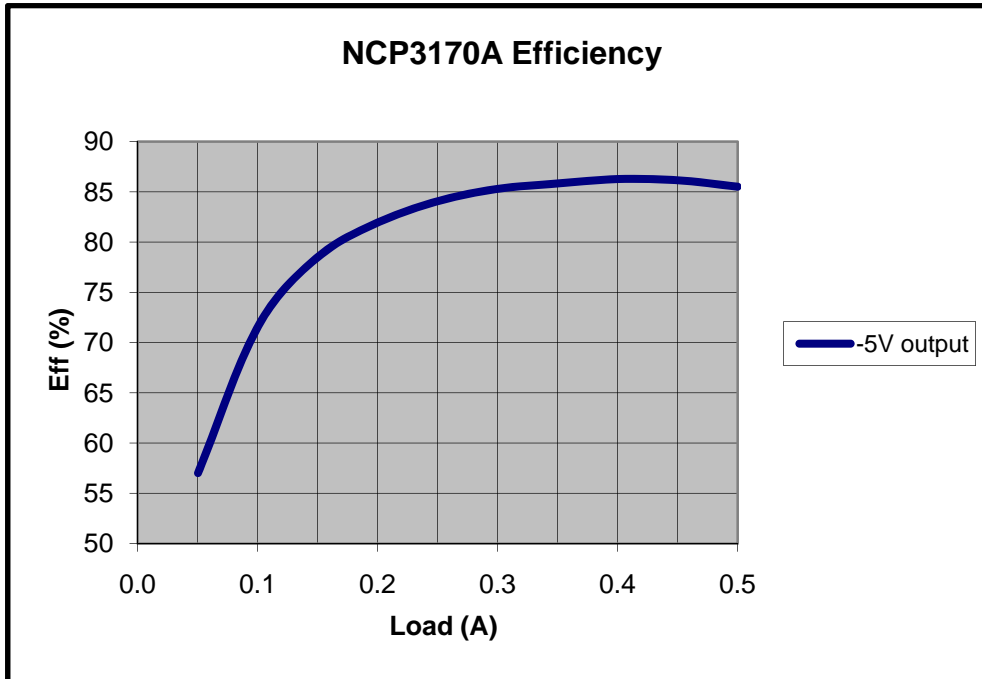

## Key Features

- Simple and familiar topology
- High efficiency
- Many options available for component selection

## References

- Data sheet [NCP3170](#): 3A Switching regulator
- Data sheet [NCP3020](#): 28V Synchronous Buck Controller

---

© 2011 ON Semiconductor.

**Disclaimer:** ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

*Design note created by Michael Borza, e-mail: mborza@onsemi.com*