

ON Semiconductor

Is Now

The logo for onsemi, featuring the word "onsemi" in a dark teal, lowercase, sans-serif font. The letter "i" is stylized with a white dot and a teal vertical bar. A small orange triangle is positioned above the top right of the "i". A trademark symbol (TM) is located to the right of the logo.

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



ON Semiconductor

20 Watt, High Efficiency, Off-line Power Supply Using Synchronous Output Rectification

Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
NCP1251B NCP4303 NCP431	White Goods, Small Instruments, E-Meters, Industrial Equipment	90 – 267 Vac	20 to 25 Watts	DCM Flyback With Synchronous Rectifier	3 kV

Other Specification

	Output 1	Output 2	Output 3	Output 4
Output Voltage	12 Vdc	N/A	N/A	N/A
Ripple	< 2%	N/A	N/A	N/A
Nominal Current	1 to 1.8 Amps	N/A	N/A	N/A
Max Current	1.8 Amps	N/A	N/A	N/A
Min Current	zero	N/A	N/A	N/A

PFC (Yes/No)	No
Typical Efficiency	84% at full load
Inrush Limiting / Fuse	Yes
Operating Temp. Range	0 to 50C
Cooling Method / Supply Orientation	Convection NA
Signal Level Control	No

Others	Input EMI filter
--------	------------------

Circuit Description

This Design Note describes a very simple, low cost, yet high efficiency off-line flyback power supply using ON Semiconductor's NCP1251B current mode controller (TSOP6 package) in conjunction with the NCP4303 synchronous MOSFET rectifier controller. This Design Note is an extension of DN05012/D for engineers who require the highest possible efficiency for a 12 volt, 15 to 25 watt application. Other output voltages from up to 28 Vdc are easily implemented by modifying the values (or ratings) of the secondary circuit components and T1's secondary turns.

The primary power circuitry and transformer design is identical to the circuit of DN05012/D. The secondary circuitry contains the NCP4303

controller driving synchronous MOSFET rectifier Q3. Details of the various features and parameters of this controller can be found in the devices' data sheet available at the ON Semiconductor web site.


The plot shown below compares the efficiency curves of the original design using Schottky rectifiers with this synchronous rectifier version.

Key Features

- Input EMI filter for conducted EMI compliance
- Simple, single switch DCM flyback topology
- Very high efficiency with synchronous output rectification
- Current mode control with adjustable output current
- Low cost components

DN05028/D

Schematic

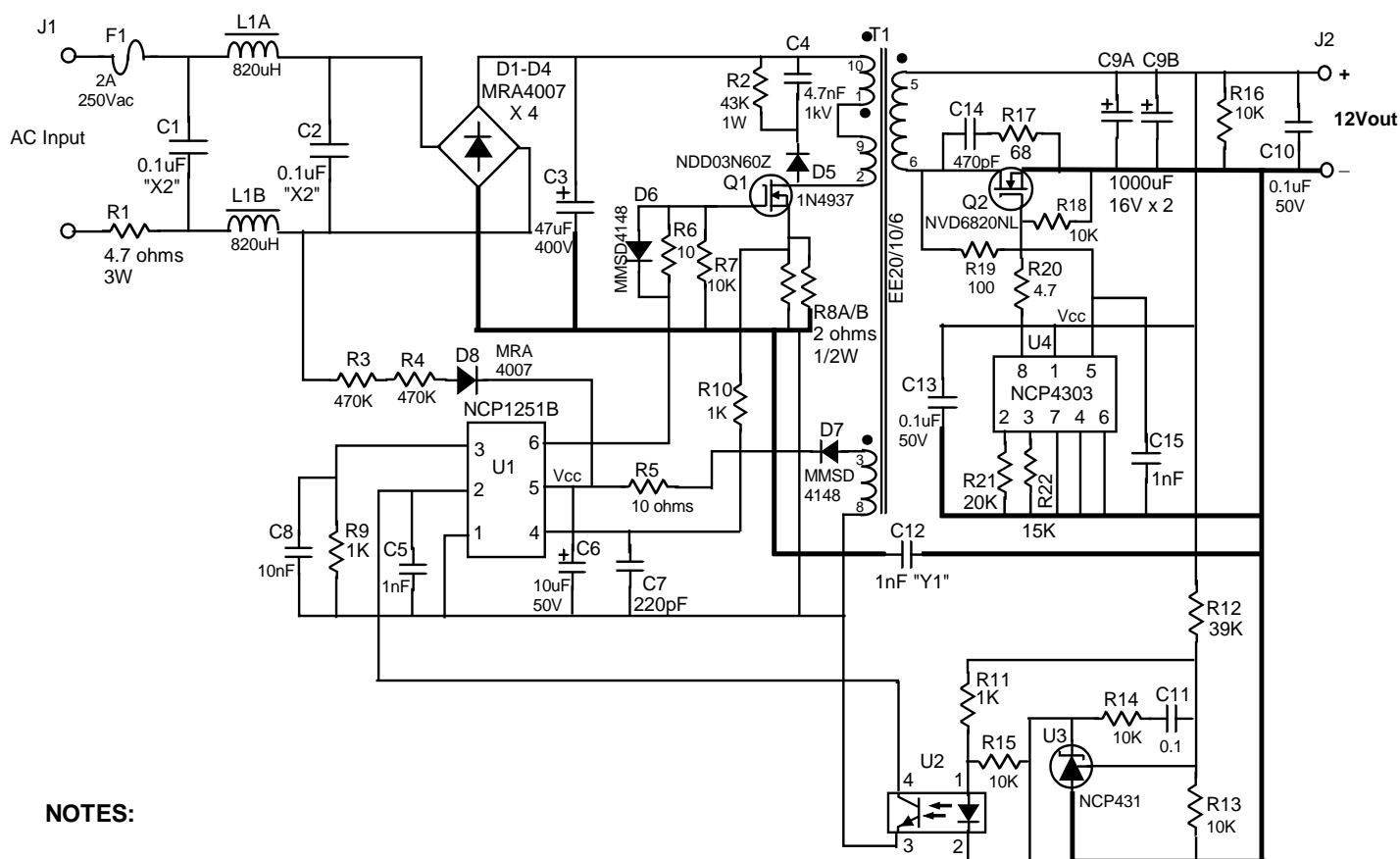

NOTES:

1. Crossed lines on schematic are NOT connected.
2. U2 is NEC PS2561L-1 or equivalent optocoupler (CTR > 50%).
3. R1 is for inrush limiting - use carbon comp or wire wound.
4. L1A/L1B are Wurth 7447728215 components (820 uH, 500mA).
5. Output caps (C9A/B) are radial lead, low impedance types (UCC LXV series or similar).
6. Heavy schematic lines are recommended ground plane areas.
7. R5 is for Vcc trimming (< 28Vmax), typically 10 ohms.
8. R8A/B sets max output current (primary peak current sense).
9. See drawing for T1 details.

20 Watt NCP1251 Power Supply with Output Synchronous Rectifier (Rev 1)

© 2012 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Frank Cathell, e-mail: f.cathell@onsemi.com

DN05028/D
MAGNETICS DESIGN DATA SHEET

Project / Customer: ON Semiconductor - 24 watt, 12 vout NCP1251 Flyback

Part Description: 24 watt flyback transformer, 12vout (Würth Electronics part # 750312495)

Schematic ID: T1

Core Type: EE20/10/6 ferrite core; 3C90 material or similar

Core Gap: Gap for 190 +/- 200uH across Primary A (pins 1 - 10)



Inductance: 750 uH total (+/- 5%) measured from pin 1 to pin 9 with pins 2 and 10 connected

Bobbin Type: 10 pin horizontal mount for EE20/10/6


Windings (in order):

Winding # / type	Turns / Material / Gauge / Insulation Data
Primary A (1 - 10)	30T of #28HN over 1 layer (25 TPL). Insulate for 1 kV to next winding. Self leads to pins.
Vcc (3 - 8)	7 turns of #28 HN over 1 layer, spiral wound over primary A. Self leads to pins. Insulate to 1 kV to next winding with tape.
12V Secondary (5 - 6)	6 turns bifilar of #24 triple insulated wire over one layer (two strands). Self leads to pins. (Note: #26 is also acceptable here if the fit is too tight for one layer)
Primary B (2 - 9)	Same as Primary A. Insulate with tape and self-leads to pins.

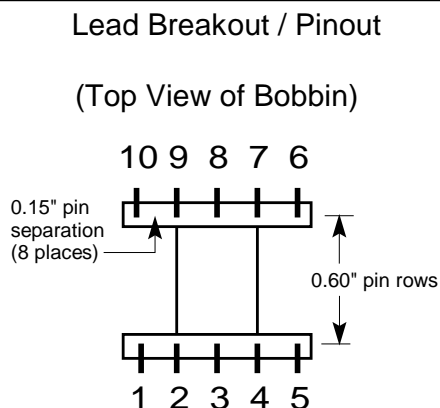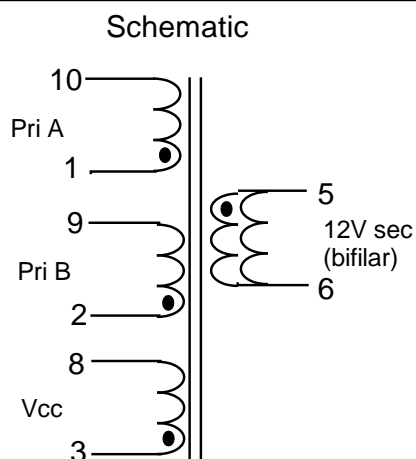Hipot: 3 kV from primaries & Vcc to secondary for 1 minute.



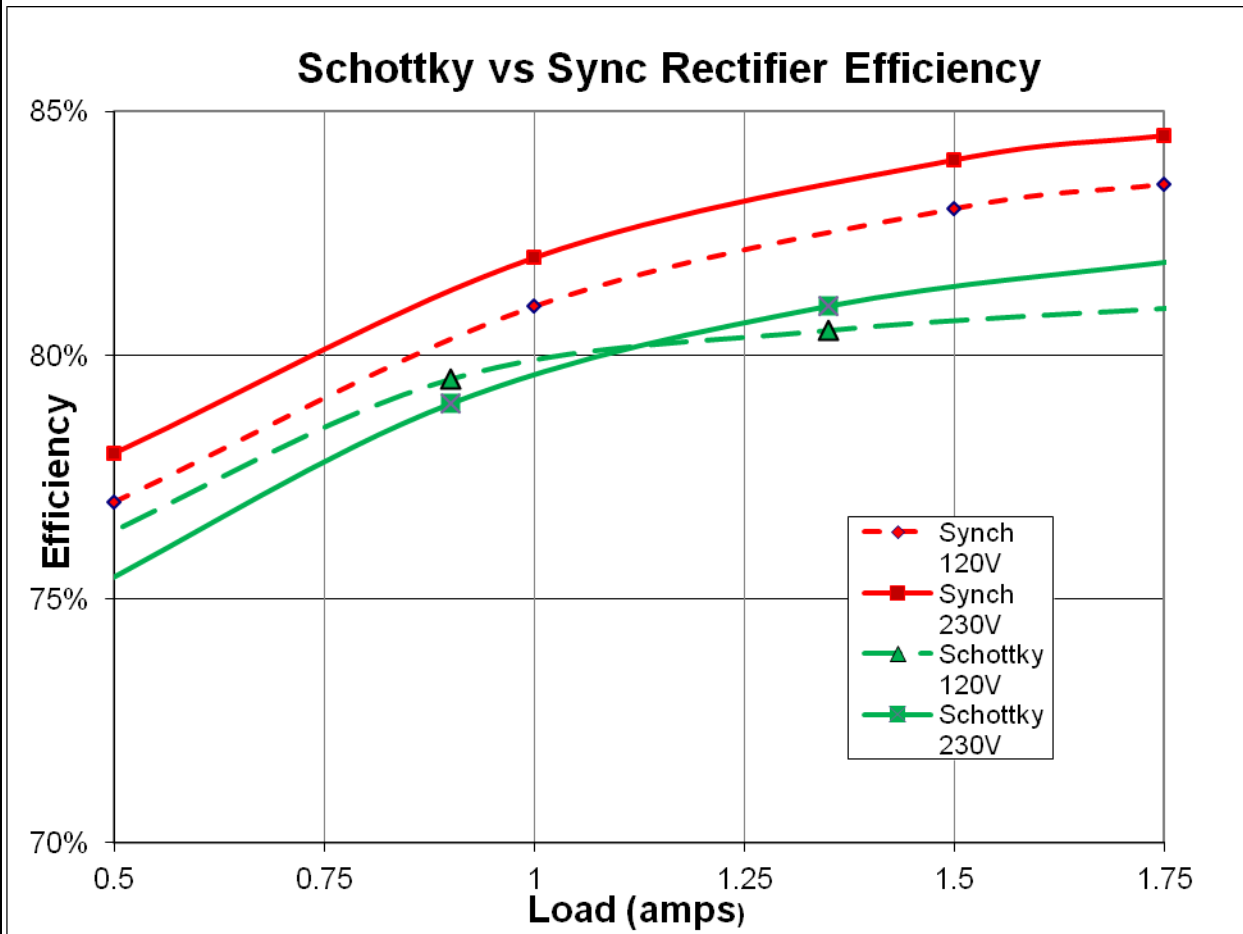Efficiency Plot Comparison (Schottky vs Synchronous Rectifiers)



References

ON Semiconductor Design Note DN05012/D
ON Semiconductor Design Note DN05017/D
ON Semiconductor NCP4303 Synchronous Rectifier Controller Data Sheet
ON Semiconductor NCP1251 Current Mode Controller Data Sheet
ON Semiconductor NCP431 Programmable Zener Data Sheet