



ON Semiconductor

Power Supply with Ultra High Voltage Linear Regulator

| Device | Application | Input Voltage | Output Power | Topology | I/O Isolation |
|---------|-------------|------------------|--------------|------------------|---------------|
| NCP785A | Consumer | 85 Vac – 265 Vac | 33 mW | Linear regulator | No |

Other Specification

| | Output 1 | Output 2 | Output 3 | Output 4 |
|------------------------|----------|----------|----------|----------|
| Output Voltage | 3.3 V | N/A | N/A | N/A |
| Ripple | N/A | N/A | N/A | N/A |
| Nominal Current | 6.5 mA | N/A | N/A | N/A |
| Max Current | 10 mA | N/A | N/A | N/A |
| Min Current | 0 | N/A | N/A | N/A |

| | |
|--|---------------|
| PFC (Yes/No) | No |
| Minimum Efficiency | N/A |
| Inrush Limiting / Fuse | No |
| Operating Temp. Range | -40 °C - 85°C |
| Cooling Method / Supply Orientation | N/A |
| Signal Level Control | N/A |

| | |
|---------------|--|
| Others | |
|---------------|--|

Circuit Description

The NCP785A is a high-performance linear regulator, offering a very wide operating input voltage range of up to 450 V DC, with an output current of up to 10 mA. Ideal for high input voltage applications such as industrial and home metering, home appliances. The NCP785A family offers $\pm 5\%$ initial accuracy, extremely high-power supply rejection ratio and ultra-low quiescent current. The NCP785A is optimized for high-voltage line and load transients, making this part ideal for harsh environment applications.

The NCP785A is offered in fixed output voltage options 3.3 V, 5.0 V, 12 V and 15 V. SOT-89 package offers good thermal performance and help to minimize the solution size

This circuit is designed to operate as a non-isolated off-line power supply with minimum external parts producing a fixed voltage 3.3 V output from a standard wide range input voltage from 85 Vac up to 265 Vac. It provides a maximum output current of 10 mA. The output ripple is significantly reduced by a linear regulator topology which has very high PSRR (70dB typ.) over the frequency range of 50 Hz to 120 Hz. This low ripple output voltage is suitable for supplying various smart metering systems sensitive to power line pollution. The NCP785A is optimized for high-voltage line and load transients, making it ideal for harsh environment applications.

Schematic

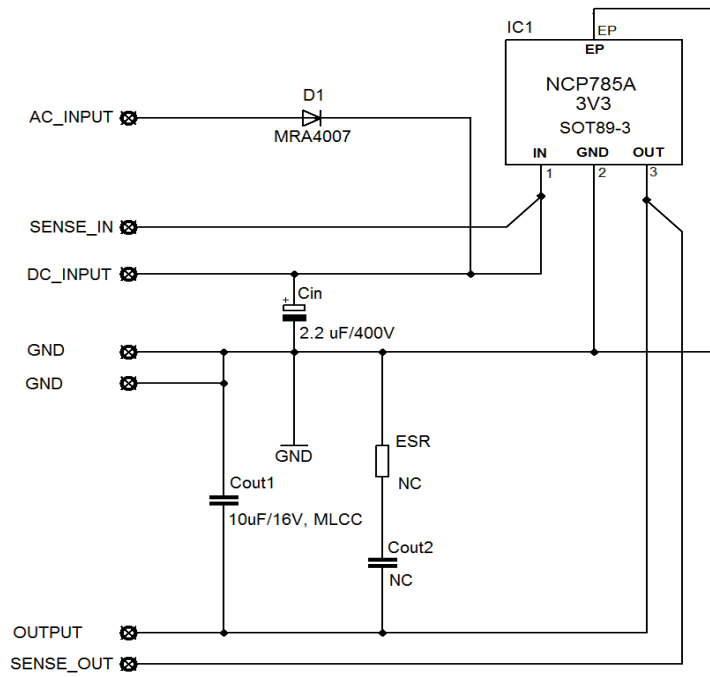



Figure 1. Schematic



Figure 2. Demoboard


PCB Details

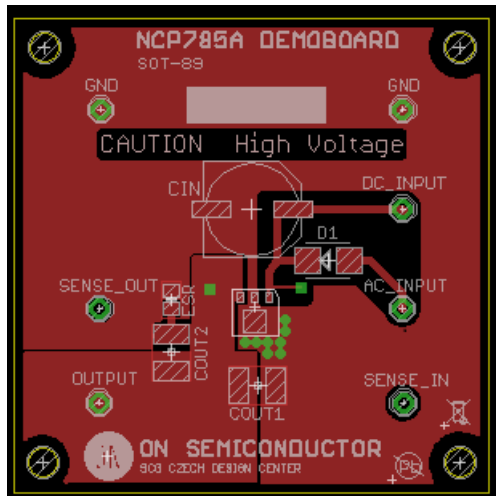Double layer PCB 50 x 50 mm, 16 um Copper plated, FR4.



PCB Top Side

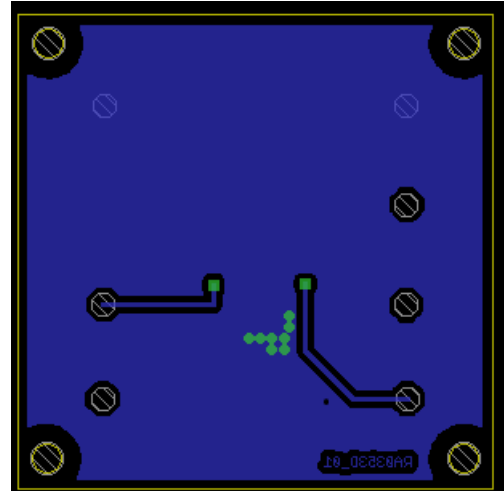1891 mm² total Cu area, 1439 mm² GND Cu area



PCB Bottom Side

2063 mm² total Cu area, 2009 mm² GND Cu area

Figure 3. PCB layout and dimensions

Note:

All charts mentioned below are related to this PCB unless otherwise noted.

Performance Information

The following Figures show typical measured performance of the NCP785A in this evaluation board.

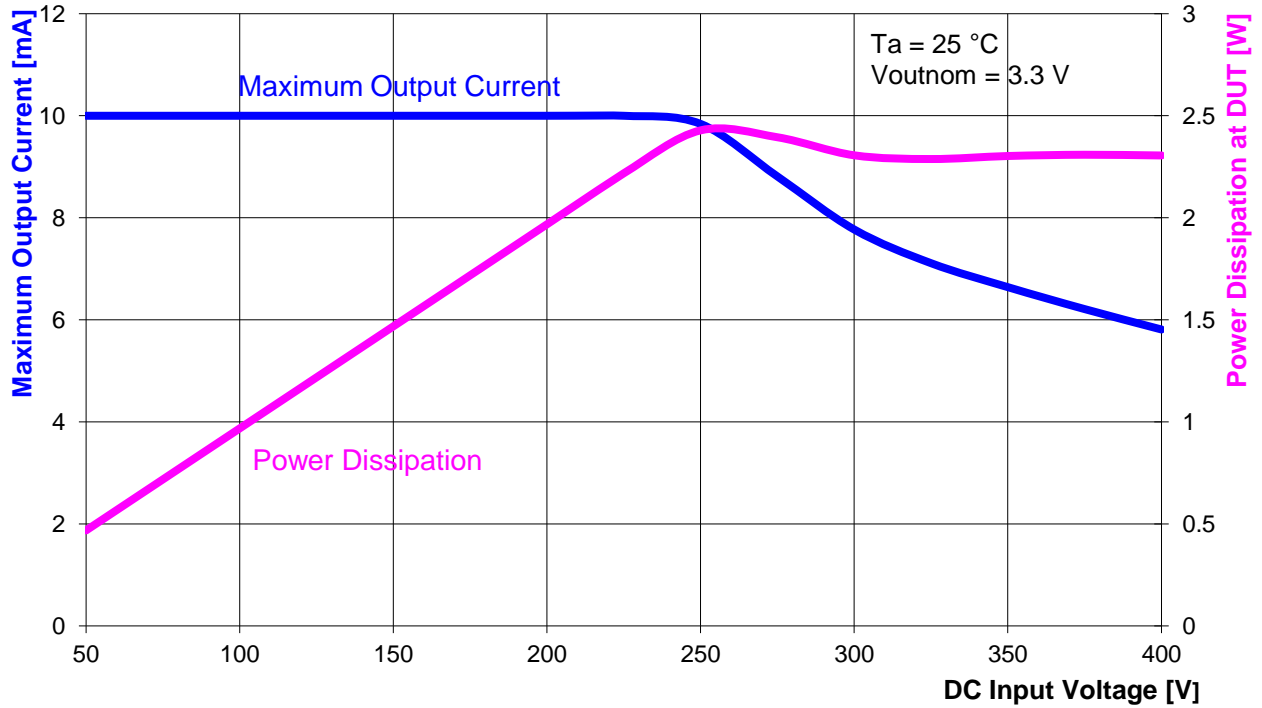


Figure 4. Maximum Output Current & Power Dissipation vs. Input Voltage

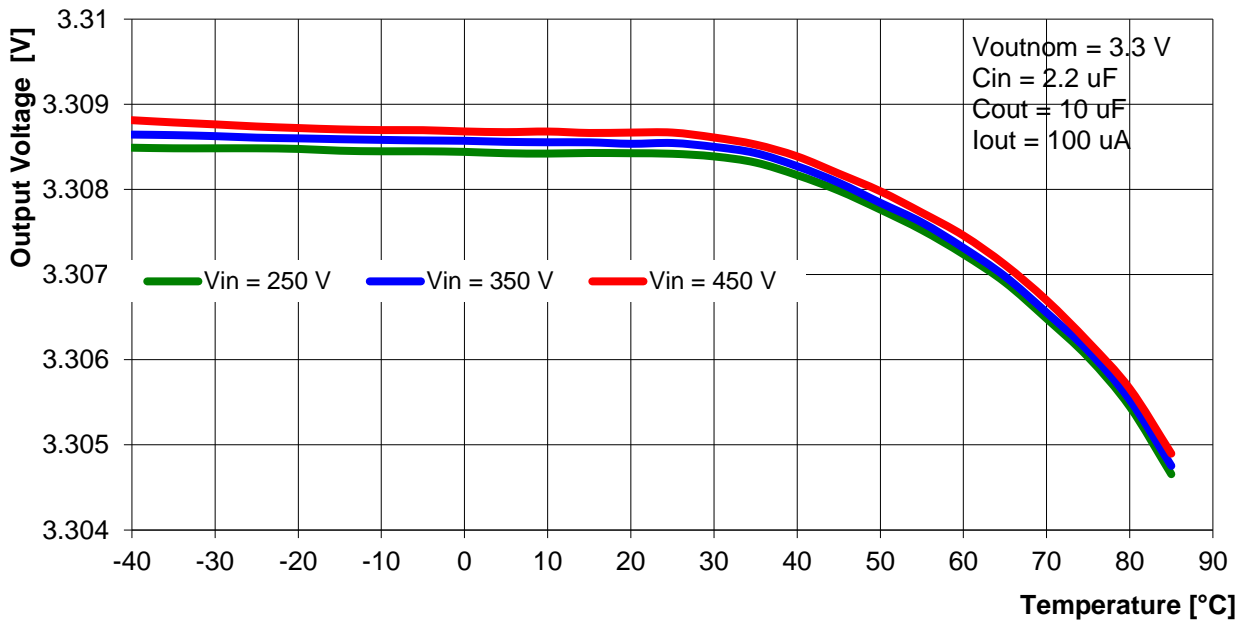


Figure 5. Output Voltage vs. Temperature

DN05094/D

The chart in Figure 4. shows the maximum allowable output current at different input voltages for 3% output voltage falling. The power dissipation of 2.35 W limits the maximum output current of the reference design board. Figure 5 shows the thermal characteristics of the board where the output voltage decreases with increasing junction temperature. The oscillogram in Figure 6. shows typical output voltage

behavior a few seconds after starting from room temperature with overloading. The overheating invokes the repetitive activation thermal shutdown protection and the output voltage is quickly switched on and off and the behavior looks like oscillation. Figure 7. shows the temperature map of the reference PCB. You can see how the top side copper helps spread the thermal load across the board and reduce the junction temperature of the part.

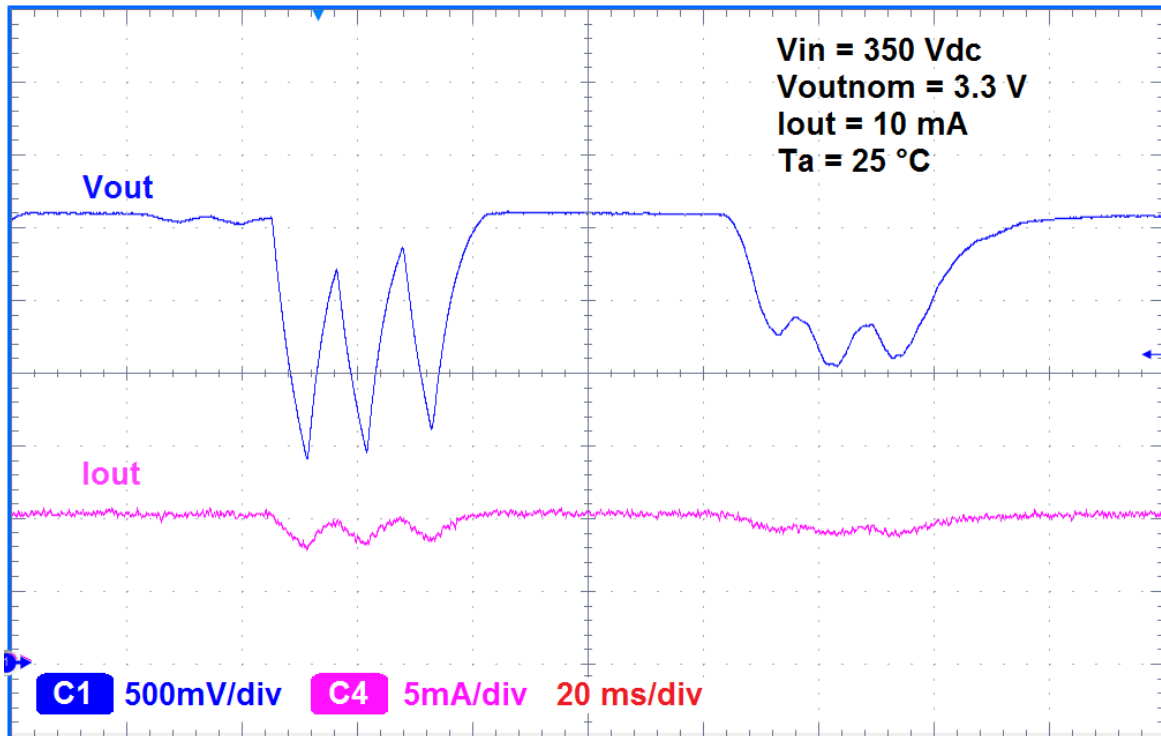


Figure 6. Thermal Shutdown Protection behavior

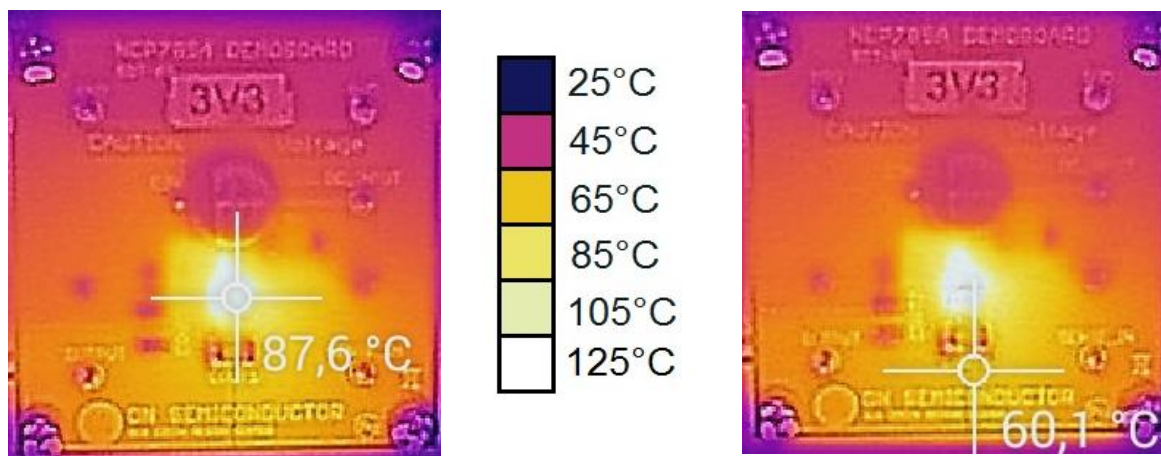


Figure 7. Thermal relief at PCB

Application Recommendations

Maximum allowed output current is strongly limited by power dissipation and proper cooling conditions. The Figure 8. shows the SOT89-3 package maximum power dissipation and Theta_{JA}

dependence on the cooper area for single side board, based on the basic thermal equation (eq.1).

$$P_{D(MAX)} = [T_{J(MAX)} - T_A] / \theta_{JA} \quad (\text{eq. 1})$$

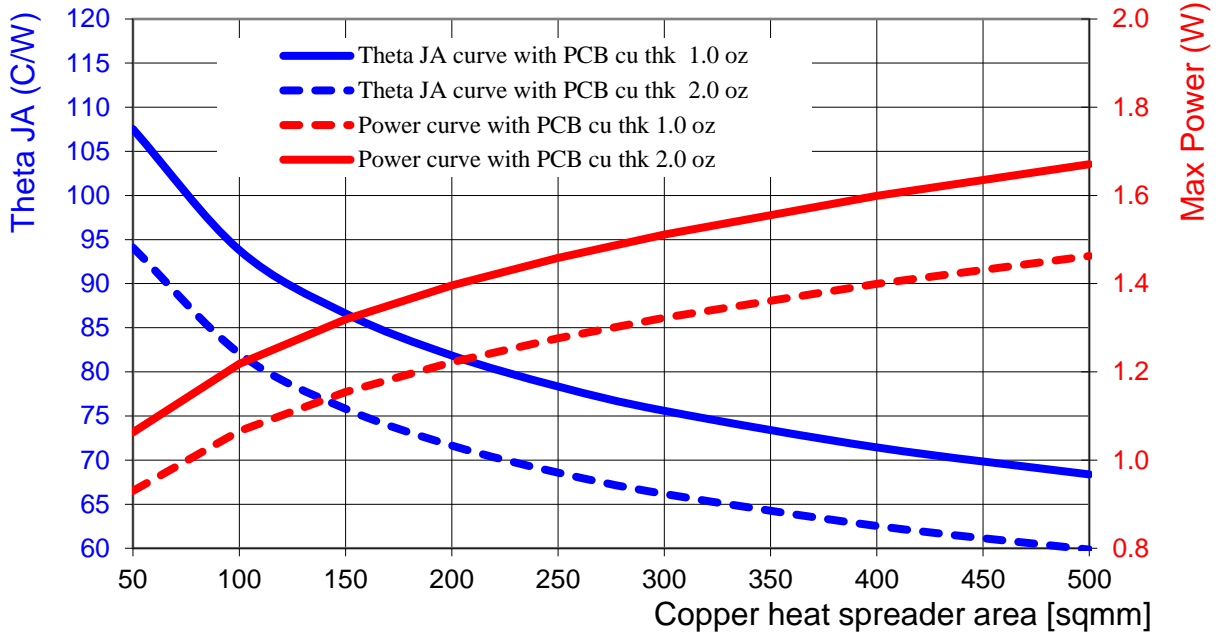


Figure 8. Maximum Power Dissipation & Theta_{JA} vs. Copper Area

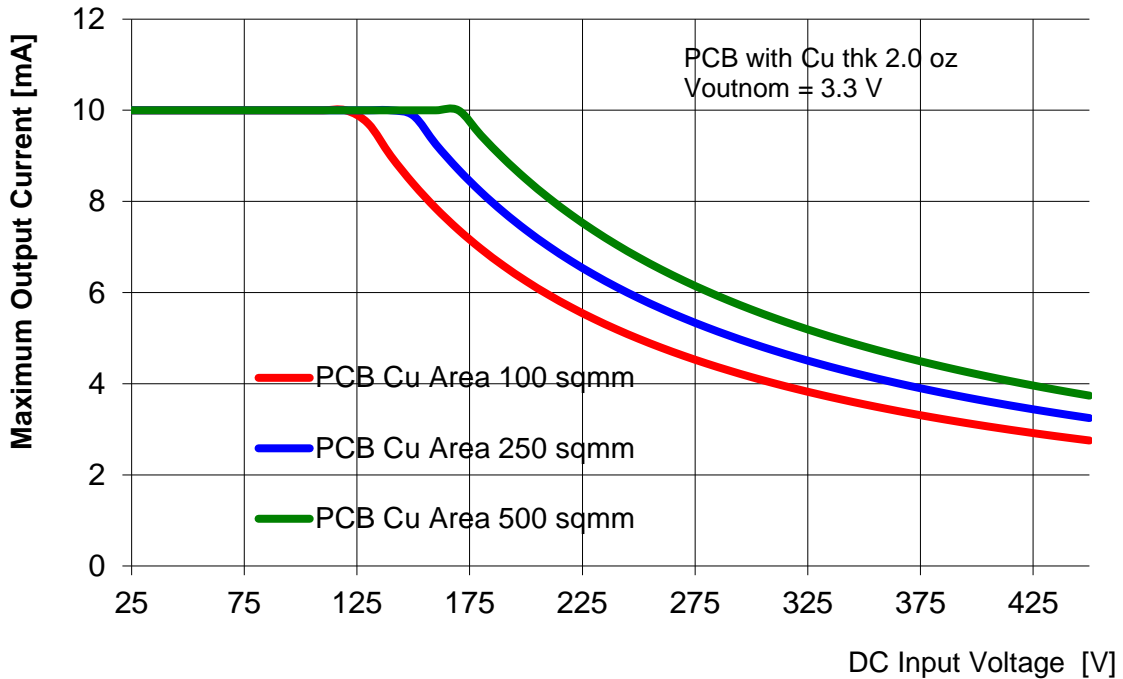


Figure 9. Maximum Power Dissipation vs. DC Input Voltage

In the real application it is very useful to check the maximum temperature on the case of the device by a thermal imaging camera. Figure 9. Shows calculated maximum output current dependence on the input voltage for three different Copper areas.

The power supply based on NCP785A linear regulator is ideal for microcontroller applications with very low consumption in stand-by or sleep mode for more than 90% of working time and for short time the device is able to deliver high current up to maximum capability limited by power dissipation for data transfer or another operations. The typical application example shown here is a wireless Bluetooth thermometer. Figure 10. shows the typical timing and consumption characteristics of this application. The

average current is 249.7 uA and the total power consumption from 235 Vac main is below 83 mW. The average current is 249.7 uA and the total power consumption from 235Vac main is below 83 mW. The consumption of SMPS in this application is usually 2 – 5 times higher and 2 – 5 times more expensive. The 66 uA consumption at sleep time is given by sum of 10 uA quiescent current and 56 uA microcontroller consumption in sleep mode. In case the average current exceed 500 uA the efficiency of the power supply based on NCP785A device rapidly fall. The current peak 3.7 mA during radio communication could be increased up to 10 mA but there is necessary to keep the duration of this current as short as possible.

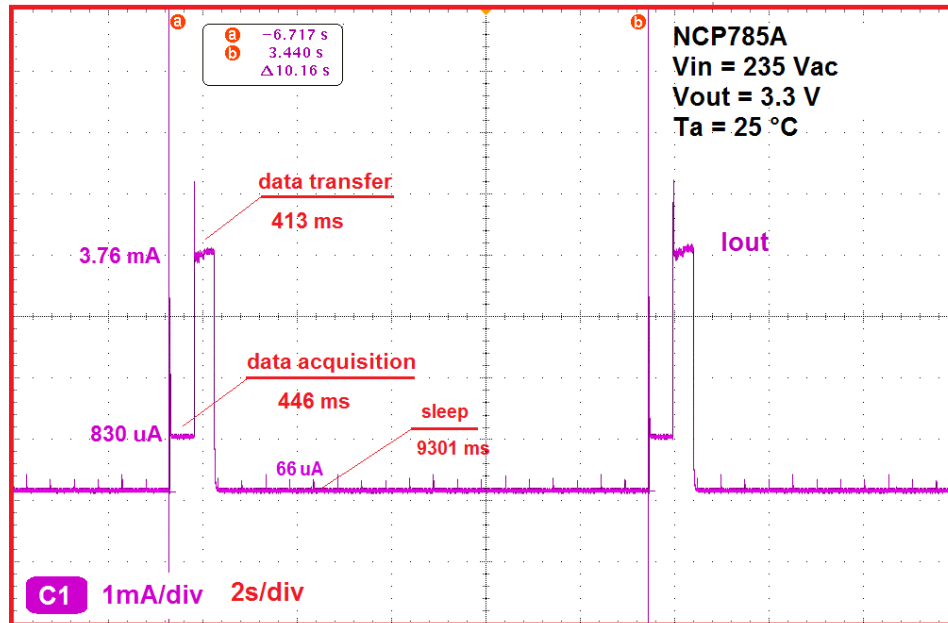


Figure 10. Timing and consumption characteristic

Input Capacitor Selection

The input capacitor C_{in} must maintain the regulator minimum input voltage 25 V at full load for AC voltage as low as 85 Vac.

For half wave rectification the recommended value is $C_{in}=2.2\mu\text{F}$, the rectifier waveforms are shown in Fig. 11. Lower capacitor values would limit the

maximum output current; only 6.5 mA can be achieved with $C_{in}=1\mu\text{F}$. If the application can be floating, it is possible to use full wave rectifier which assures the minimum input voltage at NCP785A with input capacitor $1\mu\text{F}$ up to 10 mA load. The waveforms for this case are shown in the Figure 12.

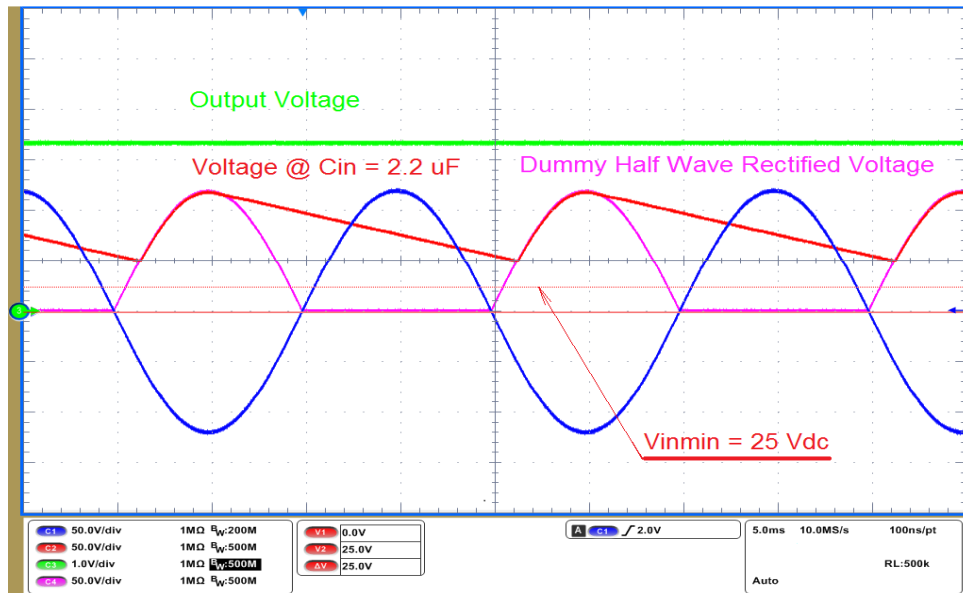


Figure 11. Output Voltage at $V_{in} = 85 \text{ Vac}$, half-wave rectifier, $C_{in} = 2.2 \mu\text{F}$, $I_{load} = 6.5 \text{ mA}$

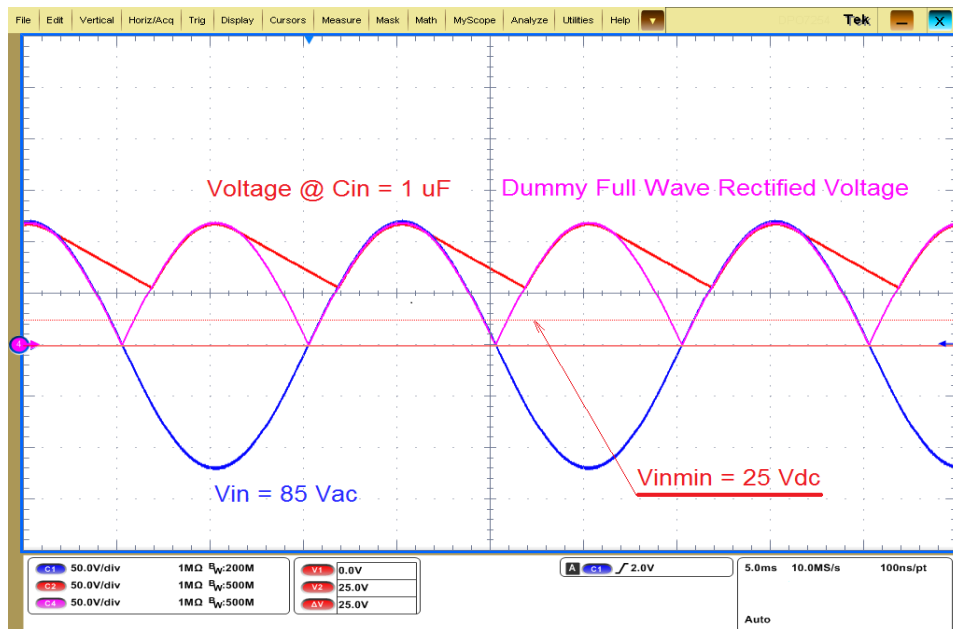


Figure 12. Output Voltage at $V_{in} = 85 \text{ Vac}$, full-wave rectifier, $C_{in} = 1 \mu\text{F}$, $I_{load} = 10 \text{ mA}$

Conclusion

The NCP785A linear regulator allows you to create a simple and cost effective non-isolated power supply.

This approach is a more efficient solution for low output power applications compared to a complex switching convertor or capacitive dropper. Maximum output current is limited by power dissipation given by PCB layout and Input Voltage.

Bill of Materials

| MM/DD/YYYY | | | | | | | | | |
|------------|----------|---------------|-------------|-----------|-----------|-------------------------|--------------------------|----------------------|-----------|
| Designator | Quantity | Description | Value | Tolerance | Footprint | Manufacturer | Manufacturer Part Number | Substitution Allowed | Lead Free |
| CIN | 1 | Capacitor | 2.2 uF | 20% | SMD | Nichicon | ULH2W2R2MNL 1GS | Yes | Yes |
| D1 | 1 | Diode | MBR4 007 | N/A | SMD | ON Semiconducto r | MBR4007T3G | Yes | Yes |
| COU | 1 | Capacitor | 10 uF | 10% | 1206 | TDK | C3225X7R1C10 6M250AC | Yes | Yes |
| REG1 | 1 | UHV Regulator | 3.3 V | 5% | SOT89-3 | ON Semiconducto r | NCP875AH330T 1G | No | Yes |

© 2017 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Rudolf Seget, e-mail: rudolf.seget@onsemi.com