

# ON Semiconductor

## Is Now

# onsemi™

To learn more about onsemi™, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

---

**onsemi** and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



ON Semiconductor

## Filtering Common Mode Overshoot at the Inputs of ON Semiconductor NCS21xR and NCS199AxR Current Sense Amplifiers (CSA's)

Device	Application	R <sub>Shunt</sub>	Input (V <sub>IN</sub> )	Output Voltage (V <sub>OUT</sub> )	Input Offset Voltage	Package
NCS213R	Consumer	25 mΩ	40 kHz Square Wave, 5VPP, 5ns edge	1.65 V to 2.15 V	±100 μV	SC70-6, UQFN10

### Circuit Description

This design note describes how to suppress transient overshoot at the input of the [NCS21xR](#) and [NCS199A1R](#) current sense amplifiers. There are two specification criteria of interest: The ABS Max range of (GND – 0.3 V) to +30 V which if exceeded could damage the device; and the specification range of -0.3 V to 26 V over which the device is guaranteed to function properly. Note that the common-mode voltage range limits are separate and independent of the supply voltage (V<sub>S</sub>) limits. This design note assumes that the power supply pin of the device is fed from a separate and conditioned source within the limits of the specifications for that pin.

At times, a current sensing application may have a large amplitude and fast switching common-mode signal on the line that the shunt is in. Frequently this signal may have overshoot on the rising or falling edge. If the overshoot exceeds the specification range of -0.3 V to 26 V the device may not function properly. Note that the negative limit of -0.3 also applies as an ABS Max rating which, if exceeded, could damage the device (with overshoot in the rising edge direction, overshoot should be below the ABS Max of 30 volts to avoid damage). In order to not damage the device and ensure proper operation, this overshoot condition must be filtered before reaching the inputs of the amplifier.

The circuit and conditions shown in Figure 1 produce a signal at the inputs to the amplifier that violates the ABS Max spec for the input common mode voltage of “GND – 0.3 V.” The first question would be why doesn't this damage the device? The ABS Max section of the data sheet allows the voltage ratings of any pin to be exceeded so long as current is limited to less than 5 mA which has been established in this example. Nonetheless, safe, proper functioning is not guaranteed unless it is clamped to less than 0.3V.

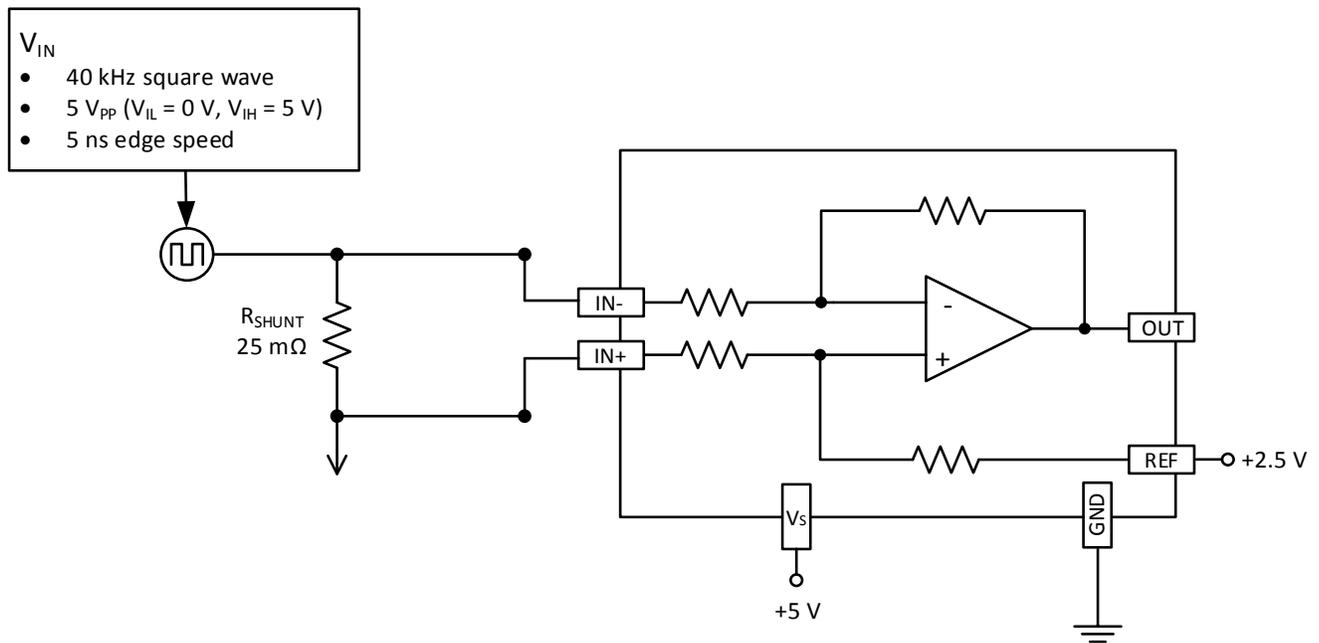


Figure 1: Circuit schematic and conditions causing overshoot that violates the ABS Max conditions of the datasheet.

### Overshoot Exceeding Absolute Maximum (ABS Max) Datasheet Spec for VCM

The yellow waveform in Figure 2 shows the unfiltered signal seen at the inputs of the amplifier. The overshoot on the falling edge reaches a maximum of -1.5 V below GND. This is 1.2 V beyond the -0.3 V spec; albeit, the time that the input signal spends at this voltage is for a very short duration since the pulse width of this overshoot is about 19 ns (See Figure 3).


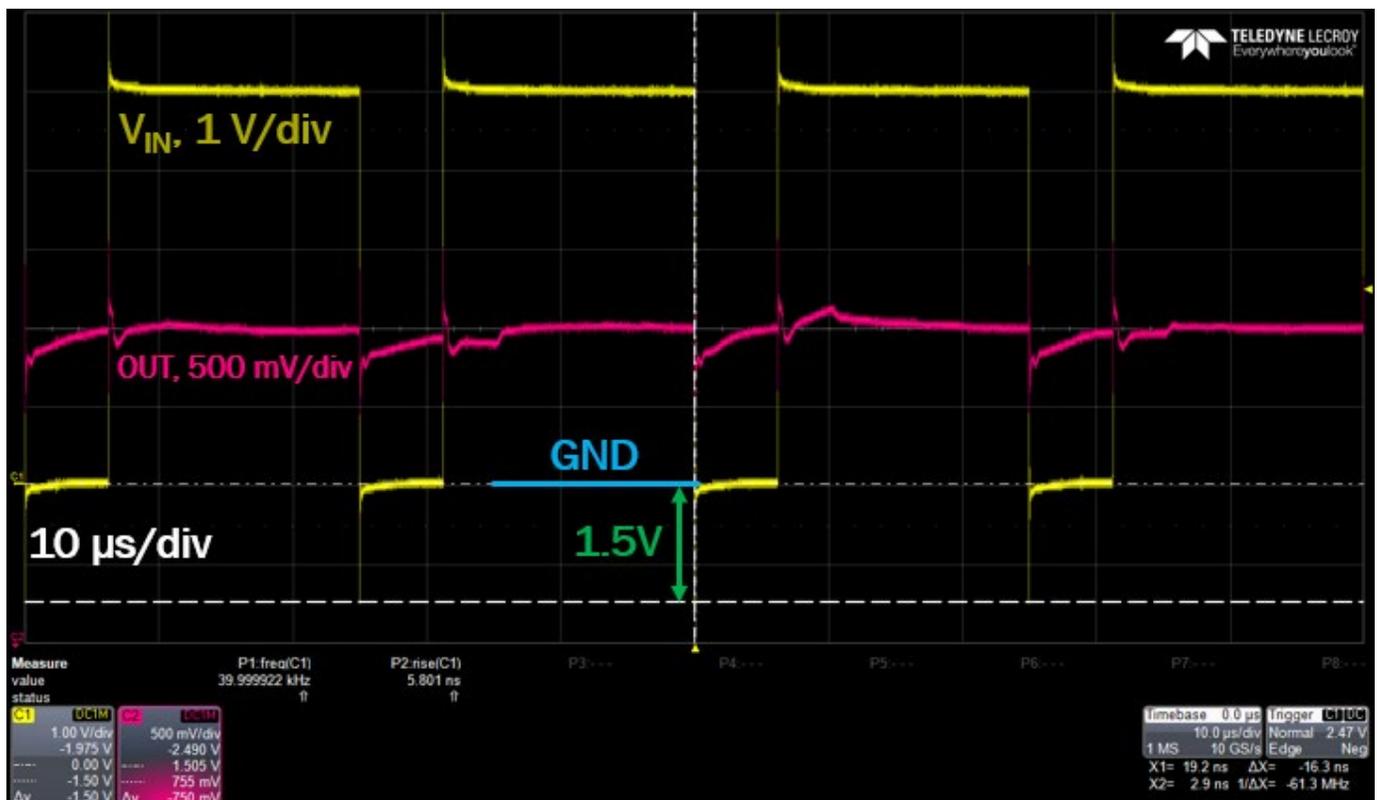


Figure 2: No common mode filter. Common mode overshoot on the falling edge of  $V_{IN}$  of -1.5 V; exceeding the spec of -0.3 V by -1.2 V (10  $\mu$ s/div).

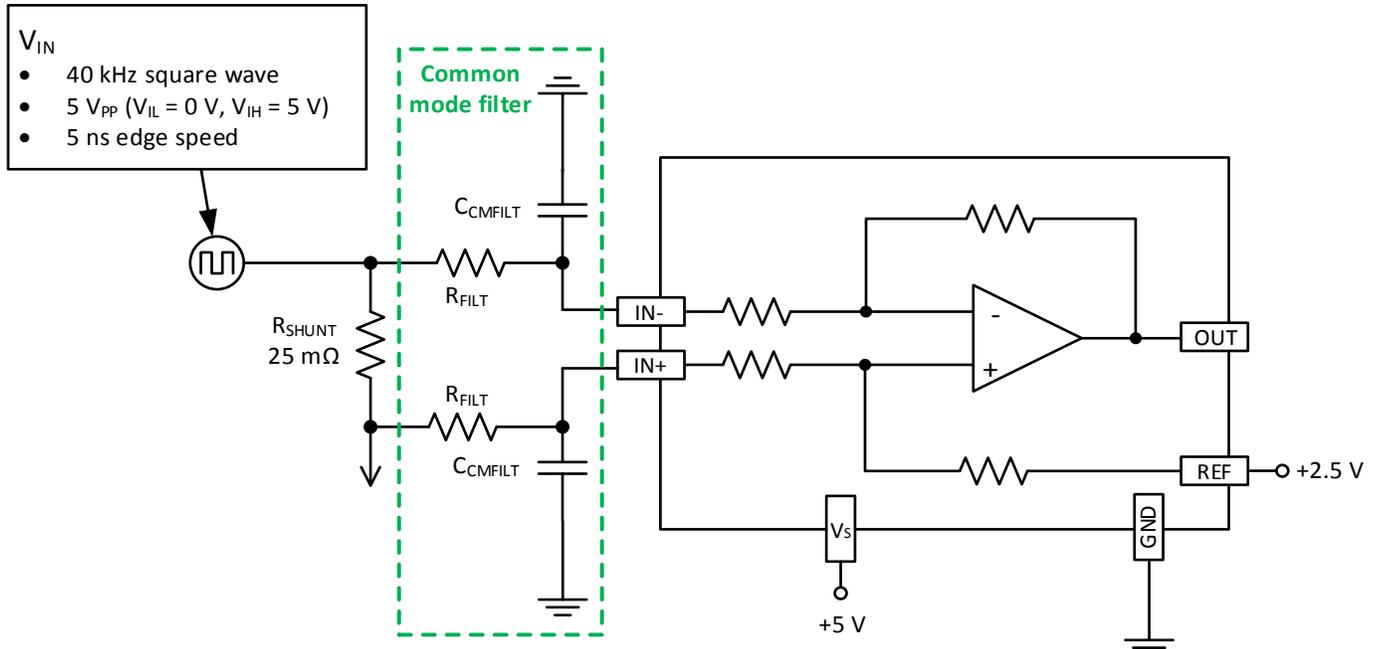

The “Edge Speed” is the measured edge of the  $V_{IN}$  signal from 10% to 90%. The -3dB frequency ( $f_{-3dB}$ ) of first order systems, such as the first order filter to be implemented, can be calculated from this equation. The goal is to filter out the high frequency content that makes up the overshoot and to use the smallest capacitor value possible and at the same time allow margin for process and temperature variation and component tolerance. Even after calculating the capacitor value, it is likely going to be necessary to experiment with different capacitor values in order to dial in the needed performance from the circuit.



**Figure 4: Common mode filtering solution schematic for the NCS21xR and NCS199AxR series current sense amplifiers;  $R_{FILT}$  and  $C_{CMFILT}$  sets up the common mode filter.**

Using the equations provided above,  $f_{-3dB}$  and  $C_{CMFILT}$  are calculated by:

- $f_{-3dB} = \frac{0.35}{\text{Edge Speed}} = \frac{0.35}{5 \text{ ns}} = 70 \text{ MHz}$
- $C_{CMFILT} = \frac{1}{2\pi f_{-3dB} R_{FILT}} = \frac{1}{2\pi(70 \text{ MHz})(10 \Omega)} = 227 \text{ pF}$

The 70 MHz is the -3dB bandwidth of  $V_{IN}$ , calculated from its rise time of 5 ns. At this point, the calculated 70 MHz is used in the capacitor calculation to arrive at a minimum capacitor value of 227 p. Through experimentation and observation, it was found that a minimum value of 300 pF for  $C_{CMFILT}$  was required to filter the falling edge overshoot transient from -1.5 V to -0.3 V, which puts the falling edge overshoot right at the ABS Max spec limit.

Figure 5 shows the effect of the implemented filter with 300 pF capacitors used for  $C_{CMFILT}$ . At this scale the overshoot is not clearly visible, so Figure 6 shows a zoomed in view of Figure 5. The cursor measurements show that the overshoot on the falling edge has been reduced to -0.3 V, meeting the spec limit.

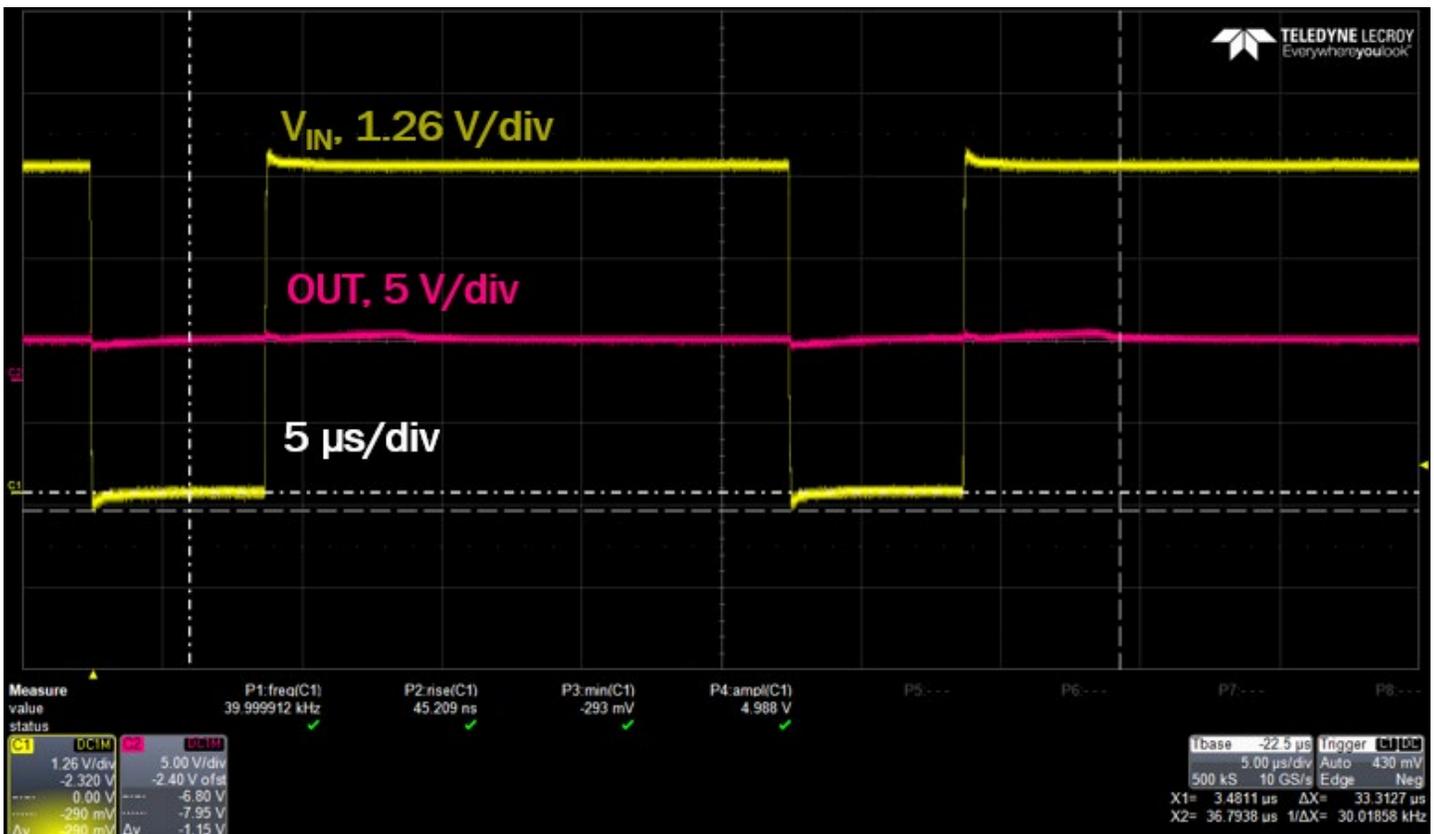


Figure 5: Common mode filter with 300 pF capacitors. Overshoot has been reduced to -0.3 V, which is right at the min spec limit.



Figure 6: Zoom view of Figure 5. Overshoot reduced to -0.3 V, which is right at the lower side of the ABS Max spec limit.

## DN05118/D

Table 1 below shows that with 100 pF capacitors, the overshoot is reduced by nearly half, but slowed the edge down to 22 ns. A 1000 pF (1 nF) capacitor value reduced the overshoot down to -0.2 V.

**Table 1: Test Results; Filtering vs Overshoot and Edge Speed**

Common Mode Input Filter Values	V <sub>IN</sub> Falling Edge Overshoot (V)	V <sub>IN</sub> Edge Speed (ns)
No Filtering	-1.5	5
R <sub>FILT</sub> = 10 Ω, C <sub>CMFILT</sub> = 20 pF	-1.36	11
R <sub>FILT</sub> = 10 Ω, C <sub>CMFILT</sub> = 100 pF	-0.945	22
R <sub>FILT</sub> = 10 Ω, C <sub>CMFILT</sub> = 200 pF	-0.37	34
R <sub>FILT</sub> = 10 Ω, C <sub>CMFILT</sub> = 300 pF	-0.3	45
R <sub>FILT</sub> = 10 Ω, C <sub>CMFILT</sub> = 1000 pF	-0.2	76

Table 2 below highlights the NCS21xR and NCS199AxR series current sense amplifiers. Customer evaluation boards for each part number can be ordered at their respective landing pages.

**Table 2: NCS21xR and NCS199AxR Series Current Sense Amplifiers**

Part Number	Gain (V/V)	Input Offset Voltage (μV)	Gain Error (%)
<a href="#">NCS210R</a>	200	±35 Max	±1
<a href="#">NCS211R</a>	500	±35 Max	±1
<a href="#">NCS213R</a>	50	±100 Max	±1
<a href="#">NCS214R</a>	100	±60 Max	±1
<a href="#">NCS199A1R</a>	50	±150 Max	±1.5
<a href="#">NCS199A2R</a>	100	±150 Max	±1.5
<a href="#">NCS199A3R</a>	200	±150 Max	±1.5

© 2019, SCILLC.

**Disclaimer:** Semiconductor Components Industries, LLC (SCILLC) ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does SCILLC convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages.