

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



ON Semiconductor

3 Output, 10 W Off-line Power Supply

Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
NCP1014	Auxiliary off-line power supply for appliances	90 to 270 Vac	10 W	Flyback	Yes

Other Specifications

	Output 1	Output 2	Output 3	Output 4
Output Voltage	5 V	12 V	-5 V isolated	N/A
Ripple	100 mV	100 mV	25 mV	N/A
Nominal Current	750 mA	300 mA	250 mA	N/A
Max Current	1 A	500 mA	400 mA	N/A
Min Current	50 mA	10 mA	0	N/A

PFC (Yes/No)	No
Minimum Efficiency	68%
Operating Temp Range	0 to +60°C
Cooling Method/Supply Orientation	Convection

Others	Isolated negative 5 volt output with tight regulation.
---------------	--

Circuit Description

This universal input, off-line switchmode power supply provides 3 mains isolated and regulated outputs. The converter circuit is a flyback based topology utilizing ON Semi's NCP1014 monolithic switcher in an SOT-223 package. The output provides 5 and 12 volts with an additional negative 5 volt output that is isolated galvanically from the other two outputs. For simplicity, the AC input is half-wave rectified via D1 and conducted EMI is attenuated by C1 and L1. A standard bridge rectifier can be substituted if desired with lower line frequency ripple. U1 is powered by an aux winding on T1 for very low standby power when the supply is unloaded. Voltage sensing, and feedback from the main 5 volt output is accomplished with a simple zener diode (Z1) and optocoupler circuit. The transformer secondary utilizes a stacked winding configuration for the 5 and 12 volt outputs which provides good cross regulation with the 5 volt output. Tight regulation is provided on the isolated – 5 volt output via a 3-terminal regulator.

Key Features

- Useful for powering telecom, LAN, appliance and industrial controls where low power is required.
- Extremely simple and low cost design.
- 10 watt output with 12 watt surge capability with properly heatsunk SOT-223 package for U1.
- 90 to 270 Vac universal input range.
- Isolated – 5 volt output with high regulation and low output ripple.
- Conducted EMI filter.
- Half-wave input rectifier for low cost.
- Output short circuit protection and overvoltage protection from open optocoupler.

DN06005/D

MAGNETICS DESIGN DATA SHEET

Project / Customer: ON Semiconductor - NCP1014 triple output supply

Part Description: 10 watt flyback transformer; triple output, universal input

Schematic ID: T1

Core Type: E25/10/6 (E24/25); 3C90 material or similar

Core Gap: Gap for 1.45 mH nominal



Inductance: L (mH) = 1.4 to 1.5 mH

Bobbin Type: E24-25 PCB1-10 (10 pin horizontal pc mount)

Windings (in order):

Winding # / type	Turns / Material / Gauge / Insulation Data
Vcc (1 - 2)	7 turns of #32HN spiral wound over window with 2 mm end margins. Tape insulate to 1 kV. Self-leads to pins.
Primary (10 - 9)	70 turns of #32HN over 2 layers, 35 TPL. Insulate with tape for 1 kV to next winding. Self-leads to pins.
5/12V Secondary (8 - 3, 7 - 4)	3 turns biflar of two different colors of #26HN flat wound over primary with 2 mm end margins. Continue winding 1 extra turn with one of the colors (4 turns total) - this will be the 12V winding. Self-leads to pins per diagram below. Insulate with tape for 3 kv to next winding.
9V Isolated Sec. (5 - 6)	5 turns of #26HN spiral wound over previous winding. allow 3 mm end margins. Insulate with tape.

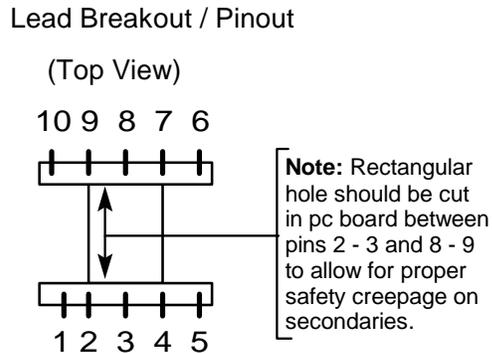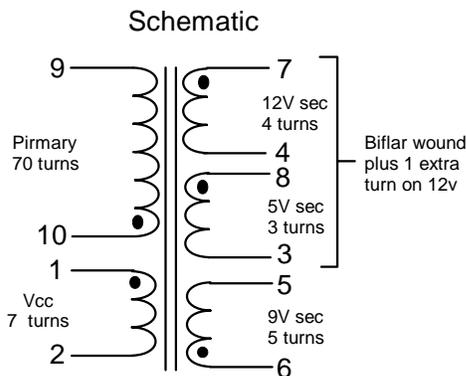Hipot: 3 kV from primary/Vcc to 5/12/-5V secondaries for 1 minute.



Proto xfmrs available from Mesa Power Systems, Escondido, CA. 1-800-515-8514

© 2006 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Frank Cathell, e-mail: f.cathell@onsemi.com