




**ON Semiconductor®**

# **Multi-Output Flyback Off-Line Power Supply**
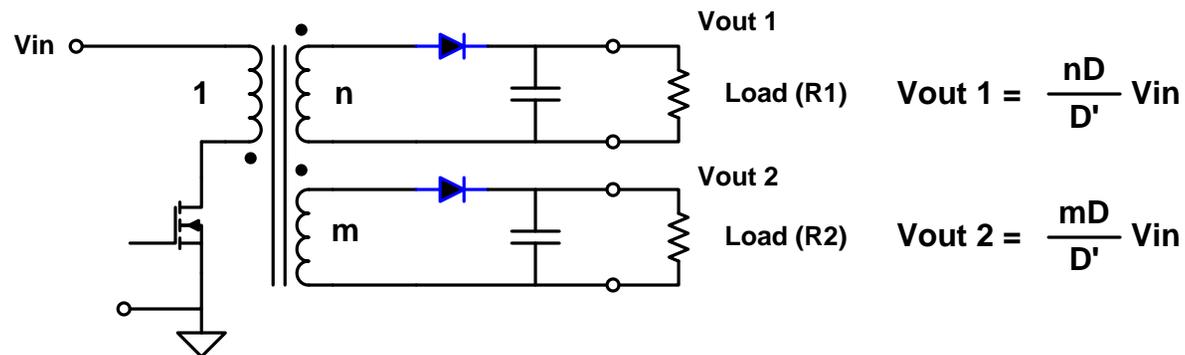
# Basic Concept


- Add additional secondary windings, using the same turns/volt as the original secondary.



- Outputs can be positive or negative, depending on which side of the output (top or bottom) is grounded.
- Either output can be the “master” by connecting it to the feedback sensing circuit
- Formulas are not exact, due to the diode drops not being proportional to the number of turns!

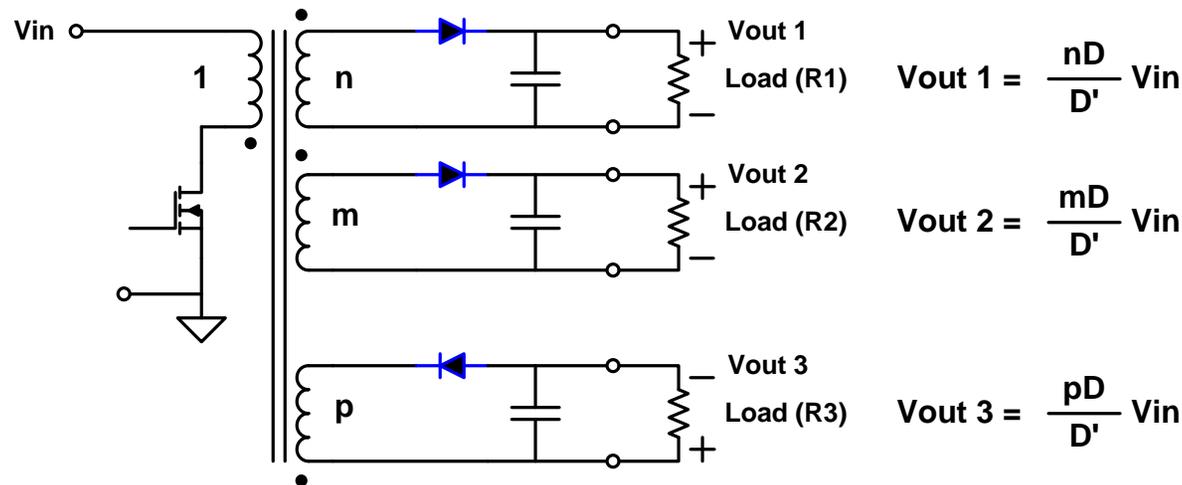
# Example of Adding a Negative Output

- There is no theoretical limit to the number of outputs.




- In this case, the negative output drawn like the positive ones, with the diode reversed and the polarity of the winding as shown.

# Two Outputs with Feedback Regulation

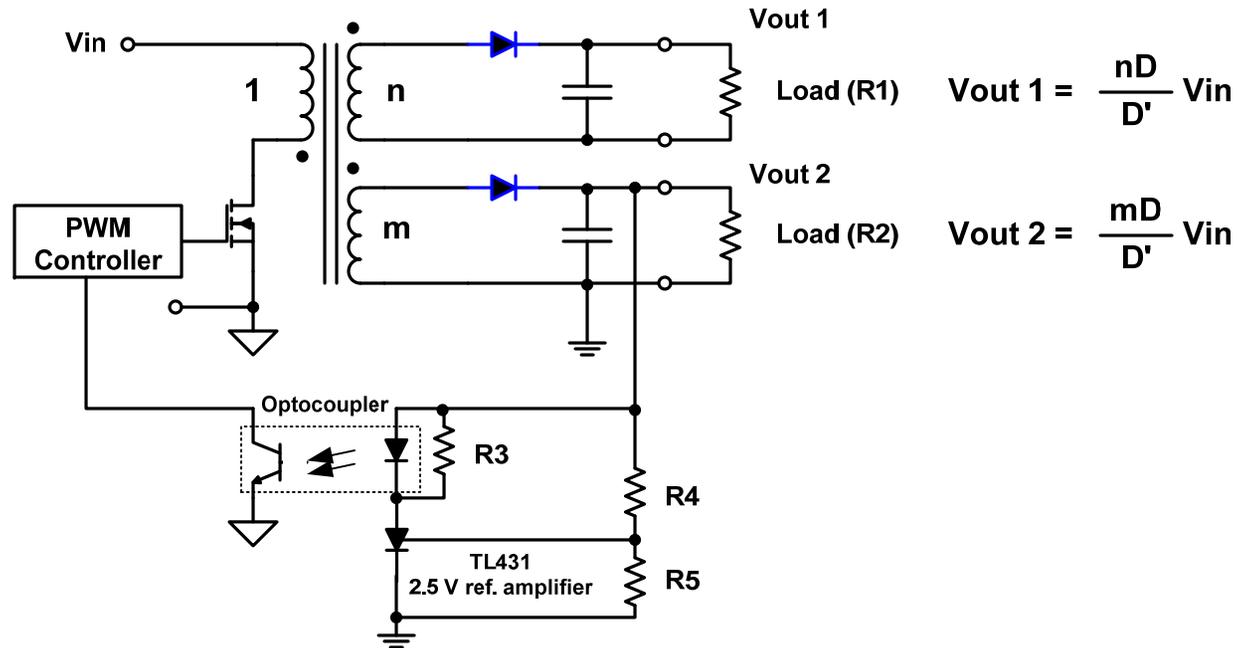


- Typical regulated flyback converter
  - One output is the master (output 2 in this case)
  - Second output (output 1, in this case) is the “slave” (quasi-regulated).
  - For output voltages less than 2.5 V, a TLV431 (1.25 V) or other can be used.
  - Why do we need R3?

# Improvement #1 – Stacked Windings

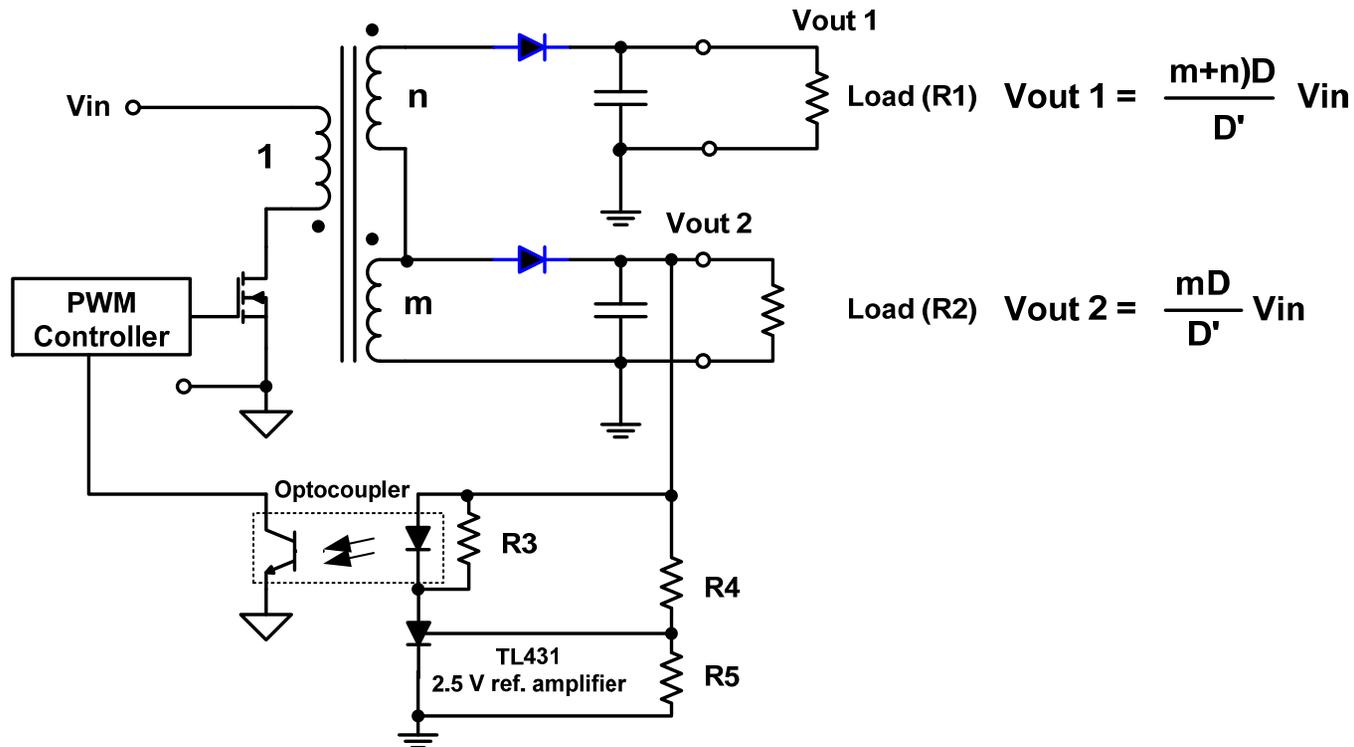


- Regulation of second output is improved, because only part of it is “alone.”
  - Only the “n” portion is unregulated. (Leakage inductance of n is less.)
- Again, one output is the master (output 2 in this case)
  - Second output (output 1, in this case) will vary with the load on the main output, due to its current flowing through the winding of output 2.

# Improvement #2 Stacked Outputs

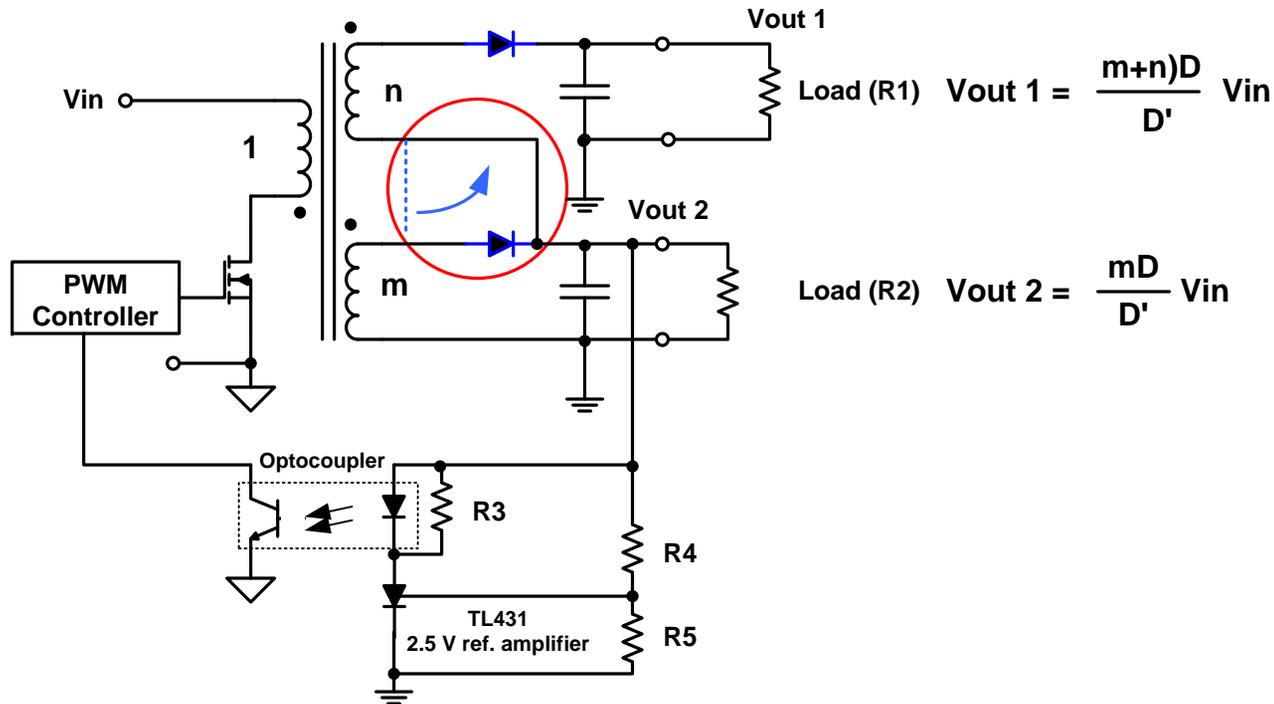


- Now, output 1 current flows through output #2's diode.
  - Output 1 is less dependent on output 2's load, because the bottom of its output doesn't move.

# Improvement #3 No-Load Clamp

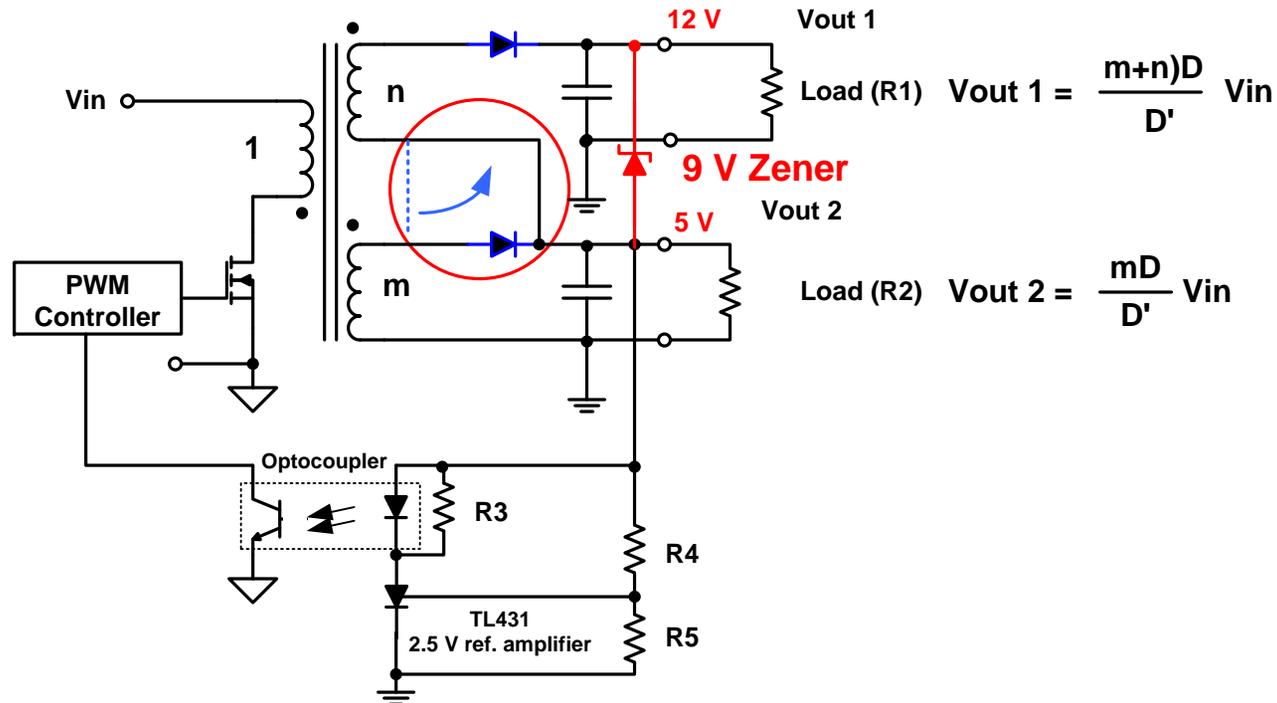


- When output 1 is unloaded, its stray output current flows down through the Zener and into the 5 V output.
- In this case, output 1 would be clamped at 14 V.

# Improvement #4 – Combined Feedback

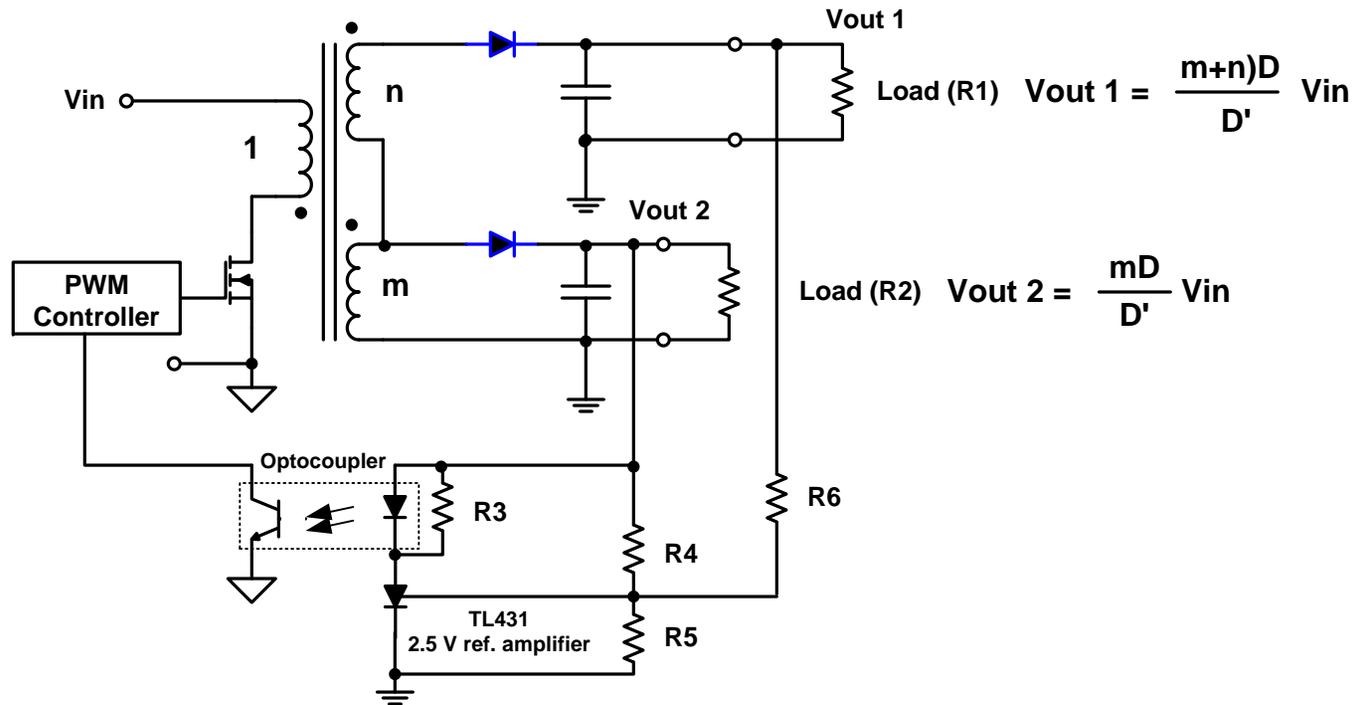

- Now, both outputs are sensed, and the regulator controls the combination of outputs.
  - Remember: There's only one feedback point. Neither output will be as tightly regulated as the main one when it had the feedback to itself!

# Weighting the Feedback

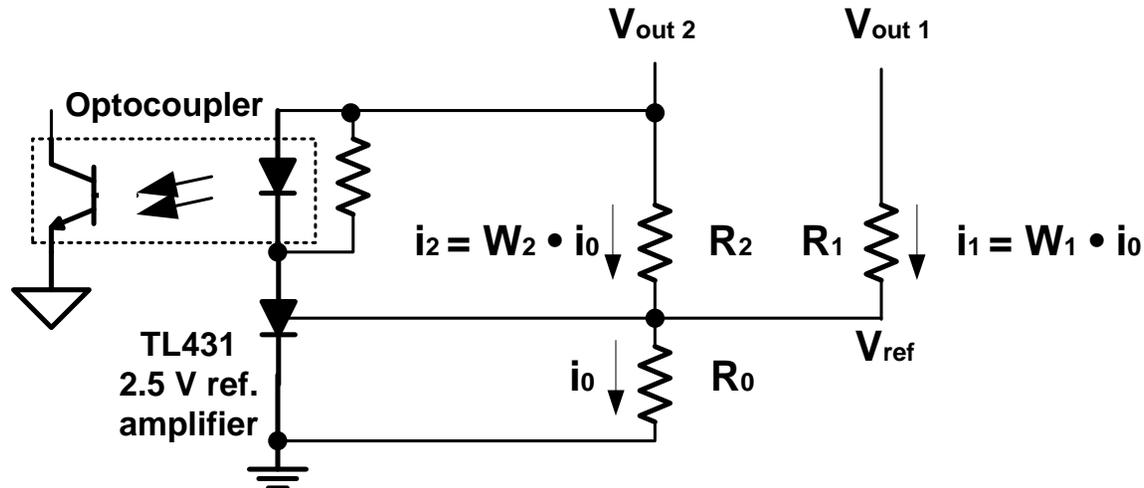


$$i_0 = i_1 + i_2 = W_1 \cdot i_0 + W_2 \cdot i_0 = i_0 (W_1 + W_2)$$

Therefore,  $W_1 + W_2 = 1$

$W_n$  is the “weight” of the feedback from output n.

- If  $W_1 = 0.9$  and  $W_2 = 0.1$ , then output 1 is nine times as important as output 2.
  - ( $W_1$  has a weight of 90%, and  $W_2$  has a weight of 10%)

# Designing the Feedback

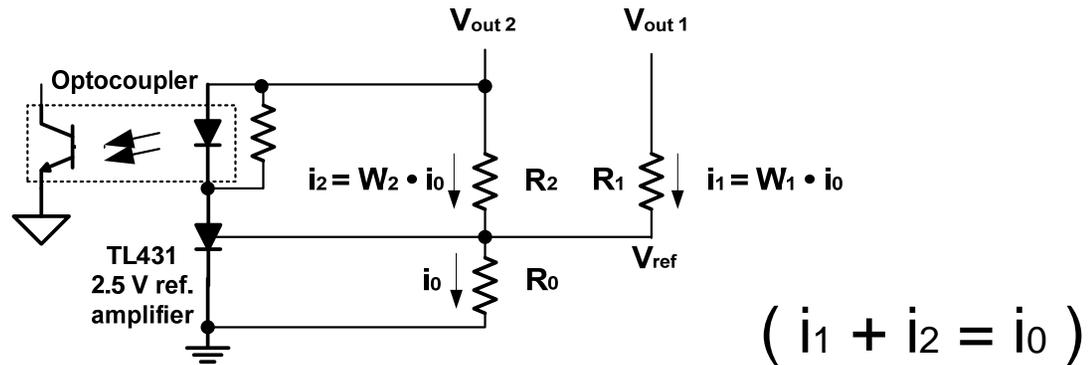

$$V_{out1} - V_{ref} = i_1 R_1$$

$$R_1 = \frac{V_{out1} - V_{ref}}{i_1} = \frac{V_{out1} - V_{ref}}{W_1 i_0}$$

$$R_2 = \frac{V_{out2} - V_{ref}}{i_2} = \frac{V_{out2} - V_{ref}}{W_2 i_0}$$

# Example

Procedure:

- Given:  $V_{out1} = 5$ ,  $V_{out2} = 12$ ,  $V_{ref} = 2.5$
- Choose  $i_0 = 1 \text{ mA}$
- Choose  $W_1 = 0.7$  and  $W_2 = 0.3$


Calculating the values:

$$R_0 = \frac{V_{ref}}{i_0} = \frac{2.5}{1 \text{ mA}} = 2.5 \text{ k}\Omega$$

$$R_1 = \frac{V_{out1} - V_{ref}}{W_1 i_0} = \frac{5 - 2.5}{0.7 \cdot 1 \text{ mA}} = 3.57 \text{ k}\Omega$$

$$R_2 = \frac{V_{out2} - V_{ref}}{W_2 i_0} = \frac{12 - 2.5}{0.3 \cdot 1 \text{ mA}} = 31.7 \text{ k}\Omega$$


# More Outputs? No Problem

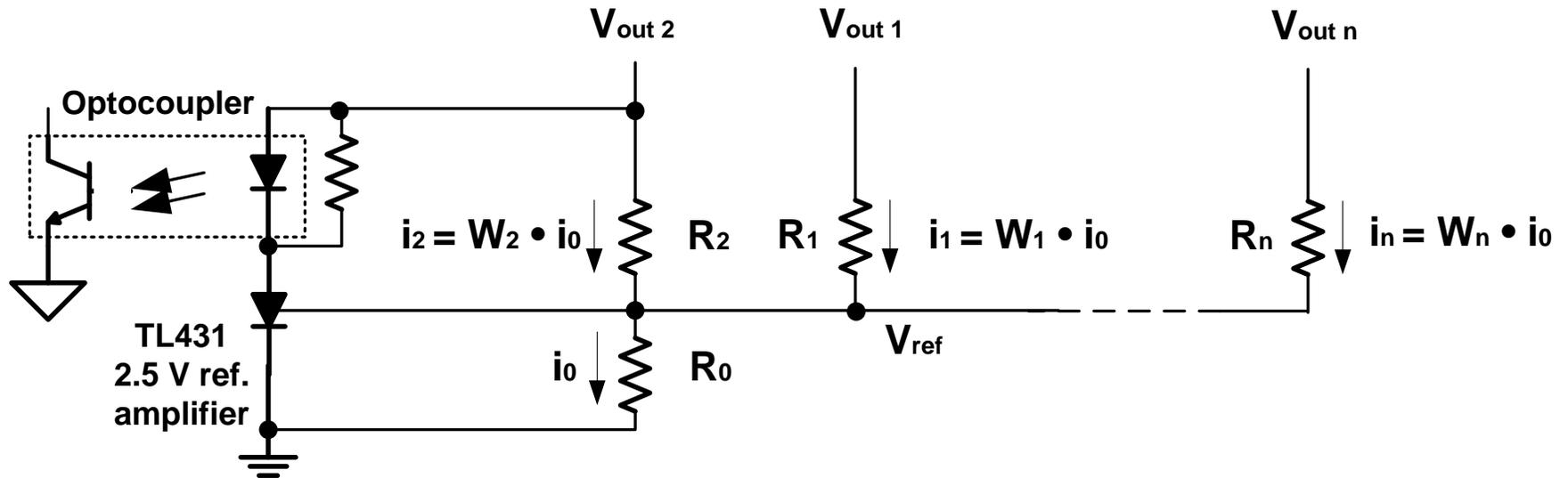


- Feedback can be from any number of outputs.
- **Provided that:  $W_1 + W_2 + \dots + W_n = 1$**

$$R_n = \frac{V_{out n} - V_{ref}}{W_n \cdot i_0}$$

# The “Magic” Capacitor

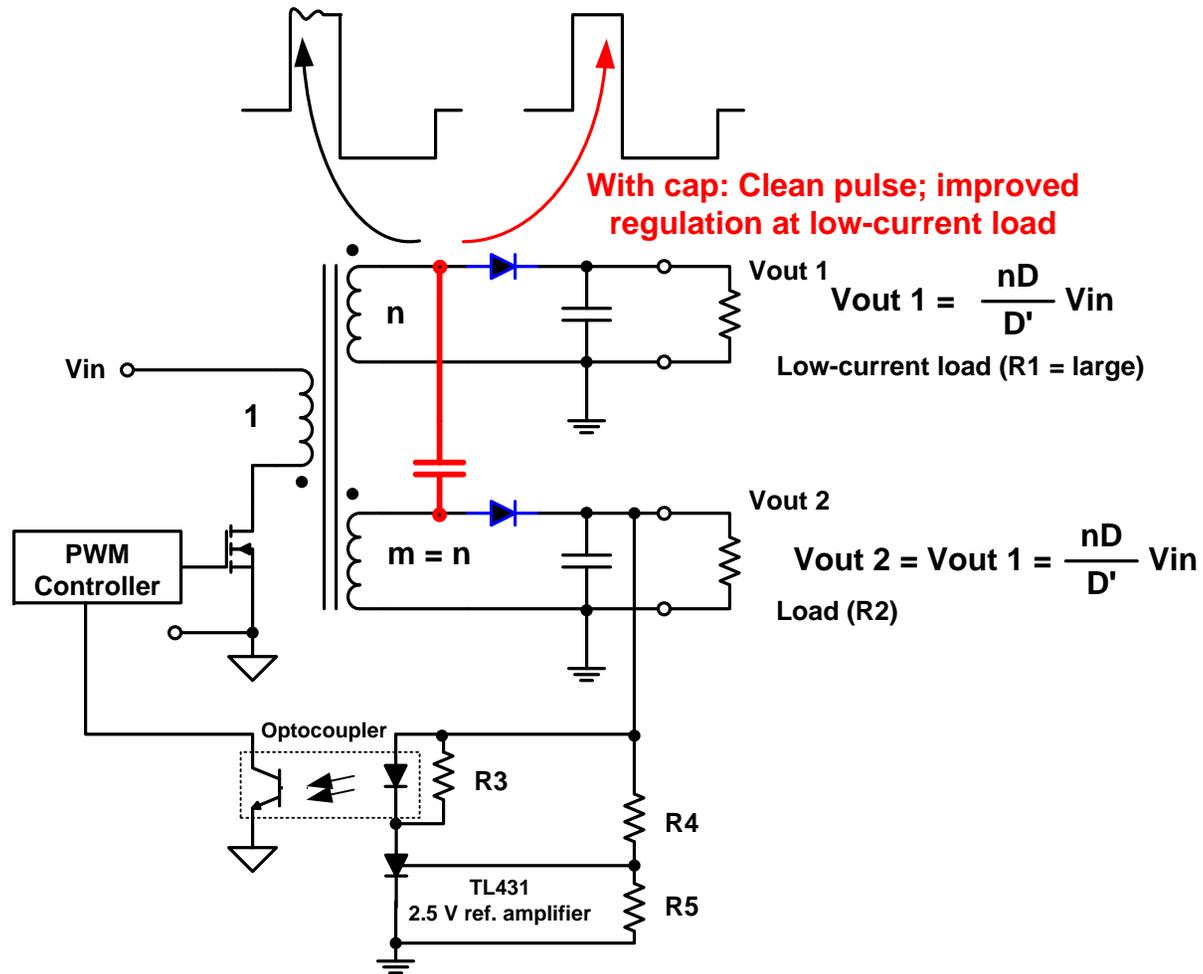

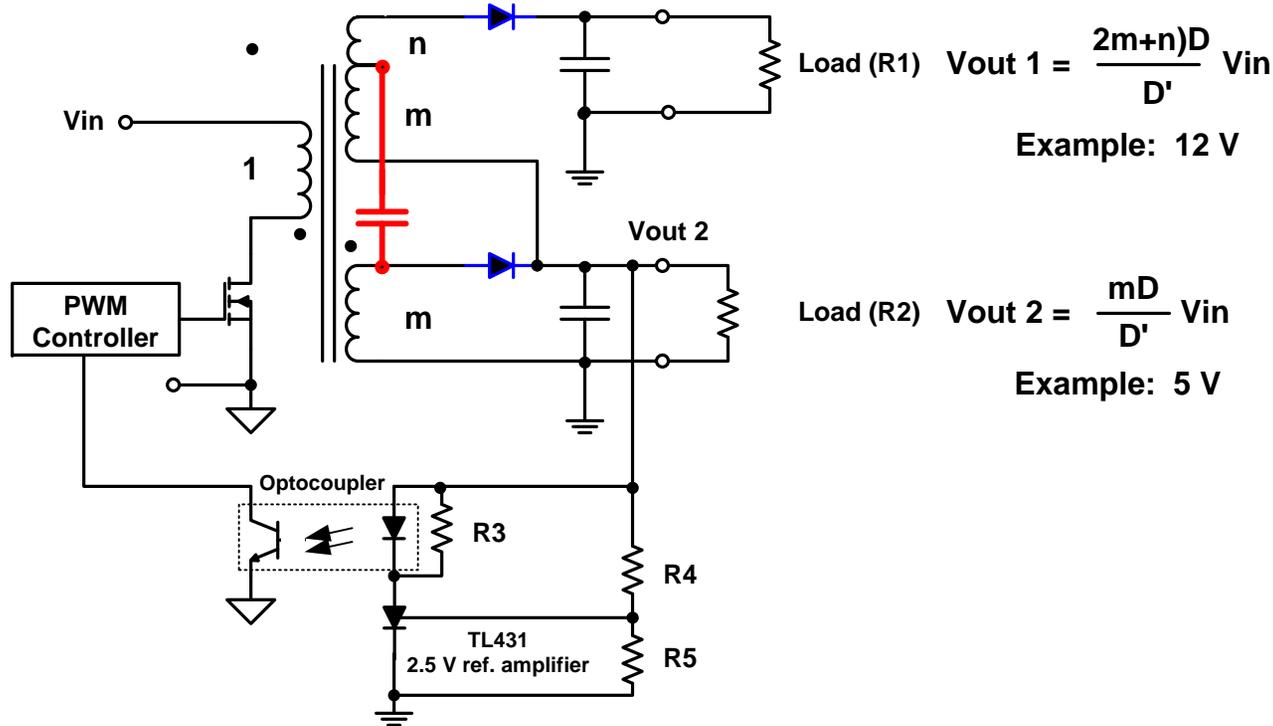
# Another Version of the “Magic” Capacitor



- Here, since the bottom of upper secondary is tied to Vout 2 (which is dc), waveforms at each end of the capacitor are identical.
- Overshoot & ringing at light load on Vout 1 is reduced by 5/7, since 5 of the 7 added turns are tightly coupled via the capacitor. (m = 5, n = 2, m+n = 7).

# Adding an Output to a Buck Converter

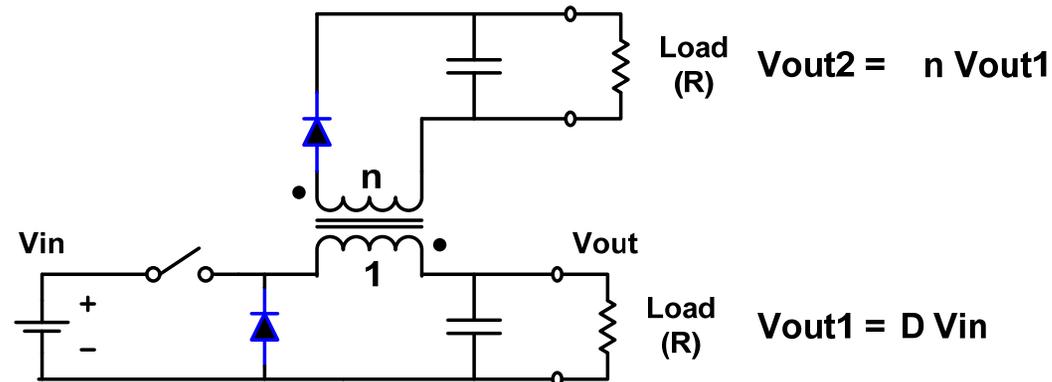

- During the “off” time of the switch, the output voltage across the inductor is coupled to a new output via an added winding!
- No free lunch. There must be enough energy stored in the choke to feed the new output.
- Ampere-turns are preserved, so current drawn from the new output causes discontinuous current in the main output.
  - Ripple current in the main output capacitor increases.

---

# Design Example, Built and Tested

## **65 Watt, 8 Output Set Top Box Power Supply**

*Frank Cathell,  
Senior Applications Engineer*



# General Specifications

- **Input:** 90 to 135 Vac, 47 – 63 Hz
- **Inrush current:** 30 A cold start; 60 A warm start
- **Efficiency:** > 80% at nominal loading
- **Output Voltages/Regulation/Ripple:**

| <u>Channel</u> | <u>Vout</u> | <u>Output type</u> | <u>Regulation</u> | <u>Max Ripple</u> | <u>Current</u> | <u>Surge</u> |
|----------------|-------------|--------------------|-------------------|-------------------|----------------|--------------|
| 1              | 2.6 V       | Buck reg.          | +/-1%             | 40 mVp/p          | 3 A            | 4 A          |
| 2              | 3.3 V       | Buck reg.          | +/-1%             | 40 mVp/p          | 4 A            | 5 A          |
| 3              | 5 V         | Main output        | +/-2%             | 50 mVp/p          | 3 A            | 4 A          |
| 4              | 6.2 V       | Quasi-reg.         | +/-6%             | 50 mVp/p          | 1.5 A          | 2 A          |
| 5              | 9 V         | 3-T reg.           | +/-1%             | 30 mVp/p          | 100 mA         | 200 mA       |
| 6              | 12 V        | Main output        | +/-2%             | 50 mVp/p          | 1 A            | 3 A          |
| 7              | 30 V        | Quasi-reg.         | +/-8%             | 100 mVp/p         | 20 mA          | 40 mA        |
| 8              | -5 V        | 3-T reg.           | +/-1%             | 30 mVp/p          | 30 mA          | 60 mA        |

- **Output overshoot:** 5% max; typically <1%
- **Overcurrent/short circuit protection:** Protected against accidental overloads via reduced duty cycle, burst mode operation
- **No load:** Output voltages are controlled and stable under no load conditions
- **Hold-up time/power fail detection:** Output will hold up for 20 ms following drop out at 100 V ac and nominal load; power fail warning following holdup period with 5 ms minimum delay to output voltage dropout.
- **Temperature:** Operation from 0 to 50° C (no over temp protection included)



# Circuit Features

- **Critical conduction mode flyback converter**
  - **NCP1207**
- **2.6 V and 3.3 V outputs derived from 12 V output**
  - **NCP1580 synchronous buck controllers**
- **Low current outputs on -5 V and +9 V allowed use of conventional 3-T regulators**
- **Control loop closed via sum of 5 V & 12 V outputs; all other outputs quasi-regulated**
- **Transformer main secondary made from foil winding for low leakage inductance**
- **“Stacked” secondary windings utilized for improved cross-regulation**
- **Simple but effective power fail detection circuit utilizing TL431 and 2N2222**
- **Overcurrent protection implemented by initiating burst mode of NCP1207A**
- **2-wire ac input with dual common mode EMI filter inductors**
- **Single-sided printed circuit board**



# Set-Top Box Test Results

## Regulation Data (120VAC input)

| Parameter                          | Outputs |       |       |           |         |        |           |         |
|------------------------------------|---------|-------|-------|-----------|---------|--------|-----------|---------|
|                                    | 2.6V    | 3.3V  | 5V    | 6V        | 9V      | 12V    | 30V       | neg 5V  |
| Output type                        | Buck    | Buck  | Main  | Quasi-reg | 3-T reg | Main   | Quasi-reg | 3-T reg |
| Vout setpoint at typical loads     | 2.53V   | 3.4V  | 4.89V | 6.27V     | 8.94V   | 12.54V | 31.0V     | 4.96V   |
| Vout setpoint at minimum loads     | 2.55V   | 3.42V | 4.96V | 6.38V     | 8.94V   | 12.33V | 32.70V    | 4.98V   |
| Vout setpoint at maximum loads     | 2.54V   | 3.34V | 4.90V | 6.29V     | 8.94V   | 12.53V | 30.10V    | 4.95V   |
| Vout setpoint at no output loading | 2.56V   | 3.43V | 5.02V | 6.54V     | 8.93V   | 12.13V | 29.60V    | 4.97V   |

Note: Vout setpoints measured at PC board



# More Test Results

## Efficiency Measurements (120VAC input)

| Parameter        | Outputs |      |       |      |      |       |       |                     |
|------------------|---------|------|-------|------|------|-------|-------|---------------------|
|                  | 2.6V    | 3.3V | 5V    | 6V   | 9V   | 12V   | 30V   | neg 5V              |
| Output Voltage   | 2.54    | 3.42 | 4.91  | 6.31 | 8.94 | 12.48 | 30.06 | 4.96                |
| Output Current   | 3.8A    | 2.9A | 1.56A | 1.3A | 91mA | 1.0A  | 30mA  | 73mA                |
| Output Power (W) | 9.65    | 9.92 | 7.66  | 8.2  | 0.81 | 12.48 | 0.9   | 0.36 (49.98W total) |

Total Pout = 49.98W

Pin at 120VAC = 61.4W

Efficiency = 81.4%

| Parameter                             | Outputs |      |      |      |      |      |       |                         |
|---------------------------------------|---------|------|------|------|------|------|-------|-------------------------|
|                                       | 2.6V    | 3.3V | 5V   | 6V   | 9V   | 12V  | 30V   | neg 5V                  |
| <u>Output Ripple</u><br>(@ max loads) | 27mV    | 45mV | 50mV | 50mV | 40mV | 30mV | 100mV | 20mV (10:1 scope probe) |
| <u>Output Overshoot</u><br>(turn-on)  | none    | none | none | none | none | none | none  | none                    |

Holdup Time (prior to PF warning) at 100 Vac in, maximum output loads: 25ms


Power Fail warning time (Vout decay to 90%): 15ms

Line Regulation: Minimal on all outputs; +/- 20mV max



# Schematic

FIGURE 1: Schematic

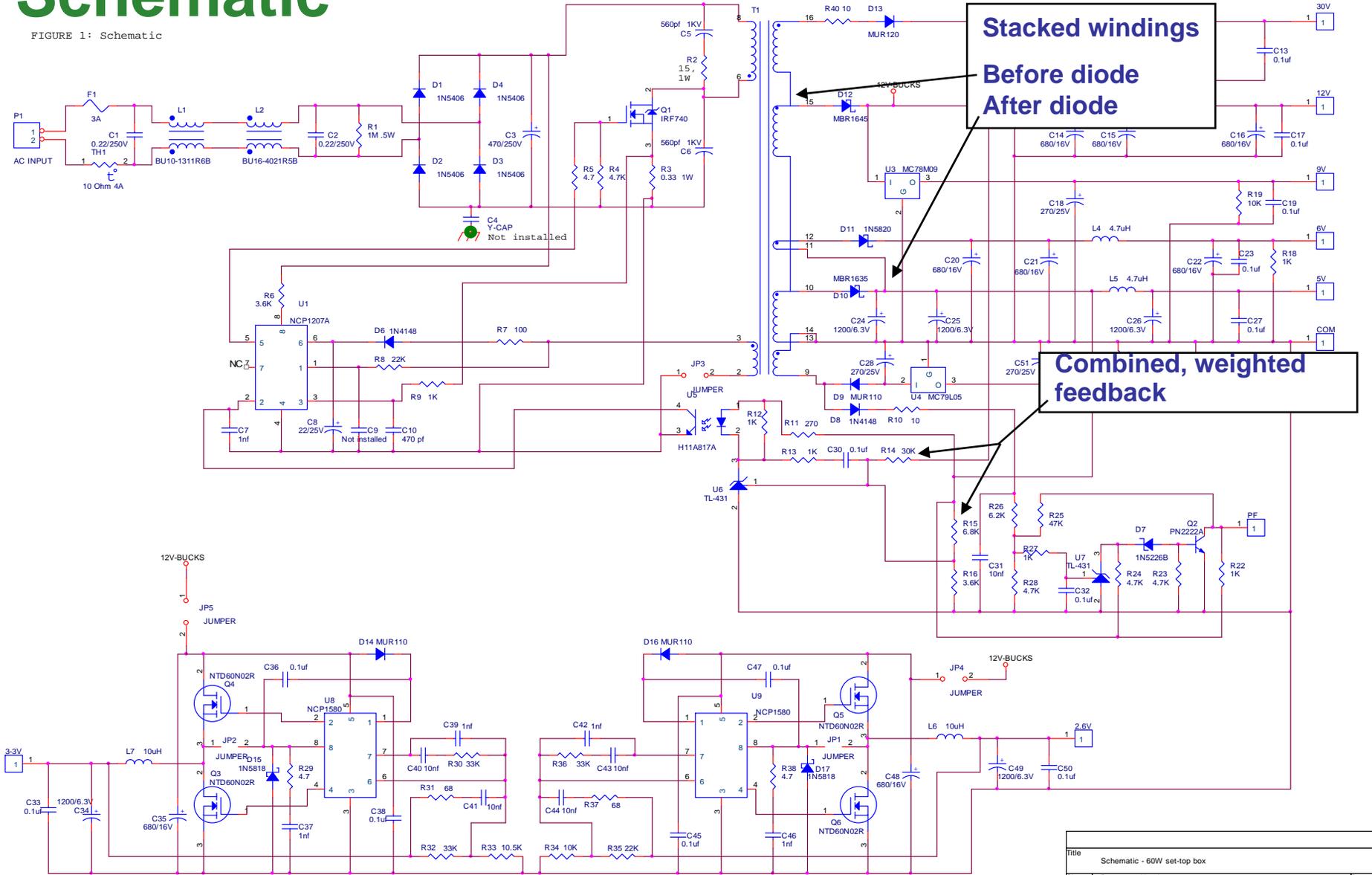

|       |                             |              |
|-------|-----------------------------|--------------|
| Title | Schematic - 60W set-top box |              |
| Size  | Document Number<br><Doc>    | Rev<br>C     |
| Date: | Tuesday, May 31, 2005       | Sheet 1 of 1 |



# Conclusion

- Multiple output switched-mode power supplies save space, save cost, and can have high performance.
  - The “tricks” you’ve seen here can make them even better!
- Flybacks are popular, because there is only one magnetic component.
- They work best where the load ranges of the outputs are well-known.
  - This allows the designer to tailor the regulation characteristics to the load regulation requirements, favoring certain loads when necessary.
- For good cross-regulation, construction of the transformer is important.
  - Beware of changing vendors during production!



---

## For More Information

- View the extensive portfolio of power management products from ON Semiconductor at [www.onsemi.com](http://www.onsemi.com)
- View reference designs, design notes, and other material supporting the design of highly efficient power supplies at [www.onsemi.com/powersupplies](http://www.onsemi.com/powersupplies)

