



**ON Semiconductor®**

**Adapters < 75 W**

---

# Agenda

- New ENERGY STAR® requirements
- Needed features to meet the new specification
- New controllers
- Practical examples
- Conclusion



# EPA 2.0 (External Power Supplies)

EPA ENERGY STAR Version 2.0 EPS Voluntary Specification  
(Effective November 1, 2008)

*Energy-Efficiency Criteria for Ac-Ac and Ac-Dc External Power Supplies  
in Active Mode: Standard Models*

| Nameplate Output Power ( $P_{no}$ ) | Minimum Average Efficiency in Active Mode<br>(expressed as a decimal) |
|-------------------------------------|---|
| 0 to $\leq$ 1 watt                  | $\geq 0.480 * P_{no} + 0.140$   |
| $> 1$ to $\leq$ 49 watts            | $\geq [0.0626 * \ln(P_{no})] + 0.622$                                 |
| $> 49$ watts                        | $\geq 0.870$  |

*(was  $> 0.84$  in previous version 1.1)*

*Energy Consumption Criteria for No-Load*

| Nameplate Output Power ( $P_{no}$ ) | Maximum Power in No-Load |                  |
|-------------------------------------|--------------------------|------------------|
|                                     | AC-AC EPS                | AC-DC EPS        |
| 0 to $<$ 50 watts                   | $\leq 0.5$ watts         | $\leq 0.3$ watts |
| $\geq 50$ to $\leq 250$ watts       | $\leq 0.5$ watts         | $\leq 0.5$ watts |

*(< 0.5 W in 1.1)*

*(< 0.75 W in 1.1)*



---

# Agenda

- New ENERGY STAR<sup>®</sup> requirements
- Needed features to meet the new specification
- New controllers
- Practical examples
- Conclusion



# Improving Efficiency


- Sources of loss:

- Switching losses:

$$P_{loss(sw)} = \frac{1}{2} \cdot C_{DRAIN} \cdot V_{DRAIN(turn-off)}^2 \cdot F_{SW}$$

- Gate charge losses:
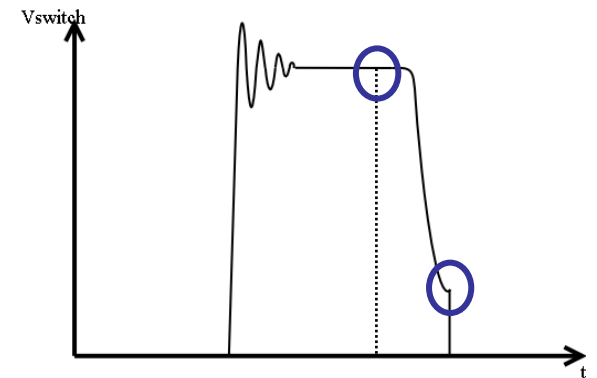
$$P_{loss(gate)} = V_{gate(high)} \cdot Q_{gate} \cdot F_{SW}$$




- Ways to improve efficiency:

- Lower the switching frequency  $F_{SW}$  → frequency foldback at light loads

- Lower the Drain voltage at turn-off → valley switching
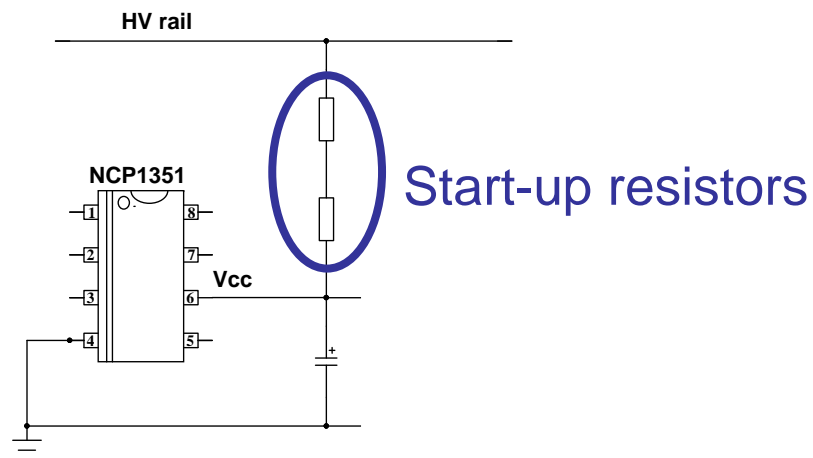
# Reducing No-load Input Power

- Static losses in the start-up circuit:
  - Start-up resistor permanently drawing current from the bulk capacitor
- Ways to lower the start-up circuit losses
  - With external start-up resistor → Extremely low start-up current
  - Integrated start-up current source → Extremely low leakage when off
  - Connect the start-up circuit to the half-wave rectified ac input



---

# Agenda

- New ENERGY STAR<sup>®</sup> requirements
- Needed features to meet the new specification
- New controllers
- Practical examples
- Conclusion



# The Right Controllers

- Two new families of controllers implement features to increase efficiency and lower no-load input power:
  - NCP1237/38/87/88:
    - fixed-frequency controllers with integrated start-up current source, frequency foldback and skip mode
    - Increased efficiency at light load and standby
  - NCP1379/80
    - valley switching controllers with extremely low start-up current and frequency foldback
    - Increased efficiency at all load levels



# NCP1237/38/87/88

## Value Proposition

The NCP12X7/X8 series represents the next generation of fixed frequency PWM controllers. It targets applications where cost-effectiveness, reliability, design flexibility and low standby power are compulsory.

### Unique Features

- High-voltage current source with built-in Brown-out and mains OVP
- Freq. reduction in light load conditions and skip mode
- Adjustable Over Power Protection

### Benefits

- Fewer components and rugged design
- Extremely low no-load standby power
- Simple option to alter the max. peak current set point at high line

### Others Features

- Latch-off input for severe fault conditions, allowing direct connection of NTC
- Timer-based protection: auto-recovery or latched
- Dual OCP option available
- Built-in ramp compensation
- Frequency jittering for a softened EMI signature
- Vcc operation up to 30 V

### Market & Applications

- AC-DC adapters for notebooks, LCD monitor, game console, printers
- CE applications (DVD, STB)

### Application Data



|          | DSS     | Dual OCP | Latch | Auto Recovery |
|----------|---------|----------|-------|---------------|
| NCP1237A | Yes     | Yes      | Yes   |               |
| NCP1237B | Yes     | Yes      |       | Yes           |
| NCP1238A | Yes     | No       | Yes   |               |
| NCP1238B | Yes     | No       |       | Yes           |
| NCP1287A | HV only | Yes      | Yes   |               |
| NCP1287B | HV only | Yes      |       | Yes           |
| NCP1288A | HV only | No       | Yes   |               |
| NCP1288B | HV only | No       |       | Yes           |



Various options available depending upon end applications needs


### Ordering & Package Information

- NCP1237/38xDR2G - NCP1287/88xDR2G
- SOIC-7 2500p per reel

 O, DW


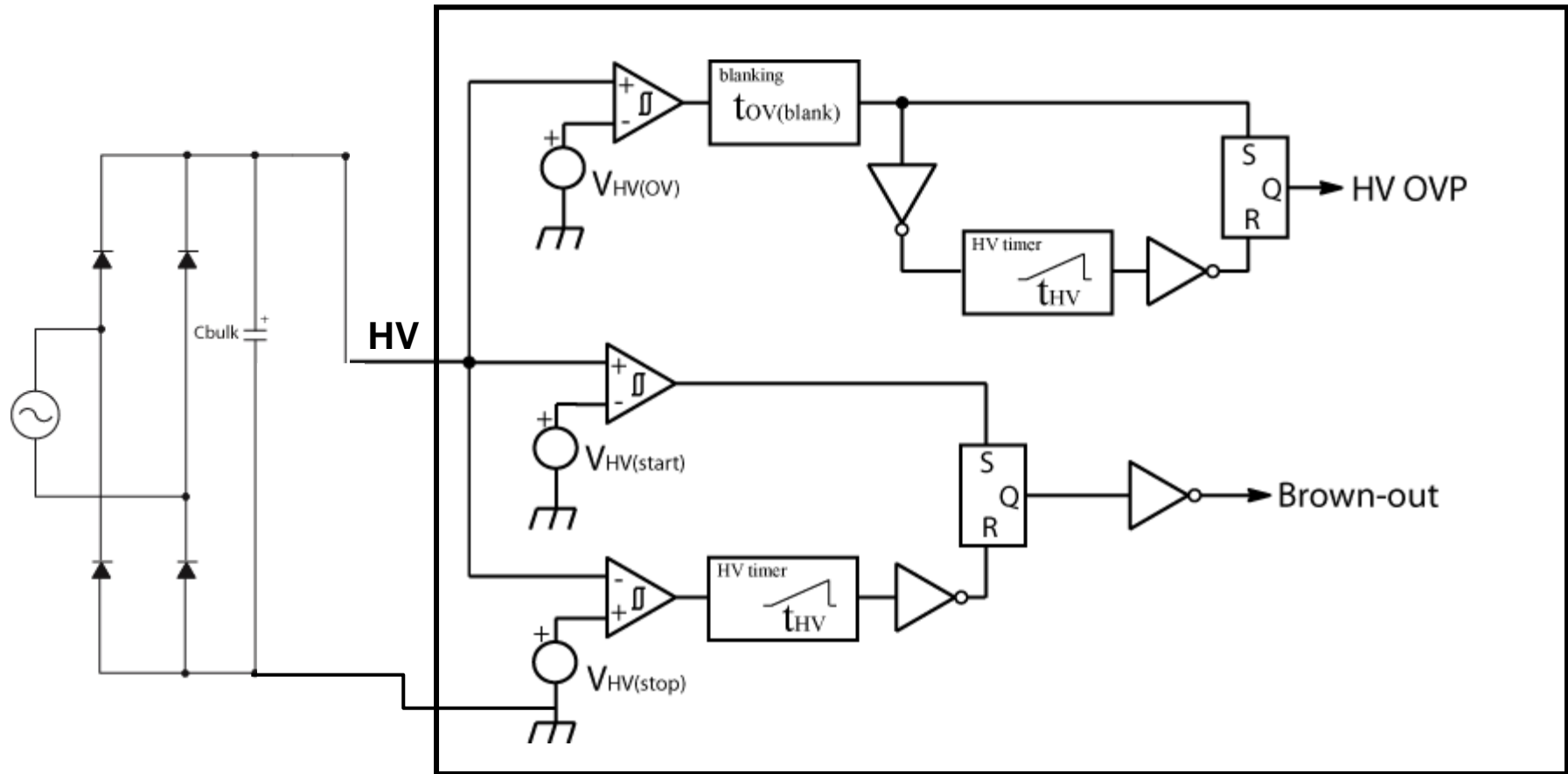
# NCP1237/38/87/88 – Brown-out and Mains OVP





Detection independent of  
Ripple on HV pin





Can be connected to the  
half-wave rectified ac line
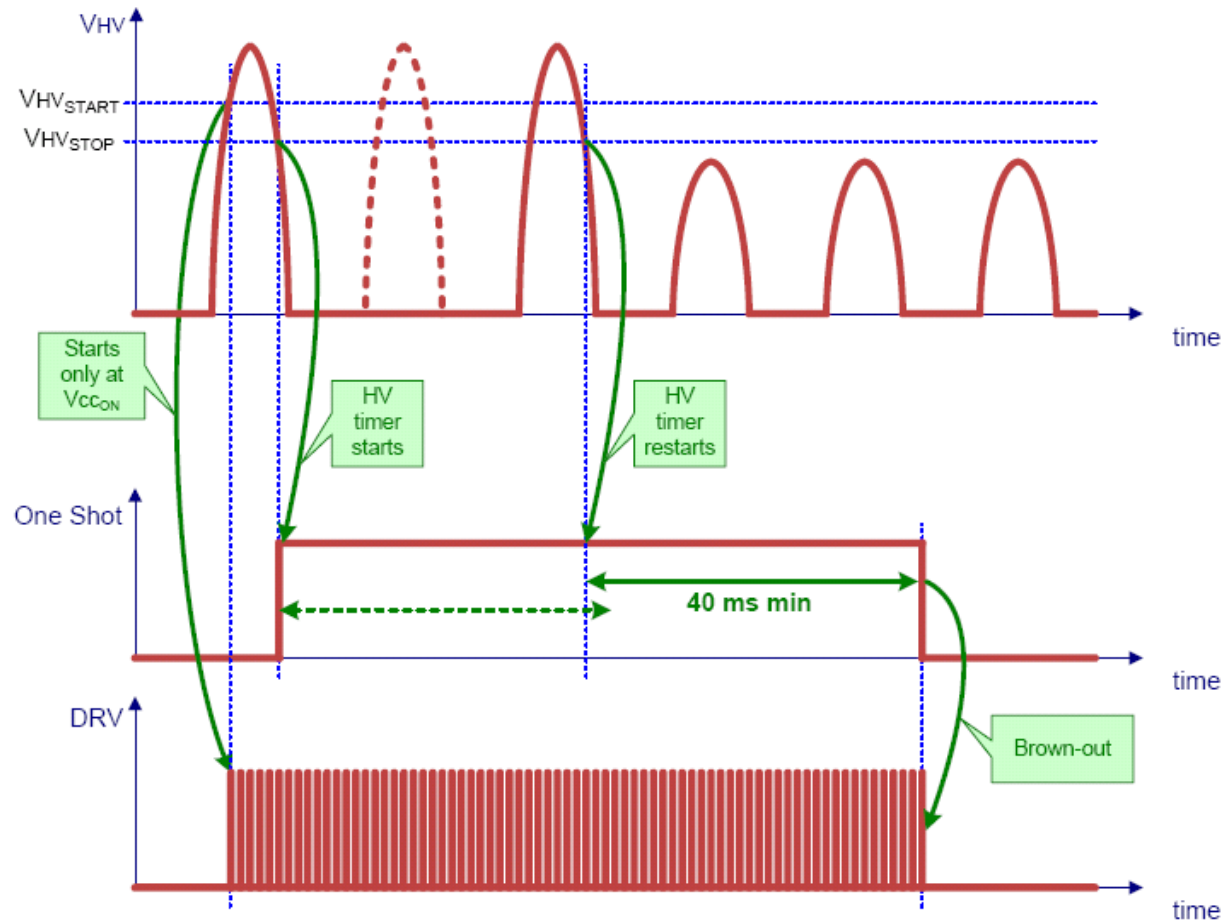
# NCP1237/38/87/88 – Brown-out and Mains OVP



Timer-based detection  Passes full line cycle drop-out
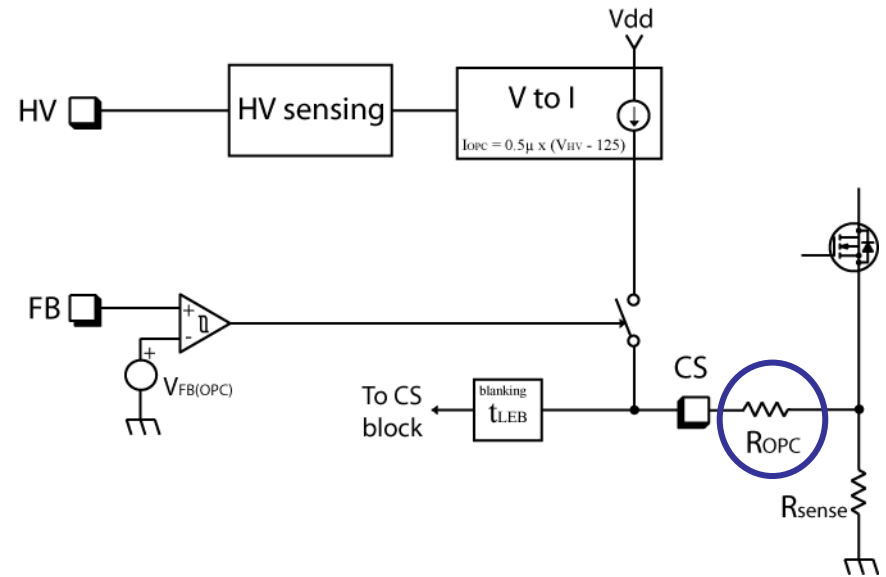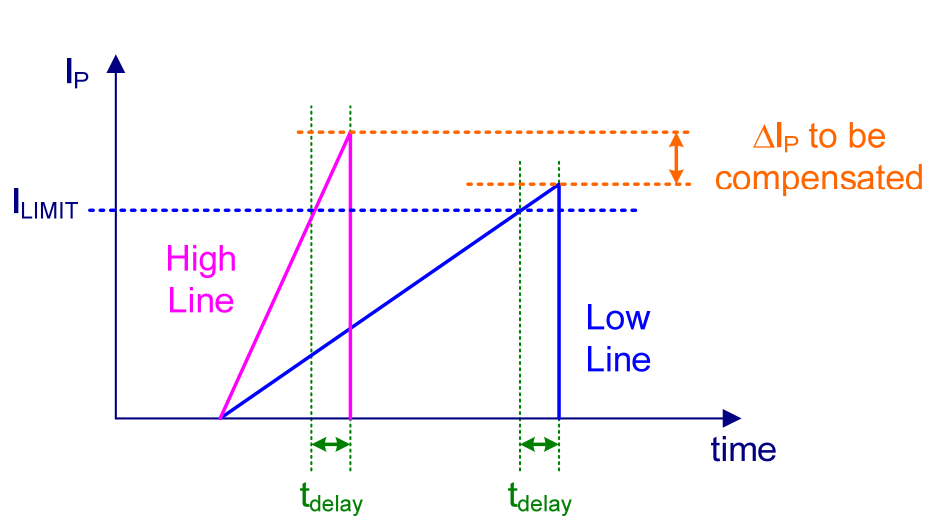
# NCP1237/38/87/88 – Over Power Protection




*Need to compensate for the effect of the propagation delay*

*The compensation current creates an offset on the Current Sense signal*

Over Power Protection  Maximum output power clamped

# NCP1237/38/87/88 – Frequency Foldback

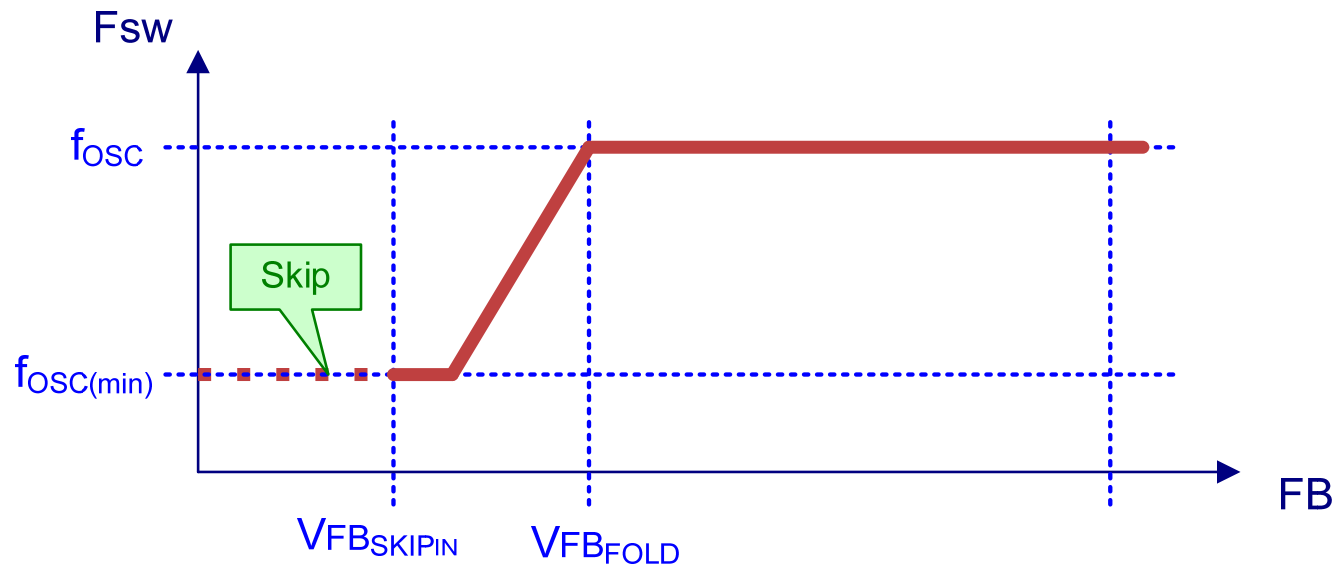

Switching frequency lowered at light load




Increased efficiency

Switching frequency clamped at 25 kHz




No audible noise
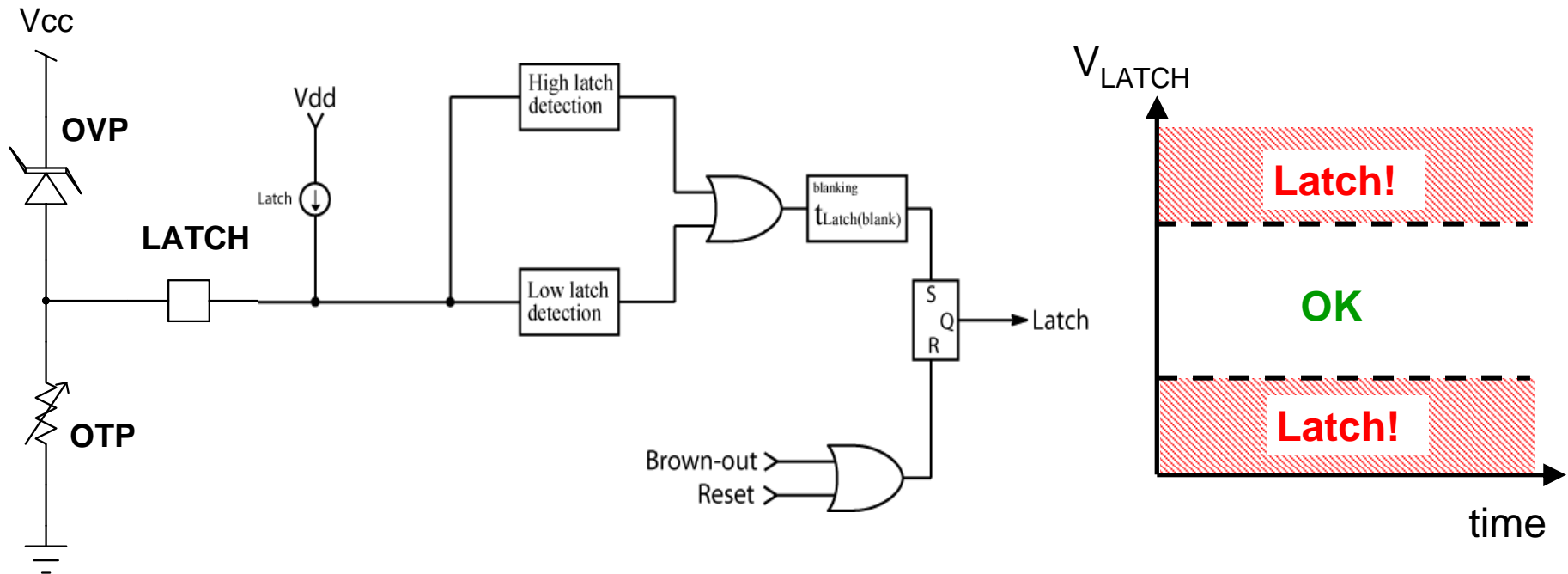
# NCP1237/38/87/88 – Latch-off Protection



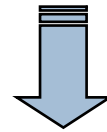An NTC thermistor can be directly connected to the IC



Less external components needed

# NCP1379/80

## Value Proposition

The NCP1380 is a high-performance circuitry aimed to powering QR converters. Capitalizing on a novel valley-lockout system, the controller shifts gears and reduces the switching frequency as the power loading becomes lighter.

## Unique Features

- Valley switching operation with valley-lockout
- Freq. reduction in light load condition
- Adjustable Over Power Protection

## Benefits

- Excellent efficiency over a wide range and noise free operation
- Extremely low no-load standby power
- Simple option to alter the max. peak current set point at high line

## Others Features


- Auto-recovery or latched internal output short-circuit protection
- Fixed 80 ms timer for short-circuit protection
- Combined Over-voltage and over-temperature protection (A and B versions)
- Combined OVP & brown-out (C and D versions)
- 3  $\mu$ s blanking delay to ignore leakage ringing at turn-off

## Market & Applications

- AC-DC adapters for notebooks, LCD monitor, game console
- Auxiliary power for Flat TVs
- CE applications (DVD, STB)



## Application Data

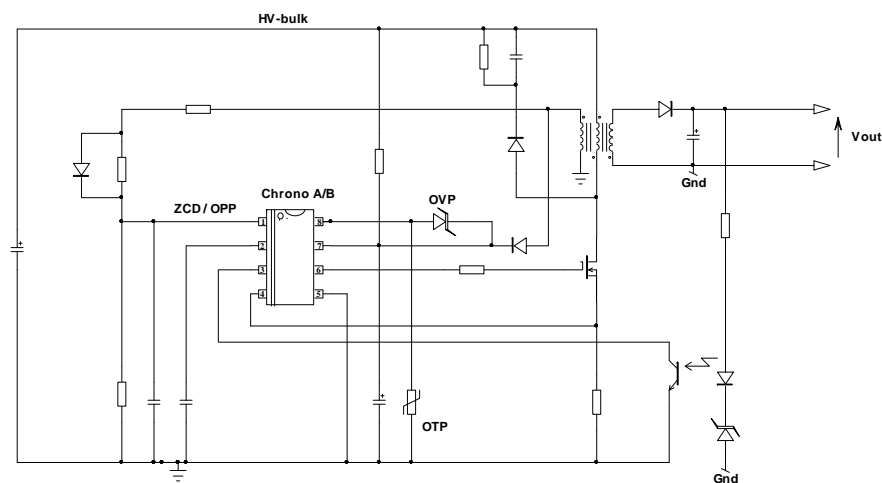

Design flexibility

## Ordering & Package Information

- NCP1380xDR2G
- SOIC-8 2500p per reel




O, DW



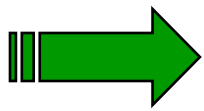
# NCP1379/80 - QR Mode with Valley Lockout

- As the load decreases, the controller changes valley (1<sup>st</sup> to 4<sup>th</sup> valley)
- The controller stays locked in a valley until the output power changes significantly.



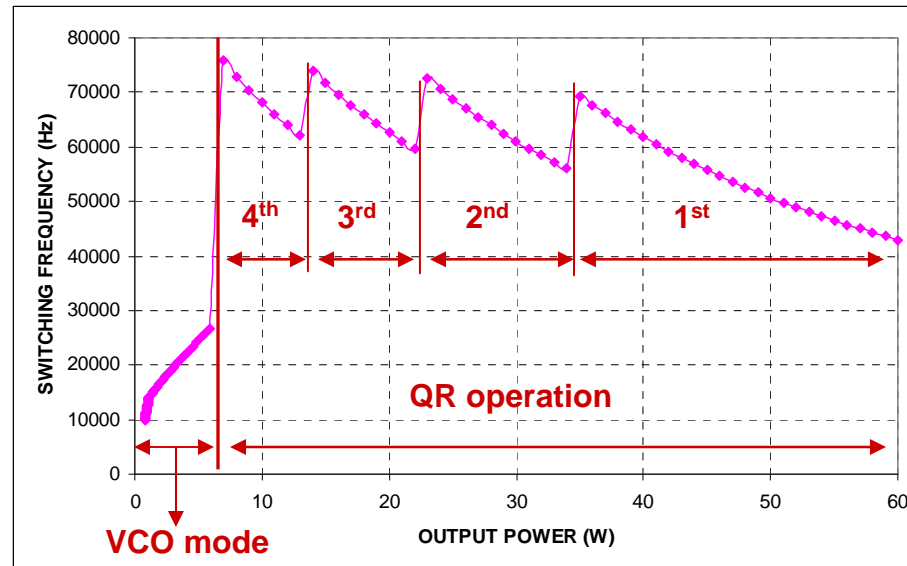
- No valley jumping noise
- Natural switching frequency limitation






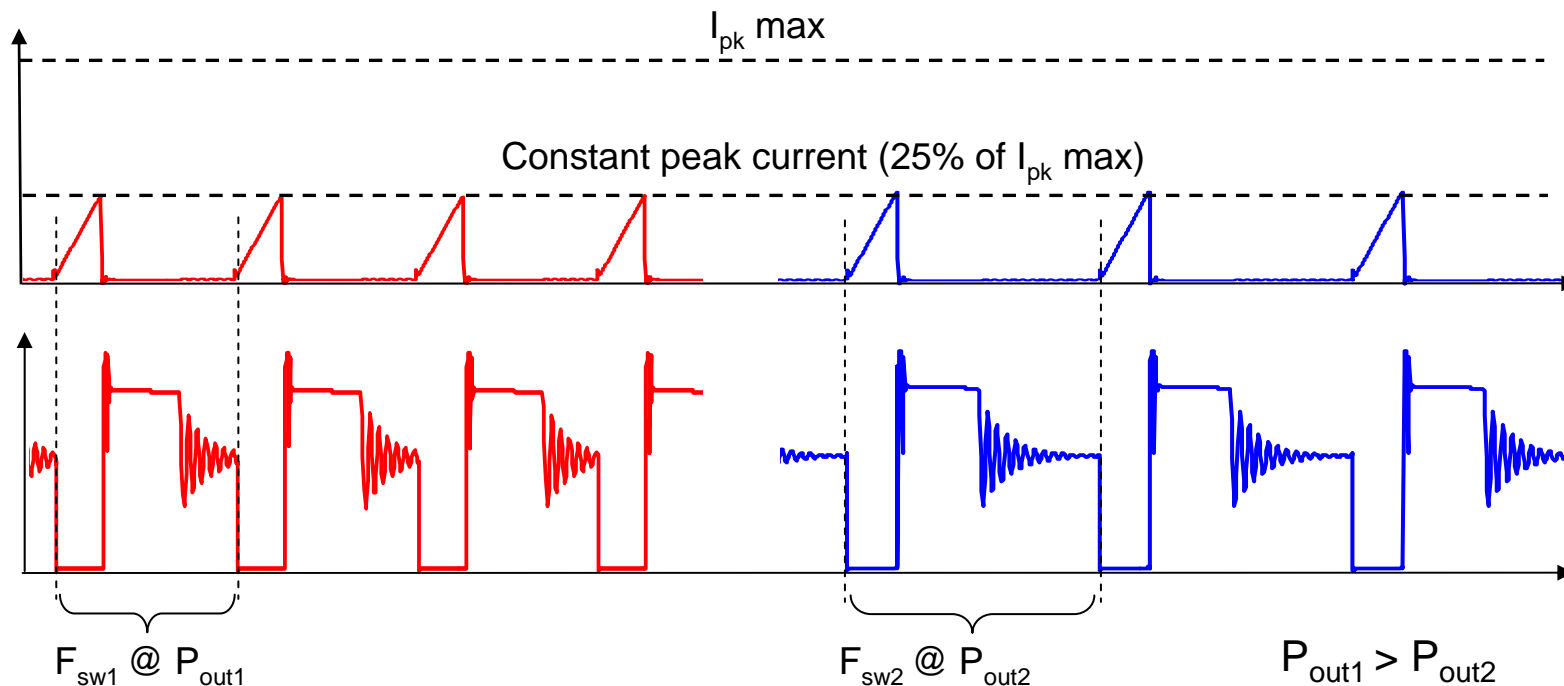
# NCP1379/80 - Frequency Foldback

- Occurs when  $V_{FB} < 0.8\text{ V}$  ( $P_{OUT}$  decreasing) or  $V_{FB} < 1.6\text{ V}$  ( $P_{OUT}$  increasing)
- Fixed peak current (25% of  $I_{pk,max}$ ), variable frequency set by the FB loop.



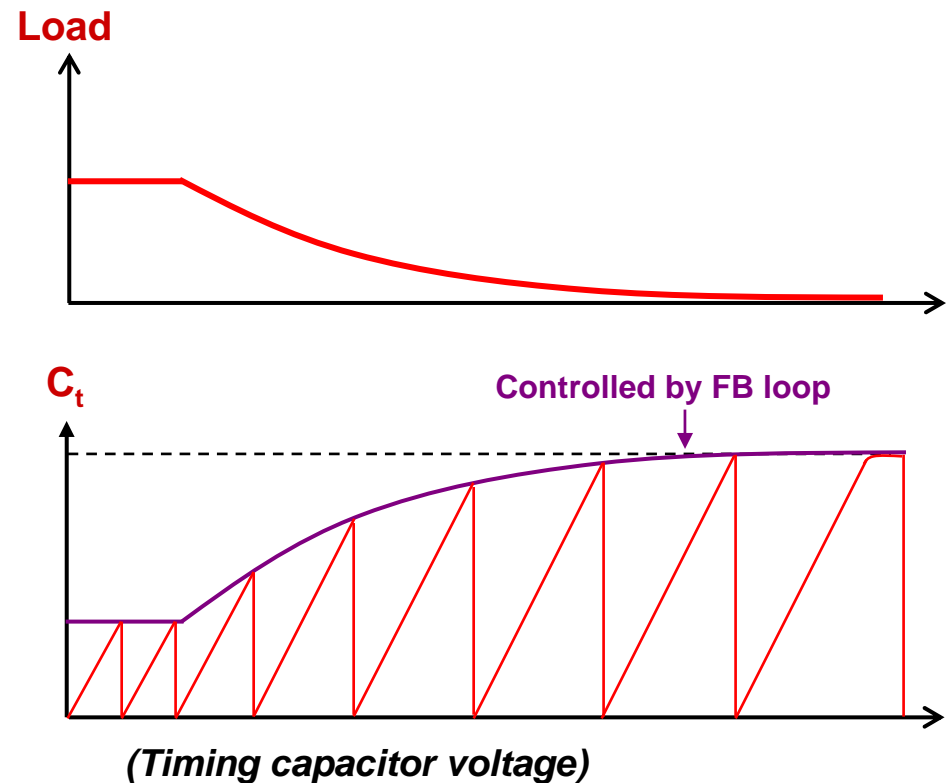
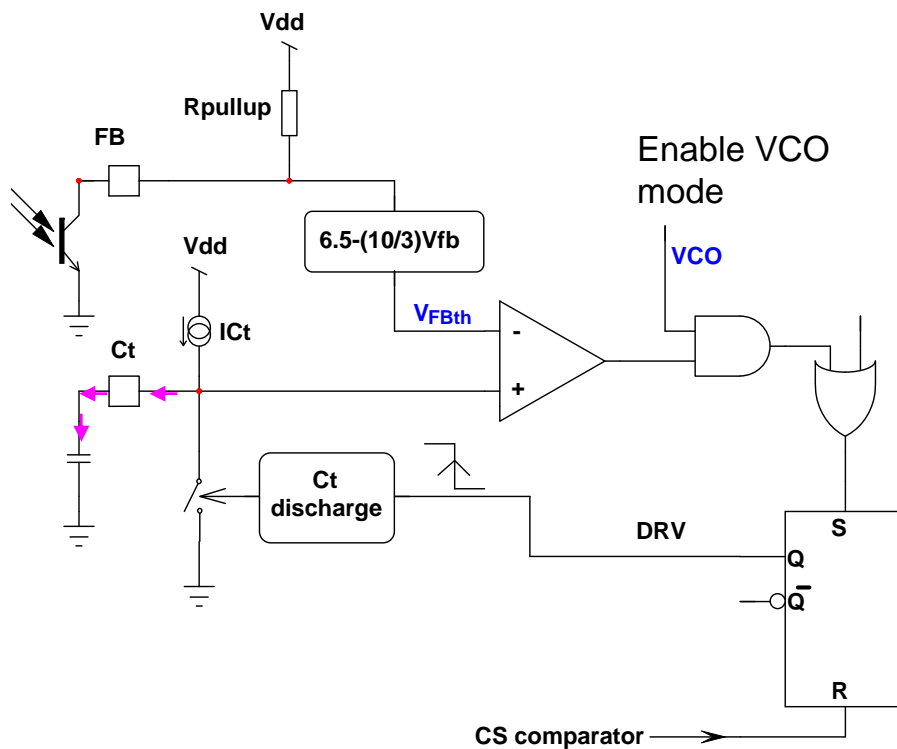
# NCP1379/80 - Frequency Foldback

- The switching frequency is set by the end of charge of  $C_t$  capacitor
- The end of charge of  $C_t$  capacitor is controlled by the FB loop


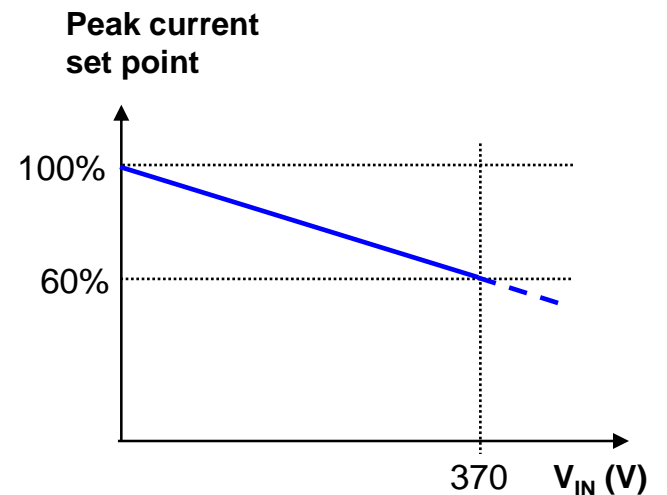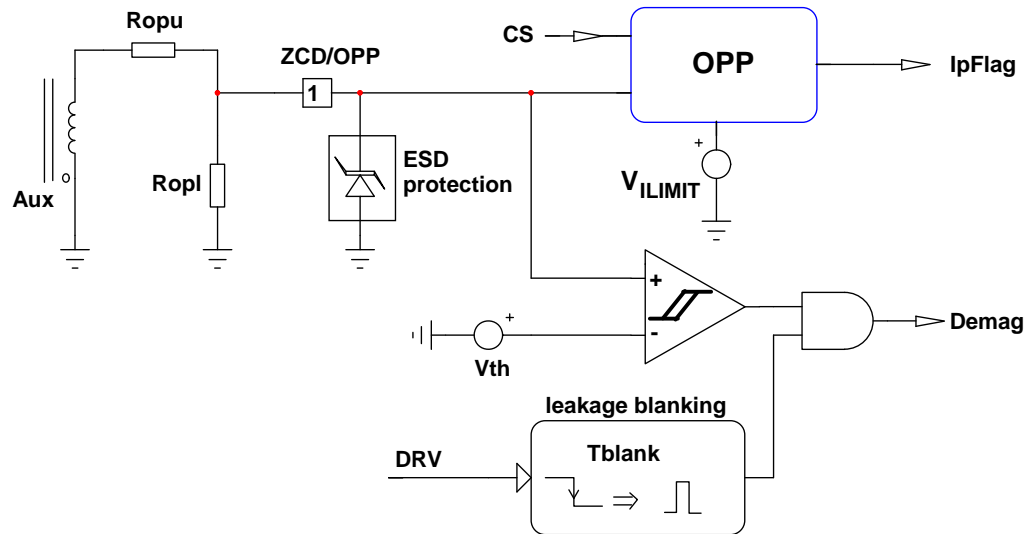
# NCP1379/80 - Overpower Protection

- $L_{aux}$  with flyback polarity swings to  $-NV_{IN}$  during the on time.
- Adjust amount of OPP voltage with  $R_{opu} // R_{opl}$ .
- $V_{CS,max} = 0.8 V + V_{OPP}$



Non dissipative OPP !

---


# Agenda

- New ENERGY STAR® requirements
- Needed features to meet the new specification
- New controllers
- Practical examples
- Conclusion


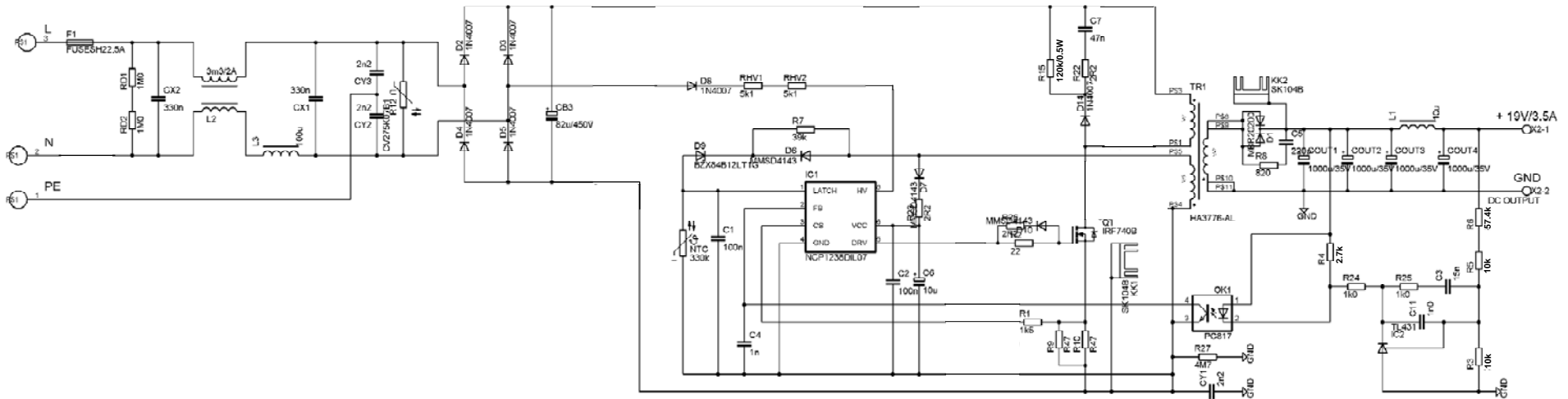
# Fixed-Frequency Example: Schematic

A typical 65 W notebook adapter (19 V output)



(not optimized for *EPS 2.0*)

# Fixed-Frequency Example: Efficiency

- EPS 2.0 efficiency (compared to NCP1271, from a previous generation)

| % of $P_{OUTnom}$<br>$V_{IN}$ | 115 Vac        |        | 230 Vac        |               |
|-------------------------------|----------------|--------|----------------|---------------|
|                               | <i>NCP1271</i> |        | <i>NCP1271</i> |               |
| 100 %<br>(65 W)               | 88.5 %         | 88.7 % | 88.4 %         | 88.2 %        |
| 75 %<br>(49 W)                | 89.2 %         | 89.1 % | 88.2 %         | 88.3 %        |
| 50 %<br>(32 W)                | 88.9 %         | 88.9 % | <u>86.8 %</u>  | <u>87.0 %</u> |
| 25 %<br>(16 W)                | 88.2 %         | 88.4 % | 87.3 %         | 84.3 %        |

Effect of the frequency foldback


**Average at 230 Vac: 87.7 %**

# Fixed-Frequency Example: Standby Power

- Light load and no load input power with the NCP1237  
(compared to NCP1271, from a previous generation)

| $P_{OUT}$ | $V_{IN}$ | 115 Vac            |                            | 230 Vac            |                             |
|-----------|----------|--------------------|----------------------------|--------------------|-----------------------------|
|           |          |                    | <i>NCP1271</i>             |                    | <i>NCP1271</i>              |
| 10.7 W    |          | 12.0 W<br>(88.7 %) | <i>12.2 W<br/>(87.5 %)</i> | 12.5 W<br>(85.1 %) | <i>13.2 W<br/>(80.76 %)</i> |
| 1.3 W     |          | 1.67 W<br>(78.0 %) | <i>1.77 W<br/>(72.9 %)</i> | 1.75 W<br>(74.2 %) | <i>2.46 W<br/>(52.4 %)</i>  |
| 0.5 W     |          | 0.74 W<br>(69.0 %) | <i>0.81 W<br/>(62.6 %)</i> | 0.76 W<br>(66.0 %) | <i>1.34 W<br/>(37.3 %)</i>  |
| No load   |          | 71 mW              | <i>76 mW</i>               | 97 mW              | <i>121 mW</i>               |

# Fixed-Frequency Example: Summary

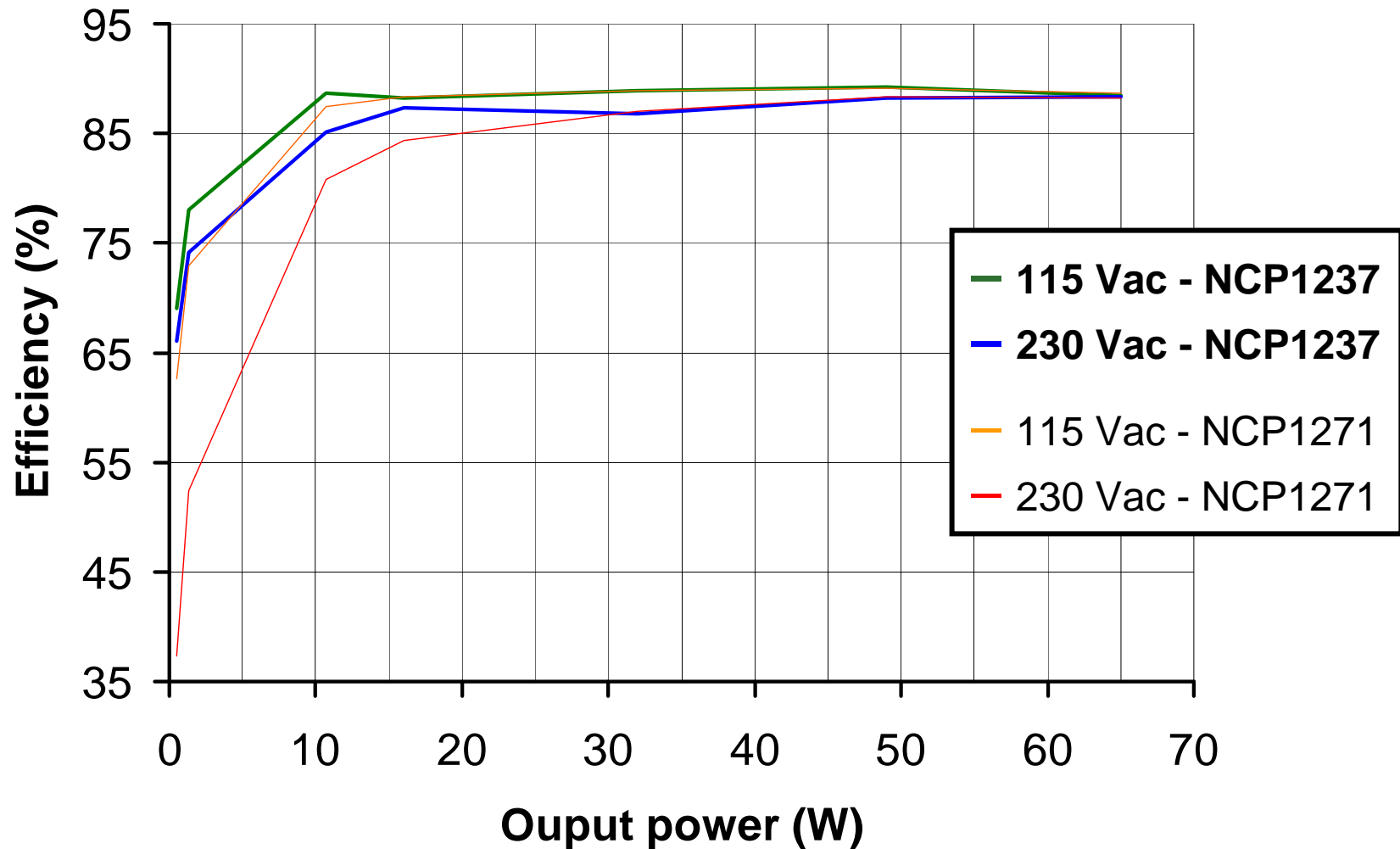



# Valley Switching Example: Efficiency

- EPS 2.0 efficiency with the NCP1380, valley switching controller

| $V_{IN}$<br>% of $P_{OUTnom}$ | 115 Vac | 230 Vac |
|-------------------------------|---------|---------|
| 100 %                         | 88.7 %  | 91.1 %  |
| 75 %                          | 88.8 %  | 90.9 %  |
| 50 %                          | 89.2 %  | 89.1 %  |
| 25 %                          | 88.2 %  | 87.9 %  |

**Average at 115 Vac: 88.7 %**

# Valley Switching Example: Standby Power

- Light load and no load input power with the NCP1380

| $P_{OUT}$ | $V_{IN}$ | 115 Vac             | 230 Vac             |
|-----------|----------|---------------------|---------------------|
| 10.7 W    |          | 12.37 W<br>(86.5 %) | 12.44 W<br>(86 %)   |
| 1.3 W     |          | 1.85 W<br>(70.3 %)  | 1.82 W<br>( 71.4 %) |
| 0.5 W     |          | 0.82 W<br>(61 %)    | 0.78 W<br>(64.1 %)  |
| No load   |          | 122 mW              | 210 mW              |

**No-load standby power meets ENERGY STAR® with a start-up resistor!**

---

# Agenda

- New ENERGY STAR<sup>®</sup> requirements
- Needed features to meet the new specification
- New controllers
- Practical examples
- Conclusion



## Adapters < 75 W: Conclusion

- Meeting the most recent requirements from ENERGY STAR® or IEC is possible with the classical **Flyback** converter
- Two new controllers sharing the same concept of frequency foldback at light load make it possible:
  - Fixed-frequency: **NCP1238** family
  - Valley-switching (Quasi-resonant, QR): **NCP1380** family
- Average efficiencies above **87%** are possible
- No-load input power below **300 mW** is possible, even with a **start-up resistor**
- No-load input power below **100 mW** is achievable, although the controller alone cannot ensure this. The whole power supply must be designed to reduce power waste.

---

## For More Information

- View the extensive portfolio of power management products from ON Semiconductor at [www.onsemi.com](http://www.onsemi.com)
- View reference designs, design notes, and other material supporting the design of highly efficient power supplies at [www.onsemi.com/powersupplies](http://www.onsemi.com/powersupplies)

