



**ON Semiconductor®**

# The TL431 in the Control of Switching Power Supplies

---

# Agenda

- ❑ Feedback generalities
- ❑ The TL431 in a compensator
- ❑ Small-signal analysis of the return chain
- ❑ A type 1 implementation with the TL431
- ❑ A type 2 implementation with the TL431
- ❑ A type 3 implementation with the TL431
- ❑ Design examples
- ❑ Conclusion


---

# Agenda

- ❑ **Feedback generalities**
- ❑ The TL431 in a compensator
- ❑ Small-signal analysis of the return chain
- ❑ A type 1 implementation with the TL431
- ❑ A type 2 implementation with the TL431
- ❑ A type 3 implementation with the TL431
- ❑ Design examples
- ❑ Conclusion



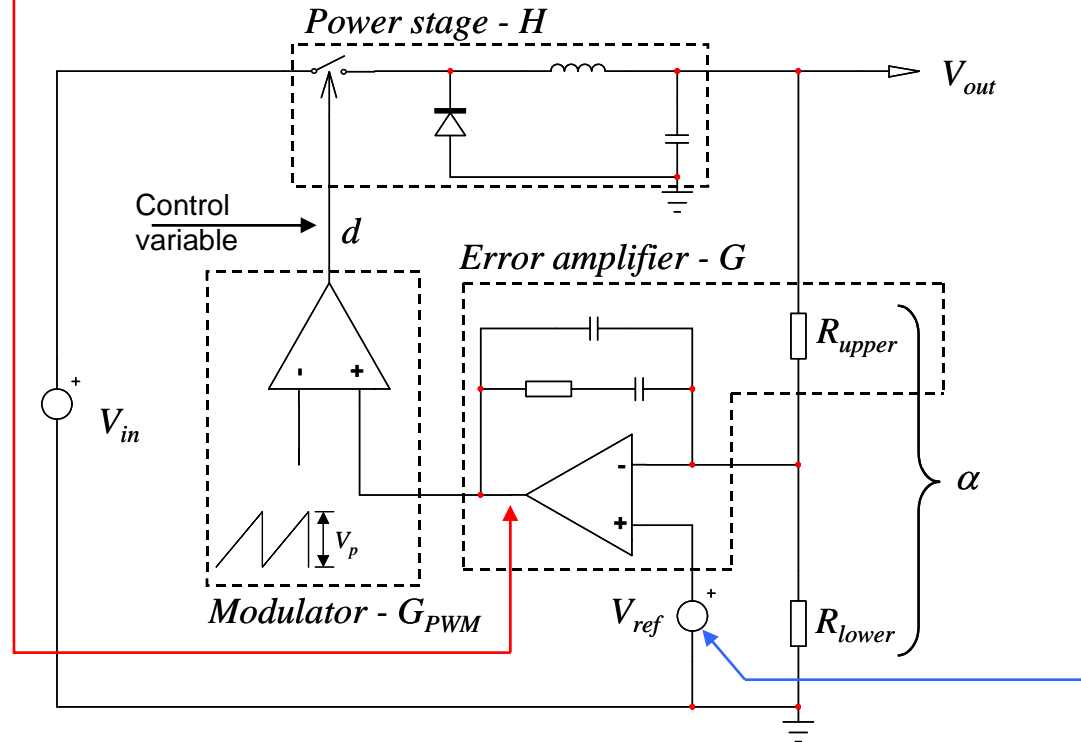
# What is a Regulated Power Supply?

- ❑  $V_{out}$  is permanently compared to a reference voltage  $V_{ref}$ .
- ❑ The reference voltage  $V_{ref}$  is precise and stable over temperature.
- ❑ The error,  $\varepsilon = V_{ref} - \alpha V_{out}$ , is amplified and sent to the control input.
- ❑ The power stage reacts to reduce  $\varepsilon$  as much as it can.


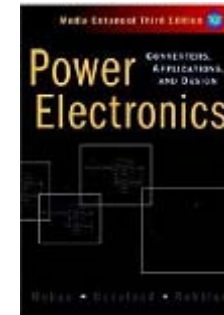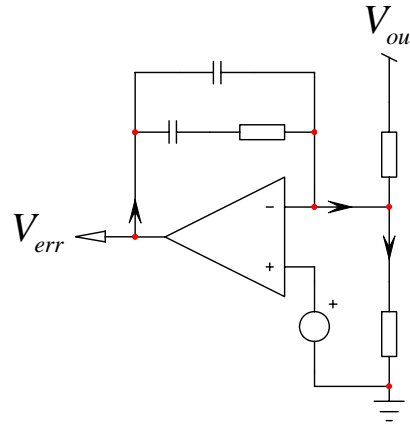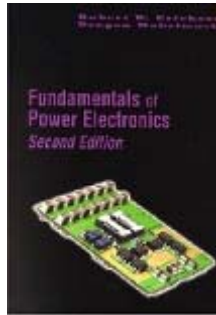
# How is Regulation Performed?

- ❑ Text books only describe op amps in compensators...



- ❑ The market reality is different: the TL431 rules!



I'm the law!



TL431




optocoupler

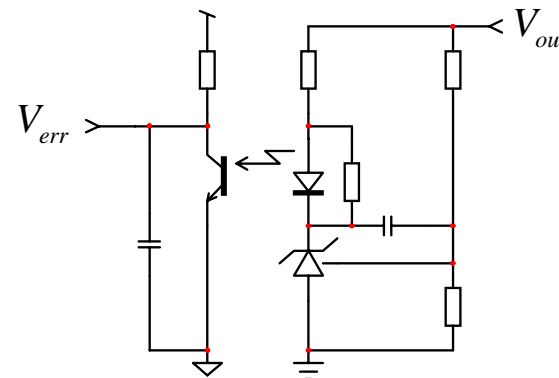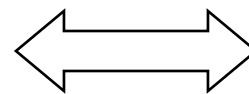


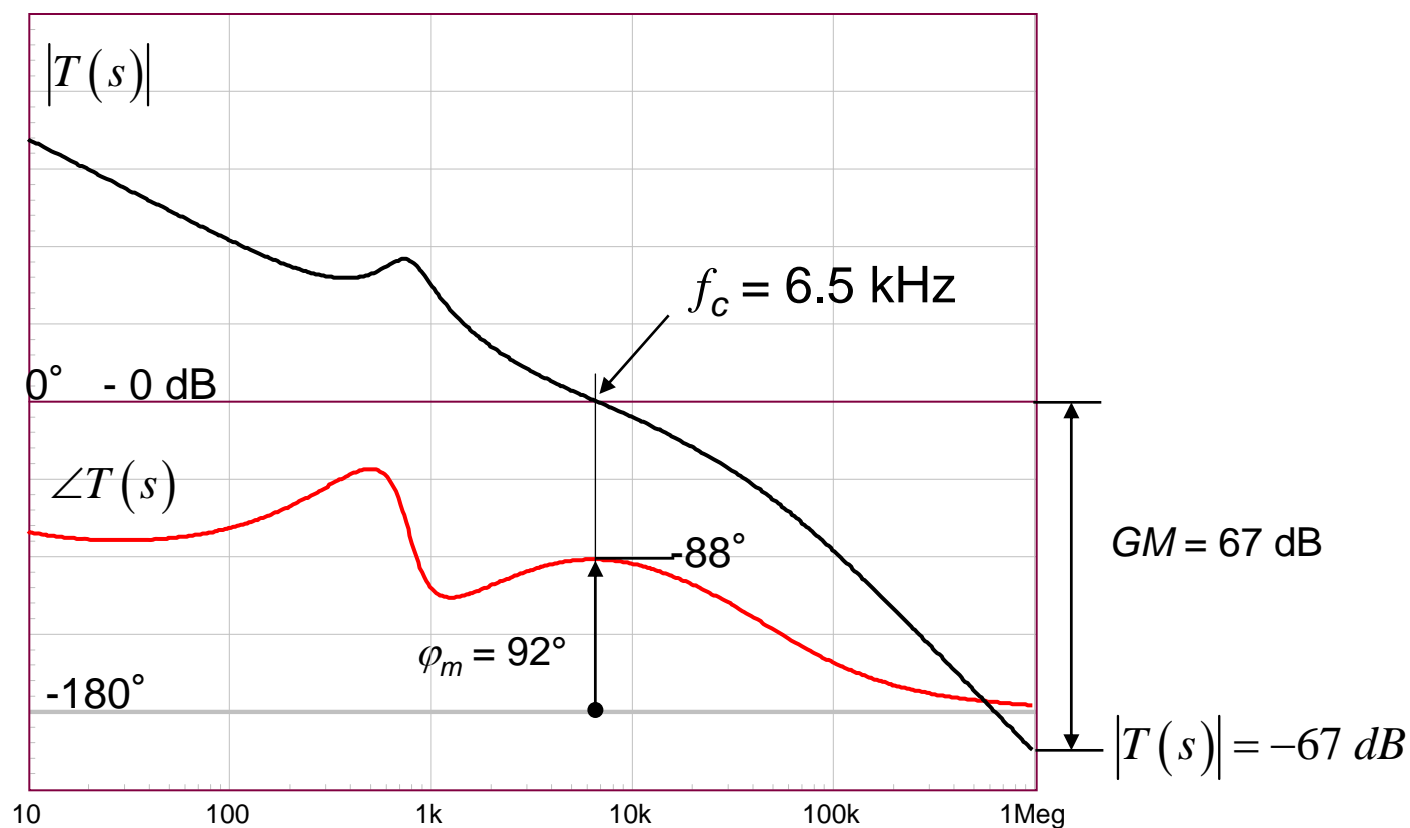
# How do we Stabilize a Converter?

- ❑ We need a high gain at dc for a low static error
- ❑ We want a sufficiently high crossover frequency for response speed
- Shape the compensator  $G(s)$  to build phase and gain margins!


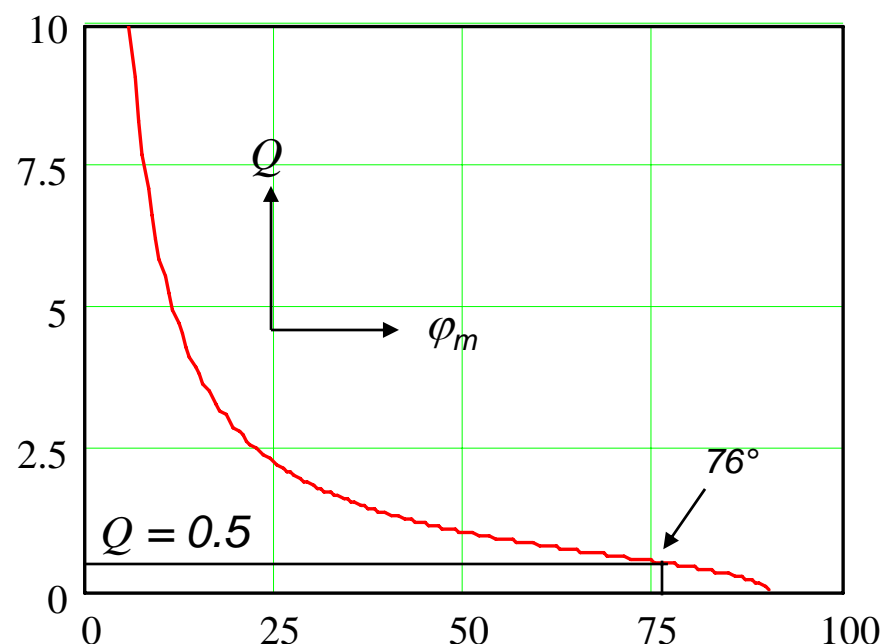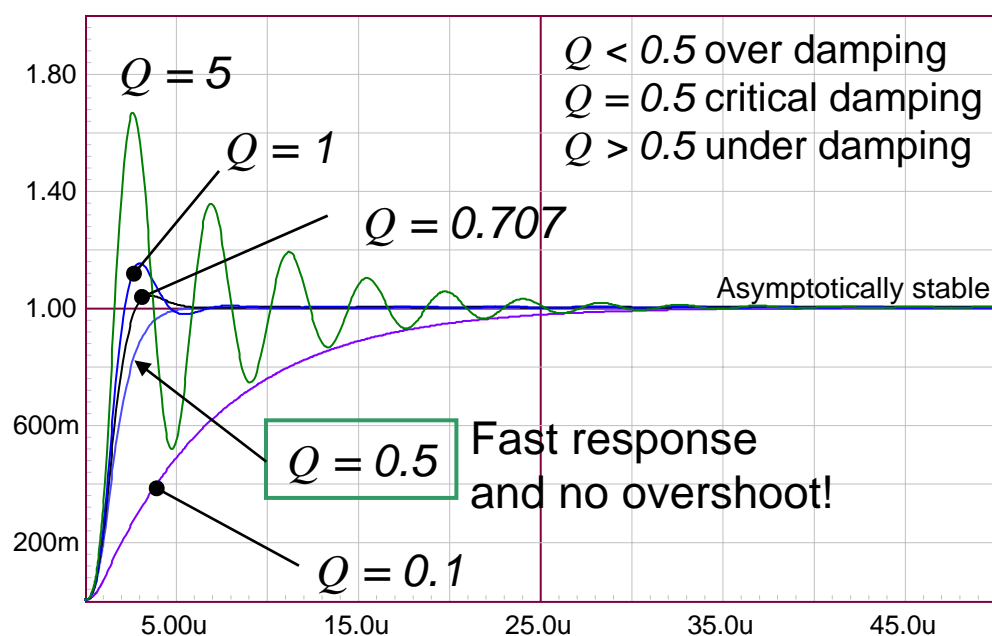
# How Much Phase Margin to Chose?


- ❑ a  $Q$  factor of 0.5 (critical response) implies a  $\varphi_m$  of  $76^\circ$
- ❑ a  $45^\circ$   $\varphi_m$  corresponds to a  $Q$  of 1.2: oscillatory response!



- ❑ phase margin depends on the needed response: fast, no overshoot...
- ❑ good practice is to shoot for  $60^\circ$  and make sure  $\varphi_m$  always  $> 45^\circ$
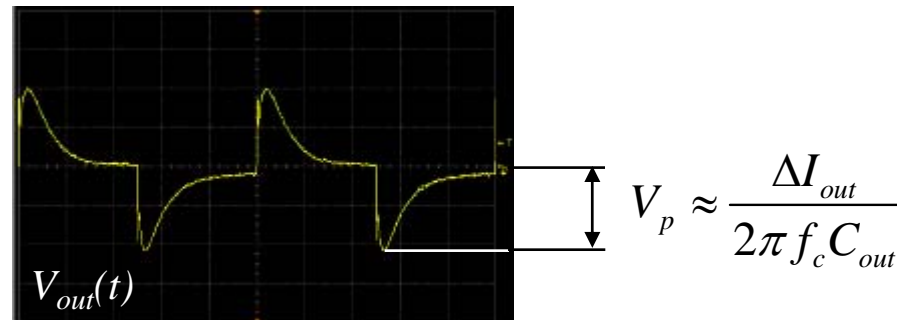
# Which Crossover Frequency to Select?

- crossover frequency selection depends on several factors:
  - *switching frequency*: theoretical limit is  $F_{sw}/2$ 
    - in practice, stay below 1/5 of  $F_{sw}$  for noise concerns
  - *output ripple*: if ripple pollutes feedback, «tail chasing» can occur.
    - crossover frequency rolloff is mandatory, e.g. in PFC circuits
  - *presence of a Right-Half Plane Zero (RHPZ)*:
    - you cannot cross over beyond 30% of the lowest RHPZ position
  - *output undershoot specification*:
    - select crossover frequency based on undershoot specs






# What Compensator Types do we Need?


- There are basically 3 compensator types:
  - type 1, 1 pole at the origin, no phase boost
  - type 2, 1 pole at the origin, 1 zero, 1 pole. Phase boost up to  $90^\circ$
  - type 3, 1 pole at the origin, 1 zero pair, 1 pole pair. Boost up to  $180^\circ$



Type 1

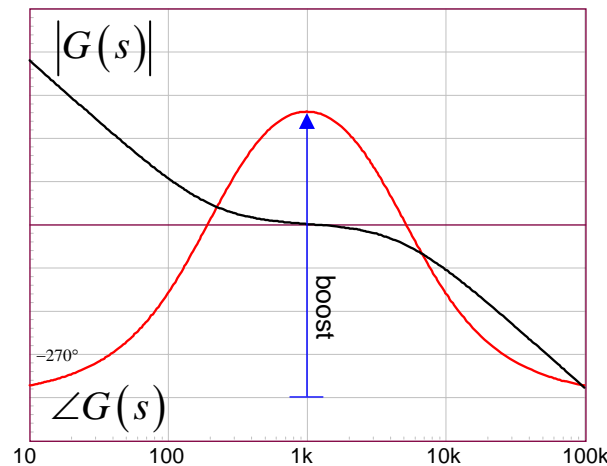

Type 2

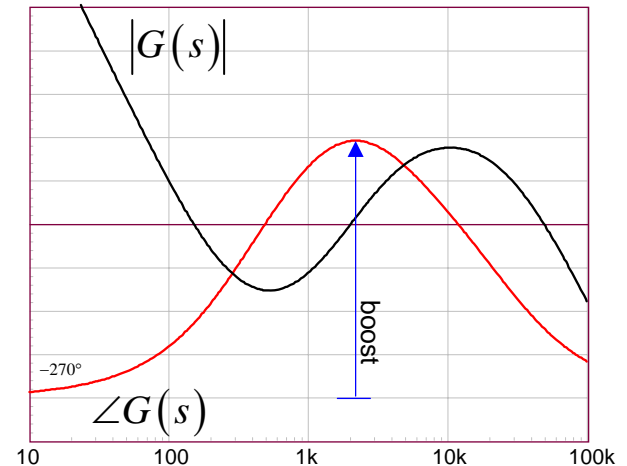

Type 3




---

# Agenda

- ❑ Feedback generalities
- ❑ **The TL431 in a compensator**
- ❑ Small-signal analysis of the return chain
- ❑ A type 1 implementation with the TL431
- ❑ A type 2 implementation with the TL431
- ❑ A type 3 implementation with the TL431
- ❑ Design examples
- ❑ Conclusion
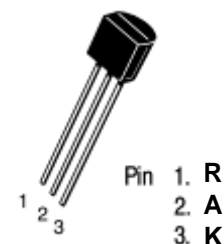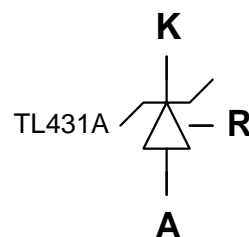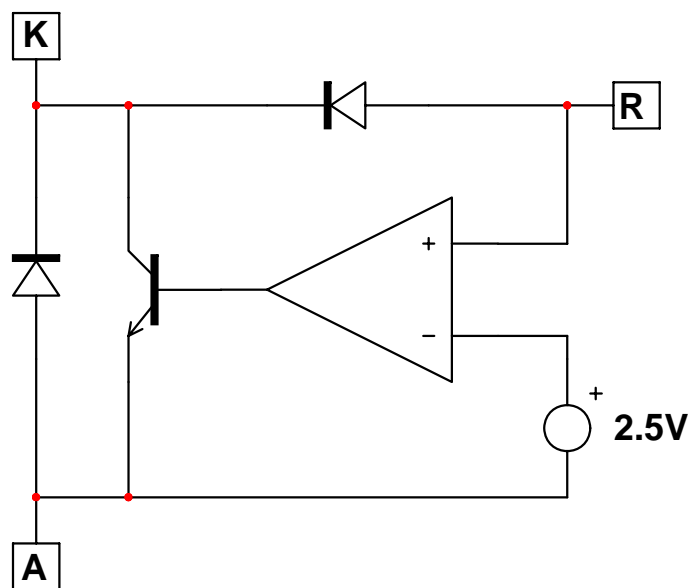
# The TL431 Programmable Zener



- ❑ The TL431 is the most popular choice in nowadays designs
- ❑ It associates an open-collector op amp and a reference voltage
- ❑ The internal circuitry is self-supplied from the cathode current
- ❑ When the R node exceeds 2.5 V, it sinks current from its cathode



- ❑ The TL431 is a shunt regulator
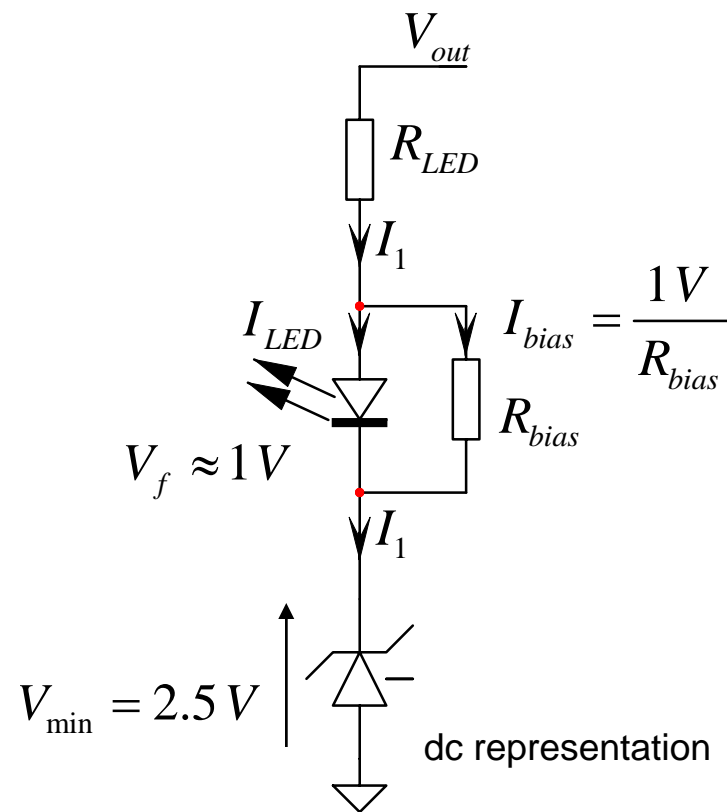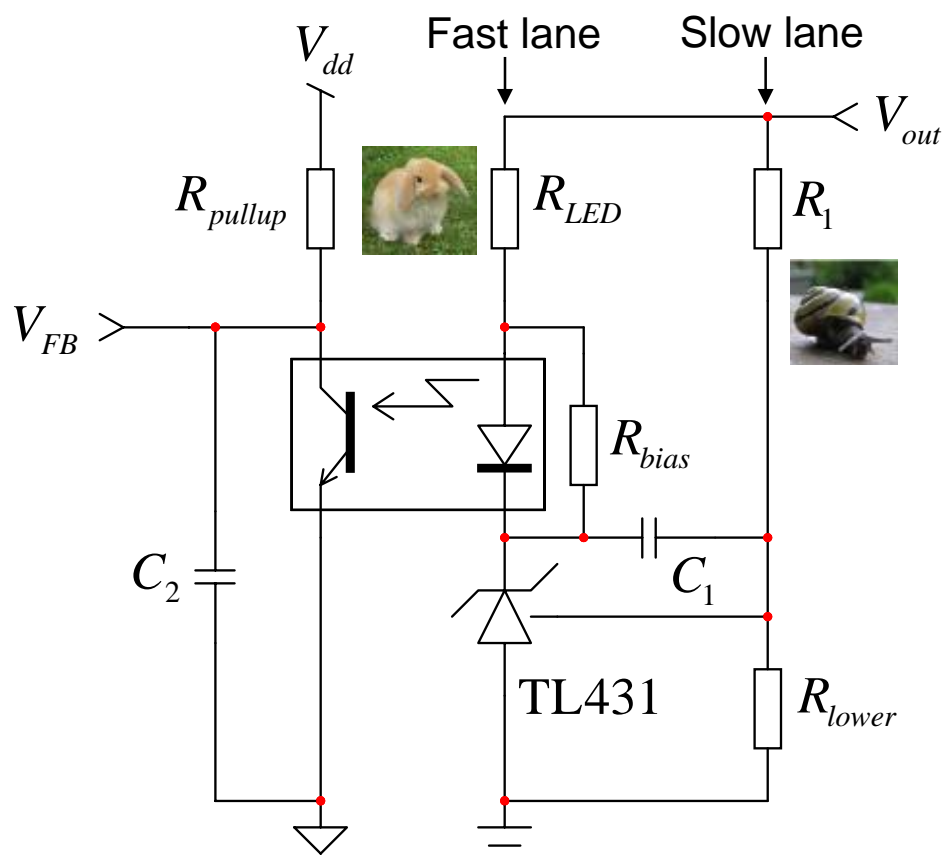
# The TL431 Programmable Zener

- The TL431 lends itself very well to optocoupler control




- $R_{LED}$  must leave enough headroom over the TL431: upper limit!

# The TL431 Programmable Zener

- This LED resistor is a design limiting factor in low output voltages:

$$R_{LED,max} \leq \frac{V_{out} - V_f - V_{TL431,min}}{V_{dd} - V_{CE,sat} + I_{bias} CTR_{min} R_{pullup}} R_{pullup} CTR_{min}$$

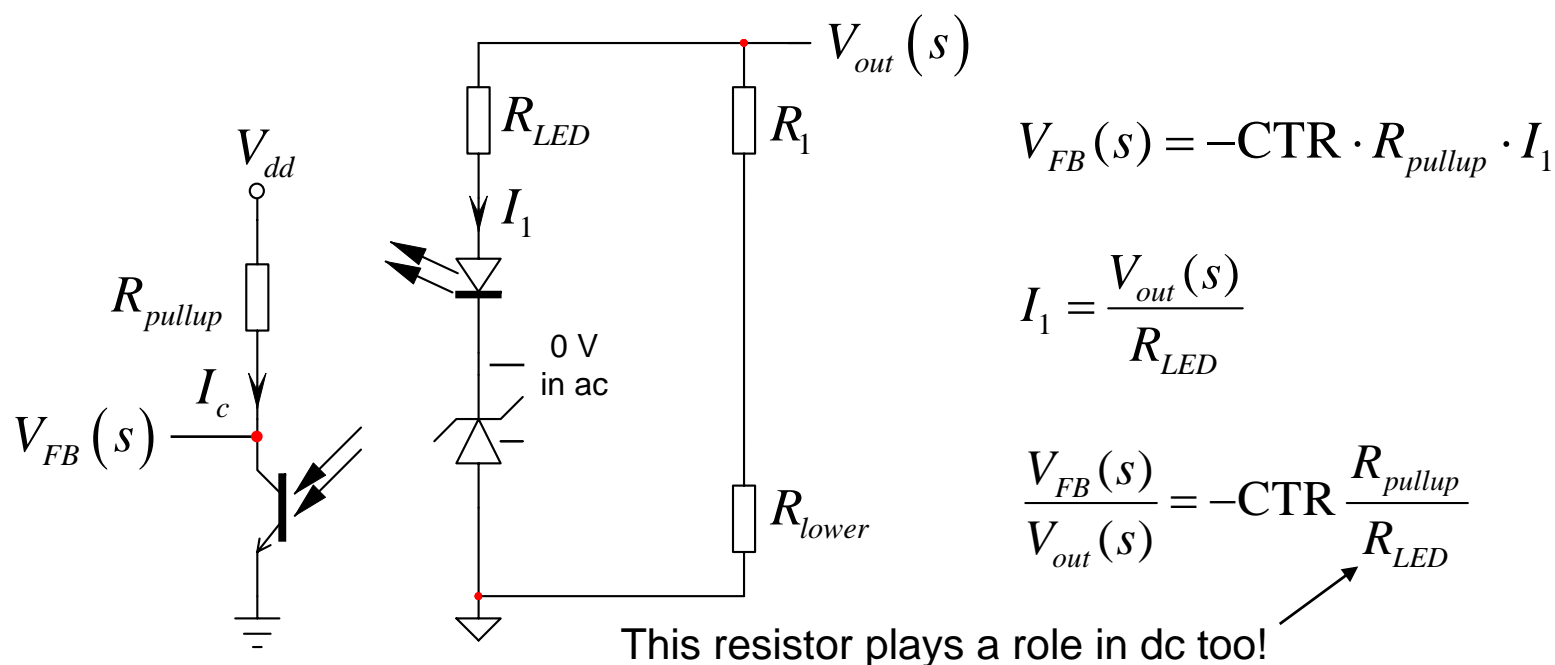- When the capacitor  $C_1$  is a short-circuit,  $R_{LED}$  fixes the fast lane gain



$$V_{FB}(s) = -CTR \cdot R_{pullup} \cdot I_1$$

$$I_1 = \frac{V_{out}(s)}{R_{LED}}$$

$$\frac{V_{FB}(s)}{V_{out}(s)} = -CTR \frac{R_{pullup}}{R_{LED}}$$

# The TL431 – the Static Gain Limit

- Let us assume the following design:

$$V_{out} = 5 V$$

$$V_f = 1 V$$

$$V_{TL431,min} = 2.5 V$$

$$V_{dd} = 4.8 V$$


$$V_{CE,sat} = 300 mV$$

$$I_{bias} = 1 mA$$


$$CTR_{min} = 0.3$$

$$R_{pullup} = 20 k\Omega$$
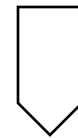
$$R_{LED,max} \leq \frac{5 - 1 - 2.5}{4.8 - 0.3 + 1m \times 0.3 \times 20k} \times 20k \times 0.3$$



$$R_{LED,max} \leq 857 \Omega$$

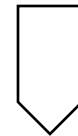


$$G_0 > CTR \frac{R_{pullup}}{R_{LED}} > 0.3 \frac{20}{0.857} > 7 \text{ or } \approx 17 \text{ dB}$$

- In designs where  $R_{LED}$  fixes the gain,  $G_0$  cannot be below 17 dB

⇒ You cannot “amplify” by less than 17 dB


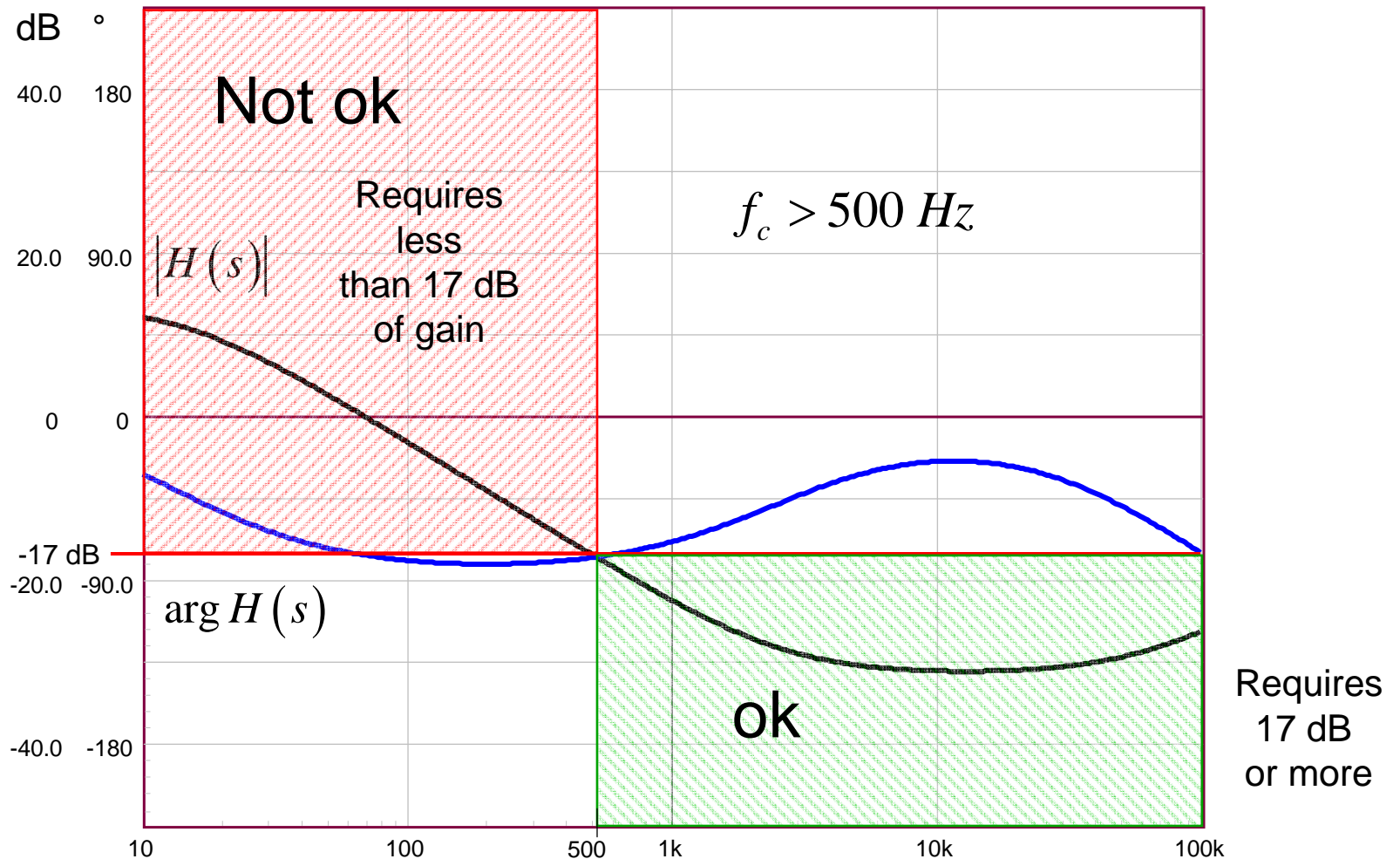
# The TL431 – the Static Gain Limit

- ❑ You must identify the areas where compensation is possible


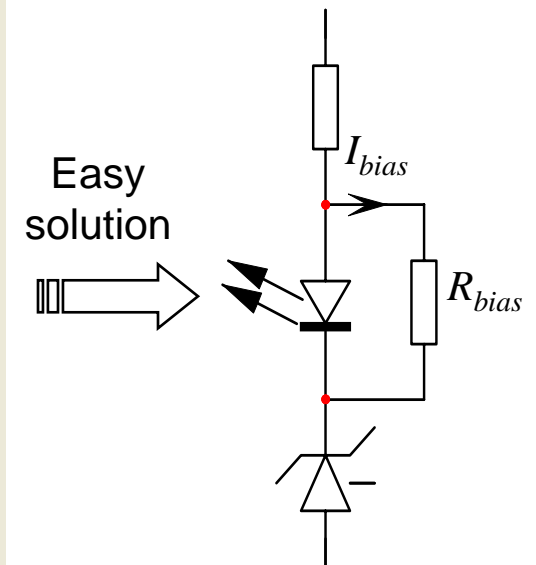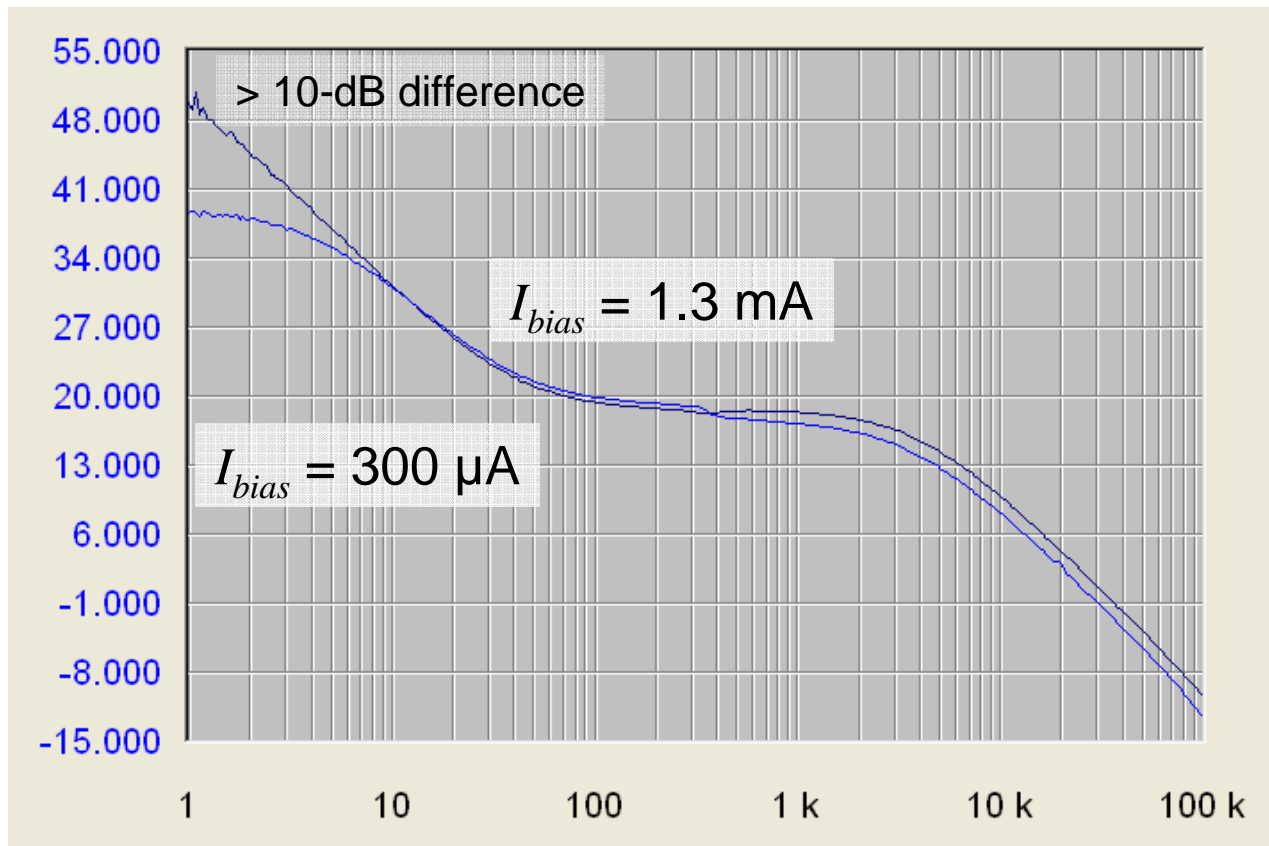
# TL431 – Injecting Bias Current

- ❑ A TL431 must be biased above 1 mA to guaranty its parameters
- ❑ If not, its open-loop suffers – a 10-dB difference can be observed!



$$R_{bias} = \frac{1}{1m} = 1 \text{ k}\Omega$$




---

# Agenda

- ❑ Feedback generalities
- ❑ The TL431 in a compensator
- ❑ **Small-signal analysis of the return chain**
- ❑ A type 1 implementation with the TL431
- ❑ A type 2 implementation with the TL431
- ❑ A type 3 implementation with the TL431
- ❑ Design examples
- ❑ Conclusion
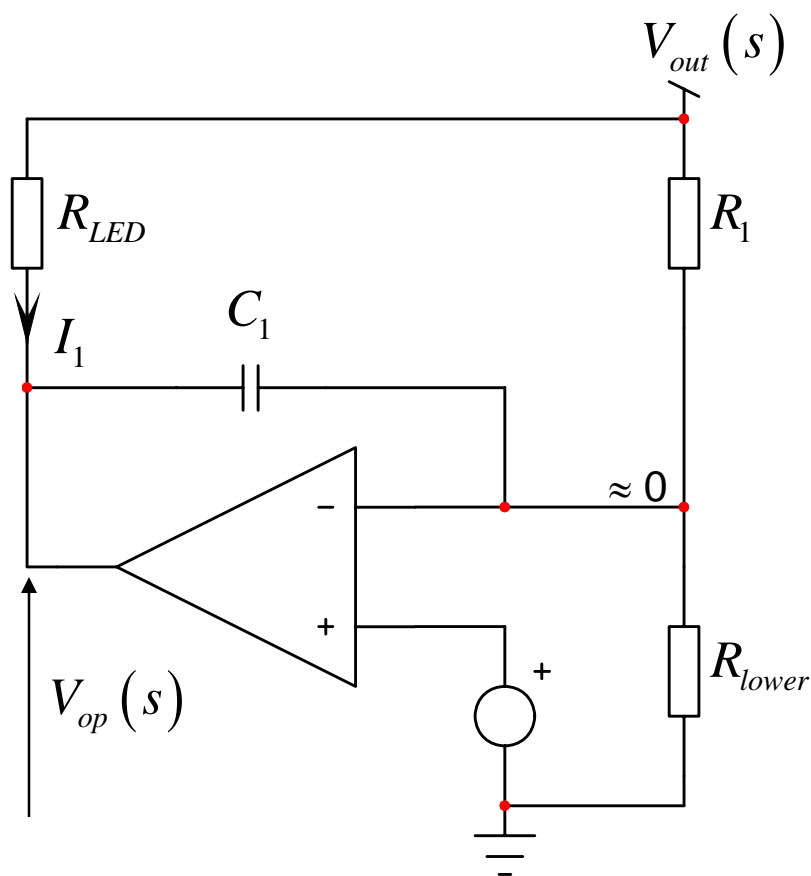
# TL431 – Small-Signal Analysis

- ❑ The TL431 is an open-collector op amp with a reference voltage
- ❑ Neglecting the LED dynamic resistance, we have:



$$I_1(s) = \frac{V_{out}(s) - V_{op}(s)}{R_{LED}} \cdot \frac{1}{sC_1}$$

$$V_{op}(s) = -V_{out}(s) \frac{sC_1}{R_{upper}} = -V_{out}(s) \frac{1}{sR_{upper}C_1}$$

$$I_1(s) = V_{out}(s) \frac{1}{R_{LED}} \left[ 1 + \frac{1}{sR_{upper}C_1} \right]$$

We know that:  $V_{FB}(s) = -CTR \cdot R_{pullup} \cdot I_1$

$$\frac{V_{FB}(s)}{V_{out}(s)} = -\frac{R_{pullup} CTR}{R_{LED}} \left[ \frac{1 + sR_{upper}C_1}{sR_{upper}C_1} \right]$$

# TL431 – Small-Signal Analysis


□ In the previous equation we have:

✓ a static gain  $G_0 = \text{CTR} \frac{R_{pullup}}{R_{LED}}$

✓ a 0-dB origin pole frequency  $\omega_{po} = \frac{1}{C_1 R_{upper}}$


✓ a zero  $\omega_{z1} = \frac{1}{R_{upper} C_1}$

□ We are missing a pole for the type 2!

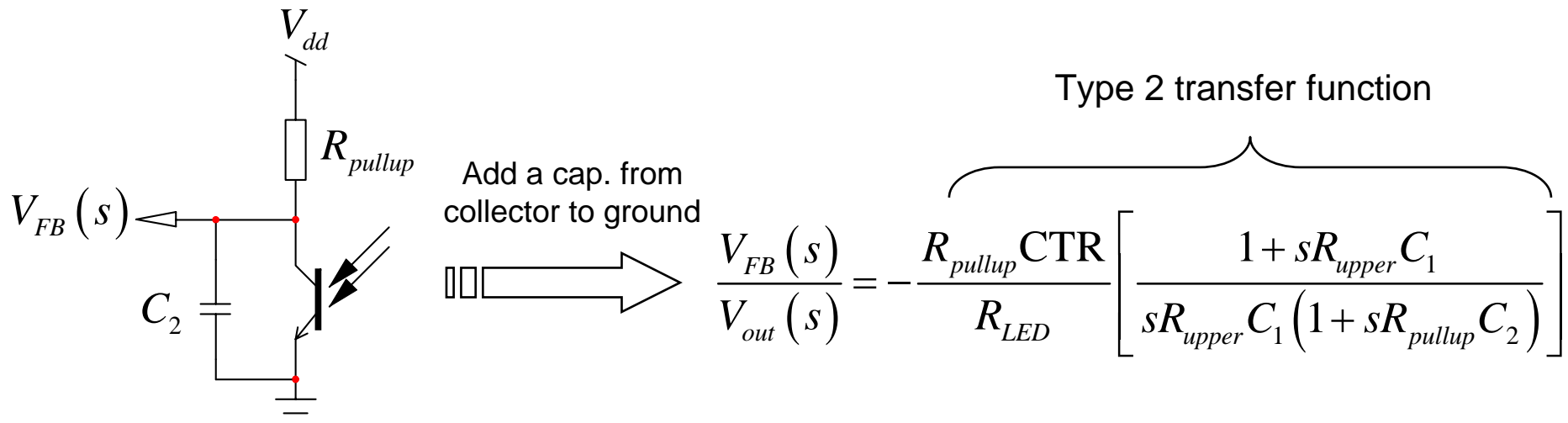


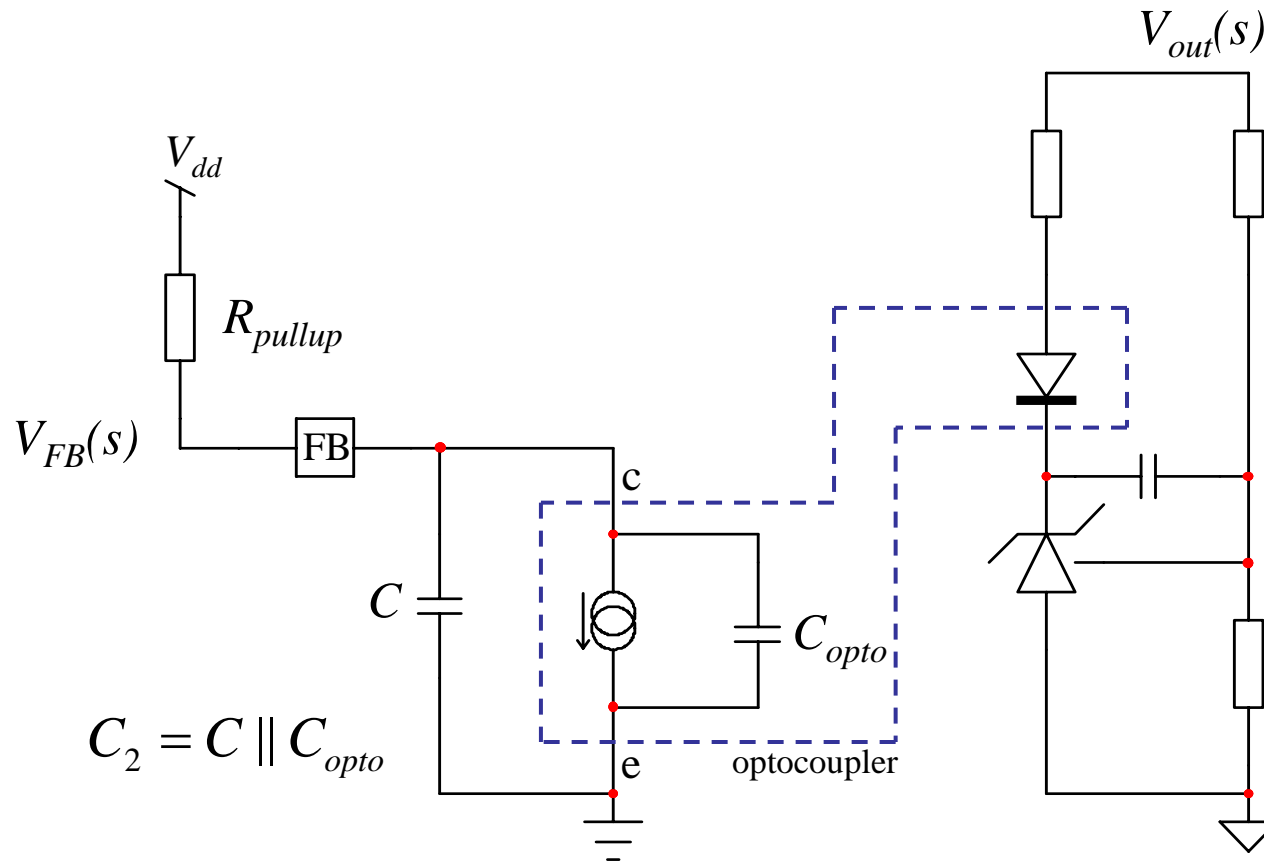
# TL431 – Small-Signal Analysis

- ❑ The optocoupler also features a parasitic capacitor
- it comes in parallel with  $C_2$  and must be accounted for


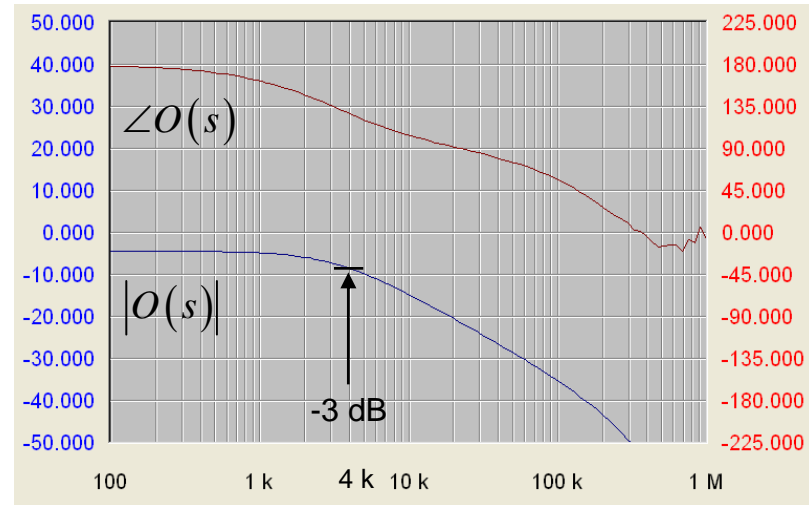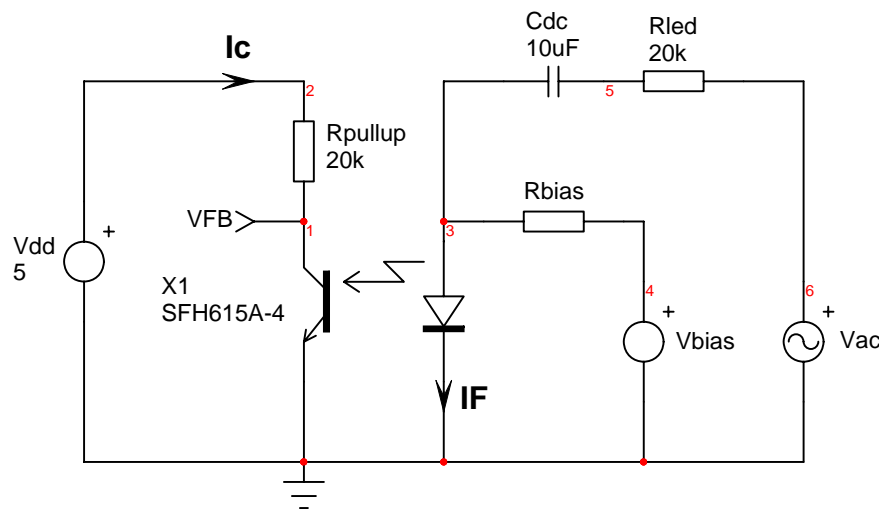
# TL431 – Small-Signal Analysis

- ❑ The optocoupler must be characterized to know where its pole is



- ❑ Adjust  $V_{bias}$  to have  $V_{FB}$  at 2-3 V to be in linear region, then ac sweep
- ❑ The pole in this example is found at 4 kHz

$$C_{opto} = \frac{1}{2\pi R_{pullup} f_{pole}} = \frac{1}{6.28 \times 20k \times 4k} \approx 2 \text{ nF}$$

Another design constraint!

---

# Agenda

- ❑ Feedback generalities
- ❑ The TL431 in a compensator
- ❑ Small-signal analysis of the return chain
- ❑ **A type 1 implementation with the TL431**
- ❑ A type 2 implementation with the TL431
- ❑ A type 3 implementation with the TL431
- ❑ Design examples
- ❑ Conclusion

# The TL431 in a Type 1 Compensator

- To make a type 1 (origin pole only) neutralize the zero and the pole

$$\frac{V_{FB}(s)}{V_{out}(s)} = -\frac{R_{pullup} CTR}{R_{LED}} \left[ \frac{1 + sR_{upper} C_1}{sR_{upper} C_1 (1 + sR_{pullup} C_2)} \right]$$

$$sR_{upper} C_1 = sR_{pullup} C_2 \implies C_1 = \frac{R_{pullup}}{R_{upper}} C_2 \quad \text{substitute} \quad \omega_{po} = \frac{1}{\frac{R_{upper} R_{LED}}{R_{pullup} CTR} C_1}$$

$$\omega_{po} = \frac{CTR}{C_2 R_{LED}} \implies C_2 = \frac{CTR}{2\pi f_{po} R_{LED}}$$

- Once neutralized, you are left with an integrator

$$G(s) = \frac{1}{s} \xrightarrow{\omega_{po}} |G(f_c)| = \frac{f_{po}}{f_c} \rightarrow f_{po} = G_{f_c} f_c \implies C_2 = \frac{CTR}{2\pi G_{f_c} f_c R_{LED}}$$

# TL431 Type 1 Design Example

□ We want a 5-dB gain at 5 kHz to stabilize the 5-V converter

$$\begin{aligned}
 V_{out} &= 5\text{ V} \\
 V_f &= 1\text{ V} \\
 V_{TL431, \min} &= 2.5\text{ V} \\
 V_{dd} &= 4.8\text{ V} \\
 V_{CE, \text{sat}} &= 300\text{ mV} \\
 I_{bias} &= 1\text{ mA} \\
 \text{CTR}_{\min} &= 0.3 \\
 R_{pullup} &= 20\text{ k}\Omega
 \end{aligned}$$

$$R_{LED, \max} \leq 857\ \Omega \xrightarrow{\text{Apply 15\% margin}} R_{LED} = 728\ \Omega$$

$$\begin{aligned}
 G_{fc} &= 10^{\frac{5}{20}} = 1.77 \\
 f_c &= 10\text{ kHz}
 \end{aligned}
 \quad \left. \vphantom{\begin{aligned} G_{fc} \\ f_c \end{aligned}} \right\} C_2 = \frac{\text{CTR}}{2\pi G_{fc} f_c R_{LED}} = \frac{0.3}{6.28 \times 1.77 \times 5k \times 728} \approx 7.4\text{ nF}$$

$$\begin{aligned}
 C_{opto} &= 2\text{ nF} \\
 \Rightarrow C &= 7.4\text{ n} - 2\text{ n} = 5.4\text{ nF} \quad C_1 = \frac{R_{pullup}}{R_{upper}} C_2 \approx 14.7\text{ nF}
 \end{aligned}$$



# TL431 Type 1 Design Example

❑ SPICE can simulate the design – automate elements calculations...

parameters

$V_{out}=5$

$V_f=1$

$V_{ref}=2.5$

$V_{CEsat}=300m$

$V_{dd}=4.8$

$I_{bias}=1m$

$A=V_{out}-V_f-V_{ref}$

$B=V_{dd}-V_{CEsat}+I_{bias}*CTR*R_{pullup}$

$R_{max}=(A/B)*R_{pullup}*CTR$

$R_{upper}=(V_{out}-2.5)/250u$

$f_c=5k$

$G_{fc}=-5$

$G=10^{(-G_{fc}/20)}$

$\pi=3.14159$

$F_{po}=G*f_c$

$R_{pullup}=20k$

$R_{LED}=R_{max}*0.85$

$C_1=C_{pole1}*R_{pullup}/R_{upper}$


$C_{pole1}=CTR/(2*\pi*F_{po}*R_{LED})$

$C_{pole}=C_{pole1}-C_{opto}$

$F_{opto}=4k$

$C_{opto}=1/(2*\pi*F_{opto}*R_{pullup})$

$CTR = 0.3$

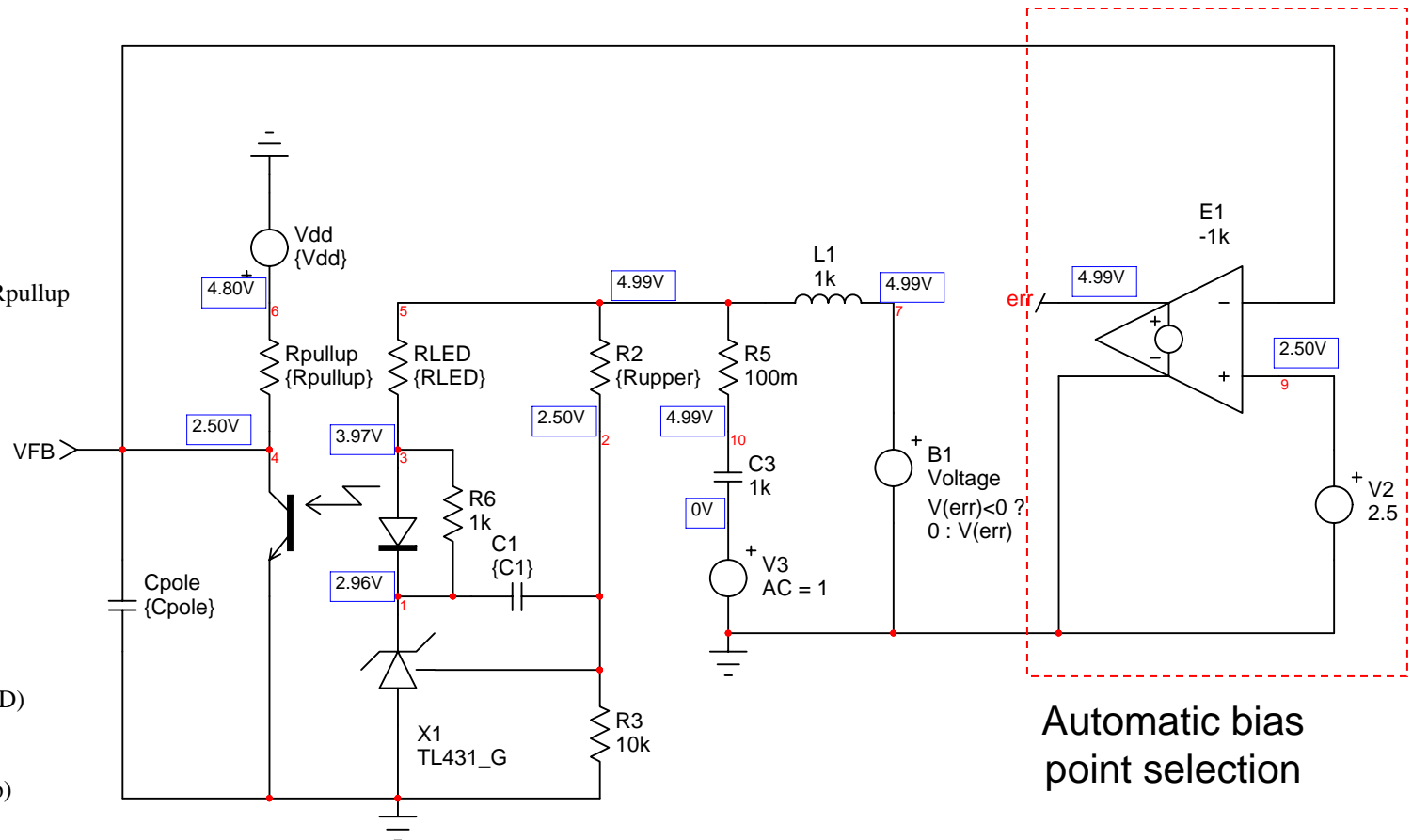


# TL431 Type 1 Design Example

- We have a type 1 but 1.3 dB of gain is missing? 🤔 Hu?


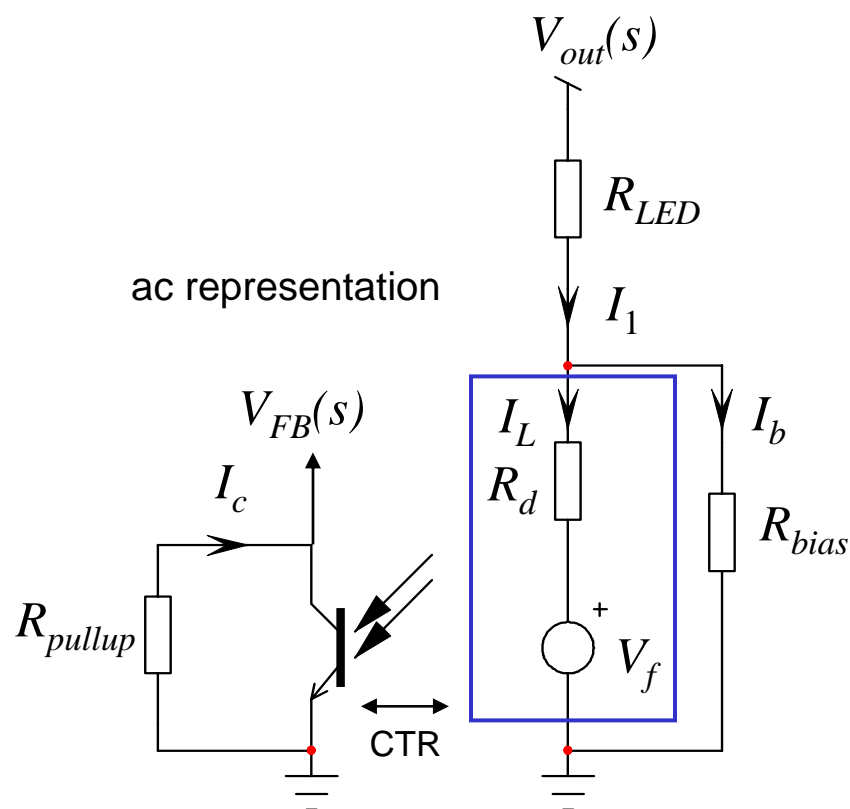
# TL431 Type 1 Design Example

- ❑ The 1-kΩ resistor in parallel with the LED is an easy bias
- ❑ However, as it appears in the loop, does it affect the gain?



$$V_{FB} = I_c R_{pullup} = I_L R_{pullup} \text{CTR}$$

$$I_L = I_1 \frac{R_{bias}}{R_{bias} + R_d}$$

$$I_L = \frac{V_{out}}{R_{LED} + R_{bias} \parallel R_d} \frac{R_{bias}}{R_{bias} + R_d}$$


$$\frac{V_{FB}}{V_{out}} \Big|_{s=0} = \frac{R_{pullup} \text{CTR}}{R_{LED} + R_{bias} \parallel R_d} \frac{R_{bias}}{R_{bias} + R_d}$$

- ❑ Both bias and dynamic resistances have a role in the gain expression

# TL431 Type 1 Design Example

- ❑ A low operating current increases the dynamic resistor

SFH615A-2 - FORWARD CHARACTERISTICS

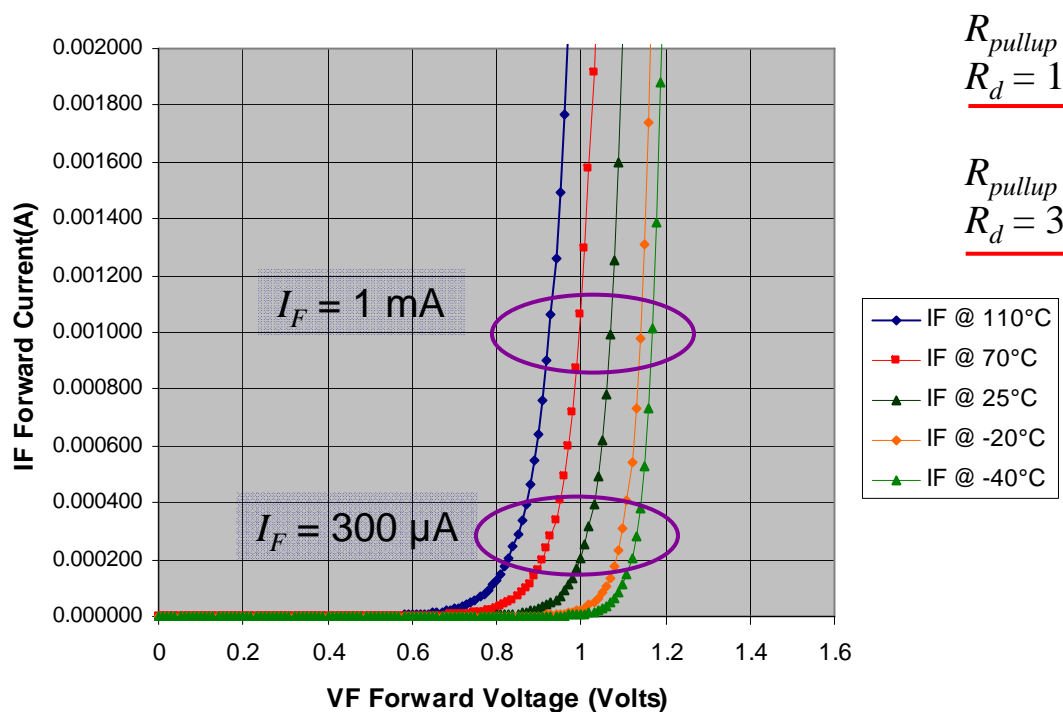


$$R_{pullup} = 20 \text{ k}\Omega, I_F = 300 \text{ } \mu\text{A} \text{ (CTR} = 0.3)$$
$$\underline{R_d = 158 \text{ } \Omega}$$

$$R_{pullup} = 1 \text{ k}\Omega, I_F = 1 \text{ mA} \text{ (CTR} = 1)$$
$$\underline{R_d = 38 \text{ } \Omega}$$

- ❑ Make sure you have enough LED current to reduce its resistance
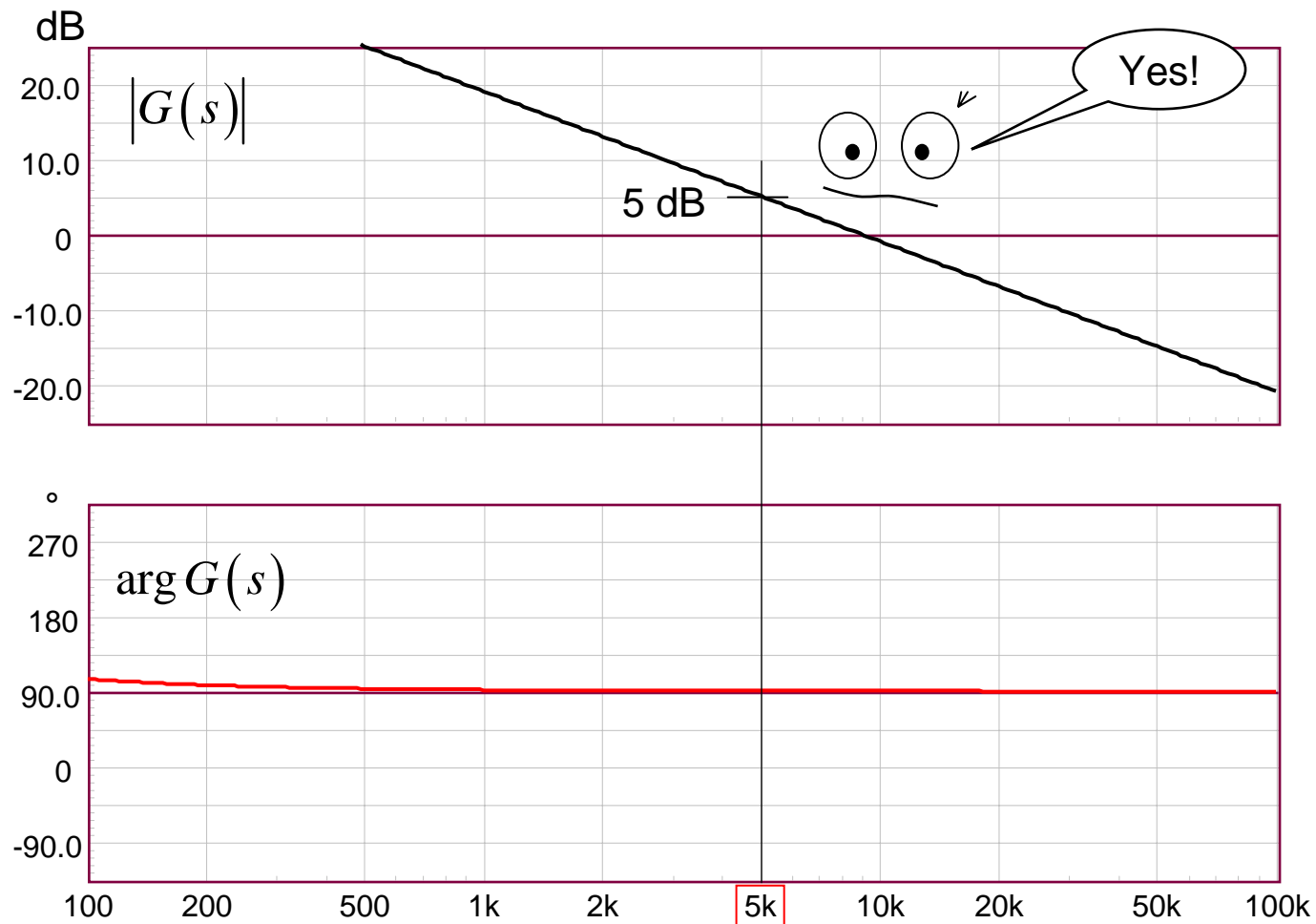
# TL431 Type 1 Design Example

- The pullup resistor is 1 k $\Omega$  and the target now reaches 5 dB




---

# Agenda

- ❑ Feedback generalities
- ❑ The TL431 in a compensator
- ❑ Small-signal analysis of the return chain
- ❑ A type 1 implementation with the TL431
- ❑ **A type 2 implementation with the TL431**
- ❑ A type 3 implementation with the TL431
- ❑ Design examples
- ❑ Conclusion
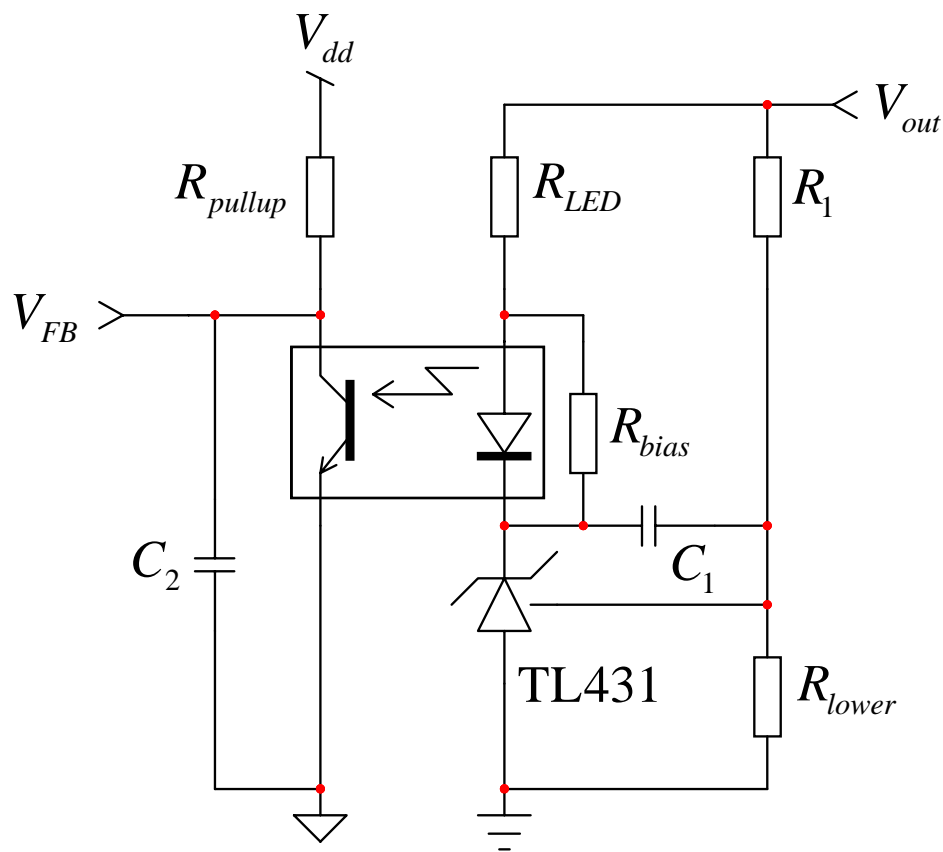
# The TL431 in a Type 2 Compensator

- Our first equation was already a type 2 definition, we are all set!



$$G_0 = \text{CTR} \frac{R_{\text{pullup}}}{R_{\text{LED}}}$$

$$\omega_{z_1} = \frac{1}{R_{\text{upper}} C_1}$$

$$\omega_{p_1} = \frac{1}{R_{\text{pullup}} C_2}$$

- Just make sure the optocoupler contribution is involved...

## TL431 Type 2 Design Example

- You need to provide a 15-dB gain at 5 kHz with a 50° boost

$$f_p = \left[ \tan(\text{boost}) + \sqrt{\tan^2(\text{boost}) + 1} \right] f_c = 2.74 \times 5k = 13.7 \text{ kHz}$$

$$f_z = f_c^2 / f_p = 25k / 13.7k \approx 1.8 \text{ kHz} \quad G_0 = \text{CTR} \frac{R_{\text{pullup}}}{R_{\text{LED}}} = 10^{15/20} = 5.62$$

- With a 250-μA bridge current, the divider resistor is made of:

$$R_{\text{lower}} = 2.5 / 250\mu = 10 \text{ k}\Omega \quad R_1 = (12 - 2.5) / 250\mu = 38 \text{ k}\Omega$$

- The pole and zero respectively depend on  $R_{\text{pullup}}$  and  $R_1$ :

$$C_2 = 1 / 2\pi f_p R_{\text{pullup}} = 581 \text{ pF} \quad C_1 = 1 / 2\pi f_z R_1 = 2.3 \text{ nF}$$

- The LED resistor depends on the needed mid-band gain:

$$R_{\text{LED}} = \frac{R_{\text{pullup}} \text{CTR}}{G_0} = 1.06 \text{ k}\Omega \xrightarrow{\text{ok}} R_{\text{LED,max}} \leq 4.85 \text{ k}\Omega$$



## TL431 Type 2 Design Example

- The optocoupler is still at a 4-kHz frequency:

$$C_{pole} \approx 2 \text{ nF}$$

Already above!

- Type 2 pole capacitor calculation requires a 581 pF cap.!

 The bandwidth cannot be reached, reduce  $f_c$ !

- For noise purposes, we want a minimum of 100 pF for  $C$
- With a total capacitance of 2.1 nF, the highest pole can be:

$$f_{pole} = \frac{1}{2\pi R_{pullup} C} = \frac{1}{6.28 \times 20k \times 2.1n} = 3.8 \text{ kHz}$$

- For a 50° phase boost and a 3.8-kHz pole, the crossover must be:

$$f_c = \frac{f_p}{\tan(\text{boost}) + \sqrt{\tan^2(\text{boost}) + 1}} \approx 1.4 \text{ kHz}$$

## TL431 Type 2 Design Example

- The zero is then simply obtained:

$$f_z = \frac{f_c^2}{f_p} = 516 \text{ Hz}$$

- We can re-derive the component values and check they are ok

$$C_2 = 1/2\pi f_p R_{pullup} = 2.1 \text{ nF} \quad C_1 = 1/2\pi f_z R_1 = 8.1 \text{ nF}$$

- Given the 2-nF optocoupler capacitor, we just add 100 pF


- In this example,  $R_{LED,max}$  is 4.85 k $\Omega$

$$G_0 > \text{CTR} \frac{R_{pullup}}{R_{LED}} > 0.3 \frac{20}{4.85} > 1.2 \text{ or } \approx 1.8 \text{ dB}$$

- You cannot use this type 2 if an attenuation is required at  $f_c$ !

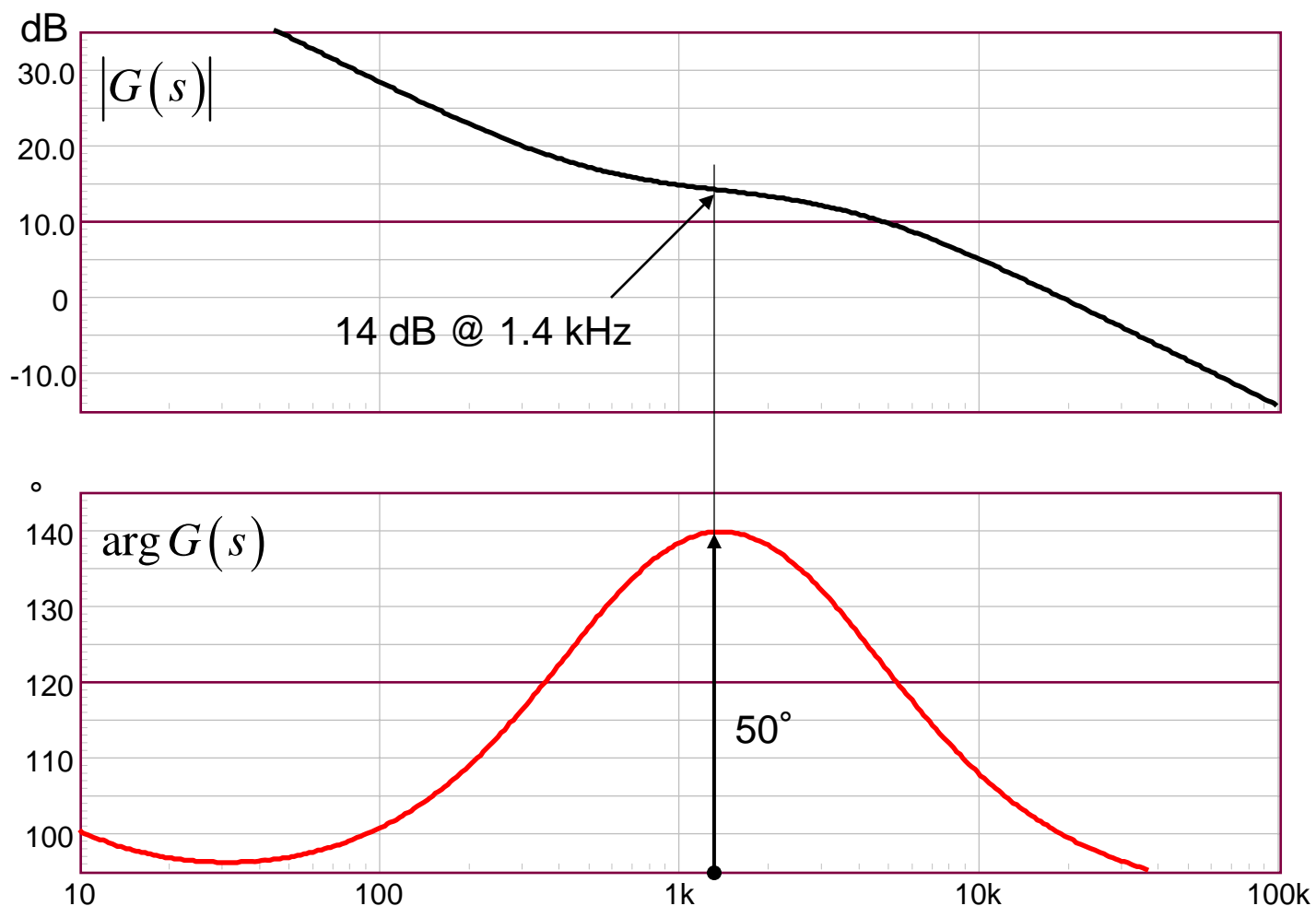
# TL431 Type 2 Design Example

- The 1-dB gain difference is linked to  $R_d$  and the bias current



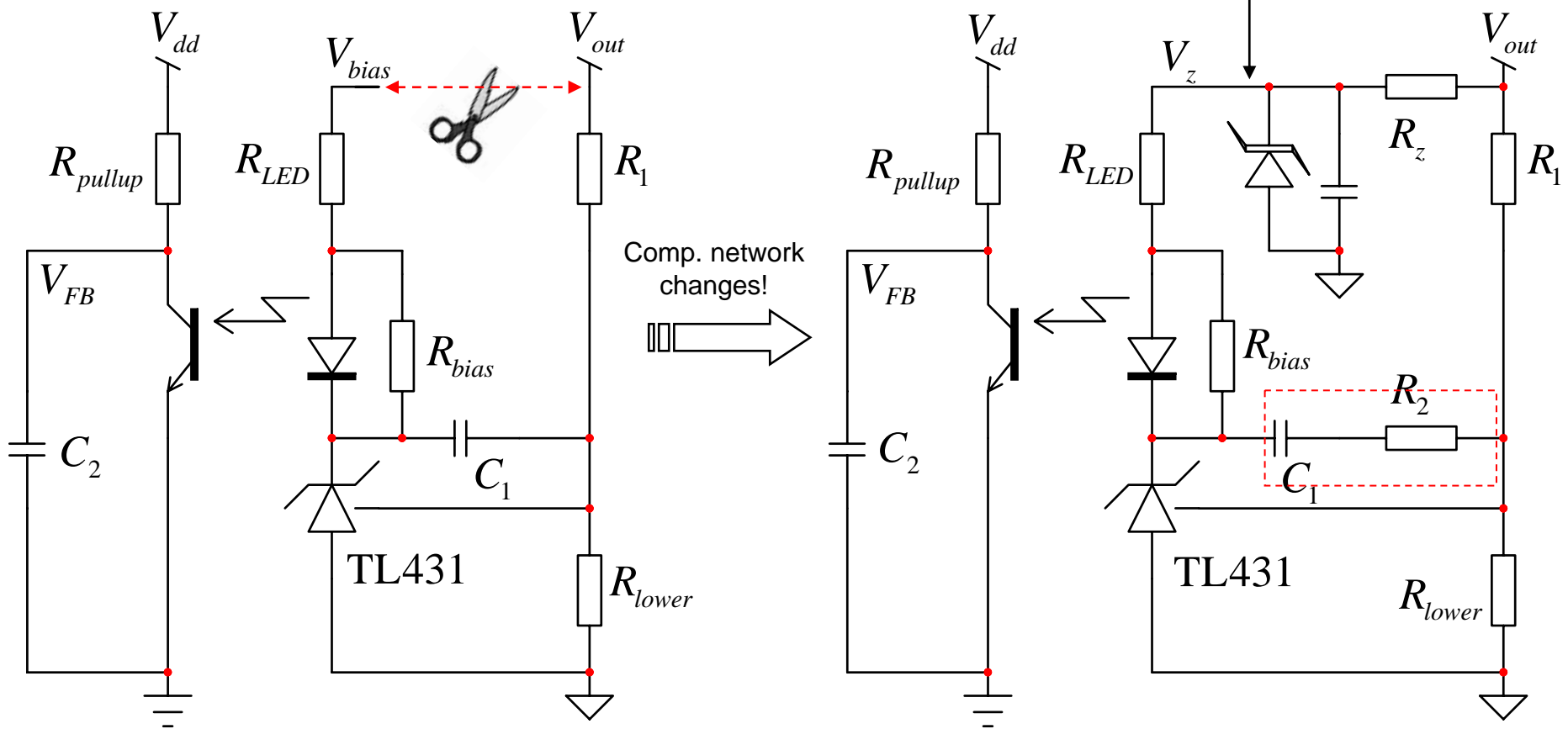
# TL431 – Suppressing the Fast Lane

- ❑ The gain limit problem comes from the fast lane presence
- ❑ Its connection to  $V_{out}$  creates a parallel input
- The solution is to hook the LED resistor to a fixed bias



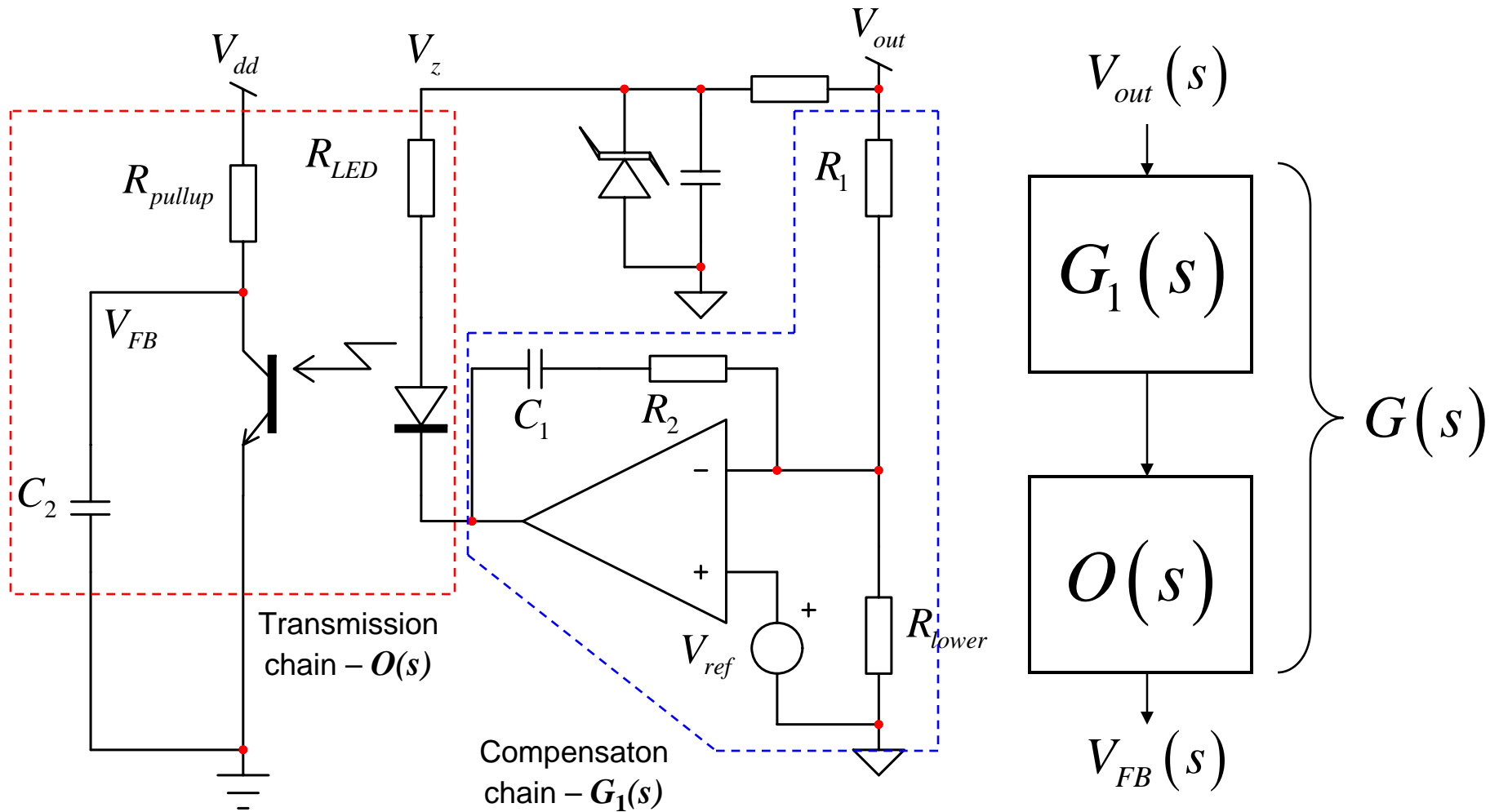
# TL431 – Suppressing the Fast Lane

- The equivalent schematic becomes an open-collector op amp


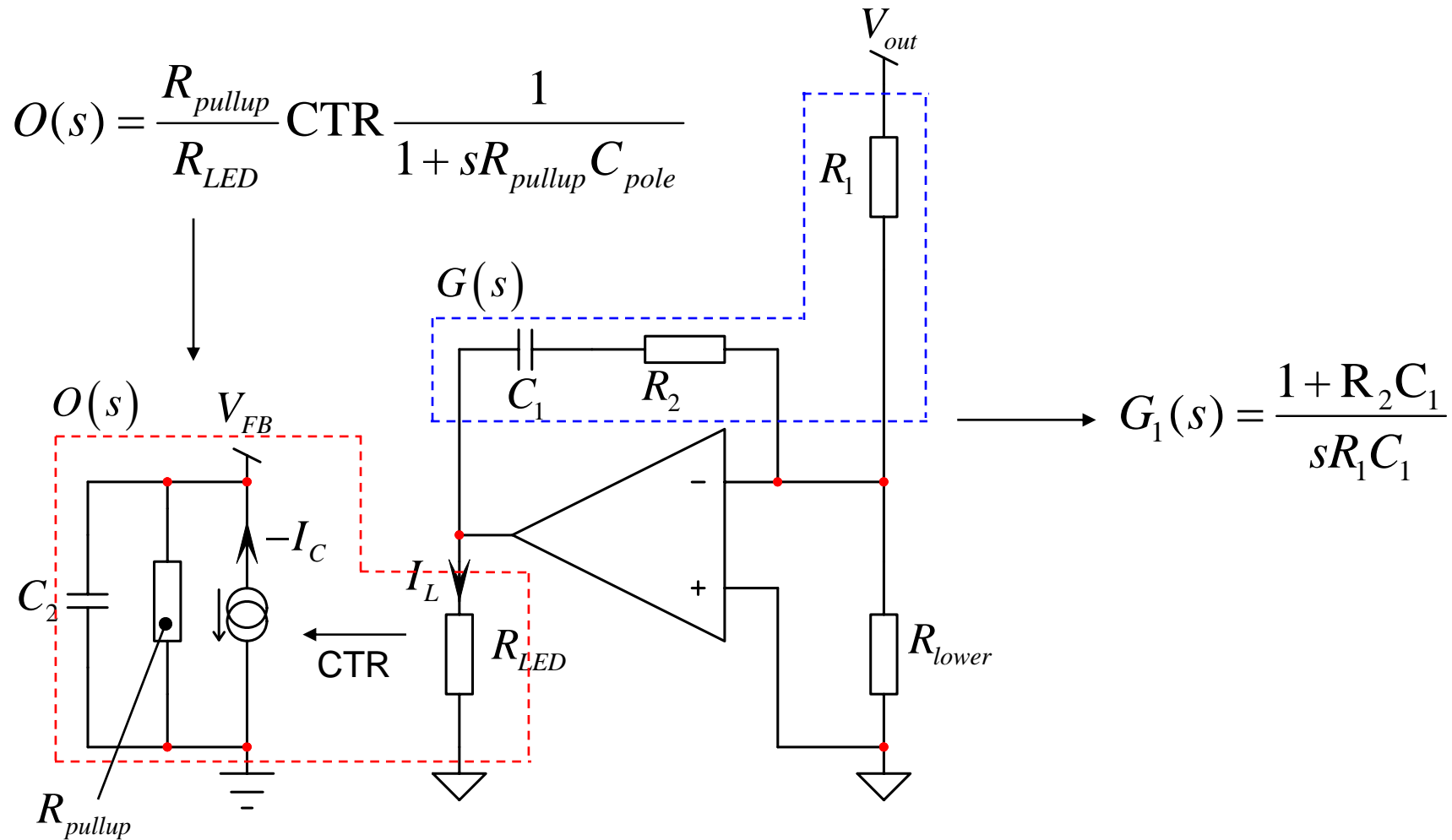
# TL431 – Suppressing the Fast Lane

- The small-signal ac representation puts all sources to 0



# TL431 – Suppressing the Fast Lane

- ❑ The op amp can now be wired in any configuration!
- ❑ Just keep in mind the optocoupler transmission chain

$$O(s) = \frac{R_{pullup}}{R_{LED}} \text{CTR} \frac{1}{1 + sR_{pullup}C_{pole}}$$

- ❑ Wire the op amp in type 2A version (no high frequency pole)

$$G_1(s) = \frac{1 + R_2C_1}{sR_1C_1}$$

- ❑ When cascaded, you obtain a type 2 with an extra gain term

$$G(s) = \frac{R_{pullup}}{R_{LED}} \text{CTR} \frac{1 + R_2C_1}{sR_1C_1 (1 + sR_{pullup}C_{pole})}$$

$G_2$

# TL431 Type 2 Design Example – No Fast Lane

- We still have a constraint on  $R_{LED}$  but only for dc bias purposes

$$R_{LED,max} \leq \frac{V_z - V_f - V_{TL431,min}}{V_{dd} - V_{CE,sat} + I_{bias} CTR_{min} R_{pullup}} R_{pullup} CTR_{min}$$

- You need to attenuate by -10-dB at 1.4 kHz with a 50° boost
- The poles and zero position are that of the previous design

$$V_z = 6.2 V$$

$$V_f = 1 V$$

$$V_{TL431,min} = 2.5 V$$

$$V_{dd} = 4.8 V$$

$$V_{CE,sat} = 300 mV$$

$$I_{bias} = 1 mA$$

$$CTR_{min} = 0.3$$

$$R_{pullup} = 20 k\Omega$$

$$R_{LED,max} \leq 1.5 k\Omega \xrightarrow{\text{Apply 15\% margin}} R_{LED} = 1.27 k\Omega$$

$$f_z = 516 Hz \quad f_p = 3.8 kHz$$



# TL431 Type 2 Design Example – No Fast Lane

- We need to account for the extra gain term:

$$G_2 = \frac{R_{pullup}}{R_{LED}} CTR = \frac{20k}{1.27k} 0.3 = 4.72$$

- The required total mid-band attenuation at 1.4 kHz is -10 dB

$$G_{f_c} = 10^{-10/20} = 0.316$$

- The mid-band gain from the type 2A is therefore:

$$G_1 = \frac{G_0}{G_2} = \frac{0.316}{4.72} = 0.067 \text{ or } -23.5 \text{ dB}$$


- Calculate  $R_2$  for this attenuation:

$$R_2 = G_1 R_1 \frac{\sqrt{\left(\frac{f_c}{f_p}\right)^2 + 1}}{\sqrt{\left(\frac{f_z}{f_c}\right)^2 + 1}} = 2.6 \text{ k}\Omega$$



# TL431 Type 2 Design Example – No Fast Lane

- The simulation results confirm the calculations are ok

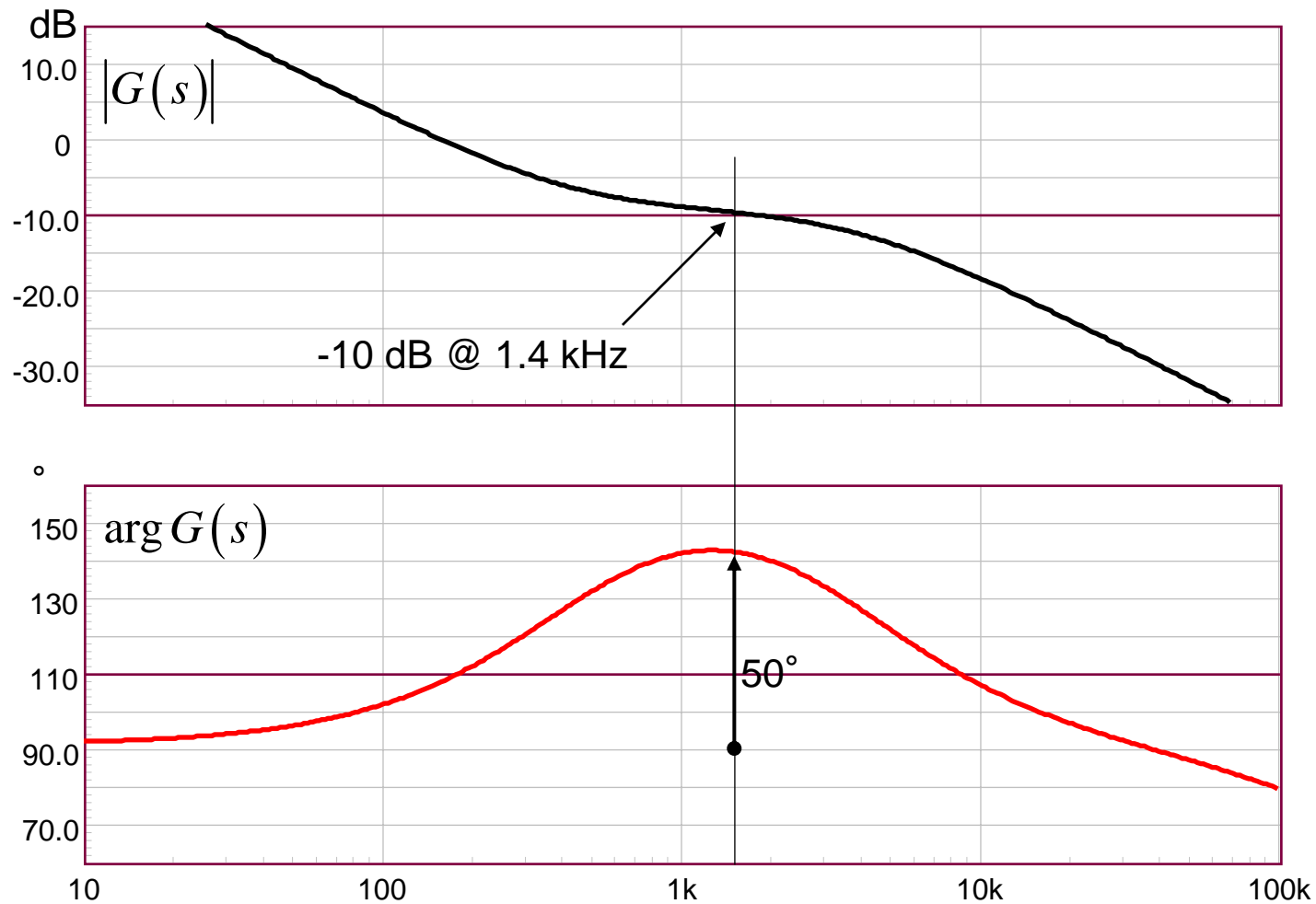

TL431


---

# Agenda

- ❑ Feedback generalities
- ❑ The TL431 in a compensator
- ❑ Small-signal analysis of the return chain
- ❑ A type 1 implementation with the TL431
- ❑ A type 2 implementation with the TL431
- ❑ **A type 3 implementation with the TL431**
- ❑ Design examples
- ❑ Conclusion
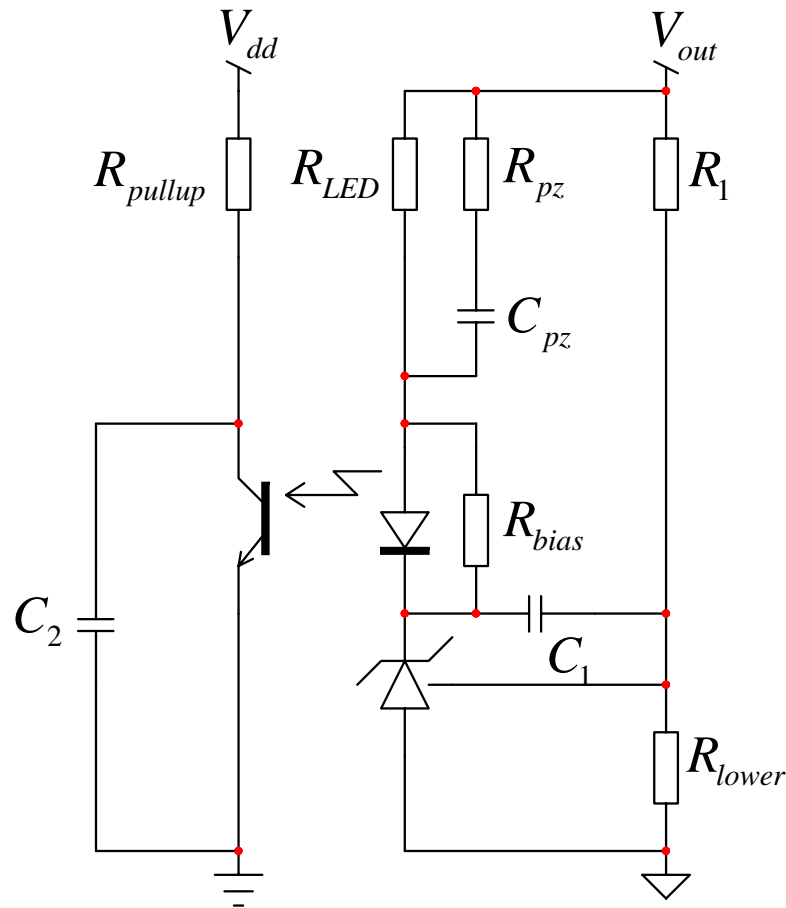
# The TL431 in a Type 3 Compensator

- The type 3 with a TL431 is difficult to put in practice



$$f_{z_1} = \frac{1}{2\pi R_1 C_1}$$

$$f_{z_2} = \frac{1}{2\pi (R_{LED} + R_{pz}) C_{pz}}$$

$$f_{p_1} = \frac{1}{2\pi R_{pz} C_{pz}}$$

$$f_{p_2} = \frac{1}{2\pi R_{pullup} (C_2 \parallel C_{opto})}$$

$$G = \frac{R_{pullup}}{R_{LED}} \text{CTR}$$


$R_{LED}$  fixes the gain and a zero position

- Suppress the fast lane for an easier implementation!

TL431
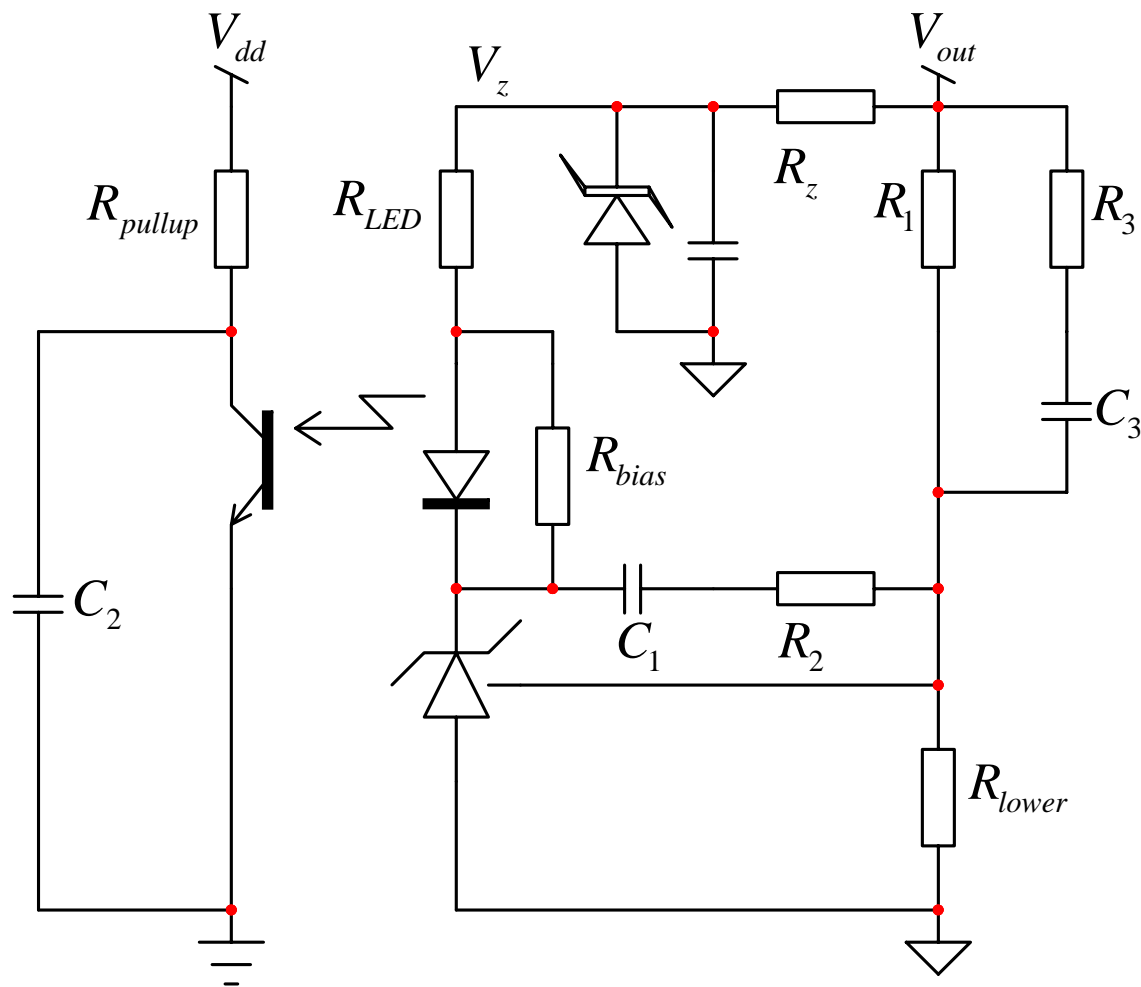
# The TL431 in a Type 3 Compensator

- Once the fast lane is removed, you have a classical configuration



$$f_{z_1} = \frac{1}{2\pi R_2 C_1}$$

$$f_{z_2} = \frac{1}{2\pi R_1 C_3}$$

$$f_{p_1} = \frac{1}{2\pi R_3 C_3}$$

$$f_{p_2} = \frac{1}{2\pi R_{pullup} (C_2 \parallel C_{opto})}$$

$$G = \frac{R_{pullup}}{R_{LED}} \text{CTR}$$

TL431

# TL431 Type 3 Design Example – No Fast Lane

- ❑ We want to provide a 10-dB attenuation at 1 kHz
- ❑ The phase boost needs to be of 120°
- place the double pole at 3.7 kHz and the double zero at 268 Hz
- ❑ Calculate the maximum LED resistor you can accept, apply margin

$$R_{LED,max} \leq \frac{V_z - V_f - V_{TL431,min}}{V_{dd} - V_{CE,sat} + I_{bias} CTR_{min} R_{pullup}} R_{pullup} CTR_{min} \leq 1.5 k\Omega \xrightarrow{\times 0.85} 1.3 k\Omega$$

- ❑ We need to account for the extra gain term:

$$G_2 = \frac{R_{pullup}}{R_{LED}} CTR = \frac{20k}{1.3k} 0.3 = 4.6$$

- ❑ The required total mid-band attenuation at 1 kHz is -10 dB

$$G_{fc} = 10^{-10/20} = 0.316$$

# TL431 Type 3 Design Example – No Fast Lane

- The mid-band gain from the type 3 is therefore:

$$G_1 = \frac{G_0}{G_2} = \frac{0.316}{4.6} = 0.068 \text{ or } -23.3 \text{ dB}$$

- Calculate  $R_2$  for this attenuation:

$$R_2 = \frac{G_1 R_1 f_{p1} \sqrt{1 + \left(\frac{f_c}{f_{p1}}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_{p2}}\right)^2}}{f_{p1} - f_{z1} \sqrt{1 + \left(\frac{f_{z1}}{f_c}\right)^2} \sqrt{1 + \left(\frac{f_c}{f_{z2}}\right)^2}} = 744 \Omega$$


$$C_1 = 800 \text{ nF} \quad C_2 = 148 \text{ pF} \quad C_3 = 14.5 \text{ nF} \quad C_{opto} = 2 \text{ nF}$$

- The optocoupler pole limits the upper double pole position
- The maximum boost therefore depends on the crossover frequency



# TL431 Type 3 Design Example – No Fast Lane

- The decoupling between  $V_{out}$  and  $V_{bias}$  affects the curves

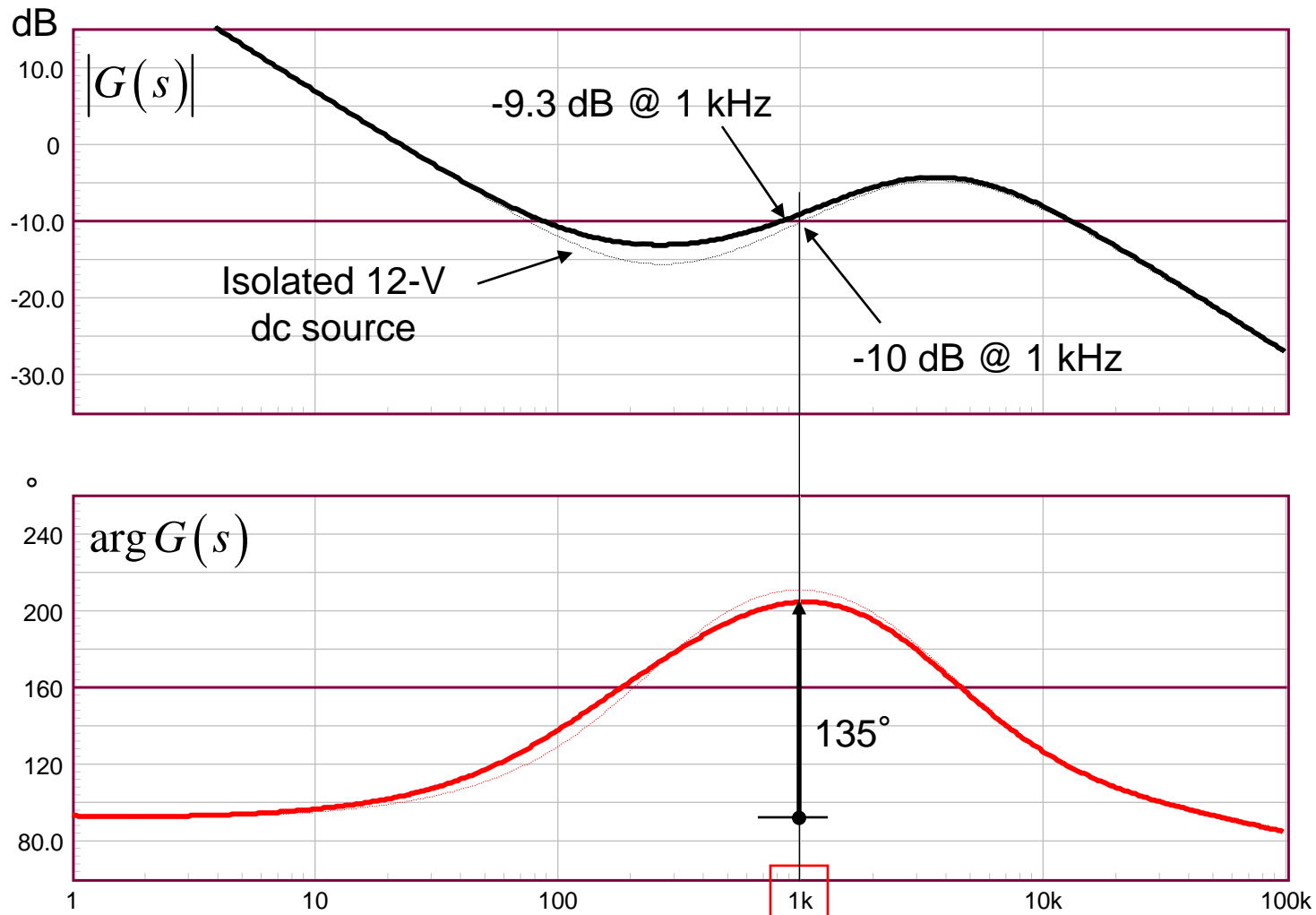

TL431


---

# Agenda

- ❑ Feedback generalities
- ❑ The TL431 in a compensator
- ❑ Small-signal analysis of the return chain
- ❑ A type 1 implementation with the TL431
- ❑ A type 2 implementation with the TL431
- ❑ A type 3 implementation with the TL431
- ❑ **Design examples**
- ❑ Conclusion

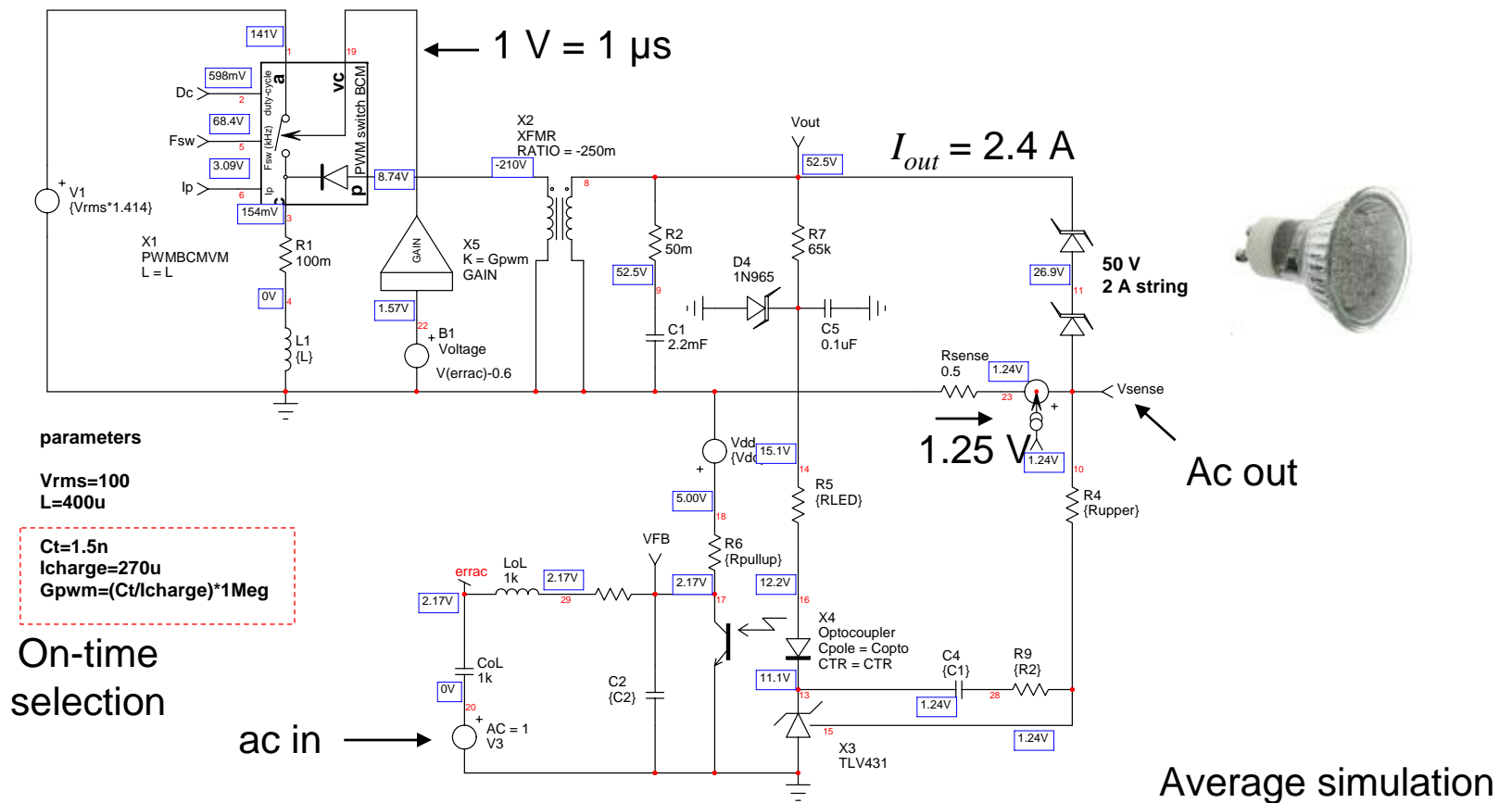
# Design Example 1 – a Single-Stage PFC

- ❑ The single-stage PFC is often used in LED applications
- ❑ It combines isolation, current-regulation and power factor correction
- ❑ Here, a constant on-time BCM controller, the **NCL30000**, is used




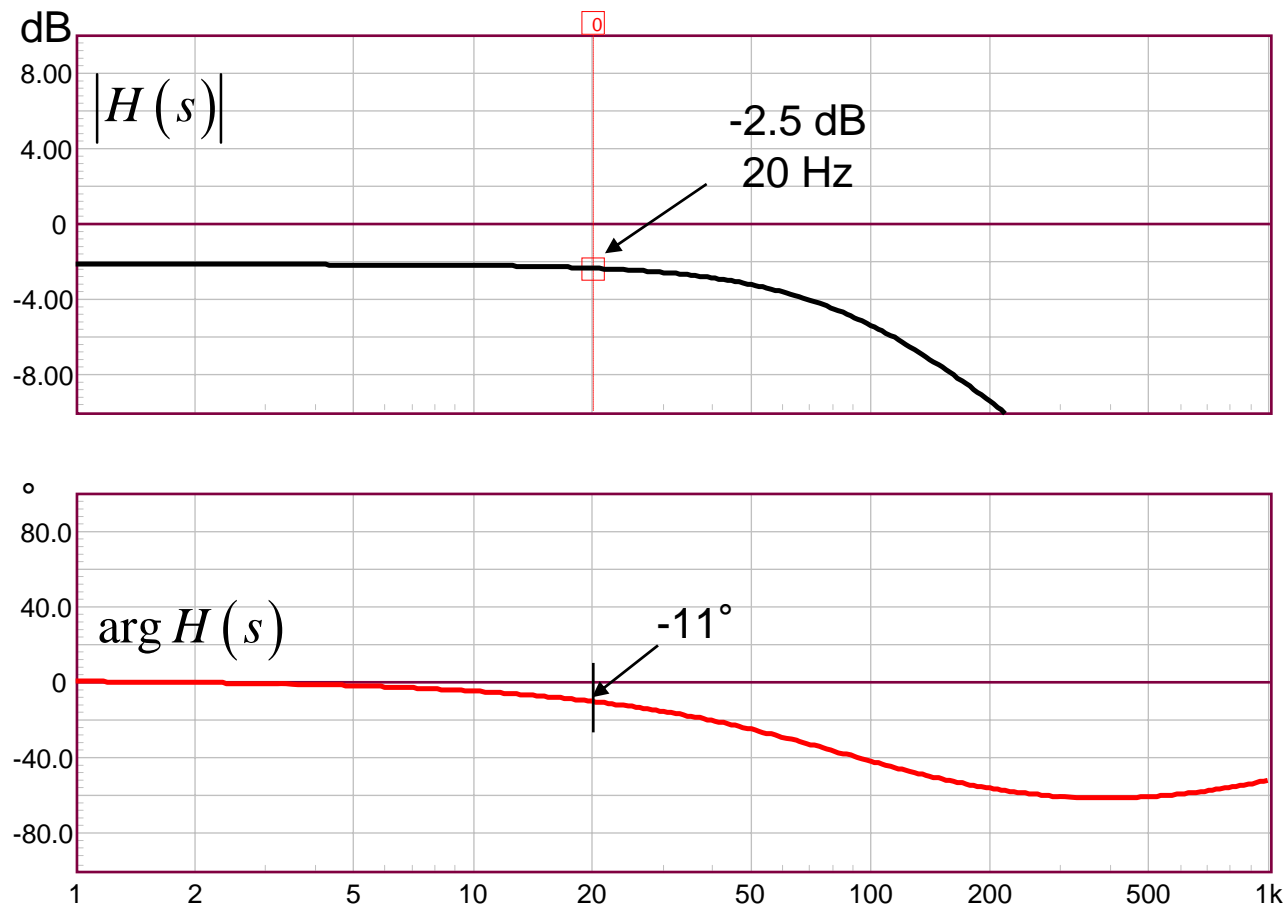
# Design Example 1 – a Single-Stage PFC

- Once the converter elements are known, ac-sweep the circuit
- Select a crossover low enough to reject the ripple, e.g. 20 Hz



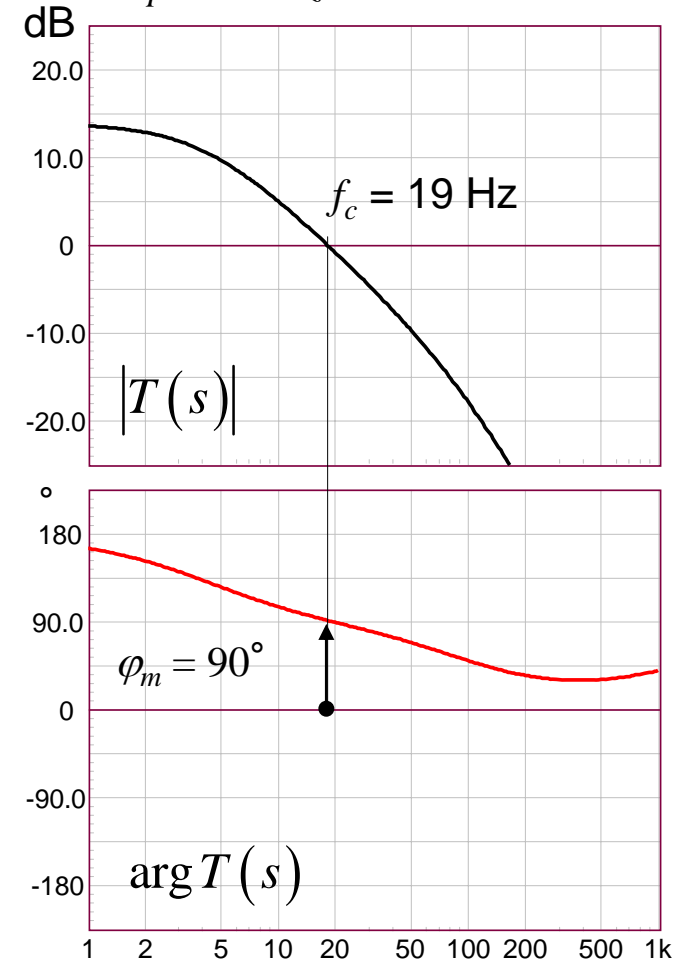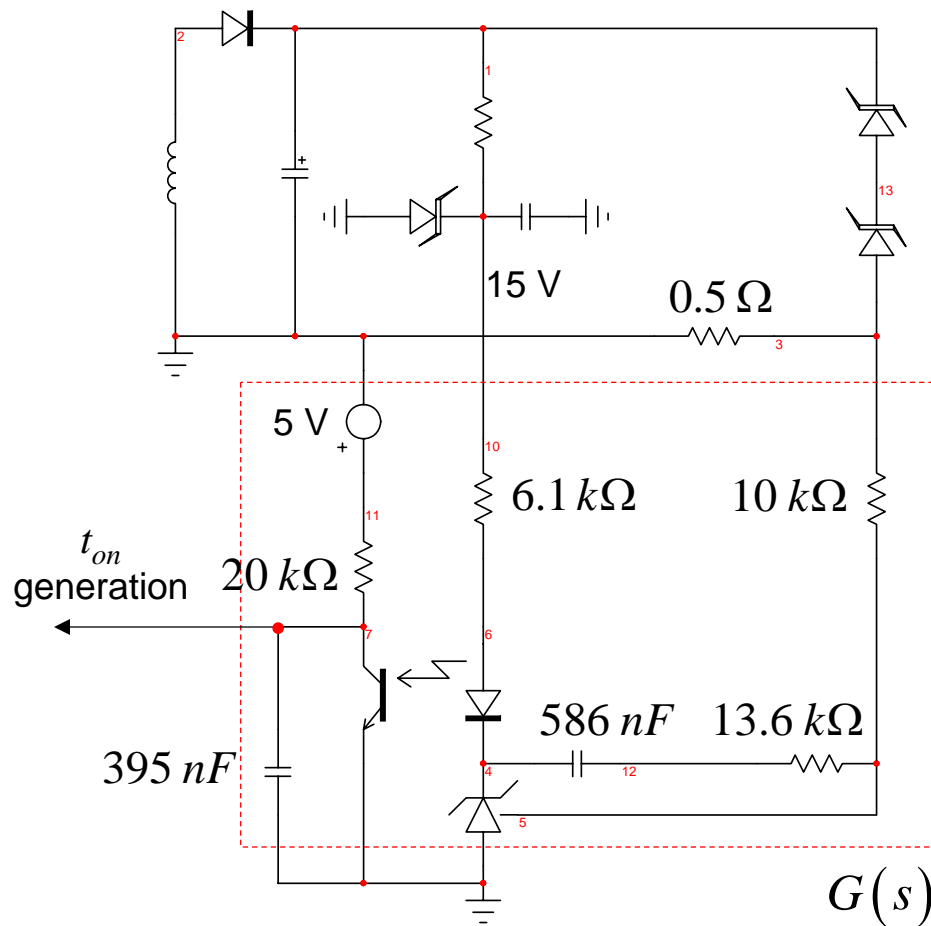
# Design Example 1 – a Single-Stage PFC

- Given the low phase lag, a type 1 can be chosen
- Use the type 2 with fast lane removal where  $f_p$  and  $f_z$  are coincident


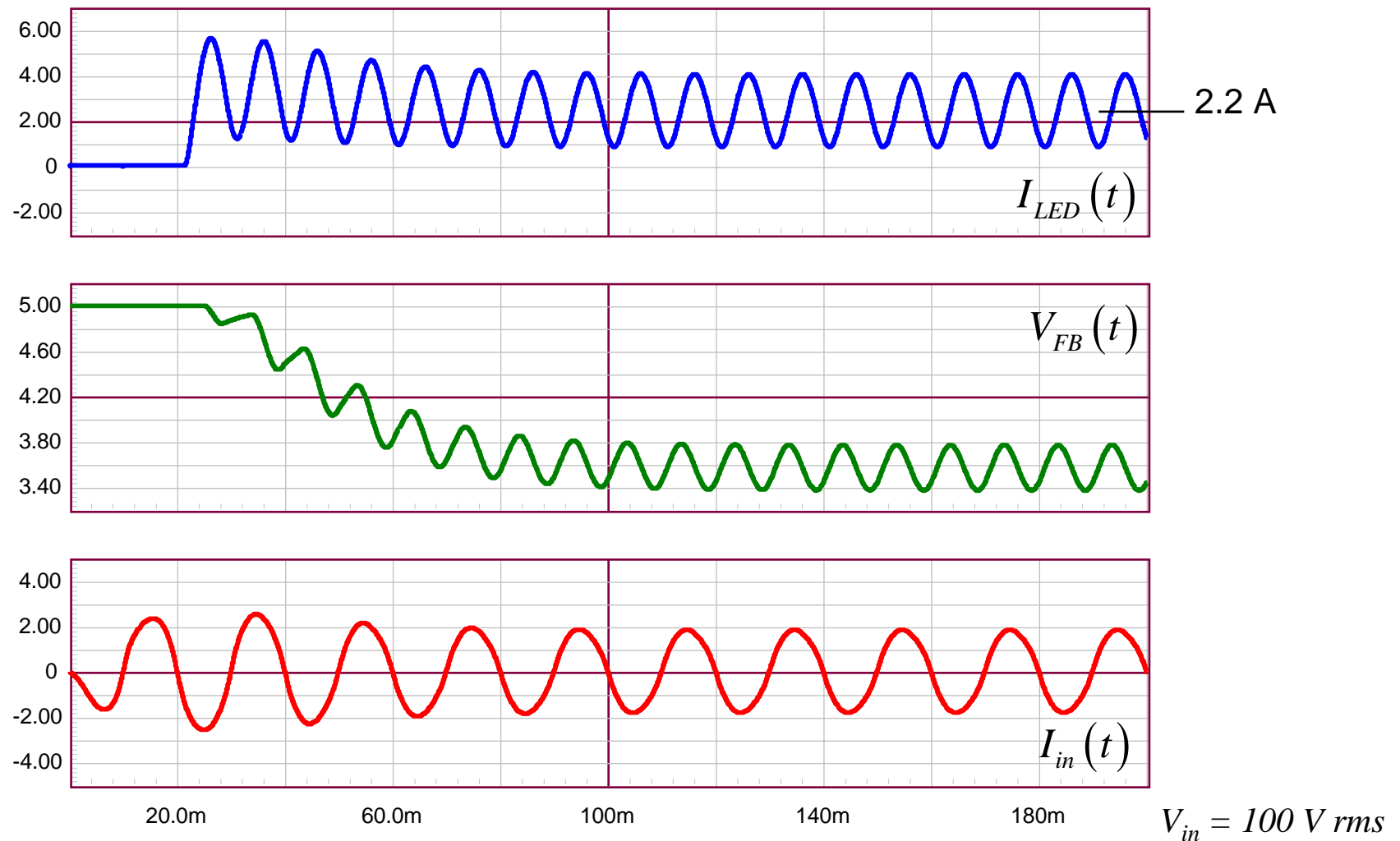
# Design Example 1 – a Single-Stage PFC

- A transient simulation helps to test the system stability




## Design Example 2: a DCM Flyback Converter

- ❑ We want to stabilize a 20 W DCM adapter
  - ❑  $V_{in} = 85$  to  $265$  V rms,  $V_{out} = 12$  V/1.7 A
  - ❑  $F_{sw} = 65$  kHz,  $R_{pullup} = 20$  k $\Omega$
  - ❑ Optocoupler is SFH-615A, pole is at 6 kHz
  - ❑ Cross over target is 1 kHz
  - ❑ Selected controller: NCP1216
1. Obtain a power stage open-loop Bode plot,  $H(s)$
  2. Look for gain and phase values at cross over
  3. Compensate gain and build phase at cross over,  $G(s)$
  4. Run a loop gain analysis to check for margins,  $T(s)$
  5. Test transient responses in various conditions
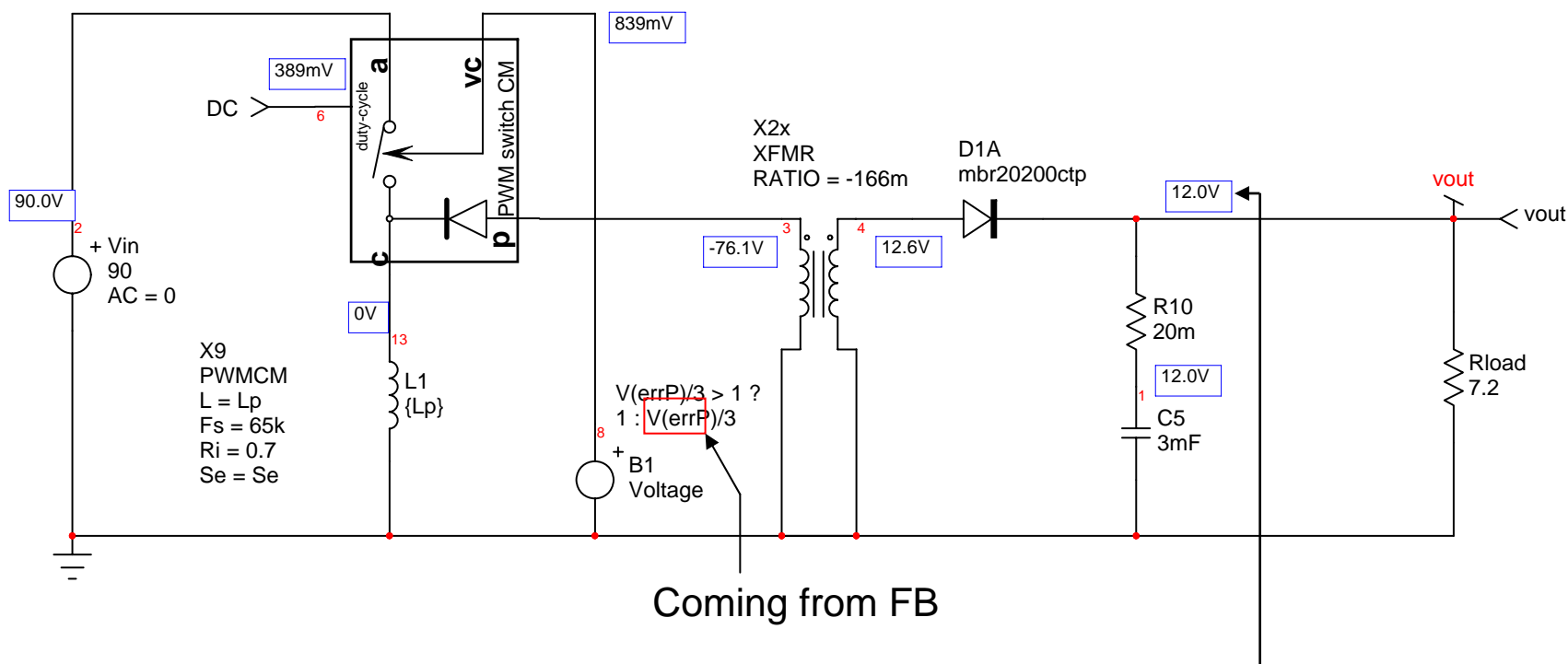
## Design Example 2: a DCM Flyback Converter

- Capture a SPICE schematic with an averaged model




- Look for the bias points values:  $V_{out} = 12\text{ V}$ , ok


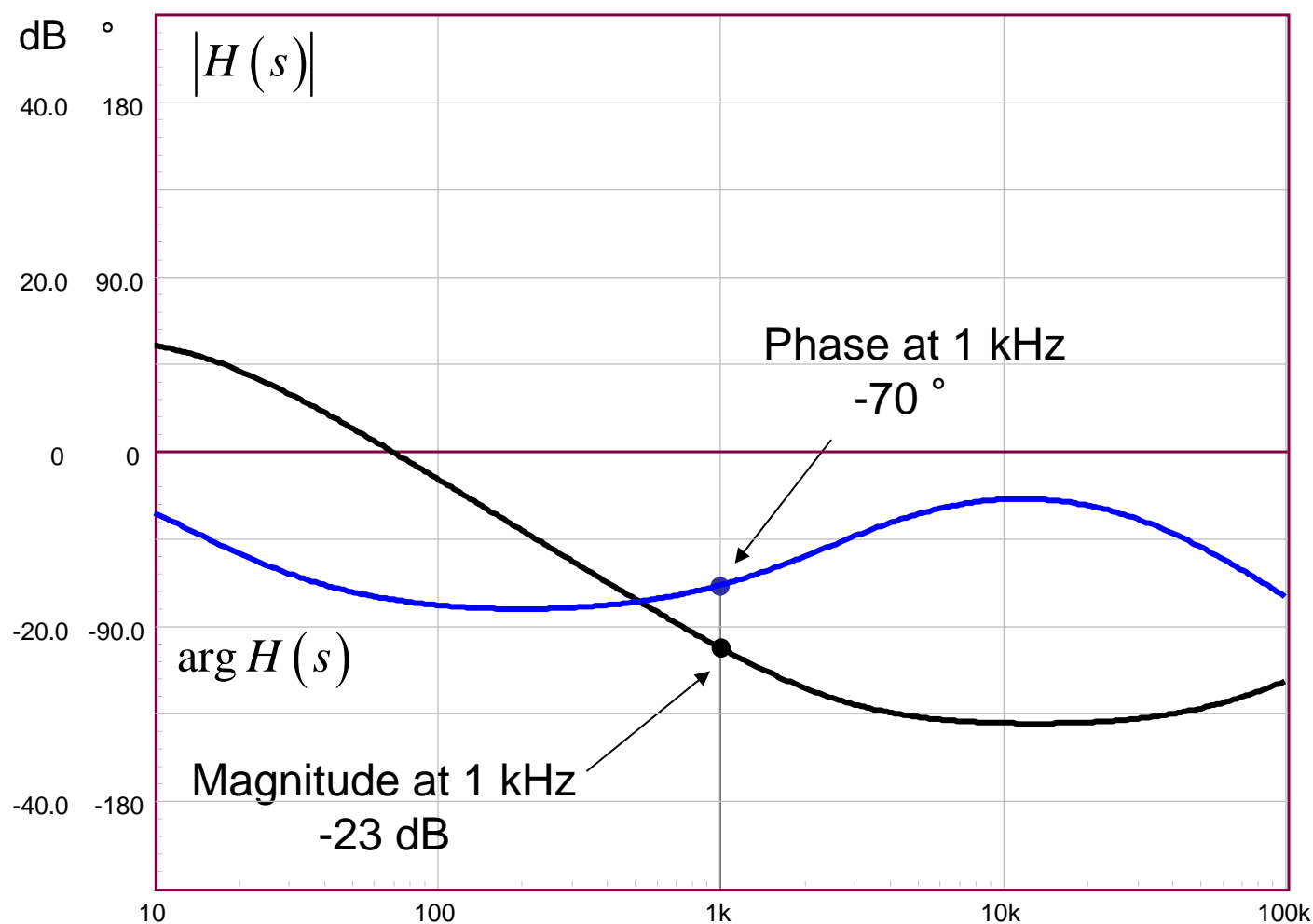
## Design Example 2: a DCM Flyback Converter


- Observe the open-loop Bode plot and select  $f_c$ : 1 kHz


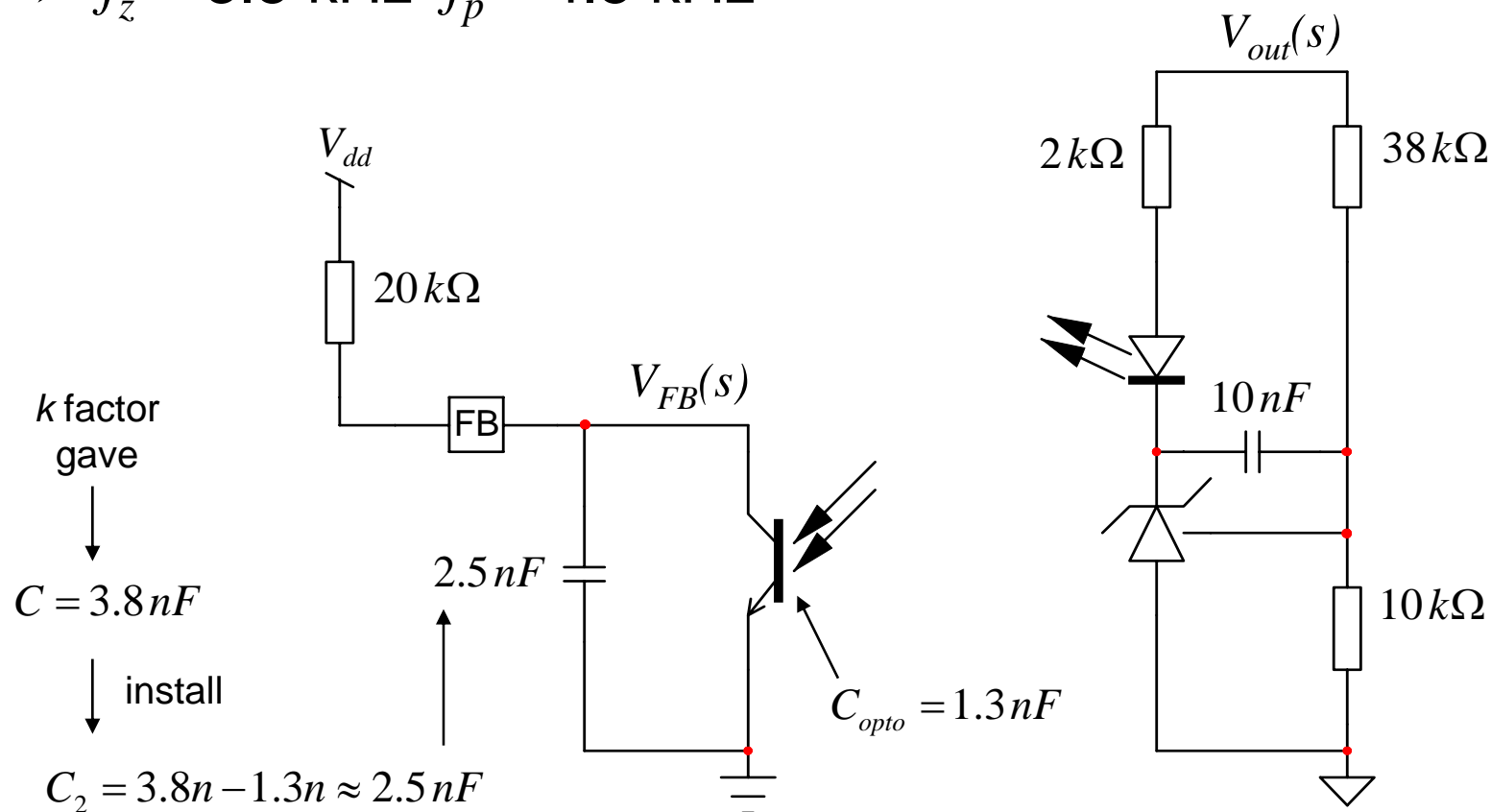
## Design Example 2: a DCM Flyback Converter


□ Apply  $k$  factor or other method, get  $f_z$  and  $f_p$

➤  $f_z = 3.5 \text{ kHz}$   $f_p = 4.5 \text{ kHz}$



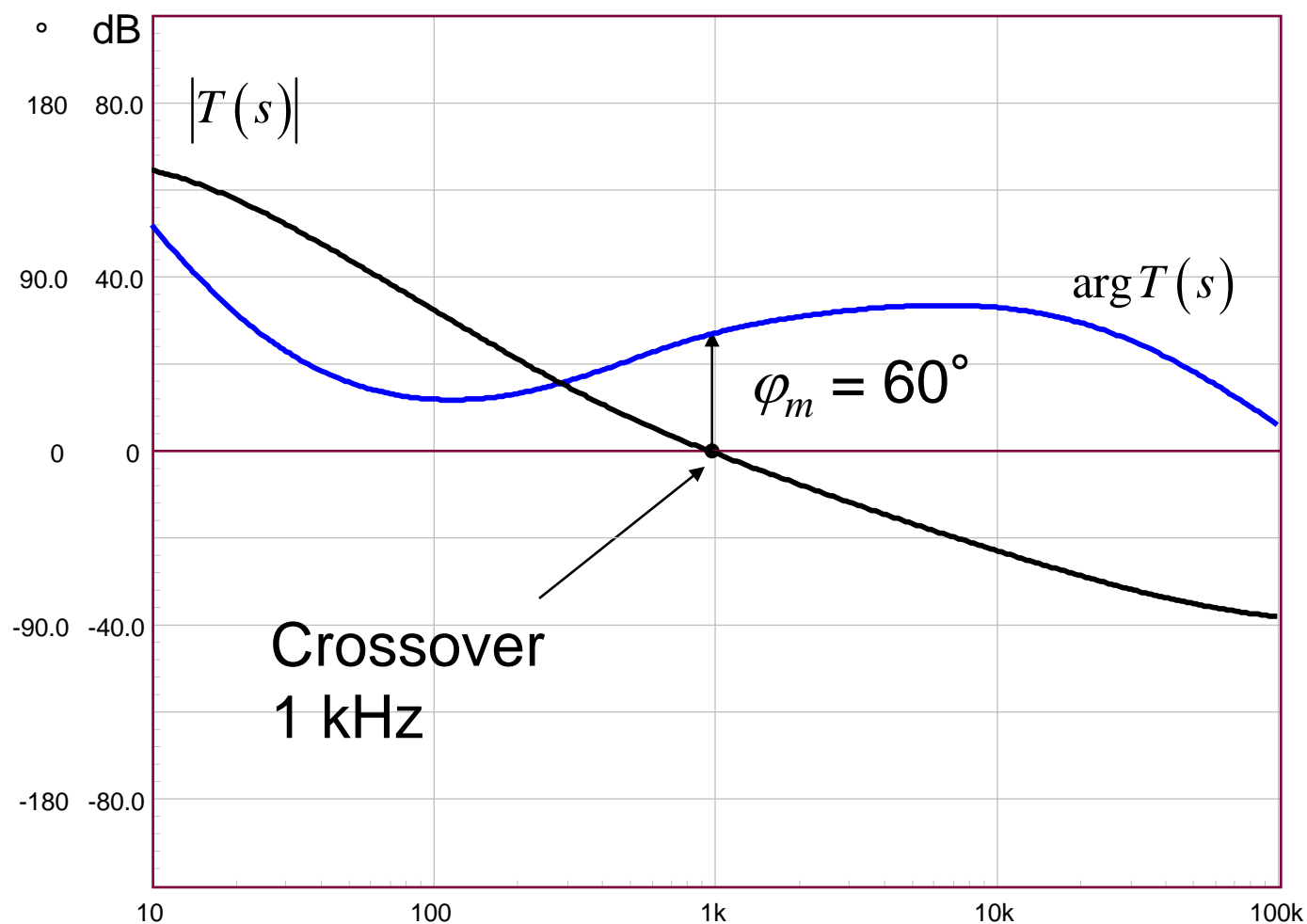
## Design Example 2: a DCM Flyback Converter

- Check loop gain and watch phase margin at  $f_c$


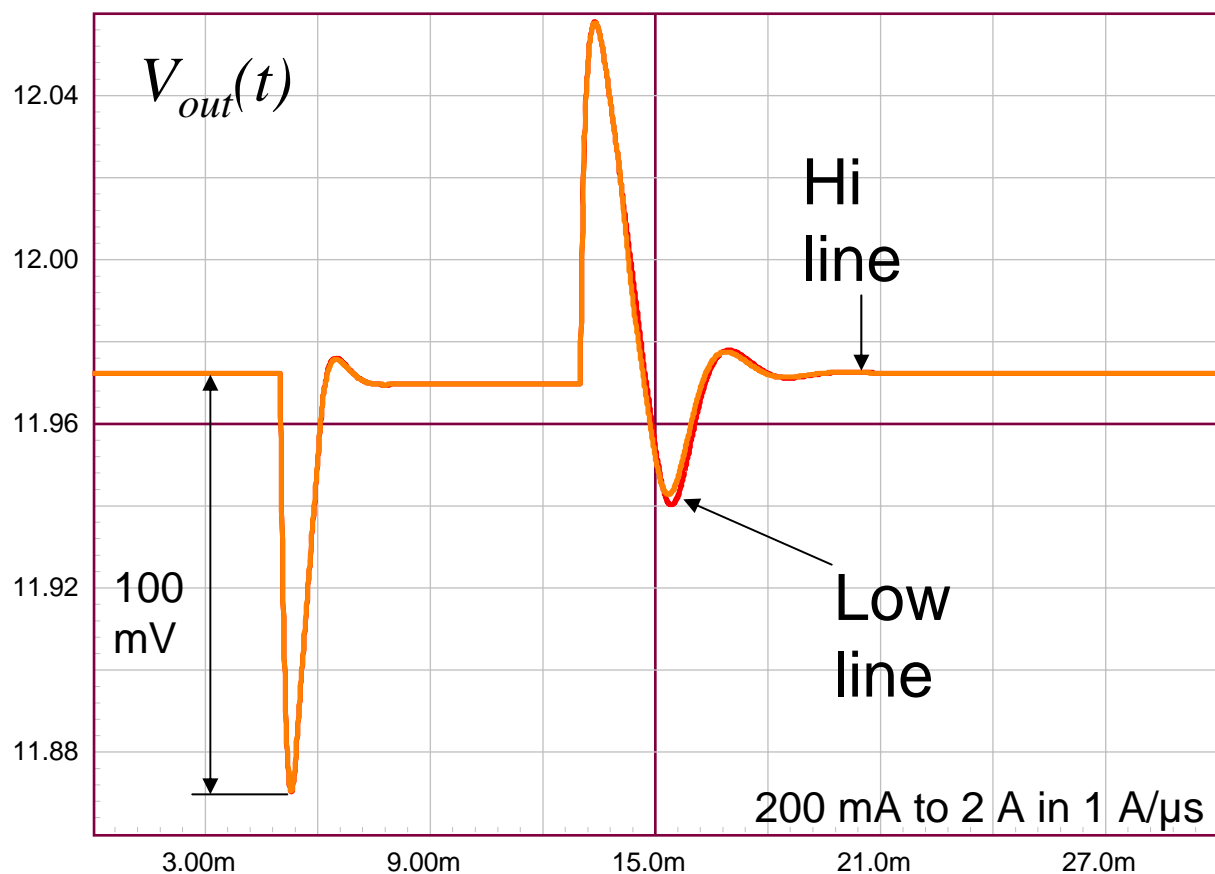
# Design Example 2: a DCM Flyback Converter

- Sweep ESR values and check margins again



Excellent!




# Use an Automated Design Tool

❑ To speed-up your design studies, use the right tool!


1.

Enter  
calculated  
values

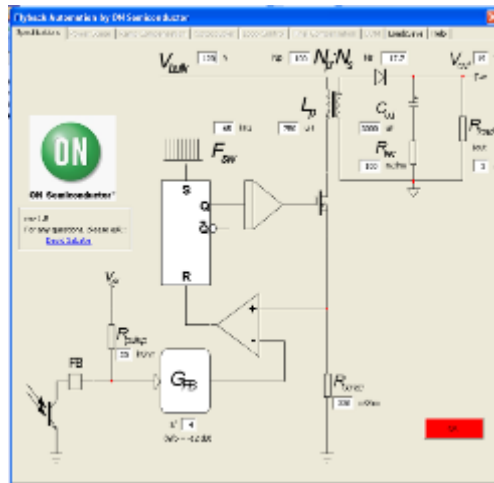


2.

Show power  
stage gain  
and phase

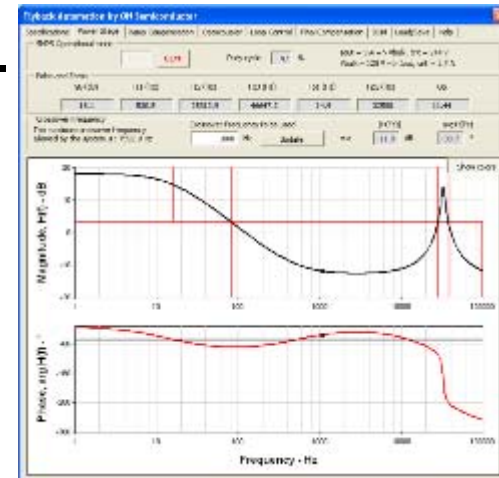

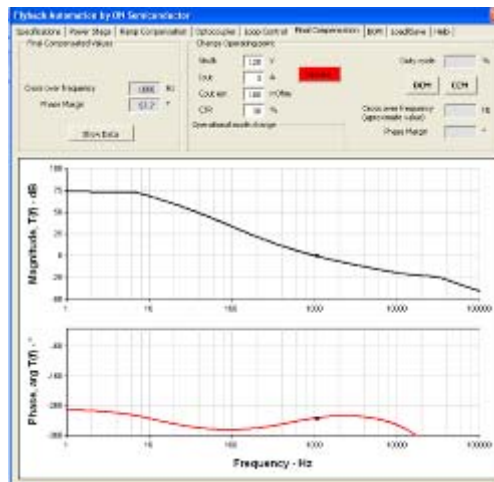
3.

Compute  
pole/zero  
check open  
loop gain



4.

See final  
values on  
TL431

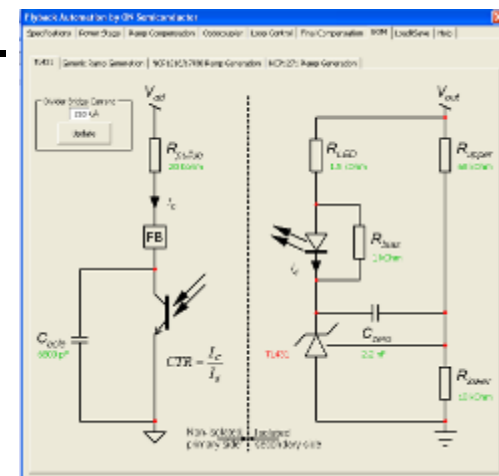

[www.onsemi.com](http://www.onsemi.com)  
NCP1200, design tools

# Conclusion

- ❑ Classical loop control theory describes op amps in compensators
- ❑ Engineers cannot apply their knowledge to the TL431
- ❑ Examples show that the TL431 with an optocoupler have limits
- ❑ Once these limits are understood, the TL431 is simple to use
- ❑ All three compensator types have been covered
- ❑ Design examples showed the power of averaged models
- ❑ Use them to extensively reproduce parameter dispersions
- ❑ Applying these recipes is key to design success!



Merci !  
Thank you!  
Xiè-xie!

---

## For More Information

- View the extensive portfolio of power management products from ON Semiconductor at [www.onsemi.com](http://www.onsemi.com)
- View reference designs, design notes, and other material supporting the design of highly efficient power supplies at [www.onsemi.com/powersupplies](http://www.onsemi.com/powersupplies)

