




ON Semiconductor[®]

Compensating a PFC Stage

Agenda

- Introduction
- Deriving a small-signal model
 - General method
 - Practical example: NCP1605-driven PFC stages
- Compensating the loop
 - Type-2 compensation
 - Influence of the line and power level
 - Computing the compensation
 - Practical example
- Conclusion

Output Voltage Low Frequency Ripple

 

- The load power demand is matched in average only
- A **low frequency ripple** is inherent to the PFC function

PFC Stages are Slow Systems...


- The output ripple must be filtered to avoid current distortion.
- In practice, the loop frequency is selected in the range of 20 Hz, which is very low.
- Even if the bandwidth is low, the loop must be compensated!

Agenda

- Introduction
- Deriving a small-signal model
 - General method
 - Practical example: NCP1605-driven PFC stages
- Compensating the loop
 - Type-2 compensation
 - Influence of the line and power level
 - Computing the compensation
 - Practical example
- Conclusion

A Simple Representation

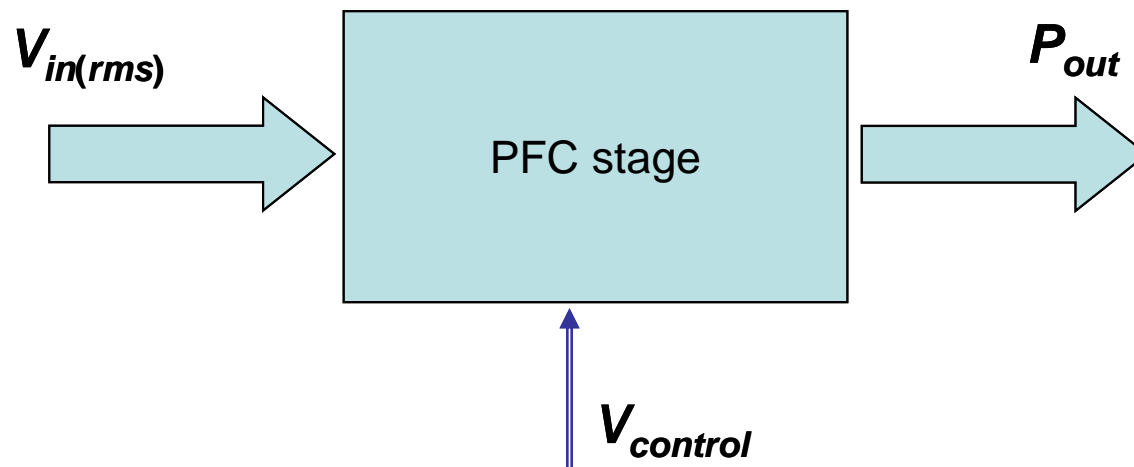
- We will consider the PFC stage as a system delivering a power under an input rms voltage and a control signal



- Details of the power processing are ignored:
 - Operation mode (CrM, CCM, Voltage or Current mode...)
 - 100% efficiency, only the average power contribution of the sinusoidal signals is considered

A Simple Large Signal Model

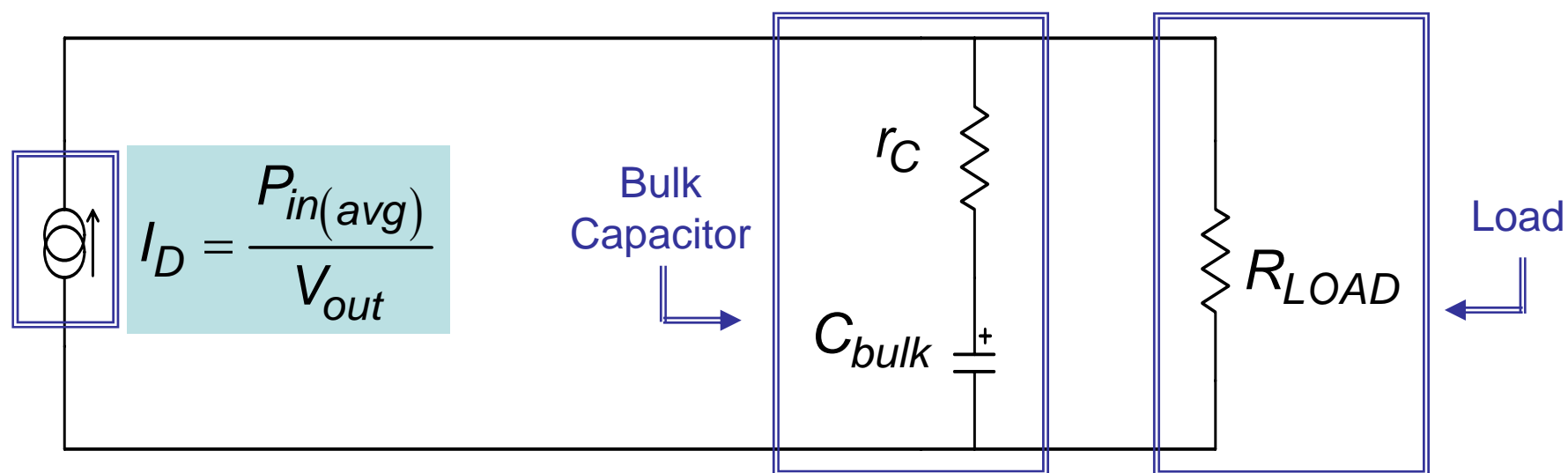
- Let's represent the PFC stage as a current source delivering the power to the bulk capacitor and the load:



- $P_{in(avg)}$ depends on $V_{control}$ (always), on $V_{in(rms)}$ (in the absence of feedforward) and sometimes on V_{out}
- 3 possible sources of perturbations: $V_{control}$, V_{out} and $V_{in(rms)}$.

NCP1605

- **Frequency Clamped Critical Conduction Mode (FCCrM)**
- Key features for a master PFC:
 - High voltage current source, Soft-Skip™ during standby mode
 - “pfcOK” signal, dynamic response enhancer
 - Bunch of protections for rugged PFC stages
- Markets: high power AC adapters, LCD TVs

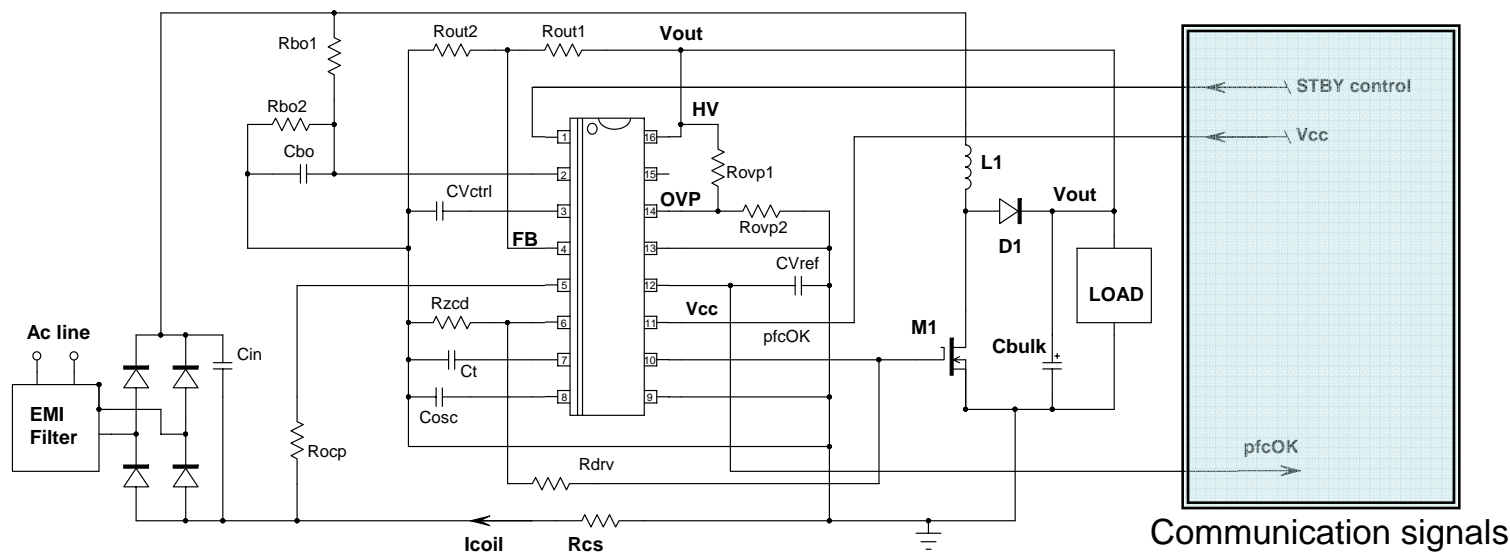

NCP1605 – Follower Boost

- Voltage mode operation: the circuit adjusts the power level by modulating the MOSFET conduction time
- The charge current of the timing capacitor is proportional to the FB square and hence to $(V_{out})^2$:

$$I_{charge} = I_t \cdot \left(\frac{V_{out}}{V_{out,nom}} \right)^2$$


where :

- $V_{out,nom}$ is the V_{out} regulation voltage
 - I_t is a 370- μ A current source
- The on-time is inversely proportional to $(V_{out})^2$ allowing the Follower boost function:

$$t_{on} = \frac{C_t \cdot V_{ton}}{I_t} \cdot \left(\frac{V_{out,nom}}{V_{out}} \right)^2$$

NCP1605 - Power Expression

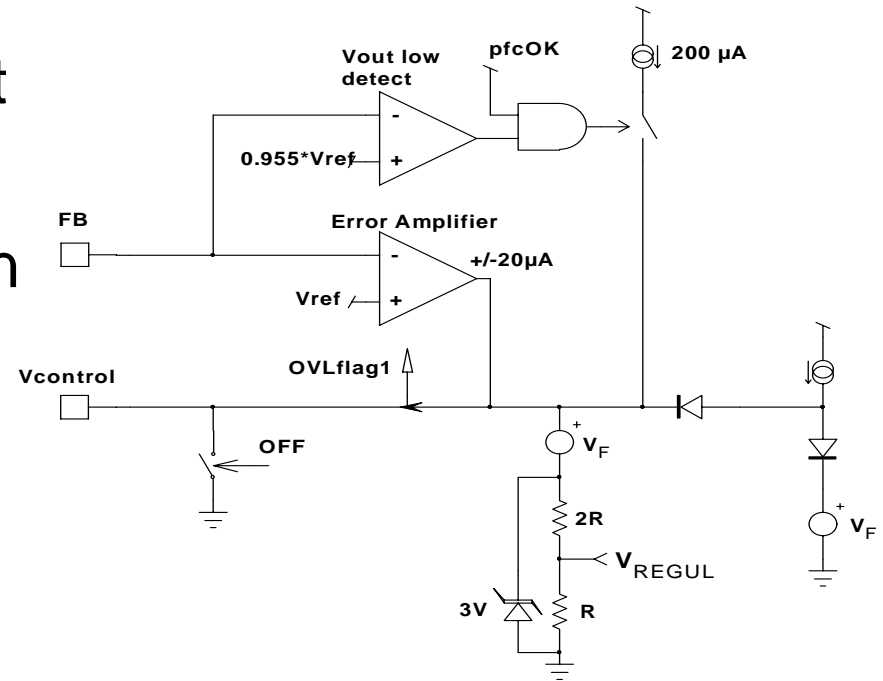- The control signal is V_F offset down and divided by 3 to form V_{REGUL} used in the PWM section




- Hence due to the follower boost function, the power is inversely dependent on $(V_{out})^2$:

$$P_{in(avg)} = \frac{C_t \cdot V_{in(rms)}^2}{2 \cdot L \cdot I_t} \cdot \left(\frac{V_{out,nom}}{V_{out}} \right)^2 \cdot \frac{(V_{control} - V_F)}{3}$$

NCP1605 - Large Signal Model

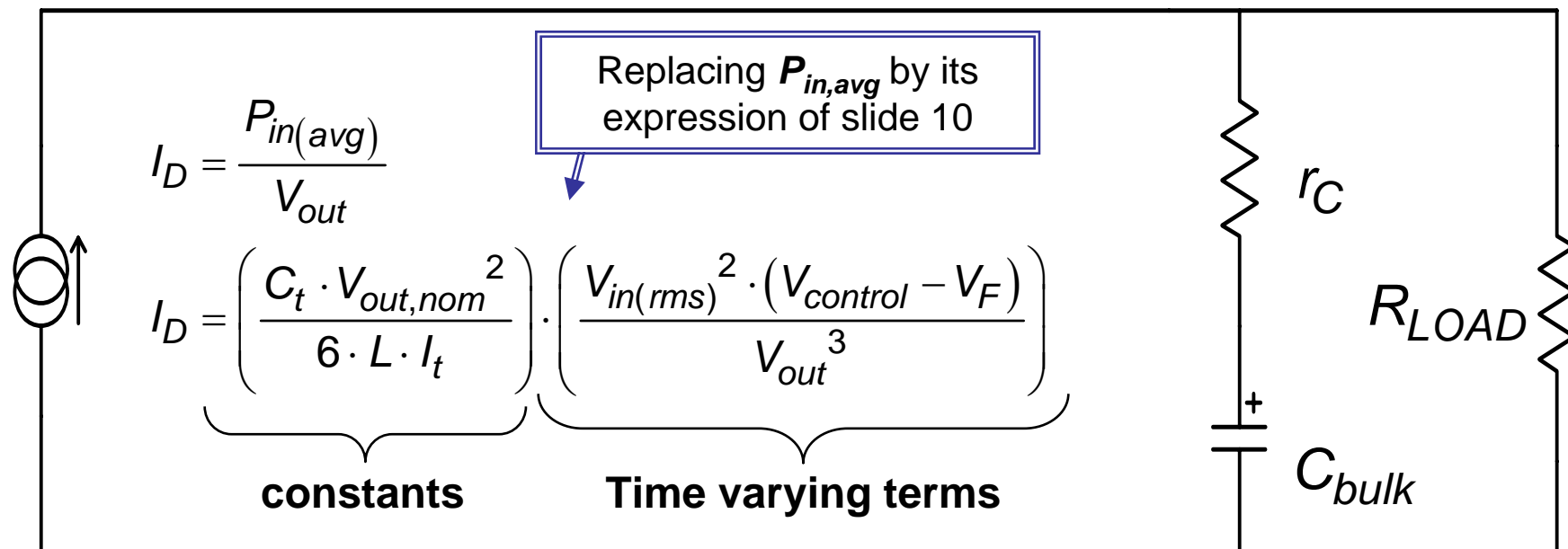- Let's represent the PFC stage as a current source delivering the power to the bulk capacitor and the load:



- 3 sources of perturbations: $V_{CONTROL}$, V_{out} and $V_{in(rms)}$.

Small Signal Model


- A large signal model is nonlinear because I_D is formed of the multiplication and division of $V_{control}$, $V_{in,rms}$ and V_{out} .
- This model needs to be linearized to assess the AC contribution of each variable
- The model is perturbed and linearized around a quiescent operating point (DC point)

Considering Variations Around the DC Value...

- Let's omit the perturbations of the line magnitude (assumed constant)
- Let's consider small variations around the DC values for V_{out} and $V_{control}$:


$$\hat{i}_D = \frac{\partial I_D}{\partial V_{control}} \cdot \hat{v}_{CONTROL} + \frac{\partial I_D}{\partial V_{out}} \cdot \hat{v}_{out}$$

- We then obtain:

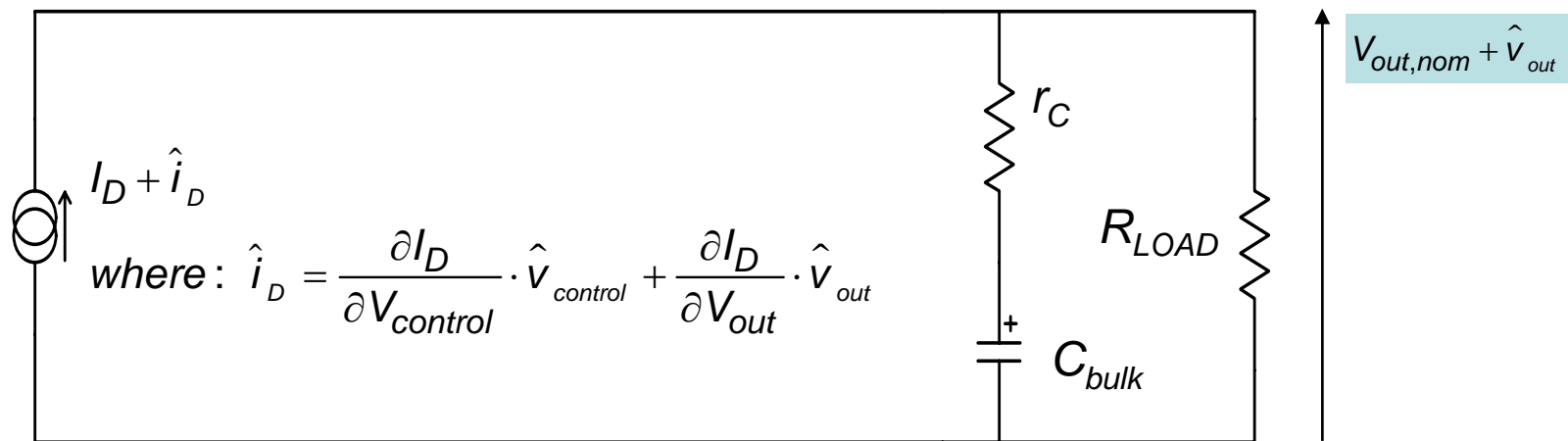

Deriving a Small Signal Model...

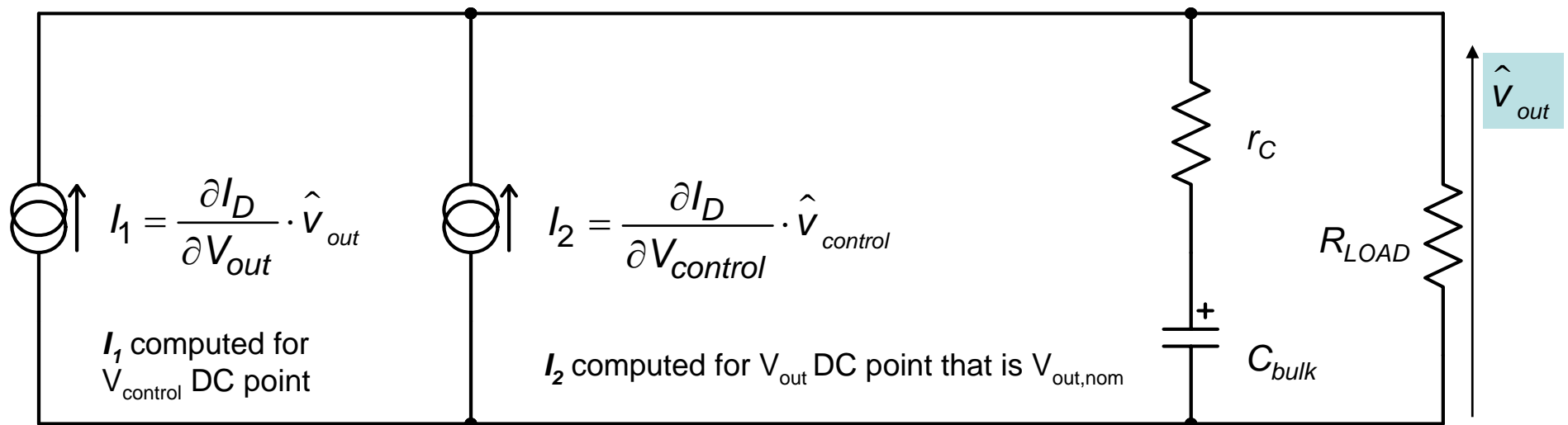- The DC portion can be eliminated
- The partial derivatives are to be computed at the DC point that is for:
 - $V_{control}$ that is the control signal DC value for the considered working point
 - $V_{out,nom}$ that is the nominal (DC) output voltage
- Replacing the derivations by their expression, we obtain:



Contribution of the V_{out} Perturbations

- Depending on the controller scheme

$$I_D = \frac{P_{in,avg}}{V_{out}} = \frac{f(V_{in(rms)}, V_{control})}{(V_{out})^{n+1}} \quad \text{where } n = 0, 1 \text{ or } 2$$

- $n=0$ for NCP1607
- $n=1$ for NCP1654 (predictive CCM PFC for which $P_{in,avg} \propto \frac{V_{control} \cdot V_{in,rms}}{V_{out}}$)
- $n=2$ for NCP1605 (follower boost – see slide 10)

- At the DC point


$$V_{out} = V_{out,nom} \quad \text{and} \quad \frac{P_{in(avg)}}{(V_{out,nom})^2} = \frac{1}{R_{LOAD}}$$

- Finally:

$$I_1 = \frac{\partial I_D}{\partial V_{out}} \cdot \hat{v}_{out} = - \frac{(n+1) \cdot f(V_{in(rms)}, V_{control})}{(V_{out})^{n+2}} \Bigg|_{V_{out}=V_{out,nom}} \cdot \hat{v}_{out} = - \frac{(n+1) \cdot P_{in(avg)}}{(V_{out,nom})^2} \cdot \hat{v}_{out} = - \frac{(n+1)}{R_{LOAD}} \cdot \hat{v}_{out}$$

2 Resistors...

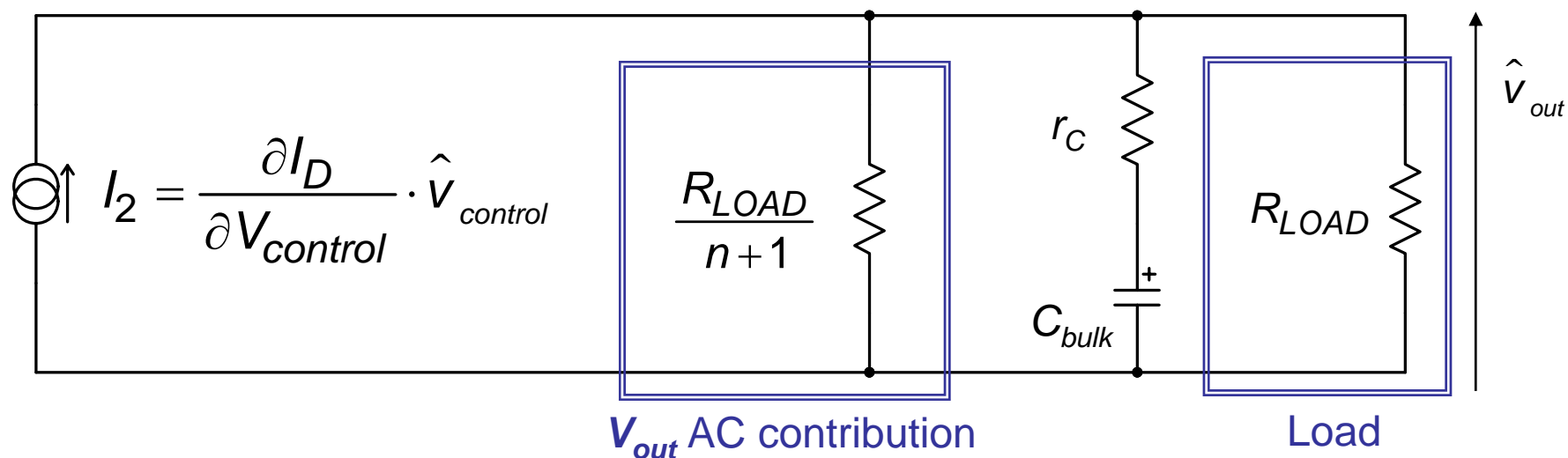
- Hence, the small signal model can be simplified as follows:



- Noting that: $\frac{R_{LOAD}}{n+1} \parallel R_{LOAD} = \frac{R_{LOAD}}{n+2}$
the model can be further simplified

Finally...

- The small signal model is:

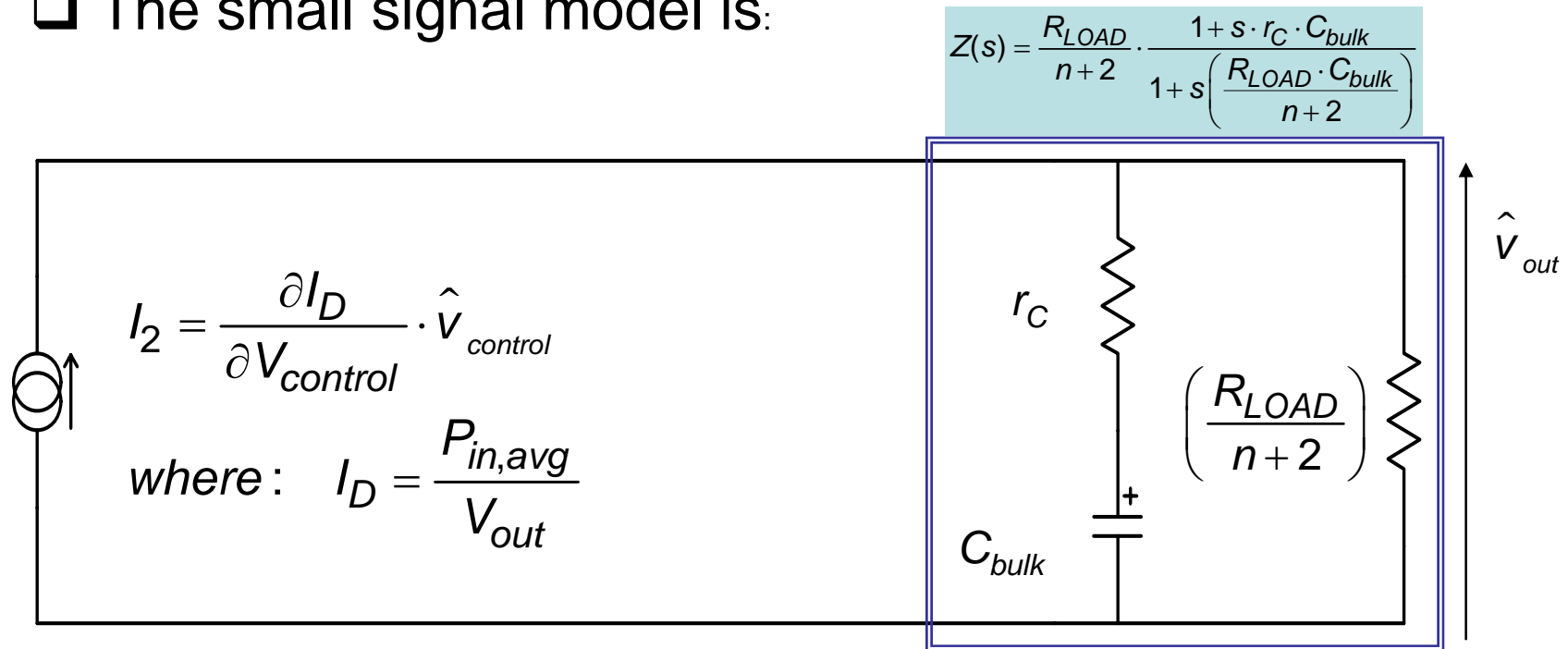

- The transfer function is:

$$\frac{\hat{V}_{out}}{\hat{V}_{control}} = \frac{R_{LOAD}}{n+2} \cdot \left(\frac{\partial I_D}{\partial V_{control}} \right) \cdot \frac{1 + s \cdot r_C \cdot C_{bulk}}{1 + s \left(\frac{R_{LOAD} \cdot C_{bulk}}{n+2} \right)}$$

NCP1605 Example

- The large signal model instructed that:

$$I_D = \frac{P_{in(avg)}}{V_{out}} = \left(\frac{C_t \cdot V_{out,nom}^2}{6 \cdot L \cdot I_t} \right) \cdot \left(\frac{V_{in(rms)}^2 \cdot (V_{control} - V_F)}{V_{out}^3} \right)$$

- Hence:

$$n = 2$$

$$\frac{\partial I_D}{\partial V_{control}} = \frac{C_t \cdot (V_{in(rms)})^2}{6 \cdot L \cdot I_t \cdot V_{out,nom}}$$


V_{out}^3

$(V_{out})^{n+1}$ term



NCP1605 - Small Signal Model


- Finally:

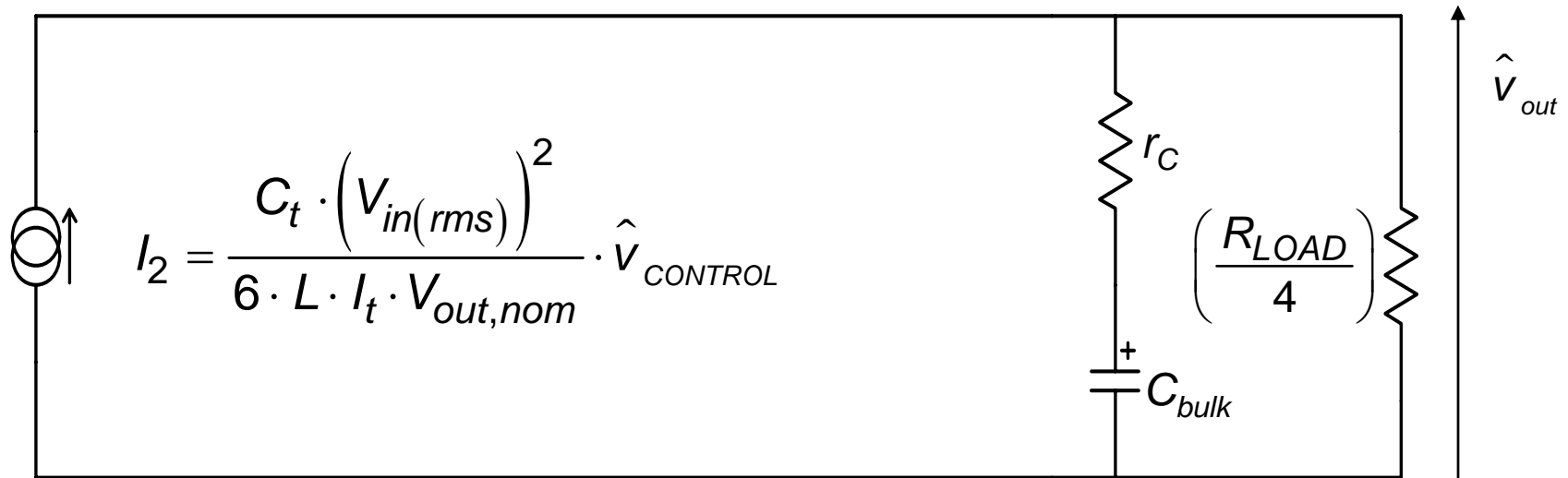

- The transfer function is:

$$\frac{\hat{V}_{out}}{\hat{V}_{CONTROL}} = \frac{R_{LOAD} \cdot C_t \cdot (V_{in(rms)})^2}{24 \cdot L \cdot I_t \cdot V_{out,nom}} \cdot \frac{1 + s \cdot r_C \cdot C_{bulk}}{1 + s \cdot \left(\frac{R_{LOAD} \cdot C_{bulk}}{4}\right)}$$

Power Stage Characteristic – Bode Plots

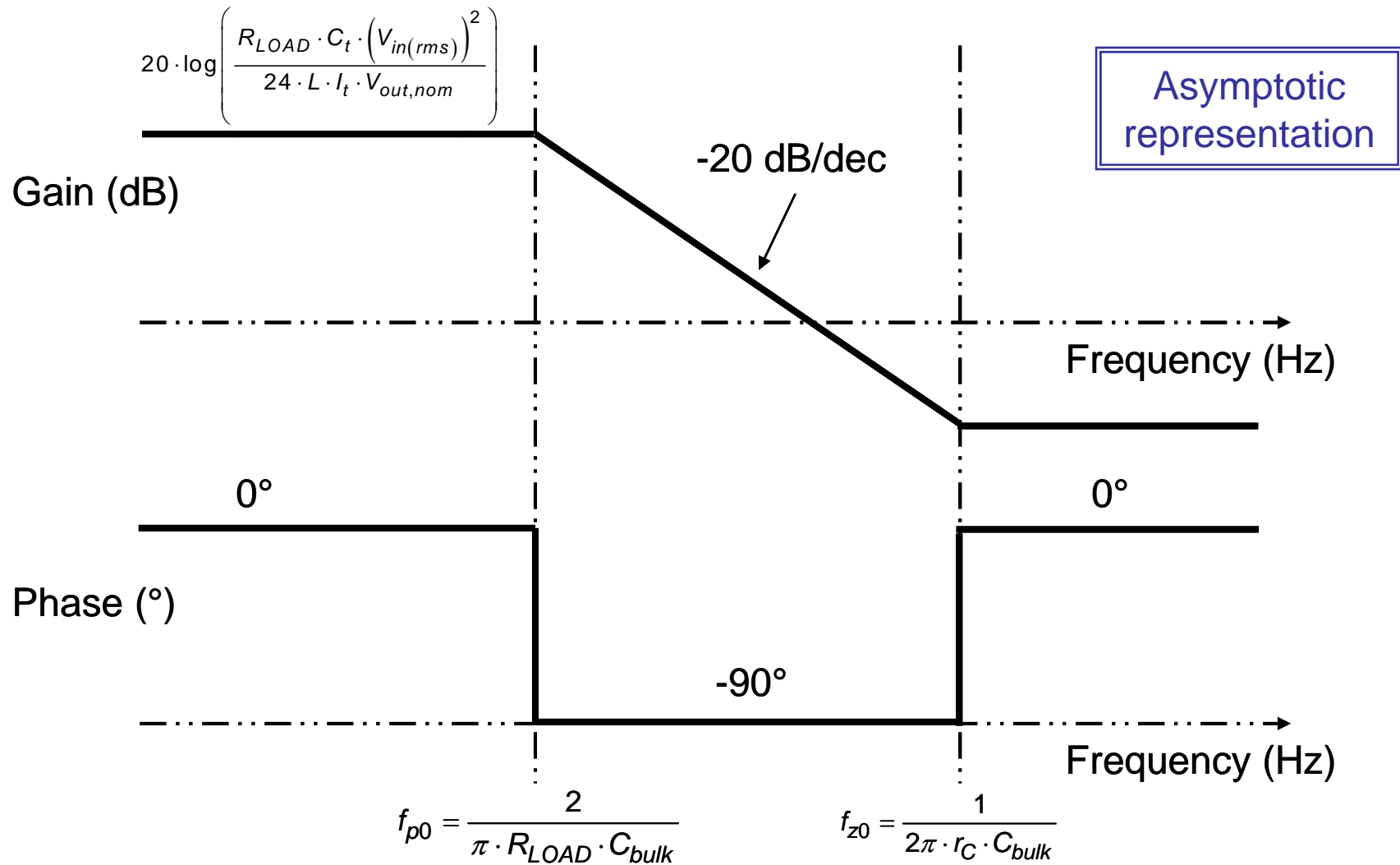

Agenda


- Introduction
- Deriving a small-signal model
 - General method
 - Practical example: NCP1605-driven PFC stages
- **Compensating the loop**
 - Type-2 compensation
 - Influence of the line and power level
 - Computing the compensation
 - Practical example
- Conclusion

Compensation Phase Boost

- The zero brought by the bulk capacitor ESR is too high to bring some phase margin. It is ignored.
- The PFC open loop inherently causes a -360° phase shift:
 - Power stage pole $\rightarrow -90^\circ$
 - Error amplifier inversion $\rightarrow -180^\circ$
 - Compensation origin pole $\rightarrow -90^\circ$
- The compensation must then provide some phase boost
- **A type-2 compensation is recommended**

Type-2 Compensation

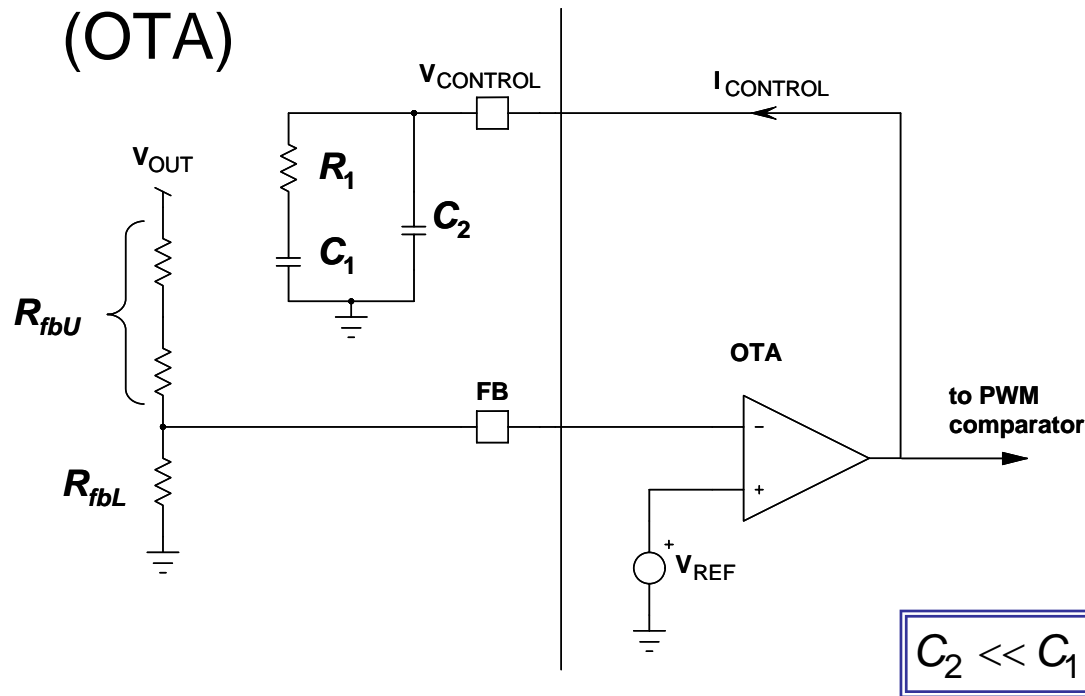- The NCP1605 embeds a transconductance error amplifier (OTA)



$$f_{z1} = \frac{1}{2\pi \cdot R_1 \cdot C_1}$$

$$f_{p2} = \frac{1}{2\pi \cdot R_1 \cdot C_2}$$

$$f_{p1} = \frac{1}{2\pi \cdot R_0 \cdot C_1}$$


pole at the origin

$$R_0 = \frac{V_{out,nom}}{V_{ref} \cdot G_{EA}}$$

- No direct influence of the R_{fbU} impedance on the compensation
- Only the feedback scale factor interferes

- V_{ref} is the reference voltage (generally 2.5 V in ON semi devices)
- G_{EA} is the OTA (200- μ S transconductance gain for NCP1605, NCP1654 and NCP1631)

Type-2 Characteristic - Example

 

f_{z1} : compensation zero (6 Hz)

f_{p2} : high frequency pole (90 Hz)

$$\sqrt{f_{z1} \cdot f_{p2}}$$

□ f_{p2} and f_{z1} set the phase boost magnitude and location (frequency)


□ The phase boost peaks at: $(f_{PhB} = \sqrt{f_{z1} \cdot f_{p2}})$ that is 27 Hz

□ The phase boost is:

$$\tan^{-1}\left(\frac{f_{phB}}{f_z}\right) - \tan^{-1}\left(\frac{f_{phB}}{f_p}\right)$$

□ The origin pole f_{p1} adjusts the gain G_c at the phase boost frequency


Phase Boost at the Crossover Frequency

 

$$\phi_B = \tan^{-1}\left(\frac{f_c}{f_{z1}}\right) - \tan^{-1}\left(\frac{f_c}{f_{p2}}\right)$$

- ❑ The lower f_{z1} and/or the higher f_{p2} , the higher the phase boost (max. value: 90°)
- ❑ Assuming the PFC power stage pole is well below the crossover frequency (f_c), the phase boost equates the phase margin ($\phi_m = \phi_B$)
- ❑ Target a phase boost between 45° and 75°

Gain Considerations

 

- In the red trace, the distance between the zero and the pole frequencies is increased
- Both characteristics generate the same attenuation at the crossover frequency
- The lower the f_{z1} frequency, the lower the gain in the low frequency region
- The higher f_{p2} , the lower the $(2 \cdot f_{line})$ ripple rejection

Type-2 Compensator - Summary

- The zero should not be placed at a too low frequency (not to penalize the low-frequency gain)
- The high frequency pole must be placed at a frequency low enough to attenuate the line ripple
- The phase boost (and phase margin) depends on the zero and high-frequency pole locations
- The origin pole is set to force the open loop gain to zero at the targeted crossover frequency

Agenda

- Introduction
- Deriving a small-signal model
 - General method
 - Practical example: NCP1605-driven PFC stages
- **Compensating the loop**
 - Type-2 compensation
 - Influence of the line and power level
 - Computing the compensation
 - Practical example
- Conclusion

Compensating for the Full Range?...

- The static gain depends on the load and if there is no feedforward, on the line magnitude

$$G_{static(dB)} = 20 \cdot \log \left(\frac{R_{LOAD}}{n+2} \cdot \left(\frac{\partial I_D}{\partial V_{control}} \right) \right) = 20 \cdot \log \left(\frac{R_{LOAD} \cdot C_t \cdot (V_{in(rms)})^2}{24 \cdot L \cdot I_t \cdot V_{out,nom}} \right) \quad (\text{NCP1605})$$


- The power stage pole varies as a function of the load:

$$f_{p0} = \frac{n+2}{2\pi \cdot R_{LOAD} \cdot C_{bulk}} = \frac{2}{\pi \cdot R_{LOAD} \cdot C_{bulk}} \quad (\text{NCP1605})$$

- What is the worst case when closing the loop?


Load Influence on the Open Loop Plots

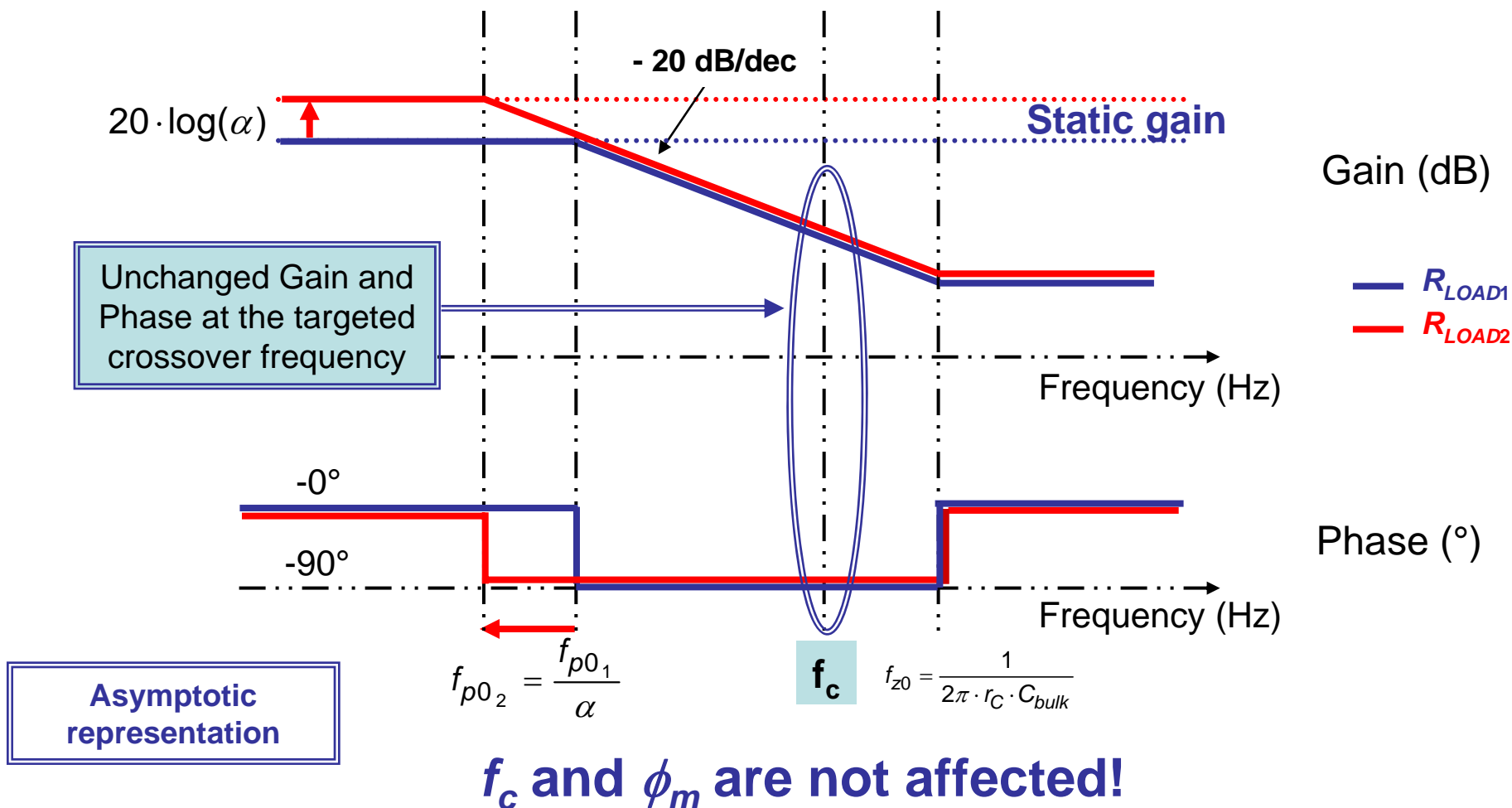- Let's increase R_{LOAD} ($R_{LOAD2} = \alpha \cdot R_{LOAD1}$ with $\alpha > 1$)



Line Influence on the Open Loop Plots

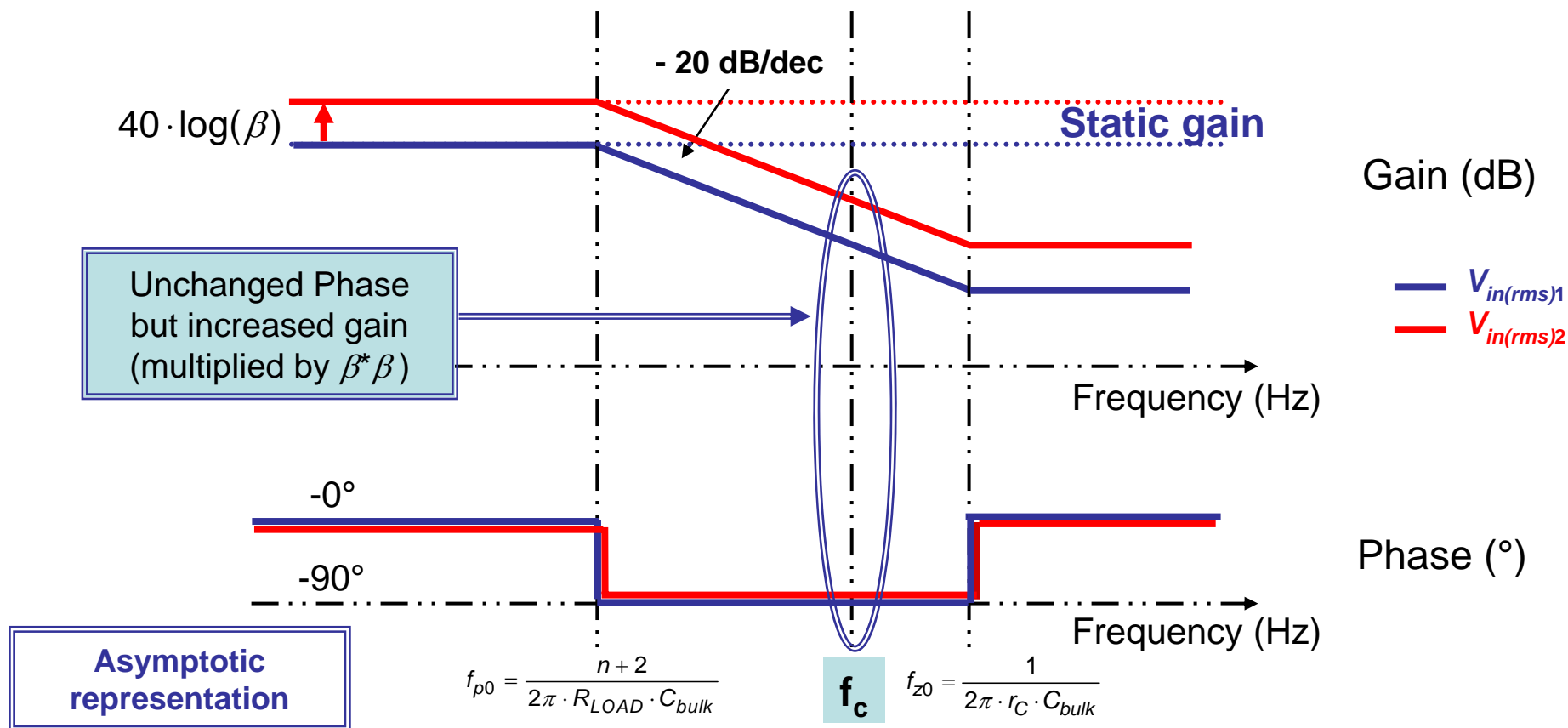- No feedforward (e.g. NCP1607) and $(V_{in(rms)2} = \beta \cdot V_{in(rms)1} \text{ with } \beta > 1)$



The loop crossover frequency is β^2 increased

Load and Line Considerations

- Compensate at full load
 - Same crossover frequency at lighter loads
 - The zero frequency is set optimally (not at a too low frequency)
- Compensate at high line
 - High line is the worst case as in the absence of feedforward, the static gain is proportional to $(V_{in(rms)})^2$

– This leads to:

$$(f_c)_{HL} = \left(\frac{(V_{in(rms)})_{HL}}{(V_{in(rms)})_{LL}} \right)^2 \cdot (f_c)_{LL}$$

Where HL stands for Highest Line and LL for Lowest Line

- In universal mains applications, the high-line crossover frequency is 9 times higher than the low-line one:

$$(f_c)_{HL} = \left(\frac{265}{90} \right)^2 \cdot (f_c)_{LL} \cong 9 \cdot (f_c)_{LL}$$

Crossover Frequency Selection

- In the absence of feedforward, $(f_c)_{HL} \leq f_{line}$ is a good option
- With feedforward, $(f_c)_{HL} \leq \frac{f_{line}}{2}$ is rather selected for a better attenuation of the low frequency ripple
- Get sure that on the line range, the PFC boost pole remains lower than the crossover frequency at full load!

$$f_{p0} \leq (f_c)_{LL}$$

- If not, increase C_{bulk}


Agenda

- Introduction
- Deriving a small-signal model
 - General method
 - Practical example: NCP1605-driven PFC stages
- **Compensating the loop**
 - Type-2 compensation
 - Influence of the line and power level
 - Computing the compensation
 - Practical example
- Conclusion

Compensation Techniques

- Several techniques exist:
 - manual placement, “k factor” (Venable)...
 - + Systematic
 - The PFC boost gain is to be computed at f_c
 - No flexibility in the zero and high pole locations $f_c = k \cdot f_{z1} = \frac{f_{p2}}{k}$
 - Pole and zero cancellation:
 - ✓ Place the compensation zero so that it cancels the power stage pole:
 - ✓ Force the pole at the origin to cancel the PFC boost gain when ($f = f_c$)
 - ✓ Adjust the phase margin with the high frequency pole

Pole and Zero Cancellation...

 

- The higher f_{p2} , the larger the phase margin
- The lower f_{p2} , the better the rejection of the low frequency ripple
- $\phi_m = 45^\circ$ if $f_{p2} = f_c$.

Poles and Zero Placement

- Design the compensation for full load, high line: $R_{LOAD} = R_{LOAD(min)}$

- Place the origin pole to cancel K_0 , the static gain at f_c :

$$f_{p0} = \frac{f_c}{K_0} \quad \text{for } R_{LOAD} = R_{LOAD(min)}$$

where:
$$\frac{\hat{V}_{out}}{\hat{V}_{CONTROL}} = K_0 \cdot \frac{1 + s \cdot r_C \cdot C_{bulk}}{1 + s \cdot \left(\frac{R_{LOAD(min)} \cdot C_{bulk}}{n + 2} \right)}$$

- Place the zero so that it cancels the PFC boost pole

$$(f_{z1} = f_{p0}) \quad \text{for } R_{LOAD} = R_{LOAD(min)}$$

- Place f_{p2} to obtain the targeted phase margin: $f_{p2} = \frac{f_c}{\tan(90^\circ - \phi_m)}$

Example

- A wide mains, 150-W application driven by the NCP1605
 - $V_{out,nom} = 390 \text{ V}$
 - $(V_{in(rms)})_{LL} = 90 \text{ V}$
 - $(V_{in(rms)})_{HL} = 265 \text{ V}$
 - $L = 150 \mu\text{H}$
 - $C_t = 4.7 \text{ nF}$
 - $C_{bulk} = 100 \mu\text{F}$
 - $r_C = 500 \text{ m}\Omega$ (ESR)
 - $f_c = 50 \text{ Hz}$
- and $\Phi_m = 60^\circ$
 @ high line (265 V)

$$\frac{\hat{V}_{out}}{\hat{V}_{CONTROL}} = K_0 \cdot \frac{1 + s \cdot r_C \cdot C_{bulk}}{1 + s \cdot \left(\frac{R_{LOAD} \cdot C_{bulk}}{4} \right)} \quad \text{where: } K_0 = \frac{R_{LOAD} \cdot C_t \cdot (V_{in(rms)})^2}{24 \cdot L \cdot I_t \cdot V_{out,nom}}$$

$$R_{LOAD(min)} = \frac{(V_{out,nom})^2}{(P_{out})_{max}} = \frac{390^2}{150} \cong 1 \text{ k}\Omega$$

$$R_0 = \frac{V_{out,nom}}{V_{ref} \cdot G_{EA}} = \frac{390}{2.5 \cdot 200 \cdot 10^{-6}} = 780 \text{ k}\Omega \quad (\text{OTA})$$

$$C_1 = \frac{K_{0(min)}}{2\pi \cdot f_c \cdot R_0} = \frac{R_{LOAD(min)} \cdot C_t \cdot (V_{in(rms)})_{HL}^2}{2\pi \cdot f_c \cdot R_0 \cdot 24 \cdot L \cdot I_t \cdot V_{out,nom}} = \frac{10^3 \cdot 4.7 \cdot 10^{-9} \cdot 265^2}{2\pi \cdot 50 \cdot 780 \text{ k} \cdot 24 \cdot 150 \mu \cdot 370 \mu \cdot 390} \cong 2.59 \mu\text{F} \implies 2.2 \mu\text{F}$$


$$R_1 = \frac{R_{LOAD(min)} \cdot C_{bulk}}{(n+2) \cdot C_1} = \frac{10^3 \cdot 100 \cdot 10^{-6}}{(2+2) \cdot 2.2 \cdot 10^{-6}} \cong 11.36 \text{ k}\Omega \implies 12 \text{ k}\Omega$$

$$C_2 = \frac{\tan(90^\circ - \phi_m)}{2\pi \cdot f_c \cdot R_1} = \frac{\tan(90^\circ - 60^\circ)}{2\pi \cdot 50 \cdot 12 \cdot 10^3} \cong 153 \text{ nF} \implies 150 \text{ nF}$$


$$f_{p1} = \frac{1}{2\pi \cdot R_0 \cdot C_1} = 93 \text{ mHz} \quad f_{z1} = \frac{1}{2\pi \cdot R_1 \cdot C_1} = 6 \text{ Hz} \quad f_{z2} = \frac{1}{2\pi \cdot R_1 \cdot C_2} = 88 \text{ Hz}$$

Simulation Validation

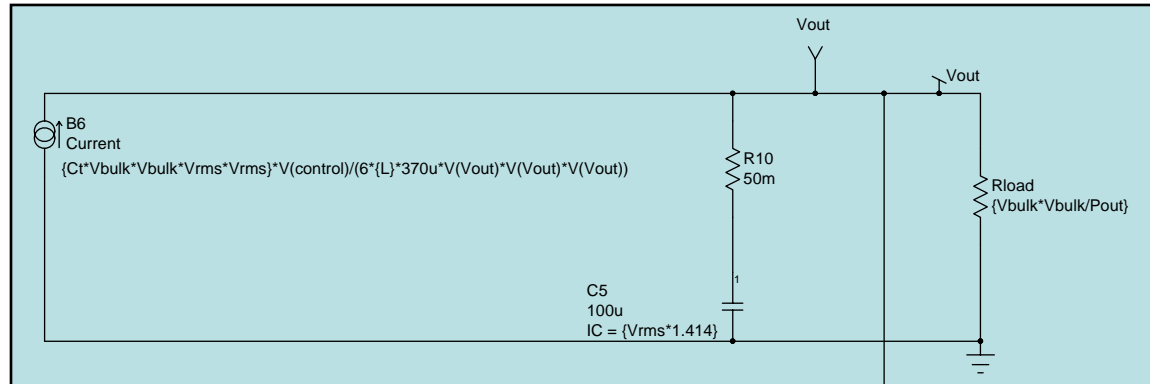
- The simulation circuit is based on the large signal model:



 ← Large signal model of the NCP1605-driven PFC stage




 ← Generation and injection of the ac perturbation




← Feedback and regulation circuit (including type-2 compensation)

Open Loop Characteristic – Full Load

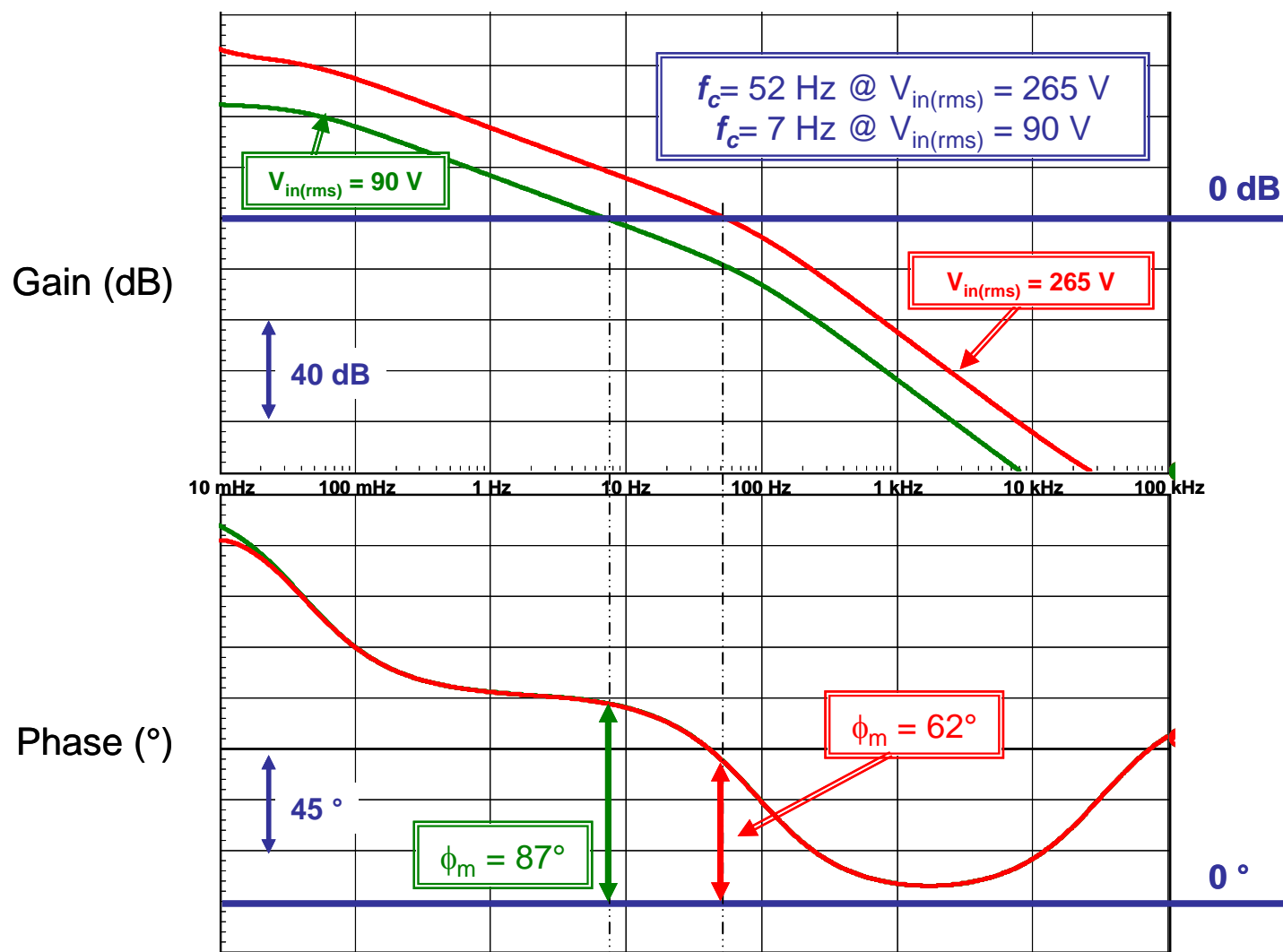


Open Loop Characteristic – Mid Load

 

Experimental Results at Full Load


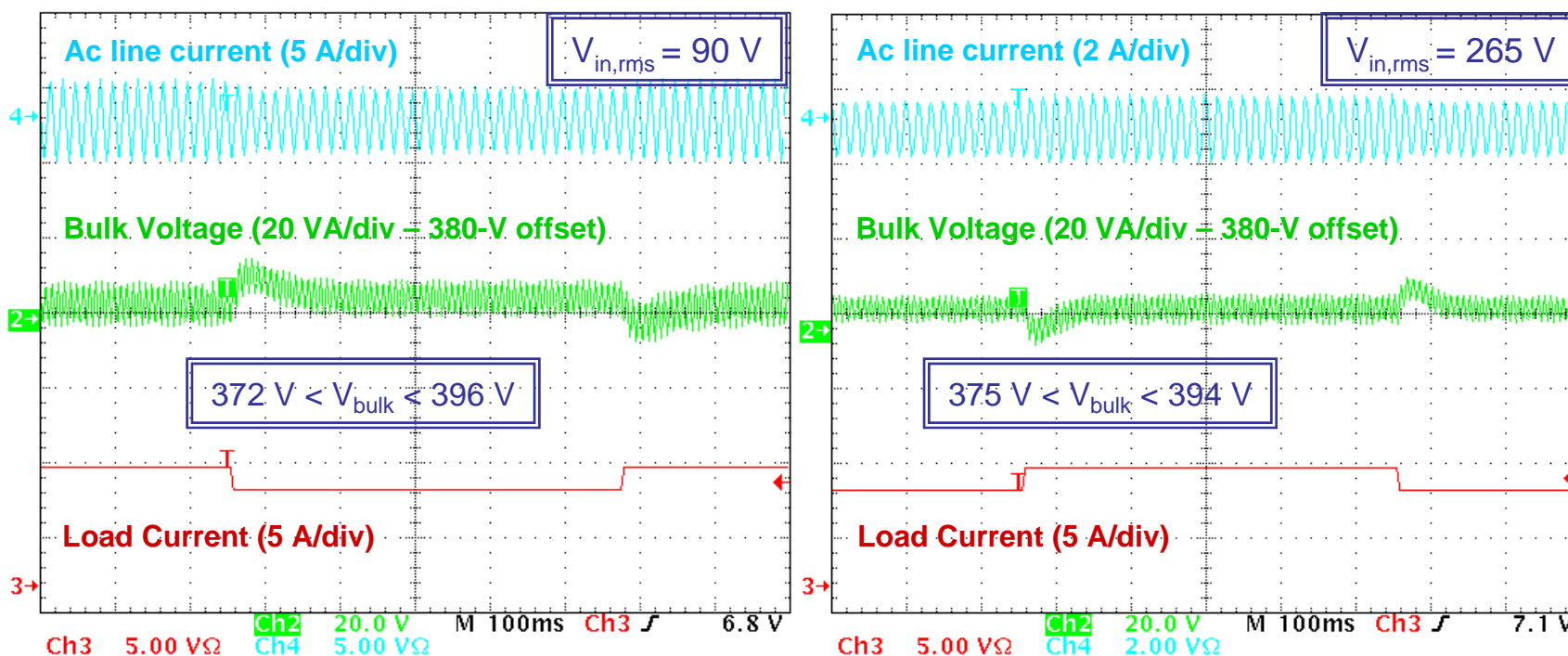
- A 19 V / 7 A loads the PFC stage
- The downstream converter swings between 6.3 A and 7.7 A (+/-10%) with a 2 A/ μ s slope



- The high-line, larger bandwidth reduces the V_{bulk} deviations and speeds-up the output voltage recovery

Experimental Results at Medium Load

 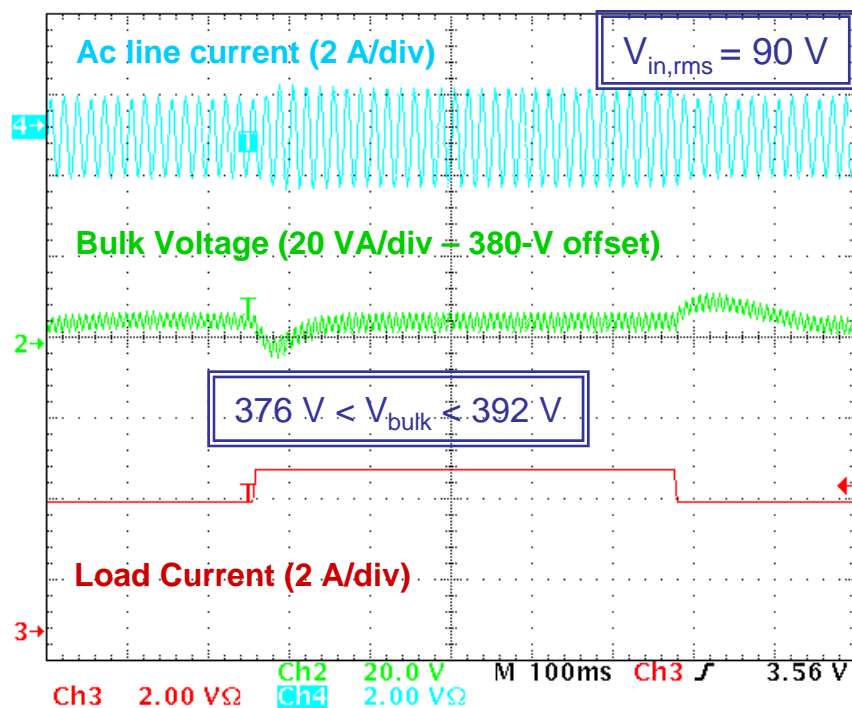
- A 19 V / 7 A loads the PFC stage
- The downstream converter swings between 3.1 A and 3.9 A (+/-10%) with a 2 A/ μ s slope



- The circuit still exhibits a first order response

Abrupt Load Changes

 - A 19 V / 7 A loads the PFC stage
- The downstream converter swings from 7.0 A to 3.5 A ($2 \text{ A}/\mu\text{s}$ slope)



The dynamic response enhancer speeds-up the loop reaction in case of a large undershoot
Implemented in NCP1605 (FCCrM), NCP1654 (CCM) and NCP1631 (Interleaved)

- The dynamic response enhancer reduces the undershoot at low line

Agenda

- Introduction
- Deriving a small-signal model
 - General method
 - Practical example: NCP1605-driven PFC stages
- Compensating the loop
 - Type-2 compensation
 - Influence of the line and power level
 - Computing the compensation
 - Practical example
- Conclusion

Conclusion

- General considerations were illustrated by the case of NCP1605-driven PFC stages
- A small signal model of PFC boosts can be easily derived
- The proposed method is independent of the operating mode
- A type-2 compensation is recommended
- If no feed-forward is implemented, the loop bandwidth and phase margin vary as a function of the line magnitude
- The crossover frequency does not vary as a function of the load
- A resistive load can be used for the computation even if the PFC stage feeds a power supply (negative impedance) – See back-up



For More Information

- View the extensive portfolio of power management products from ON Semiconductor at www.onsemi.com
- View reference designs, design notes, and other material supporting the design of highly efficient power supplies at www.onsemi.com/powersupplies

