

# ON Semiconductor

## Is Now

# onsemi™

To learn more about onsemi™, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

---

**onsemi** and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



**ON Semiconductor®**

# **Dv/dt Induced False Turn-on Issue in 4-Switch Noninverting Buck-Boost Converters**



ON Semiconductor®

## A Gate Drive Design Considerations

USB has evolved from a data interface capable of supplying limited power, to a primary provider of power with a data interface. The latest USB 3.x protocol supports power flow at a much higher level. With a default 5 V voltage, the USB-C port is capable of negotiating with a plugged-in device to raise the port voltage up to 20 V.

A unique challenge in the new power delivery requirement is how to use a 4.5 V–32 V battery voltage to provide a 5 V–20 V DC bus. A 4-switch buck-boost converter is a suitable topology to provide the buck or boost power conversion, because it provides a wide voltage conversion range, positive polarity, high efficiency and a small form factor solution size that designers and customers require.

The power stage of noninverting buck–boost converter consists of four switching devices and an inductor. As shown in Fig. 1, the four switches are grouped into a buck phase (S1 & S2) and a boost phase (S3 & S4). There is one active switch and one rectifying switch in each phase. When using a controller such as ON Semiconductor’s NCP81239 controller, this topology can operate in either synchronous buck or synchronous boost mode.


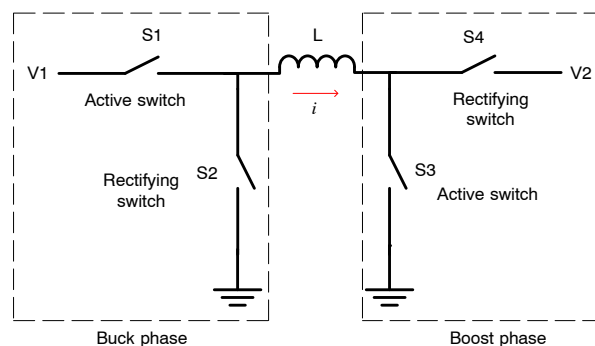


Figure 1. Diagram of a Noninverting Buck-boost Converter


## dv/dt Induced False Turn On

In synchronous buck converters, there is a well-known phenomenon called “low side false turn-on,” or “dv/dt induced turn on”, which can be potentially dangerous for the switch itself and the reliability of the entire converter. It occurs when the high-side (active) switch turns on and the drain-to-source voltage of the low-side (rectifying) switch increases rapidly. This sudden voltage increase changes the voltage across the parasitic capacitance (Miller capacitance,  $C_{gd}$ ) between the drain and the gate, and develops displacement current of  $C \times dv/dt$ . If a voltage exceeding  $V_{gs(th)}$  develops between the gate and source due to the displacement current, it triggers a false turn on of the rectifying switch. The equivalent circuit is shown in Figure 2 and the waveform is shown in Figure 3.


There is limited published information on the dv/dt induced false turn-on problem in a noninverting buck-boost converter, so it is a topic that could benefit from some explanation and demystifying. Errors are made when designers simply copy the circuit parameters of a buck converter directly to the phases of a noninverting buck-boost converter. As this topology gains more popularity in applications, the dv/dt induced turn on issue is becoming more important to understand.

 

**Figure 2. Buck Phase False Turn-on Equivalent Circuit of a Noninverting Buck-boost Converter**

 

**Figure 3. dv/dt Induced False Turn-On Waveform In Normal Operation**

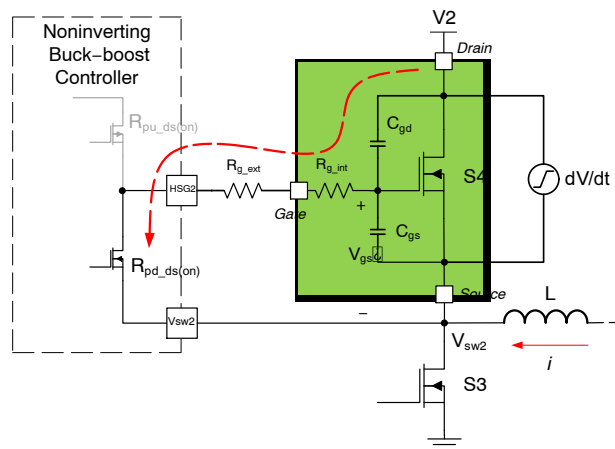

**Figure 4. Boost Phase False Turn-on Equivalent Circuit of a Noninverting Buck-Boost Converter**

Figure 4 shows a high-side MOSFET of the boost phase of a noninverting buck-boost converter at the moment a positive  $dv/dt$  transition appears across the drain-to-source junction. When the low-side MOSFET turns on, the voltage across the drain-to-source of the high-side MOSFET increases rapidly. In off state, a sudden increase in drain voltage changes the voltage across the Miller capacitance ( $C_{gd}$ ) between the drain and the gate, and develops displacement current of  $C \cdot dv/dt$ . If voltage exceeding  $V_{gs(th)}$  develops between the gate and source due to the displacement current, it generates a false turn-on signal for the MOSFET. As a result, the MOSFET can be partially turned on, creating a low-resistance path between supply voltage and GND. In severe cases, high power dissipation can develop in the device and results in destructive failure.

Equation (1) shows the voltage across the gate and source in this mode. It is assumed that  $dt/C_{gs} \gg R_{pd\_ds(on)} + R_{g\_ext} + R_{g\_int}$ , most of the displacement current through  $C_{gd}$  would ideally flow out of the gate into the gate driver resistors.

$$V_{gs'} \approx (R_{pd\_ds(on)} + R_{g\_ext} + R_{g\_int}) \times C_{gd} \times \frac{dV}{dt} \quad (\text{eq. 1})$$

If  $V_{gs'}$  is lower than the turn on threshold voltage  $V_{gs(th)}$ , the MOSFET will not turn on. Therefore, the design goal is to limit this  $dv/dt$  induced voltage to a maximum of  $V_{gs(th)}$  under all conditions. Equation (2) shows the approach:

$$(R_{pd\_ds(on)} + R_{g\_ext} + R_{g\_int}) \times C_{gd} \times \frac{dV}{dt} < V_{gs(th)} \quad (\text{eq. 2})$$

Note that there are several variables we can tune to satisfy (2).  $R_{pd\_ds(on)}$  is from the controller.  $R_{g\_int}$  and  $C_{gd}$  are from the MOSFET. They cannot be controlled once the parts are selected.

Therefore, to increase the converter's  $dv/dt$  immunity, a gate drive circuit with very low impedance should be used and higher  $V_{gs(th)}$  is preferred. In a drive circuit with low impedance, the cost is high and increasing the  $V_{gs(th)}$  is associated with rise in  $R_{ds(on)}$ . As  $V_{gs(th)}$  has a negative temperature coefficient, the possibility of a false turn-on increases as the temperature rises. Typically, gate voltage doesn't go over the threshold voltage and the high device resistance limits the device current. Device destruction due to false turn-on is rare.

### Special Case: Light Load and Low Ripple Current Condition

The analysis above is based on the assumption that the inductor current is large enough to discharge the its parasitic capacitor before the rectifying switch turns on, so that the active switch turn on is hard switching and the rectifying switch turn on is soft switching. The minimum inductor current to fully discharge the capacitor is given by:


$$I_{s\_min} \geq (C_{oss1} + C_{oss2}) \times V_1/t_{dead} \quad (\text{eq. 3})$$

Where  $I_{s\_min}$  is the inductor current when the active switch turns off.  $C_{oss1/2}$  is the output capacitance of the switch and  $t_{dead}$  is the dead-time between active switch's turn-off and rectifying switch's turn-on.


A special case appears when (3) is not satisfied. That is when the input and output voltage are close to each other and the load is close to 0. In this situation, the inductor current is too small to fully discharge the output capacitor of the switches. Take the Buck phase for example, in this case, the drain-to-source voltage of the low-side (rectifying) switch is still high at the moment the synchronous rectifying switch turns on. Therefore this voltage is yanked down to 0 rapidly when the rectifying switch turns on. As a result, in complementary, the D-S voltage of the active switch increases to  $V_1$  rapidly. This sudden voltage increase (high  $dv/dt$ ) applied to the parasitic capacitance (Miller capacitance,  $C_{gd}$ ) between drain and gate develops a displacement current of  $i = C_{gd} \times dv/dt$ . If the gate voltage developed by the displacement current exceeds  $V_{gs(th)}$ , a false turn on of the active switch can be triggered.

Similarly, when the active switch turns on, the  $dv/dt$  induced false turn on issue still exists, which means we will see a false turn on bump on the gate of rectifying switch when the active switch turns on. The waveform is shown in Figure 5. The analysis is verified by simulation results shown in Figure 6.

The analysis of Boost phase in special case is similar. It will not be discussed in this paper.

 

**Figure 5.  $dv/dt$  Induced False Turn-On Waveform of Light Load and Low Ripple Current Condition**

 

**Figure 6. Simulation Results of Light Load and Low Ripple Current Condition**


## dv/dt slew rate reduction

Equation (2) has provided us the guidelines to resolve this issue. Since it is caused by dv/dt, a first intuitive method is to reduce the dv/dt. The implementation of dv/dt control can be easily done by tuning the gate driver circuit. The active switch's pull up resistance and external gate resistance should be larger than those of the rectifying switch. This would slow down the turn on of the active switch, thus effectively decreasing the dv/dt component of (2).

Figure 7(a) shows a false turn on voltage of 1.9 V at the switching node dv/dt equals to 1.5 V/ns. Figure 7(b) has a reduced false turn on peak voltage to 1.0 V with a 0.75 V/ns dv/dt. It is verified that the magnitude of the false turn on issue can be mitigated by tuning the external gate resistor which affects the dv/dt.

A second solution is to add an RC snubber circuit to the switching node  $V_{sw1}$  and  $V_{sw2}$ . This is the most direct way to decrease the dv/dt value. The side effect of the method is that the losses will increase.

Last but not least, the dead-time of the rectifying switch turn-off edge to active switch turn-on edge should be also taken care of although it is not shown in (2). Although the dead-time doesn't directly affects the magnitude of the false turn on, it helps to guarantee that the rectifying switch gate voltage drops to zero before turning on the active switch. Noted that even if you set it long enough, the dv/dt induced turn on is still there when the active switch turns on.

 

**Figure 7. Gate Signal and Switching Node dv/dt with Different External Gate Resistors (a)  $R_{g\_s3} = 0 \Omega$ ,  $R_{g\_s4} = 3.3 \Omega$ ; (b)  $R_{g\_s3} = 3.3 \Omega$ ,  $R_{g\_s4} = 0 \Omega$**



## MOSFET Selection

Selecting the right MOSFET can also help to reduce the effect of the  $dv/dt$  induced turn-on problem. One solution would be to select the MOSFETs with high gate threshold voltage, but this may lead to increased  $R_{ds(on)}$ .

In order to prevent  $dv/dt$  induced turn-on, the criteria for selecting a rectifying switch would be based on the  $Q_{gd}/Q_{gs(th)}$  ratio.  $Q_{gs(th)}$  is the gate-to-source charge before the gate voltage reaches the threshold voltage. According to (2), lowering  $C_{gd}$  will reduce  $dv/dt$  induced voltage magnitude. Moreover, it also depends on  $dt/C_{gs}$ ,  $V_{ds}$  and threshold voltage  $V_{th}$ . One way of interpreting the  $dv/dt$  induced turn-on problem is when  $V_{ds}$  reaches the input voltage, the Miller charge should be smaller than the total charge on  $C_{gs}$  at the  $V_{th}$  level, so that the rectifying switches will not be turned on. Then we will have the following relation:

$$V_{gs} = \frac{C_{gd}}{C_{gd} + C_{gs}} \times V_{ds} < V_{gs(th)} \quad (\text{eq. 4})$$

$$Q_{gd} < Q_{gs(th)} \quad (\text{eq. 5})$$

We can simply use gate charges to evaluate the rectifying device's immunity to  $dv/dt$  induced turn on. Ideally, the charge  $Q_{gd}$  should not be greater than  $Q_{gs(th)}$  in order to leave enough margin.


## Alternative Driver Circuit Design

According to (2), the gate drive resistance  $R_{g\_ext}$  should be kept small in order to make the magnitude of the  $dv/dt$  induced false turn-on voltage low. As a result, the rectifying switch turn on and off fast, which is not an issue if it is soft switching. However, as discussed above in the special case, it will cause a false turn on bump if soft switching is not realized.

Some controllers provide an open drain and open source configuration, as shown in Figure 8. It enables customers to control the turn on and turn off speed independently.

In addition to the external gate resistance, the gate drive circuit inside the controller should be reviewed too. Similar to the consideration of  $R_{g\_ext}$ , the internal pull down resistance for the rectifying switch should be small as well.

There are several other complicated drive circuit techniques such as negative turn off voltage which need extra components. They are not covered in this article.

 


**Figure 8. Different Gate Resistance for Turn on and Turn off**


### Gate Drive Design Considerations for Special Case

As discussed in previous sections, the gate drive circuit for light load and low current ripple condition requires small HS gate resistor and large LS gate resistor, which is right the opposite of the requirement for normal operations. Therefore a tradeoff between normal and special case operation should be considered. The HS gate resistor can be replaced by a resistor in series with the boost-strap capacitor. The LS gate resistor should be kept 0. Moreover, the MOSFET selection for active switch should also follow the instructions given in the MOSFET selection section.

Figure 9(a) shows the simulated HS turn off to LS turn on waveform. Figure 9(b) shows the simulated LS turn off to HS turn on waveform. None of the  $dv/dt$  induced false turn-on bump exceeds the MOSFET turn on threshold.

 

**Figure 9. Simulated Improved Switching Waveform of Light Load and Low Ripple Current Condition**

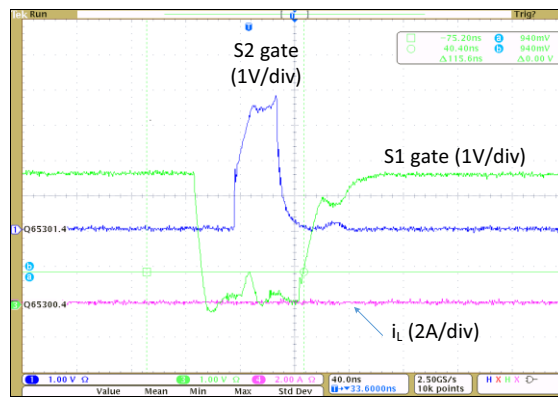


**Figure 10. Experimental Improved Switching Waveform of Light Load and Low Ripple Current Condition**

## Conclusion

Dv/dt induced turn on in a noninverting buck–boost converter is caused by a rapidly rising drain–source voltage at the synchronous rectifying MOSFET in both the buck phase and boost phase. To make things worse, both the active and the synchronous rectifying switch can suffer from this issue in the case where the load current and ripple current are small. As a result, the overall system efficiency deteriorates because of the undesired shoot through currents flowing in either phase leg. Several economical circuit solutions are available to the power supply designers, these include: minimizing rectifying switch turn off gate drive resistance, increasing the active switch turn on gate drive resistance, or adding RC snubber circuit to the switching nodes. Choosing MOSFETs with small  $Q_{gd}/Q_{gs(th)}$  ratio and high threshold voltage can also decrease dv/dt induced false turn on possibility.

## Reference:

- [1] Application Note [AN-9010/D](#), MOSFET Basics, Fairchild Semiconductor.
- [2] Jon Klein. Application Note AN-6003/D, “Shoot-through” in Synchronous Buck Converters, Fairchild Semiconductor.
- [3] Application Note [AND9419/D](#), Methods to Identify Shoot Through in Fast Switching VRM Applications, ON Semiconductor
- [4] Steve Mappus. “DV/DT Immunity Improved in Synchronous buck Converters”, Power Electronics Technology, pp30–36, July 2005
- [5] Thomas Wu. “CDV/DT induced Turn-on in Synchronous Buck Regulators”, International Rectifier.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)

**Order Literature:** <http://www.onsemi.com/orderlit>

For additional information, please contact your local Sales Representative