



Is Now Part of



**ON Semiconductor®**

To learn more about ON Semiconductor, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

# AN-4190

## Improve Flicker Performance of Direct AC Driven LED Fixtures with Self Valley Fill

### Introduction

To provide power to LED loads from AC input, Switch-Mode Power Supplies (SMPS) are generally used since LED need to be driven by regulated current. Consequently, LED lighting solution have to inherit the design complexity of a typical SMPS which includes designing the magnetic component, handling of Electromagnetic Interferences (EMI) as well as implementing Power Factor Correction (PFC). Direct-AC Drivers (DACD) for LEDs provides a new way to drive the LED load from an AC input with much simpler system architecture while satisfying EMI and power factor (PF) requirements with minimal effort. However, its drawback is flickering of light output at the zero crossing of AC line voltage due to loss of current to the LED load.

Though flicker is not always obvious, it can still cause headaches for a small percentage of people exposed to flickering lights for long periods [1]. This is a major issue for offices, schools, stores and other brightly lit commercial and industrial spaces where people spend a lot of time.

While there are currently no official standards governing flicker, most manufacturers and customers accept the US Energy Star recommended method for calculating Flicker Index. [2] [3]

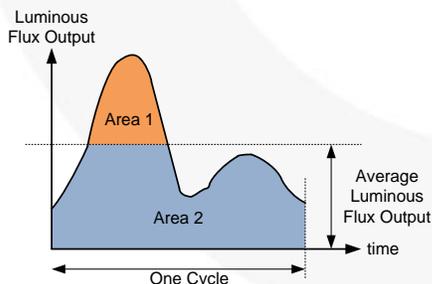


Figure 1. Definition of Flicker Index

For a periodic variation in luminous flux output as shown in Figure 1, the definition of Flicker Index (F.I.) is:

$$F.I. \equiv \frac{\text{Area 1}}{\text{Area 1} + \text{Area 2}} \quad (1)$$

In practice, F.I. below 0.15 is considered imperceptible so, naturally, lighting manufacturers aim to achieve or surpass this.

To deal with flickering, energy-storage devices are required. Capacitor is a kind of energy-storage device. A straightforward idea of applying capacitors in DACD systems is adding a valley-fill circuit to its front end, as shown in Figure 2. But, the drawback of this architecture is that input current will be distorted, which leads to degraded PF and Total Harmonic Distortion (THD). Reason of the distortion is that charging and discharging of the capacitors in valley-fill circuit change shape of input-current waveform, which is originally very close to a sinusoidal wave in-phase with input voltage for DACD systems. For example, the waveform in Figure 3 comes with THD of 21.77%. Without the valley-fill front end, THD could be as low as 11.36%.

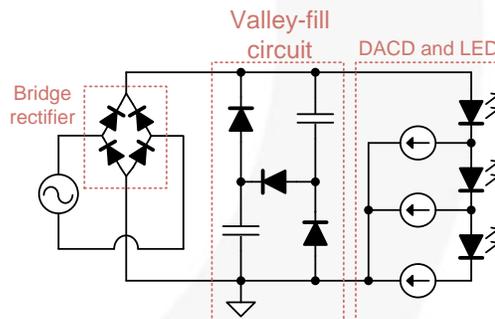


Figure 2. Traditional Valley-fill Circuitry with a DACD System

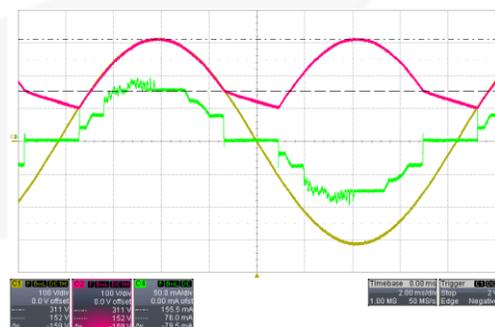


Figure 3. Waveform of DACD System with Traditional Valley-Fill Circuit (Ch1: AC Input Voltage, Ch2: Output of Valley-Fill Circuit, Ch4: AC Input Current)

This application note now proposes a new proprietary method called Self Valley Fill (SVF) which achieves low flicker, high PF and low THD at the same time, as well as outlines its practical design considerations.

### Concept of Self Valley Fill (SVF)

A typical SVF circuitry is shown in Figure 4. Originally the driver IC regulates input current to drive the LEDs. With added capacitors in the SVF circuit, the input current charges capacitor and drives LEDs simultaneously. The charged capacitors also supply LEDs when regulated driving current is cut off. Thus, LED currents get smoothed without distorting the AC input current shape. As a result, flickering of light output is reduced while maintaining high PF and THD performance.

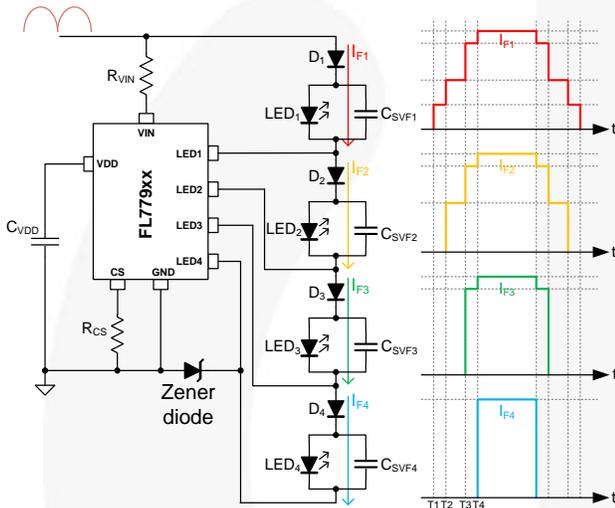


Figure 4. Self Valley Fill in a DACD System

For simplicity, the operation of the Self Valley Fill circuit is explained using one of the LED segments as an example as shown in Figure 5. Before the SVF capacitor,  $C_{SVFi}$ , is applied, the circuitry is no difference than general DACD system. When anode voltage of LEDi,  $V_{Ai}$ , is higher than forward-voltage summation of  $D_i$  and LEDi,  $I_{DRVi}$  starts conducting a regulated current until  $V_{Ai}$  drops below the summation of forward voltages.

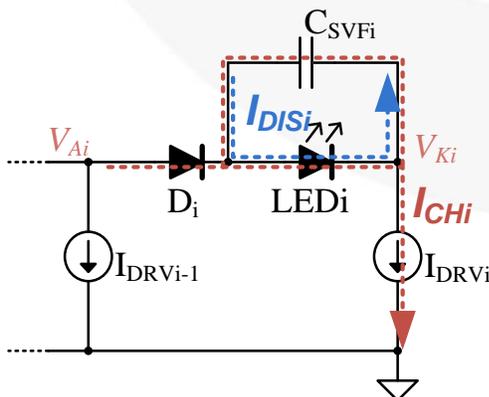


Figure 5. Self Valley Fill In One LED Segment

When the SVF capacitor is applied in the circuitry,  $I_{DRVi}$  not only drives LEDi but also charges  $C_{SVFi}$  simultaneously. Current flowing through LEDi is less than  $I_{DRVi}$  since part of the current is used to charge  $C_{SVFi}$ .  $C_{SVFi}$  will be charged up to around forward voltage of LEDi,  $V_{F-LEDi}$ , since the LED clamps voltage on the capacitor. Once  $I_{DRVi}$  is cut off, voltage accumulated on  $C_{SVFi}$  supplies LEDi until  $V_{CSVFi}$  is discharged to threshold forward voltage of LEDi. The threshold forward voltage means the forward voltage of the LED when its forward current is extremely close to zero.

From the description above, two facts can be concluded. First, since voltage on the SVF capacitor is kept around forward voltage of its parallel-connected LED, behavior of the driving current ( $I_{DRVi}$ ) will be the same. That is, when anode voltage of the LED group exceeds the LED group’s forward voltage, current starts to flow. The current ceases when the anode voltage decreases to lower than the forward voltage. As a result, input current will be almost identical to the without-SVF case. Second, LED current will be smoothed since driving current is shared to charge the capacitor and the capacitor supplies LED when driving current is absent.

The purpose of the additional diode  $D_i$  is to avoid charges on  $C_{SVFi}$  is wrongly discharged by driving current of its previous tap,  $I_{DRVi-1}$ . Note that  $D_i$  can also be an LED.

### Evaluate Required Capacitance of Self Valley Fill in a Simplified System

In this section, we try to show an analytical estimation of how effective the SVF will be with a specific capacitance, so that we can evaluate how big the capacitance should be. To simplify the system, let’s focus on a circuit like shown in Figure 5, which is redrawn in Figure 6 with its driving current waveform. The driving current has a periodic rectangular waveform with amplitude  $I_{DRV}$  and on-time  $t_{ON}$  in each period.

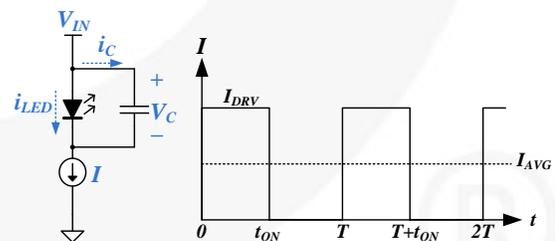



Figure 6. Simplified Schematic of SVF In One LED Segment

Without the capacitor, the driving current is equal to LED current. Average driving current in this case is:

$$I_{AVG} = \frac{I_{DRV} \cdot t_{ON}}{T} \tag{2}$$

Assume luminous flux is proportional driving current. Based on the definition, flicker index in this situation is:

$$F.I. |_{\text{noSVF}} = \frac{(I_{DRV} - I_{AVG}) \cdot t_{ON}}{I_{DRV} \cdot t_{ON}} \quad (3)$$

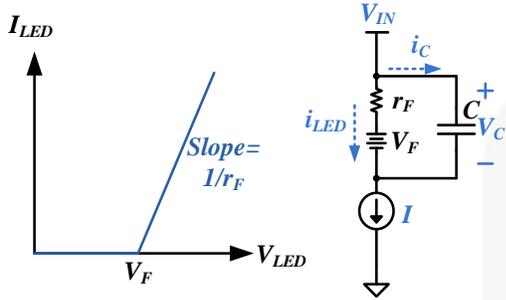

**Figure 7. Simplified LED Model with SVF Circuit**


When the SVF capacitor is added, actual LED current depends on V-I characteristics of the LED. Assume the LED can be modeled as a fixed voltage drop with a series resistor as shown in Figure 7. Assuming voltage on the SVF capacitor is always higher than  $V_F$ , LED current over one period can be calculated through circuit analysis.

$$i_{LED}(t) = \begin{cases} \frac{1 - e^{-\frac{T-t_{ON}}{r_F \cdot C}}}{1 - e^{-\frac{T}{r_F \cdot C}}} \cdot I_{DRV} \cdot e^{-\frac{t}{r_F \cdot C}} + I_{DRV} & \text{for } t \in [0, t_{ON}] \\ \frac{1 - e^{-\frac{t_{ON}}{r_F \cdot C}}}{1 - e^{-\frac{T}{r_F \cdot C}}} \cdot I_{DRV} \cdot e^{-\frac{t-t_{ON}}{r_F \cdot C}} & \text{for } t \in [t_{ON}, T] \end{cases} \quad (4)$$


Based on same assumption as in (3), flicker index of this condition can be calculated as:

$$F.I. |_{\text{SVF}} = \frac{(I_{DRV} - I_{AVG}) \cdot t_{ON}}{I_{DRV} \cdot t_{ON}} + \frac{r_F \cdot C}{t_{ON}} \cdot \ln \left( \frac{T - t_{ON}}{T} \cdot \frac{1 - e^{-\frac{T}{r_F \cdot C}}}{1 - e^{-\frac{T-t_{ON}}{r_F \cdot C}}} \right) - \frac{r_F \cdot C}{T} \cdot \ln \left( \frac{T - t_{ON}}{t_{ON}} \cdot \frac{1 - e^{-\frac{t_{ON}}{r_F \cdot C}}}{1 - e^{-\frac{T-t_{ON}}{r_F \cdot C}}} \right) \quad (5)$$

The equation is a little bit complicated to interpret. Let assume a case with  $r_F = 150 \Omega$ ,  $T = 8.33 \text{ ms}$ ,  $t_{ON} = 0.56T$ ,  $I_{DRV} = 71 \text{ mA}$ . Flicker Index can be represented as a function of the SVF capacitance as in Figure 8. Figure 8 shows that if SVF capacitance is larger, Flicker Index will be lowered. When there is no SVF capacitor, Flicker Index is 0.44 according to (3). While  $47\text{-}\mu\text{F}$  SVF capacitor is implemented in this case, F.I. can be as low as 0.06. Driving current and LED current under  $47\text{-}\mu\text{F}$  SVF capacitance are shown in Figure 9.

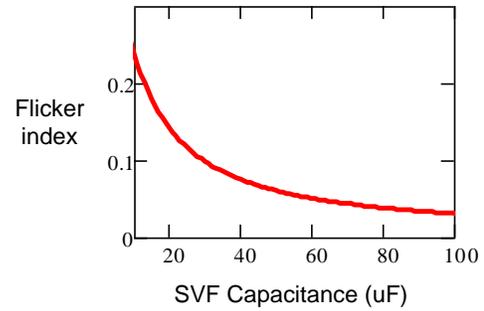

**Figure 8. Flicker Index vs. SVF Capacitance**

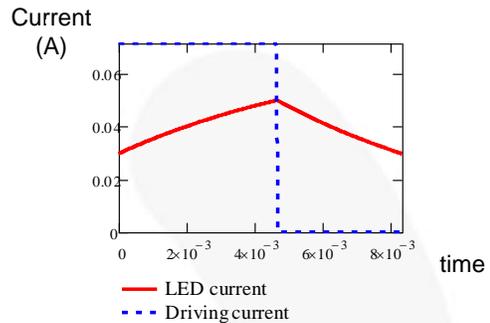


**Figure 9. Driving Current and LED Current of Simplified SVF Circuit with 100- $\mu\text{F}$  Capacitance**

# Evaluation and Measurement of a Practical DACD system with SVF

Figure 10 shows a schematic of a DACD system with SVF for reduction of flickering. It is actually schematic of the evaluation board “[FEBFL77944\\_L80H012B](#)” [4].

Calculation process of current and timing parameters of the same system without SVF can be referred to design example in FL77944’s application note [5]. It is a system designed for 220 V<sub>AC</sub> input and input wattage is 12 W. Key parameters used in this section are listed in Table 1.

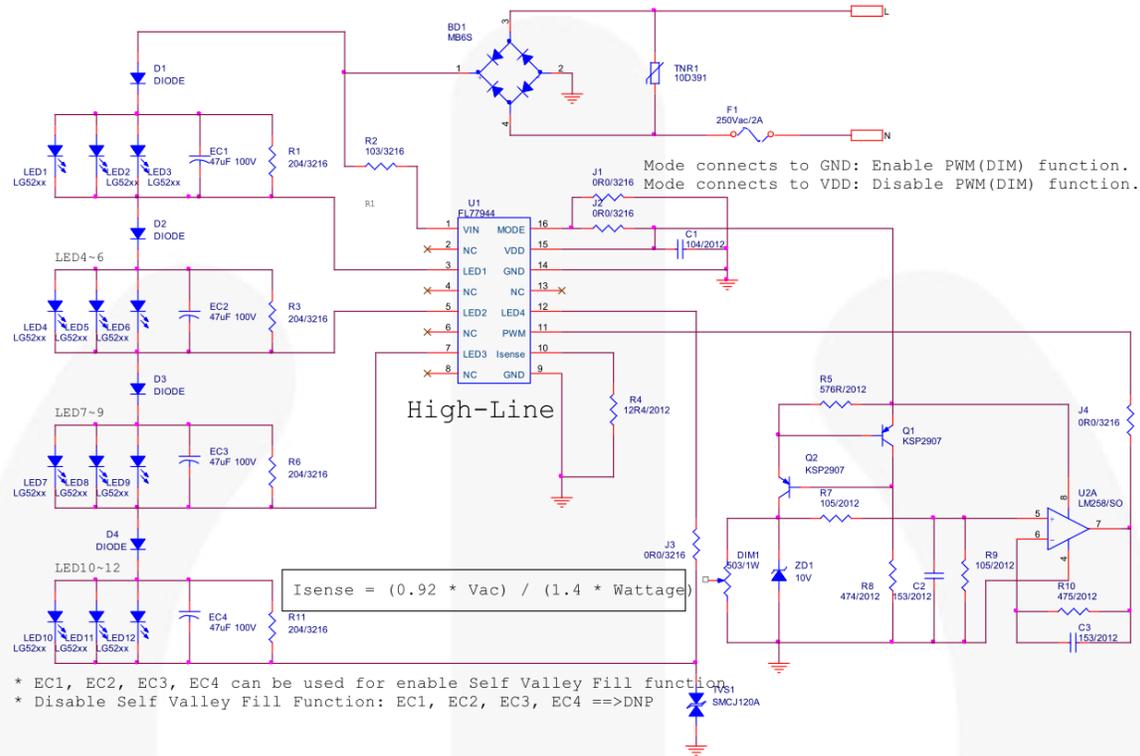


**Figure 10. Schematic of FL77944 Evaluation Board with SVF**

**Table 1. Key Parameters of the Design Example**

Parameter	Number	Unit
T	1/120	ms
I <sub>LED1</sub>	14.5	mA
I <sub>LED2</sub>	29.8	mA
I <sub>LED3</sub>	66.9	mA
I <sub>LED4</sub>	74.1	mA
T <sub>1</sub>	0.51	ms
T <sub>2</sub>	1.08	ms
T <sub>3</sub>	1.84	ms
T <sub>4</sub>	2.75	ms
I <sub>F1,AVG</sub>	47.22	mA
I <sub>F2,AVG</sub>	45.24	mA
I <sub>F3,AVG</sub>	39.8	mA
I <sub>F4,AVG</sub>	25.2	mA

To apply the equations derived above, the current waveforms I<sub>F1-4</sub> are simplified as in Figure 11. Average values of the original and simplified waveforms are the same. The t<sub>ON</sub> of the simplified waveform is equal to time duration that its original waveform is higher than its average value. Turning-on moment of the simplified waveforms is

aligned to t=0. t<sub>ON</sub> and I<sub>DRV</sub> of each group are listed in Table 2.

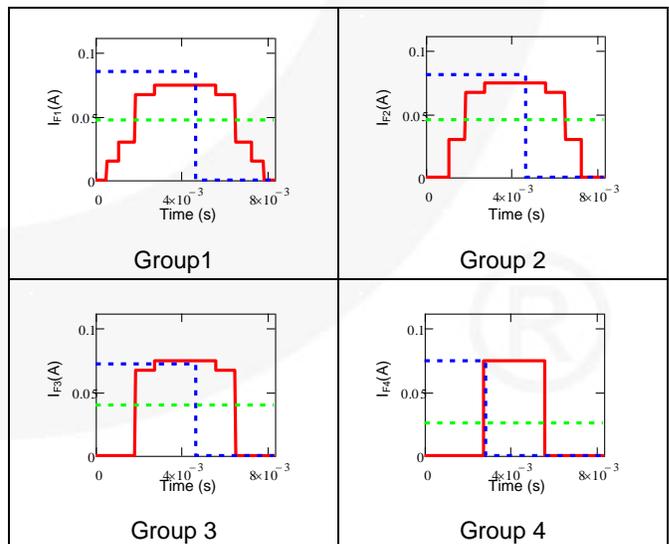


**Figure 11. LED Group Current in Half AC Period (RED: Original, Blue: Simplified, Green: Average)**

**Table 2. Parameters of the Simplified Current Waveform**

Parameter	Number	Unit
t <sub>ON1</sub>	4.65	ms
t <sub>ON2</sub>	4.65	ms
t <sub>ON3</sub>	4.65	ms
t <sub>ON4</sub>	2.83	ms
I <sub>DRV1</sub>	85	mA
I <sub>DRV2</sub>	81	mA
I <sub>DRV3</sub>	71	mA
I <sub>DRV4</sub>	74	mA

The LEDs implemented in this system has V-I curve as shown in Figure 12. It can be modeled as a fixed 55.56-V voltage drop plus a series 450-Ω resistor. Since there are three LEDs put in parallel for each LED group, the effective resistance is 150 Ω.

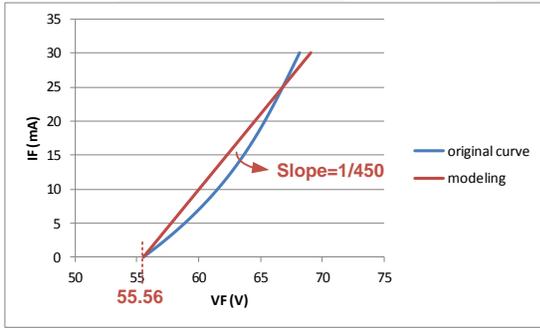


**Figure 12. V-I Curve of the LED**

t<sub>ON</sub>, I<sub>DRV</sub>, I<sub>AVG</sub>, and r<sub>F</sub> of each LED group are now calculated. So, we can have Flicker Index of each LED group according to (5). For Flicker Index of the whole system, we can simply evaluate it by weighted sum of each LED group’s Flicker Index according to their average current.

$$I_{AVG.TOTAL} = I_{AVG.F1} + I_{AVG.F2} + I_{AVG.F3} + I_{AVG.F4} \quad (6)$$


$$F.I|_{\text{wholesystem}} = F.I|_{\substack{SVF \\ I_{DRV2} \\ I_{AVG.F1} \\ T_{ON1}}} \cdot \frac{I_{AVG.F1}}{I_{AVG.TOTAL}} + F.I|_{\substack{SVF \\ I_{DRV2} \\ I_{AVG.F2} \\ T_{ON2}}} \cdot \frac{I_{AVG.F2}}{I_{AVG.TOTAL}} + F.I|_{\substack{SVF \\ I_{DRV3} \\ I_{AVG.F3} \\ T_{ON3}}} \cdot \frac{I_{AVG.F3}}{I_{AVG.TOTAL}} + F.I|_{\substack{SVF \\ I_{DRV4} \\ I_{AVG.F4} \\ T_{ON4}}} \cdot \frac{I_{AVG.F4}}{I_{AVG.TOTAL}} \quad (7)$$

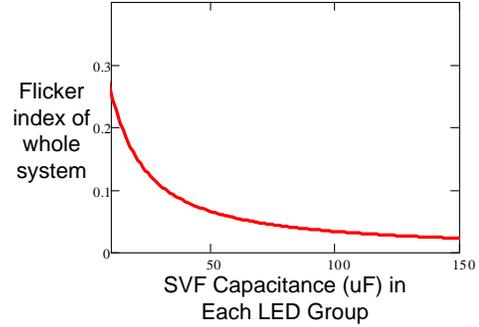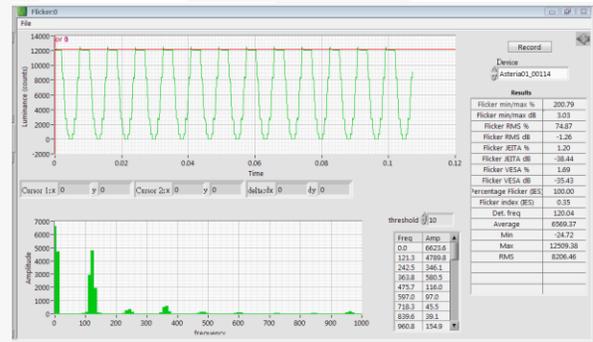Assuming same capacitance is applied in every LED group, Flicker Index versus the capacitance can be drawn as Figure 13. It indicates that Flicker Index is 0.069 when 47-μF capacitor is applied in each LED group.

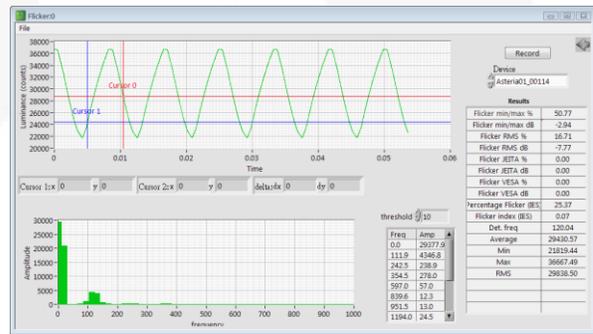


**Figure 13. Flicker Index vs. SVF Capacitance of the Design Example**

Figure 14 shows measurement result from a light meter. The “without SVF” means to simply remove the capacitors from the circuit. It can be seen that SVF improves Flicker Index from 0.35 to 0.07 in this design.



**(a) Without SVF**



**(b) With SVF**

**Figure 14. Measurement result of SVF with Light Meter**

This section shows a design example and its experiment result. The equations derived in previous section are extended to a much complicated system. There are assumptions and approximations when applying the equations.

For more complicated designs or more accurate results, the assumptions and approximations of this section may not be appropriate. For example, the capacitor may not be large enough to make the LED current not cut off, or the first-order approximation of the LED model may not be accurate enough. Since currents in LED and capacitor depend on each other, the calculation process is complicated. Computer simulation or mathematical software may be required for

design estimation. A [Design Tool](#) has been provided to assist in designing SVF capacitors [6].

If those kinds of tools are not available, the design can also be done through experimenting with different capacitances and measuring the Flicker Index directly with hardware.

## Practical Design Considerations along with SVF

### To Design by Trial

DACD system is generally designed as evenly separated LED groups, which means effective forward voltage of each LED group is identical. A simple way to design the SVF capacitance of this kind of system is to put identical capacitors to each LED group. While changing the capacitance value, replace all the capacitors at the same time.

### Discharging Resistor

Due to existence of the SVF capacitors, when input power source is turned off, luminous flux decays to zero slowly. If it is considered too long for dimmed to black, resistors can be added in parallel with the SVF capacitors. Resistance value can be achieved through making R-C time constant equal to the desired response time.

$$\tau = R \times C_{SVF} \quad (8)$$

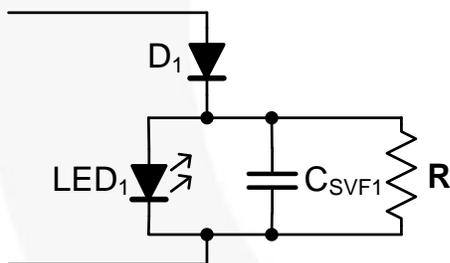


Figure 15. Adding Resistor to Discharge the SVF Capacitor

### Applying Capacitors not in Every LED Group

In Figure 4, every LED group is with SVF capacitor. Designing in this way generally leads to good results in luminary and electrical characteristics of the system. If, in some cases, it is desired to design the system to have only some LED groups having the SVF capacitors, it is also doable. The driver can still work properly. Of course, only the LED groups with SVF capacitors get smoothed luminous output.


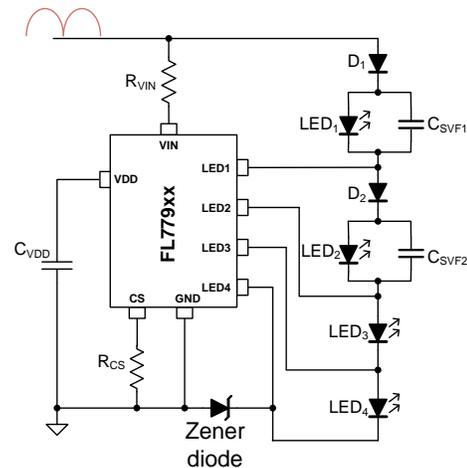


Figure 16. SVF Capacitors are only applied to some LED groups

### Clamping the Inrush Voltage Spike


One more thing to be considered is transient voltage spike when turning on input voltage to a DACD system with SVF. Before powering on, initial voltage on the capacitors will be zero. Referring to Figure 17, assuming the input is turned on at its peak value, since initial voltage is zero for all the capacitors, the LED4 pin in Figure 17 will see directly the peak value of input voltage. If this voltage is beyond voltage rating of the LED4 pin, the driver IC is very likely to be damaged. In such cases, a Zener diode as shown in Figure 17 is required. For example, when the voltage rating of LED4 is 200 V and peak of input voltage is 310 V, a less than 200 V Zener diode is required to clamp the voltage spike. Since the transient time is not too short, power rating of the Zener diode needs to be high. SMCJ200A from Little Fuse is generally applied in our evaluation board. Its power rating is 1500 W. Also worth noting is that the Zener voltage should not be smaller than difference between maximum peak input voltage and LEDs' total effective forward voltage. If so, the Zener diode will be turned on at the peak input voltage region in every AC cycle. The circuit will not operate properly, consume lots of energy, and possibly be damaged.

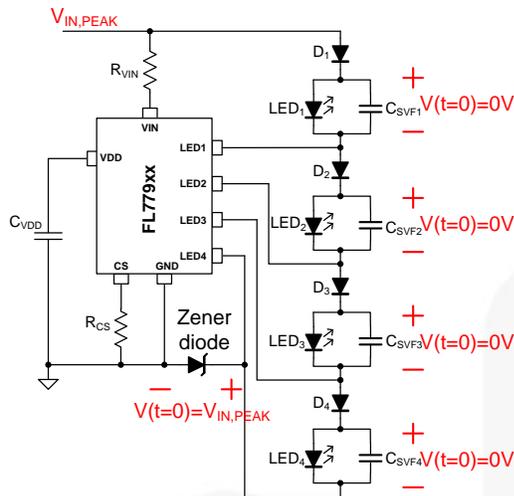

**Figure 17. Voltage Spike on LED4 pin Before SFV Capacitors Get Charged**

Another way to alleviate the impact of voltage spike and current inrush for charging the capacitors is to add inductors in front of bridge diode. Voltage spike and current inrush will be smoothed because that inductor takes time to get

energized. This inductor can also be implemented with capacitors to form an L-C filter for enhancing immunity to lighting surge.

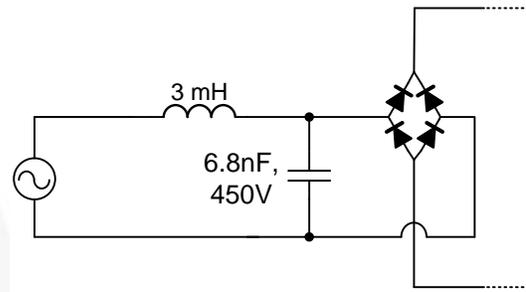

**Figure 18. Example of Input L-C Filter**

## References

- [1] Wilkins, Arnold, Jennifer Veitch, and Brad Lehman. "LED lighting flicker and potential health concerns: IEEE standard PAR1789 update." 2010 IEEE Energy Conversion Congress and Exposition. IEEE, 2010.
- [2] Kaufman, John E., H. Haynes, and Lighting Handbook IES. "Illuminating Engineering Society of North America." IES Lighting Handbook. New York, NY USA (1984).
- [3] ENERGY STAR. "Recommended Practice - Light Source Flicker (Rev. December 2015)," ENERGY STAR (2015).
- [4] "User Guide for FEBFL77944\_L80L012B Evaluation board," Fairchild Semiconductor, April 2016.
- [5] "AN-5088 Designing for High Performance Commercial and Industrial Lighting Solution Using FL77944 High Power LED Direct AC Driver," Fairchild Semiconductor, July 2016.
- [6] "AN-4189 Guidance of Using Self Valley Fill Calculation Tool for FL77904/FL77944/FL77905," Fairchild Semiconductor, July 2016.

## Reference and Related Datasheets

[FL77904 Phase-cut Dimmable Compact LED Direct AC Driver](#)

[FL77905 Analog/PWM/Phase-cut Dimmable Compact LED Direct AC Driver](#)

[FL77944 Analog/PWM Dimmable High Power LED Direct AC Driver](#)

---

### DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

### LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910  
**Japan Customer Focus Center**  
Phone: 81-3-5817-1050

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)  
**Order Literature:** <http://www.onsemi.com/orderlit>  
For additional information, please contact your local  
Sales Representative