

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



Is Now Part of



ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at

www.onsemi.com

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

AN-42036

PCB Grounding System and FAN2001/FAN2011 High Performance DC-DC Converters

Introduction

Ground wiring can often limit system performance. The purpose of this application note is to help the system designer utilize the benefits of the FAN2011 and FAN2001 families of high performance step-down DC-DC regulators, to avoid PCB layout related problems and maximize overall system performance. The basic concept of “star grounding” is presented and ways of implementing star grounding for systems like a cell phone, are shown.

Grounding Issues

Ground is defined as a reference potential for linear circuit elements such as amplifiers, voltage references, and A/D converters. It is used as the return for power systems elements such as switching regulators, power amplifiers, and digital circuit blocks. It is also used as a shield to prevent the propagation of electromagnetic noise in the circuit. Because of these diverse uses, care must be taken in laying out the PCB ground system to avoid interference between different areas of the board.

The finite resistance of the grounding path may couple the noise generated by the power elements into the signal path of the precision circuit elements, as shown in Figure 1.

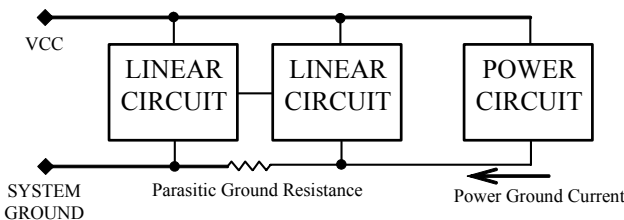


Figure 1. Coupling of Ground Current Noise

If a ground connection carries substantial current, a voltage drop will develop in the ground because of the basic resistance of the ground material. This voltage drop makes local ground different than zero volts, depending on circuit topology and element location. If the current is high and if there are ground sensitive circuits connected to this current path, the voltage drop across the parasitic ground resistance will produce offsets in the voltage measurements of the sensitive linear circuit. In the case of a switching regulator, where the power current is time varying, noise is induced in the system. Linear circuits are referenced to ground and some parameters of the converter such as load regulation and

overall output voltage accuracy are affected by this noise. Another related issue of the ground system is its tendency to carry inductively induced currents. Since the ground system can be spatially extended, it is possible to generate circulating currents in the ground caused by changing external magnetic fields. Because the ground system has usually low resistance, the ground loop currents can become quite large. This often happens in larger systems that magnetically couple to the 50 or 60 Hz power supply lines, which are common in many areas. These circulating currents can then induce noise in the sensitive linear circuits through parasitic ground resistance, as shown in Figure 2.

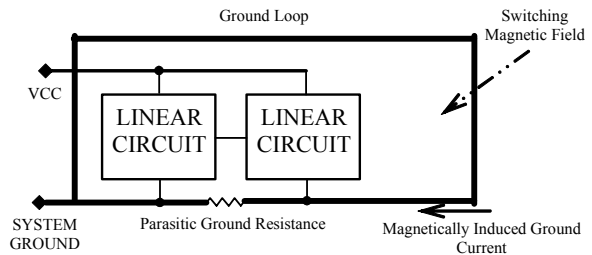


Figure 2. Coupling of Magnetically Induced Ground Current Noise

The Star Ground Technique

In all systems, the correct choice of the ground junction point or single point ground reference, as it is sometimes called, is important. The power management area in particular requires special care as it supplies the current for the whole system. It is necessary to first evaluate the flow of the power supply and signal currents, and then configure the path of the return currents and the location of the junction point. This is necessary to minimize the introduction of DC offsets and noise into the signal return paths.

In star grounding, a common point is chosen to which to connect all ground lines. A physical point is chosen on the circuit board to serve as the star ground point and all grounds radiate from that point to the separate parts of the system. Any one of the ground lines radiating from the star ground may star again, forming a local star ground for a sub-circuit. Special care must be taken to separate the signal ground from the power ground at a star, such that no power current will flow through any signal line ground. Cell phone system design is complex as it compounds various sub-circuits such as analog baseband, digital baseband, audio amplifiers, LCD

controller, power and battery management, and RF transceiver. Such a system is shown in Figure 3 with a general scheme of a “star” ground connection. Ideally, all grounds would converge on the main star and a single point ground reference would be generated at that location. It is physically difficult to bring all the traces on a board to a physical location and make contact at a mathematical point to avoid current generated interference. Therefore, the main star might be broken into sub-stars. This shifts the burden to coupling signals from one star to another, which have slightly different, time variable ground reference potentials. Signal coupling between different blocks would have to be differential to avoid all ground problems.

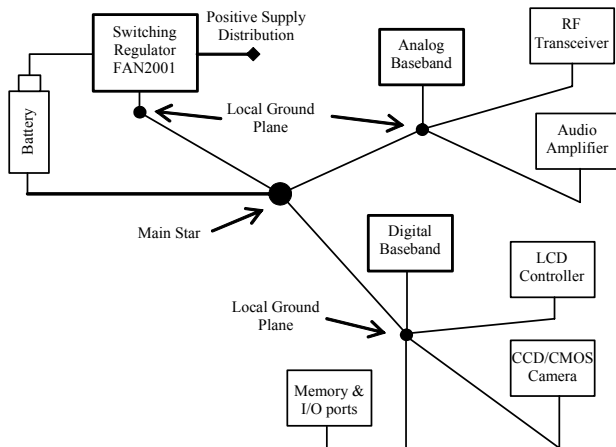


Figure 3. Star Ground Connection for a Cell Phone

FAN2011 and FAN2001 Regulators

The FAN2011 and FAN2001 series of regulators uses a current mode control loop with a fast transient response that ensures excellent line and load regulation. A star ground connection ensures that the highest performance is achieved. The local ground plane for the switching regulator is shown in Figure 4.


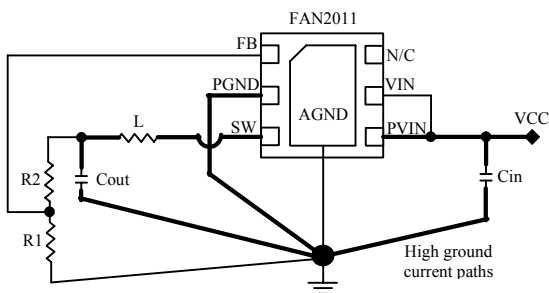


Figure 4. Star Ground Connection for High Performance DC-DC Converters

To benefit from the high performance of the FAN2011/FAN2001 families of regulators, care must be taken designing the PCB layout. The high ground current paths are identified in Figure 4 by bolded lines. The voltage feedback signal, internally connected to an error amplifier, is sensitive to noise and the resistors must be routed separately from the


high current paths. If large ground noise is coupling into the feedback signal the device may become unstable and depending on the noise magnitude, the output voltage will be out of regulation. The internal reference of the device is connected to AGND pin. This pin should also be routed separately from the high current paths directly into the “star.” Any DC offset introduced into the analog ground pin will affect the load regulation and consequently the regulator's DC output voltage accuracy. An optimum PCB layout for the FAN2011 family is shown in Figure 5.

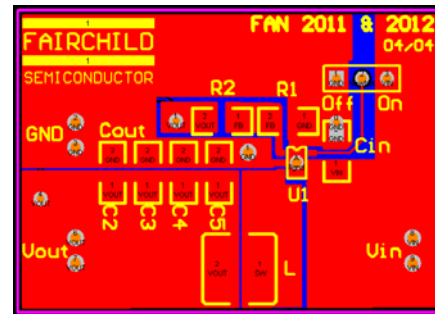

Composite



Top Layer

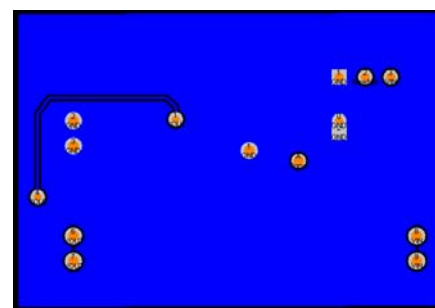

Bottom Layer

Figure 5. PCB Layout

Summary Points:

- Printed circuit board traces have substantial resistance.
- The star ground technique eliminates ground noise problems due to PCB resistance.
- When designing a PCB layout, first evaluate the flow of power supply and signal currents, and then configure the path of the return currents and the location of the junction point. This will minimize the introduction of DC offsets and noise into the signal return paths.
- To benefit from the high performance of the FAN2011 and FAN2001 families of DC-DC regulators, local star ground techniques should be considered for the switching regulator embedded in an application system.

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative