

# ON Semiconductor

## Is Now

# onsemi™

To learn more about onsemi™, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

---

**onsemi** and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



Is Now Part of



**ON Semiconductor®**

To learn more about ON Semiconductor, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## An Introduction to Fairchild Switch Products

### New Solutions

Today more systems are being designed with basic functionality integrated as much as possible with separate modules being used to add feature functions. This pushes the cost out to only those customers who want to pay for the extra features. However, modular designs add new challenges to system design.

Modular components may require hot swapping and some may also require voltage translation. A new set of logic devices are required to isolate and translate. Normally, additional logic in the signal path would add delay and require more power due to the drive capability of standard logic devices. However, a new technology in logic devices, the bus switch, is designed specifically for applications that do not need drive, yet require simple logic functions, bus isolation and/or voltage translation. Since these devices do

not add signal delay or power, timing budgets and power budgets are largely unaffected.

Fairchild Switch (FST) Bus Switch devices are just that, switches. When OPEN or OFF, the bus switch consumes no power and provides high impedance isolation between terminals. When CLOSED or ON, the bus switch acts as a low-impedance resistor (typically less than  $5\Omega$ ) that can also translate the input voltage to a lower output voltage.

In addition to providing isolation to modular components and translation between dissimilar voltage components, bus switches can provide basic logic functions such as multiplexing and bus exchange without the added penalty of propagation delay or power. This technology adds a new dimension to system design not previously available from standard logic devices.

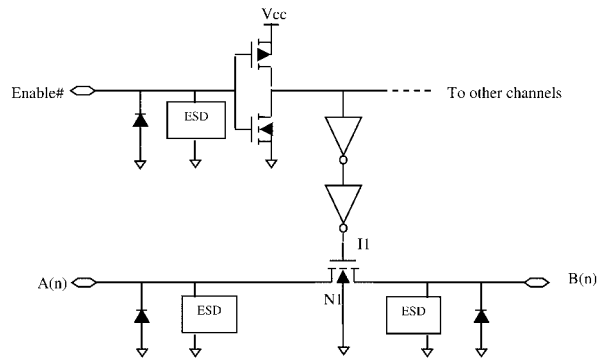


FIGURE 1. Typical NMOS Bus Switch

### MOSFET Transistor Switch Operation

To better understand how FST bus switch logic can benefit the system designer, it helps to understand the theory of operation of a MOSFET pass transistor, which is the centerpiece of a bus switch device. Most bus switch devices are comprised of NMOS pass transistors. These NMOS devices provide isolation when OFF and provide voltage translation when ON. NMOS-type logic devices have become the most popular types of bus switch used today.

As illustrated in Figure 1, the Enable circuitry of the bus switch feeds the gate of the NMOS device N1. Typically  $V_{\text{Gate}} = V_{\text{CC}}$  when enabled. The substrate of an NMOS device is tied to ground, and the threshold voltage ( $V_{\text{TN}}$ ) is nominally 1Volt. Any voltage drop between the gate and source of the NMOS ( $V_{\text{GS}}$ ) greater than 1V will cause the NMOS transistor N1 to fully turn ON. Note that since both

the "A" terminal and "B" terminal of the NMOS are N-type doped, either side can become the source once a voltage is applied to that terminal. This makes a bus switch device a bi-directional device.

The ON resistance ( $R_{\text{ON}}$ ) of the NMOS device is typically very low (less than  $5\Omega$ ). Once the NMOS pass transistor is turned ON the drain voltage will closely track the source allowing signals to "pass" freely through the NMOS transistor. As the source voltage approaches  $V_{\text{CC}}$  the voltage passed becomes limited as the NMOS begins to shut down and  $R_{\text{ON}}$  increases. This phenomenon is described in more detail below. Since the NMOS, when turned ON, acts as a resistor there is no delay added to the signal path (typically measured well below 250 picoseconds). Thus, a zero-delay logic device is created.

### Translation

Translation on an NMOS device occurs once the  $V_{GS}$  voltage reaches  $V_{TN}$ , roughly 1V, or less. At this point, the NMOS channel is closed off and  $R_{ON}$  increases dramatically clamping off any further current flow through the device. The drain, starved of current, can not exceed a voltage of  $V_{CC}-1V$ . This makes a 5V NMOS Bus Switch device a "5V-to-4V" translator (see Figure 2). An example of this type of device is the FST3384 10-Bit Bus Switch.

Since translation in typical systems today occurs between 5V and 3.3V levels, an additional 700 mV drop on the drain terminal is required. This is best accomplished by dropping the  $V_{Gate}$  to the NMOS by another 700 mV. This can be achieved by adding an internal diode between the  $V_{CC}$  terminal and the gate (see Figure 3). An example of this type of device is the Fairchild NC7SZD384 Single-Bit Bus Switch. Translation can also be achieved externally by add-

ing a resistor divider network or diode to the  $V_{CC}$  pin of the bus switch IC. External voltage drop circuits, although requiring extra components, allow the PC designer to precisely set the value of the translation voltage.

The discussion so far has focussed on translating 5V devices on the A-side down to 3.3V devices on the B-side. If the 3.3V device were to drive from the B-side to A-side, the "A" terminal will only achieve a maximum voltage of 3.3V ( $V_{CC}$  is still 5V and no clipping occurs at 3.3V). These bus switch devices are optimal for interfacing 3.3V devices to 5V TTL-compatible level inputs. If 5V CMOS-level signals were required, external pull-up resistors would be needed to pull the A-side up to 5V. For more information on translation with FST Bus Switches, refer to Application Note 996.

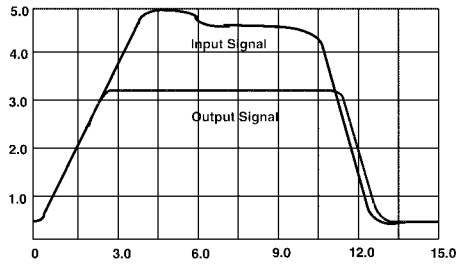


FIGURE 2. Typical NMOS Bus Switch Waveform

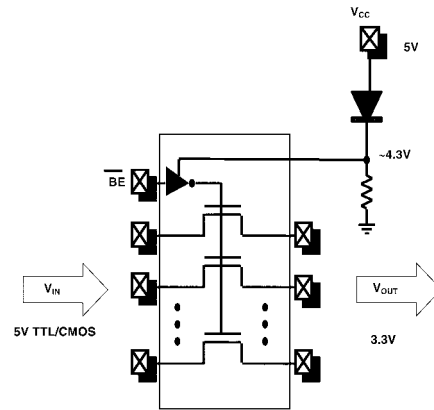


FIGURE 3. Typical 5V to 3.3V Translation Circuit

### CMOS Passgate Operation

If no translation is required, and the system designer simply requires the zero-delay feature of a bus switch, there may be two possible solutions. The NMOS pass transistor can be utilized under certain input conditions, or a device known as a CMOS Pass Gate switch is required.

If the input voltage to an NMOS device, with a  $V_{CC}$  of 5V can be maintained below that of  $V_{CC}-1V$ , the output will not be clipped, or translated. If this is not possible, or if the entire 5V swing is required, then a CMOS Pass Gate must be used. CMOS Pass Gate switches are created similarly to the NMOS switch, except that a PMOS pass transistor is added in parallel to the NMOS device (see Figure 4). The

gate node of the PMOS device is also tied to the enable circuit ( $V_{CC}$ ) but PMOS substrates are also tied to  $V_{CC}$ .

In order to turn the PMOS device P1 ON, the  $V_{GS}$  must be less than the threshold voltage,  $V_{TP}$ , or roughly 1V. With a CMOS Pass Gate device it is now possible to have the drain terminal continue to track the source terminal voltage without clipping at  $V_{CC}-1V$ . This allows the signal to fully "pass" through the switch without delay and without clipping. These devices are also called digital or analog switches. An example of this type of device is the Fairchild NC7SZ66 Single-Bit Digital Switch.

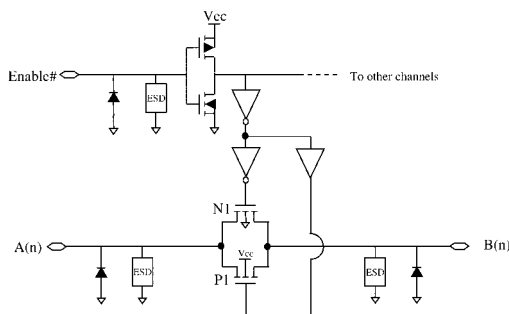


FIGURE 4. Typical CMOS Pass Gate

### Types OF Bus Switches

FST Bus Switches can be configured into three basic functional types: the Bus Switch, the Multiplexer Switch, and the Bus Exchange Switch (see Figure 5). The simple Bus Switch is the most common type of switch device. This function can come in both NMOS pass transistor configuration and CMOS pass gate configuration as described above. This type of switch can also be packaged from one

bit to several bits in width. The Multiplexer Switch can multiplex signals from one source to two or more separate destinations. An example of this type of switch is the Fairchild FST16232 16-to-32-Bit Multiplexer Switch. The Bus Exchange Switch can exchange signals between two buses. An example of this is the Fairchild FST3383 10-Bit Bus Exchange Switch.

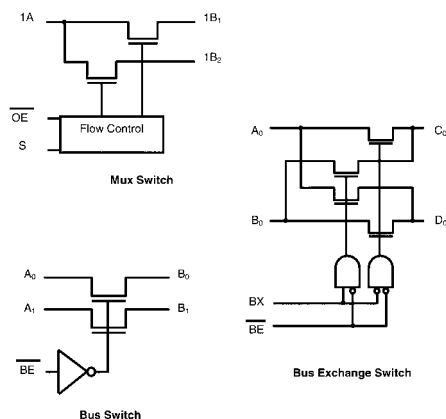


FIGURE 5. Types of Bus Switches

In addition to the functional configurations described, all three types of switches can provide the isolation and translation features without the penalty of propagation delay. These ICs are available to the system designer in a variety of packages such as SOIC, TSSOP, SSOP and QSOP for the

multi-bit switches, plus SOT23-5 and SC70-5 for the single-bit switches.

See Fairchild's web site at [www.fairchildsemi.com](http://www.fairchildsemi.com) for a complete list of available FST bus switch devices.

**Bus Switch Applications**

There are many possible applications for Fairchild Switch logic. Some applications are specifically intended for isolation or translation, those intended for multiplexing or bus exchange may also utilize the isolation and translation features of bus switch logic. The exact number of bus switch devices used varies based on the number of signals required. Examples of each of these types of bus switch applications are briefly described below.

**Hot Swapping Example**— Many systems such as docking stations for mobile PCs, PCI boards for servers, and line cards for telecommunications switches require the ability to handle hot-swapping. Hot-swapping can be achieved through the use of power-ramping design techniques. However, the ability to isolate the bus prior to insertion or removal through the use of bus switch allows more control over the hot-swap event. An example of this type of bus switch is the FST3384 10-Bit Bus Switch. In some situations, a designer might even wish to precharge the connector or have higher immunity to spurious undershoot voltages. An example of this type of bus device is Fairchild's FSTU6800 10-Bit Undershoot Hardened Bus Switch with Precharge.

**Voltage Translation Switch Example**— This application is a 3D AGP advanced graphics card for the PC. AGP graphics controllers have features such as ports and control for DVD video and CRT monitors. Many times the AGP controller IC has 3.3V I/O. Several of the video ports are 5V and translation is required between the two. An example of

this type of bus switch is Fairchild's FST16211 24-Bit Bus Switch.

**Bus Exchange Example**— This switch application is a shared memory bus exchange circuit where a single chipset memory port can access additional memory modules without the need for additional drive or delay. A bus exchange device such as Fairchild's FST16292 Bus Exchange Switch has been implemented in Intel's most recent chipset design.

**Multiplexing Bus Switch Example**— A multiplexing bus switch application is the multiplexing of the 12C serial data and serial clock lines into multiple EEPROM devices for expanding the size of the nonvolatile storage capacity in large-scale computers like servers and workstations. An example of this type of device is the Fairchild FST3253 Dual 4:1 Multiplexer Switch. Another application is the multiplexing of video signals on new 3D video boards that have added TV and MPEG DVD encoders that convert RGB to VTSC/PAL TV video. Since both the CRT and the encoder require 75Ω loads, placing both in parallel will alter the desired voltage levels, corrupting the video signals. The RGB output signals need to be multiplexed to the additional loads using a Fairchild FST3257 Quad 2:1 Multiplexer Switch to multiplex the RGB signals to either the CRT DIN connector or to the TV encoder circuit.

These are just a few of the many new applications for zero-delay bus switch logic. Visit Fairchild's web site at [www.fairchildsemi.com](http://www.fairchildsemi.com) for more applications examples.

Fairchild does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and Fairchild reserves the right at any time without notice to change said circuitry and specifications.

**LIFE SUPPORT POLICY**

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component in any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

[www.fairchildsemi.com](http://www.fairchildsemi.com)

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910  
**Japan Customer Focus Center**  
Phone: 81-3-5817-1050

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)  
**Order Literature:** <http://www.onsemi.com/orderlit>  
For additional information, please contact your local  
Sales Representative