ON Semiconductor

Is Now



To learn more about onsemi™, please visit our website at www.onsemi.com

onsemi and ONSEMI. and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "onsemi" or its affiliates and/or subsidiaries in the United States and/or other countries. onsemi owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of onsemi product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. onsemi reserves the right to make changes at any time to any products or information herein is provided "as-is" and onsemi makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does onsemi assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using onsemi products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by onsemi. "Typical" parameters which may be provided in onsemi data sheets and/ or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. onsemi does not convey any license under any of its intellectual property rights nor the rights of others. onsemi products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use onsemi products for any such unintended or unauthorized application,



Is Now Part of



ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at www.onsemi.com

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any EDA Class 3 medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, emplo



AN-6102

USB Type C, CC Pin Protection

Utilizing Zener Diode to protect CC Pin for A to C High Voltage Charging Application

When a USB Type A to USB Type C cable is used, the cable includes a Rp pull up from V_{BUS} to the CC pin, this is done so the type C device can detect the correct orientation

of the plug, Figure 1 is an example of the Type A to Type C Cable.

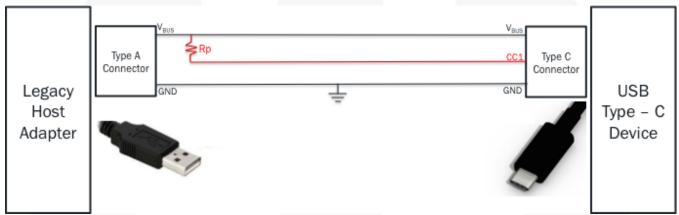


Figure 1. Example of Type A to Type C Cable

With this cable, it allows a Type C device to be backward compatible with existing devices. However, there are power adapters with fast charging protocols that utilizes the Type A connector for fast charging. When the end user enables the existing fast/high voltage charging, V_{BUS} can increase up to 20 V, this would cause the CC pin to also increase voltage beyond the absolute maximum specification of the device. To calculate the maximum voltage that could be present on the CC pin, use equation (1).

$$V_{CC} = V_{BUS} * (\frac{Rd}{Rp + Rd})$$
 (1)

With Rd enabled on the device, we can use 5.1 k for Rd and need to determine the Rp to calculate the voltage present on CC. Assuming worst case, we will use 4.7 k Ω Rp at 20 V V_{BUS}. We can see that the V_{CC} can be as high as 10.4 V, the absolute maximum of the CC pin is 6 V so we can utilize the Zener diode to clamp down the voltage to protect the CC pin. However, since the CC pin is used for Type C and PD communication picking the right clamping voltage is imperative to preventing communication errors. A clamping voltage above 5 V but below 6 V is preferred. Table 1 shows two Zener diode part numbers that meet these requirements (5.1 V & 5.6 V).

Table 1. Zener Diode Example

Manufacturer	Manufacturers Part Number	Voltage – Zener (Nom) (V _z)	Tolerance	Power- Max. (P _d)	Current-Reverse Leakage (I _r)
Bourns	CD1005-Z5V1	5.1 V	5%	200 mW	100 nA
Comchip	CZRF52C5V6	5.6 V	5%	200 mW	100 nA

AN-6102 APPLICATION NOTE

One of the considerations when picking which Zener diode to use, is to review the Zener diode power dissipation specification. When the Zener diode is activated the maximum current can be calculate by the VBUS voltage and the Rp value, If we use 20 V and 4.7 k Ω Rp we will get 4.26 mA though the Rp resistor, and the Zener diode would

need to dissipate 85 mW of power to protect the device. So selecting the correct Zener diode would be the key for this protection to work as the 2 recommended Zener diode is rated to have 200 mW maximum power and its capacitance should be no larger than 600 pF as per PD specification cReceiver requirements of 200 pF min to 600 pF maximum.

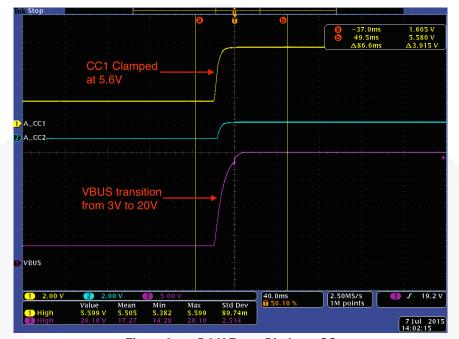


Figure 2. 5.6 V Zener Diode on CC

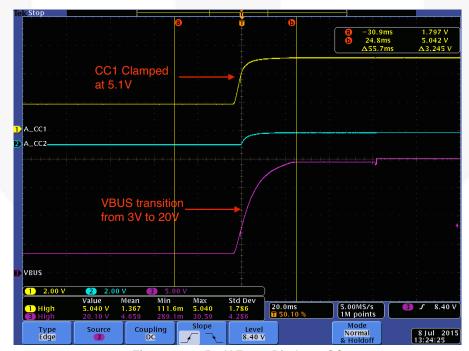


Figure 3. 5.1 V Zener Diode on CC

Reference Schematic with FUSB302

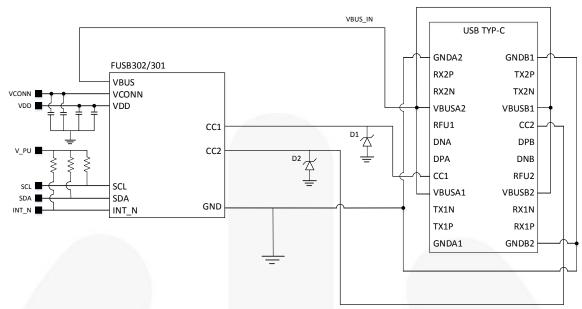


Figure 4. Reference Schematic

Note:

1. The recommended placement of the Zener diode, is as close to the device as possible.

Related Datasheets

FUSB300C—Programmable USB Type-C Controller

FUSB301—Datasheet Brief

FUSB301A—Autonomous USB Type-C Control with Configurable I²C Address

FUSB302—Programmable USB Type-C Controller w/PD

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION. As used herein:

- Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
- A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and in are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdt/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and exp

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor 19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada Email: orderlit@onsemi.com N. American Technical Support: 800–282–9855 Toll Free USA/Canada
Europe, Middle East and Africa Technical Support: Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81–3–5817–1050

ON Semiconductor Website: www.onsemi.com

Order Literature: http://www.onsemi.com/orderlit

For additional information, please contact your local Sales Representative