

# ON Semiconductor

## Is Now

# onsemi™

To learn more about onsemi™, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

---

**onsemi** and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



Is Now Part of



**ON Semiconductor®**

To learn more about ON Semiconductor, please visit our website at  
[www.onsemi.com](http://www.onsemi.com)

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

# AN-7010

## Choosing Power Switching Devices for SMPS Designs MOSFETs or IGBTs?

By Ron Randall, Staff Applications Engineer, Fairchild Semiconductor

### Introduction

This article identifies the key parametric considerations for comparing IGBT and MOSFET performance in specific SMPS (Switch Mode Power Supply) applications. Parameters such as switching losses are investigated in both hard-switched and soft-switched ZVS (Zero Voltage Switching) topologies. The three main power switch losses: turn-on, conduction and turn-off are described relative to both circuit and device characteristics. The impact of diode recovery performance on hard-switched topologies is also discussed illustrating that diode recovery is the dominant factor determining MOSFET or IGBT turn-on switching losses.

This article also shows how device selection is complicated by the specific cooling system being utilized. For example, a single IGBT may perform well in a hard-switched PFC (Power Factor Correction) circuit with sufficient cooling heatsink; while, conversely, a design that mandates a marginal heatsink for cost or space reasons may require multiple parallel power MOSFETs. The conclusion reiterates that there is no single solution for choosing and applying IGBTs or MOSFETs in SMPSs and that each application merits careful analysis selecting an optimum switching device.

Historically, the off-line SMPS (Switch Mode Power Supply) industry has been driven by the power semiconductor industry's power component advancements. As the main power-switching devices, IGBTs, Power MOSFETs, and power diodes continually improve, there are corresponding—and significant—efficiency, size, weight and cost improvements in SMPS designs. Because of this direct component-to-application performance relationship, SMPS designers must compare the many pros and cons of the various semiconductor technologies to optimize their designs. For example, MOSFETs typically excel for lower power and higher frequency applications (i.e., power levels < 1000W and switching frequencies  $\geq 100$  kHz). But IGBTs have distinct advantages for lower frequency and higher power designs. This article compares an IGBT, the FGP20N6S2D SMPS2 and a MOSFET, the FCP11N60 SuperFET (from Fairchild Semiconductor) in an SMPS application. These products exemplify state-of-the-industry parts and they have comparable die size and identical thermal resistance  $R_{\theta JC}$ .

### Turn-On Losses

The turn-on characteristics of IGBTs and power MOSFETs are quite similar, except that IGBTs have a longer voltage fall time. Referencing the basic IGBT equivalent circuit (Figure 1) the time required to fully modulate the minority carrier PNP BJT collector base region results in a turn-on voltage tail.

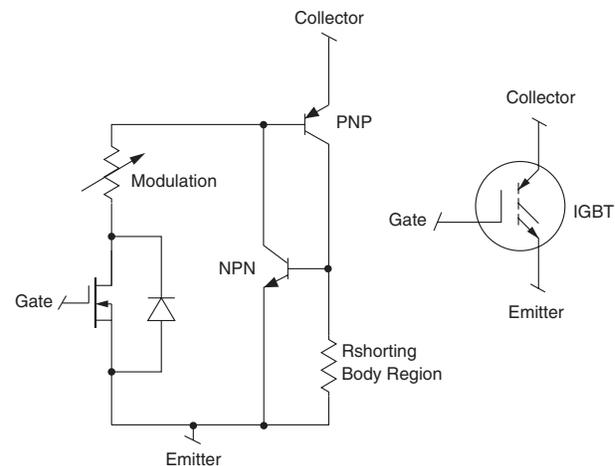


Figure 1. An IGBT Equivalent Circuit.

This delay results in a Quasi-Saturation effect wherein the collector-emitter voltage does not immediately fall to its  $V_{CE(sat)}$  value<sup>1</sup>. This turn-on effect also results in a  $V_{CE}$  voltage bump under ZVS conditions at the point where the load current transitions from the co-packed inverse parallel diode to the IGBT collector. The  $E_{on}$  energy losses specified in datasheets is the time integral of  $I_{collector}$  times  $V_{CE}$  in joules per switching cycle, and includes the additional losses associated with quasi-saturation.

Two  $E_{on}$  energy parameters,  $E_{on1}$  and  $E_{on2}$ , are provided in IGBT datasheets.  $E_{on1}$  is the energy loss without the losses associated with hard-switched diode recovery.  $E_{on2}$  includes the hard-switched turn-on energy loss do to diode recovery and is measured by recovering a diode identical to the co-packed diode associated with the device. A typical  $E_{on2}$  test circuit is illustrated in Figure 2. The test is performed with the diode at the same  $T_j$  as the DUT. The IGBT is switched through two pulses to measure  $E_{on}$ . The first pulse raises the inductor to the desired test current and the second pulse then measures the  $E_{on}$  loss recovering this current from the diode.

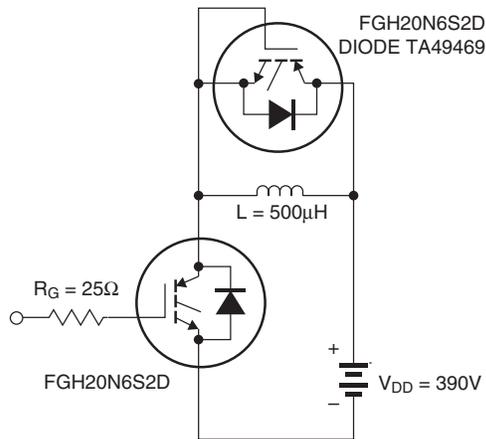


Figure 2. Typical Eon and Eoff Test Circuit.

Under hard-switched turn-on, the gate drive voltage and impedance and the recovery characteristics of the commutated diode determine the Eon switching loss. For circuits such as the conventional CCM (Continuous Current Mode) boost PFC circuit, the boost diode recovery characteristics are extremely important in controlling Eon (turn-on) energy losses. In addition to selecting a boost diode with minimal  $T_{rr}$  and  $Q_{RR}$ , it is also important to ensure that the diode has soft recovery characteristics. Softness, the ratio of  $t_b/t_a$ , has a considerable impact on the electrical noise and voltage spikes generated across the switching device. Snappy diodes with a rapid  $t_b$  period  $di/dt$  fall from  $I_{RM(REC)}$  create large voltage spikes in the circuit parasitic inductances. These voltage spikes create EMI and can result in excessive reverse voltage across the recovering diode.

In hard-switched circuits, such as the full-bridge and  $1/2$  bridge topologies where the IGBT co-packed diode or the MOSFET body diode is conducting when the alternate switching device is turned on, the diode recovery characteristics determine the Eon loss. For this reason it is important to select MOSFETs with fast body diode recovery characteristics, such as the Fairchild's FQA28N50F FRFET™. Unfortunately, MOSFET parasitic, or body diodes, are relatively slow compared to state-of-the-industry discrete diodes. For hard-switched MOSFET applications, the body diode is often the limiting factor determining the SMPS operating frequency.

Typically, IGBT co-packed diodes are selected for compatibility with their intended applications. Slower ultra-fast diodes with lower forward conduction losses are co-packed with slower lower  $V_{CE(sat)}$  motor drive IGBTs. Conversely, soft recovery hyper-fast diodes, such as the Fairchild Stealth™ series, are co-packed with the high frequency SMPS2 switched mode rated IGBTs.

Beyond selecting the right diode, a designer can control Eon losses by adjusting the gate drive turn-on source resistance. Decreasing the drive source resistance will increase the IGBT or MOSFET turn-on  $di/dt$  and decrease the Eon loss. The tradeoff is between Eon losses and EMI, since the higher

$di/dt$  will result in increased voltage spikes and radiated and conducted EMI. Selecting the correct gate drive resistance to meet a desired turn-on  $di/dt$  may require in-circuit testing and verification. A ballpark value may be determined from the MOSFET transfer curve, (Figure 3). Assuming the FET current will rise to 10 A at turn-on, and looking at the 25°C curve of Figure 3, the gate voltage must transition from 5.2 V to 6.7 V to reach 10 A and the average GFS is  $10A / (6.7V - 5.2V) = 6.7mhos$ .

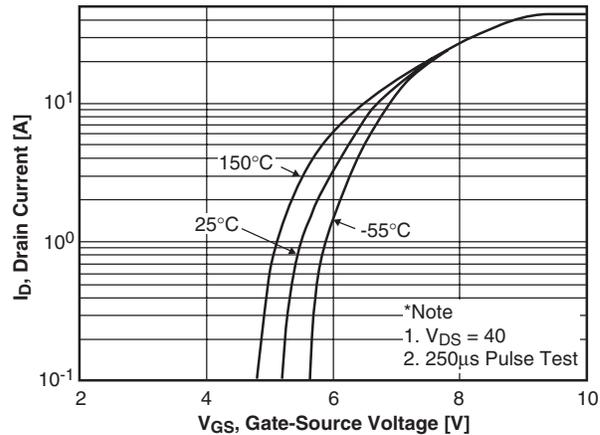


Figure 3. A MOSFET Transfer Characteristics.

$$R_{gate} = [V_{drive} - V_{GS(avg)}] \cdot \frac{G_{FS}}{(di/dt) \cdot C_{iss}}$$

Equation 1. Gate drive resistance for desired turn-on  $di/dt$ .

Applying this average  $G_{FS}$  value to Equation 1, with a gate drive of  $V_{drive} = 10V$ , a desired  $di/dt = 600A/\mu sec$  and typical FCP11N60 values  $V_{GS(avg)} = 6V$ ,  $C_{iss} = 1200pF$ ; a 37Ω turn-on gate drive resistance is calculated. Since the instantaneous  $G_{FS}$  value is the slope in Figure 3,  $G_{FS}$  will vary during the Eon period, which implies a varying  $di/dt$ . The exponentially decaying gate drive current and decreasing  $C_{iss}$  as a function of  $V_{GS}$  also enter into this equation with an overall effect of surprisingly linear current rise.

Similar gate drive turn-on resistance may be calculated for the IGBT. Again  $V_{GE(avg)}$  and  $G_{FS}$  may be determined from the IGBT transfer characteristic curve, and the  $C_{IES}$  value at  $V_{GE(avg)}$  should be substituted for  $C_{iss}$ . The comparable calculated IGBT turn-on gate drive resistance is 100Ω. This higher Ω requirement is indicative of the higher IGBT  $G_{FS}$  and lower  $C_{IES}$ . A key point here is that gate drive circuit adjustments must be made for a transition from MOSFET to IGBT.

## Conduction Losses

When comparing 600 V rated devices, IGBT conduction losses typically are less than an equivalent die size 600 V MOSFET. A qualifier is that the comparison should be made at appreciable collector and drain current densities and at the

desired worst-case operating junction temperature. For example, the FGP20N6S2D SMPS2 IGBT and FCP11N60 SuperFET both have an  $R_{\theta JC}$  value of  $1^{\circ}\text{C}/\text{W}$ . Figure 4 compares conduction loss versus DC current at a junction temperature of  $125^{\circ}\text{C}$ . It shows that the MOSFET will have more conduction losses for DC currents greater than  $2.92\text{ A}$  dc.

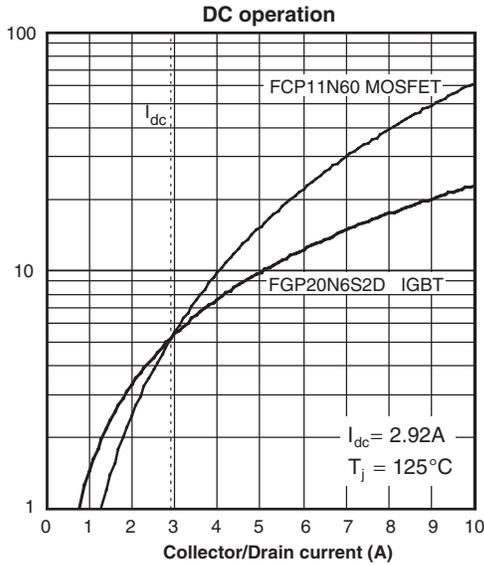


Figure 4. Conduction Losses DC Operation.

However, the DC conduction loss comparison in Figure 4 does not apply to most applications. In Figure 5, on the other hand, conduction losses are compared operating in a CCM, boost PFC circuit with a junction temperature of  $125^{\circ}\text{C}$  and Vac input of  $85\text{ V}$  and  $400\text{ Vdc}$  output. In this figure the MOSFET-IGBT crossover point is  $2.65\text{ A}$  RMS. For PFC circuit, AC input currents greater than  $2.65\text{ A}$  RMS, the MOSFET will have greater conduction losses. The  $2.65\text{ A}$  PFC AC input current equates to  $2.29\text{ A}$  RMS in the MOSFET as calculated by Equation 2. Boost switch RMS current in CCM PFC Circuit. The MOSFET conduction loss is calculated as an  $I^2R$  loss using the current defined by Equation 2. Boost switch RMS current in CCM PFC Circuit and the MOSFET  $125^{\circ}\text{C}$   $R_{DS(on)}$ . This conduction loss may be further refined by accounting for the variation of  $R_{DS(on)}$  as a function of drain current. This relationship is illustrated in Figure 6.

The impact on conduction losses may be determined as outlined in an IEEE article called *How to include the dependency of the  $R_{DS(on)}$  of power MOSFETs on the instantaneous value of the drain current into the calculation of the conduction losses of high-frequency three-phase PWM inverters*, referenced below<sup>2</sup>. The impact of  $R_{DS(on)}$  change as a function of  $I_D$  is minimal for most SMPS topologies. As an example, the impact of operating the FCP11N60 MOSFET in the PFC circuit to an  $I_D$  of  $11\text{ A}$  peak current, or two times the  $5.5\text{ A}$ , its  $R_{DS(on)}$ , is specified at will increase the effective  $R_{DS(on)}$  and conduction losses by  $5\%$ .

The  $R_{DS(on)}$  characteristic illustrated in Figure 6 should be considered in topologies where the MOSFET conducts high pulse currents for very short duty-factors. If the FCP11N60 MOSFET is operated in a circuit with a  $20\text{ A}$  pulse at  $7.5\%$  duty-factor (i.e.,  $5.5\text{ A}$  RMS), the effective  $R_{DS(on)}$  will be  $25\%$  greater than the specified  $0.32\ \Omega$  at  $5.5\text{ A}$ .

$$I_{rms_{switch}} = I_{ac_{RMS}} \cdot \sqrt{1 - \frac{8 \cdot \sqrt{2}}{3 \cdot \pi} \cdot \frac{V_{ac}}{V_{out}}}$$

**Equation 2.** Boost switch RMS current in CCM PFC Circuit

Where:

$I_{ac_{RMS}}$  is the PFC circuit RMS input current

$V_{ac}$  is the PFC circuit RMS input voltage

$V_{out}$  is the DC output voltage

It is more complex to calculate the IGBT conduction loss in applications, such as a PFC circuit, where each switching period is at a different  $I_{CE}$ . This is because the  $V_{CE(sat)}$  cannot be represented as a resistance voltage drop. A relatively straight-forward approach is to represent the IGBT  $V_{CE(sat)}$  as a fixed  $V_{FCE}$  voltage in series with a resistor  $R_{FCE}$ :  $V_{CE}(I_{CE}) = I_{CE} \times R_{FCE} + V_{FCE}$ . The conduction losses may then be calculated as the product of the average collector current times  $V_{FCE}$ , plus the RMS collector current squared, times the resistance  $R_{FCE}$ . This technique is detailed in the articles referenced below<sup>3,4</sup>, which include validation in a PFC circuit.

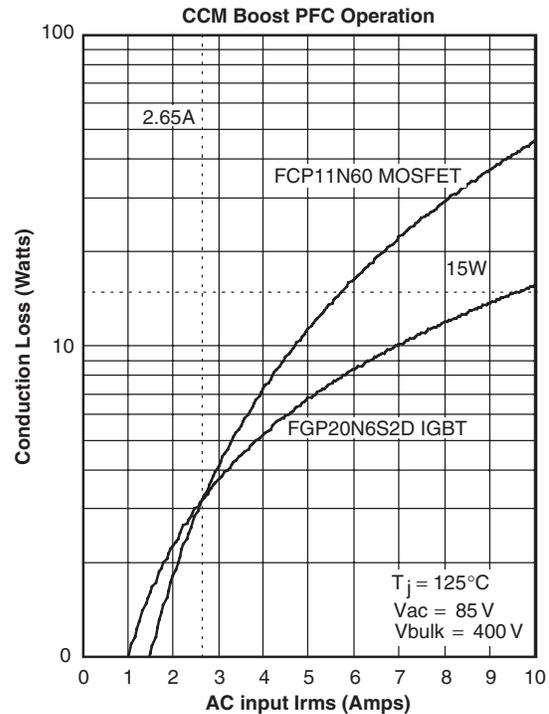


Figure 5. Conduction Losses in CCM Boost PFC Circuit.

The loss curves in Figure 5 consider only the IGBT and MOSFET conduction losses in a CCM PFC circuit. If, as an example, the design objective is to maintain the worst-case conduction losses too less than 15W then using the FCP11N60 MOSFET, the circuit is limited to 5.8A.

However, the FGP20N6S2D IGBT can operate with an AC input current of 9.8A—which means it can handle 70% more power with this 15W conduction loss restriction.

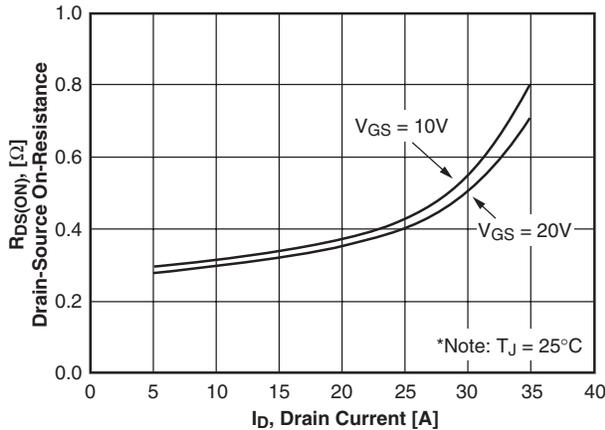


Figure 6. FCP11N60(MOSFET):  $R_{DS(on)}$  vs.  $I_{DRAIN}$  and  $V_{GE}$ .

While IGBTs will exhibit lower conduction losses, most 600V IGBTs are PT (Punch Through) devices. PT devices have a NTC (Negative Temperature Coefficient) and will not share current when operated in parallel. PT devices may be paralleled with limited success by matching device  $V_{CE(sat)}$ ,  $V_{GE(th)}$  (gate-to-emitter threshold voltage), and by mechanically packaging, such that the IGBT die temperatures will track closely. Conversely, the MOSFET has a PTC (Positive Temperature coefficient) that provides good current sharing.

### Turn Off Loss

MOSFETs have considerably lower turn-off losses than IGBTs in hard-switched, clamped inductive operation. This is because of the IGBT tail current associated with clearing the minority carriers, which are associated with the PNP BJT (Figure 1). IGBT Eoff energy curves as a function of collector current and junction temperature (Figure 7) are provided in most IGBT datasheets. These curves are applicable for a fixed clamped inductive test voltage and include the tail current energy loss. Figure 2 illustrates the typical test circuit used for measuring IGBT Eoff as a function of  $I_{CE}$  and  $T_j$ . The Eoff test voltage, the  $V_{DD}$  in Figure 2, varies with manufacturer and the specific device’s  $BV_{CES}$ . This test  $V_{DD}$  should be considered when comparing devices. Testing and operating at a lower  $V_{DD}$  clamp voltage will result in reduced Eoff energy loss.

Lowering the gate drive turn-off resistance will have minimal effect in reducing IGBT Eoff loss. As illustrated in Figure 1, once the equivalent majority carrier MOSFET is turned off there is still a  $t_{d(OFF)}$  storage time delay in the IGBT minority

carrier BJT. Lowering the Eoff drive resistance will, however, reduce the risk of the Miller capacitance  $C_{RES}$  and turn-off  $V_{CE} dv/dt$  injecting a current into the gate drive that re biases the device into conduction causing multiple Eoff switching.

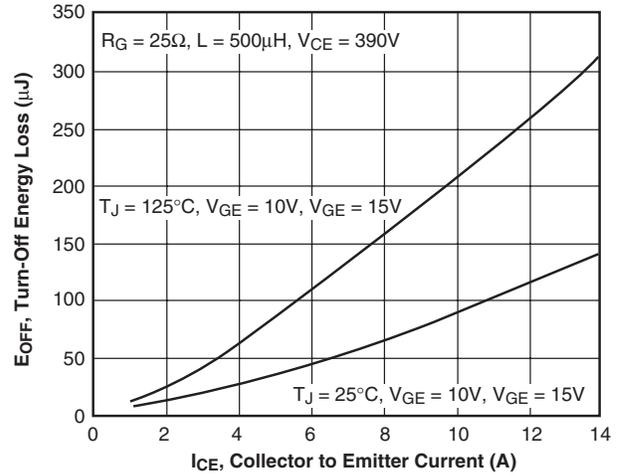


Figure 7. IGBT Eoff vs.  $I_{CE}$  and  $T_j$ .

ZVS and ZCS (Zero Current Switching) topologies have advantage in reducing turn-off losses in both MOSFETs and IGBTs. The ZVS operation advantage is not as great in IGBTs since an Eoff tail bump current, albeit smaller, will still exist once the collector voltage rises to a potential that permits dissipation of excess stored charge. ZCS topologies produce the greatest IGBT Eoff performance improvement. Proper gate drive sequence, wherein the IGBT gate signal is not removed until the point of second collector current zero crossing, can have a marked improvement in IGBT ZCS Eoff reduction<sup>5</sup>.

The MOSFET Eoff energy loss is a function of its Miller capacitance  $C_{TSS}$ , the gate drive speed, gate drive turn-off source impedance, and parasitic inductance in the source power circuit path. The circuit parasitic inductance  $L_x$ , shown in Figure 8, generates a potential that increases the turn-off loss by limiting the current fall  $di/dt$ . At turn-off, the current falls at a  $di/dt$  determined by  $L_x$  and  $V_{GS(th)}$ . If, as an example,  $L_x = 5$  nano-henries and  $V_{GS(th)} = 4V$  the maximum rate current fall will be  $V_{GS(th)} / L_x = 800A / \mu\text{sec}$ .

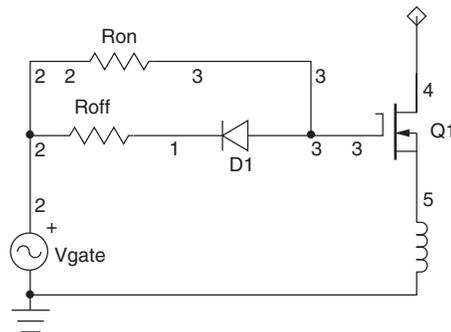


Figure 8. Gate Drive Circuit in Typical Hard-Switched Applications.

## Gate Drive Requirements

While both MOSFETs and IGBTs have high gate impedance and are voltage-controlled devices, the minimum-drive voltage requirements are different. The minimum acceptable gate drive voltage is important, since falling below this value will result in switching from the “ON” state to a highly dissipative linear mode. Drive circuits for either device should be designed such that the gate drive does not fall below the minimum value under any condition. Good circuit-design hygiene mandates that a gate drive UFLO (Under Voltage Lock Out) circuit be incorporated to ensure that gate drive is removed for low drive voltage conditions to prevent the switching devices from entering the linear conduction mode.

When comparing the FGP20N60S2D and FCP11N60 gate characteristics, the FGP20N60S2D’s  $V_{GEP}$  plateau voltage is 8 V max and the FCP11N60  $V_{GS(th)}$  threshold voltage is 5 V max. The FGP20N60S2D IGBT  $V_{GEP}$  value is meaningful since it is tested at an appreciable 7 A current. However, the FCP11N60 MOSFET  $V_{GS(th)}$  voltage is measured at 250  $\mu$ A and does not guarantee that the device will be “ON” at a  $V_{GS}$  of 5V. Further useful information may be obtained from the MOSFET’s  $V_{GS}$  versus  $I_D$  on-region characteristic curve. For example, in order to guarantee that the FCP11N60 is “ON” for a 10 A load, the  $V_{GS}$  should be 6.5 V minimum. Parasitic gate capacitances heavily impact the switching characteristics of both MOSFETs and IGBTs. For the MOSFET the drain-to-gate  $C_{TSS}$ , reverse transfer capacitance, in conjunction with the Gate drive source resistance, determines the rate of drain voltage fall at turn-on and rise at turn-off.

The IGBT collector-gate  $C_{RES}$  capacitance acts similarly by limiting the rate of  $V_{CE}$  fall at turn-on. At turn-off, the IGBT  $C_{RES}$  may cause multiple switching if the gate drive resistance  $R_{off}$  is not sufficiently small. In this case, the equivalent MOSFET (Figure 1) turns off, but the VCE does not rise until after the excess charge is cleared from the BJT. At that point, the rapidly rising collector voltage and  $C_{RES}$  may drive a current into  $R_{off}$  that re biases the N-channel MOSFET back into conduction.

The gate drive coulomb charge  $Q_G$  required to switch MOSFETs and IGBTs are very similar. The FGP20N60S2D IGBT  $Q_G = 30$  nC for  $V_{CE} = 300$  V,  $I_{CE} = 7$  A and  $V_{gate} = 15$  V. Gate charge for FCP11N60 is 40 nC for  $V_{DS} = 400$  V,  $I_D = 11$ A and  $V_{gate} = 10$  V.

In typical hard-switched applications, different gate drive turn-on and turn-off impedances are required, as illustrated in Figure 8. As previously described, turn-on resistance is typically set to control turn-on  $di/dt$ . The turn-off impedance is set much lower, particularly for MOSFETs where the switching speed can be greatly impacted by the speed at which the  $V_{GE}$  voltage is pulled to zero potential.

The FOM, or Figure of Merit, which is the gate charge  $Q_{G(on)}$  times  $R_{DS(on)}$  is often used for comparing MOSFETs; the lower the FOM, the better the devices performance. This comparison is only valid, however, if compared under identical conditions. That is typical parameter versus typical parameter or max versus max at the same  $T_j$ ,  $V_{DS}$ ,  $V_{GS}$  and  $I_D$ .

## Thermal Management

One of the more critical parameters in optimizing SMPS component selection is the thermal system. If the SMPS will operate in a high thermal ambient, or has a marginal heatsink, the only solution may be to select a larger die size or to parallel power devices. Another key thermal factor is the thermal interaction between power devices. A good example is the boost diode and boost switch in a CCM boost PFC circuit. If the circuit is hard-switched then the primary switch loss is the Eon turn-on, which is predominantly a function of the boost diode. If the boost diode is closely coupled thermally to the boost switch, an interaction will occur. Eon loss in the switch will raise the boost diode temperature. This in turn will increase the diode  $I_{RRM}$  further increasing the switch Eon loss.

For hard-switched operating frequencies in the range of 50 kHz or greater, the cooling system often determines the choice between IGBTs and MOSFETs. If the design is below 50 kHz, and sufficient cooling is available, the IGBT may be the optimum choice. However, if the boost switch losses must be spread out over a broader area requiring device paralleling, the MOSFET should be chosen since its PTC characteristics will ensure load current sharing.

## Conclusions

While IGBT and MOSFET gate drive requirements are similar, subtle differences in minimum required gate drive voltage and gate drive source resistance require adjustments when switching from one device to the other. There is no across-the-board solution when using power switching devices; circuit topology, operating frequency, ambient temperature and physical size constraints all play a part in determining the optimum choice. In ZVS and ZCS applications with minimized Eon losses, MOSFETs are capable of operating at higher frequencies because of their faster switching and lower turn-off losses. For hard-switched applications, the MOSFET parasitic body diodes recovery characteristics can be a detriment. Conversely, since IGBT co-pack diodes are matched to the specific application, excellent soft-recovery diodes are matched with the higher speed SMPS rated devices.

## Endnotes

<sup>1</sup>Pittet, Serge and Rufer, Alfred *Analytical analysis of Quasi-Saturation Effect in PT and NPT IGBTs* PCIM Europe 2002  
[http://leiwwww.epfl.ch/publications/pittet\\_rufer\\_pcim\\_02.pdf](http://leiwwww.epfl.ch/publications/pittet_rufer_pcim_02.pdf)

<sup>2</sup>Kolar, J.W., Ertl, H., and Zach, F.C. (1998), *How to include the dependency of the  $R_{ds(on)}$  of power MOSFETs on the instantaneous value of the drain current into the calculation of the conduction losses of high-frequency three-phase PWM inverters*, IEEE Trans. Ind. Electronics, Vol. 45, No.3, pp. 369–375, June 1998.

<sup>3</sup>Stuart, T.A., and Shaoyan Ye (1994), *Computer simulation of IGBT losses in PFC circuits*, IEEE 4th Workshop on Computers in Power Electronics, pp.85–90, 1994.

<sup>4</sup>Masserant, B. and Stuart, T.A., (1996), *Experimental verification of calculated IGBT losses in PFCs*, IEEE Transactions on Aerospace and Electronic Systems, Vol. 32, No. 3, pp. 1154–1158, July 1996.

<sup>5</sup>Elasser, A., Parthasarathy, V., and Torrey, D. A. *A Study of the Internal Device Dynamics of Punch-Through and Nonpunch-Through IGBT's Under Zero-Current Switching*, IEEE Trans. on Power Electronics, Vol. 12 No. 1, pp 21–35, January 1997.

## About the author

Ron Randall is staff applications engineer, Fairchild Semiconductor

Ron.Randall@fairchildsemi.com

phone: 585-968-2892

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at [www.onsemi.com/site/pdf/Patent-Marking.pdf](http://www.onsemi.com/site/pdf/Patent-Marking.pdf). ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA  
**Phone:** 303-675-2175 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 303-675-2176 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada  
**Europe, Middle East and Africa Technical Support:**  
Phone: 421 33 790 2910  
**Japan Customer Focus Center**  
Phone: 81-3-5817-1050

**ON Semiconductor Website:** [www.onsemi.com](http://www.onsemi.com)  
**Order Literature:** <http://www.onsemi.com/orderlit>  
For additional information, please contact your local  
Sales Representative