

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



Is Now Part of



ON Semiconductor®

To learn more about ON Semiconductor, please visit our website at
www.onsemi.com

ON Semiconductor and the ON Semiconductor logo are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.



Mid-Voltage Shielded PowerTrench® MOSFET in High Step-Up DC-DC for Edge-Lit LED TV Backlighting

1. Introduction

Thanks to lower power consumption and longer life, coupled with increased demands for a wide color gamut; light-emitting diodes (LEDs) are steadily replacing the Cold-Cathode Fluorescent Lamp (CCFL) as the backlight source for Liquid Crystal Display (LCD) panel television sets. To generate sufficient brightness for large-scale LCD TVs, backlight requires many series or parallel LED arrays. Arrangement of the arrays determines whether an LED Backlight Unit (BLU) is an edge-lit or a direct-lit type, as shown in Figure 1 and Figure 2. Because the number of LEDs and strings can be reduced, edge-lit BLUs are increasingly popular. In edge-lit BLUs, high-efficiency and high step-up ratio DC-DC converters are required to operate the serially connected LED strings. Fairchild's mid-voltage shielded PowerTrench® gate technology allows reduced on-resistance ($R_{DS(ON)}$) without incurring a gate-charge (Q_g) characteristics penalty, which results in reducing conduction loss and switching loss in high step-up DC-DC converters.



Figure 1. Edge-Lit LEDs

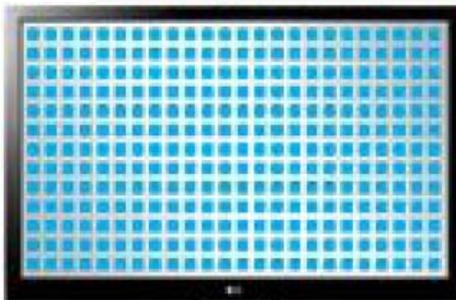


Figure 2. Direct-Lit LEDs

2. Edge-Lit LED BLU Power Requirement

The BLU in LCD TV sets plays an important role in the overall cost of the application. It can account for 30-40% of the total cost and is integral in the final angular luminance, contrast ratio, and brightness.

For an edge-lit BLU in large-size TV sets, approximately 36 LEDs are placed in series at the edge of the BLU. This requires the power supply to deliver a high voltage, up to 120V, from 24V of SMPS output and a stable current source over a 40-inch panel.

Table 1. Edge-Lit LED BLU Power Build Example

Panel Size	>40 Inches
V_{IN}	24V
V_{OUT}	120V
I_{LED}	120mA
f_{sw}	300KHz
LEDs per String	36
Strings	4

3. Coupled-Inductor Boost DC-DC Converter

To meet the requirements of edge-type LED backlight power, such as high step-up voltage gain and high efficiency, a coupled-inductor boost DC-DC converter like the one shown in Figure 3 is a viable solution. It can deliver high step-up voltage gain without the penalty of extreme duty ratio and can reduce the conduction loss of the MOSFET because a lower B_{VDSS} MOSFET can be applied against single-boost DC-DC converter by using the turn ratio of the coupled inductor.

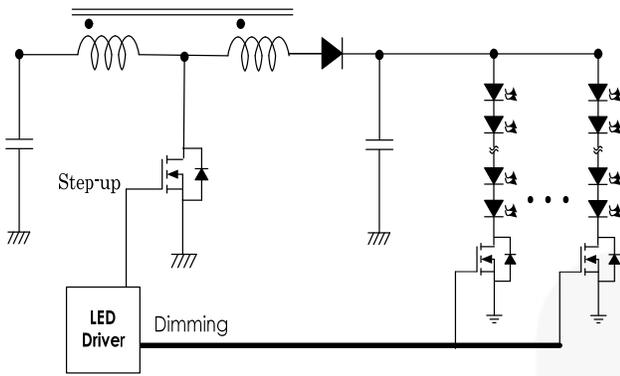


Figure 3. Simplified LED Driver Block Diagram: Coupled-Inductor Boost Converter

A coupled-inductor boost converter has two operation modes in one switching cycle, MOSFET on and off state, as shown in Figure 4. Figure 5 shows converter waveforms through one switching cycle. During $t_0 - t_1$, the MOSFET is turned on and the output rectifier D_{out} is reversed-biased. The magnetizing inductor, L_m , is charged linearly by the input voltage source. When the MOSFET is turned off, all magnetizing current is reflected to the secondary winding, N_s , from the primary winding, N_p , during $t_1 - t_2$. The output rectifier, D_{out} , is conducting and all the energy stored in the inductor has been delivered to the output load.

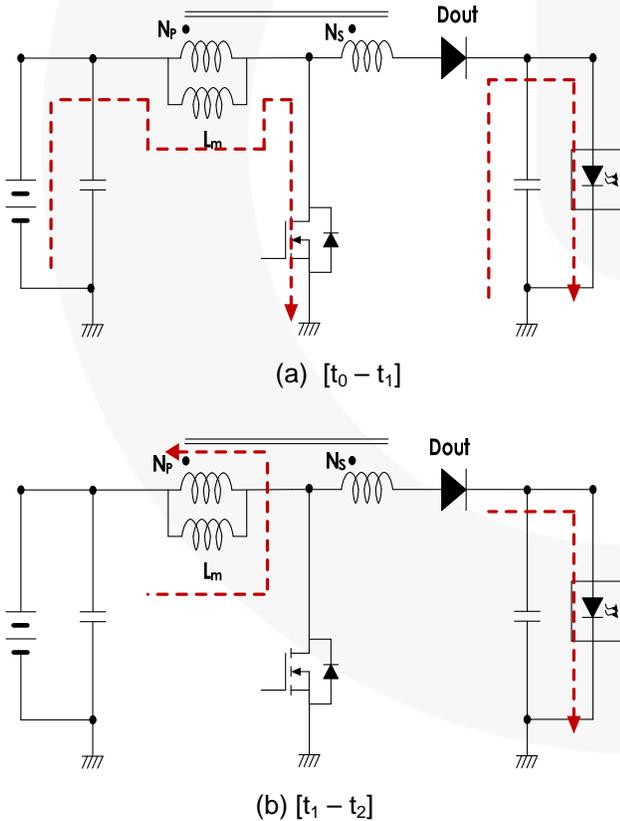


Figure 4. Topological Stages with Reference Directions of Key Current

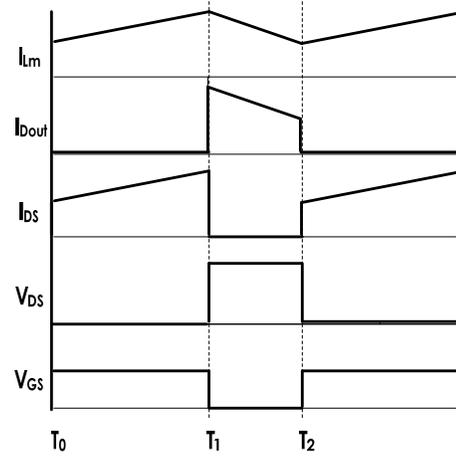


Figure 5. Converter Waveforms

The voltage conversion ratio is given by:

$$D = \frac{V_{OUT} - V_{IN}}{V_{OUT} + N \times V_{IN}} \tag{Eq 1}$$

where D is duty cycle and n is the turns-ratio of the coupled inductor, calculated as:

$$n = \frac{N_s}{N_p} \tag{Eq 2}$$

4. Mid-Voltage Shielded Power Trench[®] MOSFET

The trend in TV set power-supply design focuses on increasing efficiency by reducing power losses. To maximize a power system's efficiency, it is important to select a switching device with low on-resistance ($R_{DS(ON)}$) and gate charge (Q_g) characteristics.

A new trench MOSFET process allows for a reduction in $R_{DS(ON)}$ without incurring a Q_g penalty. This technology, known as shielded gate, enables reduction of the epi resistance associated with achieving the $B_{V_{dss}}$, the key component of $R_{DS(ON)}$, in mid-voltage MOSFETs. This technology has particular benefits in the $>100V$ area.

Table 2. Components of $R_{DS(ON)}$ for Conventional Trench, $R_{DS(ON)}$ $V_g = 10V, 200A/cm^2$

	$V_{DS} = 30V$	$V_{DS} = 100V$
R_{Chan}	47%	16%
R_{EPI}	29%	78%
R_{Sub}	24%	6%

Table 2 shows the $R_{DS(ON)}$ components, comparing a 30V-rated with a 100V-rated conventional trench MOSFET. The $R_{DS(ON)}$ contribution from the epitaxial is a much larger percentage for the 100V MOSFET. Using a charge-balance technique like the shielded gate, this epitaxial resistance can be reduced by more than half without increasing the total Q_g or the Q_{gd} component.

5. The Charge Balance Technique

Figure 6 compares the cross-sections of a conventional and a shielded-gate trench device. By incorporating a shield electrode for charge balancing, the resistance and length of the voltage-supporting region is reduced and a significant reduction in $R_{DS(ON)}$ can be realized.

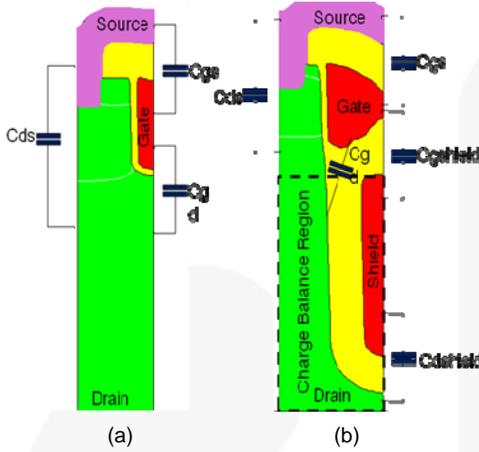


Figure 6. Conventional (a) vs. Shielded-Gate (b) Charge-Balance Trench Structure

The shield electrode resides below the gate electrode, converting most of the gate-to-drain capacitance (C_{gd} or C_{rss}) at the bottom of the conventional trench MOSFET to gate-to-source capacitance (C_{gs}). The shield electrode shields the gate electrode from the drain potential.

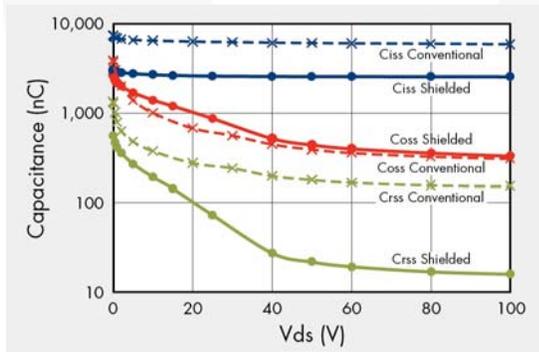


Figure 7. Comparison of Capacitive Components for Conventional and Shielded-Gate Trench with Equivalent 20A $R_{DS(ON)}$ 5.7m Ω

Figure 7 compares the capacitive components of a conventional and a shielded-gate trench MOSFET with equivalent $R_{DS(ON)}$. By reducing C_{rss} , switching losses are minimized by shortening the time it takes to transition from OFF to ON state or from ON to OFF state. In particular, reducing the Q_{gd} , as show in Figure 8, reduces the switching energy losses by minimizing the time the device has the simultaneous application of high voltage and current.

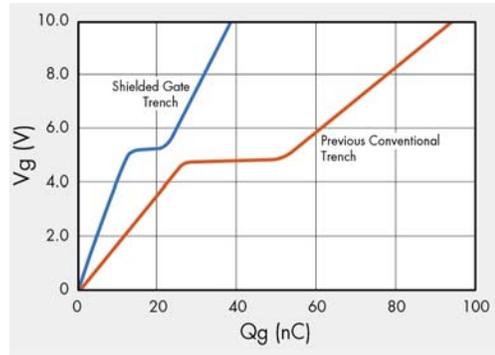


Figure 8. Comparison of Q_g Curves at 20A and 50V for Conventional and Shielded-Gate Trench with Equivalent 20A $R_{DS(ON)}$ 5.7m Ω

The shield and its resistance act as a snubbing resistance (R_{shield}) and capacitance ($C_{dshield}$) network, depicted as a component of the C_{oss} in Figure 9.

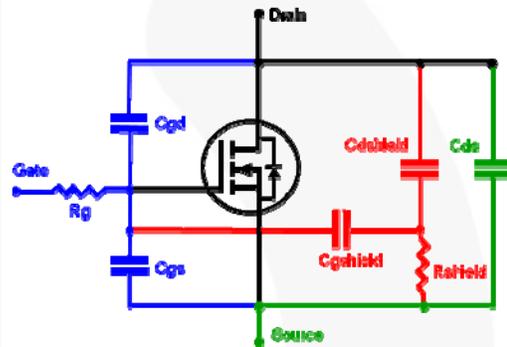


Figure 9. Shielded-Gate MOSFET Resistive and Capacitance Equivalent Circuit

This snubbing network slows down the transition of the switching from low to high voltage. This feature of the shielded gate helps to reduce EMI, dv/dt induced turn-on, and avalanching during switching transitions.

Fairchild Semiconductor offers all these features of mid-voltage shielded PowerTrench[®] gate technology (B_{VDSS} : 60-150V), which provides low gate-charge and on-resistance ratings to achieve low switching, conduction losses, and minimized EMI.

6. Performance Improvements in Coupled-Inductor Boost DC-DC Converter

Fairchild's 100V-rated FDD86102 shielded PowerTrench[®] MOSFET is compared with conventional trench MOSFET on a coupled-inductor boost DC-DC converter to step up from 24V to 120V, which is a suitable solution for a more than 40-inch edge-lit type BLU. Table 3 shows the shielded device's superior $R_{DS(ON)}$ and Q_g performance with shielded PowerTrench[®] process. Figure 10 shows how much switching energy can be reduced with FDD86102 compared to conventional trench-gate technology.

Table 3. Comparison with Conventional Trench
 $R_{DS(ON)}$: Max. Value, R_{sp} (Die Size x $R_{DS(ON)}$), Relative)

Device	$R_{DS(ON)}$	R_{sp}	Q_g	Q_{gd}	Q_{gs}	FOM
FDD86102	24	1	13.4	3.7	4	88.8
Conventional	28	2.2	38.5	10	8	280

In Figure 10 through Figure 12, the FDD86102 with shielded PowerTrench[®] MOSFET shows a minimum of 3.5% efficiency improvement and better thermal performance than conventional trench-gate technology by minimizing conduction loss and switching loss.

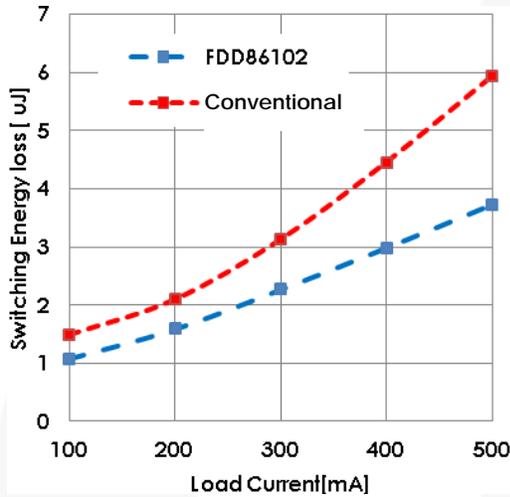


Figure 10. Switching-Energy Loss Comparison
 $24V_{IN}$ $120V_{OUT}$ $300KHz$ $500mA_{OUT}$


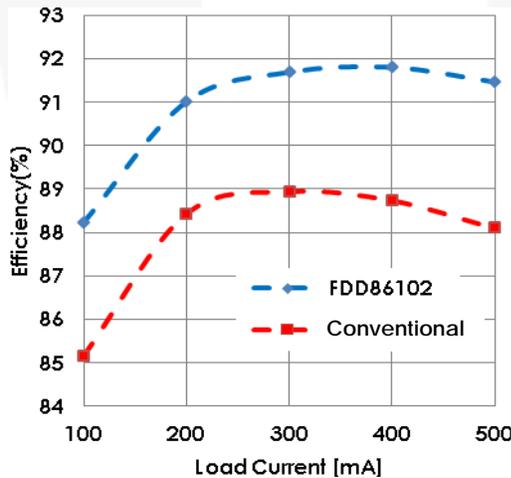


Figure 11. Efficiency Comparison
 $24V_{IN}$ $120V_{OUT}$ $300KHz$ $500mA_{OUT}$

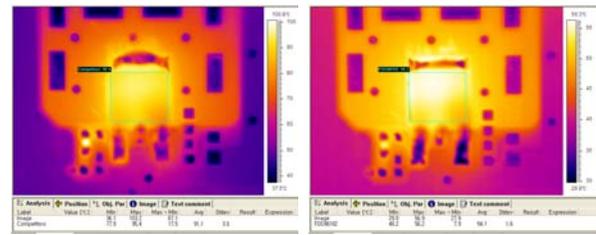

(a) FDD86102: 56.2°C (b) Conventional: 95.4°C

Figure 12. Thermal Performance Comparison
 $24V_{IN}$ $120V_{OUT}$ $300KHz$ $500mA_{OUT}$

Higher efficiency and low temperature characteristics are critical parameters in LCD displays with respect to size and thickness. Generally, a thermal increase of the main component in display systems, such as a MOSFET and inductor, should not exceed 65°C at 25°C room temperature without airflow.

7. Conclusion

Compare with conventional trench MOSFET, Fairchild’s mid-voltage shielded PowerTrench[®] MOSFET technology can achieve higher efficiency by minimizing conduction loss and switching loss.

Authors

SungJin Kuen – LV Applications Engineer
Dongsup Eom – LV Applications Engineer
Joe. Yedinak – Product design Engineer

Related Datasheets

[FDD86102 — 100V N-Channel PowerTrench[®] MOSFET](#)

DISCLAIMER

FAIRCHILD SEMICONDUCTOR RESERVES THE RIGHT TO MAKE CHANGES WITHOUT FURTHER NOTICE TO ANY PRODUCTS HEREIN TO IMPROVE RELIABILITY, FUNCTION, OR DESIGN. FAIRCHILD DOES NOT ASSUME ANY LIABILITY ARISING OUT OF THE APPLICATION OR USE OF ANY PRODUCT OR CIRCUIT DESCRIBED HEREIN; NEITHER DOES IT CONVEY ANY LICENSE UNDER ITS PATENT RIGHTS, NOR THE RIGHTS OF OTHERS.

LIFE SUPPORT POLICY

FAIRCHILD'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF FAIRCHILD SEMICONDUCTOR CORPORATION.

As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, or (c) whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local
Sales Representative