

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



High-Performance CMOS Analog Switches

Prepared by: Fred Zlotnick
Logic Applications Engineering

APPLICATION NOTE

INTRODUCTION

Eleven new devices have recently been introduced by ON Semiconductor, adding to its large array of analog switches, already available. The new devices are offered in multi-gate and one-gate configurations. This latest offering entails a low-resistance, high frequency response product, providing improved performance for a lower cost to the designer.

Less than 15-Ohms Resistance

The eleven new analog switches include the MC74LVX4066, 8051, and 8053; their TTL-Compatible versions – MC74LVXT4066, 8051, and 8053; two new one-gate devices – M7CVHC1G66 and 1GT66; and three new VHC products – the MC74VHC4051, 4052, and 4053. The new devices compliment the standard offering of analog switches, multiplexers, and demultiplexers.

Designed as either a single-voltage supply from two to six volts for the standard parts or five volts for the TTL-compatible “T” versions, the additions will suit many applications. Typical resistance values are less than 15 ohms for many of the devices when operating at five volts compared to the industry-standard of 80 ohms to 100 ohms. The multi-gate products are available in both 16-lead SOIC, as well as TSSOP packages, while the single-gate devices are available in industry-standard SC-88a, five-lead packages.

Ideal for Wireless, Analog or Digital

ON Semiconductor’s new high-performance portfolio can be utilized in many diverse, applications and markets, including wireless, computing, and standard telecommunication systems. The devices primarily accomplish the switching, multiplexing, and demultiplexing of both analog and digital signals. Many so-called digital signals are actually quasi-analog in nature, such as frequency shift key (FSK), phase-shift key (PSK), quadrature amplitude modulation (QAM), code division multiplex (CDMA), and time division multiplexing (TDMA). As a result, they need to share the decoding from several different input sources, with minimum distortion to the signal. And in consumer products, switching between two or more analog sources is a constant requirement.

As an example of an application (Figure 1), one of eight sources could be selected to decode for a Dolby Digital or DTS decoder. A stereo receiver would likely have a single audio decoder, but would need to switch between up to eight inputs to be connected to a single (potentially costly) decoder. The demultiplexer is not only low cost, but also minimizes the loss and distortion that is added to the circuit. The frequency required for an example, such as the one pictured, falls in the 10 MHz range.

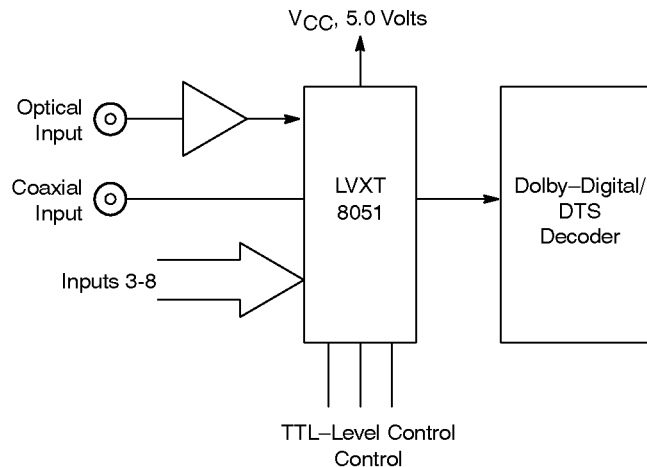


Figure 1.

Very High-Speed CMOS Offerings

Among the eleven analog-switch family additions, ON Semiconductor is offering three new Very High Speed CMOS (VHC) devices – the MC74VHC4051, 4052, and 4053 that provide improved performance over previous offerings. These new VHC devices allow operation with both positive and negative supplies. This feature allows for switching an AC waveform that is centered approximately zero volts with no coupling capacitors.

A ± 3.3 V-supply allows for a 5 V peak-to-peak waveform, with LVTTL/CMOS compatibility. The DC level is preserved for the case of video switching. The VHC4053 is especially ideal for switching beyond 30 MHz. The following diagram (Figure 2) illustrates switching two audio channels from three sources and three video channels simultaneously. The signal levels may be ± 2.5 volts.

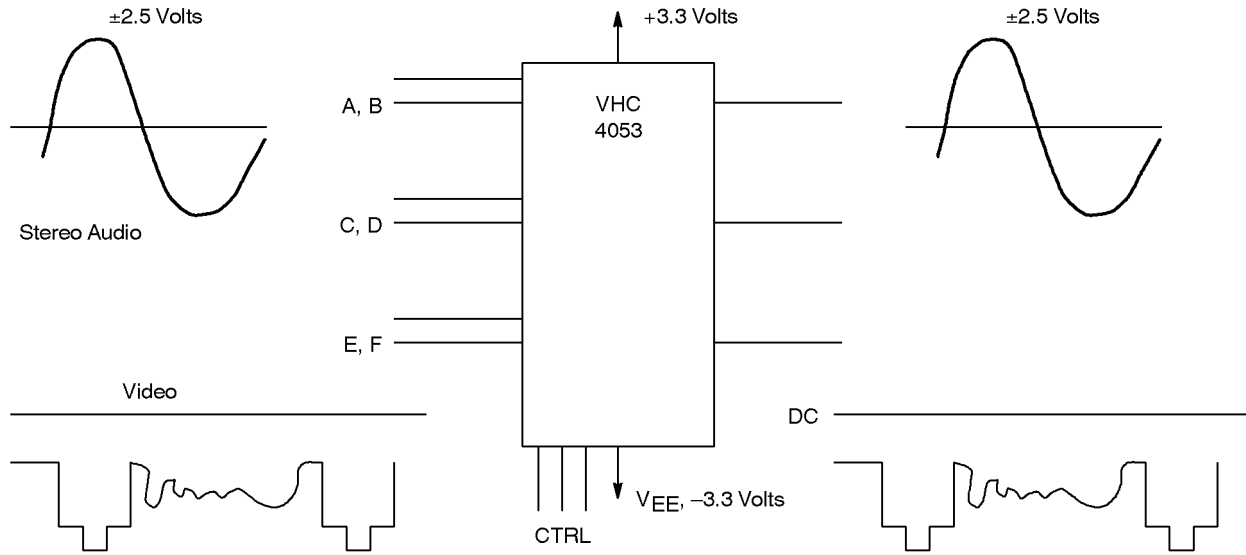


Figure 2.

Two Dynamic New One-Gate CMOS

Two new single-gate products were also introduced into ON Semiconductor's advanced, sub-micron VHC family – the MC74VHC1G66 and MC74VHC1GT66. These new devices offer a single analog-switch function and

impressive AC-performance levels. Figure 3 illustrates a way to change a time constant in a loop filter application for fast "attack" stable "hold" using the MC74VHC1G66.

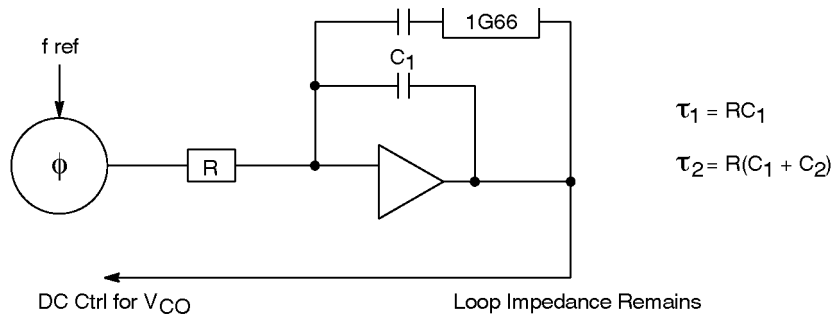



Figure 3.

Notes

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer.

PUBLICATION ORDERING INFORMATION

NORTH AMERICA Literature Fulfillment:

Literature Distribution Center for ON Semiconductor
 P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: ONlit@hibbertco.com
 Fax Response Line: 303-675-2167 or 800-344-3810 Toll Free USA/Canada

N. American Technical Support: 800-282-9855 Toll Free USA/Canada

EUROPE: LDC for ON Semiconductor – European Support

German Phone: (+1) 303-308-7140 (Mon-Fri 2:30pm to 7:00pm CET)
Email: ONlit-german@hibbertco.com
French Phone: (+1) 303-308-7141 (Mon-Fri 2:00pm to 7:00pm CET)
Email: ONlit-french@hibbertco.com
English Phone: (+1) 303-308-7142 (Mon-Fri 12:00pm to 5:00pm GMT)
Email: ONlit@hibbertco.com

EUROPEAN TOLL-FREE ACCESS*: 00-800-4422-3781

*Available from Germany, France, Italy, UK, Ireland

CENTRAL/SOUTH AMERICA:

Spanish Phone: 303-308-7143 (Mon-Fri 8:00am to 5:00pm MST)
Email: ONlit-spanish@hibbertco.com
Toll-Free from Mexico: Dial 01-800-288-2872 for Access –
 then Dial 866-297-9322

ASIA/PACIFIC: LDC for ON Semiconductor – Asia Support

Phone: 303-675-2121 (Tue-Fri 9:00am to 1:00pm, Hong Kong Time)
Toll Free from Hong Kong & Singapore:
001-800-4422-3781
Email: ONlit-asia@hibbertco.com

JAPAN: ON Semiconductor, Japan Customer Focus Center

4-32-1 Nishi-Gotanda, Shinagawa-ku, Tokyo, Japan 141-0031
Phone: 81-3-5740-2700
Email: r14525@onsemi.com

ON Semiconductor Website: <http://onsemi.com>

For additional information, please contact your local Sales Representative.