

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.

Make a White-LED Torch Using a Buck Converter

Prepared by: Bertrand RENAUD
ON Semiconductor



ON Semiconductor®

<http://onsemi.com>

APPLICATION NOTE

Introduction

Very popular in portable backlight applications, the white LED finds more and more derivatives on adjacent market. Its small package size and light efficient conversion contribute to replace standard illumination solution. White LED considerably improves their technologies in the last years and where a DC-DC boost or buck-boost converter was required for a given illumination, you can now place a DC-DC buck converter.

Higher current with lower forward voltages and you can now address flashlights, head-mounted lighting, bicycle lighting, solar-powered lighting, torch and other battery-powered lighting applications.

This application note will detail the method of making White LED torch application using NCP1529.

NCP1529 integrated circuit is a high frequency stand alone DC to DC buck converter. Designed for portable markets, it is able to supply voltages from 0.9 V to 3.3 V by an external resistor divider and to provide up to 1 A. Based on current mode architecture, its large bandwidth fills fast transient requirements of handled devices. Additional features include integrated soft-start, cycle-by-cycle current limiting and thermal shutdown protection.

Application Objective

Knowing that light intensity of a White LED depends on its forward current, not on its forward voltage; the main objective of this application is to regulate a constant current with a converter typically used to regulate a constant voltage. The proposal must be both accurate and energy efficient and must be able to support low frequency dimming (below 10 Hz) for distress alert application and PWM medium frequency dimming (from 100 Hz to 1 kHz) to adjust light intensity.

This application note will take the example of regulating a constant current of 800 mA through a single die LED. Input voltage range can be based on standard 5 V rails or battery cells arrangement which does not exceed maximum rating of the NCP1529.

The NCP1529 – DC-DC buck converter housed in UDFN-6 package – is selected for its high power conversion and high thermal dissipation capabilities. Moreover, loop control which allows 100 % duty cycle operation extends play time when battery voltage is closed to forward voltage.

The White LED of interest selected for this demonstration is the CREE XP-G which delivers unprecedented levels of light output and efficacy for a single die LED. At 800 mA forward current, following figure shows that forward voltage is below 3.25 V.

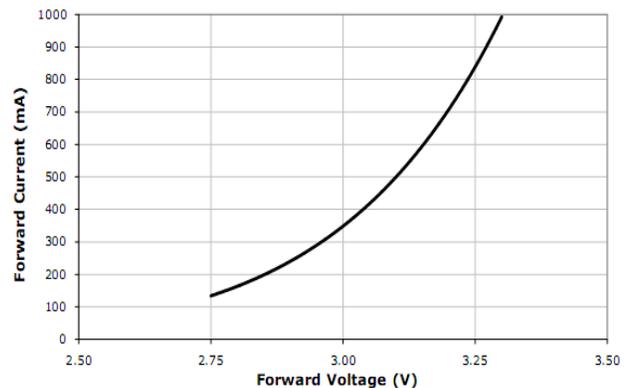


Figure 1. Shows CREE XP-G Forward Voltage Characteristics

Making a Schematic

Most of the DC-DC step down converters regulate a constant voltage using a divider network set to provide a given feedback voltage at 500 mV or 600 mV. The NCP1529 reference voltage is 600 mV.

Reducing this voltage to 80 mV for instance will considerably increase play time of your torch and improve system efficiency.

A simple and low cost solution could be to reduce feedback network using an additional resistor as shown in Figure 2.

AND8465/D

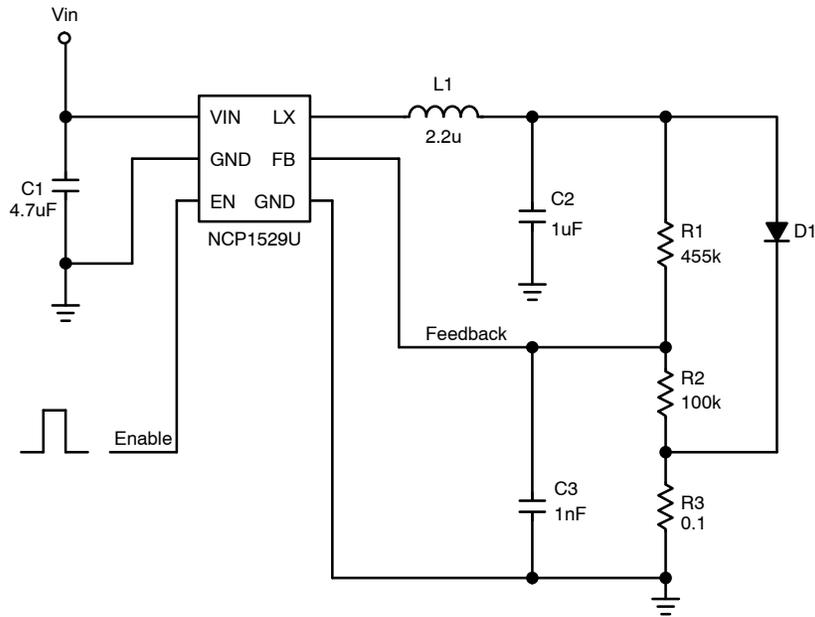


Figure 2. Presents a Simple Solution to Reduce Current Sense Voltage

To get 800 mA through the White LED implies $R3 = 0.1 \Omega$. The resistor bridge R1 and R2 is given by:

$$R1/R2 = (V_f + 80 \text{ mV}) / 600 \text{ mV} - 1 \quad (\text{eq. 1})$$

Having $R2 = 100 \text{ k}\Omega$ leads to $R1 = 455 \text{ k}\Omega$

This equation puts forward that NCP1529 is still used as voltage regulator. Consequently light intensity will vary upon the forward voltage of the LED and this parameter is generally subject to a large deviation. At the end, system

engineer will observe a light intensity differences from one torch to another one.

A method to regulate a constant current uses the benefits of current mirror with a high divider ratio. Two additional PNP bipolar transistors are required for the proposal shown in Figure 3. Bipolar used for mirroring are usually paired on the same die for maximum matching and proposed as a single solution.

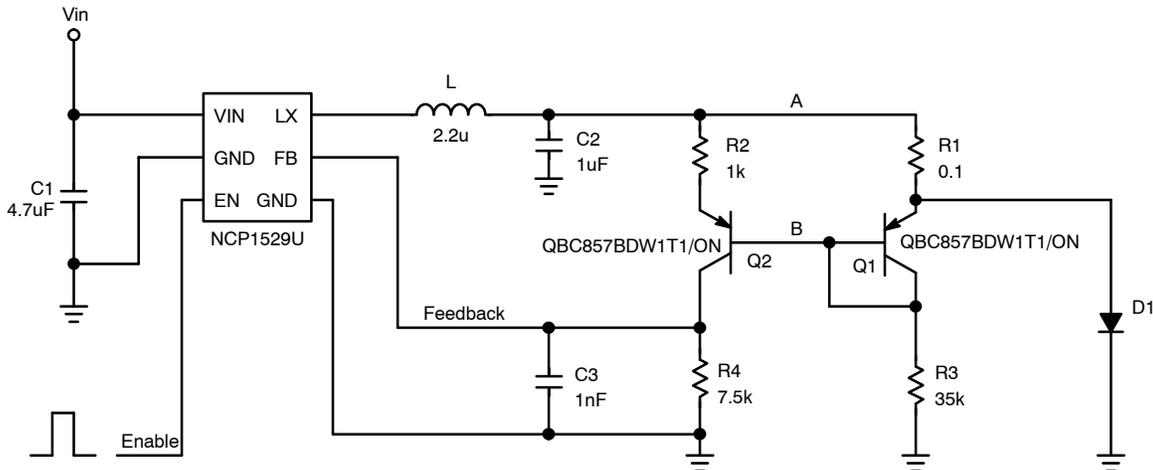


Figure 3. Regulates the Forward Current of the LED

In that example, the current flowing R3 can be considered as negligible. R1 is the sense resistor used to regulate the 800 mA of interest, e.g. $I1$. The voltage drop across Q1 is V_{be1} . Q1 is diode connected and sets V_{be2} for transistor Q2. Because Q1 and Q2 are matched and their β_0 agreed, V_{be2}

$= V_{be1}$. The node law leads to write the equation between nodes A and B:

$$R2 \times I2 = R1 \times I1 \quad (\text{eq. 2})$$

AND8465/D

I2 is the current flowing transistor Q2, this current is given by the 600 mV reference voltage.

$$I2 = \text{Feedback} / R4 \quad (\text{eq. 3})$$

Finally, the equation given by the mirror is:

$$I1 = \text{Feedback} \times R2 / (R1 \times R4) \quad (\text{eq. 4})$$

Normally the complete equation without the assumption on R3 is:

$$I1 = \text{Feedback} \times R2 / (R1 \times R4) - I3 \quad (\text{eq. 5})$$

Most of the design engineers will be satisfied by this proposal both accurate and efficient. Compensate the current flowing R3 is also possible but require two additional NPN paired bipolar transistor as pictures by Figure 4.

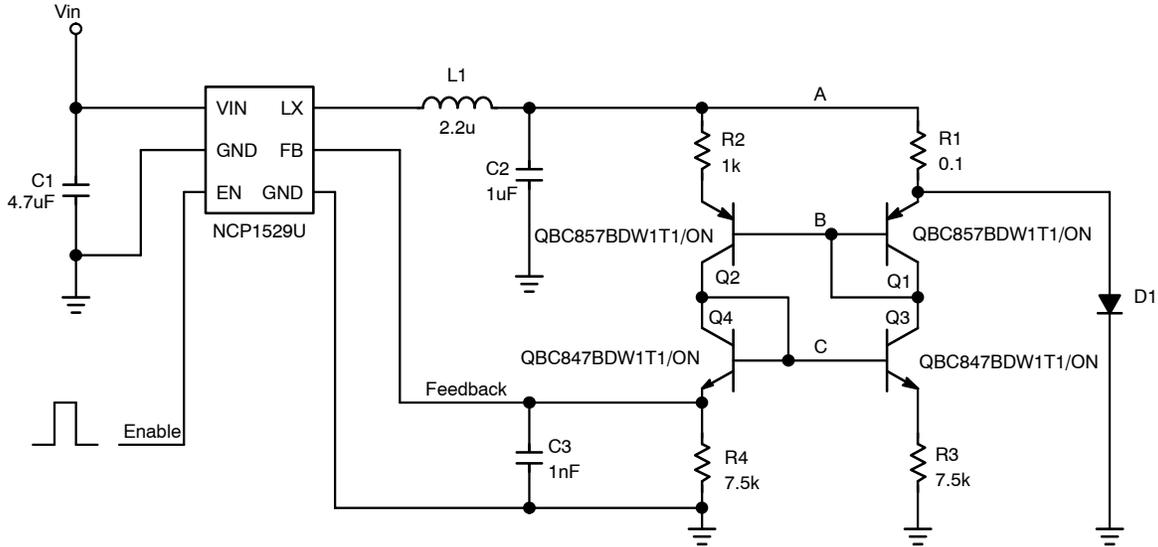


Figure 4. Eliminates the Current Mismatch Due to R3

The difference with previous proposal is to compensate current flowing R3. In that case, the complete equation is:

$$I1 = \text{Feedback} \times R2 / (R1 \times R4) \quad (\text{eq. 6})$$

This schematic will serve as reference for the rest the application note.

AND8465/D

Dimming

Schematic of Figure 4 provides good results on system accuracy (LED current is 800 mA as expected), on loop stability and control and on use of dimming from 0% to 100%. It is recommended to apply a dimming signal on EN

pin below 1 kHz in order to minimize soft start over the dimming period and keep the benefit of system accuracy.

Figures from 5 to 7 illustrate dimming examples at 200 Hz from 10% to 90%.

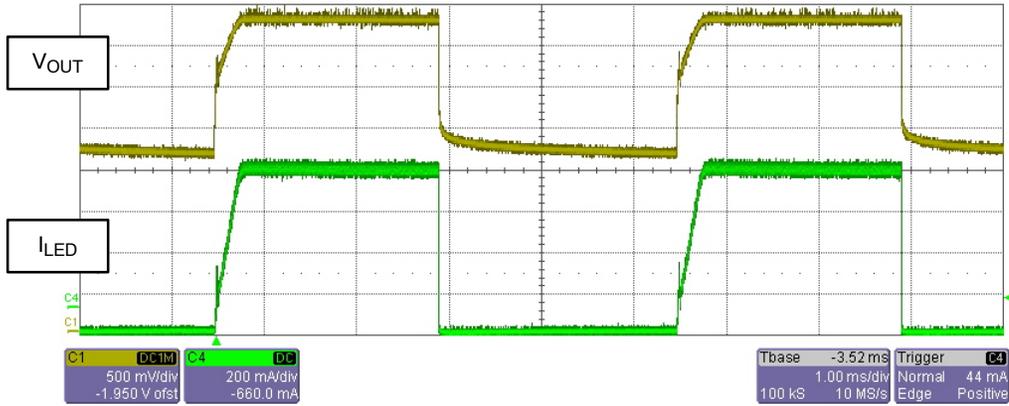


Figure 5. Is 50% at 200 Hz Dimming on EN Pin

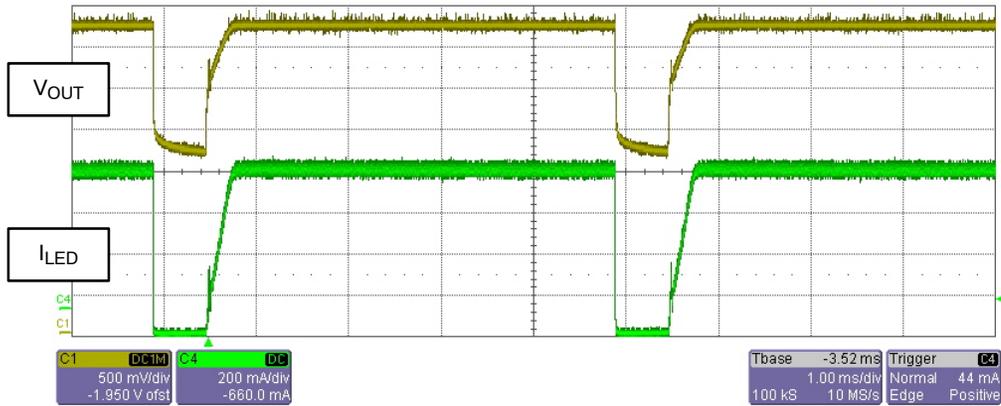


Figure 6. Is 90% at 200 Hz Dimming on EN Pin

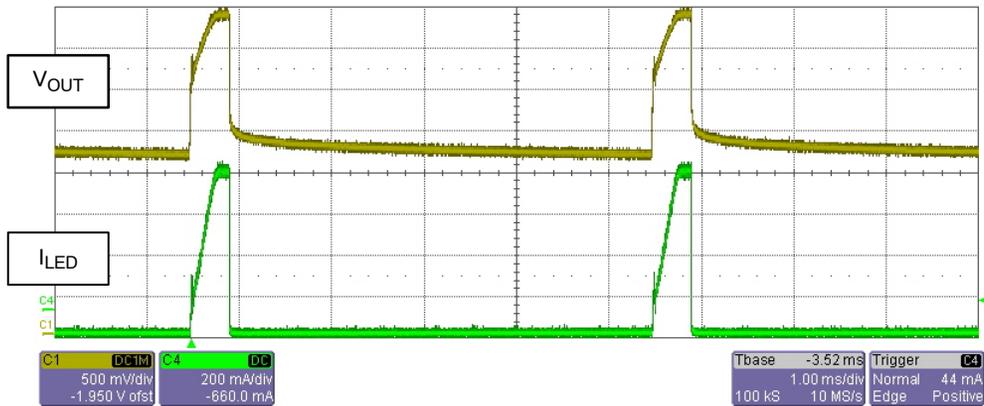


Figure 7. Is 10% at 200 Hz Dimming on EN Pin

The soft start phase can be adjusted by C3 capacitor. A lower capacitor will decrease soft start time but will increase inrush current. Due to the integrated peak current protection which can protect the device and the application if peak

inductor current is higher than 1.6 A. A larger capacitor will increase soft start time but will reduce dimming accuracy as detailed before.

AND8465/D

Removing the output capacitor C2

Figure 8 pictures main operating signals when the device is supplied from a 5 V rail. To regulate the White LED forward current at 800 mA, the DC to DC converter regulates an output voltage at 3.43 V. This voltage includes

the forward voltage of the White LED plus the sense voltage through R1.

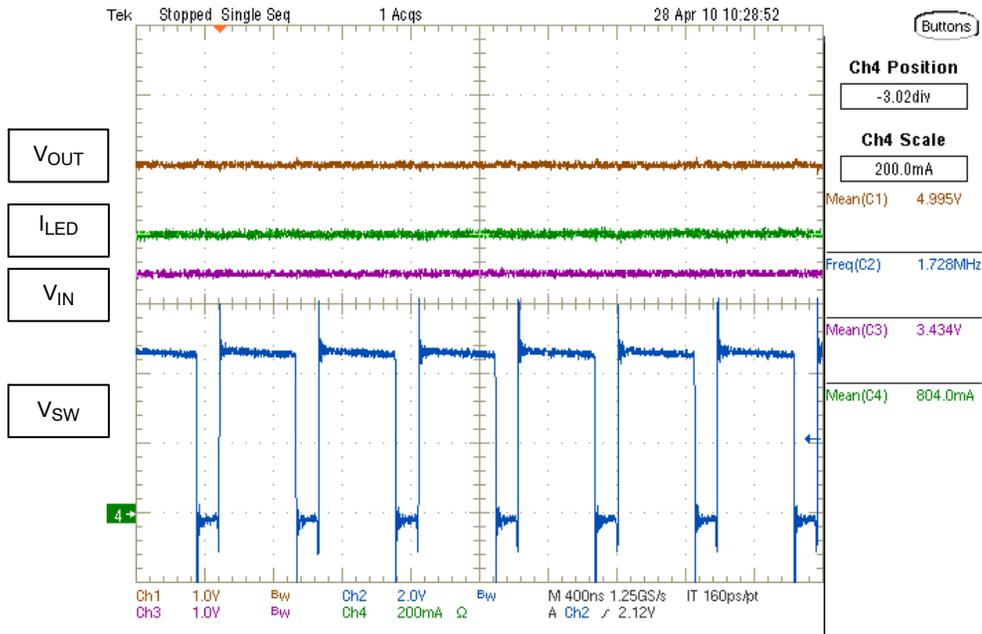


Figure 8. Zoom on Main Operating Signals

The simplest approach of the output capacitor on a high frequency switching step down converter is to form with the associated inductor a L-C filter. Its principle characteristics allow recovering a DC voltage from a square signal which operates from V_{IN} to GND.

Because the main criteria in this application is the forward current, not the output voltage; we can remove the output

capacitor, save one external component and lose the benefit of having a DC voltage at the output. In that case, forward current becomes a triangular signal which operates at NCP1529 switching frequency of 1.7 MHz: too fast to be visible.

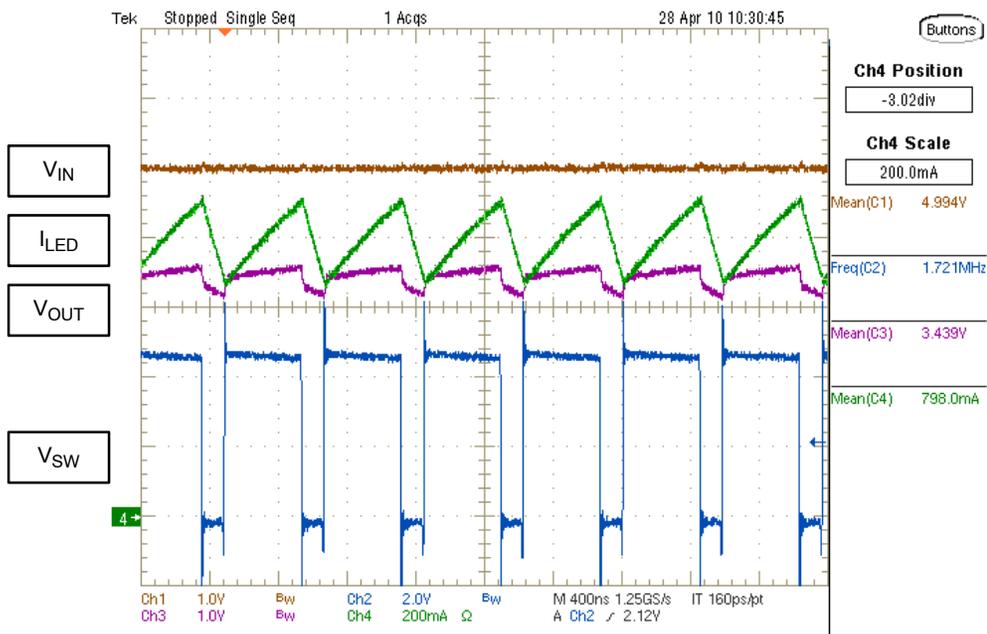


Figure 9. Presents Main Operating Signal Without Output Capacitor C2

AND8465/D

Demonstration Board Overview

A dedicated demonstration board is available upon demand. This board is valid for both schematics of Figure 4. and 5. Three high current White LED footprints are proposed:

- Phillips LUXEON® Rebels series
- OSRAM Golden DRAGON Plus series
- Cree XLamp™ XP series

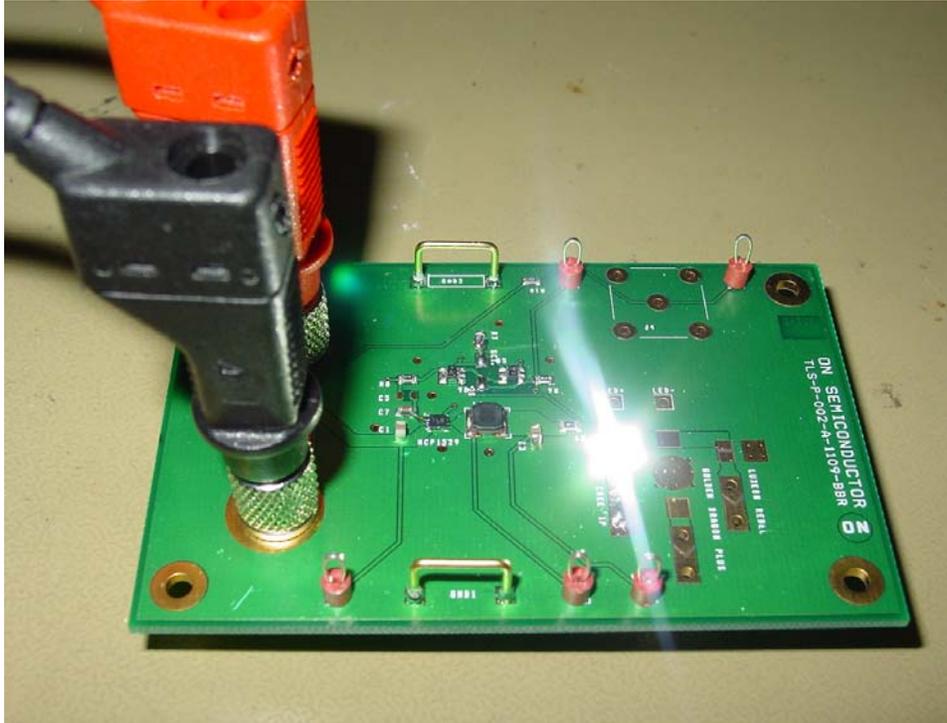


Figure 10. Is NCP1529 Torch Application Demonstration Board

The board is ideal for test purpose providing a dazzling amount of light. Knowing that the application will be optimized with a metallic cavity, we can imagine without

difficulty end result of this power efficient DC to Light conversion using NCP1529.

Golden DRAGON Plus is a registered trademark of OSRAM Opto Semiconductor.

LUXEON is a registered trademark of Phillips Lumileds Lighting Company and Royal Philips Electronics of the Netherlands.

XLamp is a trademark of Cree, Inc.

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada

Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910

Japan Customer Focus Center
Phone: 81-3-5773-3850

ON Semiconductor Website: www.onsemi.com

Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local
Sales Representative