

ON Semiconductor

Is Now

The logo for onsemi, featuring the word "onsemi" in a dark teal, lowercase, sans-serif font. The letter "i" is stylized with a white dot and a teal vertical bar. A small orange triangle is positioned above the top right of the "i". A trademark symbol (TM) is located to the right of the logo.

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.

An Off-Line, Power Factor Corrected, Buck-Boost Converter for Low Power LED Applications



ON Semiconductor®

<http://onsemi.com>

APPLICATION NOTE

Introduction

This application note introduces a universal input, off-line buck-boost converter with inherent power factor correction (PFC) for driving constant current LED lighting applications. The converter is intended for series string LED applications where currents up to 100 mA are required with series forward voltage drops from 35 to 120 Vdc. LED applications include strip lighting, linear fluorescent replacements, and wall packs where AC line-to-output isolation is not required. The circuit design is also compatible with most existing triac dimmers and is applicable for power levels up to about 8 W maximum, depending on the output voltage and current combinations. The maximum open circuit output voltage is easily adjustable as well as the output current. The buck-boost circuit is designed around ON Semiconductor's NCP1014 series of monolithic switcher ICs and provides a very simple and low cost approach to LED lighting applications. The buck-boost inductor is also available as an off-the-shelf component.

Basic Circuit Operation

The NCP1014 buck-boost converter circuit is shown in Figure 1 and is configured for a 65 mA output with a V_f maximum of 80 V with the open circuit output clamped at about 90 V. The output current is set by current sense resistor R10 ($I_{out} = 0.95/R10$). The forward voltage drop of the photo diode in optocoupler U2 provides the effective reference voltage for current sensing.

The output current can be trimmed upward with R14. $V_{out\ max}$ is set by the total series Zener diode voltage of $Z1 + Z2 + Z3 + 1$ V. R16 is for discharging output caps C9A/B when the converter is off and provides a pre-load which helps set the minimum dimness level when triac dimming is used.

The buck-boost converter is configured around monolithic controller U1 (NCP1014), rectifier D5, inductor L3 and output capacitors C9A and C9B. The inductor L3 is operated in continuous conduction mode (CCM) to minimize the peak-to-average current ratio and to maximize overall circuit efficiency. Efficiency curves for various output V_f values and for both nominal line voltages are shown in Figure 2 below.

AND9043/D

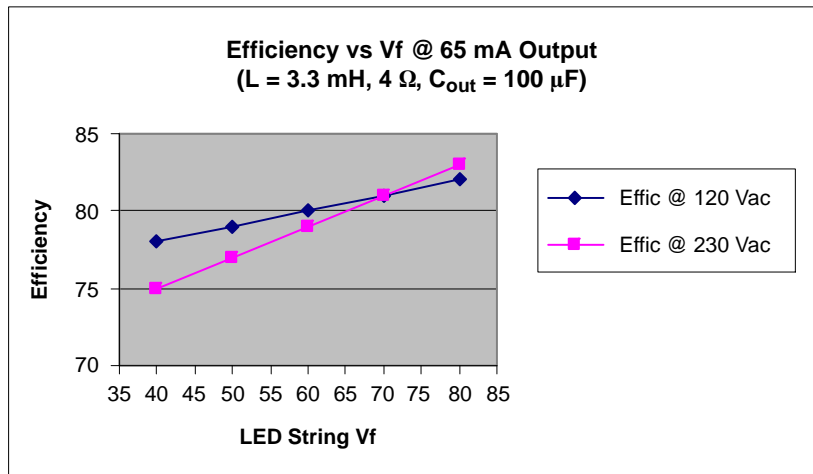


Figure 2. Efficiency versus Output Vf

The converter input circuit employs a conducted EMI filter comprised of L1, L2, L4, and C1. This filter is adequate for meeting FCC level B for conducted emissions as shown

in the green plot (average) of Figure 3. This is for the maximum rated output current of 100 mA.

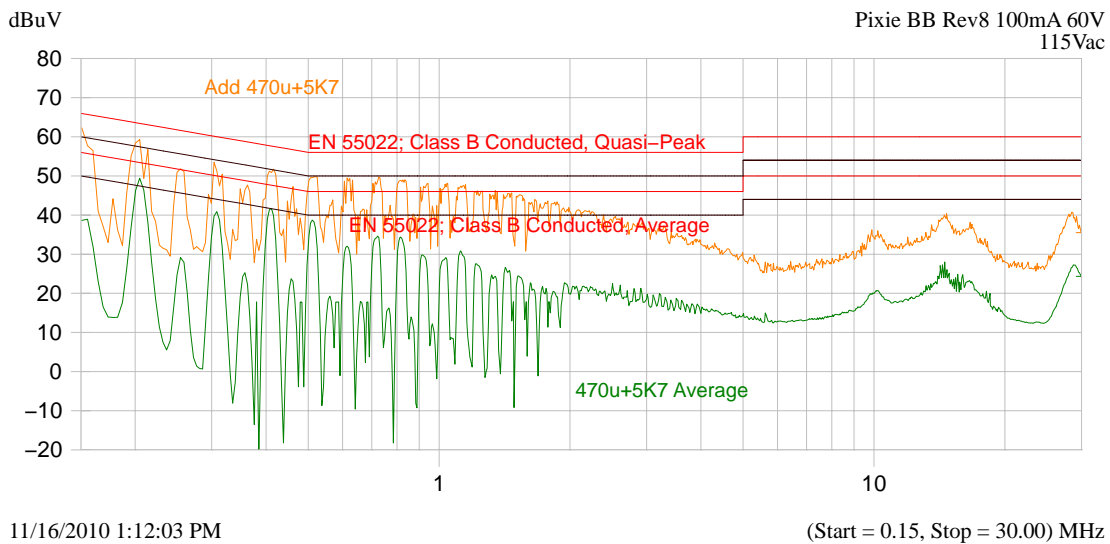


Figure 3. Conducted EMI for 100 mA with Vf = 60 Vdc (Green = Average; Orange = Peak)

By utilizing minimal input bulk capacity for C2, and low capacitance values for EMI “X” cap C1, relatively high power factor is achieved by switching the converter directly from the full-wave rectified line voltage. The unity gain

bandwidth of the converter feedback loop is also set below 40 Hz via C7 and this also improves the through-put power factor. The power factor versus Vf for both nominal line voltages is shown in Figure 4 below:

AND9043/D

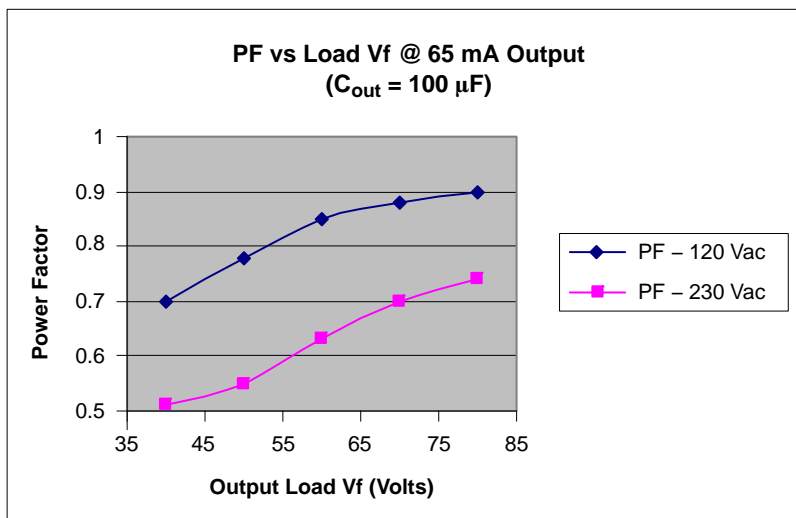


Figure 4. Power Factor versus LED Vf

Despite the simple, relatively low gain current sense and feedback design, current regulation over the typical Vf range is better than 4% as shown in Figure 5.

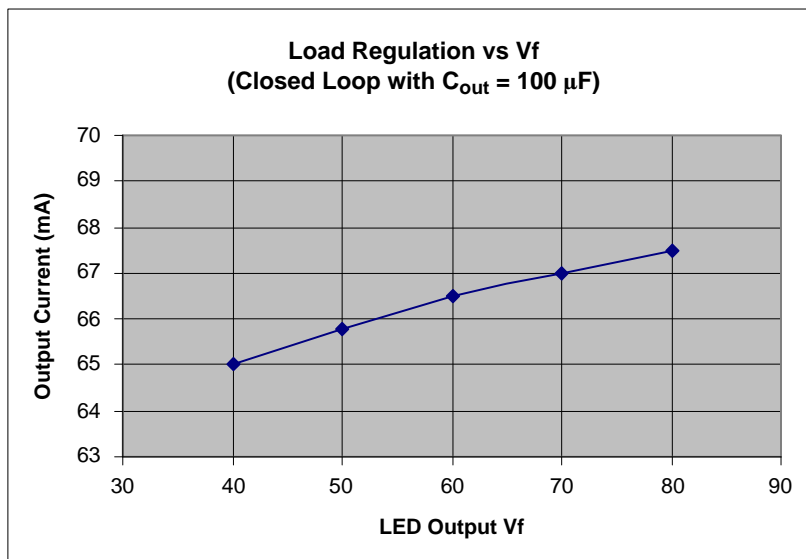


Figure 5. Current Regulation versus Vf

The 120 Hz output current ripple for 100 mA into an LED load with two 47 μF output capacitors in parallel (C9A/B) is shown in Figure 6. The output current ripple for a single output capacitor of 47 μF is shown in Figure 7. The scale is 50 mA per division vertically. The current ripple amplitude is dependent on the amount of filter capacity on the converter's output, since the slow feedback loop causes this

ripple to pass directly through the converter. It should be noted that the power factor and current regulation will degrade with decreasing output capacity. A minimum output capacity of about 47 μF (peak-to-peak ripple = 30% max) was found to be adequate for most applications up to 100 mA output current.

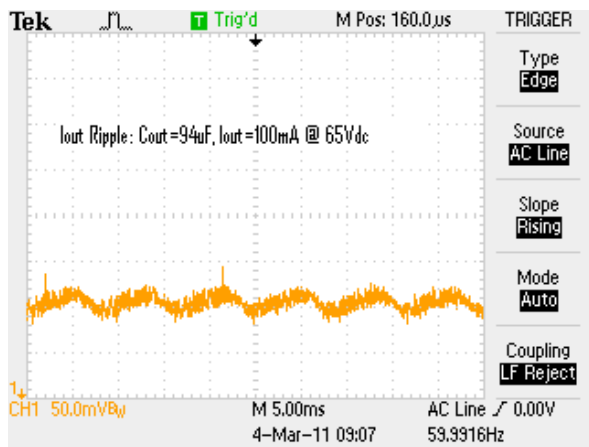


Figure 6. Output Current Ripple with $C_{out} = 94 \mu F$ and LED Load = 100 mA ($V_f = 65 Vdc$)

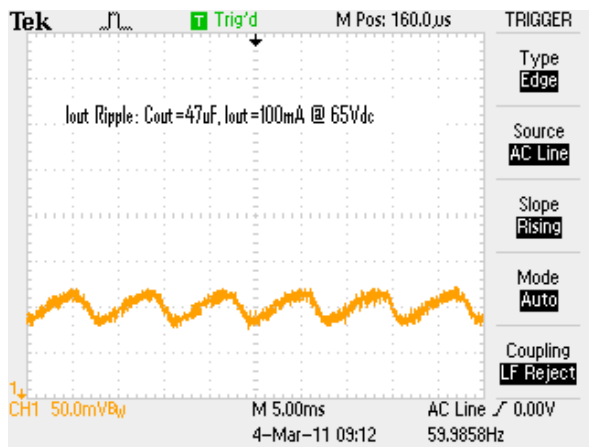


Figure 7. Output Current Ripple with $C_{out} = 47 \mu F$ and LED Load = 100 mA

Inductor Selection

The buck-boost inductor was selected for continuous conduction mode (CCM) operation so as to minimize the peak-to-average current ratio in the converter and make maximum use of the current capability of the NCP1014’s internal MOSFET. In addition, it was desired to use an off-the-shelf available inductor so as to avoid the expense of custom made inductors. As such, a commercially available inductor from Würth Elektronik with a nominal inductance of 3.3 mH and a dc resistance of about 4 Ω was selected and appeared adequate for the application. It should be noted that a custom made inductor with lower dc resistance would improve the overall efficiency; however, the cost would also probably increase. The minimum required inductance for CCM operation can be determined as follows:

The minimum lower tolerance on the MOSFET current limit level in the NCP1014 is 400 mA. For CCM operation let’s figure on the inductor magnetizing current being no more than 50% of this amount, or 200 mA. Assuming a minimum nominal ac input of 90 Vac, this translates to 120 Vdc peak. Now, since we are not using a bulk input

capacitance that can charge to peak, the average value of the input is 60 Vdc. Assuming a typical output voltage V_f (in this example) of 60 V and the fact that the transfer function for a CCM buck-boost is $V_{in}/V_{out} = D/(1-D)$ where D is the duty ratio, we can solve for D to determine the average on-time of the MOSFET at low ac input:

$$D/(1 - D) = V_{in}/V_{out} = 60 V/60 V = 1,$$

so solving for D we get $D = 0.5$.

So, for a 100 kHz switching frequency the average on-time will be 5 μs . From this we can now calculate a minimum inductance value:

$$L = V_{pk} \times dt/dI = 120 \times 5 \mu s/0.2 A = 3000 \mu H$$

where V_{pk} is the peak voltage across the inductor at low line and dI is the maximum selected peak-to-peak value of the choke magnetizing current. Since 3.3 mH is a common value, this was selected.

Triac Dimming

Triac dimming is possible with this buck-boost circuit as long as the triac holding current is low enough for stable operation at the lowest desired dimming current. One advantage of this circuit implementation that helps stability during dimming is the fact that the NCP1014 utilizes current mode control. This control approach does deteriorate the power factor somewhat since it attempts to instantaneously control the 120 Hz output ripple by adjusting the duty ratio, however, this effect also tends to shape the line current as a trapezoidal waveform. With a trapezoidal current waveform, the trailing edge at the end of a line cycle is still relatively high as opposed to the sinusoidal “tail-off” typical of a normal sine wave. The fact that the current remains high at the end of the half-cycle current pulse helps to maintain the triac holding current for the very short conduction angles necessary for low level dimming. Figures 8 and 9 show the 120 Vac input line current (yellow) and voltage (blue) during dimming for conduction angles of 100° and 22° respectively.

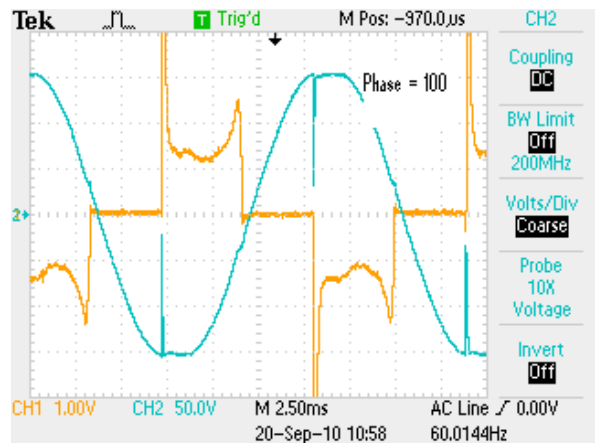


Figure 8. Line Current and Voltage – Triac Conduction Angle of 100°

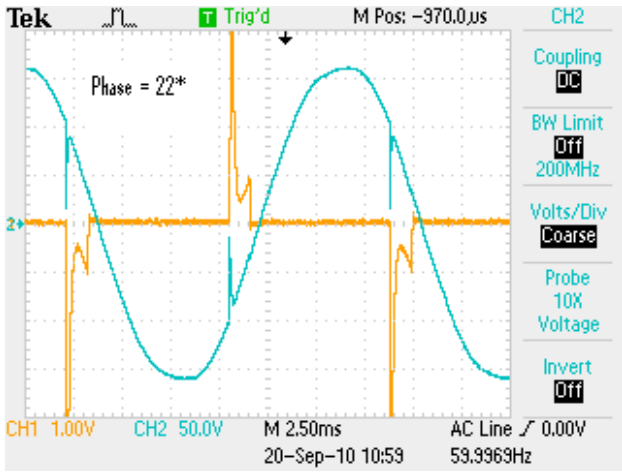


Figure 9. Line Current and Voltage – Conduction Angle of 22°

Referring to the schematic in Figure 1, the input current limiting resistor R1 and the damping network of R4 and C3 help to nullify the capacitive loading effects that the converter presents to the triac at its initial turn-on. The inhibit circuit composed of Q1 and Q2 monitors the line voltage and inhibits U1 via the feedback pin when the line voltage is below approximately 15 V during triac dimming. Diode D6 prevents discharge of the frequency compensation capacitor C7 during the triac zero conduction periods. This circuitry enhances the stability and performance of the converter when triac dimming is utilized. For applications where dimming is not required, the components of the inhibit circuit can be omitted and D6 replaced with a zero ohm resistor. Depending on the triac dimmer circuit characteristics, it may be necessary to adjust the resistance of the output pre-load resistor R16 to set the minimum desired dimness at minimum triac phase angle.

Figure 10 shows the converter output current versus line phase angle for the 120 Vac Leviton Sureslide and Rotary triac line dimmers (65 mA max, 60 Vf LED load).

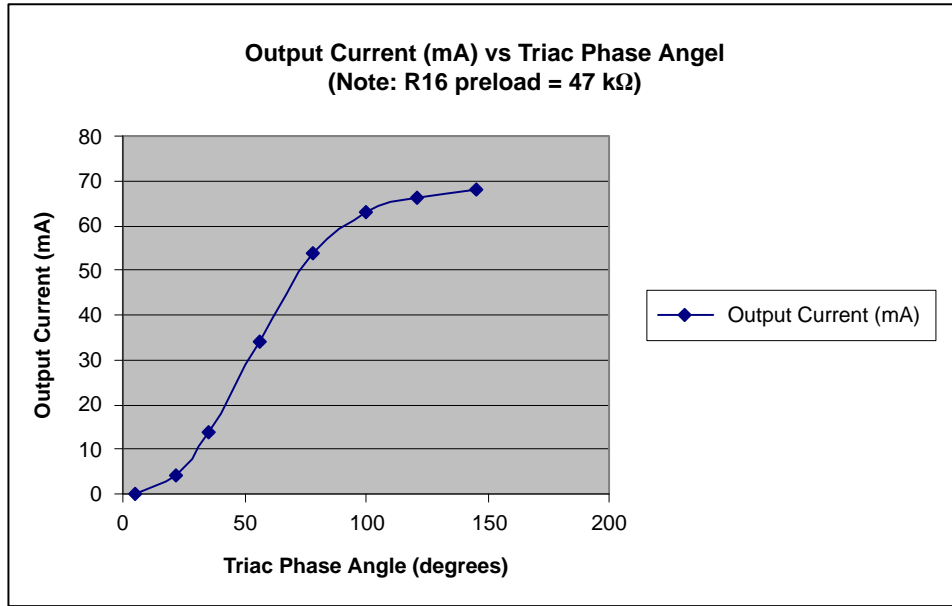


Figure 10. Converter Output Current versus Triac Phase Angle

AND9043/D

REFERENCES

[1] NCP1014 Data Sheet:


http://www.onsemi.com/pub_link/Collateral/NCP1010-D.PDF

[2] NCP1014 Application Notes:

<http://www.onsemi.com/PowerSolutions/supportDoc.do?type=AppNotes&rpn=NCP1014>

[3] NCP1014 Design Notes:

<http://www.onsemi.com/PowerSolutions/supportDoc.do?type=Design Notes&rpn=NCP1014>

ON Semiconductor and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of SCILLC's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com

Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local Sales Representative