



ON Semiconductor®

www.onsemi.com

Buck Converter External Components Selection

The Buck Converter is used in SMPS (switched mode power supply) circuits when the DC output voltage has to be lower than the DC input voltage. It is extensively used when high efficiency is required, especially in battery supplied applications where it improves battery life and reduces power dissipation.

This document describes step by step how to select the external components that are used by the buck converter. Although generally applicable, this selection method is in particular of interest for the members of the NCP63xx and NCV63xx family.

BUCK CONVERTER BASICS

A synchronous buck converter is comprised of two power MOSFETs, an inductor and input/output capacitors arranged as depicted in the Figure 1. The MOSFETs maintain energy level in the inductor, and the on/off control is synchronizing to regulate the output voltage.

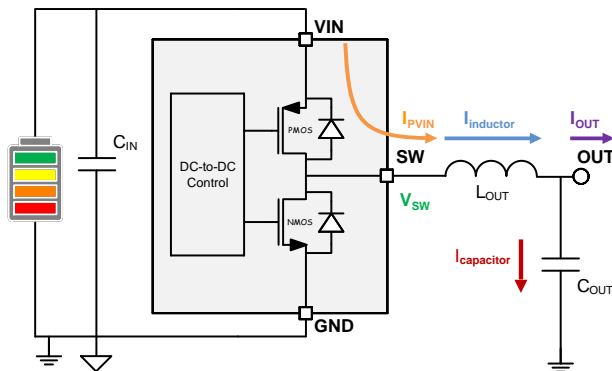


Figure 1. Synchronous Buck Converter

The PMOS connected between VIN and SW allows charging the LC filter: when ON, it transfers energy from input to output. The NMOS is off during this phase. When the PMOS turns off, the NMOS is activated and the energy stored in the inductor is provided to the output.

APPLICATION NOTE

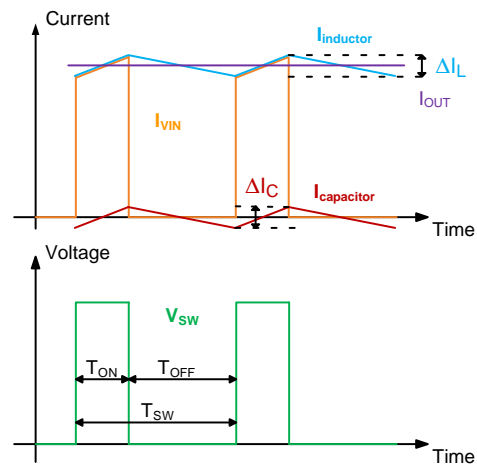


Figure 2. Synchronous Buck Converter Waveforms

The PMOS is commonly named High Side Switch (HSS) and the NMOS is Low Side Switch (LSS) or synchronous rectifier.

Figure 2 illustrates the voltage and current waveforms of the buck converter. This will help to understand the rest of this document

$$D = \frac{T_{ON}}{T_{ON} + T_{OFF}} = \frac{T_{ON}}{T_{SW}} = T_{ON} \cdot F_{SW}$$

$$T_{OFF} = \frac{1 - D}{F_{SW}} \text{ and } T_{ON} = \frac{D}{F_{SW}} \quad (\text{eq. 1})$$

COMPONENTS SELECTION

Inductor Selection

Let's start with the governing inductor current/voltage equation to obtain relation between L and ΔI_L :

$$V_L = L \cdot \frac{dI_L}{dt}$$

During on-time, assuming ideal HSS, the voltage across the inductor is $(V_{IN} - V_{OUT})$, so we have

$$\begin{aligned} V_{LON} &= (V_{IN} - V_{OUT}) = L \cdot \frac{dI_L}{dt_{ON}} = L \cdot \frac{\Delta I_L}{T_{ON}} \\ &= L \cdot \frac{\Delta I_L}{D \cdot T_{SW}} \Rightarrow L = \frac{D(V_{IN} - V_{OUT})}{\Delta I_L \cdot F_{SW}} \end{aligned}$$

During off-time, assuming ideal LSS, the inductor voltage is V_{OUT} , so we have

$$\begin{aligned} V_{LOFF} &= L \cdot \frac{dI_L}{dt_{OFF}} = L \cdot \frac{\Delta I_L}{T_{OFF}} = L \cdot \frac{\Delta I_L}{1 - D} \cdot F_{SW} \\ \Rightarrow L &= \frac{V_{OUT}(1 - D)}{\Delta I_L \cdot F_{SW}} \end{aligned}$$

Form the two previous equations we can extract:

$$D = \frac{V_{OUT}}{V_{IN}}$$

Finally the inductance corresponding to a given current ripple ΔI_L is:

$$L = \frac{(V_{IN} - V_{OUT}) \cdot V_{OUT}}{\Delta I_L \cdot F_{SW} \cdot V_{IN}} \quad (\text{eq. 2})$$

Note that the inductance of the inductor is selected such that the peak-to-peak ripple current ΔI_L is approximately 20% to 50% of the maximum output current I_{OUT_MAX} . This provides the best trade-off between transient response and output ripple.

The selected inductor must have a saturation current rating higher than the maximum peak current which is calculated by:

$$I_{L_SAT} = I_{OUT_MAX} + \frac{\Delta I_L}{2}$$


Moreover the inductor must also have a high enough current rating to avoid self-heating effect. A low DCR is therefore preferred to limit IR losses and optimize the total efficiency.

Output Capacitor Selection

The output capacitor selection is determined by the output voltage ripple and the load transient response requirement.

Ripple

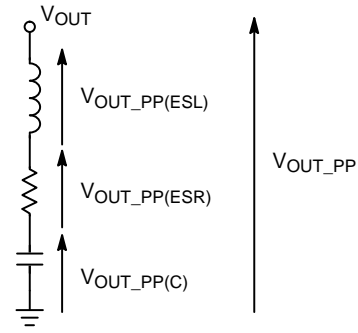For a given peak-to-peak ripple current ΔI_L in the inductor of the output filter, the output voltage ripple across the output capacitor V_{OUT_PP} is the sum of three components as shown below:



$$V_{OUT_PP} = V_{OUT_PP(ESL)} + V_{OUT_PP(ESR)} + V_{OUT_PP(C)}$$

With

- $V_{OUT_PP(C)}$ is the ripple voltage of the capacitor
- $V_{OUT_PP(ESR)}$ is the ripple voltage due to the ESR of the capacitor
- $V_{OUT_PP(ESL)}$ is the ripple voltage generated by the ESL of the capacitor

$V_{OUT_PP(C)}$ Equation:

From the Figure 2, we can extract the inductor and capacitor currents, and illustrate the charge of the capacitor:

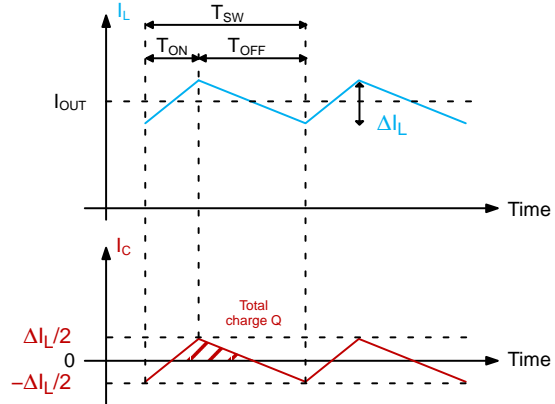


Figure 3. Inductor and Capacitor Current Waveforms

We can see that the capacitor current waveform is the same as the inductor current waveform, but without the I_{OUT} component.

The basic capacitor current/voltage equation is:

$$I_C = C \cdot \frac{dV_C}{dt} \Rightarrow dt \cdot I_C = C \cdot dV_C$$

And the relation between charge and capacitor is:

$$Q = C \cdot dV_C$$

Knowing that the charge is the area of the positive portion of the $I_C(t)$ waveform (in red in Figure 3). This area can be easily expressed as the area of a triangle:

$$Q = \frac{1}{2} \cdot \left(\frac{\Delta I_L}{2}\right) \cdot \left(\frac{T_{SW}}{2}\right) = \frac{\Delta I_L}{8 \cdot F_{SW}}$$

So

$$V_{OUT_PP(C)} = \frac{\Delta I_L}{8 \cdot C \cdot F_{SW}} \quad (\text{eq. 3})$$

$V_{OUT_PP(ESR)}$ Equation:

The $V_{OUT_PP(ESR)}$ due to the ESR can be extract easily thanks to the $I \times R$ formula: The ESR can be modeled as a resistor in series with the capacitor

$$V_{OUT_PP(ESR)} = \Delta I_L \cdot ESR \quad (\text{eq. 4})$$

$V_{OUT_PP(ESL)}$ Equation:

Again, let's start with the governing inductor current/voltage equation:

$$\begin{aligned} V_{ESL} &= L_{ESL} \cdot \frac{dI_{L_{ESL}}}{dt} \Rightarrow V_{ESL} = L_{ESL} \cdot \Delta I_L \cdot \left(\frac{1}{T_{ON}} + \frac{1}{T_{OFF}} \right) \\ &= L_{ESL} \cdot \Delta I_L \cdot \frac{F_{SW}}{D \cdot (1 - D)} \end{aligned}$$

By using $D = \frac{V_{OUT}}{V_{IN}}$ and $\Delta I_L = \frac{(V_{IN} - V_{OUT}) V_{OUT}}{L \cdot F_{SW} \cdot V_{IN}}$ we have

$$V_{OUT_PP(ESL)} = L_{ESL} \cdot \frac{V_{IN}}{L} \quad (\text{eq. 5})$$

In applications with all ceramic output capacitors, the main ripple component of the output ripple is $V_{OUT_PP(C)}$. The minimum output capacitance can be calculated based on a given output ripple requirement $V_{OUT_PP(C)}$ in continuous current mode (CCM):

$$C_{PP} = \frac{\Delta I_L}{8 \cdot V_{OUT_PP(C)} \cdot F_{SW}} \quad (\text{eq. 6})$$

Example:

3 MHz DCDC, $V_{IN} = 3.3$ V, $V_{OUT} = 1.1$ V, $L = 0.470$ μ H

$$\begin{aligned} \Delta I_L &= \frac{(V_{IN} - V_{OUT}) V_{OUT}}{L \cdot F_{SW} \cdot V_{IN}} \\ &= \frac{(3.3 - 1.1) 1.1}{0.00000047 \cdot 3000000 \cdot 3.3} = 520 \text{ mA} \end{aligned}$$

With 10 mV of desired output ripple, the minimum output capacitor will be:

$$\begin{aligned} C_{PP} &= \frac{\Delta I_L}{8 \cdot V_{OUT_PP(C)} \cdot F_{SW}} \\ &= \frac{0.520}{8 \cdot 0.01 \cdot 3000000} = 2.2 \text{ } \mu\text{F} \end{aligned}$$

Load Transient

For the estimation of the capacitor during load transient, the starting point is that the total energy of the output stage has to be constant during the transition.

The total energy of the output stage is:

$$E = E_C + E_L = \frac{1}{2} C \cdot V_C^2 + \frac{1}{2} L \cdot I_L^2$$

When the load current changes from load to no load, this will introduce temporary an increase of the output voltage (this is generally named output overshoot V_{OV}).

The energy with load is:

$$E = \frac{1}{2} C \cdot V_{OUT}^2 + \frac{1}{2} L \cdot I_{LPEAK}^2, \quad I_{LPEAK} = I_{OUT} + \frac{\Delta I_L}{2}$$

The energy without load is:

$$E = \frac{1}{2} C \cdot (V_{OUT} + V_{OV})^2$$

The energy preceding the load change has to be equal to the energy after the load change:

$$\frac{1}{2} C \cdot V_{OUT}^2 + \frac{1}{2} L \cdot I_{LPEAK}^2 = \frac{1}{2} C (V_{OUT} + V_{OV})^2$$

Finally

$$C_{LT} = \frac{L \cdot I_{LPEAK}^2}{(V_{OUT} + V_{OV})^2 - V_{OUT}^2} \quad (\text{eq. 7})$$


Example:

3 MHz DCDC, $V_{IN} = 3.3$ V, $V_{OUT} = 1.1$ V, $L = 0.470$ μ H. 3 A load transient, 50 mV overshoot:

$$\begin{aligned} C_{LT} &= \frac{L \cdot I_{LPEAK}^2}{(V_{OUT} + V_{OV})^2 - V_{OUT}^2} \\ &= 0.00000047 \cdot \frac{(3 + 0.26)^2}{(1.1 + 0.05)^2 - 1.1^2} = 44 \text{ } \mu\text{F} \end{aligned}$$

Input Capacitor Selection

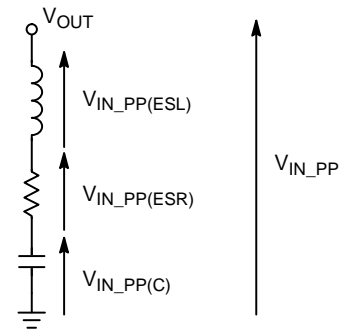One of the input capacitor selection requirements is the input voltage ripple. For a given output current I_{OUT} , the input voltage ripple across the output capacitor V_{IN_PP} is, like the output capacitor, the sum of three components as shown below:



$$V_{IN_PP} = V_{IN_PP(ESL)} + V_{IN_PP(ESR)} + V_{IN_PP(C)}$$

With:

- $V_{IN_PP(C)}$ is the ripple voltage of the capacitor
- $V_{IN_PP(ESR)}$ is the ripple voltage due to the ESR of the capacitor
- $V_{IN_PP(ESL)}$ is the ripple voltage generated by the ESL of the capacitor

$V_{IN_PP(C)}$ Equation:

The current flowing into the input capacitor is:

- The difference between input and inductor currents during the ON-time
- The input current during the OFF-time

During the OFF-time, the capacitor is charged with current I_{IN} , while during the ON-time it is discharged. In steady state the charge and discharge of the capacitor is equal and generates the input voltage ripple.

By using the governing capacitor current/voltage equation during OFF-time we have:

$$I_{IN} = C_{IN} \cdot \frac{dV_C}{dt} = C_{INPP} \cdot \frac{V_{IN_PP(C)}}{T_{OFF}} \Rightarrow C_{INPP} = \frac{I_{IN} \cdot T_{OFF}}{V_{IN_PP(C)}}$$

With $I_{IN} = D \cdot I_{OUT}$ and $T_{OFF} = \frac{1 - D}{F_{SW}}$

The minimum input capacitance with respect to the input ripple voltage $V_{IN_PP(C)}$ is:

$$C_{INPP} = \frac{I_{OUT}(D - D^2)}{V_{IN_PP(C)} \cdot F_{SW}} \quad (\text{eq. 8})$$

$V_{IN_PP(ESR)}$ Equation:

The $V_{IN_PP(ESR)}$ due to the ESR can be extract easily thanks to the $I \cdot R$ formula: The ESR can be modeled as a resistor in series with the capacitor, and the I_{IN} extracted from I_{OUT} (see Figure 4). Generally the ripple current is low compare to output current, so the input current is assimilated to square current (0 to/from I_{OUT})

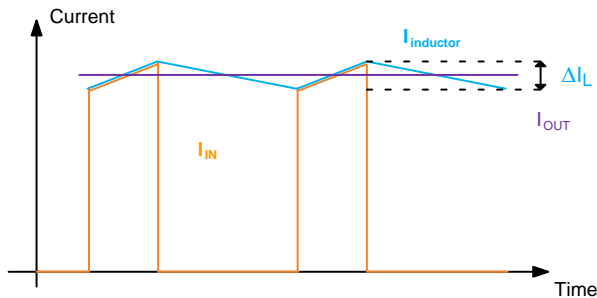


Figure 4. Input and Output Current Waveforms

$$V_{IN_PP(ESR)} = \Delta I_{IN} \cdot ESR$$

So

$$V_{IN_PP(ESR)} = I_{OUT} \cdot ESR \quad (\text{eq. 9})$$

$V_{IN_PP(ESL)}$ Equation:

Again, let's start with the governing inductor current/voltage equation:

$$V_{ESL} = L_{ESL} \cdot \frac{dI_{IN}}{dt}$$

With input current approximated to square current

$$V_{IN_PP(ESL)} = L_{ESL} \cdot \frac{I_{OUT}}{dt} \quad (\text{eq. 10})$$

To minimize the input voltage ripple and get better decoupling at the input power supply rail, a ceramic capacitor is recommended due to low ESR and ESL.

Example:

3 MHz DCDC, $V_{IN} = 3.3$ V, $V_{OUT} = 1.1$ V, $I_{OUT} = 3.0$ A, $L = 0.470$ μ H.

With 50 mV of desired input ripple, the minimum input capacitor will be:

$$C_{INPP} = \frac{I_{OUT}(D - D^2)}{V_{IN_PP(C)} \cdot F_{SW}} = \frac{3 \cdot \left(\frac{1.1}{3.3} - \frac{1.1}{3.3} \cdot \frac{1.1}{3.3} \right)}{0.05 \cdot 3000000} = 4.4 \mu\text{F}$$

Summary

Table 1. SUMMARY


Components	Equation
Output Inductor	$L = \frac{(V_{IN} - V_{OUT}) \cdot V_{OUT}}{\Delta I_L \cdot F_{SW} \cdot V_{IN}}$
Output Capacitor	<p>For Ripple</p> $C_{PP} = \frac{\Delta I_L}{8 \cdot V_{OUT_PP(C)} \cdot F_{SW}}$ <p>For Transient Load</p> $C_{LT} = \frac{L \cdot I_{IPEAK}^2}{(V_{OUT} + V_{OV})^2 - V_{OUT}^2}$
Input Capacitor	$C_{INPP} = \frac{I_{OUT}(D - D^2)}{V_{IN_PP(C)} \cdot F_{SW}}$

NCP63xx and NCV63xx Family

The NCP63xx and NCV63xx family of products are synchronous buck converters with both high side and low side integrated switches. Neither external transistor nor diodes are required for proper operation.

The feedback and compensation networks are also fully integrated. The high switching frequency allows the use of smaller size output filter components: This contributes to reducing overall solution size.

During external component selection, please verify compatibility with the recommended components described in the datasheet.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>

For additional information, please contact your local Sales Representative