

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



eFuse Load Current Measurement

APPLICATION NOTE

Introduction

The On Semiconductor eFuse protection devices are primarily used for limiting the system load current in the event of overload or short circuit conditions. Almost all of those eFuse protection devices provide additional features such as soft start, output voltage clamp, reverse current protection, adjustable load current limit with external resistor and so on. Some of the eFuses provide additional feature of load current monitoring which is implemented as a voltage output through an IMON pin. The user can measure the voltage at the IMON pin which would be proportional to the load current.

This application note describes the load current measurement solution for the eFuses which do not provide load current monitoring feature. Since almost all of the eFuses provide adjustable current limit functionality by utilizing an external current limiting resistor between I_{LIMIT}

and Source pins, it is possible to connect a current sense amplifier across that resistor and measure the voltage drop across it which would be proportional to the load current. This method mainly requires a current sense amplifier and allows user to measure the system load current without introducing any additional resistance in series with the load path.

Schematics

A typical schematics of an eFuse configuration together with the $20\ \Omega$ R_{LIMIT} resistor used for load current limit programming is shown in Figure 1. The load current measurement circuit implementation is shown within a dashed rectangle. Only current sense amplifier with a decoupling capacitor is required.

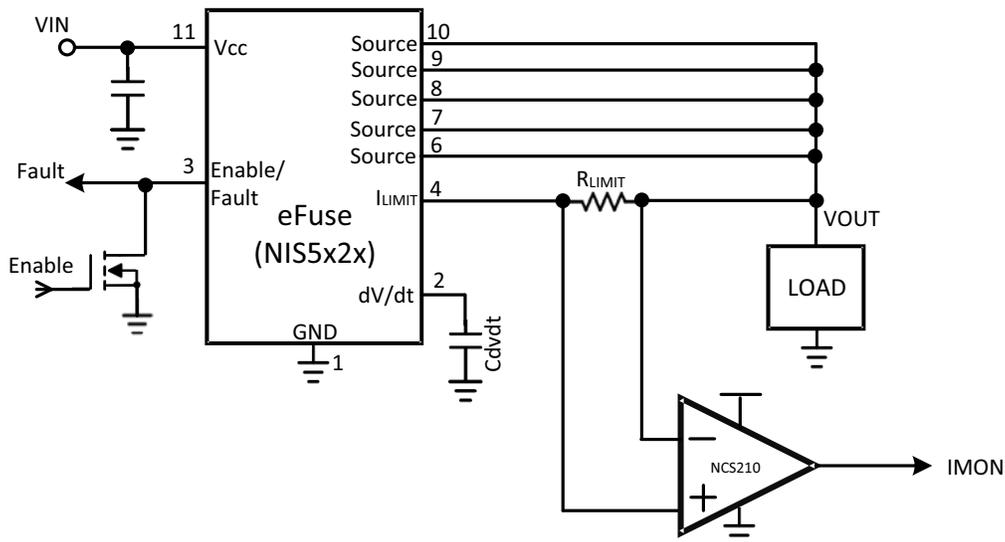


Figure 1. 12 V eFuse Configuration with Load Current Measurement Circuit

One of the most important parameters to consider when selecting a current sense amplifier are: wide common mode range, low offset voltage, low gain error, rail-to-rail input and output and a wide input supply range which exceeds the supply range of the eFuse input and output voltage.

Typical current sense or current shunt amplifiers also have integrated gain and feedback resistors. It is important to utilize such a current sense amplifier where those integrated resistors have much higher resistance than the resistance of the external R_{LIMIT} current programming resistor. The schematics in Figure 1 shows a 12 V eFuse together with the NCS210 rail-to-rail current sense amplifier with a gain of 200, ±60 μV offset voltage, 1% gain error and supply range up to 26 V.

The Source output pin of the eFuse will be at a lower voltage potential than the VCC input pin due to a small voltage drop across the eFuse input and output pins. The I_{LIMIT} pin also has a lower voltage potential than the VCC pin, but slightly higher voltage potential than Source pins. The higher the load current, the higher the voltage drop across the R_{LIMIT} resistor. This voltage drop will be amplified by a current sense amplifier and used as a measure of load current. It is important to connect the positive input of the current sense amplifier to the I_{LIMIT} pin and negative input to Source pins of the eFuse. The Reference pin of the current sense amplifier should be connected to ground. It is also recommended to use a 1% accuracy R_{LIMIT} resistor.

The output of the current sense amplifier can easily drive high impedance, low capacitance load such as an ADC or

measurement equipment. If a low impedance or high capacitance load needs to be driven it is recommended to use additional buffer amplifier with a high slew rate after the current sense amplifier. If the output of current sense amplifier is fed to ADC for digitizing, it would be reasonable to connect a shunt Zener diode at the output of the current sense amplifier in order to limit its output voltage during the eFuse current overload events in order to protect ADC input.

Layout

Typical current sense amplifiers usually come in a small packages such as SOT-363 or UQFN10. It is important to place a current sense amplifier close to the R_{LIMIT} resistor and decoupling capacitor close to the supply rail of current sense amplifier. Use value of 0.1 μF and thick traces for decoupling capacitor. The traces connecting current sense amplifier with R_{LIMIT} resistor should not be close to any traces carrying fast switching signals.

Refer to Figure 2 for an example layout configuration when using current sense amplifier to measure the eFuse load current. The decoupling capacitor is connected close to the current sense amplifier supply pins. The input positive and negative terminals of current sense amplifier are connected to the R_{LIMIT} resistor with minimal routing. The R_{LIMIT} resistor is also connected to output node and I_{LIMIT} pin of eFuse with minimal routing. Overall solution is no larger than a 4x4 mm footprint of NIS5021.

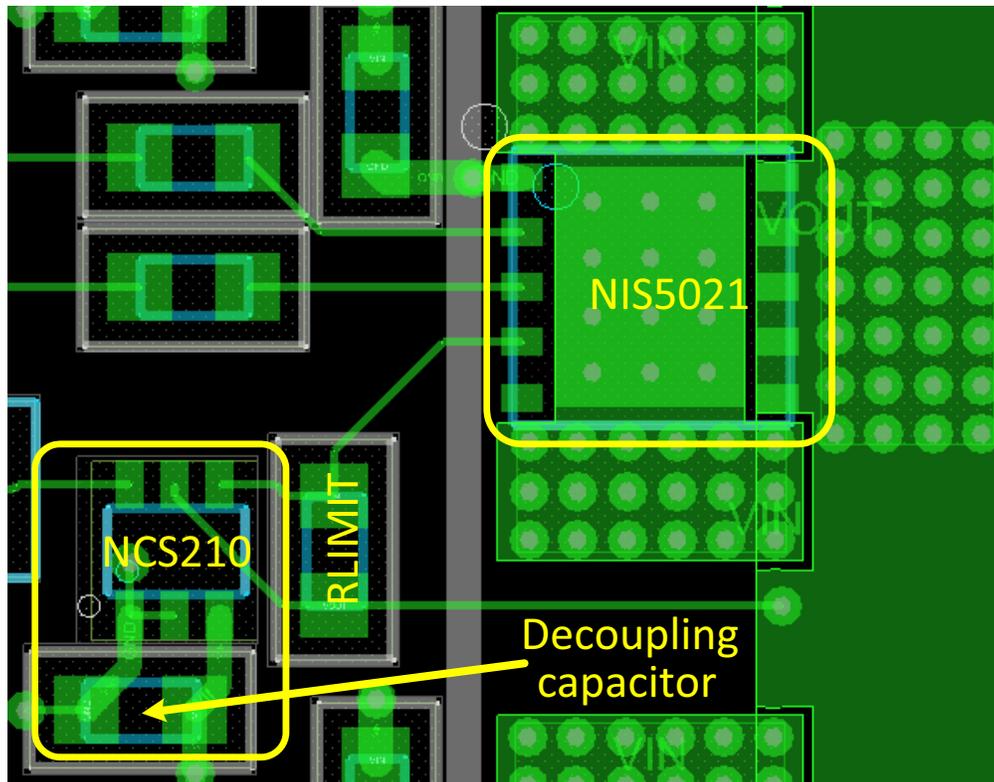


Figure 2. Example PCB Layout for the Load Current Sense Solution

AND9685/D

Performance

The typical voltage drop across R_{LIMIT} resistor versus load current for one of the ON Semiconductor 12V NIS5x2x eFuses is shown in Figure 3. For every 1 Amp of load current there is approximately 7.5 mV voltage drop across 20 Ω

R_{LIMIT} resistor, this voltage drop will depend on the value of the resistor and eFuse type, since every family of eFuse has its own proportion between the main load current and the current flowing across the R_{LIMIT} resistor.

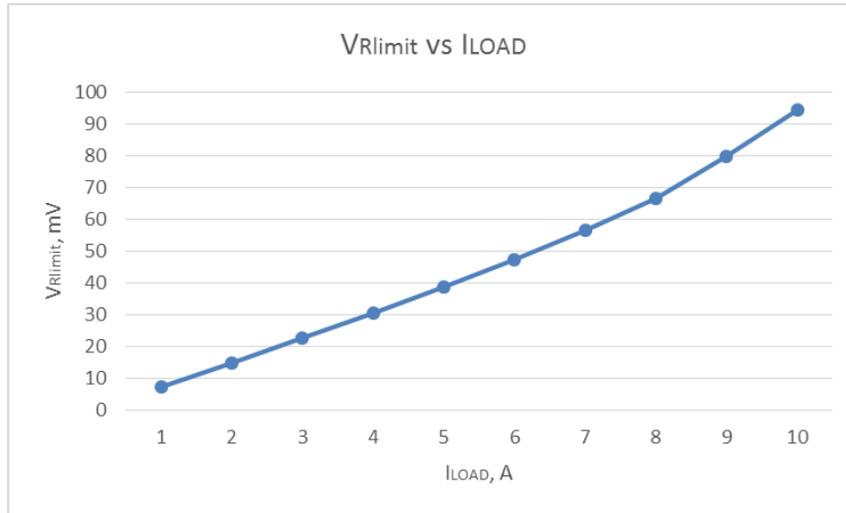


Figure 3. Voltage drop across R_{LIMIT} versus the load current

The Figure 4 shows a schematics of two NIS5x2x eFuses connected in parallel.

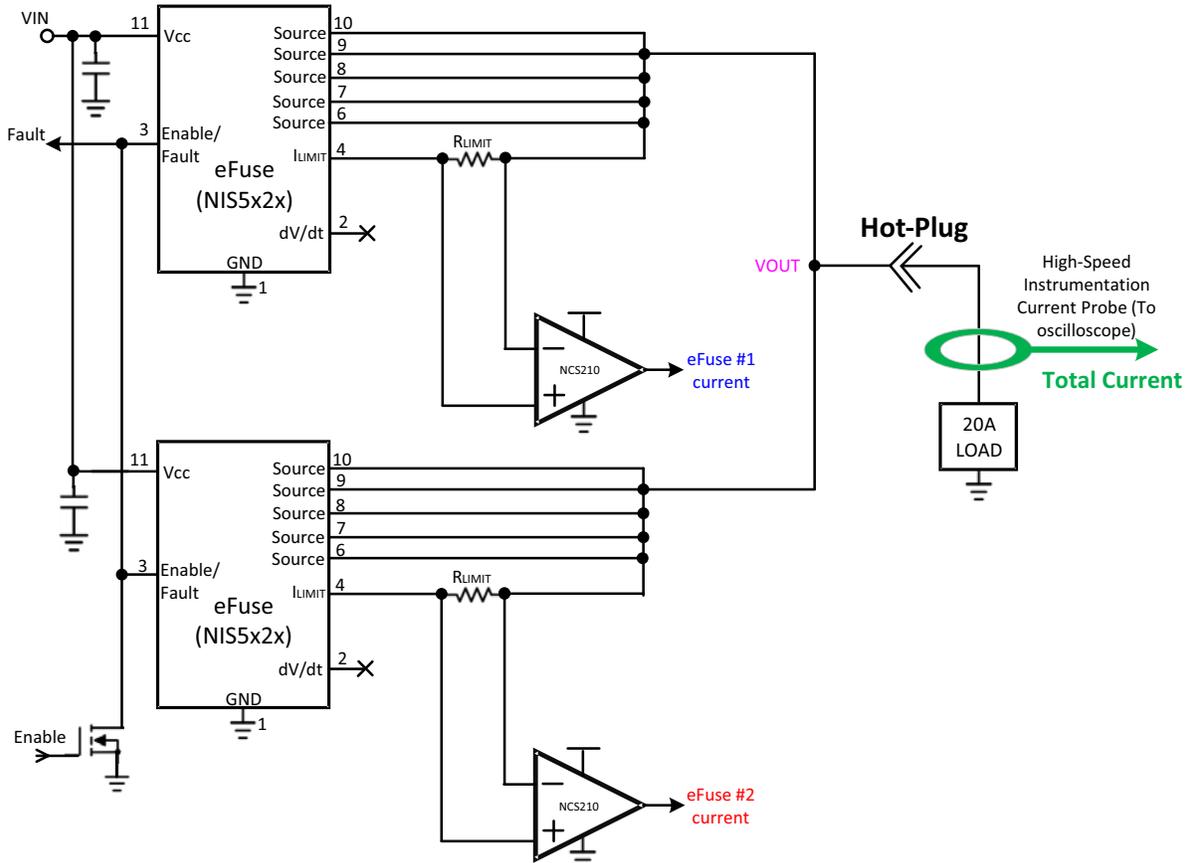


Figure 4. Parallel configuration of two NIS5x2x eFuses with individual load current monitoring

The Figure 5 shows the measurement error versus load current for the 12 V NIS5x2x eFuse. In this case one can achieve around 90% accuracy for most of the eFuse

continuous current capability. The measurement accuracy would drop another 10–12% if the eFuse is operated at the maximum current rating.

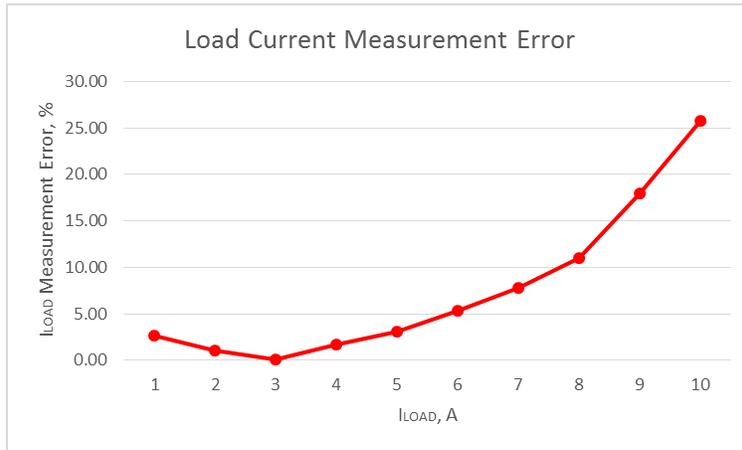


Figure 5. Load current measurement error vs Load Current

The Figure 6 shows a scope screenshot of a 20 A load hot plugged to the outputs of two NIS5x2x 12 V eFuses connected in parallel. Each eFuse in that configuration utilized a current sense amplifier across the RLIMIT resistor, the output of each current sense amplifier is connected to a scope and plotted as a red and blue traces. The purple trace

shows the common connected VOUT voltage of two eFuses and the green trace shows the overall total current measured with instrumentation grade high-speed current probe. In this configuration a current sense amplifier similar to NCS210 but with a gain of 50 was used.

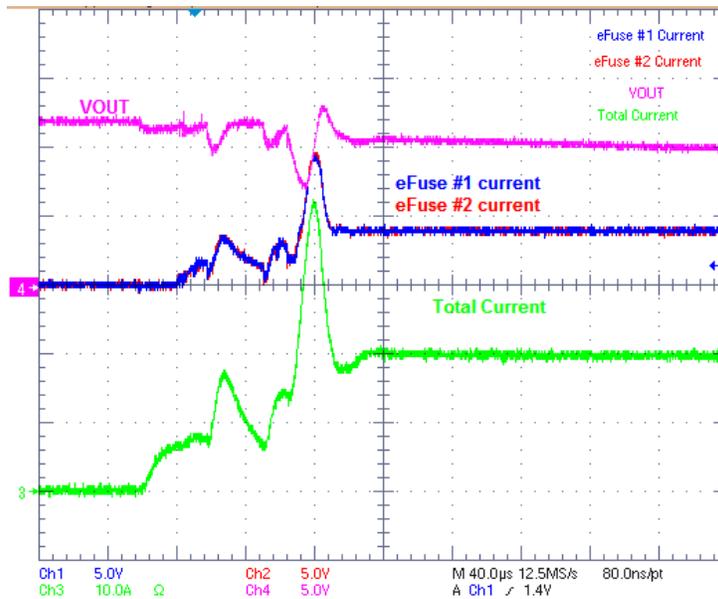


Figure 6. Hot plug to 20 A load and eFuse load current measurement

Once the hot plug event is gone the total current measured by an instrumentation current probe is settled to 20 A. Since the current is equally shared by eFuses connected in parallel, each eFuse in this case carries around 10 A current. From Figure 3, the voltage drop across 20 Ω RLIMIT resistor for this eFuse at 10 A load is around 94.3 mV, since we are using a current sense amplifier with a gain of 50, we see a voltage

of around 94.3 mV x 50 = 4.7 V at the outputs of both current sense amplifiers as shown in red and blue traces in Figure 6.

The current is also perfectly shared among eFuses during a fast output load hot-plug event and properly measured by current sense amplifiers as seen from the scope shot in Figure 6, this can be achieved if current sense amplifiers are fast enough and provide 25–40 kHz 3dB bandwidth.

Conclusion

This application note demonstrated a cheap and effective way of adding a load current measurement solution to current limiting electronic fuses. The solution requires only one active device in a compact SOT-363 or UQFN10

package and minimum supporting passive components for it, such as decoupling capacitor. This solution provides measured load current not only in a static configuration but also during dynamic events.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC dba ON Semiconductor or its subsidiaries in the United States and/or other countries. ON Semiconductor owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of ON Semiconductor's product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. ON Semiconductor reserves the right to make changes without further notice to any products herein. ON Semiconductor makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does ON Semiconductor assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using ON Semiconductor products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by ON Semiconductor. "Typical" parameters which may be provided in ON Semiconductor data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. ON Semiconductor does not convey any license under its patent rights nor the rights of others. ON Semiconductor products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use ON Semiconductor products for any such unintended or unauthorized application, Buyer shall indemnify and hold ON Semiconductor and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that ON Semiconductor was negligent regarding the design or manufacture of the part. ON Semiconductor is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

PUBLICATION ORDERING INFORMATION

LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor
19521 E. 32nd Pkwy, Aurora, Colorado 80011 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: orderlit@onsemi.com

N. American Technical Support: 800-282-9855 Toll Free
USA/Canada
Europe, Middle East and Africa Technical Support:
Phone: 421 33 790 2910
Japan Customer Focus Center
Phone: 81-3-5817-1050

ON Semiconductor Website: www.onsemi.com
Order Literature: <http://www.onsemi.com/orderlit>
For additional information, please contact your local Sales Representative