

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



ON Semiconductor

NCP1077, 12 Vout, 6 Watt, Off-line Buck Regulator Using a Tapped Inductor

Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
NCP1077	Smart Meters Electric Meters, White Goods	85 to 265 Vac	6W at 12Vout 12W peak	Off-Line 100 kHz Buck	Non-isolated

Output Specification	
Output Voltage	3.3 to 28 Vdc depending on selected Z1 zener value
Output Ripple	Less than 1%
Typical Current	500 mA continuous
Max Current	1 amp maximum (several second surge – thermally limited)
Min Current	zero

PFC (Yes/No)	No, Pout < 25 watts
Efficiency	>75% typical at 120Vac
Inrush Limiting / Fuse	Fused input
Operating Temp. Range	0 to +50°C (dependent on U1 heatsinking)
Cooling Method / Supply Orientation	Convection
Signal Level Control	None

Circuit Description

This design note describes a simple, low power, constant voltage output variation of the buck power converter intended for powering electronics for white goods, electrical meters, and industrial equipment where isolation from the AC mains is not required and maximum efficiency is essential. This buck circuit design has been modified by tapping the freewheel diode connection to the inductor to provide several advantages over the conventional buck circuit. ON Semiconductor application note AND8318 provides a detailed discussion of the tapped inductor buck circuit theory which will not be covered in detail in this design note.


One of the major disadvantages of the conventional buck circuit configuration is that for off-line applications, the typical dc input-to-output voltage differential is very high; resulting is a very short operational duty ratio (D) in the power MOSFET. Since the buck's input-to-output voltage transfer function is defined as $V_{out} = D \times V_{in}$, we can see that for a rectified input of 165 Vdc and an output of 12 Vdc, D will be $12/165 = 0.07$ or 7%. Assuming a switching frequency of 100 kHz ($T = 10 \mu s$), this results in a typical on-time of 0.7 μs . With this short of a duty ratio, the conversion efficiency is not very good and this short of pulse width is approaching the propagation delay time for some control chips which can affect switching stability at light load and higher input voltages. In addition, the

maximum dc output load current of the conventional buck cannot be any greater than the peak current limitation of the monolithic switcher, and is typically less due to the magnetizing component of the inductor current.


By tapping the freewheel diode connection to halfway point on the inductor, two advantages are achieved: 1) The output current can be effectively boosted nearly double that possible with the conventional buck configuration because the power MOSFET duty cycle is expanded by a factor of 2 without any increase in peak current; and, 2) The normally high turn-on switching losses caused by the freewheel diode recovery current in the conventional buck are reduced due to the leakage inductance component of the coupled winding in the tapped choke.

The actual tap point on the inductor can be anywhere, and, the closer it is to the output end of the inductor, the greater the current boosting effect and extension of the effective MOSFET duty ratio. For this design note, a center tap inductor was chosen because several commercial vendors provide such a part in a surface mount configuration that can handle up to one amp peak. Typical efficiency improvements of 5% or more over a conventional buck have been achieved with this tapped configuration and it is particularly effective when low output voltages of 12V or less are required with highest efficiency and low standby power.


Efficiency vs Load

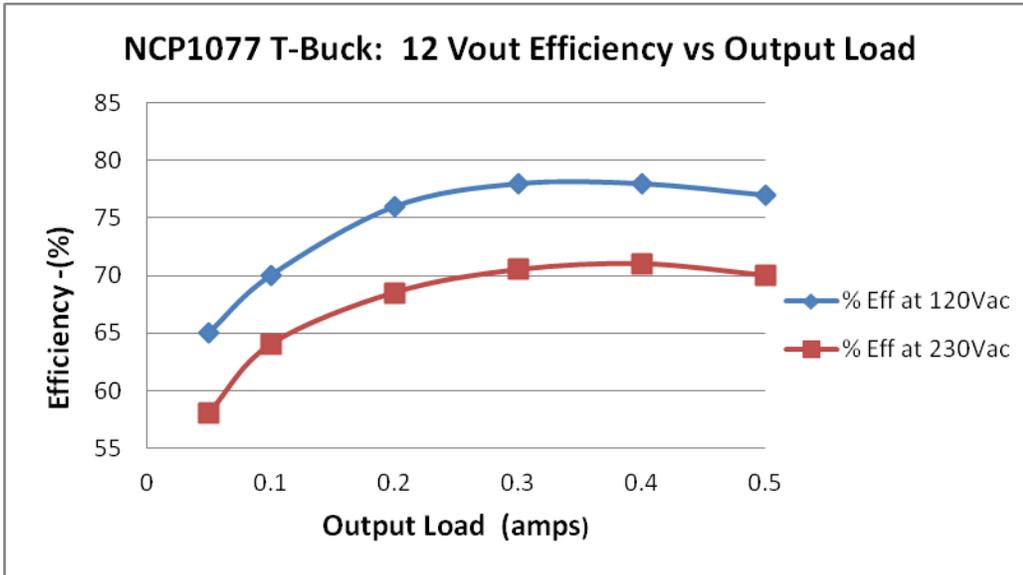

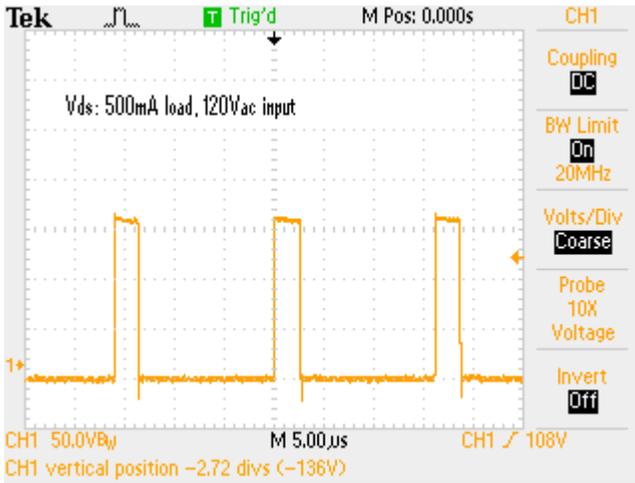
Mosfet Source Voltage – 500 mA Load, 120 Vac Input



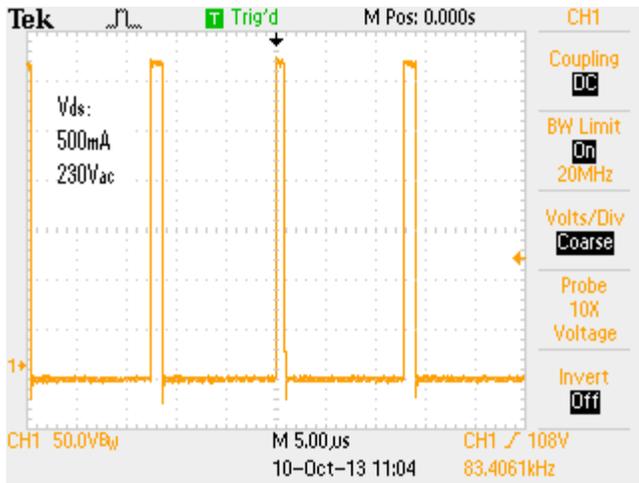Mosfet Source Voltage – 500 mA Load, 230 Vac Input




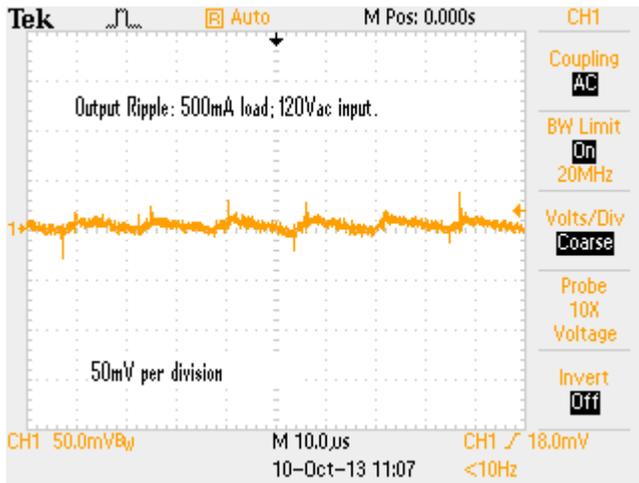Output Ripple – 500 mA Load, 120 Vac Input




PC Board Layout Details

Top

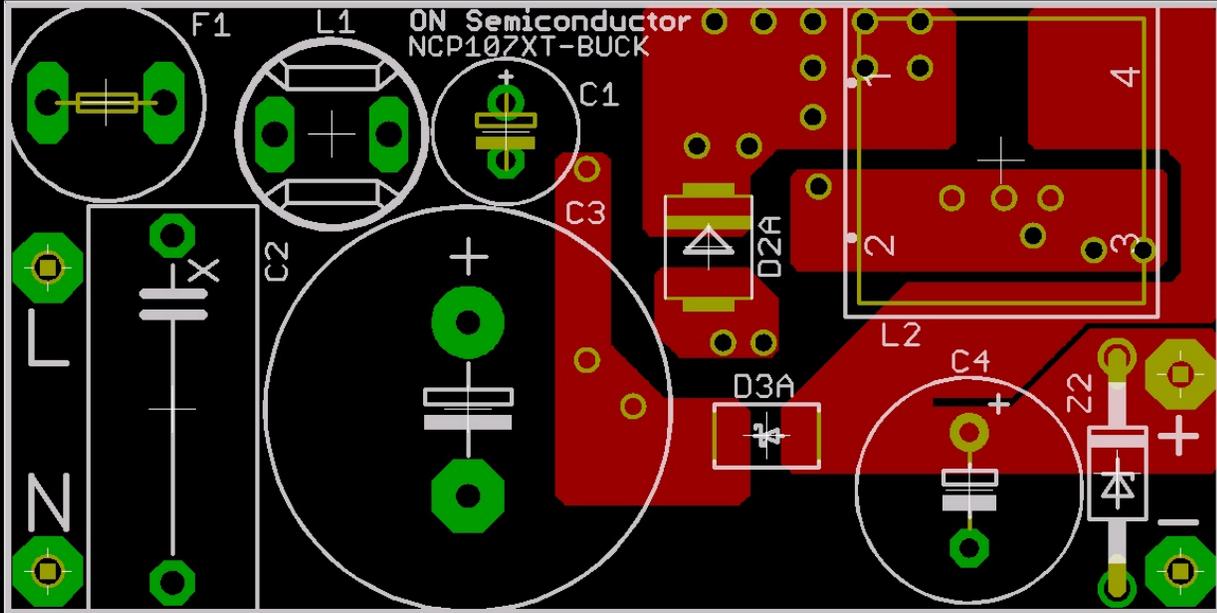


Bottom

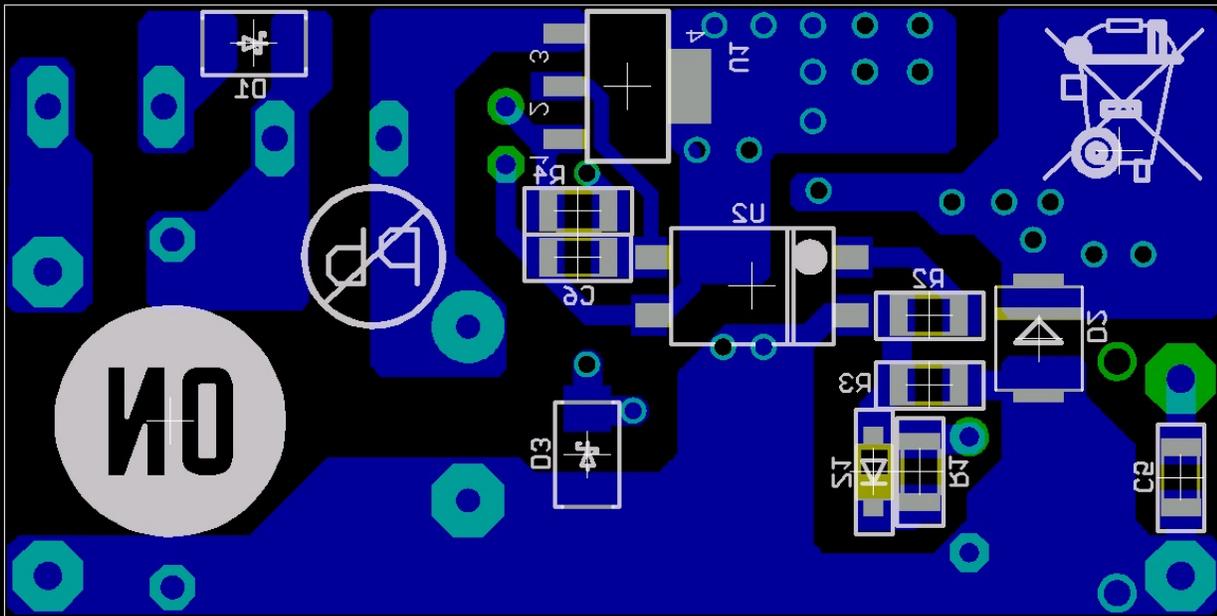

DN05059/D

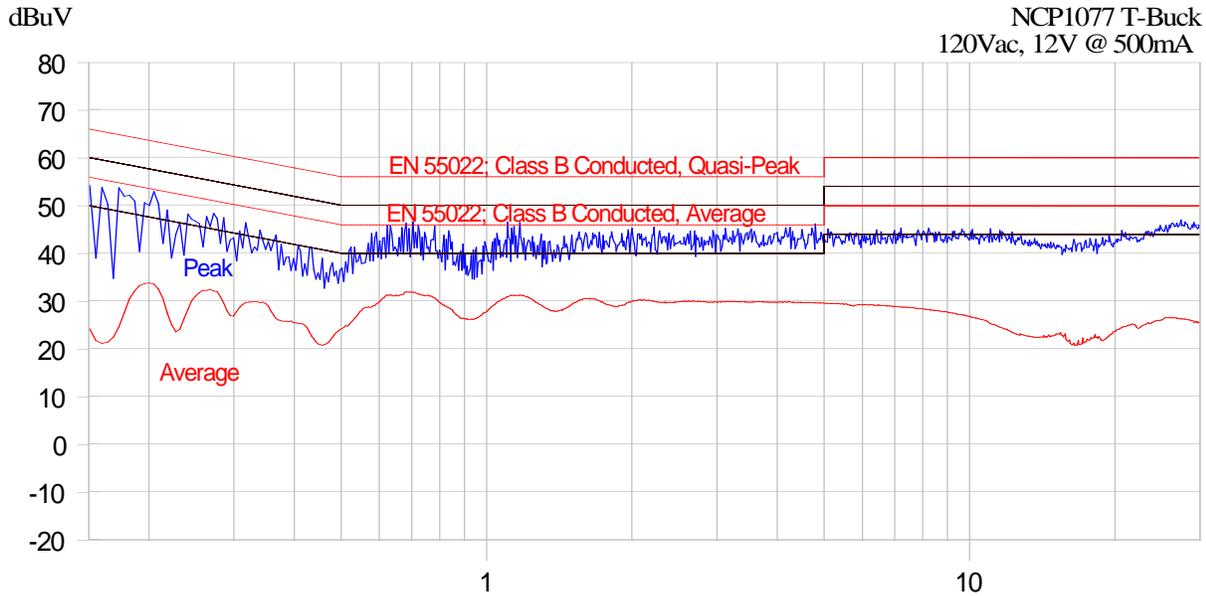Conducted EMI Profile: Peak (blue) and Average (red)



10/16/2013 8:15:19 AM

(Start = 0.15, Stop = 30.00) MHz

BOM

Designator	Qty	Description	Value	Tolerance	Footprint	Manufacturer	Manufacturer Part Number
D1	1	Diode - 60 Hz,	1A, 800V		SMA	ON Semi	MRA4007
D2 (or D2A)	1	Ultra-fast rectifier	2A, 600V		SMB	ON Semi	MURS260T3
D3 (or D3A)	1	Ultra-fast rectifier	1A, 600V		SMA		
Note: For non-tapped Buck configuration, install D2 and D3 in D2A and D3A positions on PCB							
D3	1	Diode - UFR	1A, 600V		SMA	ON Semi	MURA160
Z1	1	Zener diode	11V		SOD-123	ON Semi	MMSZ5241B
Z2	1	Zener diode	15V/5W		Axial lead	ON Semi	1N5352B or 1N5929B
U2	1	Optocoupler	CTR >= 0.5		4-pin SMD	Vishay or NEC	SFH6156A-4 or PS2561L-1
U1	1	Controller - NCP1077	100 kHz		SOT223	ON Semi	NCP1077-100
C2	1	"X" cap, box type	100nF, X2		LS = 15 mm	Rifa, Wima	TBD
C6	1	Ceramic cap, monolythic	10 nF, 50V	10%	1206	AVX, Murata	TBD
C5	1	Ceramic cap, monolythic	100nF, 50V	10%	1206	AVX, Murata	TBD
C3	1	Electrolytic cap	33uF, 400V	10%	LS=7.5mm, D=18mm	UCC	TBD
C1	1	Electrolytic cap	22uF, 50Vdc	10%	LS=2.5mm, D=6.3mm	Panasonic - ECG	ECA-1HM220
C4	1	Electrolytic cap	1000uF, 16V	10%	10x20mm, LS=5mm	UCC, Panasonic	TBD
R4	1	Resistor, 1/4W SMD	1.5K	5%	SMD 1206	AVX, Vishay, Dale	TBD
R2	1	Resistor, 1/4W SMD	33 ohms	5%	SMD 1206	AVX, Vishay, Dale	TBD
R3	1	Resistor, 1/4W SMD	680 ohms	5%	SMD 1206	AVX, Vishay, Dale	TBD
R1	1	Resistor, 1/4W SMD	68 ohms	5%	SMD 1206	AVX, Vishay, Dale	TBD
F1	1	Fuse, TR-5 style	1A		TR-5, LS=5mm	Minifuse	TBD
L1	1	Inductor (EMI choke)	820 uH, 500 mA		LS=5mm, Dia=8.5mm	Wurth Magnetics	7447728215
L2	1	Coupled Output Inductor	220uH, 3Apk		15mm x 15mm SMD	Coilcraft	MSD1583-224KE

References:

ON Semiconductor Application Notes: AND8318, AND8328
ON Semiconductor Design Notes: DN05014, DN05023, DN06011, DN06052
ON Semiconductor NCP1077 monolithic switcher data sheet.

© 2013 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note "AS IS" and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party's intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Frank Cathell, e-mail: f.cathell@onsemi.com