

ON Semiconductor

Is Now

onsemi™

To learn more about onsemi™, please visit our website at
www.onsemi.com

onsemi and **onsemi** and other names, marks, and brands are registered and/or common law trademarks of Semiconductor Components Industries, LLC dba "**onsemi**" or its affiliates and/or subsidiaries in the United States and/or other countries. **onsemi** owns the rights to a number of patents, trademarks, copyrights, trade secrets, and other intellectual property. A listing of **onsemi** product/patent coverage may be accessed at www.onsemi.com/site/pdf/Patent-Marking.pdf. **onsemi** reserves the right to make changes at any time to any products or information herein, without notice. The information herein is provided "as-is" and **onsemi** makes no warranty, representation or guarantee regarding the accuracy of the information, product features, availability, functionality, or suitability of its products for any particular purpose, nor does **onsemi** assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. Buyer is responsible for its products and applications using **onsemi** products, including compliance with all laws, regulations and safety requirements or standards, regardless of any support or applications information provided by **onsemi**. "Typical" parameters which may be provided in **onsemi** data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. **onsemi** does not convey any license under any of its intellectual property rights nor the rights of others. **onsemi** products are not designed, intended, or authorized for use as a critical component in life support systems or any FDA Class 3 medical devices or medical devices with a same or similar classification in a foreign jurisdiction or any devices intended for implantation in the human body. Should Buyer purchase or use **onsemi** products for any such unintended or unauthorized application, Buyer shall indemnify and hold **onsemi** and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that **onsemi** was negligent regarding the design or manufacture of the part. **onsemi** is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner. Other names and brands may be claimed as the property of others.



Low Power, Off-Line, CVCC Power Supply

ON Semiconductor

Device	Application	Input Voltage	Output Power	Topology	I/O Isolation
NCP1014	LED Driver, Chargers	90 – 260 Vac	Up to 10W	Off-Line Buck	Non-isolated

Other Specifications

Parameter	Output Specification
Output Voltage	5 to 28 Vdc depending on selected Z1 zener value
Ripple	Dependent on L2 inductance and C6 ESR, typically 1%
Nominal Current	50 to 350 mA typical
Max Current	350 mA, set by R3
Min Current	zero

PFC (Yes/No)	No, Pout < 25 watts
Minimum Efficiency	65% (dependent on Vout and Iout combination)
Inrush Limiting / Fuse	Inrush resistor (R1)
Operating Temp. Range	0 to +60°C (dependent on U1 heatsinking)
Cooling Method/Supply Orientation	Convection
Signal Level Control	None

Others	For applications where isolation from AC line is not required.
---------------	--


Circuit Description

This Design Note describes a simple, low power (10 W or less), constant voltage, constant current (CVCC) power supply intended for LED strings, battery chargers or similar applications where the CVCC load characteristic is necessary, and isolation from the AC mains is not required. The output voltage can be set from 5 to approximately 28 volts by using the appropriate zener diode for Z1. Output voltage sensing is accomplished by utilizing a level shifting circuit comprised of D7, C8, Z1, Q2 and the associated resistors. In applications where the output negative must be common with the input bulk capacitor negative, voltage sensing of the output directly is not possible. This is because the ground node of the controller is switched between the peak input dc voltage and the common line. In order to sense the voltage without an optocoupler in the feedback path, the level shifting “bootstrap” circuit acts as a sample and hold network which stores a sample of the output voltage on C8 (through D7) when the Mosfet in U1 is in the off state. During the on-time, U1’s ground reference is shifted up to to the input voltage level of choke L2, and sense diode D7 is back biased. When the voltage on C8 exceeds Z1’s

breakdown level and the B-E drop on Q2, then the feedback pin of U1 (pin 2) is pulled down to achieve regulation.

The output current is regulated during the constant current mode by the peak sensing circuit of D5, R3, R2, C5 and Q1. The max current is actually limited by the NCP1014 controller’s internal circuitry to about 450 mA, but is controlled externally by this circuit and the value of R3 by detecting the peak inductor current which is a good representation of the dc output current. Due to the additive magnetizing component of L2, the true load current should be limited to about 350 mA maximum for reliable constant current operation. A lower inductance than approximately 2.5 mH for L2 will probably lower the effective usable output current, so a minimum inductance value of 2.5 mH is recommended to keep the choke’s magnetizing current low. For lower currents and/or output voltages some compromises can be made on the maximum inductance value, however, lower values could also impact the output ripple if output capacitor C6 has high ESR. The schematic, V/I plot, and switching waveform are for an 18 volt, 325 mA prototype.

DN06037/D

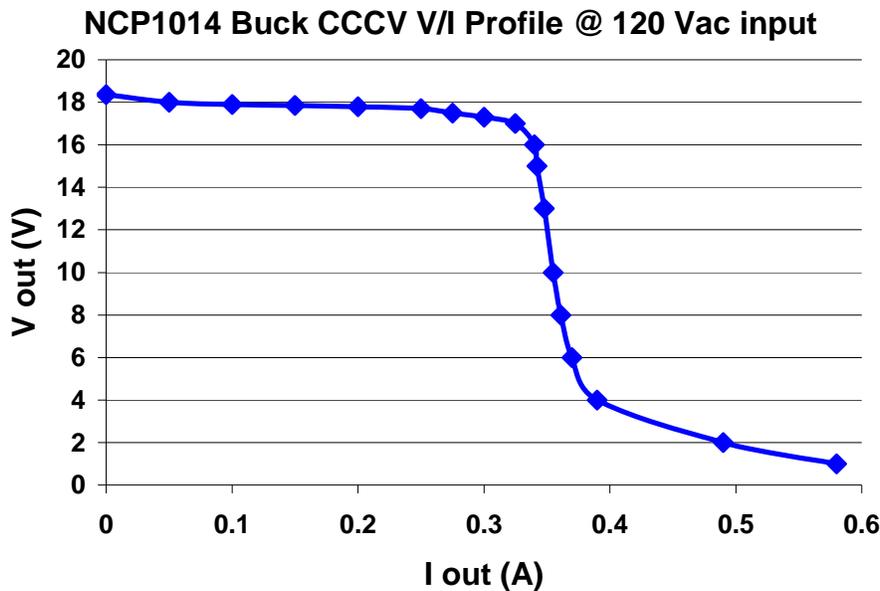


Note the “current tail” below 5 volts output due to the very short pulse width and the subsequent propagation delay effects in the controller. This sets a lower useful output level to the supply when in the CVCC mode to about 5 volts.

Efficiency:

- 18 volts, 275 mA output (CV mode): 77%
- 17 volts, 325 mA output (CVCC knee): 76%
- 14 volts 375 mA output (CC mode): 74%

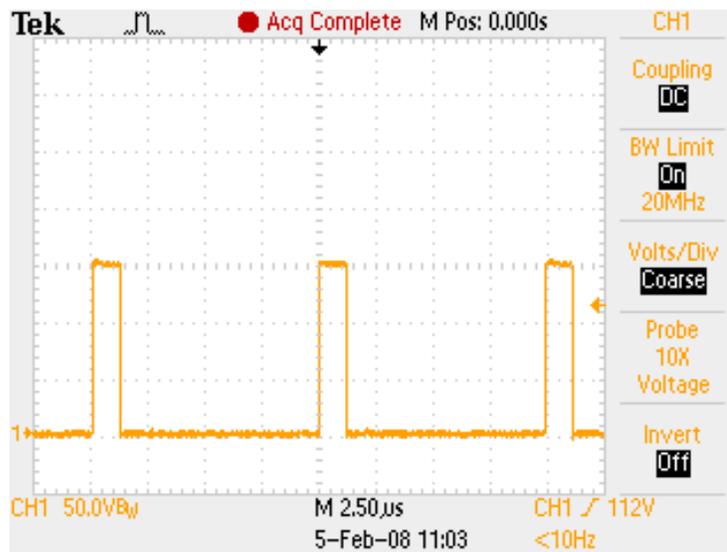Input Voltage to Choke (Cathode of D6) During Operation at CVCC Knee (120 Vac input):



© 2008 ON Semiconductor.

Disclaimer: ON Semiconductor is providing this design note “AS IS” and does not assume any liability arising from its use; nor does ON Semiconductor convey any license to its or any third party’s intellectual property rights. This document is provided only to assist customers in evaluation of the referenced circuit implementation and the recipient assumes all liability and risk associated with its use, including, but not limited to, compliance with all regulatory standards. ON Semiconductor may change any of its products at any time, without notice.

Design note created by Frank Cathell, e-mail: f.cathell@onsemi.com