

**Modeling Digitally Controlled PFCs Made Easy**

by Nikhilesh Kamath, ON Semiconductor, Phoenix, Ariz.

The emergence of server farms storing and processing vast amounts of data has spurred interest in highly efficient and compact hardware infrastructure. Naturally, these requirements extend to the server power supplies. To achieve these objectives, power supply designers need simulations to evaluate tradeoffs in selecting parameters like inductance, switching frequency, current sense gain etc. while optimizing system performance metrics like power factor (PF), total harmonic distortion (THD), control loop bandwidth and phase margin.

However, simulation of digitally controlled power supplies has its challenges. For example, it is easy to lose track of the gain at various points in the system that may occur while converting floating-point compensator coefficients to fixed-point representation. This article discusses how to address these types of challenges in a specific application of digital control—power factor correction (PFC) circuits. In particular, this article aims to serve as a guide for designing a digital average-current-mode control scheme, a popular choice for high-power PFC applications. The techniques and procedures laid out in this article can be extended to voltage-mode control or peak-current-mode architectures as well.

Running simulations typically requires making tradeoffs between run time and accuracy. A smaller simulation step size yields results that are more accurate but also requires more time for the simulation to complete. This tradeoff is particularly important in the case of power factor correction circuits that are designed with a voltage loop control bandwidth of less than 10 Hz. Since such systems may take hundreds of milliseconds to reach steady state during startup and on application of load transients, simulating all operating points may not be feasible. This article discusses the steps involved in modeling a 500-W average-current-mode-controlled PFC circuit using MATLAB, which features a SPICE-like circuit solver.

A switching model is simulated using power stage components from the Simscape Electrical toolkit. The Simscape toolkit is an extension of the capabilities of the Simulink programming environment and provides a convenient means to model a physical system (in our case an electrical system). An average model is developed in the Simulink environment to analyze the system stability. The approach presented here is a simple, quick and effective means to visualize system behavior. The data handling capabilities of MATLAB software allow for parameterizing simulation models, running from scripts and data logging; important in the data driven decision-making world we now live in.

**Example PFC Requirements For A Server Power Supply**

A typical server power supply would have voltage, PF, and efficiency specifications similar to those in Table 1.

Table 1. Example server power supply specifications.<sup>[1]</sup>

Ac input voltage range	180 to 265 Vac
Ac input frequency	60 Hz (typical)
PF, measured at 230 Vac	> 0.97, 30% to 100% of full load > 0.85, 10% to 30% of full load
THD	< 5%, 50% to 100% of full load < 10%, 20% to 100% of full load
Efficiency, measured at 230 Vac, 60 Hz with fan	Peak efficiency > 97%, 30% to 100% of full load Min. efficiency > 95%, 30% to 100% of full load Min. efficiency > 92%, 10% to 30% of full load

If we look at a typical server power supply design, we then see power supply parameters such as those shown in Table 2, which includes parameters needed for simulation.

Table 2. Simulation system parameters.

Ac input voltage	230 Vac
Ac input frequency	60 Hz
Output voltage	384 V
Output power	500 W
Boost inductor	500 $\mu$ H
PWM switching frequency	100 kHz
Output capacitance	220 $\mu$ F
Current sense ratio	0.62

Next, let's consider the basic structure and control scheme of the circuit we'll be simulating. Fig. 1 shows a high-level block diagram of a digitally controlled PFC. An outer voltage loop regulates the output voltage (bulk voltage) while an inner current loop helps shape the input current by comparing the sensed inductor current with a current reference derived by multiplying the output of the voltage loop with the rectified line voltage.

Fast analog comparators are used for cycle-by-cycle overcurrent protection (OCP). Both voltage and current loops are analyzed below for various loads because PFC is a front-end converter that can be followed by a constant power, constant current or constant resistance stage based on the application.

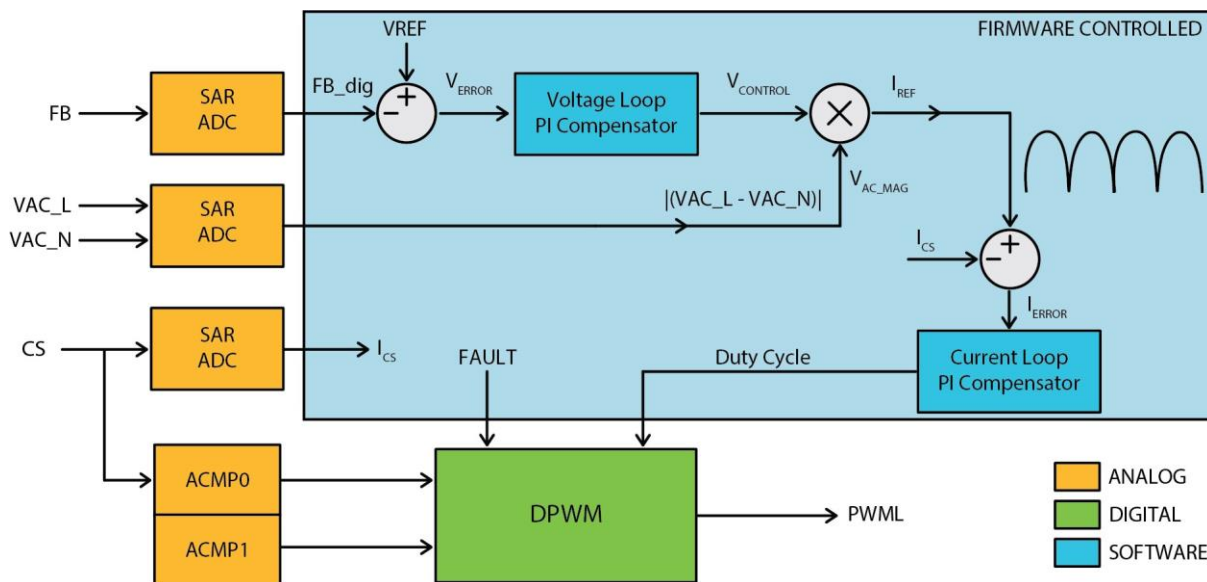


Fig. 1. A simplified overall block diagram of a digitally controlled PFC.

### Voltage-Loop Analysis

Ray Ridley developed a small-signal circuit model of the boost power factor circuit<sup>[2]</sup> in 1987. The current reference that the inductor current tracks is derived from the line voltage. Ignoring disturbances due to input voltage, the circuit reduces to the network shown in Fig. 2 and the control-to-output transfer function is given by:

$$\frac{\tilde{V}_o}{\tilde{V}_c} = g_c * \frac{(r_o // Z_L)}{(1 + s * C * (r_o // Z_L))} \quad (1)$$

where  $\tilde{V}_o$  is the average output voltage,  $\tilde{V}_c$  is the average control voltage,  $Z_L$  is the load impedance,  $r_o$  is the small-signal output resistor given by  $V_o/I_o$ ,  $C$  is the output capacitance, and  $g_c$  is a constant given by  $(V_{IN})^2/(k * V_o)$ , where  $1/(k)$  is the line voltage scaling factor.<sup>[2]</sup>

 


Fig. 2. A reduced small-signal circuit model of the boost power factor correction circuit.

For a constant-resistance load,  $Z_L = R_L$ ,  $(r_o // Z_L) = R_L/2$ , the transfer function becomes:

$$\frac{\tilde{V}_o}{\tilde{V}_c} = g_c * \frac{(R_L)}{(2 + s * C * R_L)} \quad (2)$$

For a constant-current load,  $Z_L = \infty$ ,  $(r_o // Z_L) = r_o$ :

$$\frac{\tilde{V}_o}{\tilde{V}_c} = g_c * \frac{(r_o)}{(1 + s * C * r_o)} \quad (3)$$

And finally for a constant-power load,  $Z_L = -V_o/I_o = -r_o$ ,  $(r_o // Z_L) = \infty$ :

$$\frac{\tilde{V}_o}{\tilde{V}_c} = g_c * \frac{1}{(s * C)} \quad (4)$$

The expressions for  $I_L$  and  $g_c$ <sup>[2]</sup> are given by:

$$I_{IN} = \frac{(V_{IN} * V_c)}{(k)} = I_L$$

$$g_c = \frac{V_{IN}}{(k * M)} = \frac{(V_{IN})^2}{(k * V_o)}, \text{ where } M \text{ is the conversion ratio given by } \frac{V_o}{V_{IN}}.$$

This result can be substituted into equations 2, 3 and 4 to obtain the transfer function from  $I_L$  to  $\tilde{V}_o$ :

$$\frac{\tilde{V}_o}{I_L} = \frac{V_{IN}}{V_o} * \frac{(R_L)}{(2 + s * C * R_L)} \quad \text{for constant resistance load}$$

$$\frac{\tilde{V}_o}{I_L} = \frac{V_{IN}}{V_o} * \frac{(r_o)}{(1 + s * C * r_o)} \quad \text{for constant current load}$$

$$\frac{\tilde{V}_o}{I_L} = \frac{V_{IN}}{V_o} * \frac{1}{(s*C)} \quad \text{for constant power load}$$

We can then use these expressions to plot the response of our design example. Table 3 shows the plant transfer function for our system parameters:  $C = 220 \mu\text{F}$ ,  $V_{IN} = 230 \text{ Vac}$ ,  $V_o = 384 \text{ V}$ ,  $R_L = 295 \Omega$  and  $I_o = 1.3 \text{ A}$ .

Table 3. Plant transfer functions for different load models.

Load model	Pole location	Bode plot
<p>Constant resistance</p> $\frac{\tilde{V}_o}{I_L} = \frac{176}{(2 + 0.0649s)}$	$\frac{2}{C*R_L} = 4.9 \text{ Hz}$	
<p>Constant current</p> $\frac{\tilde{V}_o}{I_L} = \frac{176}{(1 + 0.0649s)}$	$\frac{2}{C*r_o} = 2.45 \text{ Hz}$	
<p>Constant power</p> $\frac{\tilde{V}_o}{I_L} = \frac{0.5989}{(0.00022s)}$	<p>Origin pole intersects 0 dB at 434 Hz.</p>	

With expressions for the plant transfer function in hand, we can begin the process of compensating the voltage loop. Fig. 3 represents the voltage-loop block diagram of the simplified boost converter shown earlier in Fig. 1.

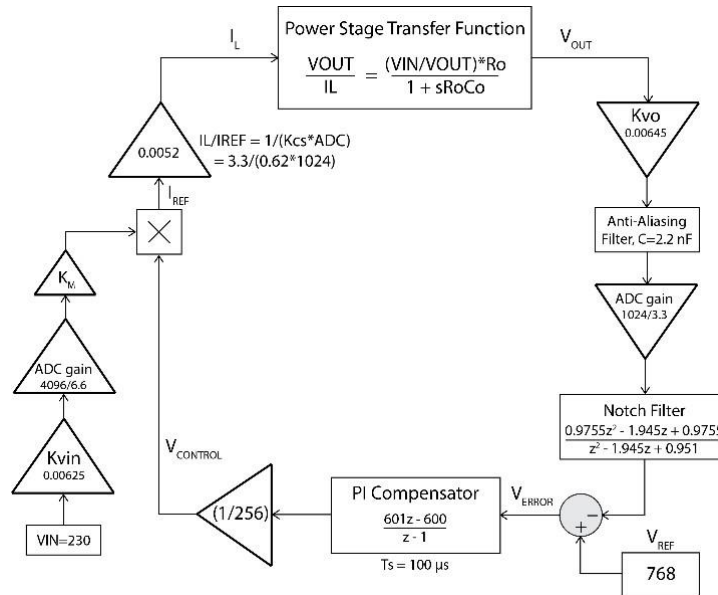


Fig. 3. Voltage-loop block diagram with constant-current plant model.

$K_{VIN}$  represents the external resistor divider gain (160:1 ratio) similar to that of the output voltage  $K_{VO}$  (155:1). (The voltage divider ratio (155 to 160) is commonly used for interfacing a 400-V output to a microcontroller on a 3.3-V rail.)

A 12-bit SAR ADC senses the line voltage differentially. The analog signal over a range of -3.3 V to 3.3 V is converted to an integer in the range of 0 to 4096. The effective ADC gain is (4096/6.6).

The gain factor  $K_M$  is shown to represent any feedforward function or normalization. In this simulation, line feedforward is not used.

For current sensing, a 10-bit SAR ADC is used and external current-sense gain is 0.62. This gives us the relationship between the digital current reference ( $I_{REF}$ ) and inductor current ( $I_L$ ):

$$\frac{I_L}{I_{REF}} = \frac{1}{(K_{CS} * ADC)} = 0.0052$$

For output voltage sensing, a 10-bit SAR ADC is used.

A 2.2-nF capacitor placed on the feedback resistor divider provides a low-pass RC filter for anti-aliasing. This upper resistor in the divider = 4160 kΩ. The lower resistor in the divider = 27 kΩ.

The cut-off frequency is:

$$\frac{1}{(2 * \pi * R_{EQ} * C)} = \frac{1}{(6.28 * 26.826 \text{ k}\Omega * 2.2 \text{ nF})} = \sim 2.7 \text{ kHz}$$

The feedback voltage is sampled at 10 kHz. This sample rate is sufficient since the target voltage control loop bandwidth is very low (less than 10 Hz).

A notch filter can be used to attenuate the 2x line frequency ripple present on the control voltage (output of voltage compensator) or feedback voltage signal. Since the control voltage is used to generate the current reference for the inner current-loop control, the reference is more accurate, leading to better system performance (PF, THD).

Reference 6 was consulted to ensure that all components in Fig. 3 were accounted for and that the sample rate selections for the sense signals were reasonable. Final values (for example, the current-sense gain) were adjusted based on emulation results.

Fig. 4 shown below is a Simulink model of the voltage-loop block diagram presented in Fig. 3.

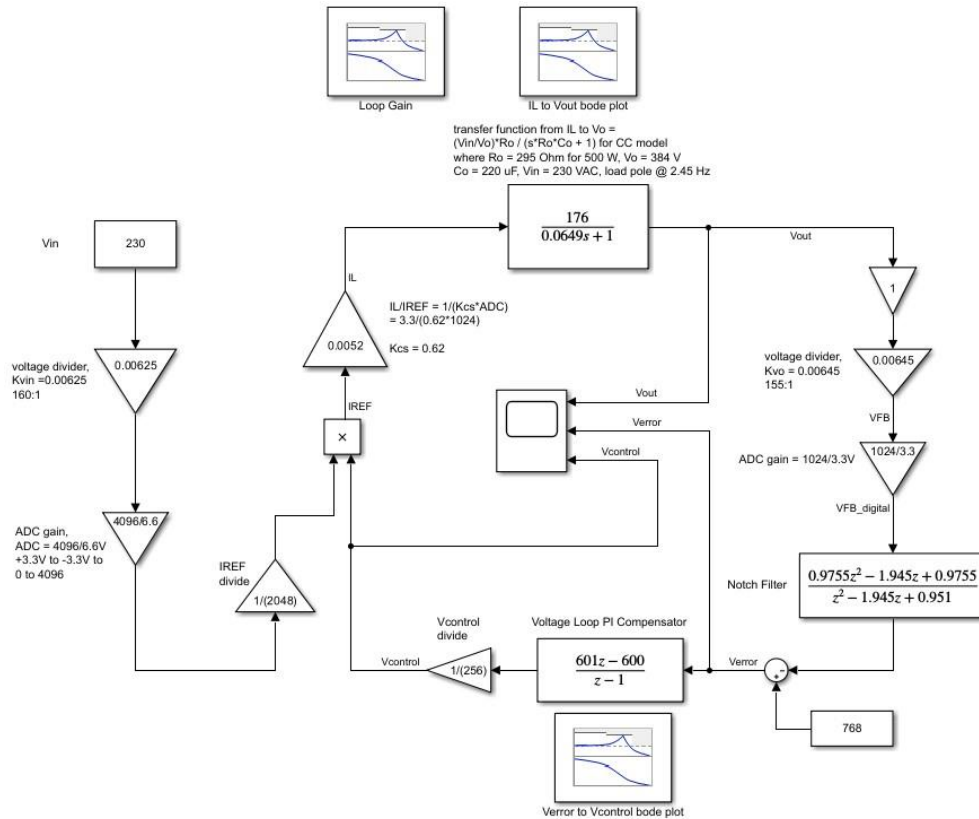


Fig. 4. A Simulink model for the voltage loop with a constant-current plant model.

For the constant-resistance model, optimal placement of the compensation zero is at the location of the plant pole.<sup>[2]</sup> The amount of output capacitance is typically based on the hold-up time requirement. A common rule of thumb is 0.5 to 1  $\mu\text{F}$  per W.

For a 500-W design, an output capacitance of 440  $\mu\text{F}$  is reasonable. This leads to a compensation zero at 2.5 Hz in order to cancel the load pole. For this simulation, the selected output capacitance is 220  $\mu\text{F}$ , which corresponds to a load pole at 4.9 Hz for the constant-resistance model and a load pole at 2.45 Hz for the constant-current load.

The procedure is to plot the plant transfer function, place the compensation zero and adjust the compensator gain to achieve the target crossover frequency.

An S-domain PI compensator with a compensation zero placed at 2.5 Hz and 40 dB gain at 0.1 Hz is described by the following expression:

$$Comp(s) = \frac{\left(1 + \frac{s}{wz}\right)}{\left(\frac{s}{wp}\right)} = Kp + \frac{Ki}{s} = \frac{\left(1 + \frac{s \cdot Kp}{Ki}\right)}{\left(\frac{s}{Ki}\right)}$$

where the origin pole is given by  $w_p = Ki$  and  $w_z = Ki/Kp$  with the following values:

$$w_z = 2 \cdot \pi \cdot 2.5 = 15.7 \text{ rad/s}$$

$$w_p = 2 \cdot \pi \cdot 10 = 62.8 \text{ rad/s}$$

In our example, this leads to the following expression for the compensator:

$$Comp(s) = \frac{\left(1 + \frac{s}{15.7}\right)}{\left(\frac{s}{62.8}\right)} = \frac{(62.8 + 4s)}{s}$$

Now, converting to the z-domain using the backward Euler method and a sample rate of 100  $\mu$ s yields

$$\begin{aligned} Comp(z) &= Kpz + Kiz * \frac{(z)}{(z-1)} = 4 + 0.00628 * \frac{(z)}{(z-1)} = \frac{(4.00628z-4)}{(z-1)} \\ &= \frac{(4.00628-4z^{-1})}{(1-z^{-1})} \end{aligned}$$

Comparing to a generic z-domain digital filter with format  $\frac{(B0+B1z^{-1})}{(1+A1z^{-1})}$ , the coefficients are:

$$B0 = 4.00628, B1 = -4, A1 = -1$$

Divide by  $2^3$  to bring the coefficients into the range -1 to +1. Then multiply by  $2^{15}$ :

$$B0 = 4.00628 * 4096 = 16,409.723 = 16410$$

$$B1 = -4 * 4096 = -16384$$

$$A1 = -1 * 4096 = -4096$$

The implemented difference equation becomes:

$$U(n) = U(n-1) + 16410 * E(n) - 16384 * E(n-1)$$

and remember to divide by  $2^{12}$ .

$$Comp(z) = \frac{1}{4096} * \frac{(16410z-16384)}{(z-1)}$$

Alternately,

$$Comp(z) = 4 + 0.00628 * \frac{(z)}{(z-1)} = \frac{1}{4096} * [16384 + 26 * \frac{(z)}{(z-1)}]$$

where  $Kpz = 16384$ ,  $Kiz = 26$  and  $div. = 4096$ .

Table 4 shows the PI compensator coefficients for the compensator example given above along with the coefficients obtained for other compensator values. The response obtained for case (b) is plotted in Fig. 5, while Fig 6 shows the PI coefficients plugged into a block diagram for the compensator.

Table 5 depicts what the compensation coefficients in cases (b) and (c) (and a variation on case (c)) mean in terms of loop bandwidth and stability under the different load models. These illustrate tradeoffs in loop response and stability.

Table 4. A few different voltage compensators with different zero locations and dc gain.

	Backward Euler transformation, $T_s = 100 \mu s$	Zero location (Hz)	Gain at 0.1 Hz (dB)	Gain at 100 Hz (dB)
(a)	$K_{pz} = 16384, K_{iz} = 26, \text{divide} = 4096$	2.52	40	12.1
(b)	$K_{pz} = 600, K_{iz} = 1, \text{divide} = 256$	2.65	35.8	7.41
(c)	$K_{pz} = 800, K_{iz} = 1, \text{divide} = 128$	1.99	41.9	15.9

 


Fig. 5. Voltage-loop PI compensator Bode plot for case (b), overall Bode (with 180-Vac input and the constant-current load model).

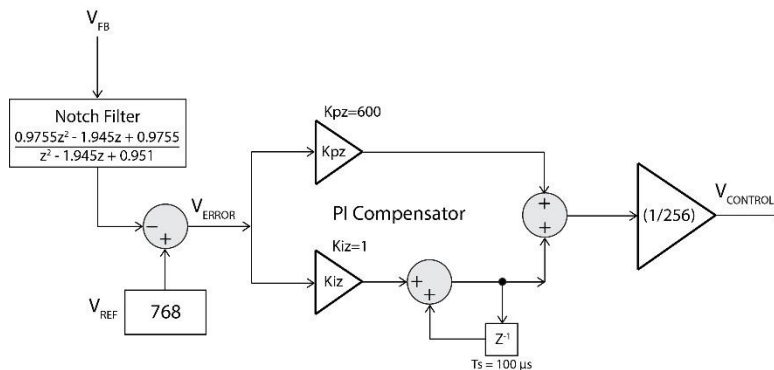


Fig. 6. Voltage-loop compensator for case (b).



Table 5. Voltage-loop bandwidth and phase margin for different load models and compensators.

Voltage compensator	Crossover frequency and phase margin (PM)					
	Constant-resistance model		Constant-current model		Constant-power model	
	180 Vac	230 Vac	180 Vac	230 Vac	180 Vac	230 Vac
Kpz = 600, Kiz = 1, divide = 256, IREF div. = 2048	1.7 Hz (103° PM)	3.25 Hz (106° PM)	2.9 Hz (87° PM)	4.65 Hz (86.7° PM)	3.52 Hz (52° PM)	5.16 Hz (61° PM)
Kpz = 800, Kiz = 1, divide = 128, IREF div. = 4096	1.98 Hz (112° PM)	4.49 Hz (112° PM)	3.51 Hz (94° PM)	5.92 Hz (92° PM)	4.15 Hz (63° PM)	6.4 Hz (70.7° PM)
Kpz = 800, Kiz = 1, divide = 128, IREF div. = 2048	6.12 Hz (109° PM)	11.3 Hz (100° PM)	7.34 Hz (91° PM)	12.1 Hz (88° PM)	7.73 Hz (73° PM)	12.3 Hz (77° PM)

**Current-Loop Analysis**

A similar approach to that described above can be applied to compensating the current loop. In place of the voltage-loop diagram from Fig. 3, we have the current-loop diagram shown in Fig. 7.

In this case, the plant transfer function is the load current as a function of duty cycle. From reference 7, we have the following expression for the small-signal duty to inductor current transfer function:

$$\frac{I_L}{\text{duty}} = \frac{2 * V_{OUT} * (1 + s * R_L * \frac{C}{2})}{R_L * (1 - D)^2 * [1 + \frac{sL}{R_L * (1 - D)^2} + \frac{s^2 LC}{(1 - D)^2}]}$$

Applying the high-frequency approximation:[7]

$$\frac{I_L}{\text{duty}} = \frac{V_{OUT}}{sL}, \text{ which is also shown in Fig. 7.}$$

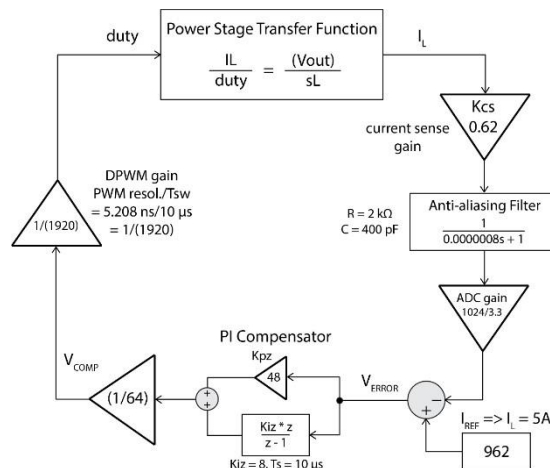


Fig. 7. Current-loop block diagram.  
© 2020 How2Power. All rights reserved.

For our system parameters,  $L = 500 \mu\text{H}$  and  $V_o = 384 \text{ V}$ , we have:

$$\frac{I_L}{\text{duty}} = \frac{384}{0.0005s}$$

When a Bode plot of this transfer function is plotted, the magnitude plot intersects 0 dB at  $\sim 122 \text{ kHz}$ .

As given previously, the current sense gain is 0.62.

A low-pass RC filter is used as an anti-aliasing filter.  $R = 2 \text{ k}\Omega$  and  $C = 400 \text{ pF}$ .

The cut-off frequency is:  $\frac{1}{(2 \cdot \pi \cdot R \cdot C)} = \sim 200 \text{ kHz}$

**Current Reference Generation,  $I_{REF}$**

The current reference is the product of the output of the voltage control loop ( $V_{CONTROL}$ ) and instantaneous line voltage sense ( $V_{LINE}$ ). The reference current level rises in response to an increased load demand.

For analyzing the dynamics of the current loop,  $I_{REF}$  is held constant. It is external to the loop of interest and its magnitude plays no role.

**Digital PWM Gain**

The output of the current-loop compensator is stored in a 16-bit compare register. The digital PWM output toggles once the module’s base timer/counter crosses the compare value. The base timer resolution is determined by the peripheral clock configuration. The PWM clock is set to 192 MHz corresponding to a 5.208-ns duty cycle resolution. The desired PWM switching frequency is 100 kHz. Hence, a compare register value of 1920 corresponds to 100% duty cycle. In reality, a maximum duty cycle exists, set at  $\sim 97\%$ .

$$DPWM \text{ gain} = \frac{PWM \text{ resolution}}{PWM \text{ switching period}} = \frac{\frac{1}{192} MHz}{\frac{1}{100} kHz} = \frac{1}{1920}$$

The target bandwidth of the current loop is typically around 6 to 10 kHz. The uncompensated Bode plot from  $I_{comp}$  to  $I_{cs}$  digital, pictured in Fig. 8, shows that the loop gain is already close to 0 dB at the target crossover frequency of 10 kHz. So the current compensator need not provide any gain in this region. The compensation zero can be placed sufficiently low to provide the necessary phase boost at 10 kHz as shown in the Bode plots on the right in Fig. 8.

 


Fig. 8. Bode plots of the uncompensated (left) and compensated (right) current loop.

Since the system is first order, a simple PI compensator comprised of a pole at the origin and a zero at a desired location is suitable. A block diagram of the current-loop compensator is presented in Fig. 9 with coefficients shown for case (c) in Table 6 and the corresponding Bode plots for this compensator design.

The current-loop compensator values were derived in a similar manner to that described for the voltage-loop compensator. Table 6 shows the compensator coefficients along with the resulting bandwidth and stability results obtained for different zero placements. A Simulink model of the current loop is pictured in Fig. 10.

 


Fig. 9. Current-loop PI compensator and Bode plot.

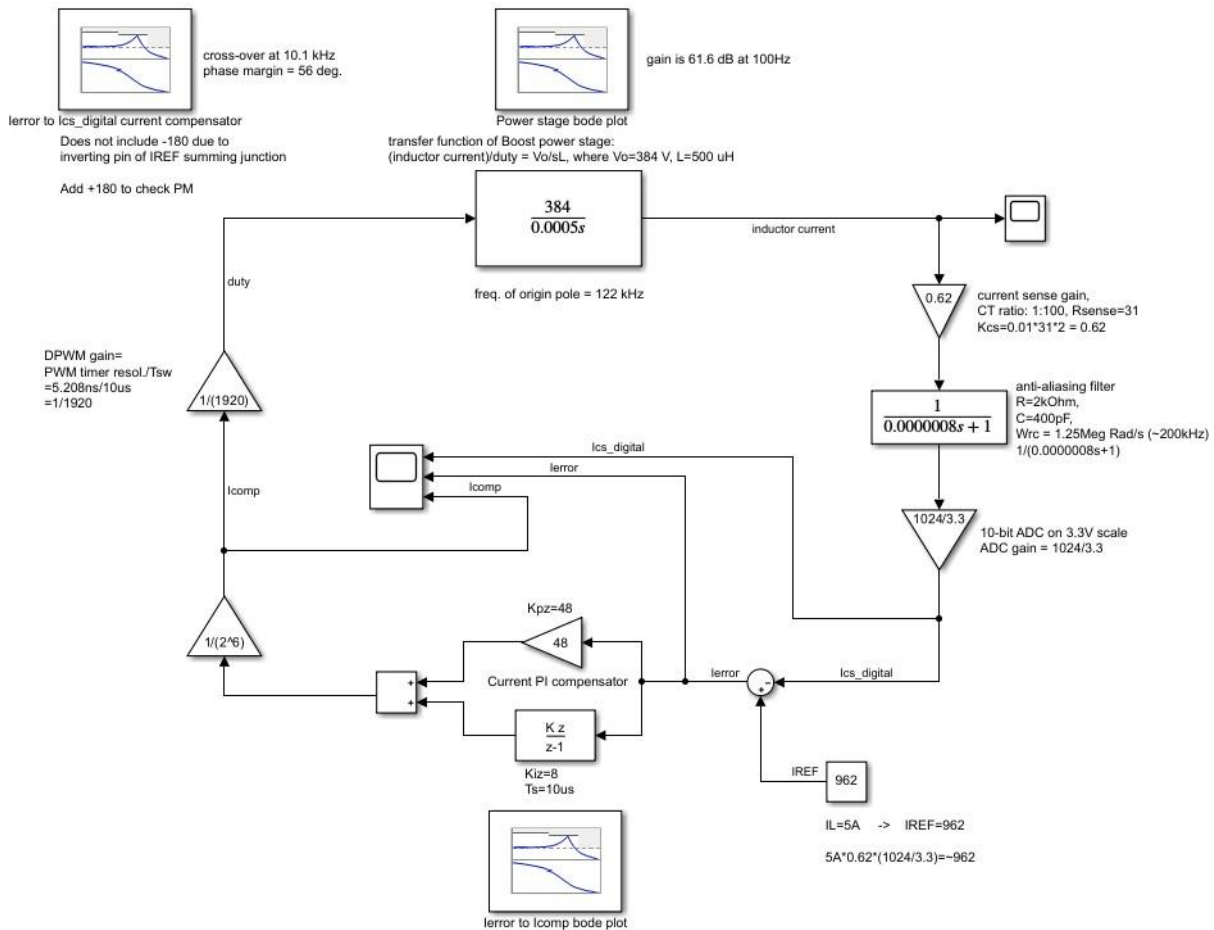


Fig. 10. Simulink model for the current loop.

Table 6. A few current-loop compensators with different zero locations and the resultant bandwidths and phase margins.

	Current compensator values with 1/64 post-scale Backward Euler transformation, $T_s = 10 \mu s$	Zero location (Hz)	Crossover frequency & phase margin
Case (a)	$K_{pz} = 48, K_{iz} = 1$	328	9.24 kHz, 69°
Case (b)	$K_{pz} = 48, K_{iz} = 4$	1270	9.56 kHz, 63°
Case (c)	$K_{pz} = 48, K_{iz} = 8$	2440	10.1 kHz, 56°
Case (d)	$K_{pz} = 48, K_{iz} = 12$	3500	10.7 kHz, 50°

The final current-loop PI compensator selected is case (c):  $K_{pz} = 48$  and  $K_{iz} = 8$  with 1/64 post-scale since it provides sufficient phase margin while achieving high bandwidth.

**Simscape Model**

Once the compensators are designed, they are used in the Simscape model shown in Fig. 11 to observe steady-state waveforms, inductor current ripple, output voltage ripple, transient performance, etc. The filtered line current is passed to the THD block to get a rough measurement of distortion. Fig. 12 shows the simulation waveforms at steady state: inductor current, output voltage, output of the current loop compensator and THD.

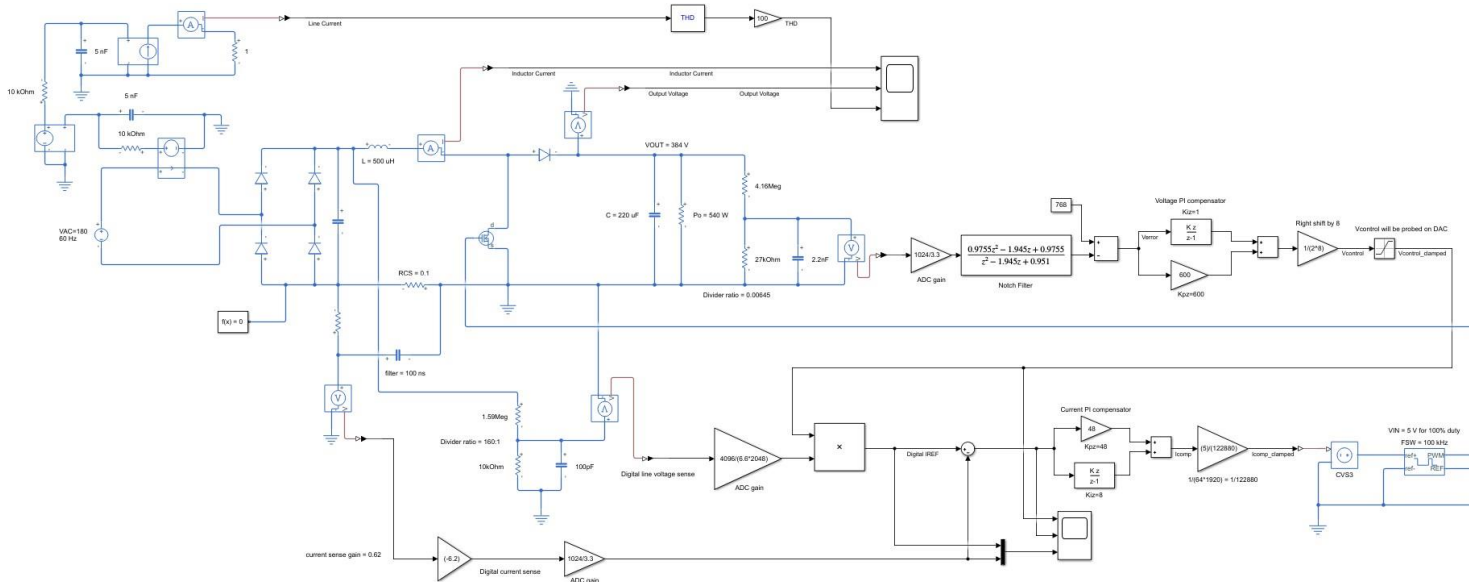


Fig. 11. The Simscape model.

 


Fig. 12. Simscape waveforms.

### Experimental Validation

The performance of the PFC design developed above was evaluated on a 500-W totem-pole bridgeless PFC board shown in Fig. 13. The above stability analysis and compensator design for a single-channel CCM boost PFC is no different for the totem-pole PFC.

 


Fig. 13. 500-W totem-pole PFC evaluation board.

Fig. 14 shows a scope capture with current-sense signal (blue), switch-node waveform (green), and fast-leg PWM drive outputs (yellow and purple).

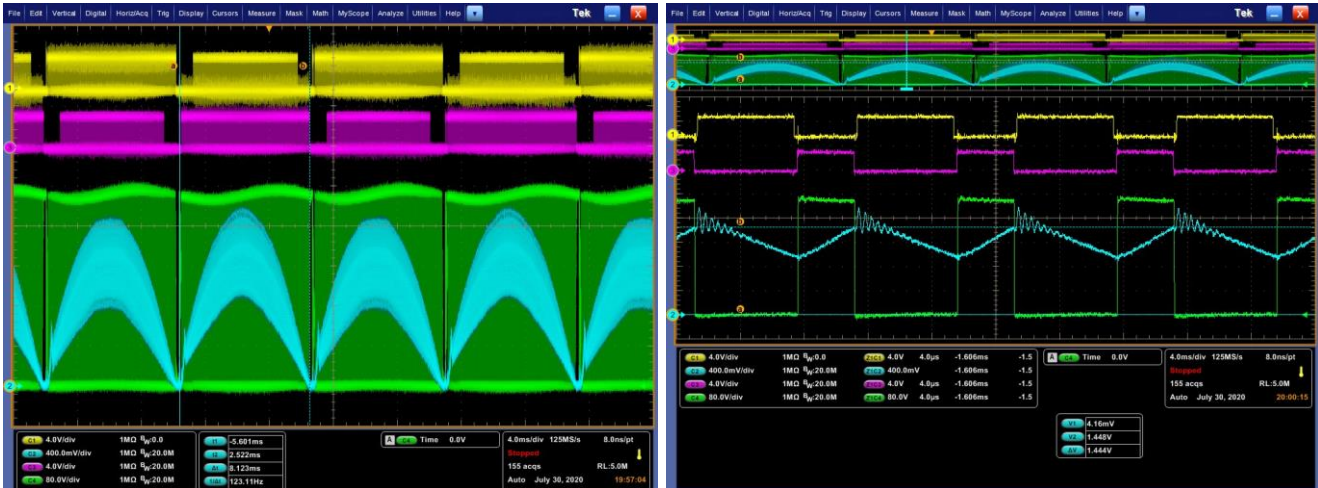


Fig. 14. Waveforms obtained from the 500-W totem-pole PFC evaluation board with 180-Vac, 540-W, 60-Hz ac input with PF = 0.995 and THD <3%.

Fig. 15 shows a scope capture with current-sense signal (blue), output voltage (green), slow-leg low-side drive SRLO (yellow) and the output of the voltage-loop compensator (Vcontrol DAC, purple).



Fig. 15. Additional waveforms obtained from the totem-pole PFC evaluation board with  $V_{in} = 180$  Vac and output power = 500 W.

Fig. 16 compares the expected bandwidth and phase margin from Simulink to actual measurements using a network analyzer. The plots match quite well.

 


Fig. 16. Bode plot: simulation versus measured results at 180-Vac input and 500-W output using the constant-current model.

Fig. 17 shows the power factor across load for two different line-voltage levels, 180 Vac and 230 Vac.

 


Fig. 17. Power factor vs output power.

**Conclusion**


Simulink and Simscape have been used to analyze an average-current-mode-controlled power factor correction circuit for a 500-W server power supply application. The selected simulation parameters are validated on a prototype board.

**References**

1. [Open Rack Specification V2.2](#)
2. "Average small-signal analysis of the boost power factor correction circuit" by R.B. Ridley, 1987. (This source provides a PDF preview of the paper when viewed in Internet Explorer.)
3. "Compensating a PFC Stage, TND382-D," ON Semiconductor presentation.
4. [Second-order IIR notch filter](#), filter model described in MathWorks Help Center.

5. "[Applying Digital Technology to PWM Control-Loop Designs](#)" by Mark Hagen and Vahid Yousefzadeh, Texas Instruments seminar paper.
6. "Introduction to Digital Control of Switched Mode Power Converters," seminar delivered by Delta Electronics to ON Semiconductor, Nov. 2014.
7. "[Digital control for power factor correction](#)" by Manjing Xie, Master Thesis, Virginia Tech, 2003

### About The Author

 

*Nikhilesh Kamath currently works as a staff applications engineer for the Power Conversion Solutions business unit under the Advanced Solutions Group (ASG) at ON Semiconductor. He works on product definition, emulation, silicon evaluation and reference design development. Nikhilesh joined ON Semiconductor in February 2015. Nikhilesh holds a master of science in electrical engineering from North Carolina State University and a bachelor of technology in electrical and electronics engineering from National Institute of Technology Karnataka, India*

*For more information on designing power factor correction circuits, see the How2Power's [Design Guide](#), locate the Popular Topics category and select "Power Factor Correction".*